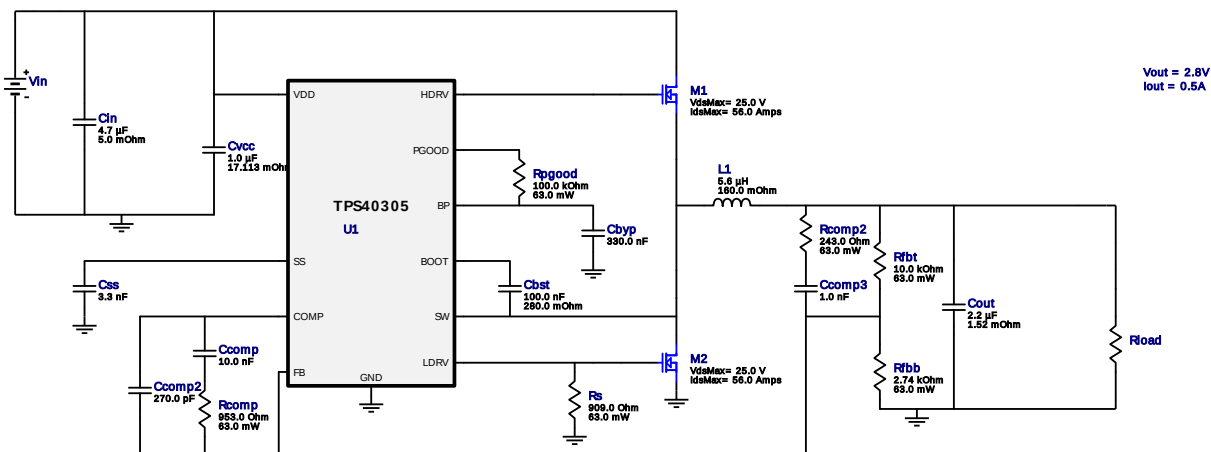


WEBENCH® Design Report



Design : 4406513/25 TPS40305DRCR
TPS40305DRCR 3.7V-4.2V to 2.80V @ 0.5A















Electrical BOM







#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	Cbst	AVX	08053C104KAT2A Series= X7R	Cap= 100.0 nF ESR= 280.0 mOhm VDC= 25.0 V IRMS= 0.0 A	1	\$0.01	0805 7 mm ²
2.	Cbyp	Kemet	C0603C334K8RACTU Series= X7R	Cap= 330.0 nF VDC= 10.0 V IRMS= 0.0 A	1	\$0.02	0603 5 mm ²
3.	Ccomp	MuRata	GRM216R71H103KA01D Series= X7R	Cap= 10.0 nF VDC= 50.0 V IRMS= 0.0 A	1	\$0.01	0805 7 mm ²
4.	Ccomp2	MuRata	GRM033R71C271KA01D Series= X7R	Cap= 270.0 pF VDC= 16.0 V IRMS= 0.0 A	1	\$0.01	0201 2 mm ²
5.	Ccomp3	Samsung Electro-Mechanics	CL21C102JBCNFNC Series= C0G/NP0	Cap= 1.0 nF VDC= 50.0 V IRMS= 0.0 A	1	\$0.01	0805 7 mm ²
6.	Cin	MuRata	GRM188R60J475KE19D Series= X5R	Cap= 4.7 uF ESR= 5.0 mOhm VDC= 6.3 V IRMS= 2.0 A	1	\$0.01	0603 5 mm ²
7.	Cout	Taiyo Yuden	JMK105BJ225MV-F Series= X5R	Cap= 2.2 uF ESR= 1.52 mOhm VDC= 6.3 V IRMS= 0.0 A	1	\$0.03	0402 3 mm ²
8.	Css	MuRata	GRM216R71E332KA01D Series= X7R	Cap= 3.3 nF VDC= 25.0 V IRMS= 0.0 A	1	\$0.01	0805 7 mm ²
9.	Cvcc	MuRata	GRM188R61E105KA12D Series= X5R	Cap= 1.0 uF ESR= 17.113 mOhm VDC= 25.0 V IRMS= 979.39 mA	1	\$0.01	0603 5 mm ²
10.	L1	Bourns	SDR0302-5R6ML	L= 5.6 uH DCR= 160.0 mOhm	1	\$0.18	SDR0302 15 mm ²






#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
11. M1		Texas Instruments	CSD16411Q3	VdsMax= 25.0 V IdsMax= 56.0 Amps	1	\$0.34	 TRANS_NexFET_Q3 18 mm²
12. M2		Texas Instruments	CSD16411Q3	VdsMax= 25.0 V IdsMax= 56.0 Amps	1	\$0.34	 TRANS_NexFET_Q3 18 mm²
13. Rcomp		Vishay-Dale	CRCW0402953RFKED Series= CRCW..e3	Res= 953.0 Ohm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm²
14. Rcomp2		Vishay-Dale	CRCW0402243RFKED Series= CRCW..e3	Res= 243.0 Ohm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm²
15. Rfbb		Vishay-Dale	CRCW04022K74FKED Series= CRCW..e3	Res= 2.74 kOhm Power= 63.0 mW Tolerance= 1.0%	1	NA	 0402 3 mm²
16. Rfbt		Vishay-Dale	CRCW040210K0FKED Series= CRCW..e3	Res= 10.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm²
17. Rpgood		Vishay-Dale	CRCW0402100KFED Series= CRCW..e3	Res= 100.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm²
18. Rs		Vishay-Dale	CRCW0402909RFKED Series= CRCW..e3	Res= 909.0 Ohm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm²
19. U1		Texas Instruments	TPS40305DRCR	Switcher	1	\$0.95	 S-PVSON-N10 17 mm²

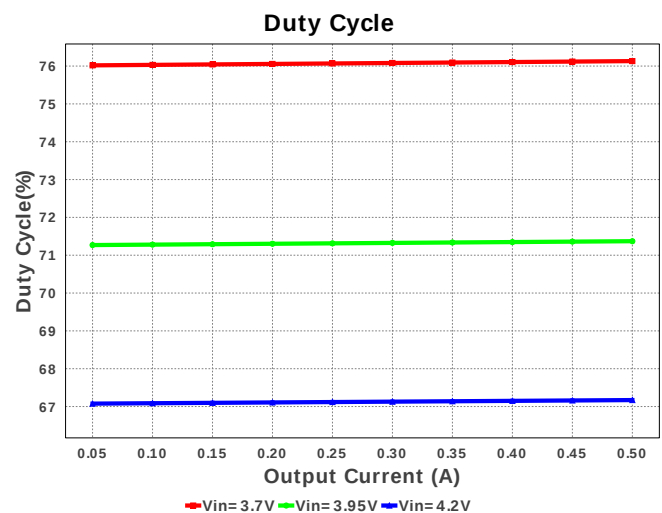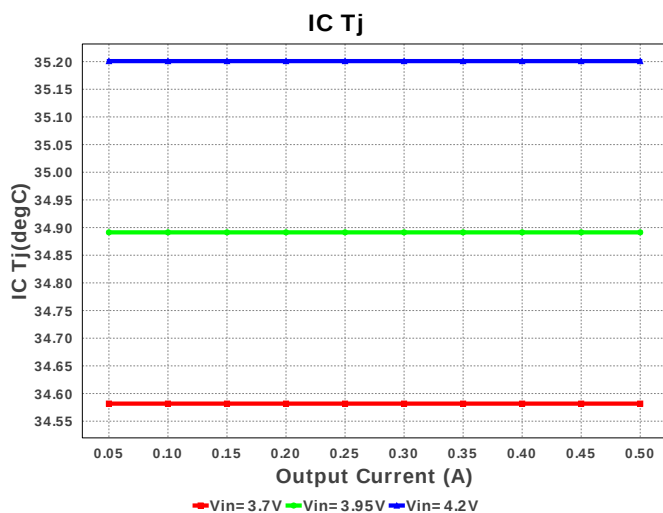

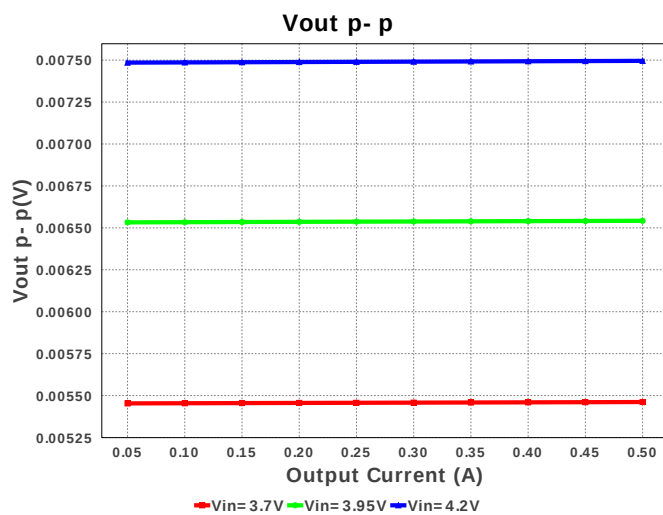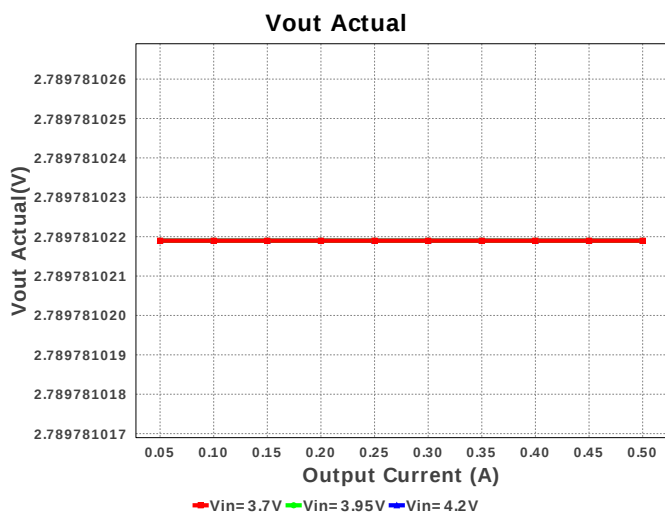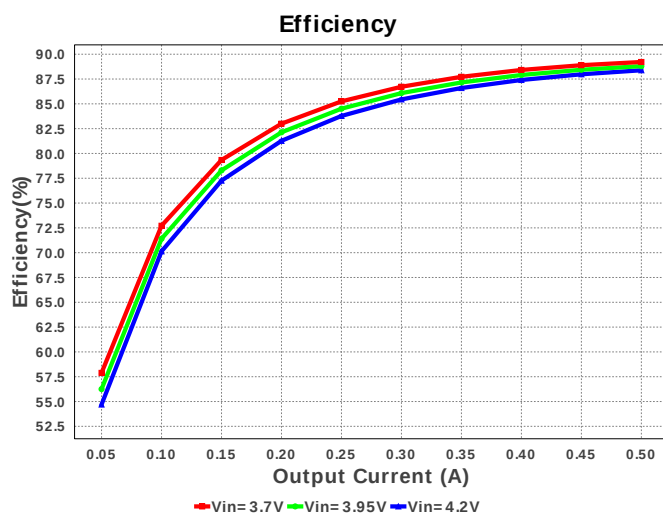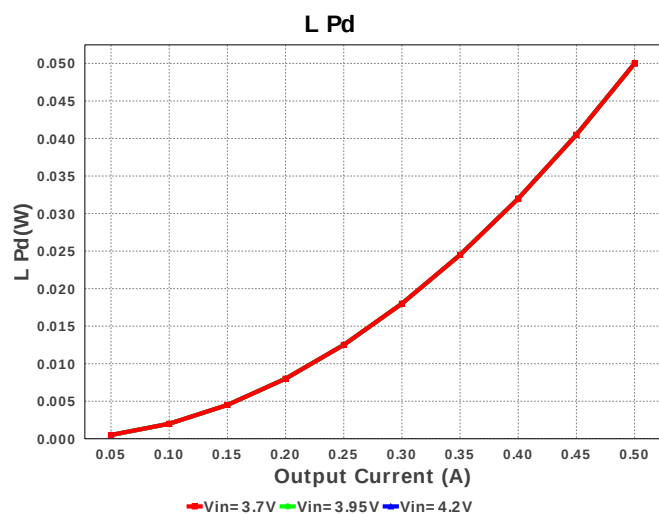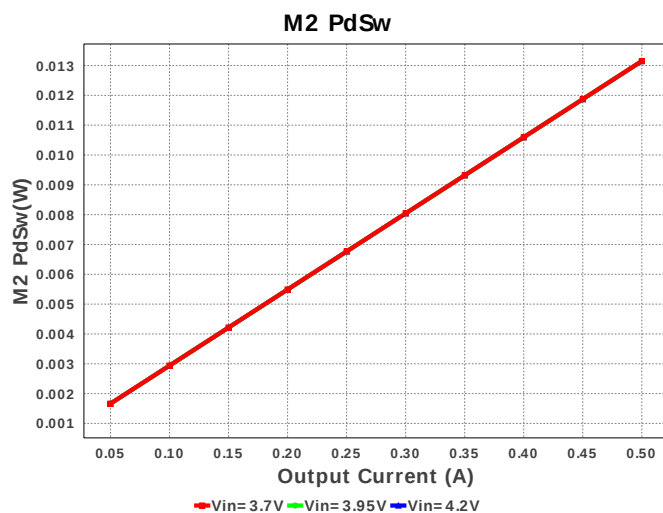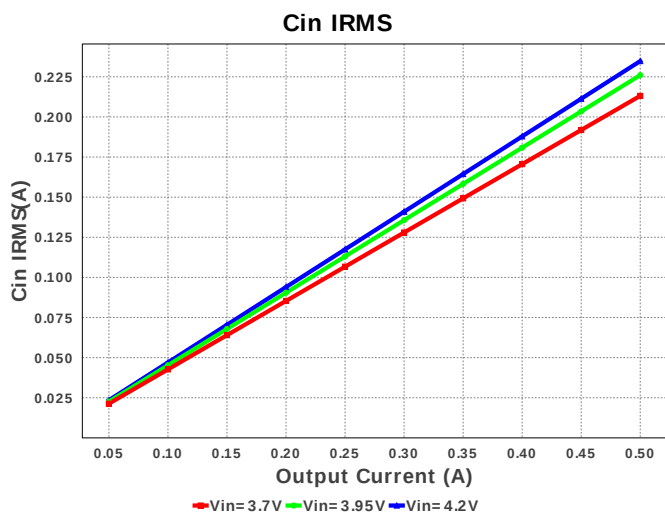

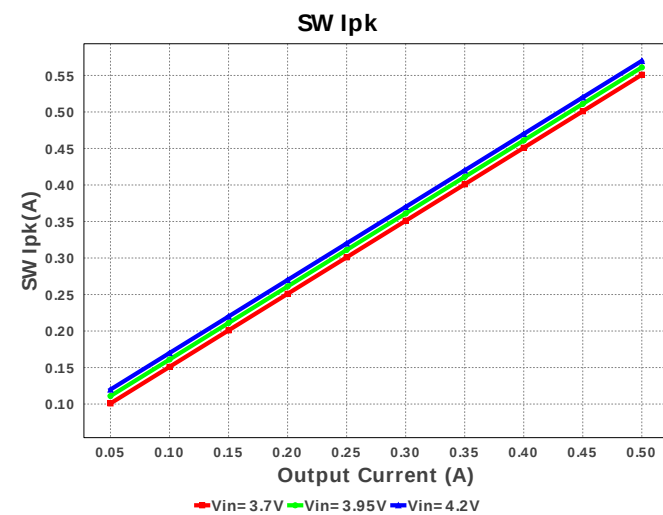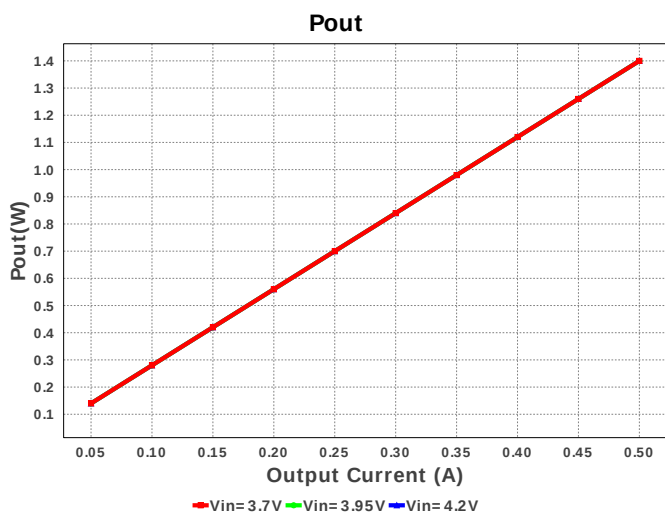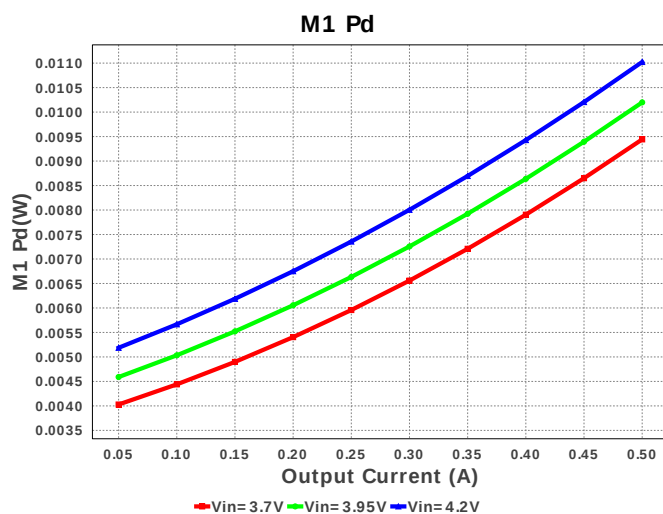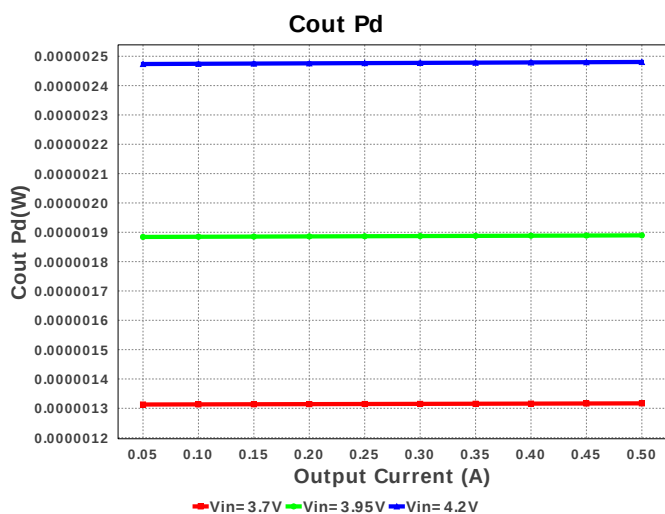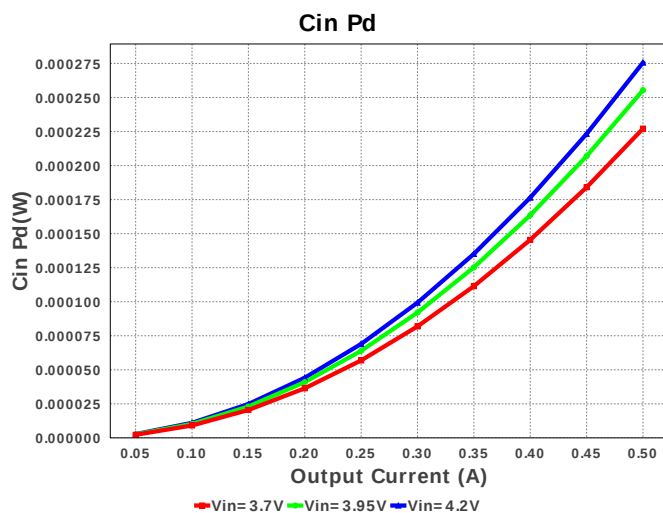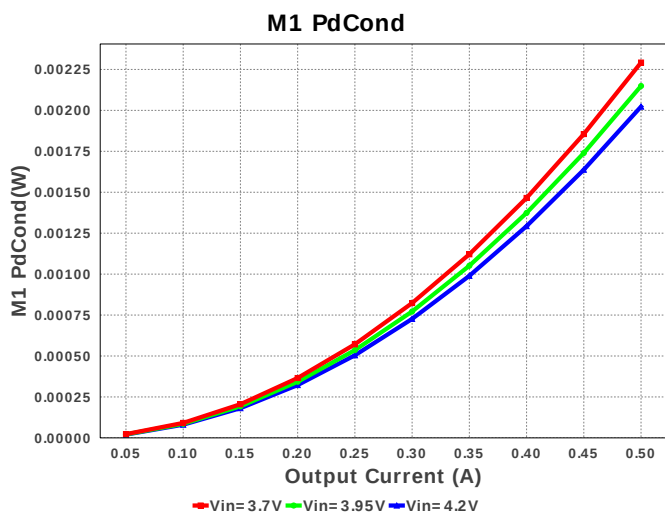

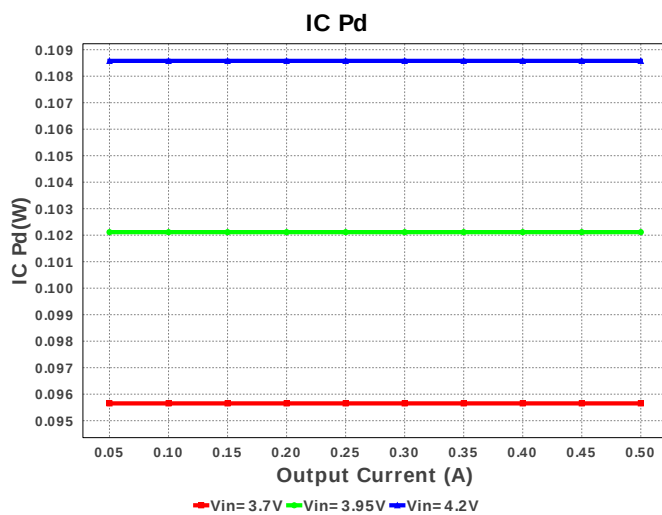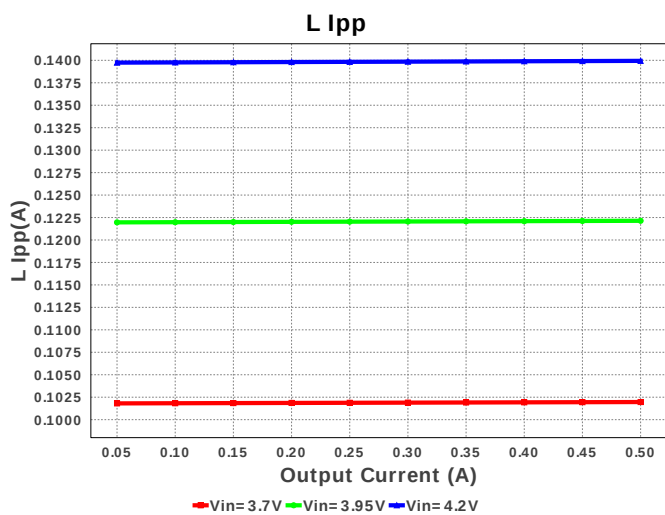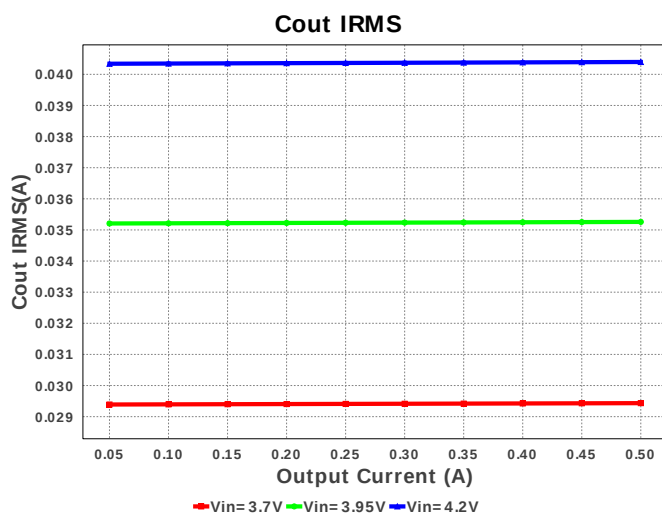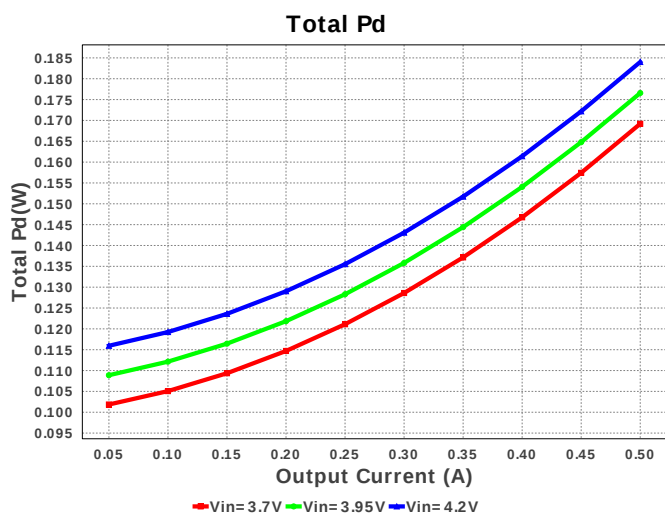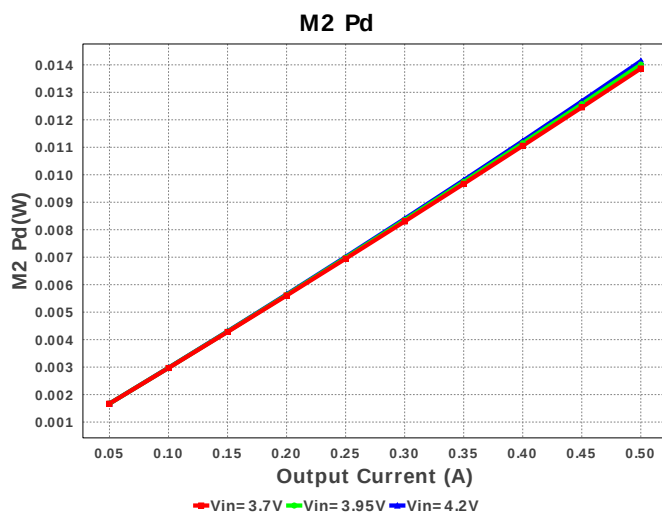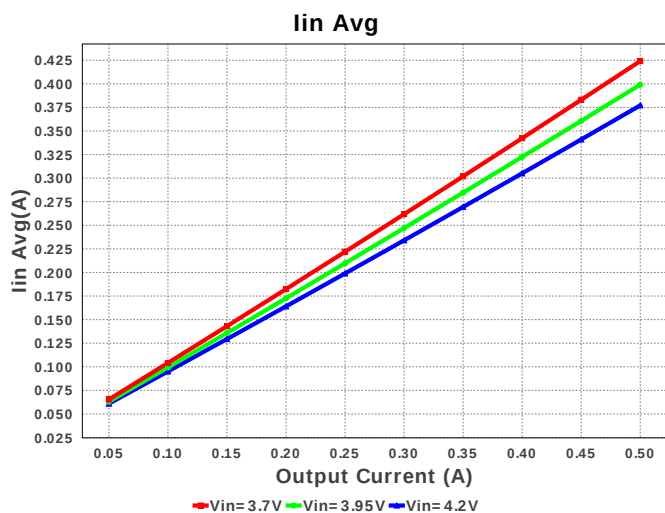

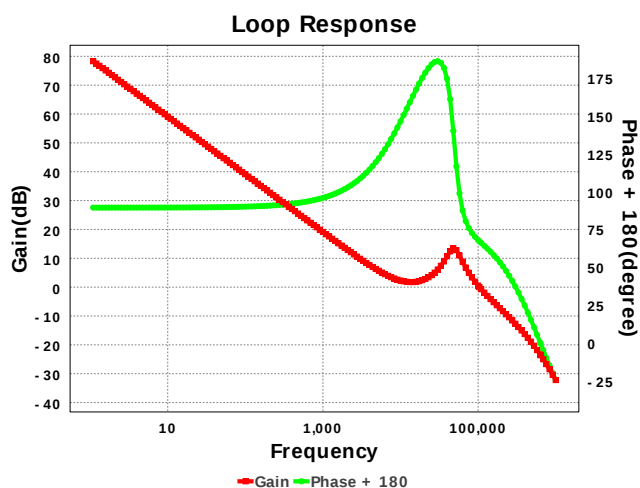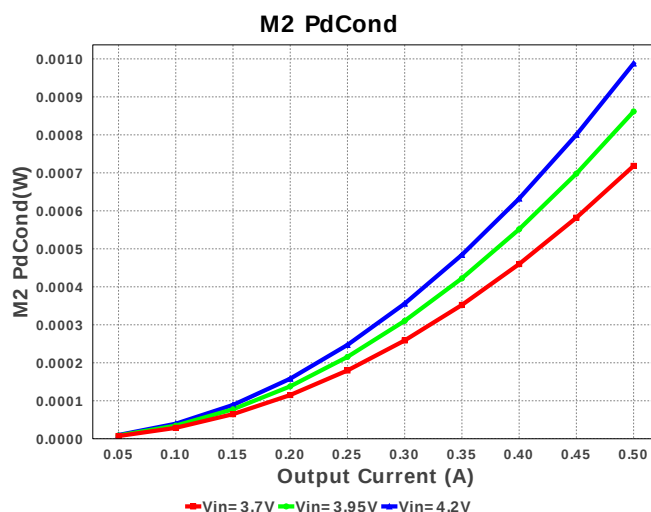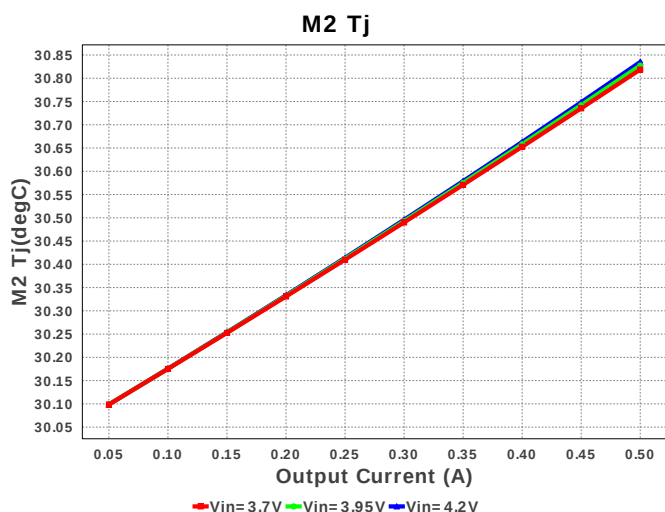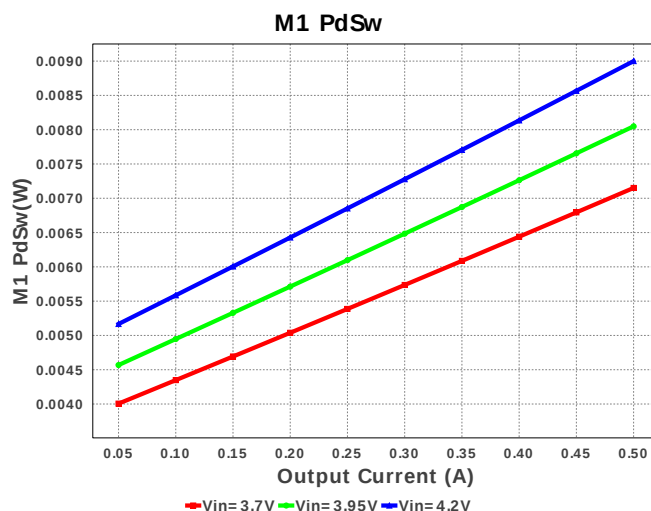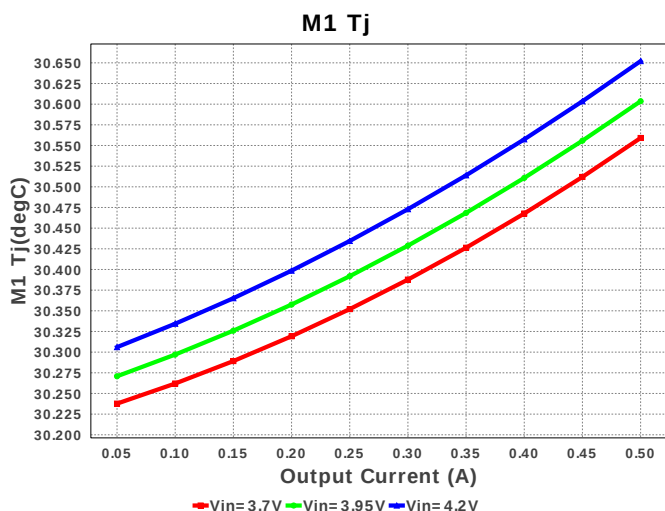

Operating Values

#	Name	Value	Category	Description
1.	Cin IRMS	234.796 mA	Current	Input capacitor RMS ripple current
2.	Cout IRMS	40.397 mA	Current	Output capacitor RMS ripple current
3.	Iin Avg	377.15 mA	Current	Average input current
4.	L Ipp	139.94 mA	Current	Peak-to-peak inductor ripple current
5.	SW Ipk	569.97 mA	Current	Peak switch current
6.	BOM Count	19	General	Total Design BOM count
7.	FootPrint	133.0 mm ²	General	Total Foot Print Area of BOM components
8.	Frequency	1.2 MHz	General	Switching frequency
9.	IC Tolerance	10.0 mV	General	IC Feedback Tolerance
10.	Pout	1.4 W	General	Total output power
11.	Total BOM	\$0.0	General	Total BOM Cost

#	Name	Value	Category	Description
12.	Low Freq Gain	78.323 dB	Op_Point	Gain at 10Hz
13.	Vout Actual	2.79 V	Op_Point	Vout Actual calculated based on selected voltage divider resistors
14.	Cross Freq	94.658 kHz	Op_point	Bode plot crossover frequency
15.	Duty Cycle	67.171 %	Op_point	Duty cycle
16.	Efficiency	88.383 %	Op_point	Steady state efficiency
17.	Gain Marg	-24.666 dB	Op_point	Bode Plot Gain Margin
18.	IC Tj	35.201 degC	Op_point	IC junction temperature
19.	IOUT_OP	500.0 mA	Op_point	Iout operating point
20.	M1 Tj	30.652 degC	Op_point	M1 MOSFET junction temperature
21.	M2 Tj	30.835 degC	Op_point	M2 MOSFET junction temperature
22.	Phase Marg	67.694 deg	Op_point	Bode Plot Phase Margin
23.	VIN_OP	4.2 V	Op_point	Vin operating point
24.	Vout p-p	6.626 mV	Op_point	Peak-to-peak output ripple voltage
25.	Cin Pd	275.645 μ W	Power	Input capacitor power dissipation
26.	Cout Pd	2.481 μ W	Power	Output capacitor power dissipation
27.	IC Pd	108.578 mW	Power	IC power dissipation
28.	L Pd	50.0 mW	Power	Inductor power dissipation
29.	M1 Pd	11.023 mW	Power	M1 MOSFET total power dissipation
30.	M1 PdCond	2.023 mW	Power	M1 MOSFET conduction losses
31.	M1 PdSw	9.0 mW	Power	M1 MOSFET switching losses
32.	M2 Pd	14.136 mW	Power	M2 MOSFET total power dissipation
33.	M2 PdCond	987.882 μ W	Power	M2 MOSFET conduction losses
34.	M2 PdSw	13.148 mW	Power	M2 MOSFET switching losses
35.	Total Pd	184.017 mW	Power	Total Power Dissipation
36.	Vout Tolerance	3.279 %		Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable

Design Inputs

#	Name	Value	Description
1.	Iout	500.0 m	Maximum Output Current
2.	VinMax	4.2	Maximum input voltage
3.	VinMin	3.7	Minimum input voltage
4.	Vout	2.8	Output Voltage
5.	base_pn	TPS40305	Texas Instruments Base Part Number
6.	source	DC	Input Source Type
7.	ta	30.0	Ambient temperature

Design Assistance

1. TPS40305 Product Folder : <http://www.ti.com/product/TPS40305> : contains the data sheet and other resources.

Texas Instruments' WEBENCH simulation tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Simulations are created using Texas Instruments' published specifications as well as the published specifications of other device manufacturers. While Texas Instruments does update this information periodically, this information may not be current at the time the simulation is built. Texas Instruments does not warrant the accuracy or completeness of the specifications or any information contained therein. Texas Instruments does not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. Texas Instruments does not warrant that the designs are production worthy.

You should completely validate and test your design implementation to confirm the system functionality for your application prior to production.

Use of Texas Instruments' WEBENCH simulation tools is subject to [Texas Instruments' Site Terms and Conditions of Use](#). Prototype boards based on WEBENCH created designs are provided AS IS without warranty of any kind for evaluation and testing purposes and are subject to the terms of the [Evaluation License Agreement](#).