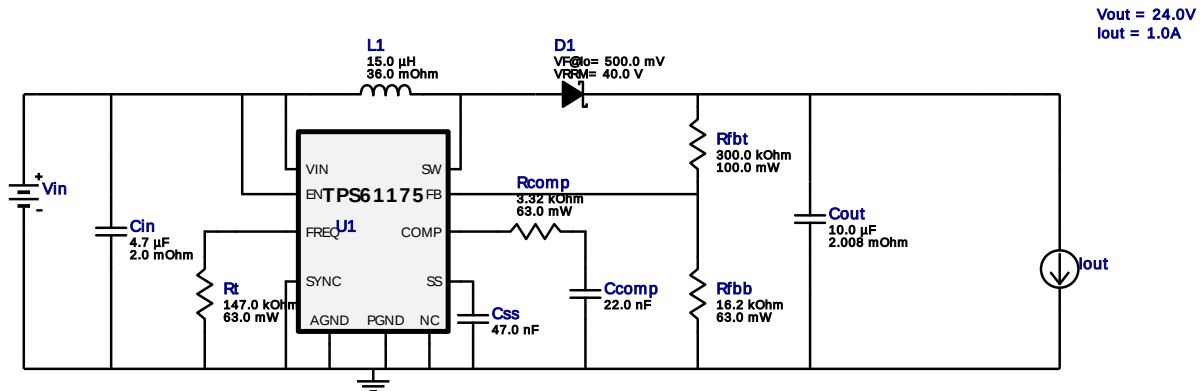


WEBENCH® Design Report





Design : 4738396/12 TPS61175PWPR
TPS61175PWPR 12.0V-12.5V to 24.00V @ 1.0A















Electrical BOM


#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	Ccomp	Yageo America	CC0805KRX7R9BB223 Series= X7R	Cap= 22.0 nF VDC= 50.0 V IRMS= 0.0 A	1	\$0.01	0805 7 mm ²
2.	Cin	MuRata	GRM21BR61E475MA12L Series= X5R	Cap= 4.7 uF ESR= 2.0 mOhm VDC= 25.0 V IRMS= 7.29 A	1	\$0.02	0805 7 mm ²
3.	Cout	MuRata	GRM32ER7YA106KA12L Series= X7R	Cap= 10.0 uF ESR= 2.008 mOhm VDC= 35.0 V IRMS= 4.6772 A	1	\$0.22	1210_280 15 mm ²
4.	Css	Taiyo Yuden	TMK212B7473KD-T Series= X7R	Cap= 47.0 nF VDC= 25.0 V IRMS= 0.0 A	1	\$0.01	0805 7 mm ²
5.	D1	Diodes Inc.	B340A-13-F	VF@Io= 500.0 mV VRRM= 40.0 V	1	\$0.11	SMA 37 mm ²
6.	L1	Bourns	SRR1208-150ML	L= 15.0 uH DCR= 36.0 mOhm	1	\$0.37	SRR1208 216 mm ²
7.	Rcomp	Vishay-Dale	CRCW04023K32FKED Series= CRCW..e3	Res= 3.32 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²
8.	Rfbb	Vishay-Dale	CRCW040216K2FKED Series= CRCW..e3	Res= 16.2 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²
9.	Rfbi	Yageo America	RC0603FR-07300KL Series= ?	Res= 300.0 kOhm Power= 100.0 mW Tolerance= 1.0%	1	\$0.01	0603 5 mm ²
10.	Rt	Vishay-Dale	CRCW0402147KFKED Series= CRCW..e3	Res= 147.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
11. U1		Texas Instruments	TPS61175PWPR	Switcher	1	\$1.40	 R-PDSO-G14 61 mm ²

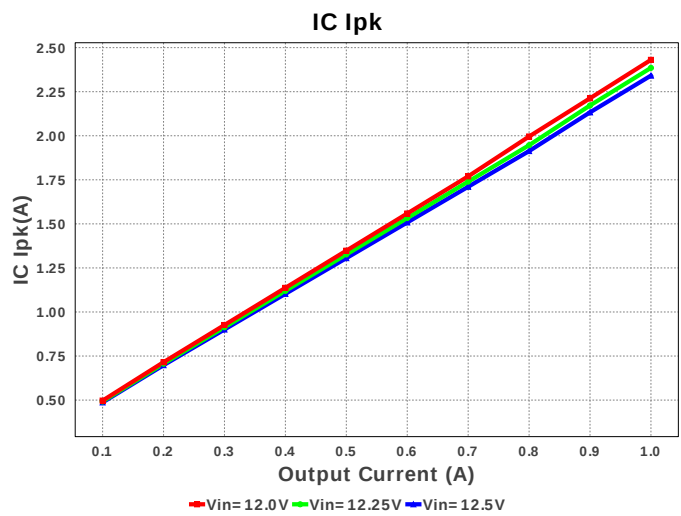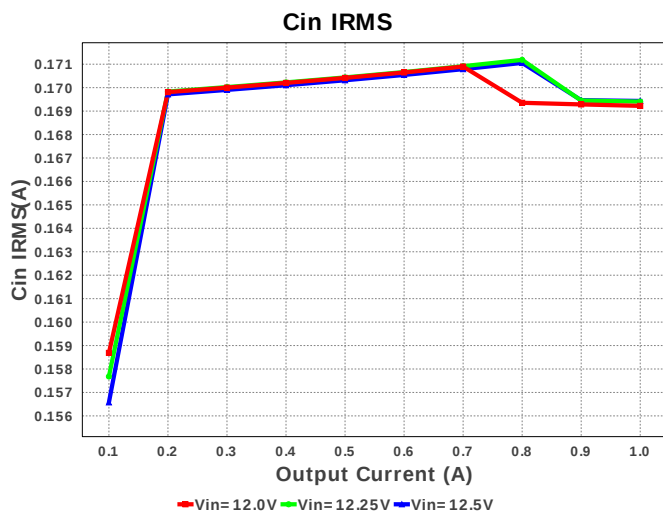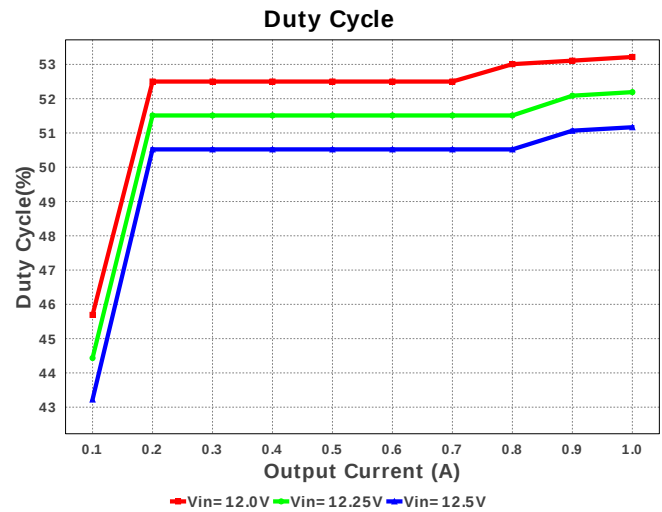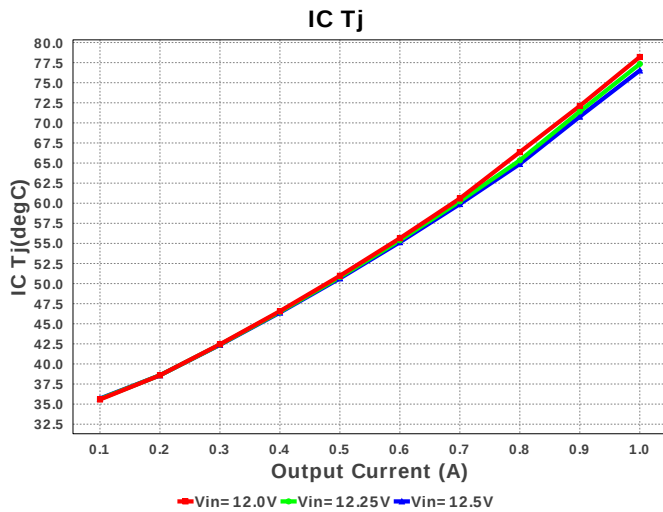

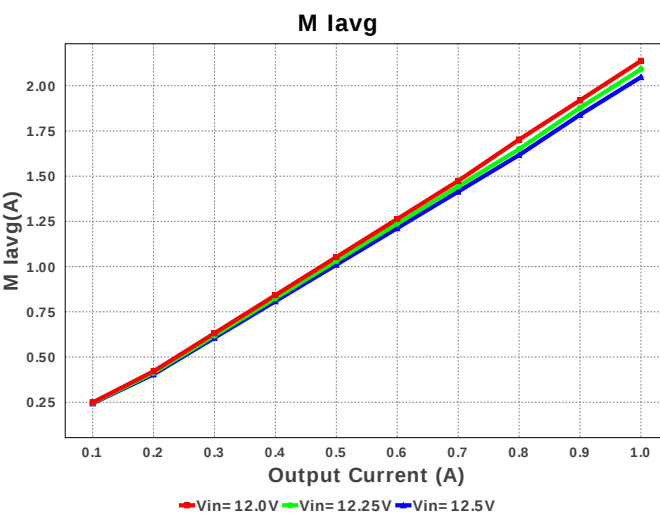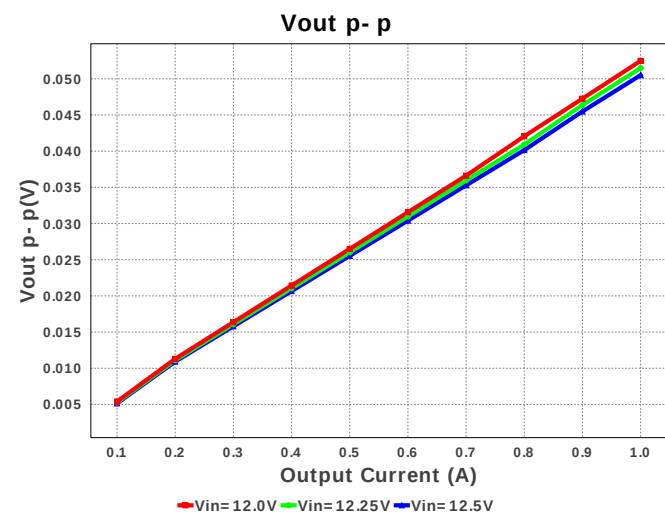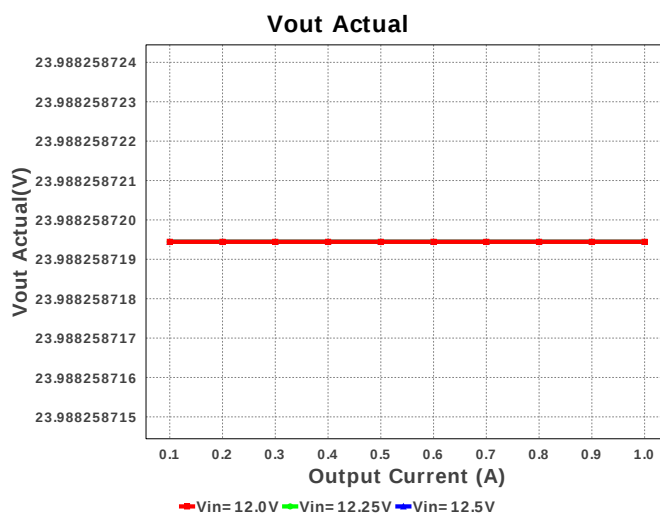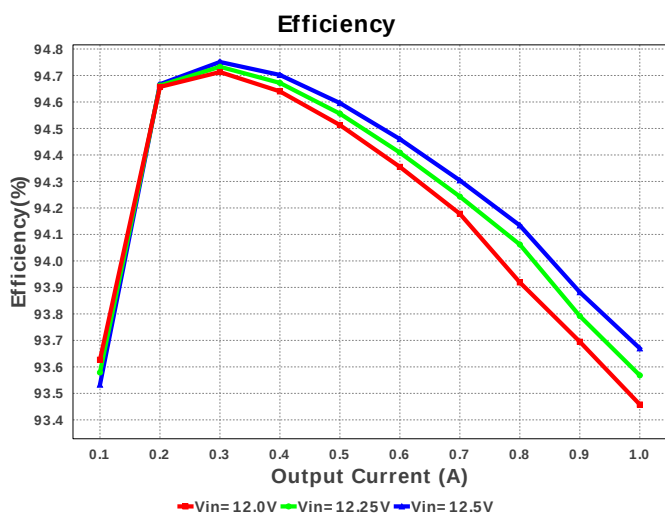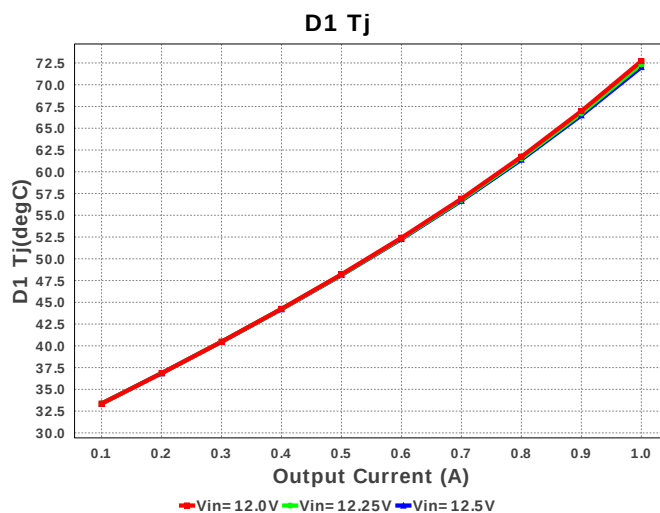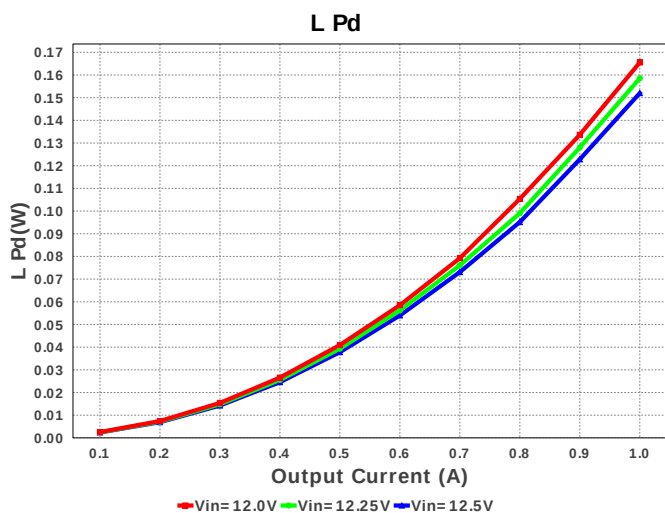

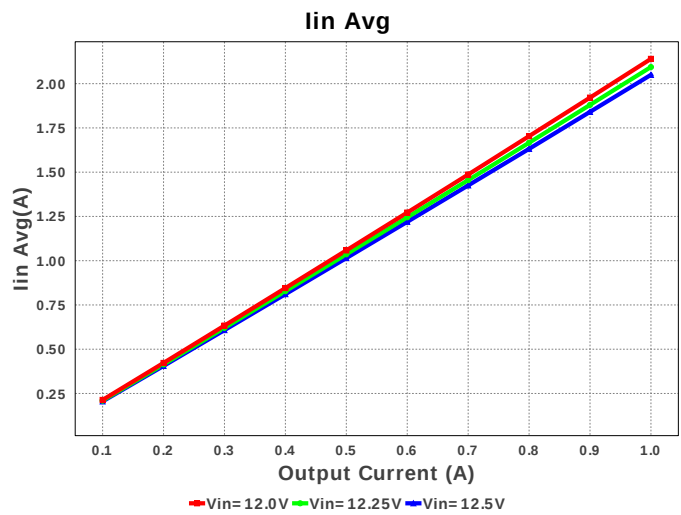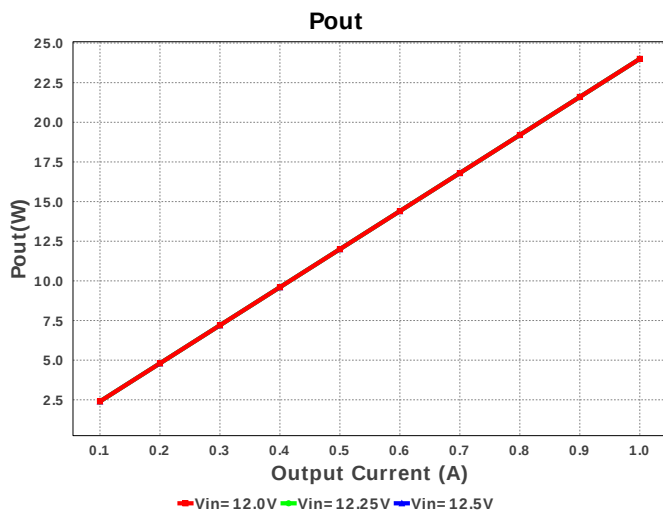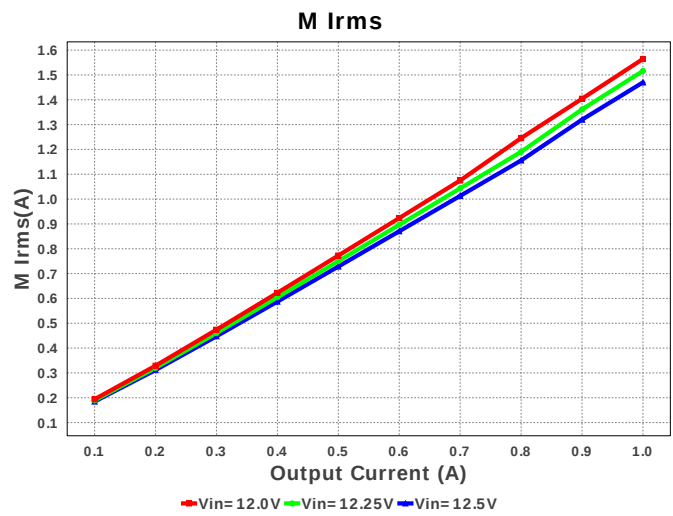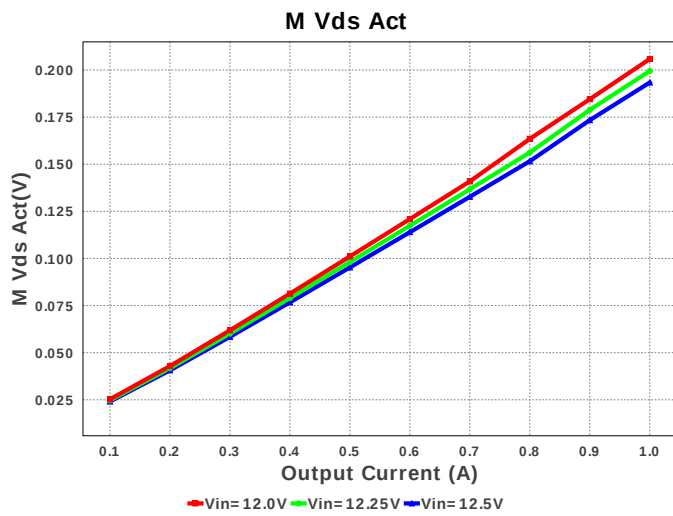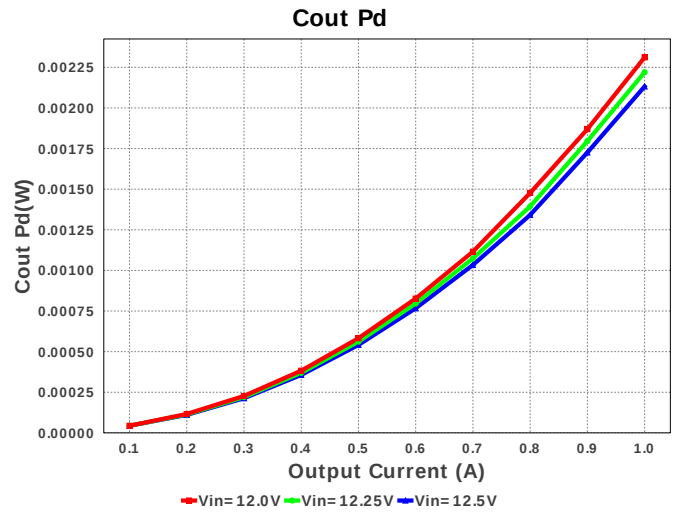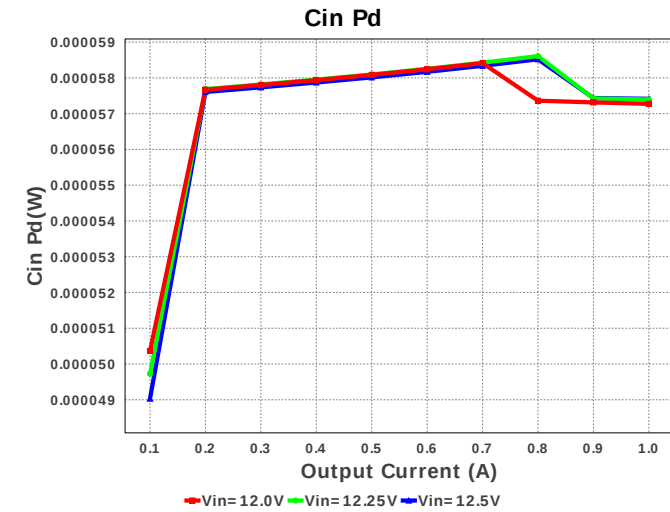

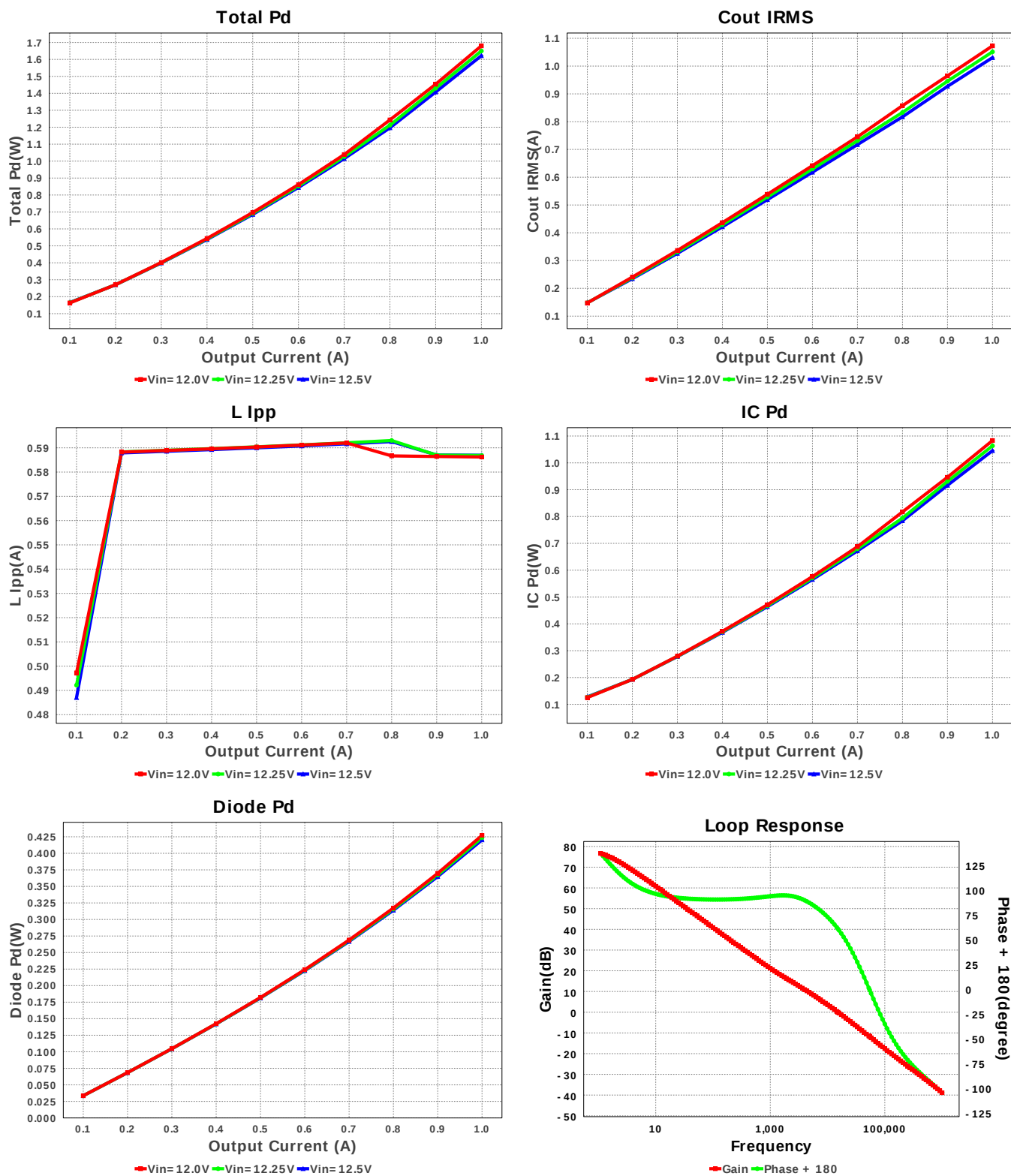

Operating Values

#	Name	Value	Category	Description
1.	Cin IRMS	169.223 mA	Current	Input capacitor RMS ripple current
2.	Cout IRMS	1.073 A	Current	Output capacitor RMS ripple current
3.	IC Ipk	2.431 A	Current	Peak switch current in IC
4.	Iin Avg	2.14 A	Current	Average input current
5.	L Ipp	586.21 mA	Current	Peak-to-peak inductor ripple current
6.	M Iavg	2.138 A	Current	MOSFET Average current
7.	M1 Irms	1.564 A	Current	Q Iavg
8.	BOM Count	11	General	Total Design BOM count
9.	FootPrint	363.0 mm ²	General	Total Foot Print Area of BOM components
10.	Frequency	665.27 kHz	General	Switching frequency
11.	IC Tolerance	20.0 mV	General	IC Feedback Tolerance

#	Name	Value	Category	Description
12.	M Vds Act	205.843 mV	General	Voltage drop across the MosFET
13.	Pout	24.0 W	General	Total output power
14.	Total BOM	\$2.18	General	Total BOM Cost
15.	D1 Tj	72.714 degC	Op_Point	D1 junction temperature
16.	Low Freq Gain	76.527 dB	Op_Point	Gain at 10Hz
17.	Vout Actual	23.988 V	Op_Point	Vout Actual calculated based on selected voltage divider resistors
18.	Vout OP	24.0 V	Op_Point	Operational Output Voltage
19.	Cross Freq	11.346 kHz	Op_point	Bode plot crossover frequency
20.	Duty Cycle	53.217 %	Op_point	Duty cycle
21.	Efficiency	93.458 %	Op_point	Steady state efficiency
22.	Gain Marg	-13.634 dB	Op_point	Bode Plot Gain Margin
23.	IC Tj	78.203 degC	Op_point	IC junction temperature
24.	ICThetaJA	44.5 degC/W	Op_point	IC junction-to-ambient thermal resistance
25.	IOUT_OP	1.0 A	Op_point	Iout operating point
26.	Phase Marg	65.871 deg	Op_point	Bode Plot Phase Margin
27.	VIN_OP	12.0 V	Op_point	Vin operating point
28.	Vout p-p	41.174 mV	Op_point	Peak-to-peak output ripple voltage
29.	Cin Pd	57.273 μW	Power	Input capacitor power dissipation
30.	Cout Pd	2.311 mW	Power	Output capacitor power dissipation
31.	Diode Pd	427.14 mW	Power	Diode power dissipation
32.	IC Pd	1.083 W	Power	IC power dissipation
33.	L Pd	165.516 mW	Power	Inductor power dissipation
34.	Total Pd	1.68 W	Power	Total Power Dissipation
35.	Vout Tolerance	3.575 %		Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable

Design Inputs

#	Name	Value	Description
1.	Iout	1.0	Maximum Output Current
2.	VinMax	12.5	Maximum input voltage
3.	VinMin	12.0	Minimum input voltage
4.	Vout	24.0	Output Voltage
5.	base_pn	TPS61175	Base Product Number
6.	source	DC	Input Source Type
7.	Ta	30.0	Ambient temperature

Design Assistance

1. **TPS61175 Product Folder** : <http://www.ti.com/product/TPS61175> : contains the data sheet and other resources.

Texas Instruments' WEBENCH simulation tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Simulations are created using Texas Instruments' published specifications as well as the published specifications of other device manufacturers. While Texas Instruments does update this information periodically, this information may not be current at the time the simulation is built. Texas Instruments does not warrant the accuracy or completeness of the specifications or any information contained therein. Texas Instruments does not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. Texas Instruments does not warrant that the designs are production worthy.

You should completely validate and test your design implementation to confirm the system functionality for your application prior to production.

Use of Texas Instruments' WEBENCH simulation tools is subject to [Texas Instruments' Site Terms and Conditions of Use](#). Prototype boards based on WEBENCH created designs are provided AS IS without warranty of any kind for evaluation and testing purposes and are subject to the terms of the [Evaluation License Agreement](#).