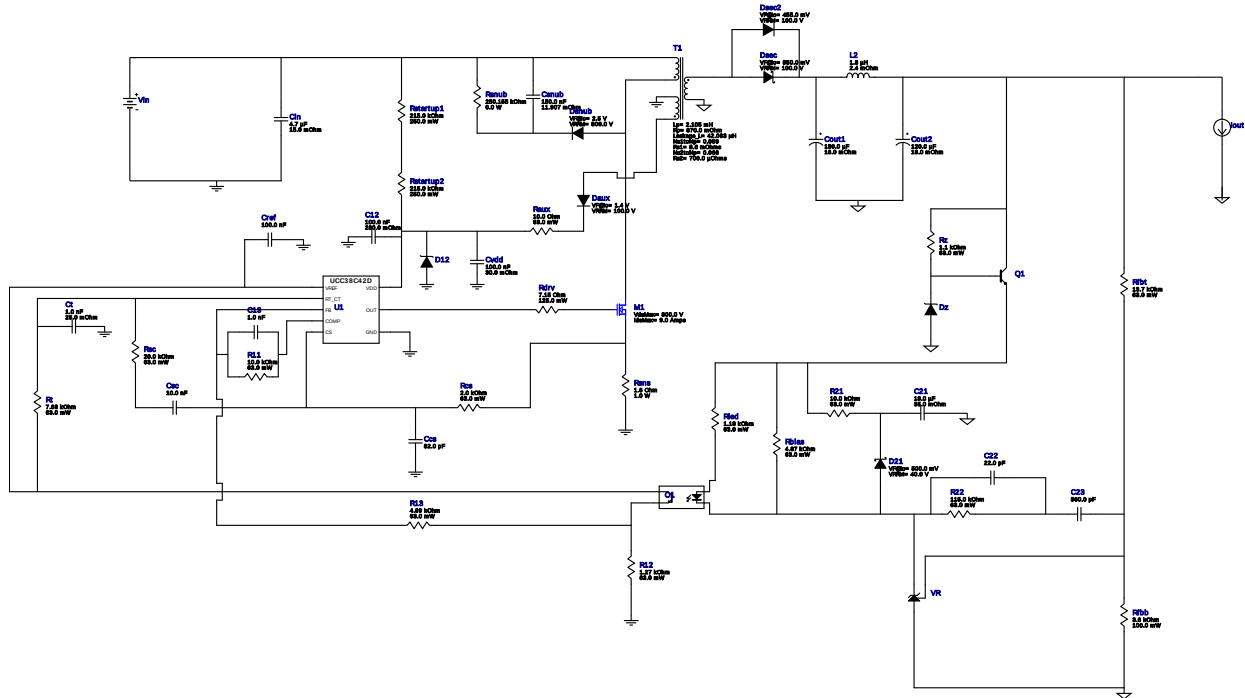




WEBENCH® Design Report


Design : 4354914/10 UCC38C42DR
UCC38C42DR 150.0V-280.0V to 12.00V @ 2.0A





Electrical BOM







#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	C12	AVX	0805C104KAT2A Series= X7R	Cap= 100.0 nF ESR= 280.0 mOhm VDC= 25.0 V IRMS= 0.0 A	1	\$0.01	0805 7 mm ²
2.	C13	MuRata	GRM033R71C102KA01D Series= X7R	Cap= 1.0 nF VDC= 16.0 V IRMS= 0.0 A	1	\$0.01	0201 2 mm ²
3.	C21	Panasonic	50SVPF18M Series= ?	Cap= 18.0 uF ESR= 35.0 mOhm VDC= 50.0 V IRMS= 2.7 A	1	\$0.53	CAPSMT_62_E7 106 mm ²
4.	C22	Kemet	C0805C220K3GACTU Series= C0G/NP0	Cap= 22.0 pF VDC= 25.0 V IRMS= 0.0 A	1	\$0.01	0805 7 mm ²
5.	C23	MuRata	GRM033R71C561KA01D Series= X7R	Cap= 560.0 pF VDC= 16.0 V IRMS= 0.0 A	1	\$0.01	0201 2 mm ²
6.	Ccs	TDK	C0603C0G1E820J030BA Series= C0G/NP0	Cap= 82.0 pF VDC= 5.0 V IRMS= 0.0 A	1	\$0.01	0201 2 mm ²





 
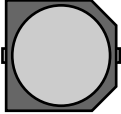
#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
7.	Cin	TDK	B32924D3475K Series= B32924	Cap= 4.7 uF ESR= 15.0 mOhm VDC= 630.0 V IRMS= 457.0 mA	1	\$1.68	 B32924_31mm 770 mm ²
8.	Cout1	Panasonic	25SVPF180M Series= ?	Cap= 180.0 uF ESR= 16.0 mOhm VDC= 25.0 V IRMS= 4.65 A	1	\$0.61	 CAPSMT_62_E12 106 mm ²
9.	Cout2	Panasonic	35SVPF120M Series= ?	Cap= 120.0 uF ESR= 18.0 mOhm VDC= 35.0 V IRMS= 4.4 A	1	\$0.70	 CAPSMT_62_F12 151 mm ²
10.	Cref	MuRata	GRM155R61C104KA88D Series= X5R	Cap= 100.0 nF VDC= 16.0 V IRMS= 0.0 A	1	\$0.01	 0402 3 mm ²
11.	Csc	MuRata	GRM033R60J103KA01D Series= X5R	Cap= 10.0 nF VDC= 6.3 V IRMS= 0.0 A	1	\$0.01	 0201 2 mm ²
12.	Csnub	TDK	C3225X7T2J154K Series= X7T	Cap= 150.0 nF ESR= 11.907 mOhm VDC= 630.0 V IRMS= 0.0 A	1	\$0.19	 1210 15 mm ²
13.	Ct	Kemet	C0805C102J5GACTU Series= C0G/NP0	Cap= 1.0 nF ESR= 25.0 mOhm VDC= 50.0 V IRMS= 1.71 A	1	\$0.01	 0805 7 mm ²
14.	Cvdd	MuRata	GRM188R71E104KA01D Series= X7R	Cap= 100.0 nF ESR= 30.0 mOhm VDC= 25.0 V IRMS= 1.51 A	1	\$0.01	 0603 5 mm ²
15.	D12	Diodes Inc.	MMSZ5248B-7-F	Zener	1	\$0.04	 SOD-123 13 mm ²
16.	D21	Vishay-Semiconductor	SS14-E3/61T	VF@Io= 500.0 mV VRRM= 40.0 V	1	\$0.08	 SMA 37 mm ²
17.	Daux	NXP Semiconductor	BAS316,115	VF@Io= 1.4 V VRRM= 100.0 V	1	\$0.02	 SOD-323 9 mm ²
18.	Dsec	Comchip Technology	CDBC5100-G	VF@Io= 850.0 mV VRRM= 100.0 V	1	\$0.26	 SMC 83 mm ²
19.	Dsec2	STMicroelectronics	STPS20M100SG-TR	VF@Io= 455.0 mV VRRM= 100.0 V	1	\$1.33	 DDPAK 210 mm ²
20.	Dsnub	Bourns	CD1408-FU1800	VF@Io= 2.5 V VRRM= 800.0 V	1	\$0.13	 Diode_1408 13 mm ²
21.	Dz	ON Semiconductor	BZX84C9V1LT1G	Zener	1	\$0.02	 SOT-23 14 mm ²






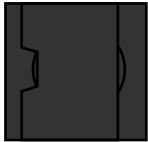
#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
22.	L2	Coilcraft	SER1360-182KLB	L= 1.8 µH DCR= 2.4 mOhm	1	\$0.72	 SER1360 225 mm²
23.	M1	STMicroelectronics	STF10N80K5	VdsMax= 800.0 V IdsMax= 9.0 Amps	1	\$2.52	 TO-220FP 79 mm²
24.	O1	Vishay-Semiconductor	TCMT1107	Optocoupler	1	\$0.21	 SOP-4 44 mm²
25.	Q1	ON Semiconductor	BC846BLT1G	Bipolar Transistor	1	\$0.02	 SOT-23 14 mm²
26.	R11	Vishay-Dale	CRCW040210K0FKED Series= CRCW..e3	Res= 10.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm²
27.	R12	Vishay-Dale	CRCW04021K27FKED Series= CRCW..e3	Res= 1.27 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm²
28.	R13	Vishay-Dale	CRCW04024K99FKED Series= CRCW..e3	Res= 4.99 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm²
29.	R21	Vishay-Dale	CRCW040210K0FKED Series= CRCW..e3	Res= 10.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm²
30.	R22	Vishay-Dale	CRCW0402115KFKED Series= CRCW..e3	Res= 115.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm²
31.	Raux	Vishay-Dale	CRCW040210R0FKED Series= CRCW..e3	Res= 10.0 Ohm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm²
32.	Rbias	Vishay-Dale	CRCW04024K87FKED Series= CRCW..e3	Res= 4.87 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm²
33.	Rcs	Vishay-Dale	CRCW04022K00FKED Series= CRCW..e3	Res= 2.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm²
34.	Rdrv	Vishay-Dale	CRCW08057R15FKEA Series= CRCW..e3	Res= 7.15 Ohm Power= 125.0 mW Tolerance= 1.0%	1	\$0.01	 0805 7 mm²
35.	Rfbb	Yageo America	RC0603FR-073K6L Series= ?	Res= 3.6 kOhm Power= 100.0 mW Tolerance= 1.0%	1	\$0.01	 0603 5 mm²
36.	Rfbt	Vishay-Dale	CRCW040213K7FKED Series= CRCW..e3	Res= 13.7 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm²
37.	Rled	Vishay-Dale	CRCW04021K18FKED Series= CRCW..e3	Res= 1.18 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm²
38.	Rsc	Vishay-Dale	CRCW040220K0FKED Series= CRCW..e3	Res= 20.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm²
39.	Rsns	Panasonic	ERJ-1TRQF1R6U Series= ?	Res= 1.6 Ohm Power= 1.0 W Tolerance= 1.0%	1	\$0.19	 2512 43 mm²
40.	Rsns	CUSTOM	CUSTOM Series= ?	Res= 250.155 kOhm Power= 0.0 W Tolerance= 0.0%	1	NA	CUSTOM 0 mm²







#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
41.	Rstartup1	Panasonic	ERJ-8ENF2153V Series= ERJ-8E	Res= 215.0 kOhm Power= 250.0 mW Tolerance= 1.0%	1	\$0.01	 1206 11 mm ²
42.	Rstartup2	Panasonic	ERJ-8ENF2153V Series= ERJ-8E	Res= 215.0 kOhm Power= 250.0 mW Tolerance= 1.0%	1	\$0.01	 1206 11 mm ²
43.	Rt	Vishay-Dale	CRCW04027K68FKED Series= CRCW..e3	Res= 7.68 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
44.	Rz	Vishay-Dale	CRCW04021K10FKED Series= CRCW..e3	Res= 1.1 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
45.	T1	CUSTOM	CUSTOM	Lp= 2.105 mH Rp= 870.0 mOhm Leakage_L= 42.093 μH Ns1toNp= 0.059 Rs1= 8.6 mOhms Ns2toNp= 0.066 Rs2= 700.0 μOhms	1	NA	CUSTOM 0 mm ²
46.	U1	Texas Instruments	UCC38C42DR	Switcher	1	\$0.60	 D0008A 57 mm ²
47.	VR	Texas Instruments	TL431AIDBVR	Voltage References	1	\$0.07	 R-PDSO-G3 16 mm ²

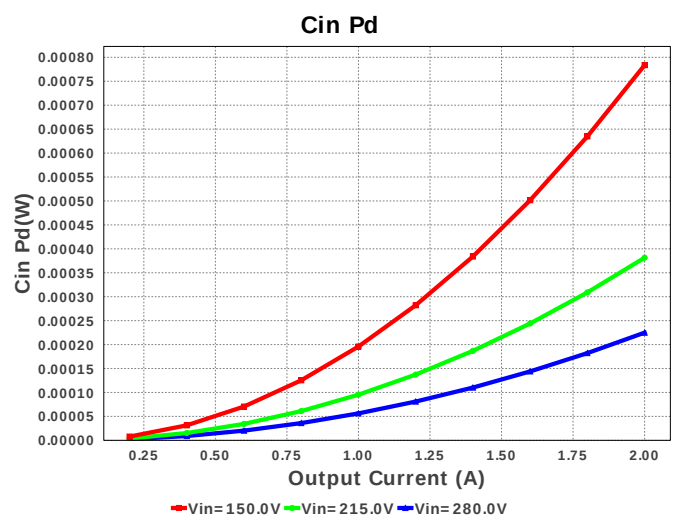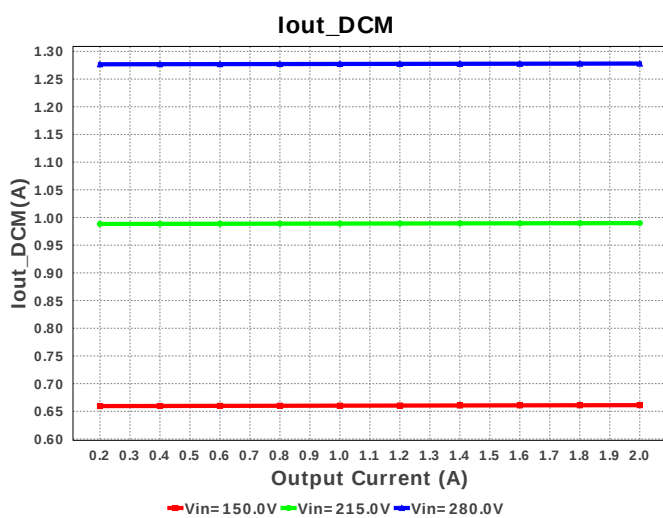

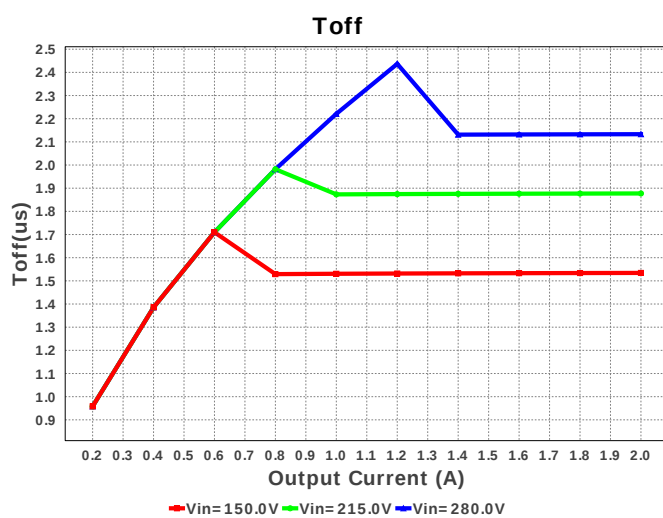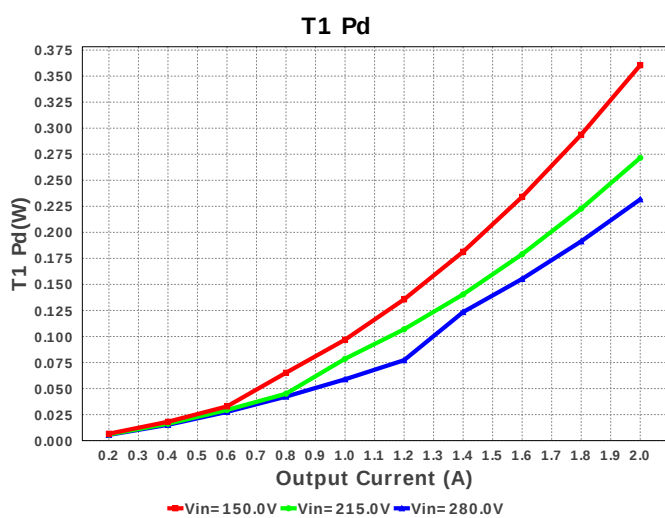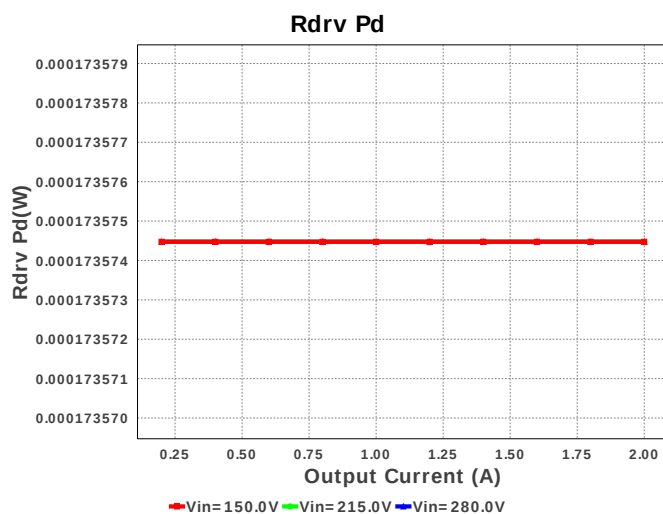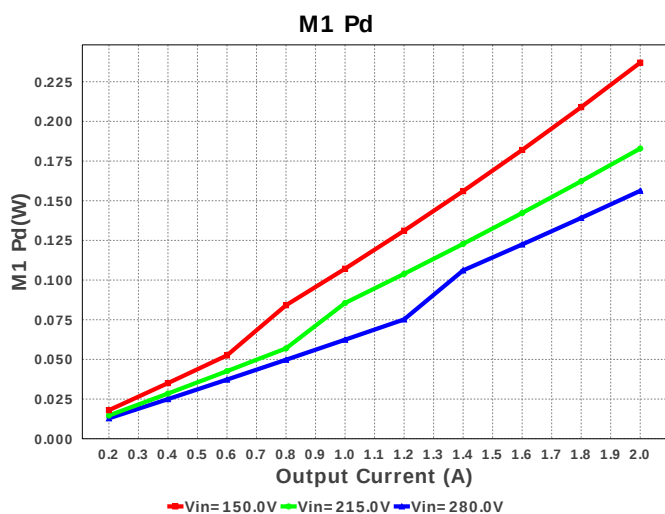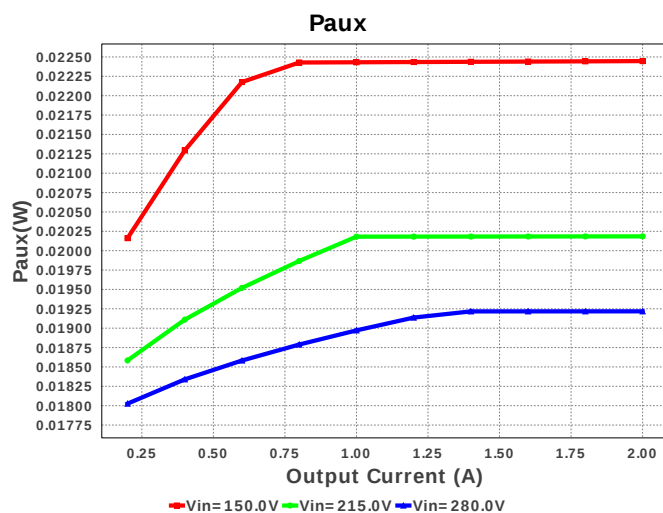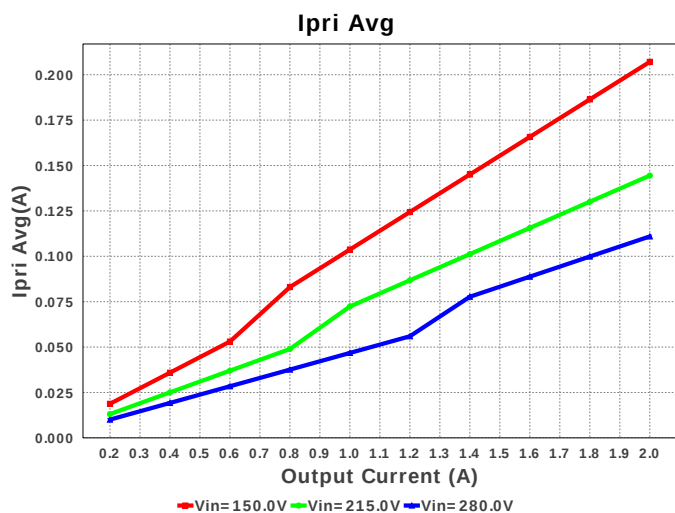


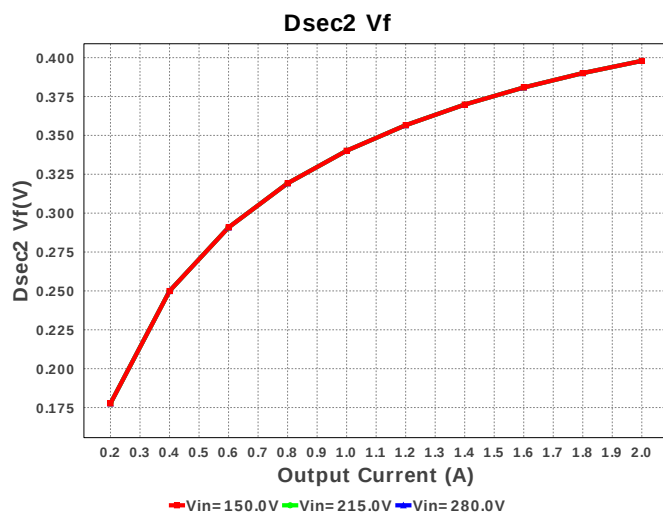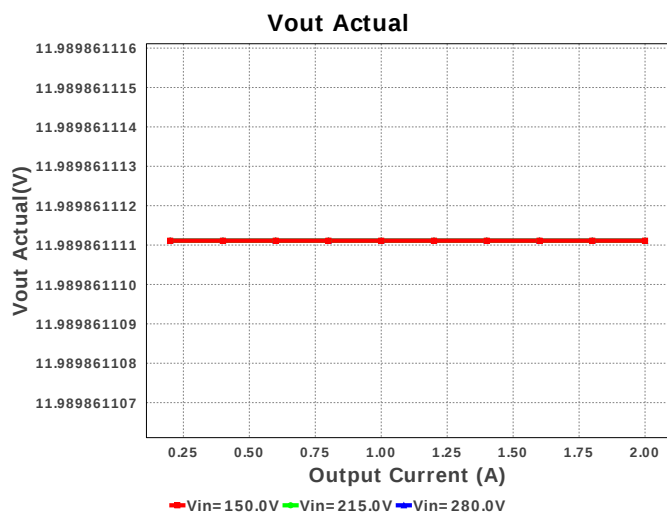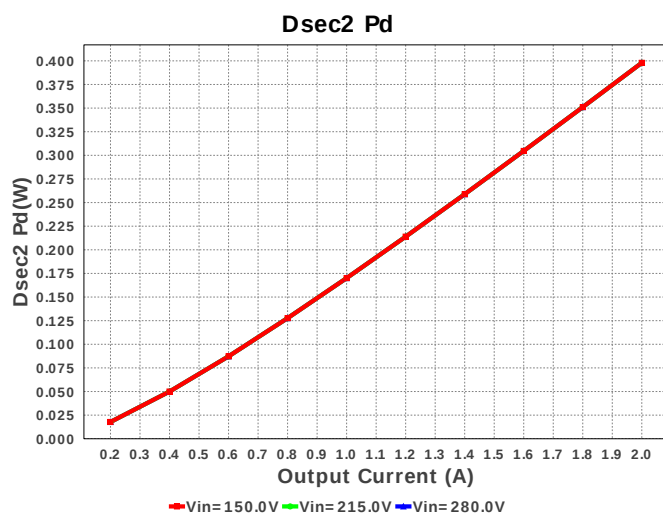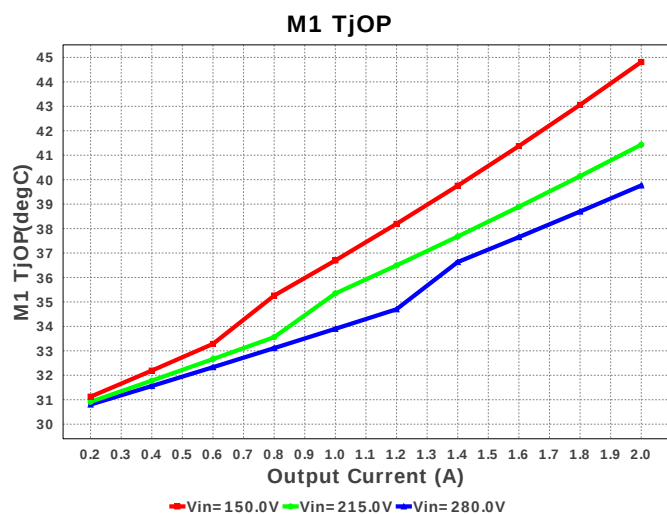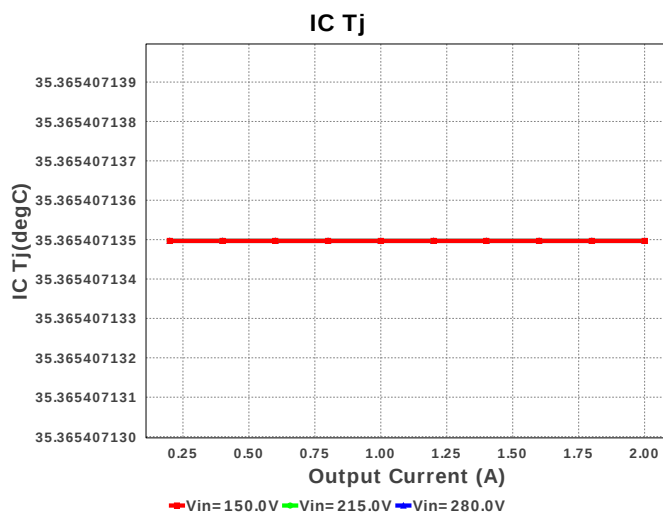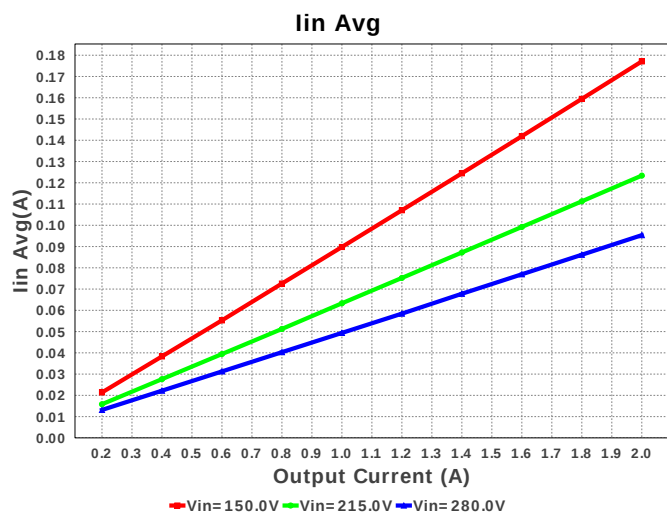

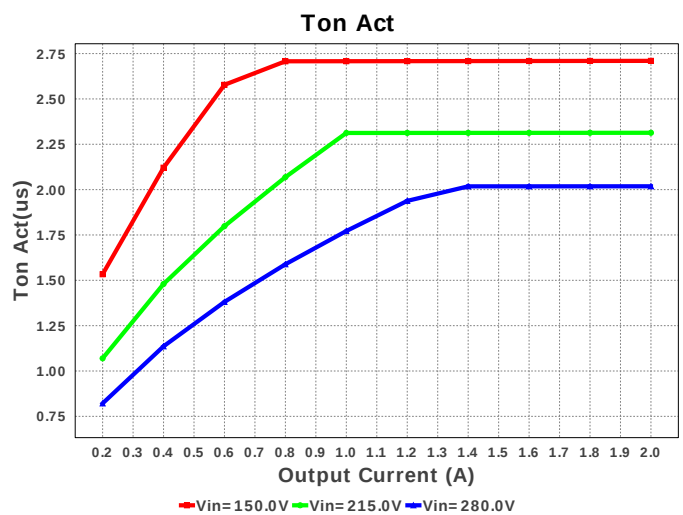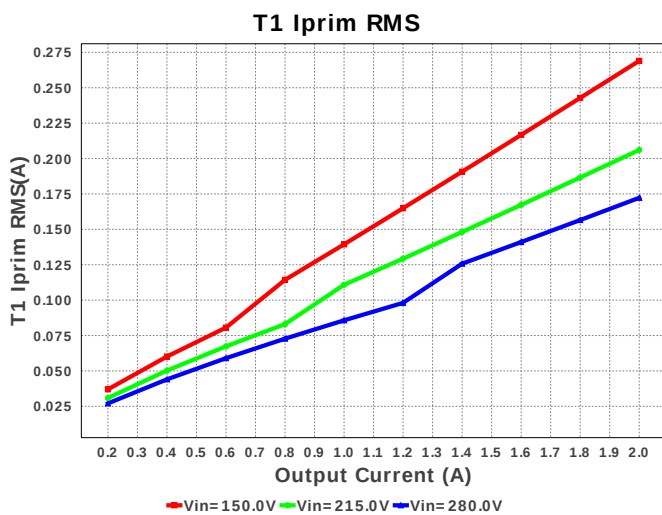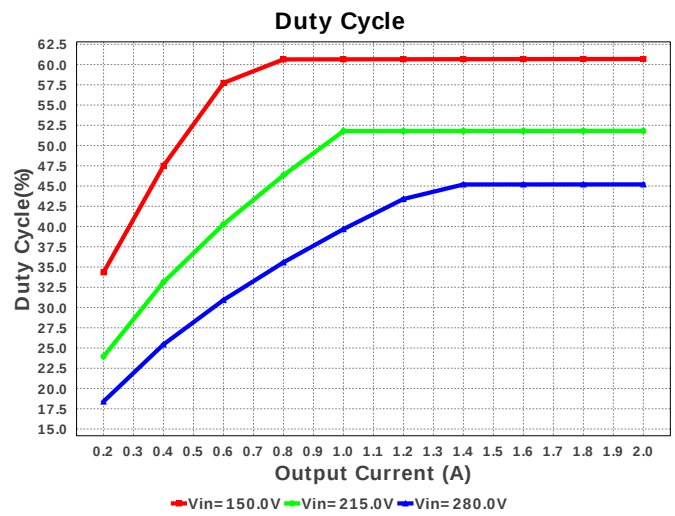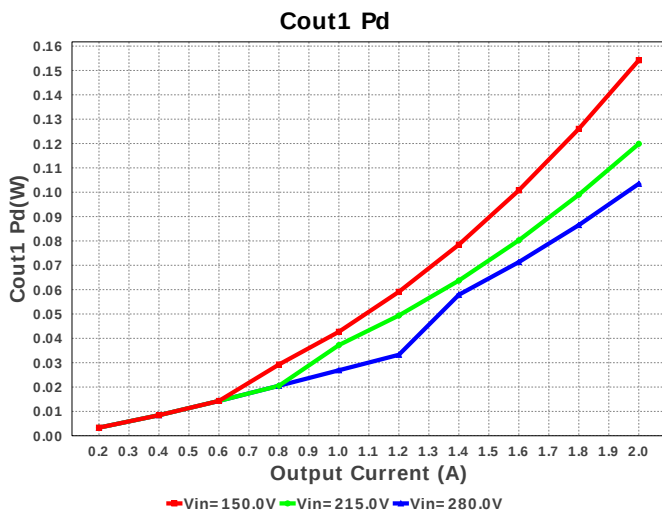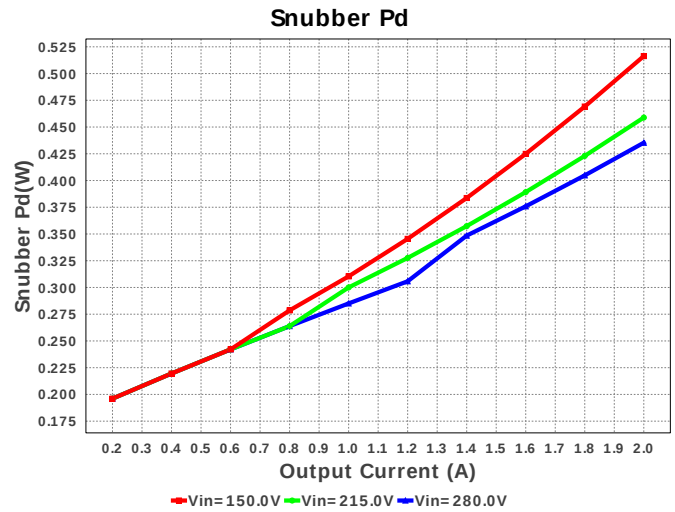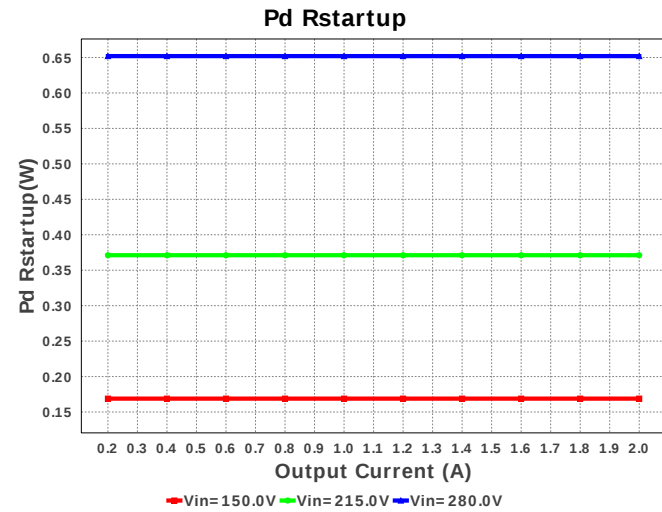


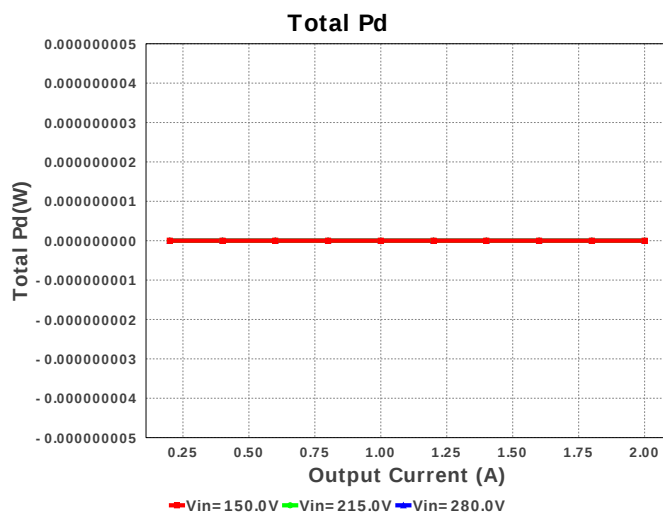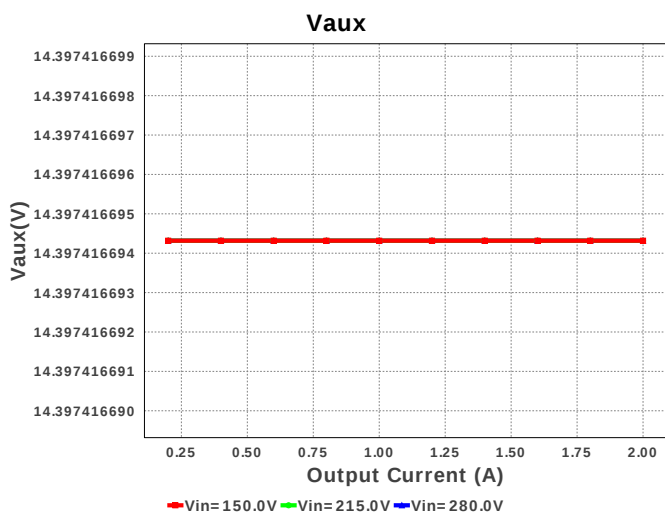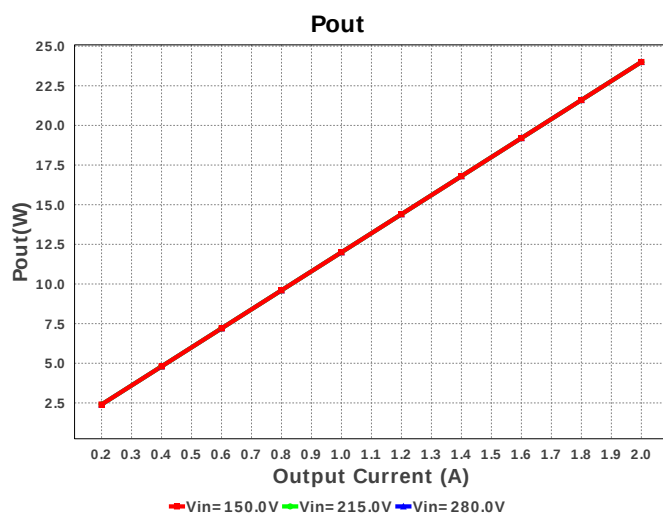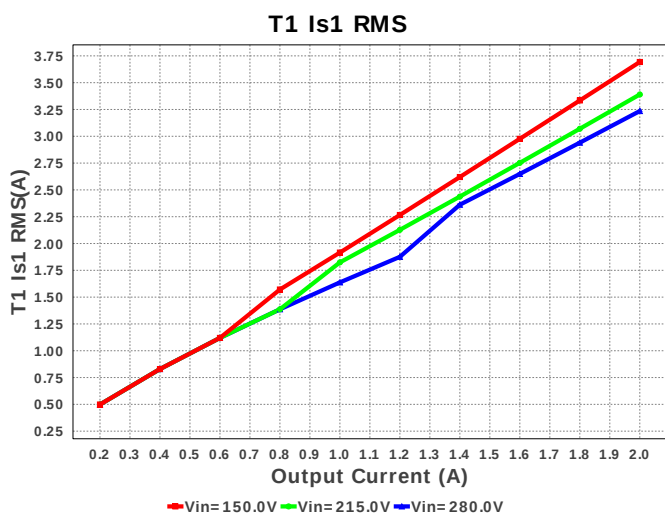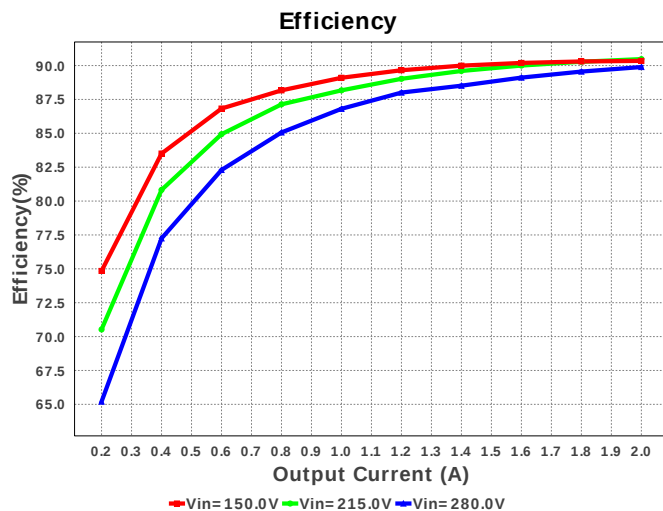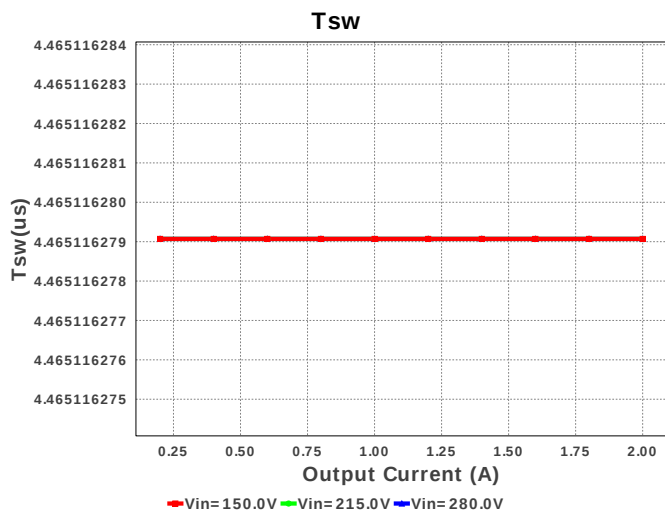


T1 Is1 pk

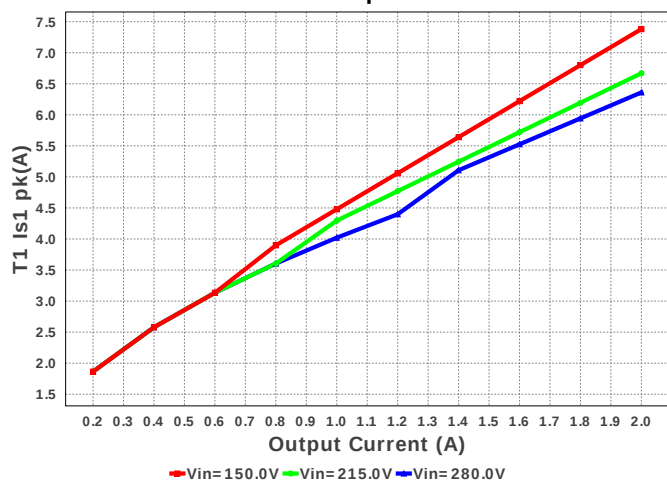


Dsec Pd

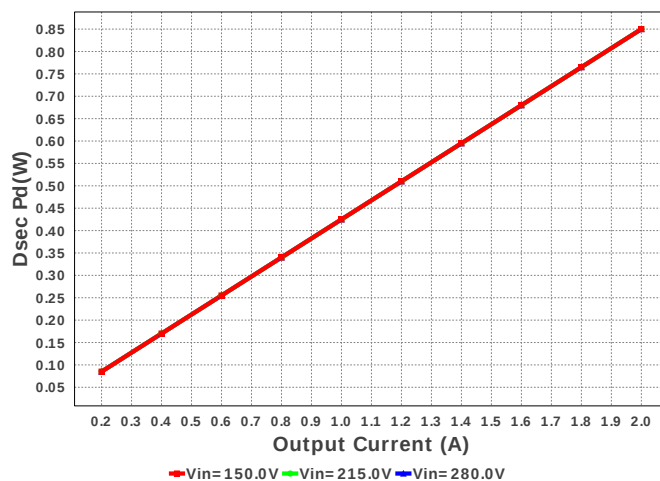


Tdead

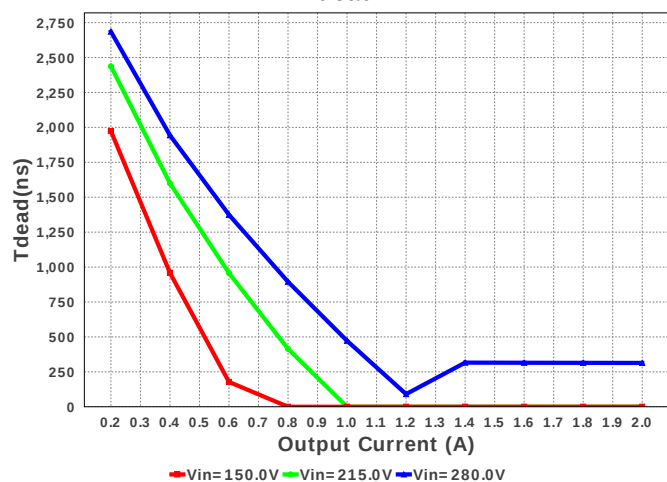


IC Pd






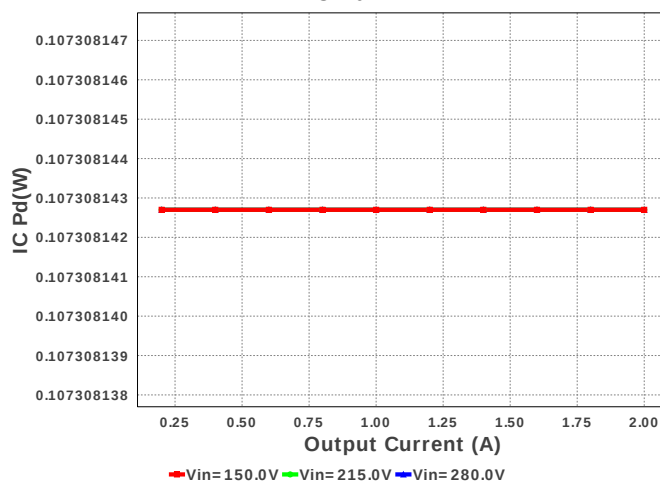






Cout1 IRMS

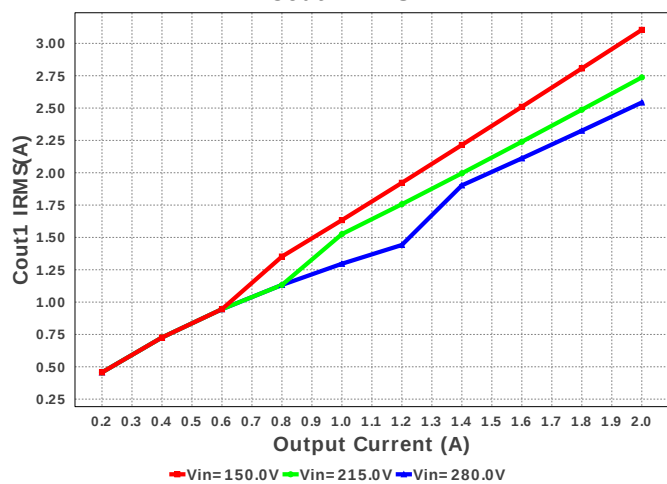

Dsec Vf

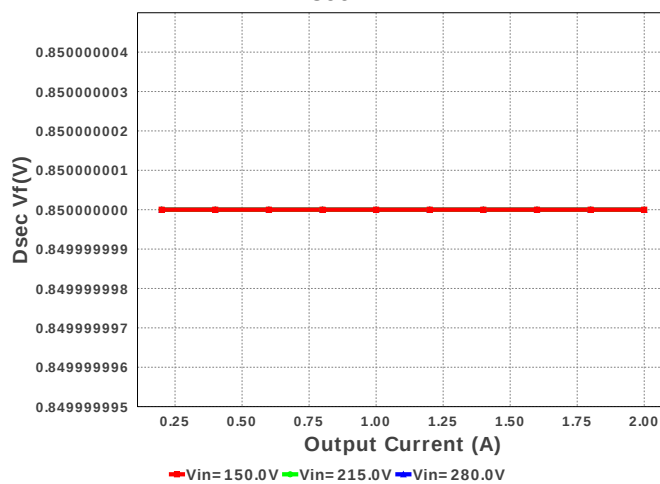

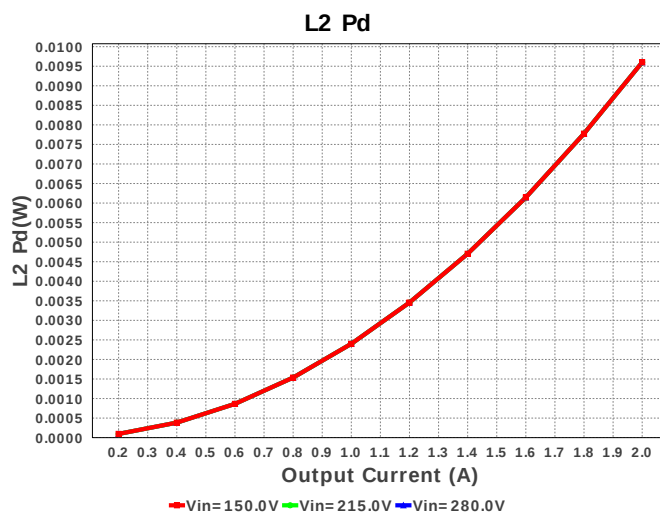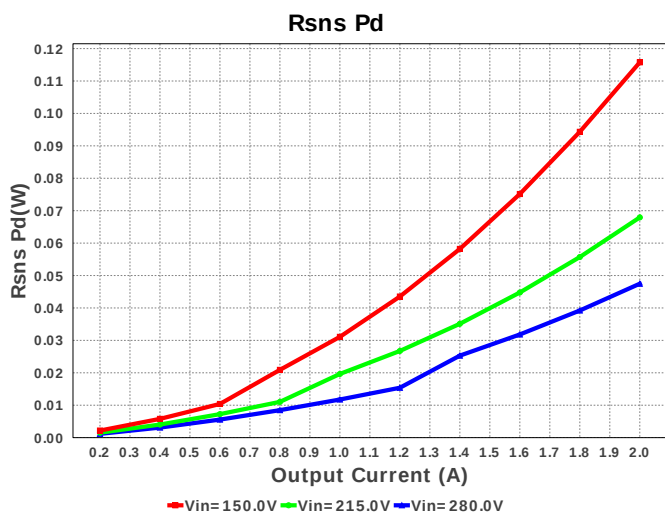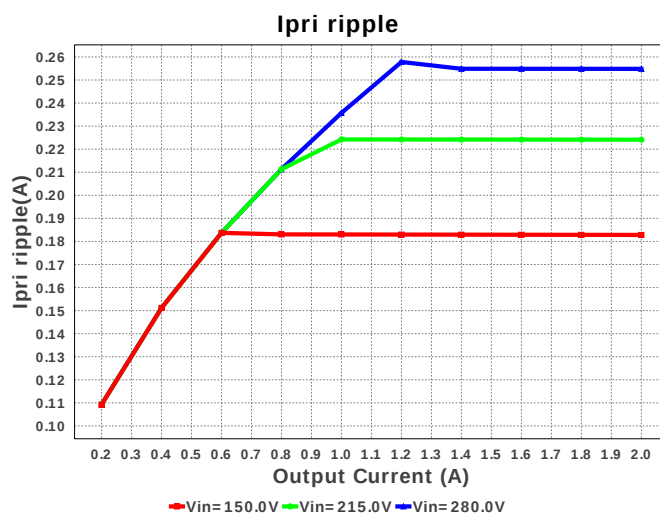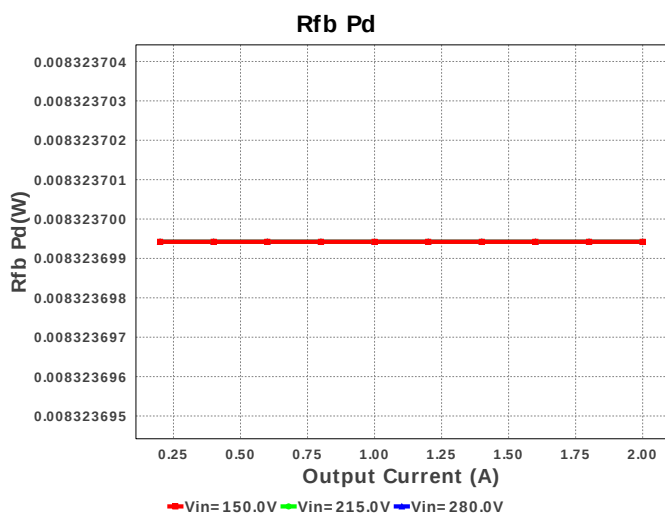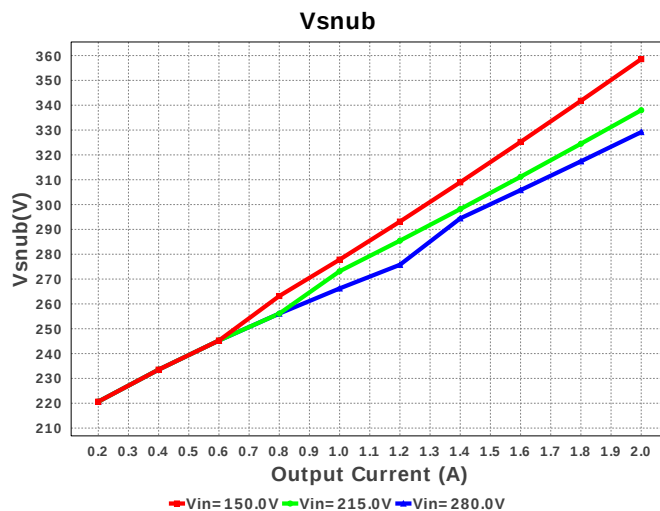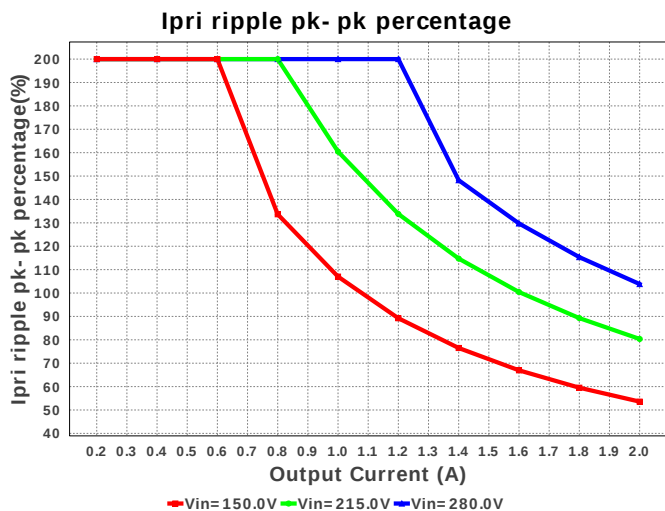

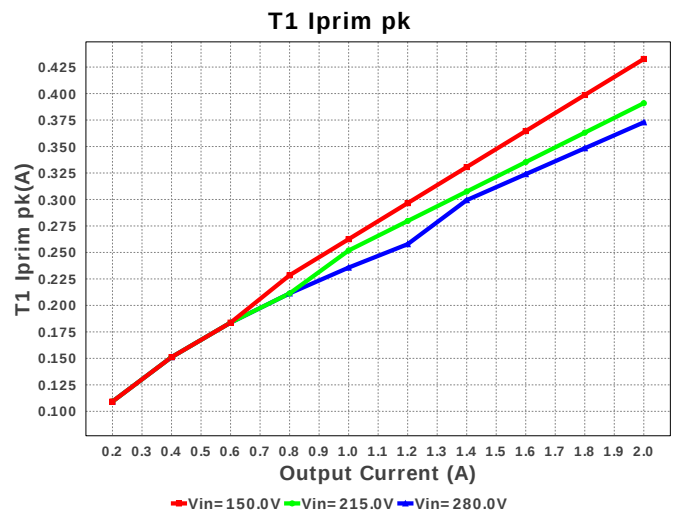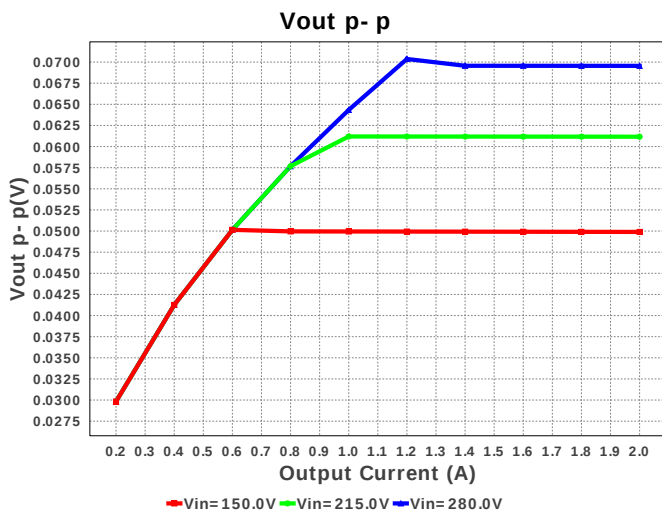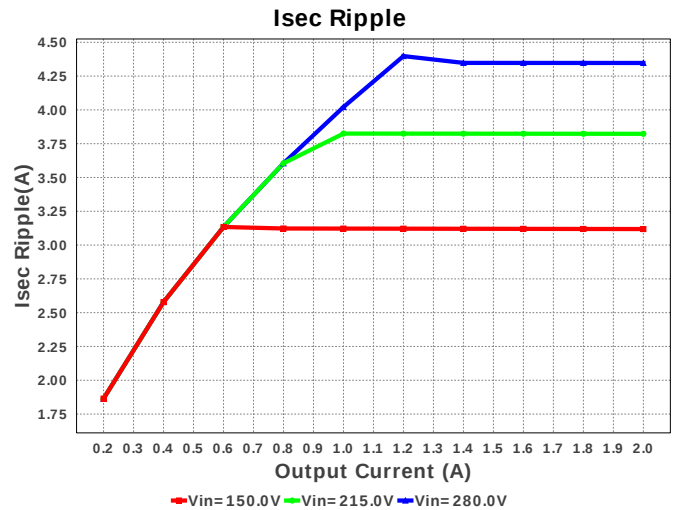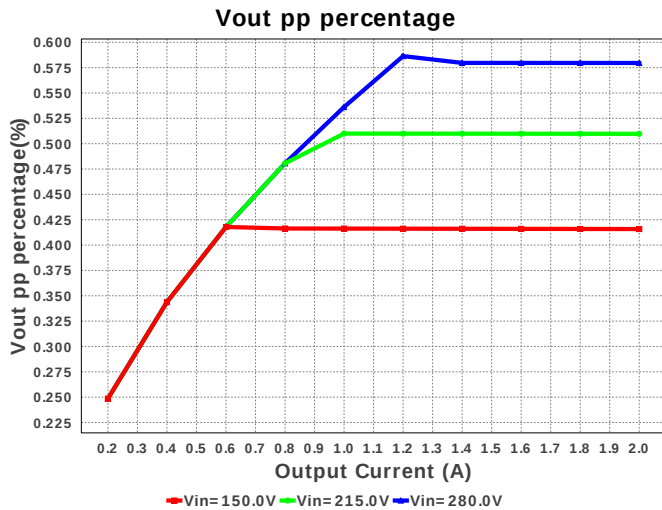

Operating Values

#	Name	Value	Category	Description
1.	Cout1 IRMS	3.104 A	Current	Output capacitor1 RMS ripple current
2.	Iin Avg	177.099 mA	Current	Average input current
3.	Iout_DCM	661.13 mA	Current	Approximate Current below which DCM mode of operation will begin
4.	Ipri Avg	207.085 mA	Current	Average Current in Primary Winding over the complete Switching Period
5.	Ipri ripple	182.817 mA	Current	Ripple Current in the Primary Winding
6.	Ipri ripple pk-pk percentage	53.576 %	Current	Primary Current pk-pk ripple percentage(of Ipri avg during ton only)
7.	Isec Ripple	3.119 A	Current	Ripple Current in the Secondary Winding
8.	T1 Iprim RMS	268.985 mA	Current	Transformer Primary RMS Current
9.	T1 Iprim pk	432.634 mA	Current	Transformer Primary Peak Current
10.	T1 Is1 RMS	3.693 A	Current	Transformer Secondary1 RMS Current
11.	T1 Is1 pk	7.38 A	Current	Transformer Secondary1 Peak Current
12.	BOM Count	47	General	Total Design BOM count
13.	Daux trr	4.0 ns	General	Auxiliary Diode Reverse Recovery Time
14.	Dsec Vf	850.0 mV	General	Effective Forward Voltage Drop at the Operating Current
15.	Dsec trr	0.0 ns	General	Output Diode Reverse Recovery Time
16.	Dsec2 Vf	397.923 mV	General	Effective Forward Voltage Drop at the Operating Current
17.	Dsnub trr	35.0 ns	General	Snubber Diode Reverse Recovery Time
18.	FootPrint	2.124 k mm ²	General	Total Foot Print Area of BOM components
19.	Frequency	223.958 kHz	General	Switching frequency
20.	Pout	24.0 W	General	Total output power
21.	Tdead	0.0 ns	General	Approximate Dead Time of the Regulator
22.	Toff	1.534 us	General	Approximate Converter Off Time
23.	Ton Act	2.71 us	General	Approximate Converter On Time
24.	Total BOM	\$0.0	General	Total BOM Cost
25.	Tsw	4.465 us	General	Switching Time Period
26.	Vaux	14.397 V	General	Auxiliary Voltage
27.	Vsnub	358.571 V	General	Voltage Across the Snubber
28.	Vout Actual	11.99 V	Op_Point	Vout Actual calculated based on selected voltage divider resistors
29.	Vout OP	12.0 V	Op_Point	Operational Output Voltage

#	Name	Value	Category	Description
30.	Duty Cycle	60.688 %	Op_point	Duty cycle
31.	Efficiency	90.345 %	Op_point	Steady state efficiency
32.	IC Tj	35.365 degC	Op_point	IC junction temperature
33.	ICThetaJA	50.0 degC/W	Op_point	IC junction-to-ambient thermal resistance
34.	IOUT_OP	2.0 A	Op_point	Iout operating point
35.	M1 TjOP	44.813 degC	Op_point	M1 MOSFET junction temperature
36.	Vout p-p	49.897 mV	Op_point	Peak-to-peak output ripple voltage
37.	Cin Pd	783.673 μ W	Power	Input capacitor power dissipation
38.	Cout1 Pd	154.203 mW	Power	Output capacitor1 power dissipation
39.	Dsec Pd	850.0 mW	Power	Secondary Diode Power Dissipation
40.	Dsec2 Pd	397.923 mW	Power	Secondary Diode Power Dissipation
41.	IC Pd	107.308 mW	Power	IC power dissipation
42.	L2 Pd	9.6 mW	Power	Average Power Dissipation in the Inductor Over the AC Line Period
43.	M1 Pd	237.014 mW	Power	M1 MOSFET total power dissipation
44.	Paux	22.446 mW	Power	Power Dissipation in Raux and Daux
45.	Pd Rstartup	168.888 mW	Power	Power Dissipation in Rstartup1 and Rstartup2
46.	Rdrv Pd	173.574 μ W	Power	Power Dissipation in Gate Drive Resistor
47.	Rfb Pd	8.324 mW	Power	Rfb Power Dissipation
48.	Rsns Pd	115.765 mW	Power	Current Limit Sense Resistor Power Dissipation
49.	Snubber Pd	516.321 mW	Power	Snubber Power Dissipation
50.	T1 Pd	360.463 mW	Power	Estimated Losses in Transformer
51.	Total Pd	0.0 W	Power	Total Power Dissipation
52.	Vout Tolerance	1.926 %		Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable
53.	Vout pp percentage	415.805 m%		Output Voltage ripple percentage

Design Inputs

#	Name	Value	Description
1.	Iout	2.0	Maximum Output Current
2.	VinMax	280.0	Maximum input voltage
3.	VinMin	150.0	Minimum input voltage
4.	Vout	12.0	Output Voltage
5.	base_pn	UCC38C42	Texas Instruments Base Part Number
6.	source	DC	Input Source Type
7.	ta	30.0	Ambient temperature

Design Assistance

1. UCC38C42 Product Folder : <http://www.ti.com/product/UCC38C42> : contains the data sheet and other resources.

Texas Instruments' WEBENCH simulation tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Simulations are created using Texas Instruments' published specifications as well as the published specifications of other device manufacturers. While Texas Instruments does update this information periodically, this information may not be current at the time the simulation is built. Texas Instruments does not warrant the accuracy or completeness of the specifications or any information contained therein. Texas Instruments does not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. Texas Instruments does not warrant that the designs are production worthy.

You should completely validate and test your design implementation to confirm the system functionality for your application prior to production.

Use of Texas Instruments' WEBENCH simulation tools is subject to [Texas Instruments' Site Terms and Conditions of Use](#). Prototype boards based on WEBENCH created designs are provided AS IS without warranty of any kind for evaluation and testing purposes and are subject to the terms of the [Evaluation License Agreement](#).