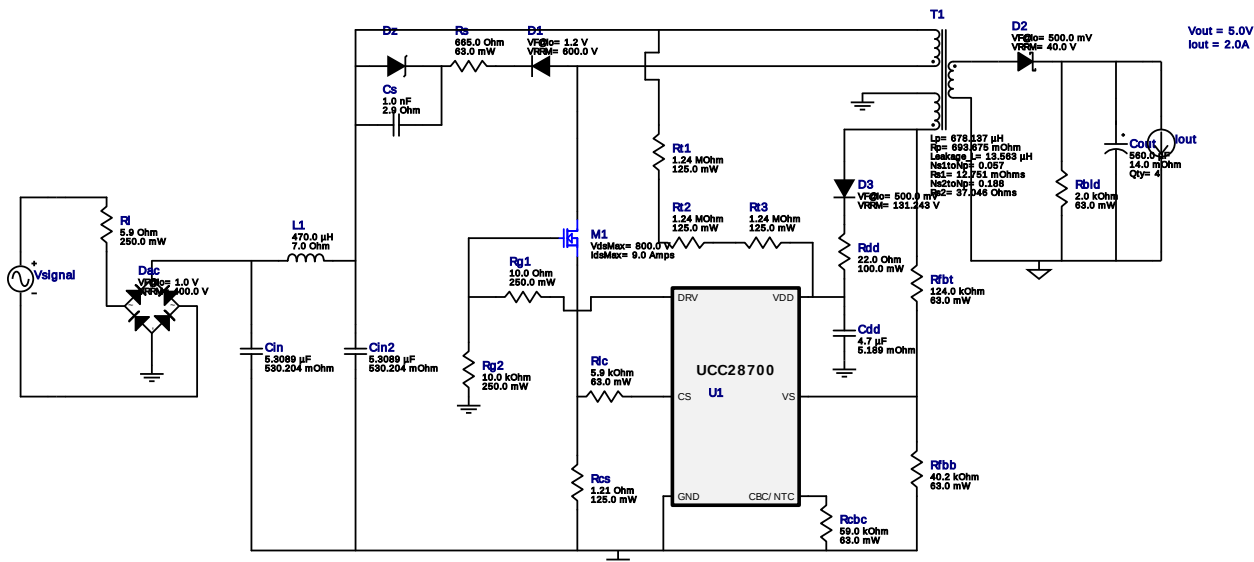


WEBENCH[®] Design Report

Design : 4737466/4 UCC28700DBVR
UCC28700DBVR 110.0V-130.0V to 5.11V @ 2.0A

VinMin = 110.0V
VinMax = 130.0V
Vout = 5.0V
Iout = 2.0A

Device = UCC28700DBVR
Topology = Flyback
Created = 7/12/16 12:13:17 AM
BOM Cost = \$0.00
BOM Count = 31
Total Pd = 2.06W







1. R_{ld} is a starting point, but may need to be experimented with in order to get minimum current needed to hold V_{out} at no load. R_{lc} and the feedback resistors may also need adjustment based on the actual transformer used. For more information please click the design assistance button.







Electrical BOM

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	Cdd	MuRata	GRM21BR61E475KA12L Series= X5R	Cap= 4.7 uF ESR= 5.189 mOhm VDC= 25.0 V IRMS= 2.03531 A	1	\$0.02	 0805 7 mm²
2.	Cin	CUSTOM	CUSTOM Series= ?	Cap= 5.3089 uF ESR= 530.2 mOhm VDC= 275.769 V IRMS= 423.78 mA	1	NA	CUSTOM 0 mm²
3.	Cin2	CUSTOM	CUSTOM Series= ?	Cap= 5.3089 uF ESR= 530.2 mOhm VDC= 275.769 V IRMS= 423.78 mA	1	NA	CUSTOM 0 mm²
4.	Cout	Panasonic	16SVPF560M Series= ?	Cap= 560.0 uF ESR= 14.0 mOhm VDC= 16.0 V IRMS= 4.95 A	4	\$0.61	 CAPSMT_62_E12 106 mm²
5.	Cs	MuRata	GRM188R72E102KW07D Series= X7R	Cap= 1.0 nF ESR= 2.9 Ohm VDC= 250.0 V IRMS= 90.0 mA	1	\$0.01	 0603 5 mm²
6.	D1	Bourns	CD214B-F3600	VF@lo= 1.2 V VRRM= 600.0 V	1	\$0.14	 SMB 44 mm²
7.	D2	Diodes Inc.	B340A-13-F	VF@lo= 500.0 mV VRRM= 40.0 V	1	\$0.11	 SMA 37 mm²
8.	D3	CUSTOM	CUSTOM	VF@lo= 500.0 mV VRRM= 131.243 V	1	NA	CUSTOM 0 mm²


#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
9.	Dac	Diodes Inc.	HD04-T	VF@Io= 1.0 V VRRM= 400.0 V	1	\$0.12	 MiniDIP 62 mm²
10.	Dz	ON Semiconductor	1SMB5951BT3G	Zener	1	\$0.10	 SMB 44 mm²
11.	L1	Bourns	SDR0403-471KL	L= 470.0 µH DCR= 7.0 Ohm	1	\$0.18	 SDR0403 28 mm²
12.	M1	STMicroelectronics	STF10N80K5	VdsMax= 800.0 V IdsMax= 9.0 Amps	1	\$2.52	 TO-220FP 79 mm²
13.	Rbld	Vishay-Dale	CRCW04022K00FKED Series= CRCW..e3	Res= 2.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm²
14.	Rcbc	Vishay-Dale	CRCW040259K0FKED Series= CRCW..e3	Res= 59.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm²
15.	Rcs	Vishay-Dale	CRCW08051R21FKEA Series= CRCW..e3	Res= 1.21 Ohm Power= 125.0 mW Tolerance= 1.0%	1	\$0.01	 0805 7 mm²
16.	Rdd	Yageo America	RC0603FR-0722RL Series= ?	Res= 22.0 Ohm Power= 100.0 mW Tolerance= 1.0%	1	\$0.01	 0603 5 mm²
17.	Rfbb	Vishay-Dale	CRCW040240K2FKED Series= CRCW..e3	Res= 40.2 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm²
18.	Rfbt	Vishay-Dale	CRCW0402124KFKED Series= CRCW..e3	Res= 124.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm²
19.	Rg1	Panasonic	ERJ-8ENF10R0V Series= ERJ-8E	Res= 10.0 Ohm Power= 250.0 mW Tolerance= 1.0%	1	\$0.01	 1206 11 mm²
20.	Rg2	Panasonic	ERJ-8ENF1002V Series= ERJ-8E	Res= 10.0 kOhm Power= 250.0 mW Tolerance= 1.0%	1	\$0.01	 1206 11 mm²
21.	RI	Vishay-Dale	CRCW12065R90FKEA Series= CRCW..e3	Res= 5.9 Ohm Power= 250.0 mW Tolerance= 1.0%	1	\$0.01	 1206 11 mm²
22.	Rlc	Vishay-Dale	CRCW04025K90FKED Series= CRCW..e3	Res= 5.9 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm²
23.	Rs	Vishay-Dale	CRCW0402665RFKED Series= CRCW..e3	Res= 665.0 Ohm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm²
24.	Rt1	Vishay-Dale	CRCW08051M24FKEA Series= CRCW..e3	Res= 1.24 MOhm Power= 125.0 mW Tolerance= 1.0%	1	\$0.01	 0805 7 mm²
25.	Rt2	Vishay-Dale	CRCW08051M24FKEA Series= CRCW..e3	Res= 1.24 MOhm Power= 125.0 mW Tolerance= 1.0%	1	\$0.01	 0805 7 mm²
26.	Rt3	Vishay-Dale	CRCW08051M24FKEA Series= CRCW..e3	Res= 1.24 MOhm Power= 125.0 mW Tolerance= 1.0%	1	\$0.01	 0805 7 mm²
27.	T1	CUSTOM	CUSTOM	Lp= 678.137 µH Rp= 693.675 mOhm Leakage_L= 13.563 µH Ns1toNp= 0.057 Rs1= 12.751 mOhms Ns2toNp= 0.188 Rs2= 37.046 Ohms	1	NA	CUSTOM 0 mm²

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
28.	U1	Texas Instruments	UCC28700DBVR	Switcher	1	\$0.35	 SOT-23-6 15 mm ²

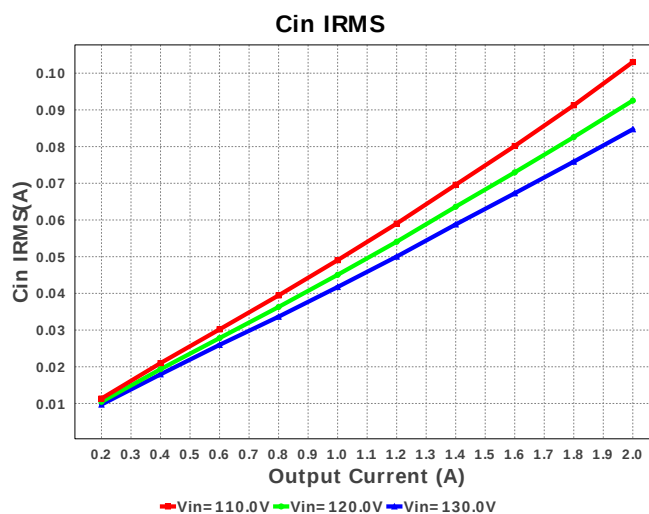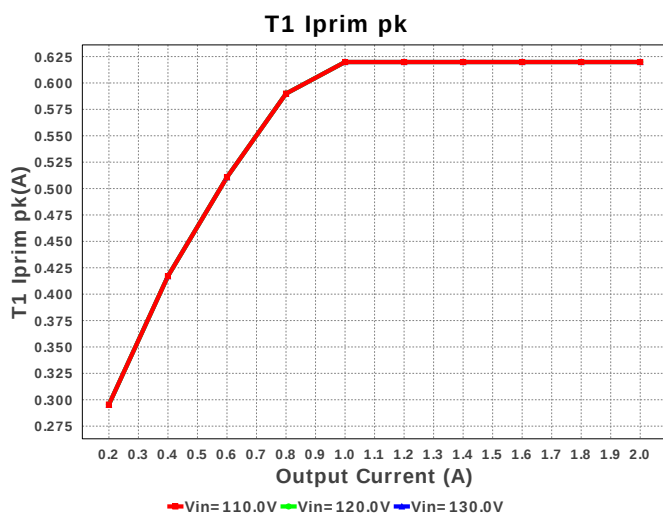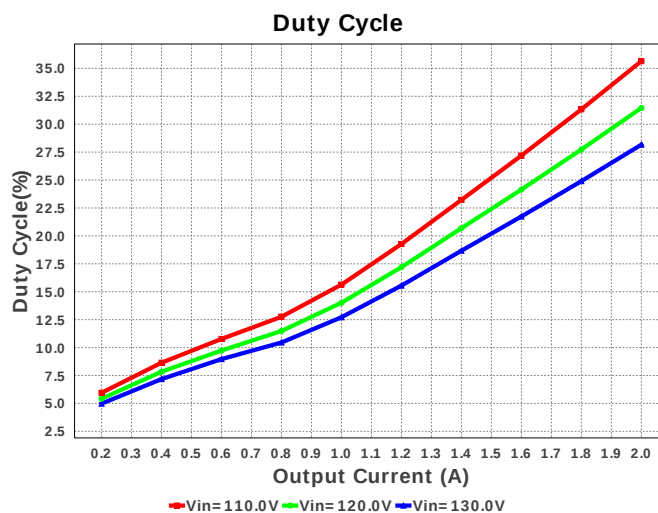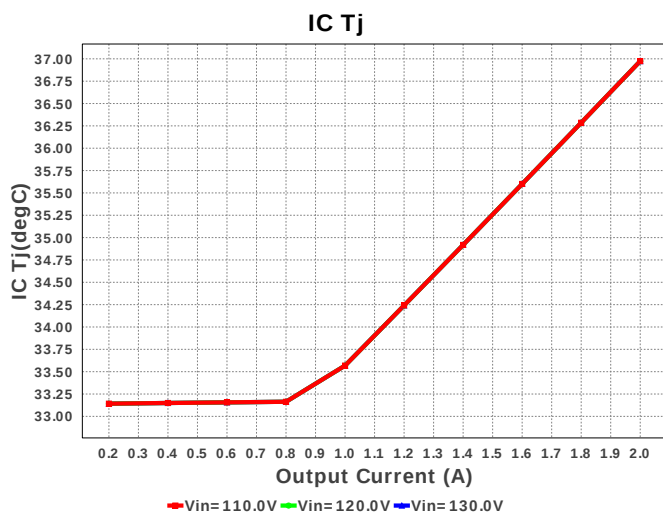


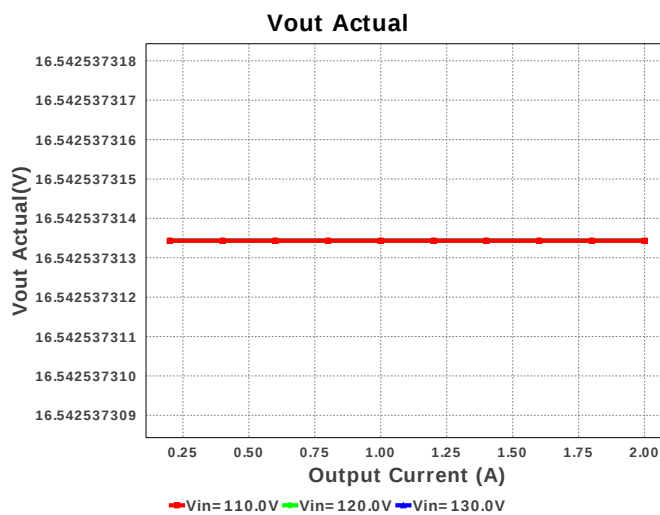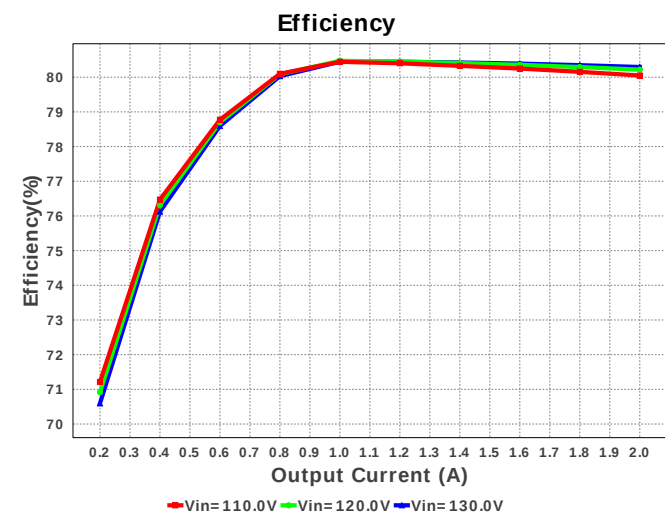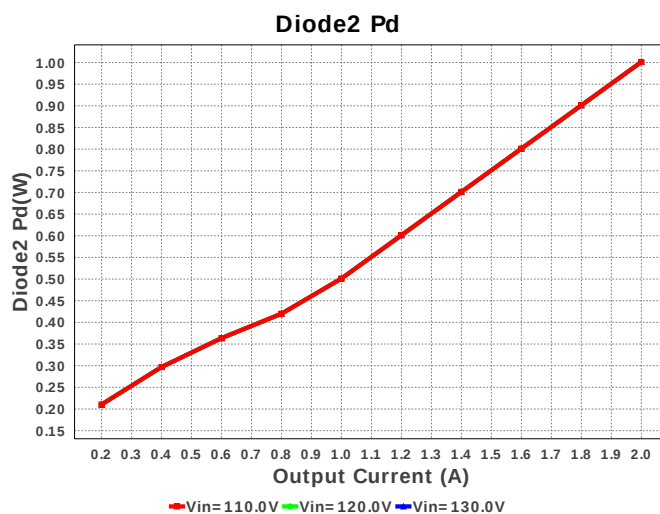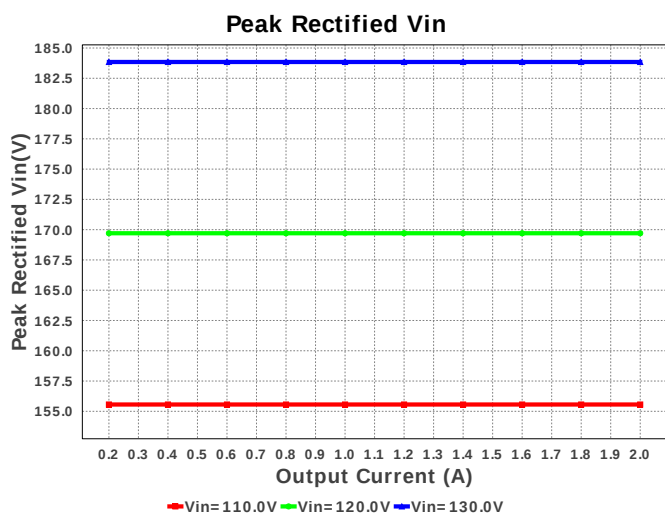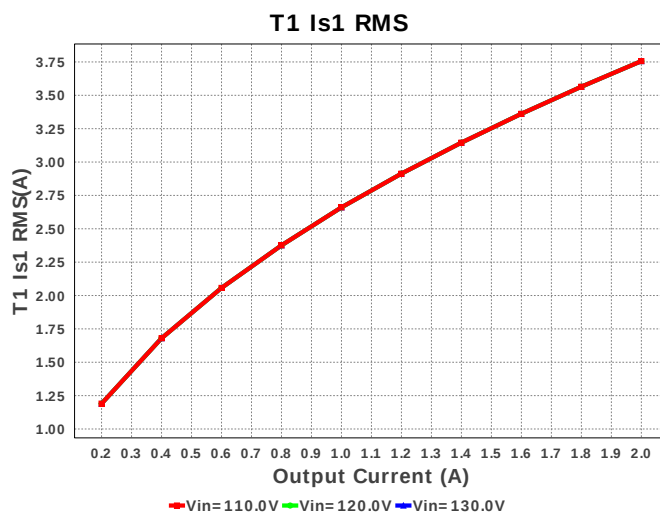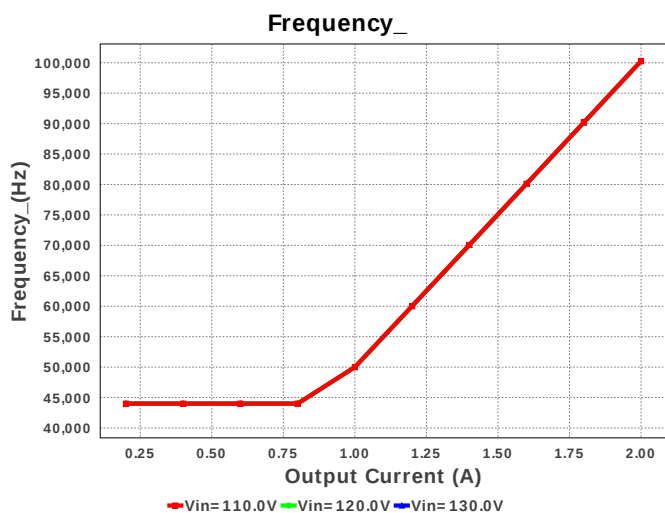


M1 TjOP

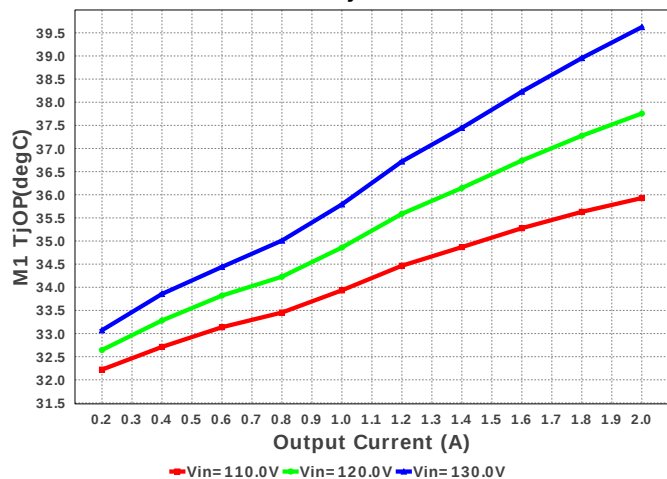


Cin2 IRMS

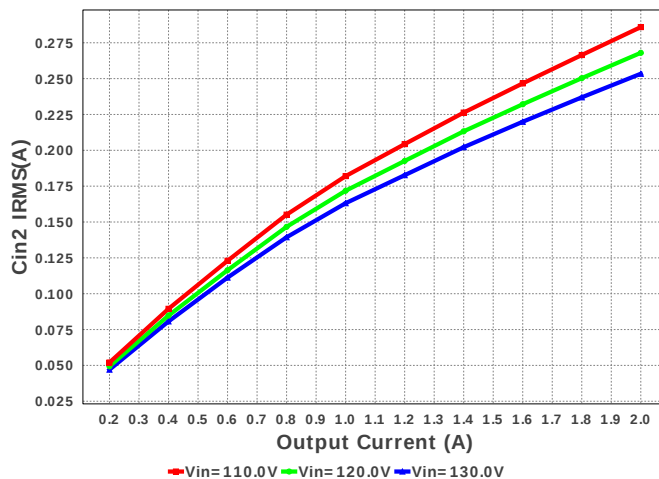


Vout p- p

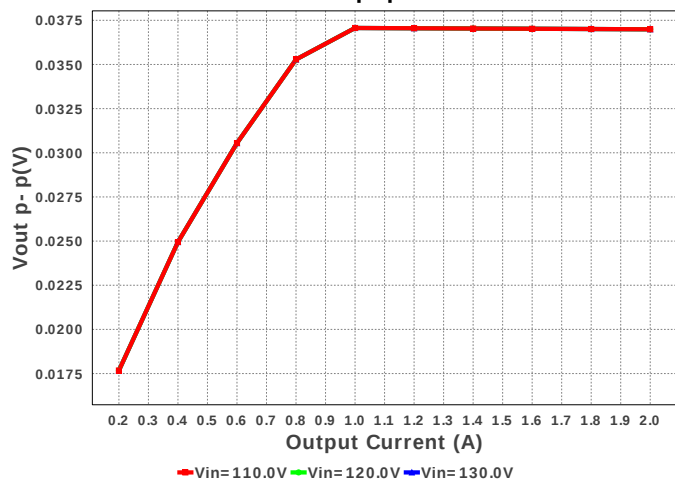


T1 Iprim RMS






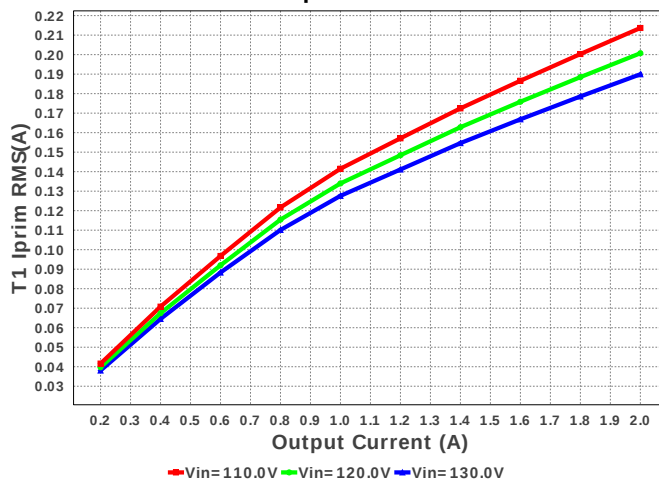



Zener Pd



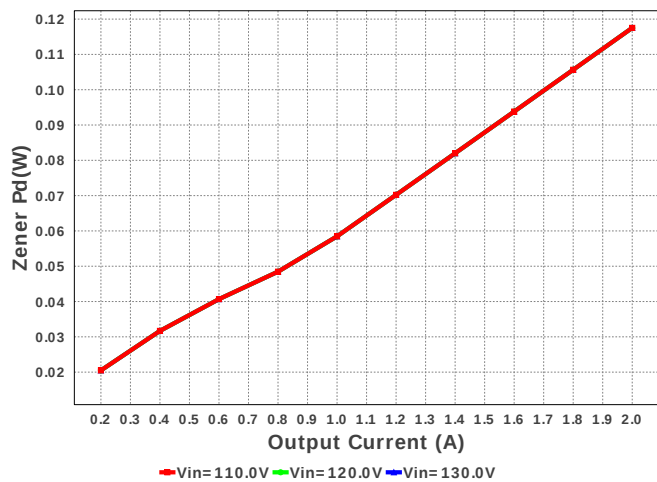


Iin rms

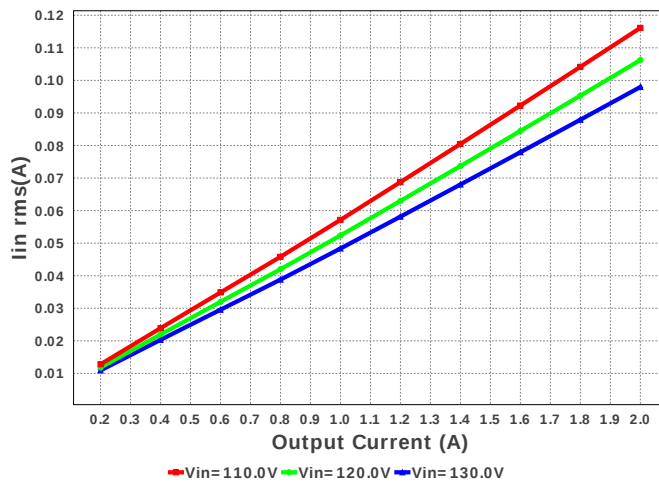

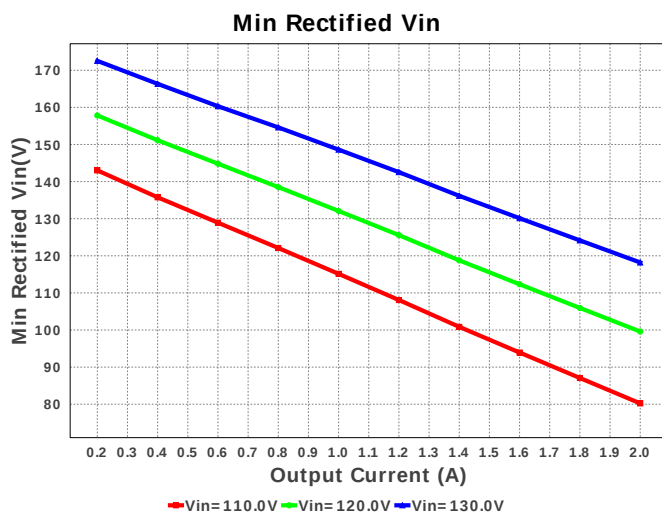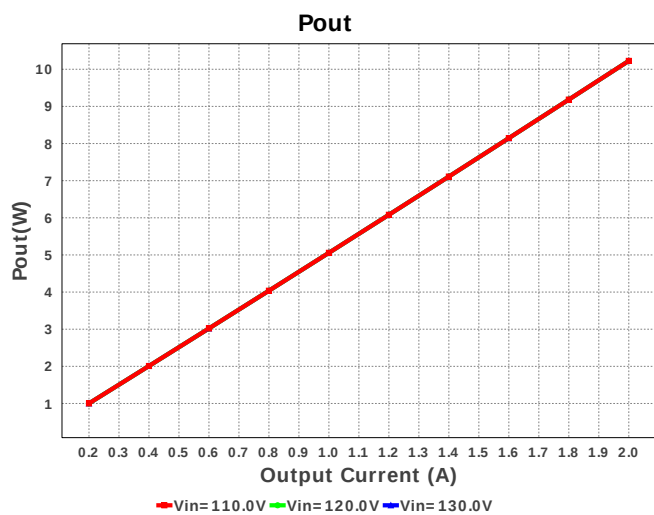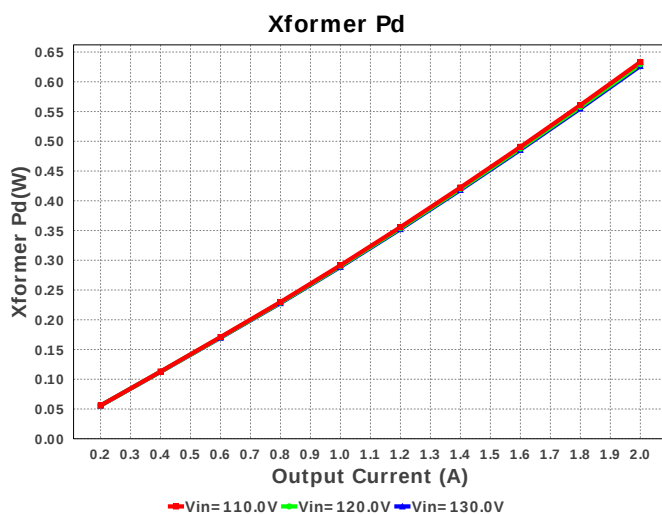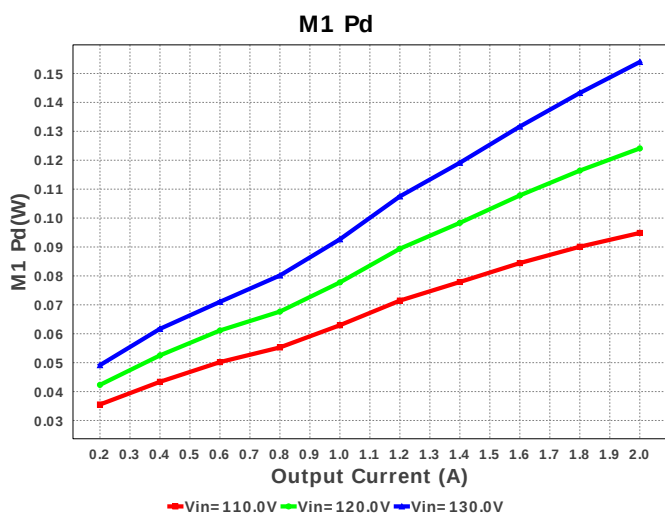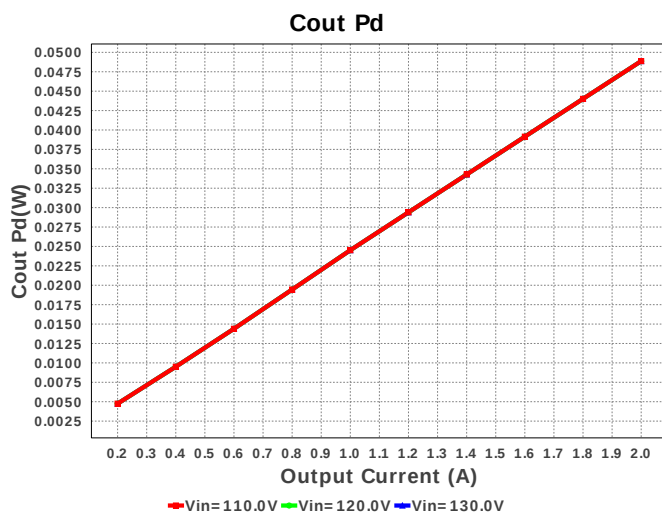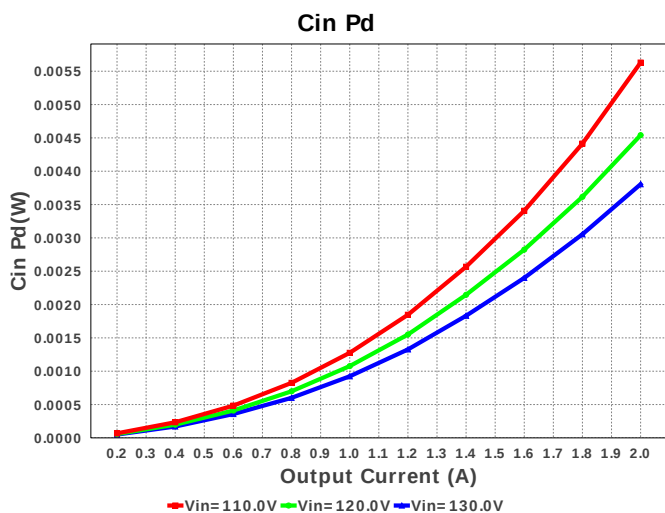

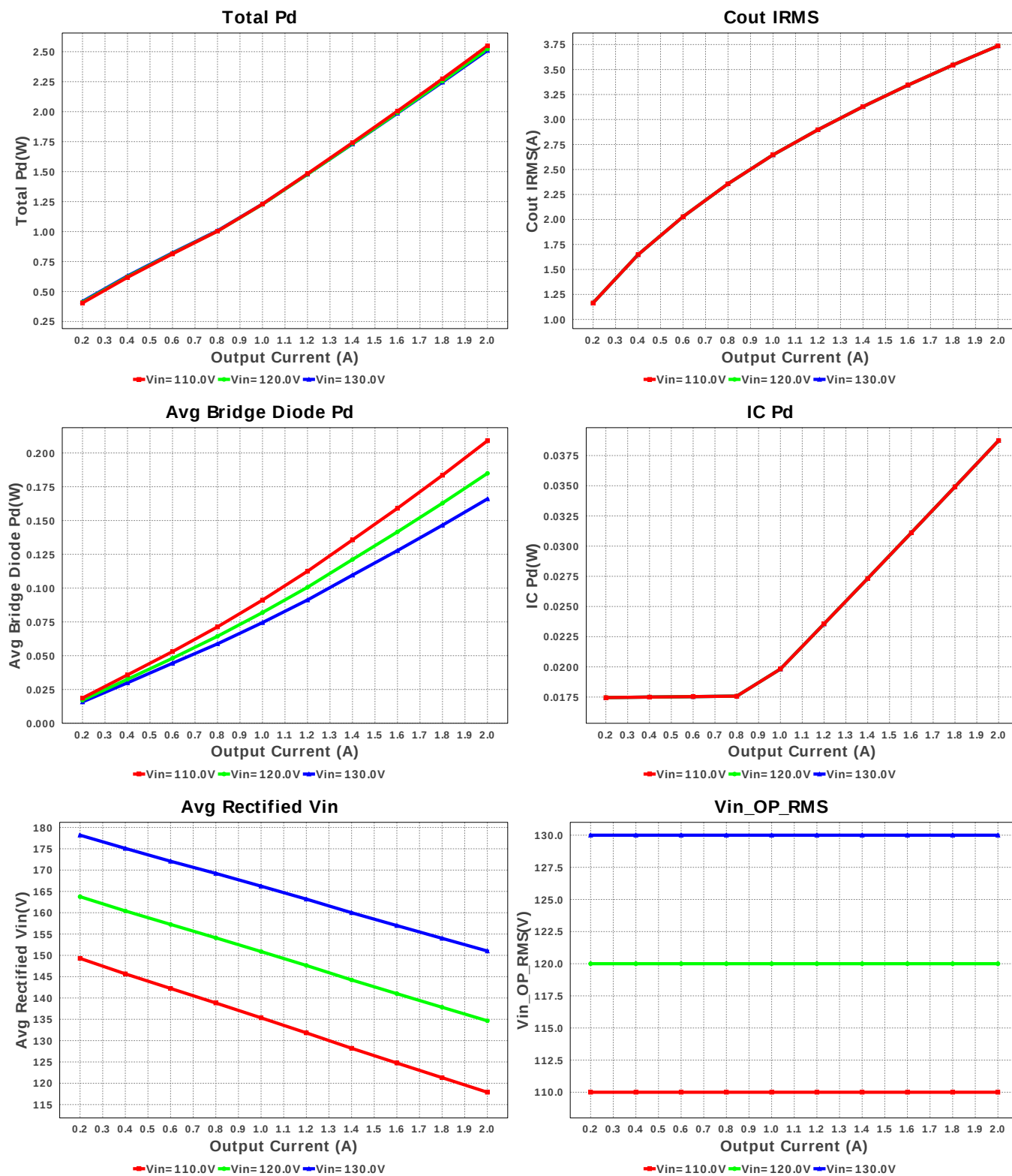

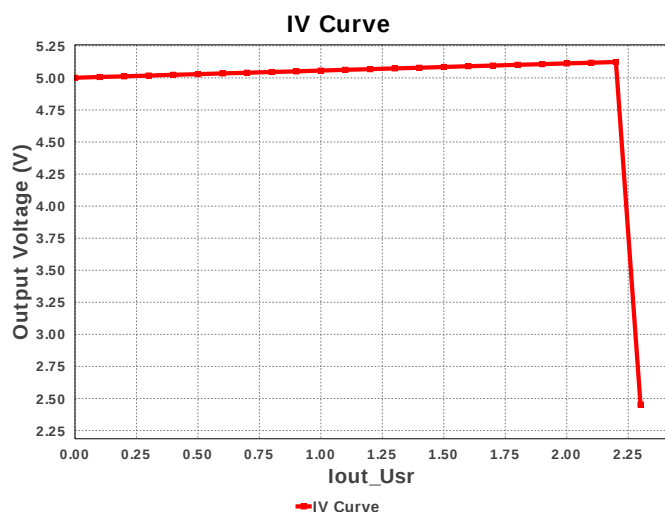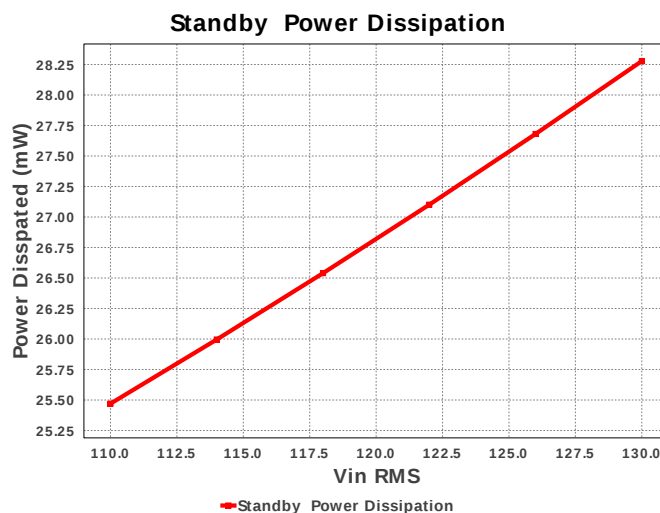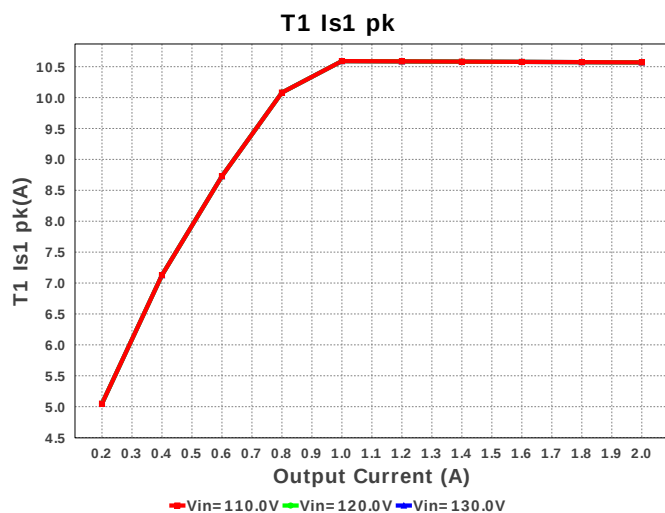

Operating Values

#	Name	Value	Category	Description
1.	Cin IRMS	81.772 mA	Current	Input capacitor RMS ripple current
2.	Cin2 IRMS	246.164 mA	Current	Input Capacitor Cin2 RMS Ripple Current
3.	Cout IRMS	3.752 A	Current	Output capacitor RMS ripple current
4.	Iin rms	94.515 mA	Current	RMS Input Current
5.	T1 Iprim RMS	183.466 mA	Current	Transformer Primary RMS Current
6.	T1 Iprim pk	619.835 mA	Current	Transformer Primary Peak Current
7.	T1 Is1 RMS	3.772 A	Current	Transformer Secondary1 RMS Current
8.	T1 Is1 pk	10.656 A	Current	Transformer Secondary1 Peak Current
9.	Avg Rectified Vin	157.333 V	General	Average Rectified Voltage for the AC Line Period
10.	BOM Count	31	General	Total Design BOM count
11.	FootPrint	1.001 k mm ²	General	Total Foot Print Area of BOM components
12.	Pout	10.226 W	General	Total output power
13.	Total BOM	\$0.0	General	Total BOM Cost
14.	Vout Actual	16.543 V	Op_Point	Vout Actual calculated based on selected voltage divider resistors
15.	Vout OP	5.113 V	Op_Point	Operational Output Voltage
16.	Duty Cycle	26.283 %	Op_point	Duty cycle
17.	Efficiency	83.227 %	Op_point	Steady state efficiency
18.	Frequency_	97.077 kHz	Op_point	Switching frequency
19.	IC Tj	32.629 degC	Op_point	IC junction temperature
20.	ICThetaJA	70.0 degC/W	Op_point	IC junction-to-ambient thermal resistance
21.	IOUT_OP	2.0 A	Op_point	Iout operating point
22.	M1 TJOP	40.152 degC	Op_point	M1 MOSFET junction temperature
23.	Min Rectified Vin	130.821 V	Op_point	Minimum voltage seen at rectified input
24.	Peak Rectified Vin	183.846 V	Op_point	Peak voltage seen at rectified input
25.	Vin_OP_RMS	130.0 V	Op_point	AC Input RMS Voltage
26.	Vout p-p	37.297 mV	Op_point	Peak-to-peak output ripple voltage
27.	Avg Bridge Diode Pd	109.409 mW	Power	Average Power Dissipation in the Bridge Diode over the AC Line Period
28.	Cin Pd	3.545 mW	Power	Input capacitor power dissipation
29.	Cout Pd	49.276 mW	Power	Output capacitor power dissipation
30.	Diode2 Pd	822.579 mW	Power	Diode2 power dissipation
31.	IC Pd	37.557 mW	Power	IC power dissipation

#	Name	Value	Category	Description
32.	M1 Pd	162.427 mW	Power	M1 MOSFET total power dissipation
33.	Total Pd	2.061 W	Power	Total Power Dissipation
34.	Xformer Pd	616.997 mW	Power	Transformer power dissipation
35.	Zener Pd	31.175 mW	Power	Zener power dissipation
36.	Vout Tolerance	1.726 %		Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable

Design Inputs

#	Name	Value	Description
1.	Iout	2.0	Maximum Output Current
2.	VinMax	130.0	Maximum input voltage
3.	VinMin	110.0	Minimum input voltage
4.	Vout	5.0	Output Voltage
5.	acFrequency	60.0	Light Output in Lumen
6.	base_pn	UCC28700	Texas Instruments Base Part Number
7.	source	AC	Input Source Type
8.	ta	30.0	Ambient temperature

Design Assistance

1. Application Hints Rbld Rbld is used to set a minimum load for the circuit, so that in standby the output voltage does not float up. The value chosen by WEBENCH should be a good starting point but may need to be adjusted to achieve minimum power dissipation at standby as well. Rlc Rlc provides the function of feed-forward line compensation to eliminate change in IPP due to change in di/dt and the propagation delay of the internal comparator and MOSFET turn-off time. For best results the chosen value may need to be adjusted based on board, FET and transformer parasitics. Rfbt & Rfbb The feedback resistors will set the output voltage of the circuit. The values chosen may need to be fine tuned based on the final Transformer turns ratios and the voltage across the output diode at close to zero current. Cdd Cdd supplies the device operating current until the output of the converter reaches the target minimum operating voltage. The value calculated by WEBENCH for Cdd is a good starting point since it assumes that the output current of the Flyback is available to charge the output capacitance until the minimum output voltage is achieved, but may need to be adjusted. Part Description The UCC28700 family of flyback power supply controllers provides Constant-Voltage (CV) and Constant-Current (CC) output regulation. Primary-Side Regulation (PSR) eliminates the use of an Opto-Coupler. Please see the datasheet for further design guidance. <http://www.ti.com/lit/ds/symlink/ucc28700.pdf>

2. UCC28700 Product Folder : <http://www.ti.com/product/UCC28700> : contains the data sheet and other resources.

Texas Instruments' WEBENCH simulation tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Simulations are created using Texas Instruments' published specifications as well as the published specifications of other device manufacturers. While Texas Instruments does update this information periodically, this information may not be current at the time the simulation is built. Texas Instruments does not warrant the accuracy or completeness of the specifications or any information contained therein. Texas Instruments does not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. Texas Instruments does not warrant that the designs are production worthy.

You should completely validate and test your design implementation to confirm the system functionality for your application prior to production.

Use of Texas Instruments' WEBENCH simulation tools is subject to [Texas Instruments' Site Terms and Conditions of Use](#). Prototype boards based on WEBENCH created designs are provided AS IS without warranty of any kind for evaluation and testing purposes and are subject to the terms of the [Evaluation License Agreement](#).