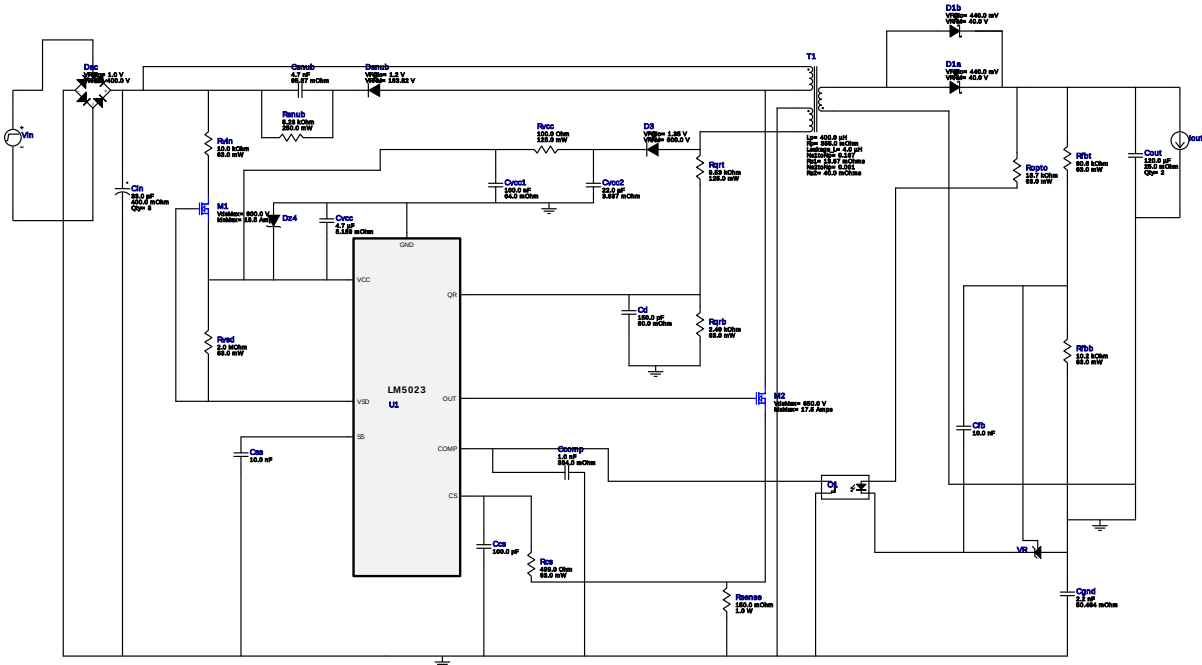


WEBENCH® Design Report

Design : 4737466/26 LM5023MM-2/NOPB
LM5023MM-2/NOPB 110.0V-130.0V to 22.21V @ 5.0A






1. Rbld is a starting point, but may need to be experimented with in order to get minimum current needed to hold Vout at no load. Rlc and the feedback resistors may also need adjustment based on the actual transformer used. For more information please click the design assistance button.







Electrical BOM







#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	Ccomp	Kemet	C0805C102K5RACTU Series= X7R	Cap= 1.0 nF ESR= 384.0 mOhm VDC= 50.0 V IRMS= 214.0 mA	1	\$0.01	0805 7 mm ²
2.	Ccs	Kemet	C0201C101K3GACTU Series= C0G/NP0	Cap= 100.0 pF VDC= 10.0 V IRMS= 0.0 A	1	\$0.01	0201 2 mm ²
3.	Cd	Kemet	C0805C151J5GACTU Series= C0G/NP0	Cap= 150.0 pF ESR= 60.0 mOhm VDC= 50.0 V IRMS= 676.0 mA	1	\$0.01	0805 7 mm ²
4.	Cfb	MuRata	GRM155R71E103KA01D Series= X7R	Cap= 10.0 nF VDC= 25.0 V IRMS= 0.0 A	1	\$0.01	0402 3 mm ²
5.	Cgnd	TDK	C3225X7S3D222K Series= X7S	Cap= 2.2 nF ESR= 50.484 mOhm VDC= 2.0 kV IRMS= 0.0 A	1	\$0.22	1210 15 mm ²
6.	Cin	Rubycon	200RX3033M10X20 Series= ?	Cap= 33.0 µF ESR= 400.0 mOhm VDC= 200.0 V IRMS= 320.0 mA	3	\$0.28	RX30_1000x2000 144 mm ²







#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
7.	Cout	Panasonic	20SVPF120M Series= ?	Cap= 120.0 uF ESR= 25.0 mOhm VDC= 20.0 V IRMS= 3.2 A	2	\$0.43	 CAPSMT_62_F61 74 mm ²
8.	Csnub	TDK	C3216X5R2J472K Series= X5R	Cap= 4.7 nF ESR= 95.87 mOhm VDC= 630.0 V IRMS= 0.0 A	1	\$0.03	 1206 11 mm ²
9.	Css	MuRata	GRM155R71E103KA01D Series= X7R	Cap= 10.0 nF VDC= 25.0 V IRMS= 0.0 A	1	\$0.01	 0402 3 mm ²
10.	Cvcc	MuRata	GRM21BR61E475KA12L Series= X5R	Cap= 4.7 uF ESR= 5.189 mOhm VDC= 25.0 V IRMS= 2.03531 A	1	\$0.02	 0805 7 mm ²
11.	Cvcc1	Kemet	C0805C104K5RACTU Series= X7R	Cap= 100.0 nF ESR= 64.0 mOhm VDC= 50.0 V IRMS= 1.64 A	1	\$0.01	 0805 7 mm ²
12.	Cvcc2	MuRata	GRM31CR61C226ME15L Series= X5R	Cap= 22.0 uF ESR= 3.637 mOhm VDC= 16.0 V IRMS= 3.4771 A	1	\$0.13	 1206_190 11 mm ²
13.	D1a	Vishay-Semiconductor	SL44-E3/57T	VF@Io= 440.0 mV VRRM= 40.0 V	1	\$0.32	 SMC 83 mm ²
14.	D1b	Vishay-Semiconductor	SL44-E3/57T	VF@Io= 440.0 mV VRRM= 40.0 V	1	\$0.32	 SMC 83 mm ²
15.	D3	Micro Commercial Components	ES1J-TP	VF@Io= 1.35 V VRRM= 600.0 V	1	\$0.08	 SMA 37 mm ²
16.	Dac	Diodes Inc.	HD04-T	VF@Io= 1.0 V VRRM= 400.0 V	1	\$0.12	 MiniDIP 62 mm ²
17.	Dsnub	CUSTOM	CUSTOM	VF@Io= 1.2 V VRRM= 183.82 V	1	NA	CUSTOM 0 mm ²
18.	Dz4	NXP Semiconductor	BZX585-C22,115	Zener	1	\$0.02	 SOD-523 5 mm ²
19.	M1	STMicroelectronics	STW21N90K5	VdsMax= 900.0 V IdsMax= 18.5 Amps	1	\$3.94	 TO-247 123 mm ²
20.	M2	Infineon Technologies	IPP65R190CFD	VdsMax= 650.0 V IdsMax= 17.5 Amps	1	\$2.34	TO-220 0 mm ²
21.	O1	California Eastern Laboratories	PS2811-1	Optocoupler	1	\$0.38	 SSOP-4 111 mm ²
22.	Rcs	Vishay-Dale	CRCW0402499RFKED Series= CRCW..e3	Res= 499.0 Ohm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
23.	Rfbb	Vishay-Dale	CRCW040210K2FKED Series= CRCW..e3	Res= 10.2 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
24.	Rfbt	Vishay-Dale	CRCW040280K6FKED Series= CRCW..e3	Res= 80.6 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
25.	Ropto	Vishay-Dale	CRCW040218K7FKED Series= CRCW..e3	Res= 18.7 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²






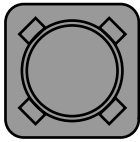
#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
26.	Rqrb	Vishay-Dale	CRCW04022K49FKED Series= CRCW..e3	Res= 2.49 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm²
27.	Rqrt	Panasonic	ERJ-6ENF9531V Series= ERJ-6E	Res= 9.53 kOhm Power= 125.0 mW Tolerance= 1.0%	1	\$0.01	 0805 7 mm²
28.	Rsense	Stackpole Electronics Inc	CSRN2010FKR150 Series= ?	Res= 150.0 mOhm Power= 1.0 W Tolerance= 1.0%	1	\$0.11	 2010 32 mm²
29.	Rsnuv	Panasonic	ERJ-8ENF5231V Series= ERJ-8E	Res= 5.23 kOhm Power= 250.0 mW Tolerance= 1.0%	1	\$0.01	 1206 11 mm²
30.	Rvcc	Vishay-Dale	CRCW0805100RFKEA Series= CRCW..e3	Res= 100.0 Ohm Power= 125.0 mW Tolerance= 1.0%	1	\$0.01	 0805 7 mm²
31.	Rvin	Vishay-Dale	CRCW040210K0FKED Series= CRCW..e3	Res= 10.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm²
32.	Rvsd	Vishay-Dale	CRCW04022M00FKED Series= CRCW..e3	Res= 2.0 MOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm²
33.	T1	Würth Elektronik	750313417	Lp= 400.0 µH Rp= 355.0 mOhm Leakage_L= 4.0 µH Ns1toNp= 0.167 Rs1= 13.67 mOhms Ns2toNp= 0.091 Rs2= 40.0 mOhms	1	NA	 WE-DD-L 210 mm²
34.	U1	Texas Instruments	LM5023MM-2/NOPB	Switcher	1	\$0.38	 MUA08A 24 mm²
35.	VR	Texas Instruments	TL431AIDBVR	Voltage References	1	\$0.07	 R-PDSO-G3 16 mm²

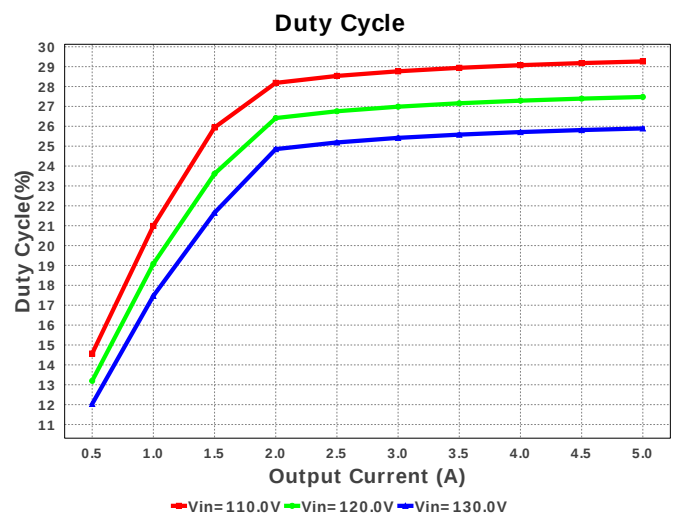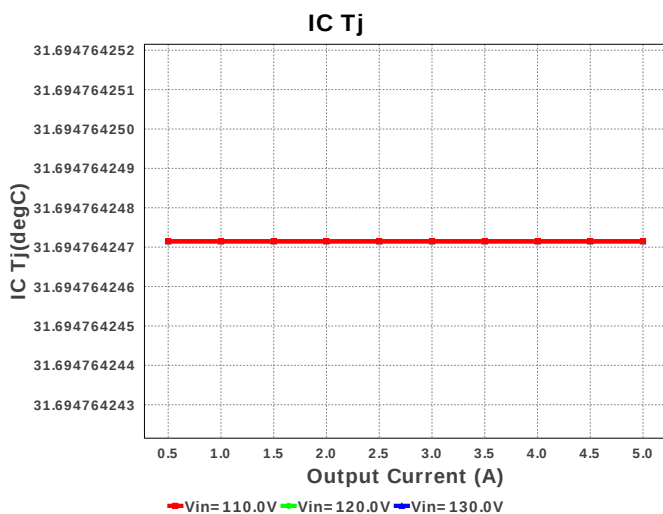


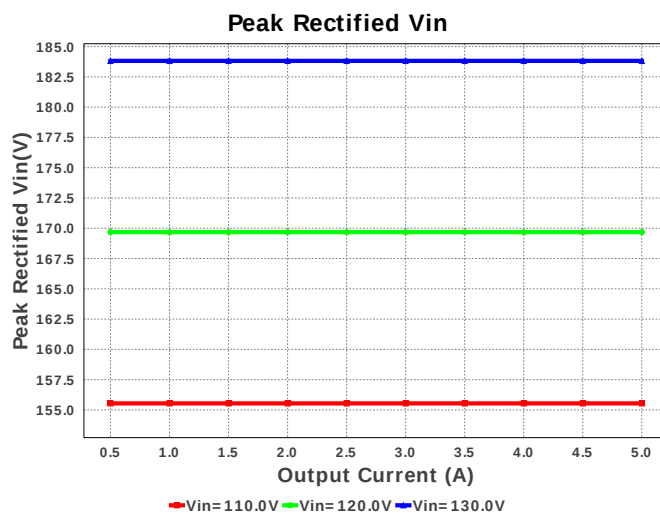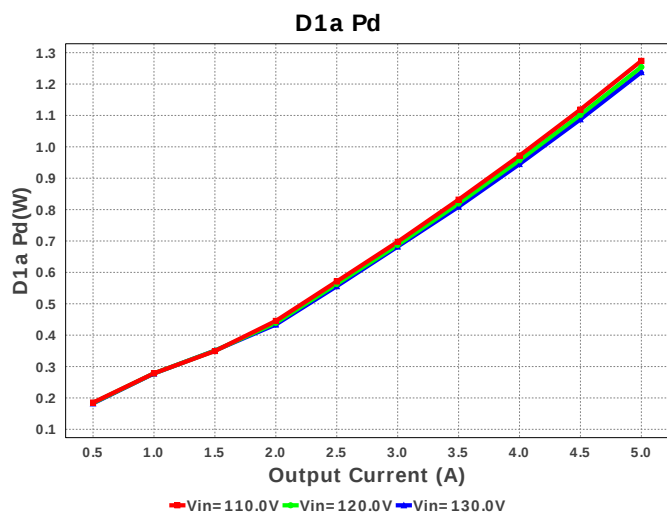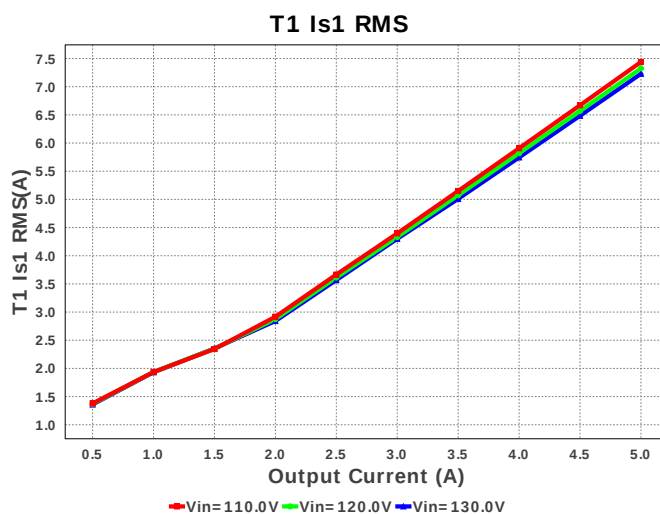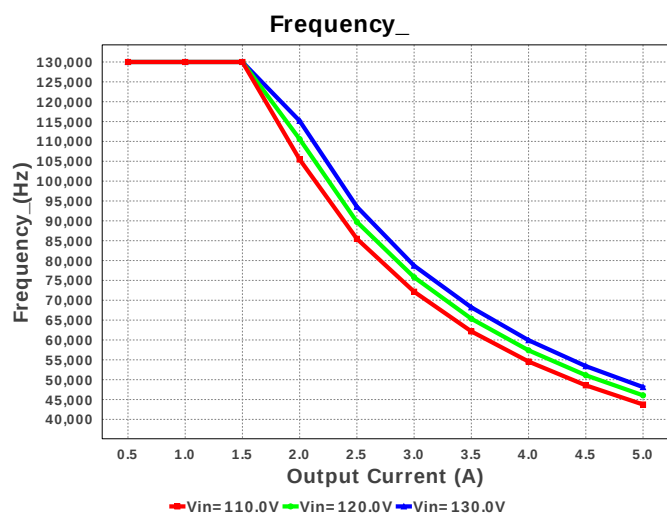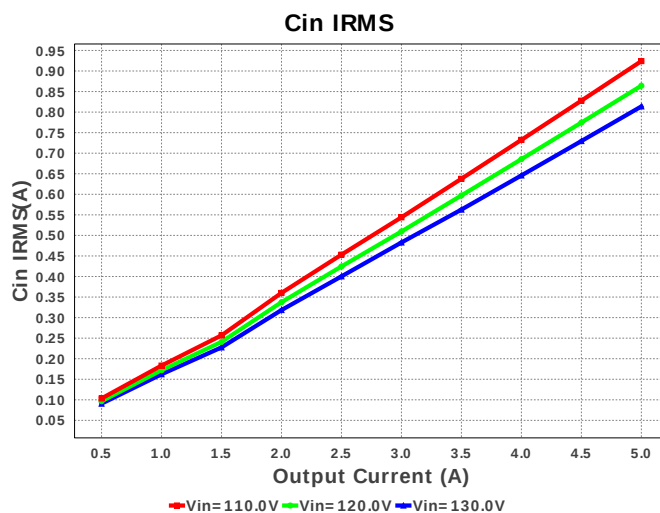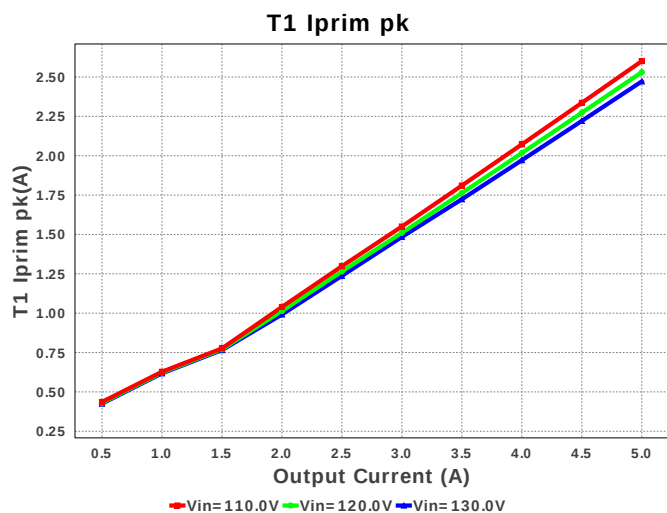

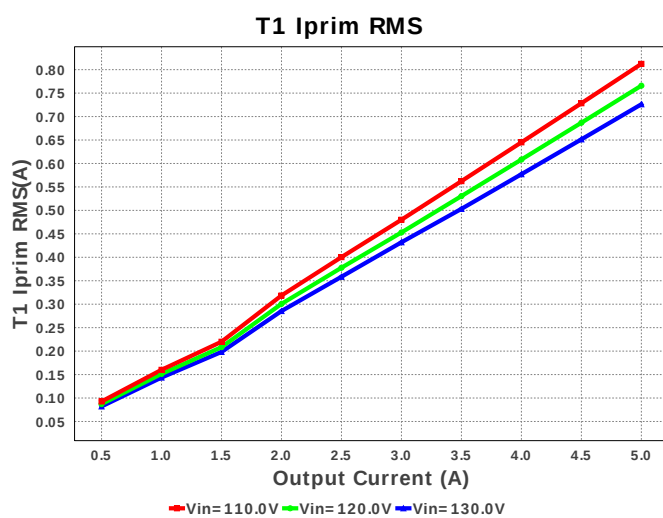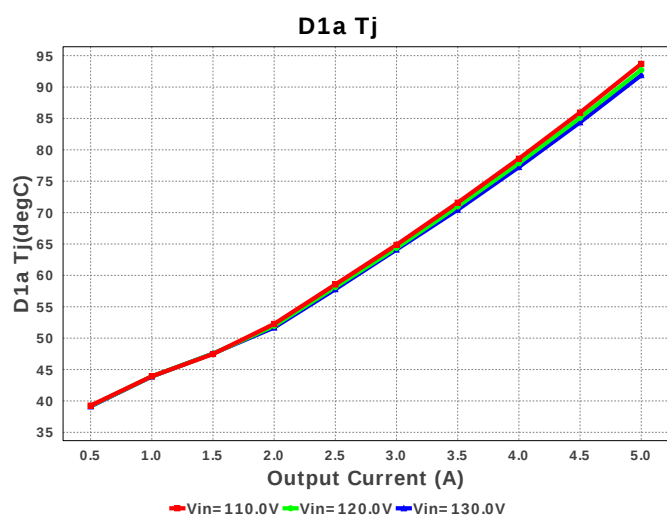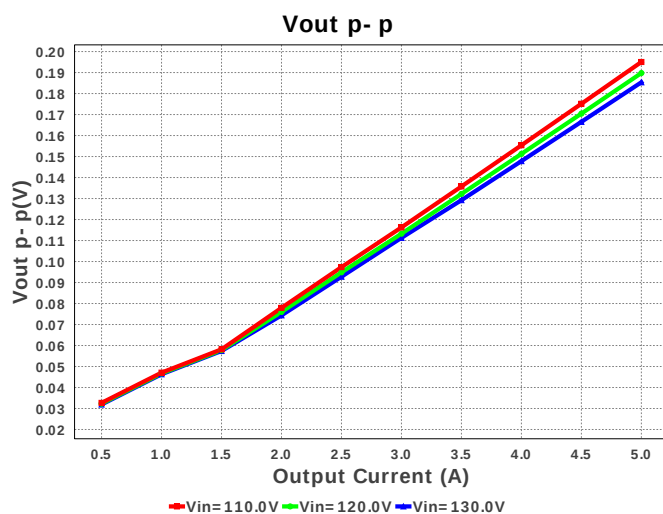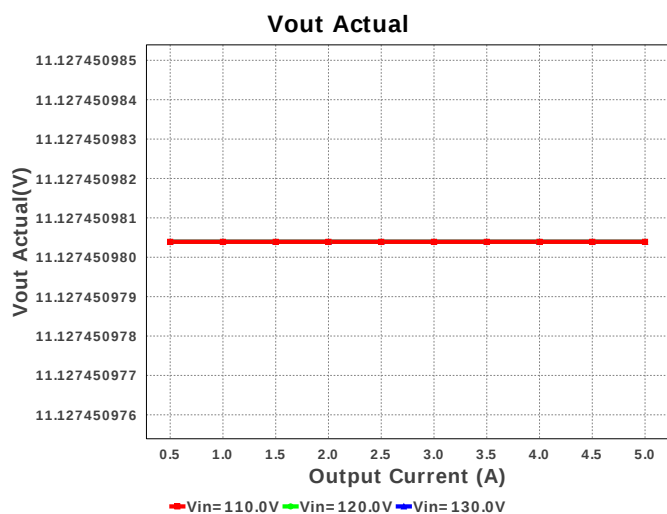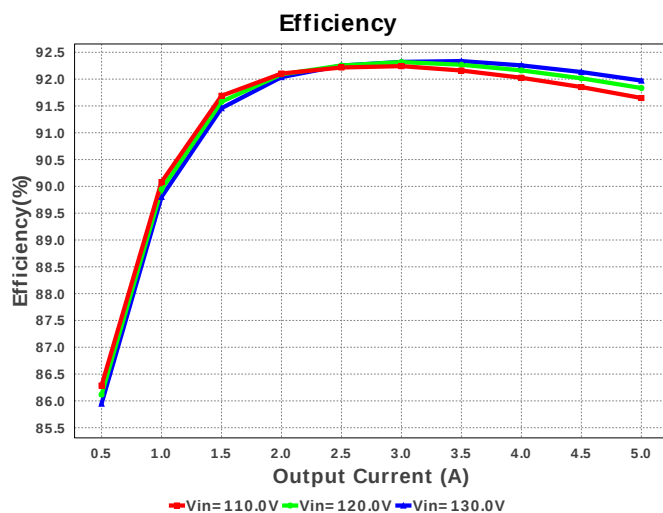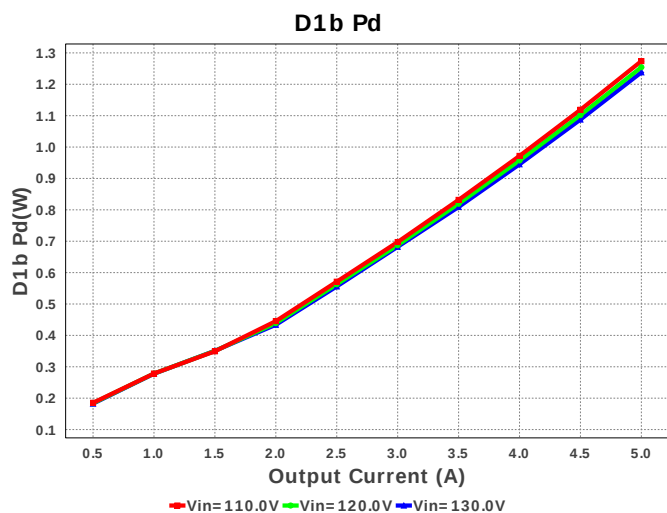

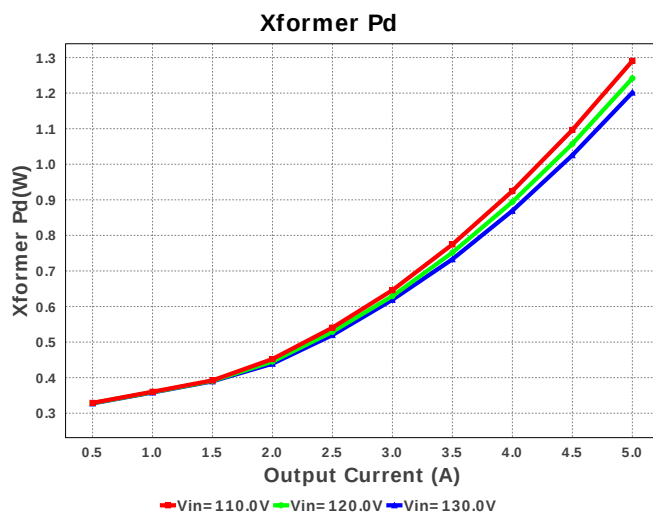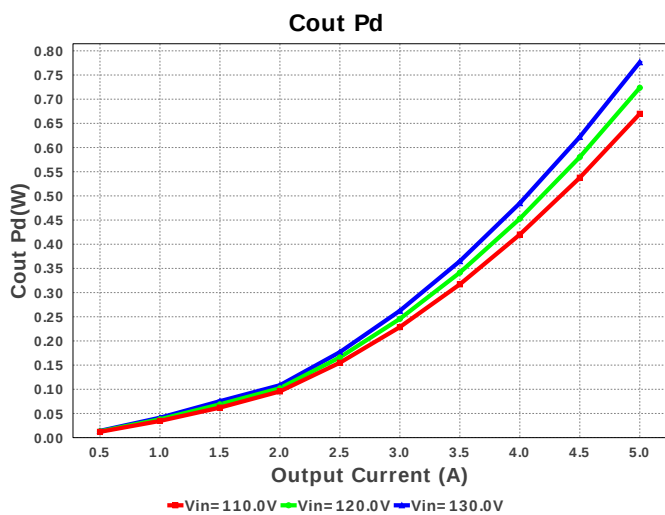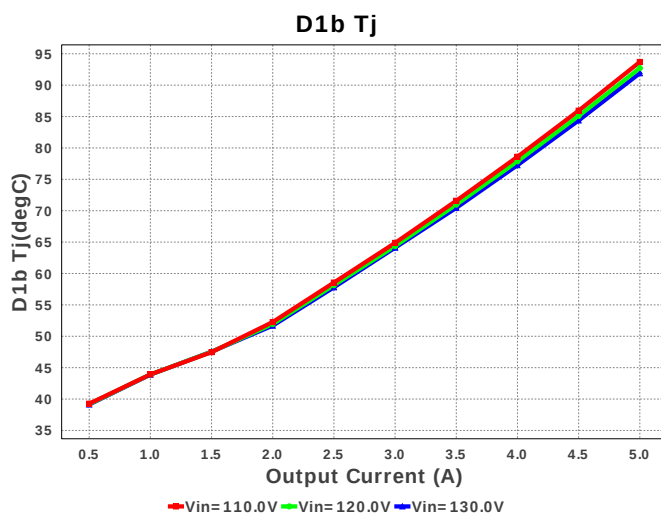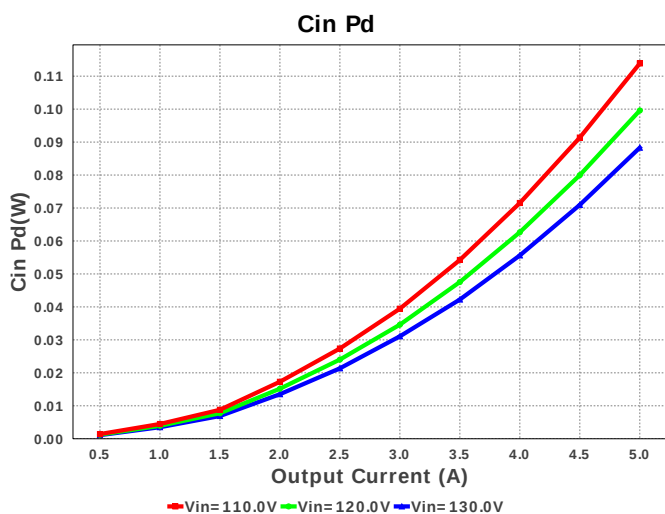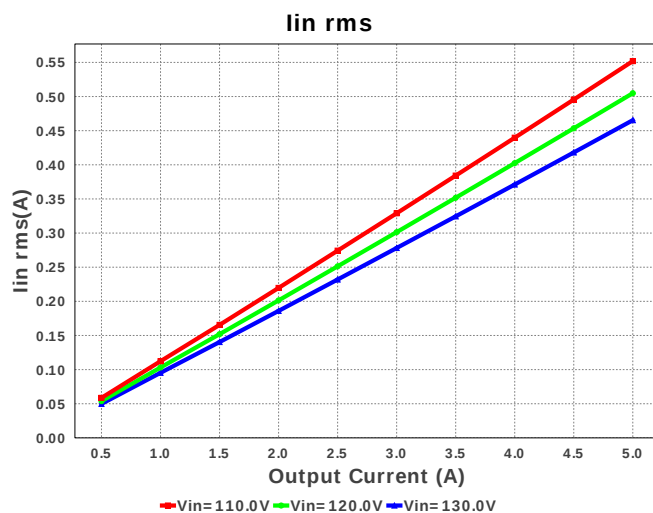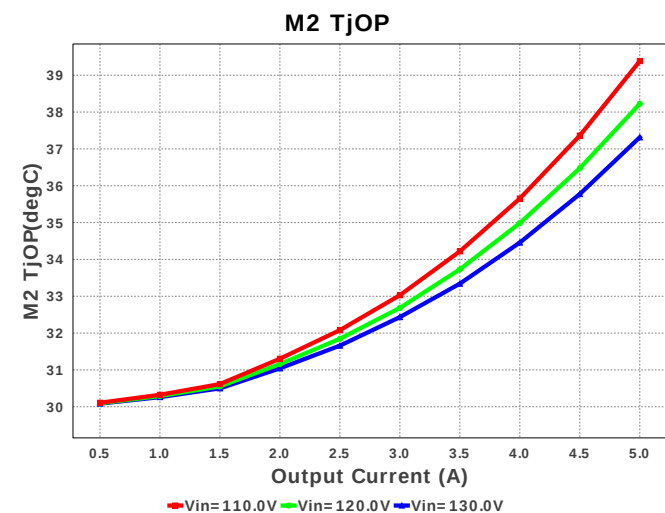

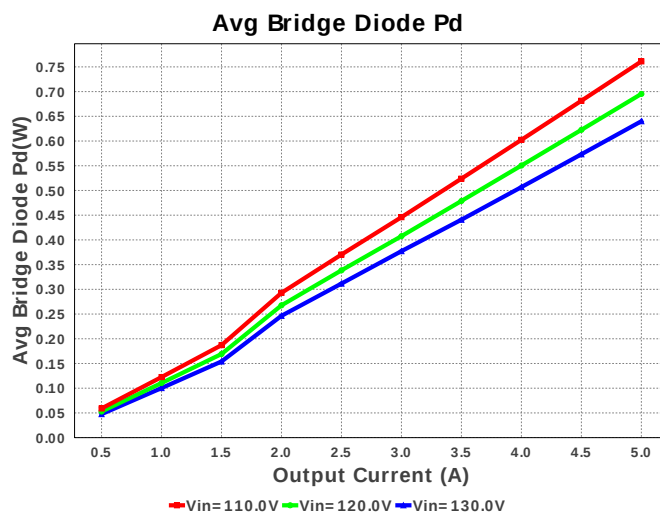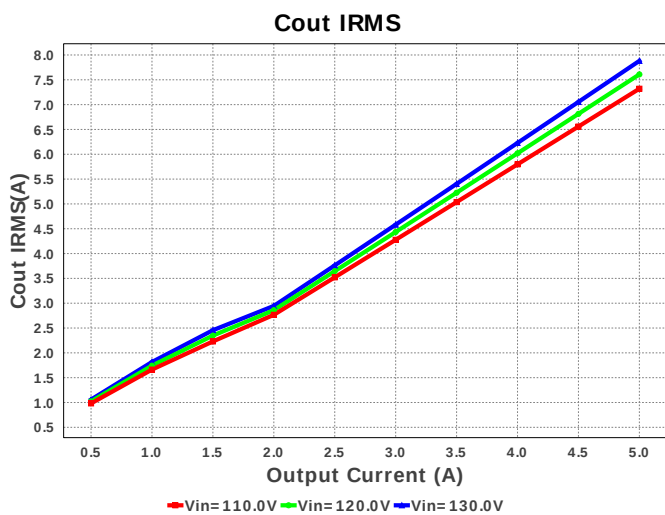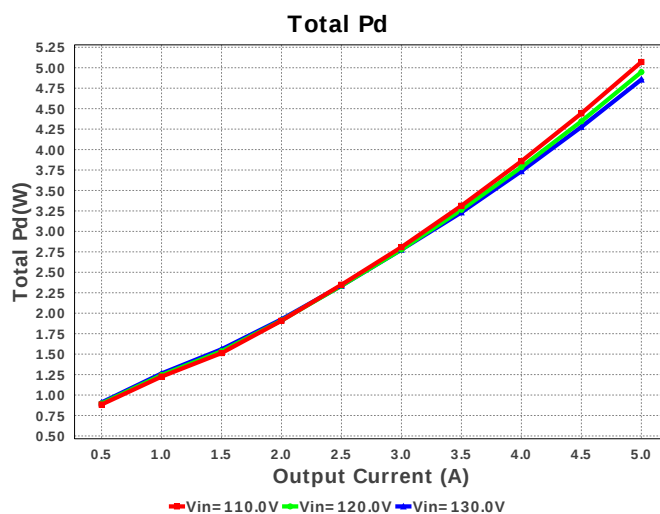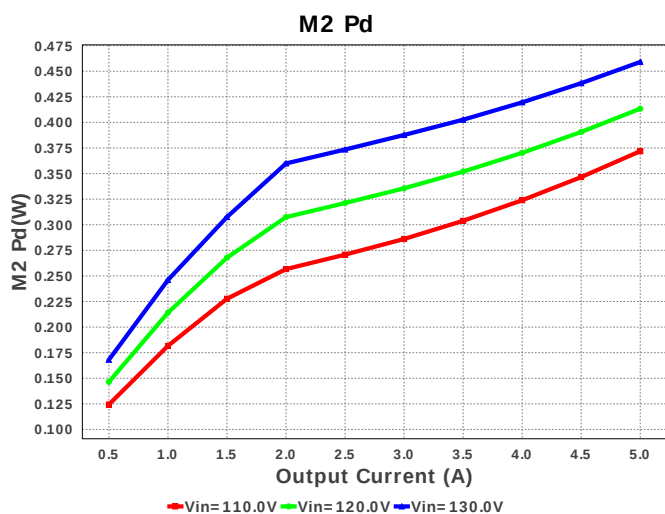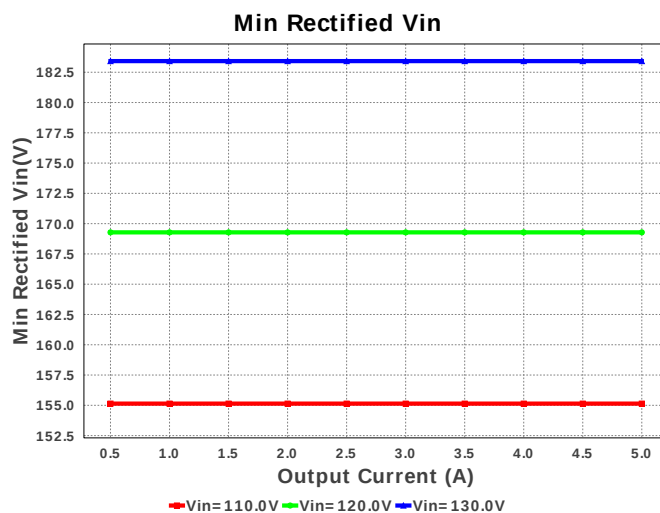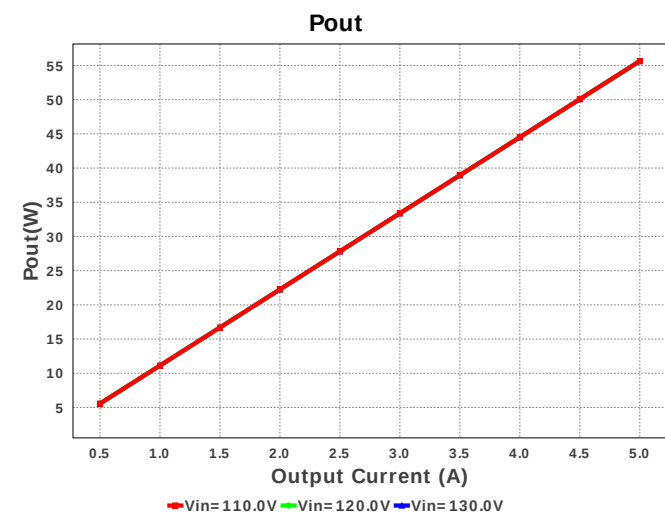

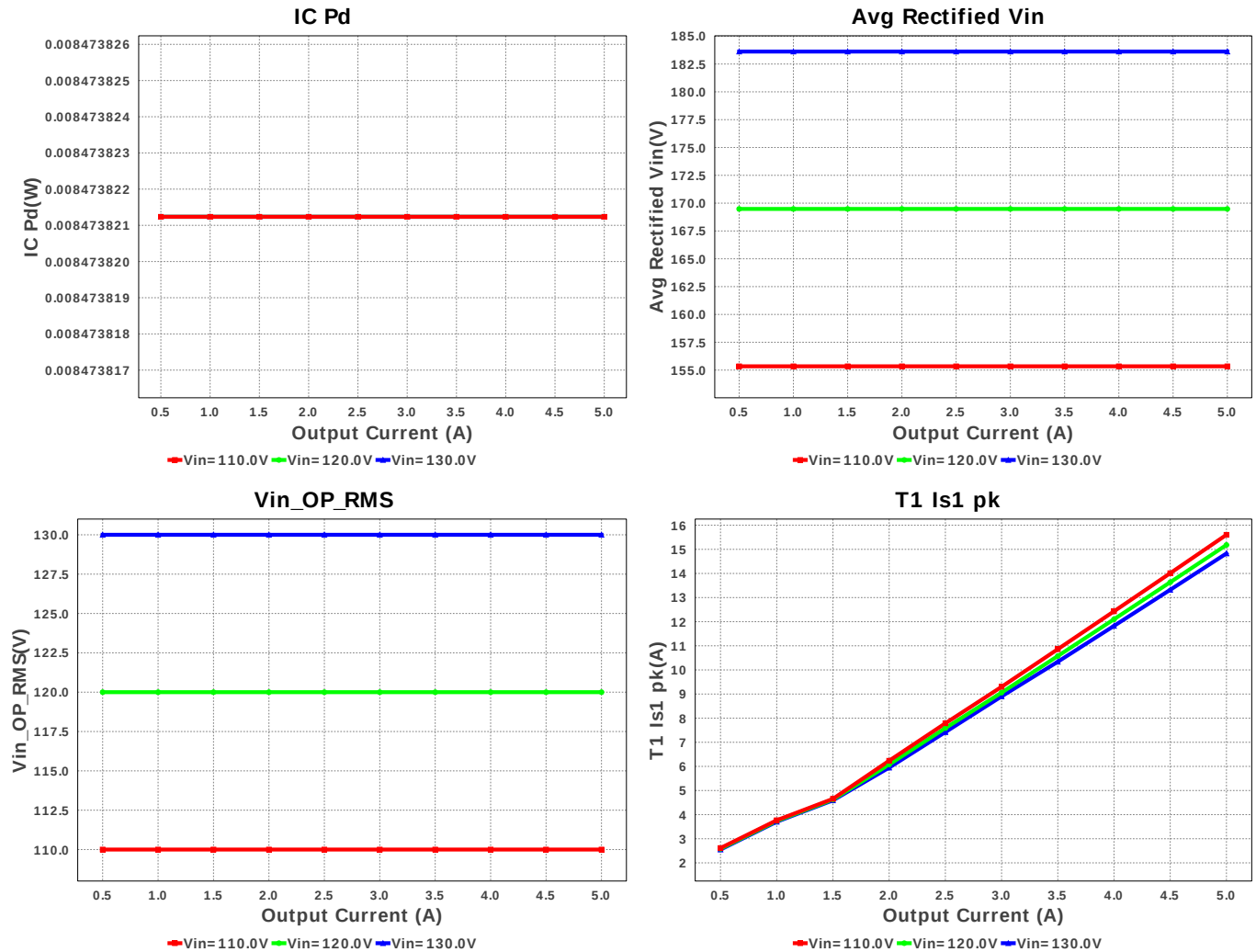

Operating Values

#	Name	Value	Category	Description
1.	Cin IRMS	1.313 A	Current	Input capacitor RMS ripple current
2.	Cout IRMS	5.55 A	Current	Output capacitor RMS ripple current
3.	Iin rms	896.01 mA	Current	RMS Input Current
4.	T1 Iprim RMS	1.1 A	Current	Transformer Primary RMS Current
5.	T1 Iprim pk	2.971 A	Current	Transformer Primary Peak Current
6.	T1 Is1 RMS	7.374 A	Current	Transformer Secondary1 RMS Current
7.	T1 Is1 pk	17.822 A	Current	Transformer Secondary1 Peak Current
8.	Avg Rectified Vin	183.62 V	General	Average Rectified Voltage for the AC Line Period
9.	BOM Count	38	General	Total Design BOM count
10.	FootPrint	1.589 k mm ²	General	Total Foot Print Area of BOM components
11.	Pout	111.052 W	General	Total output power
12.	Total BOM	\$0.0	General	Total BOM Cost
13.	D1a Tj	93.143 degC	Op_Point	D1 junction temperature
14.	D1b Tj	93.143 degC	Op_Point	D1 junction temperature
15.	Vout Actual	22.21 V	Op_Point	Vout Actual calculated based on selected voltage divider resistors
16.	Vout OP	22.21 V	Op_Point	Operational Output Voltage
17.	Duty Cycle	41.093 %	Op_point	Duty cycle
18.	Efficiency	95.339 %	Op_point	Steady state efficiency
19.	Frequency_	63.564 kHz	Op_point	Switching frequency
20.	IC Tj	32.618 degC	Op_point	IC junction temperature
21.	ICThetaJA	200.0 degC/W	Op_point	IC junction-to-ambient thermal resistance
22.	IOUT_OP	5.0 A	Op_point	Iout operating point
23.	M2 TjOP	49.206 degC	Op_point	M2 MOSFET junction temperature
24.	Min Rectified Vin	183.42 V	Op_point	Minimum voltage seen at rectified input
25.	Peak Rectified Vin	183.82 V	Op_point	Peak voltage seen at rectified input
26.	Vin_OP_RMS	130.0 V	Op_point	AC Input RMS Voltage
27.	Vout p-p	222.774 mV	Op_point	Peak-to-peak output ripple voltage
28.	Avg Bridge Diode Pd	947.892 mW	Power	Average Power Dissipation in the Bridge Diode over the AC Line Period
29.	Cin Pd	229.982 mW	Power	Input capacitor power dissipation
30.	Cout Pd	385.094 mW	Power	Output capacitor power dissipation
31.	D1a Pd	1.263 W	Power	Diode1 power dissipation

#	Name	Value	Category	Description
32.	D1b Pd	1.263 W	Power	Diode1 power dissipation
33.	IC Pd	13.091 mW	Power	IC power dissipation
34.	M2 Pd	302.194 mW	Power	M2 MOSFET total power dissipation
35.	Total Pd	5.429 W	Power	Total Power Dissipation
36.	Xformer Pd	1.473 W	Power	Transformer power dissipation
37.	Vout Tolerance	2.12 %		Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable

Design Inputs

#	Name	Value	Description
1.	Iout	5.0	Maximum Output Current
2.	VinMax	130.0	Maximum input voltage
3.	VinMin	110.0	Minimum input voltage
4.	Vout	22.2	Output Voltage
5.	acFrequency	60.0	Light Output in Lumen
6.	base_pn	LM5023	Texas Instruments Base Part Number
7.	source	AC	Input Source Type
8.	ta	30.0	Ambient temperature

Design Assistance

1. The feedback resistors will set the output voltage of the circuit. The values chosen may need to be fine tuned based on the final Transformer turns ratios and the voltage across the output diode at close to zero current. Please see the datasheet for further design guidance. <http://www.ti.com/lit/ds/symlink/lm5023.pdf>

2. LM5023 Product Folder : <http://www.ti.com/product/LM5023> : contains the data sheet and other resources.

Texas Instruments' WEBENCH simulation tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Simulations are created using Texas Instruments' published specifications as well as the published specifications of other device manufacturers. While Texas Instruments does update this information periodically, this information may not be current at the time the simulation is built. Texas Instruments does not warrant the accuracy or completeness of the specifications or any information contained therein. Texas Instruments does not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. Texas Instruments does not warrant that the designs are production worthy.

You should completely validate and test your design implementation to confirm the system functionality for your application prior to production.

Use of Texas Instruments' WEBENCH simulation tools is subject to [Texas Instruments' Site Terms and Conditions of Use](#). Prototype boards based on WEBENCH created designs are provided AS IS without warranty of any kind for evaluation and testing purposes and are subject to the terms of the [Evaluation License Agreement](#).