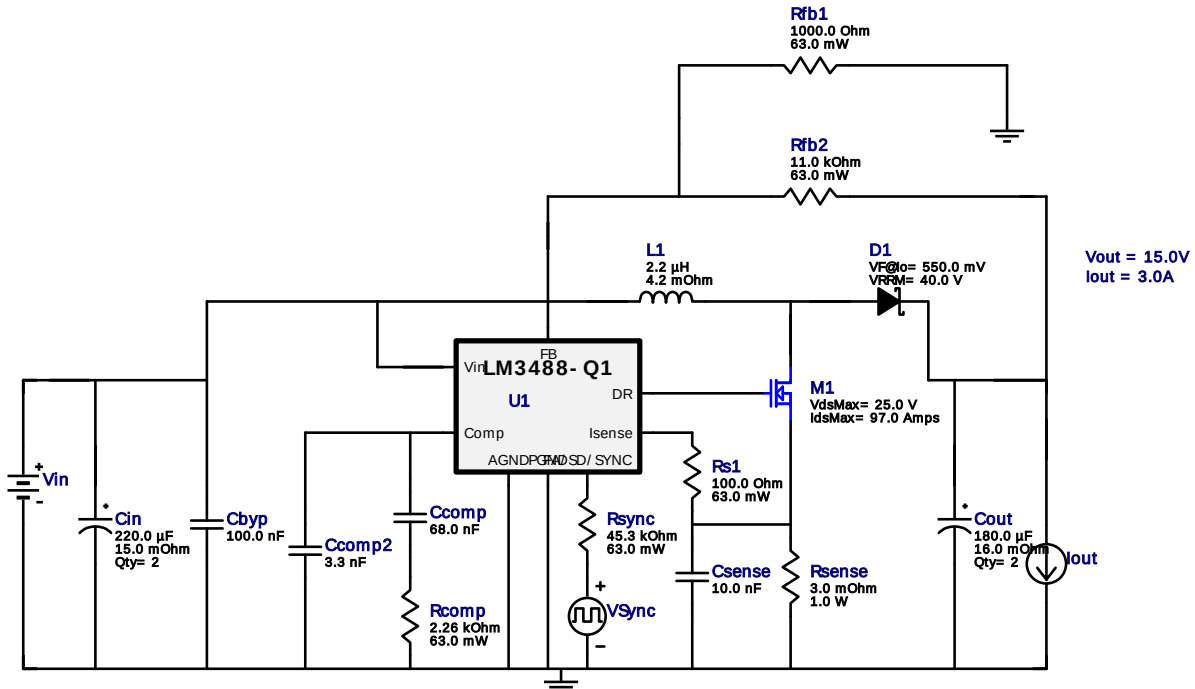


WEBENCH® Design Report



Design : 4737466/38 LM3488QMMX/NOPB
LM3488QMMX/NOPB 3.7V-4.2V to 15.00V @ 3.0A

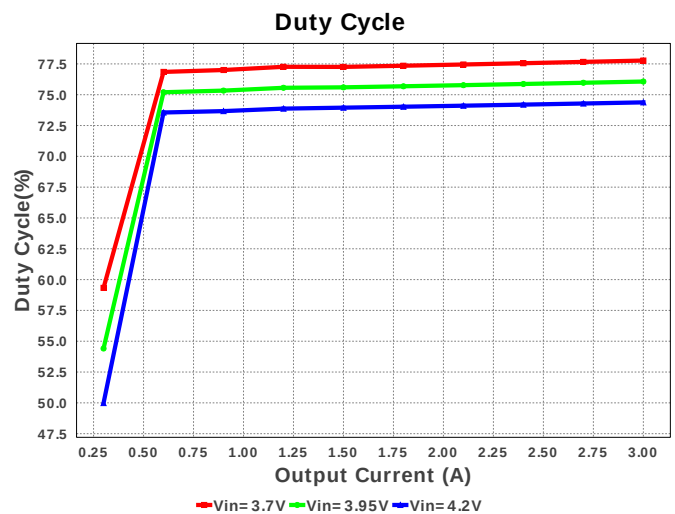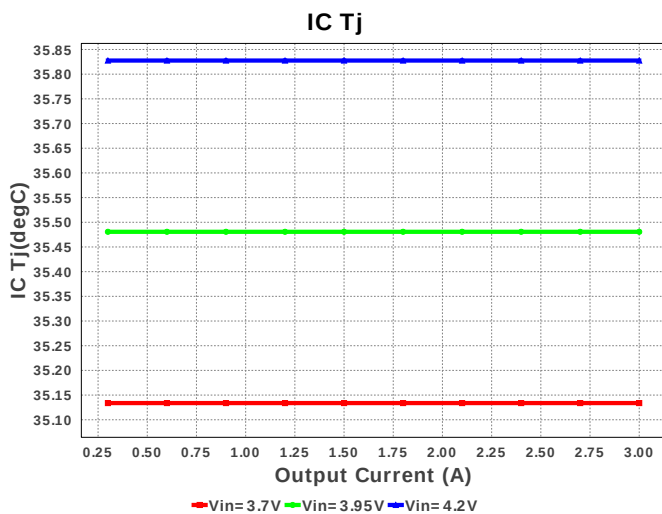
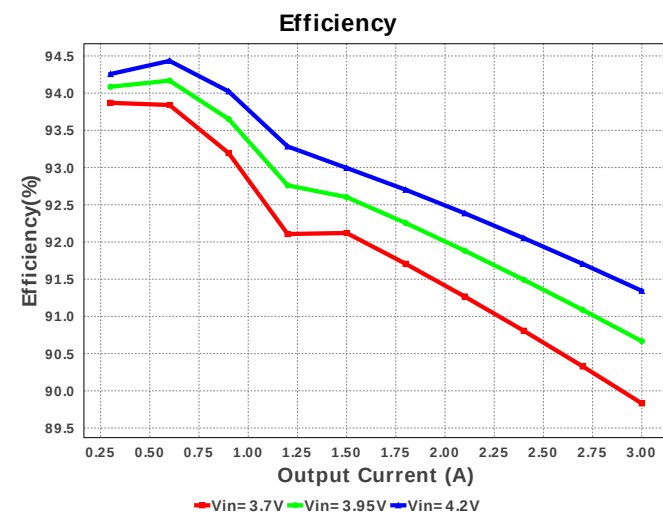
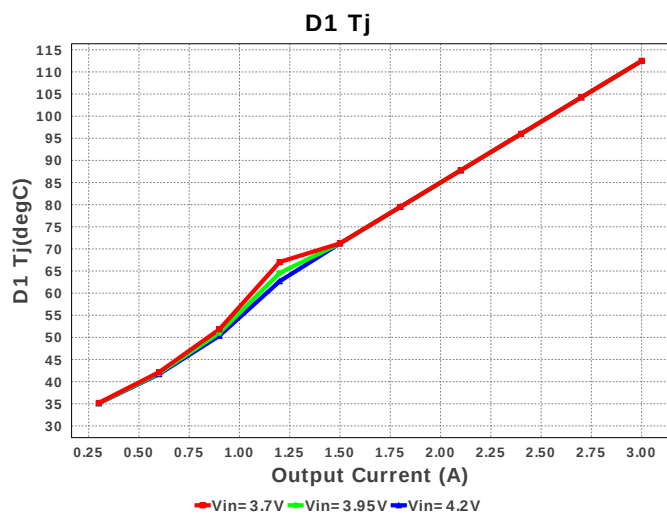
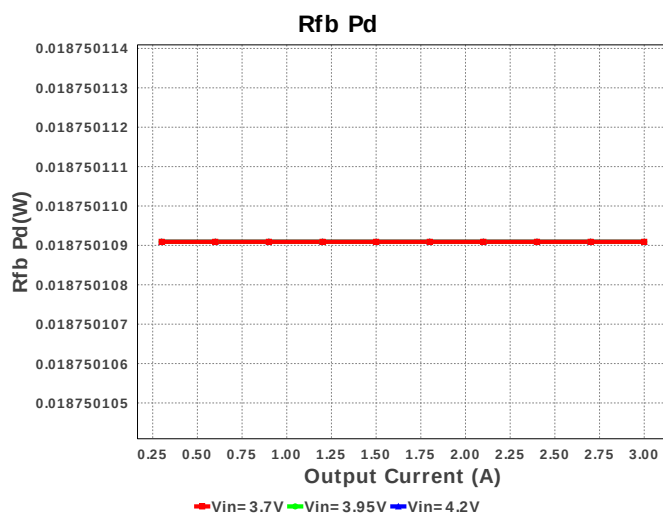
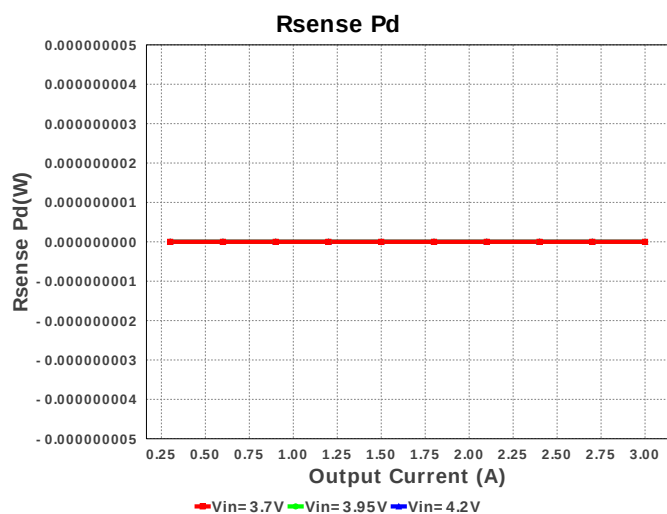
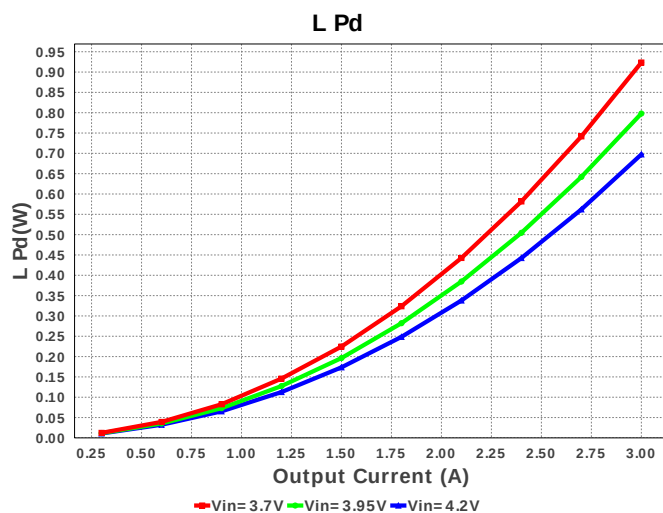
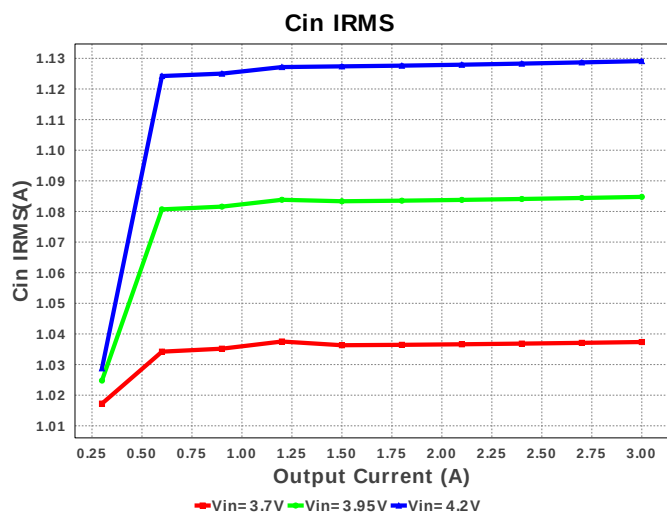
1. With the low turn of voltage of the LM34x8 your power supply may current limit before you reach your working input voltage. If this happens, or to preempt this from happening, you can include a low pass RC filter from input voltage to Vin on the IC. Make sure the rise time on the RC network is slower than your supply's rise time. If you are not using the synchronization feature of the part use the LM3478.







Electrical BOM







#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	Cbyp	MuRata	GRM155R60J104KA01D Series= X5R	Cap= 100.0 nF VDC= 6.3 V IRMS= 0.0 A	1	\$0.01	0402 3 mm ²
2.	Ccomp	MuRata	GRM155R61A683KA01D Series= X5R	Cap= 68.0 nF VDC= 10.0 V IRMS= 0.0 A	1	\$0.01	0402 3 mm ²
3.	Ccomp2	MuRata	GRM216R71E332KA01D Series= X7R	Cap= 3.3 nF VDC= 25.0 V IRMS= 0.0 A	1	\$0.01	0805 7 mm ²
4.	Cin	Panasonic	6SVPE220MW Series= SVPE	Cap= 220.0 µF ESR= 15.0 mOhm VDC= 6.3 V IRMS= 3.15 A	2	\$0.20	CAPSMT_62_E61 53 mm ²
5.	Cout	Panasonic	25SVPF180M Series= ?	Cap= 180.0 µF ESR= 16.0 mOhm VDC= 25.0 V IRMS= 4.65 A	2	\$0.61	CAPSMT_62_E12 106 mm ²
6.	Csense	MuRata	GRM216R71H103KA01D Series= X7R	Cap= 10.0 nF VDC= 50.0 V IRMS= 0.0 A	1	\$0.01	0805 7 mm ²
7.	D1	Diodes Inc.	B540C-13-F	Vf@Io= 550.0 mV VRRM= 40.0 V	1	\$0.17	SMC 83 mm ²







#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
8.	L1	Bourns	SRP1270-2R2M	L= 2.2 μ H DCR= 4.2 mOhm	1	\$0.60	 SRP1270 246 mm ²
9.	M1	Texas Instruments	CSD16322Q5C	VdsMax= 25.0 V IdsMax= 97.0 Amps	1	\$0.50	 TRANS_NexFET_Q5C 56 mm ²
10.	Rcomp	Vishay-Dale	CRCW04022K26FKED Series= CRCW..e3	Res= 2.26 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
11.	Rfb1	Vishay-Dale	CRCW04021K00FKED Series= CRCW..e3	Res= 1000.0 Ohm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
12.	Rfb2	Vishay-Dale	CRCW040211K0FKED Series= CRCW..e3	Res= 11.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
13.	Rs1	Vishay-Dale	CRCW0402100RFKED Series= CRCW..e3	Res= 100.0 Ohm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
14.	Rsense	Stackpole Electronics Inc	CSNL1206FT3L00 Series= CSNL	Res= 3.0 mOhm Power= 1.0 W Tolerance= 1.0%	1	\$0.19	 1206 11 mm ²
15.	Rsync	Vishay-Dale	CRCW040245K3FKED Series= CRCW..e3	Res= 45.3 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
16.	U1	Texas Instruments	LM3488QMMX/NOPB	Switcher	1	\$0.96	 MUA08A 24 mm ²






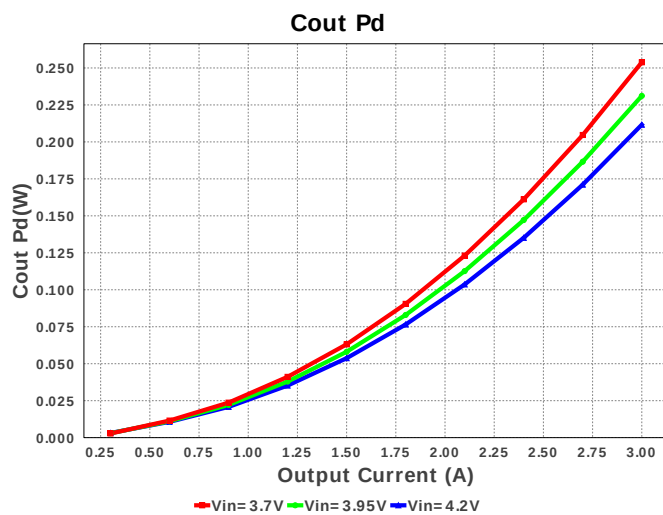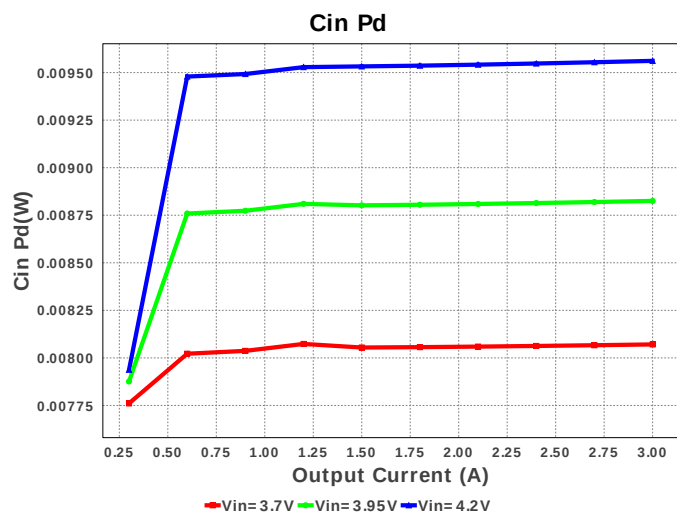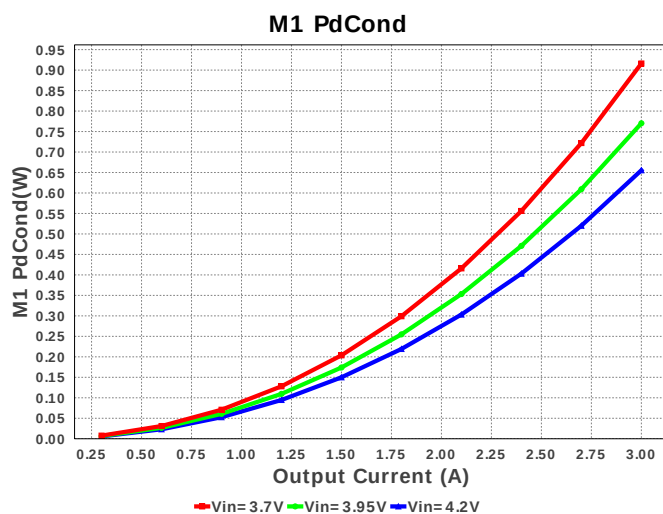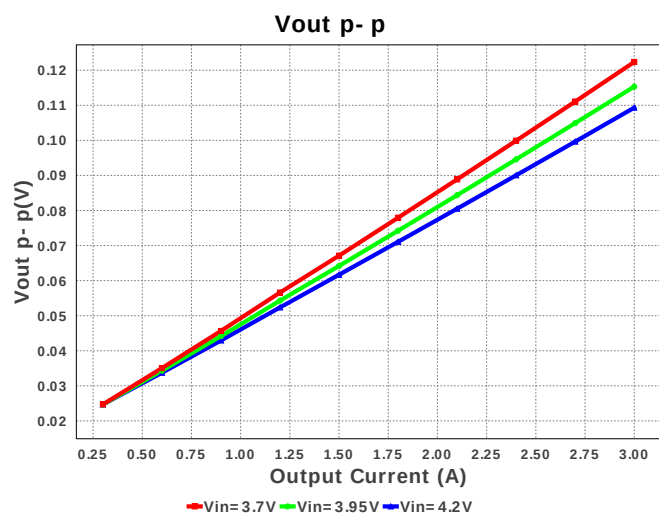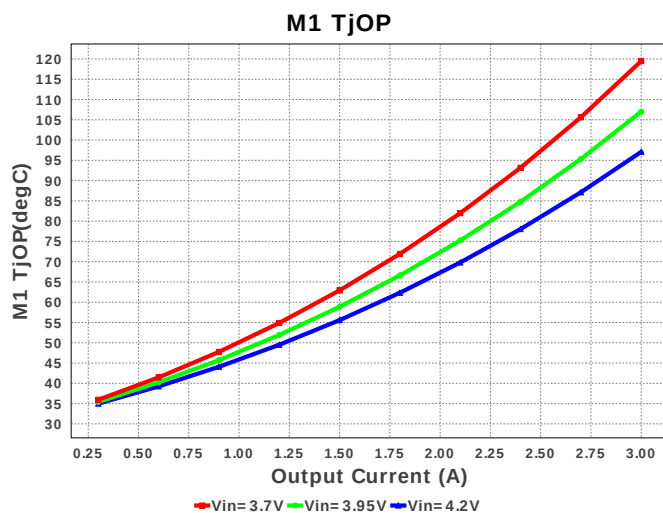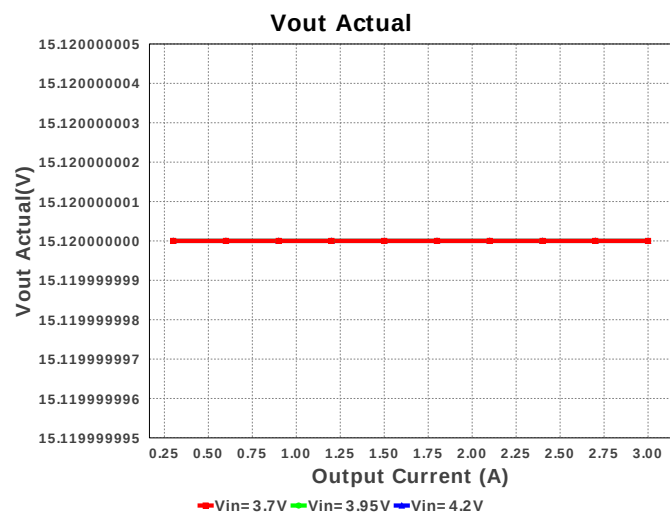

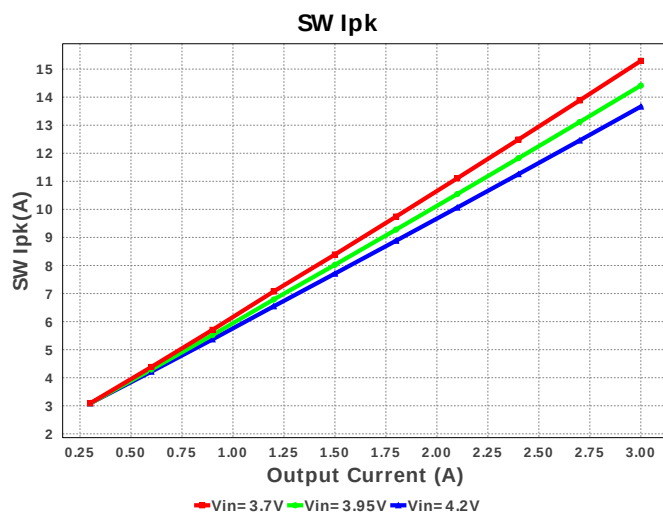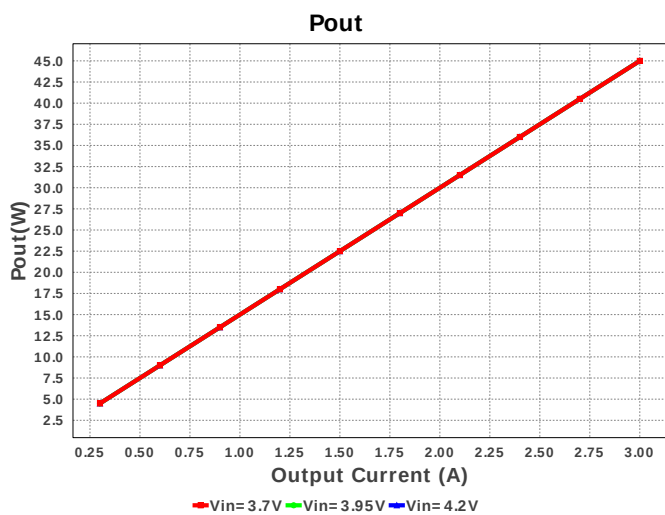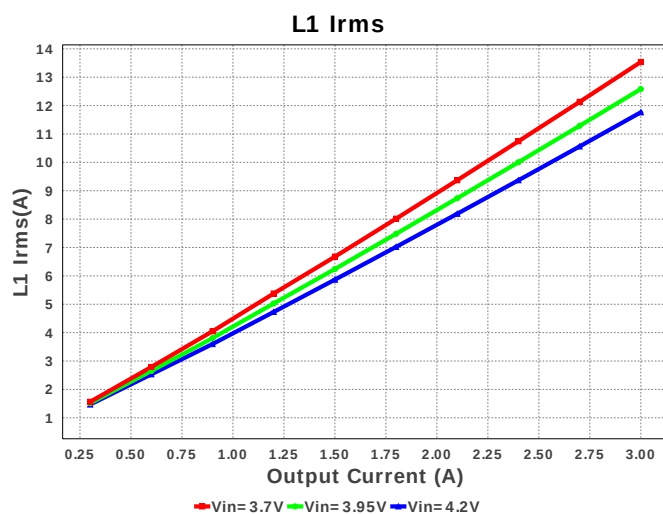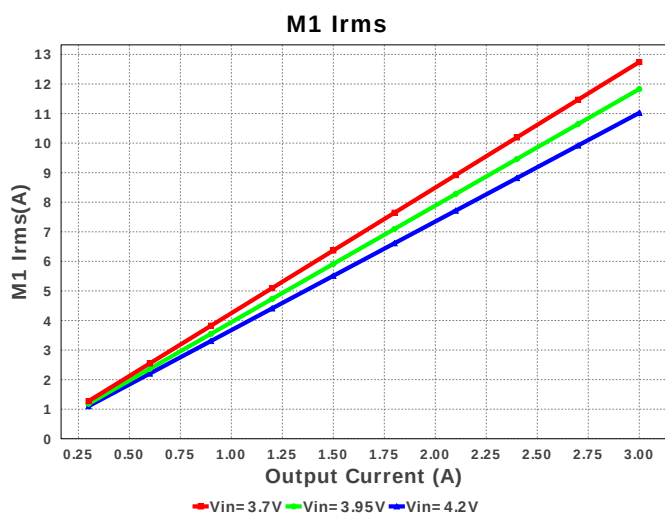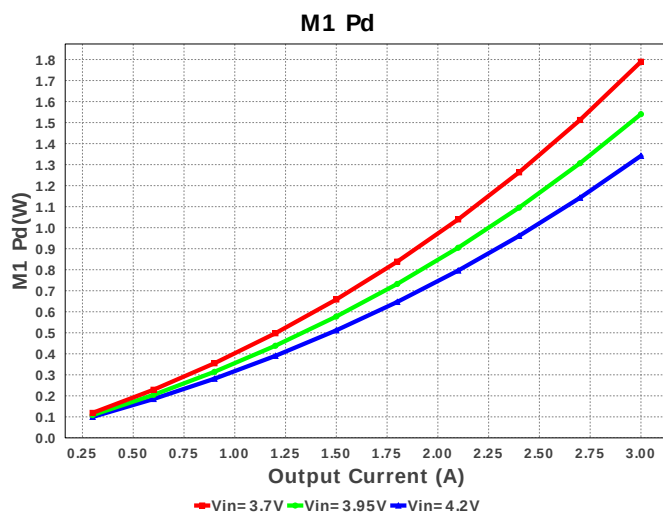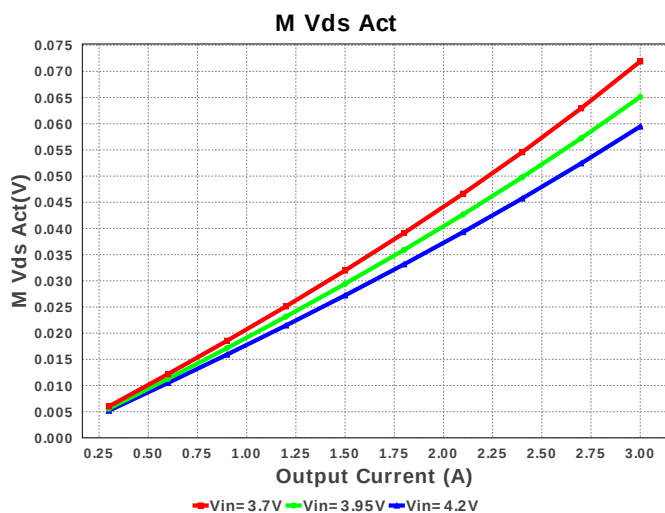

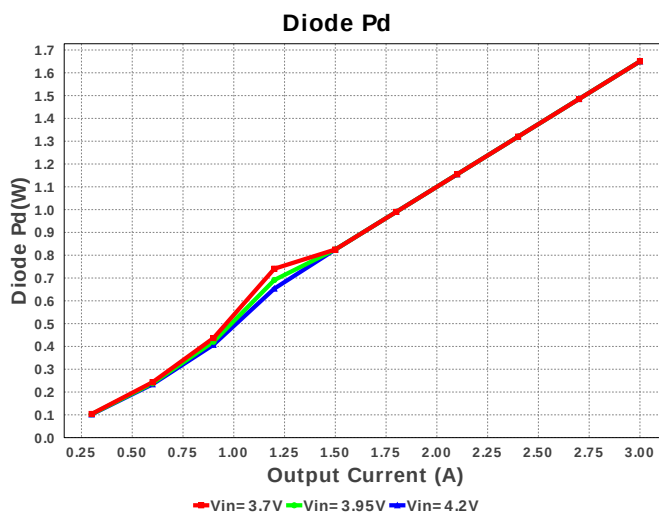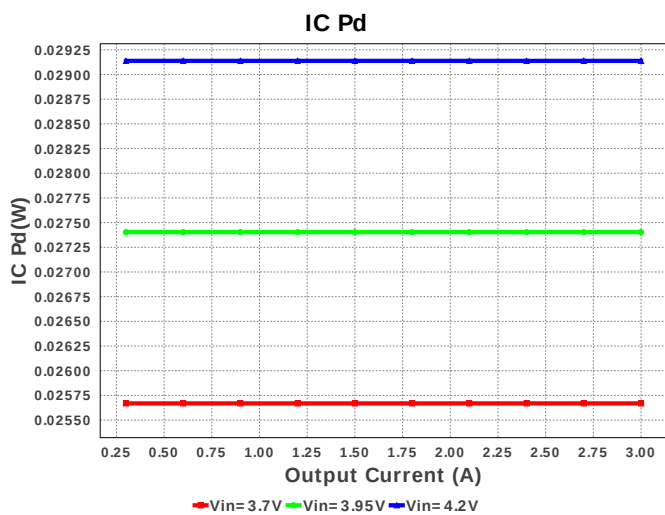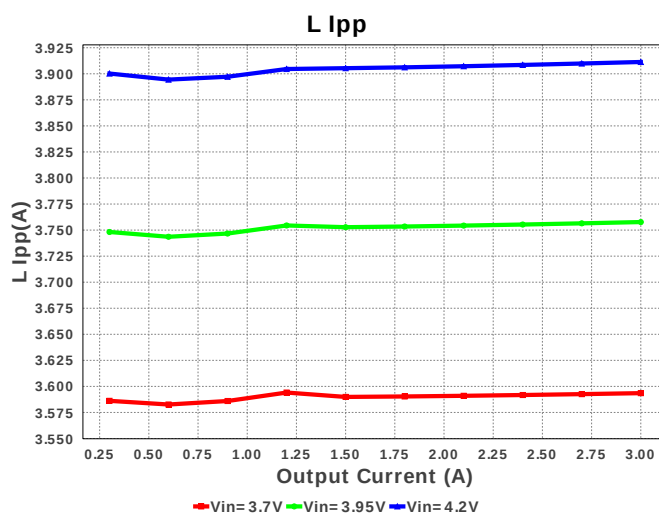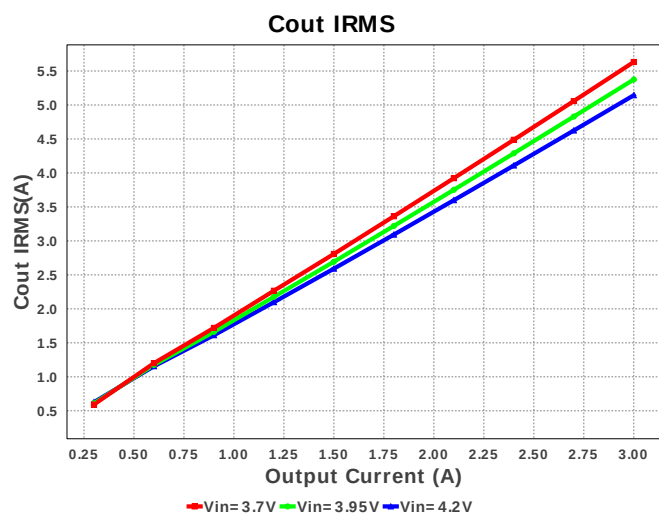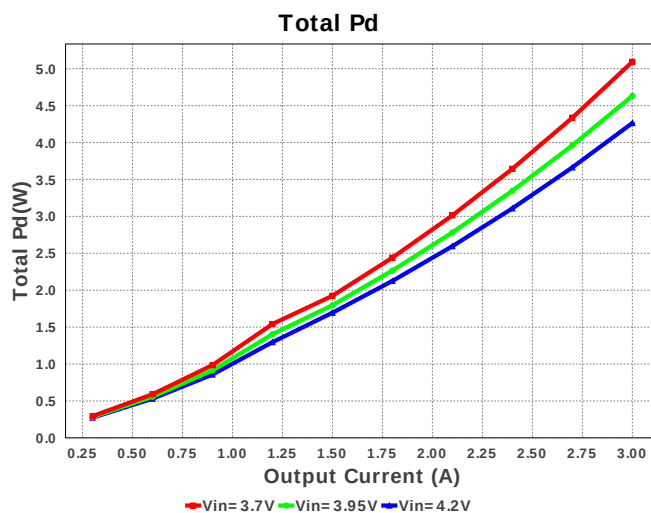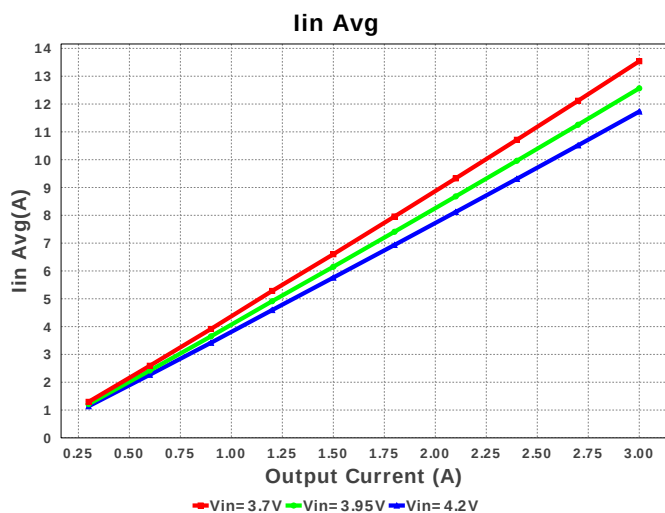

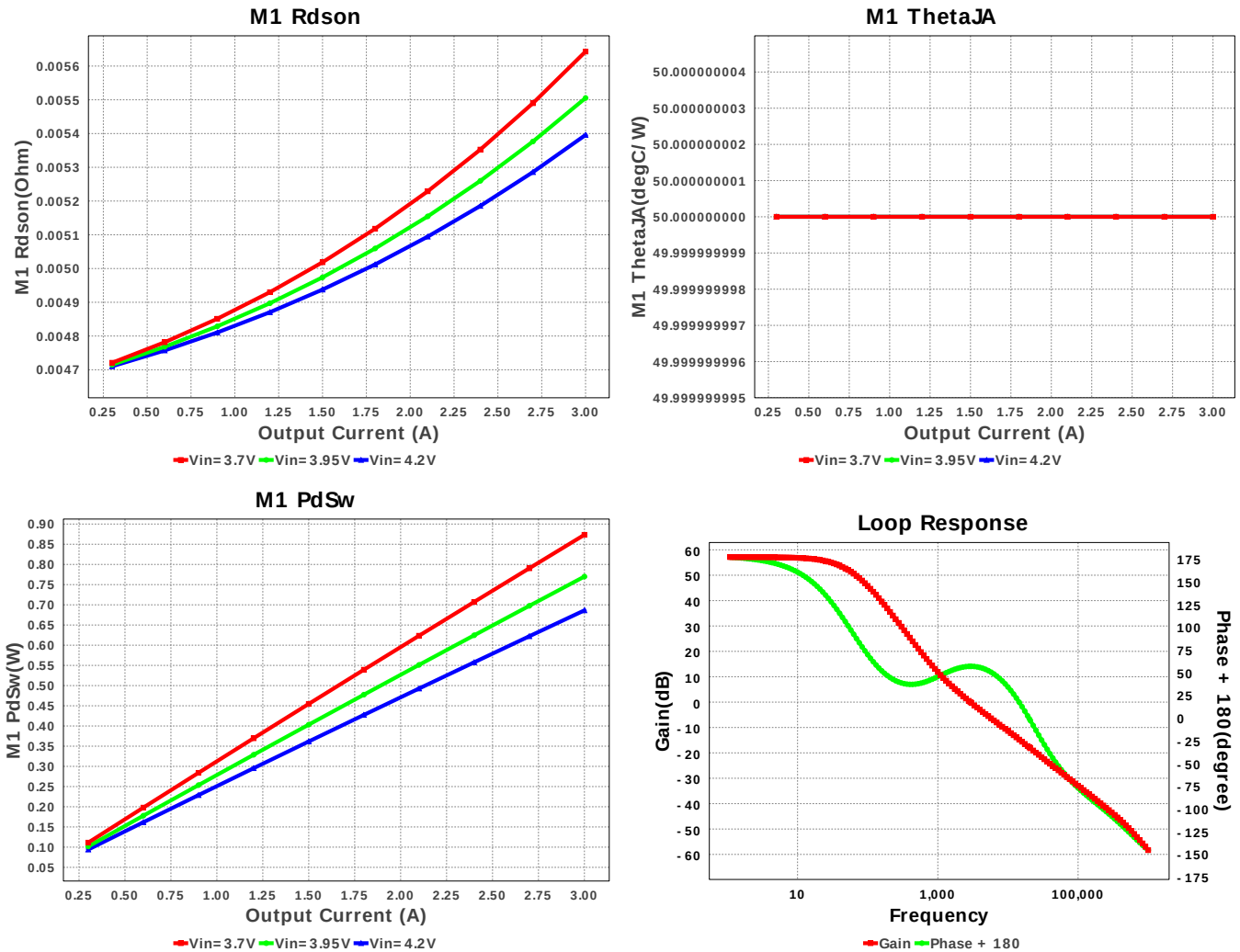

Operating Values

#	Name	Value	Category	Description
1.	Cin IRMS	1.037 A	Current	Input capacitor RMS ripple current
2.	Cout IRMS	5.633 A	Current	Output capacitor RMS ripple current
3.	Iin Avg	13.539 A	Current	Average input current
4.	L Ipp	3.594 A	Current	Peak-to-peak inductor ripple current
5.	L1 Irms	13.536 A	Current	Inductor ripple current
6.	M1 Irms	12.741 A	Current	M1 MOSFET Irms
7.	SW Ipk	15.293 A	Current	Peak switch current
8.	BOM Count	18	General	Total Design BOM count
9.	FootPrint	774.0 mm ²	General	Total Foot Print Area of BOM components
10.	Frequency	360.0 kHz	General	Switching frequency
11.	IC Tolerance	15.3 mV	General	IC Feedback Tolerance
12.	M Vds Act	71.9 mV	General	M Vds
13.	M1 Rdson	5.643 mOhm	General	Drain-Source On-resistance
14.	M1 ThetaJA	50.0 degC/W	General	MOSFET junction-to-ambient thermal resistance
15.	Pout	45.0 W	General	Total output power
16.	Total BOM	\$4.13	General	Total BOM Cost
17.	D1 Tj	112.5 degC	Op_Point	D1 junction temperature
18.	Low Freq Gain	55.878 dB	Op_Point	Gain at 10Hz
19.	Vout Actual	15.12 V	Op_Point	Vout Actual calculated based on selected voltage divider resistors
20.	Vout OP	15.0 V	Op_Point	Operational Output Voltage
21.	Cross Freq	2.574 kHz	Op_point	Bode plot crossover frequency
22.	Duty Cycle	77.772 %	Op_point	Duty cycle
23.	Efficiency	89.831 %	Op_point	Steady state efficiency
24.	Gain Marg	-16.8 dB	Op_point	Bode Plot Gain Margin
25.	IC Tj	35.134 degC	Op_point	IC junction temperature
26.	ICThetaJA	200.0 degC/W	Op_point	IC junction-to-ambient thermal resistance
27.	IOUT_OP	3.0 A	Op_point	Iout operating point
28.	M1 TJOP	119.473 degC	Op_point	M1 MOSFET junction temperature
29.	Phase Marg	55.602 deg	Op_point	Bode Plot Phase Margin
30.	VIN_OP	3.7 V	Op_point	Vin operating point
31.	Vout p-p	122.345 mV	Op_point	Peak-to-peak output ripple voltage

#	Name	Value	Category	Description
32.	Cin Pd	8.071 mW	Power	Input capacitor power dissipation
33.	Cout Pd	253.827 mW	Power	Output capacitor power dissipation
34.	Diode Pd	1.65 W	Power	Diode power dissipation
35.	IC Pd	25.669 mW	Power	IC power dissipation
36.	L Pd	923.475 mW	Power	Inductor power dissipation
37.	M1 Pd	1.789 W	Power	M1 MOSFET total power dissipation
38.	M1 PdCond	916.111 mW	Power	M1 MOSFET conduction losses
39.	M1 PdSw	873.354 mW	Power	M1 MOSFET switching losses
40.	Rfb Pd	18.75 mW	Power	Rfb Power Dissipation
41.	Rsense Pd	488.664 mW	Power	Rsense Power Dissipation
42.	Total Pd	5.094 W	Power	Total Power Dissipation
43.	Vout Tolerance	3.089 %		Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable

Design Inputs

#	Name	Value	Description
1.	Iout	3.0	Maximum Output Current
2.	VinMax	4.2	Maximum input voltage
3.	VinMin	3.7	Minimum input voltage
4.	Vout	15.0	Output Voltage
5.	base_pn	LM3488-Q1	Texas Instruments Base Part Number
6.	source	DC	Input Source Type
7.	ta	30.0	Ambient temperature
8.	userfsw	360.0 k	Customer Selected Frequency

Design Assistance

1. Feature Highlights: Automotive Qualified, 40V Wide Vin Low-Side N-Channel Controller for Switching Regulators
2. LM3488-Q1 Product Folder : <http://www.ti.com/product/lm3488q%2Dq1> : contains the data sheet and other resources.

Texas Instruments' WEBENCH simulation tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Simulations are created using Texas Instruments' published specifications as well as the published specifications of other device manufacturers. While Texas Instruments does update this information periodically, this information may not be current at the time the simulation is built. Texas Instruments does not warrant the accuracy or completeness of the specifications or any information contained therein. Texas Instruments does not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. Texas Instruments does not warrant that the designs are production worthy.

You should completely validate and test your design implementation to confirm the system functionality for your application prior to production.

Use of Texas Instruments' WEBENCH simulation tools is subject to [Texas Instruments' Site Terms and Conditions of Use](#). Prototype boards based on WEBENCH created designs are provided AS IS without warranty of any kind for evaluation and testing purposes and are subject to the terms of the [Evaluation License Agreement](#).