


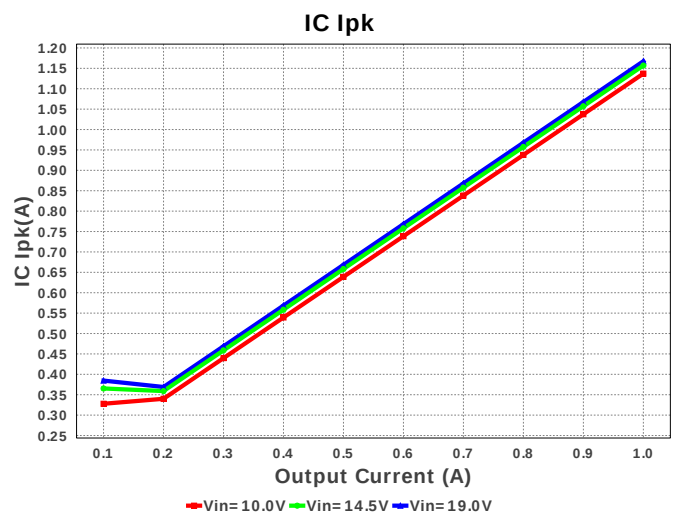
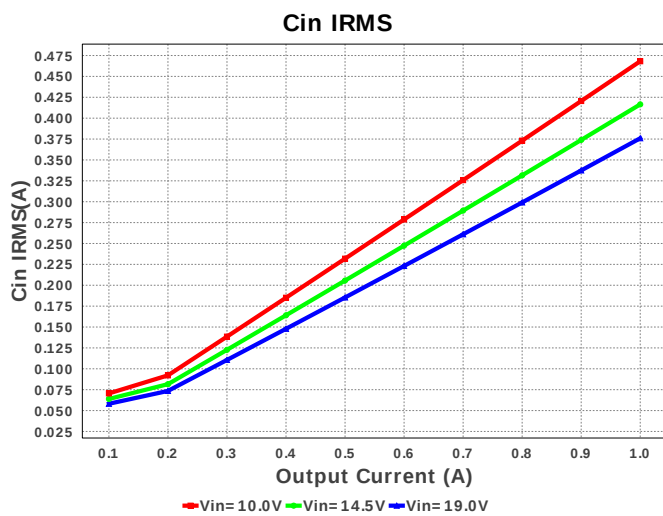
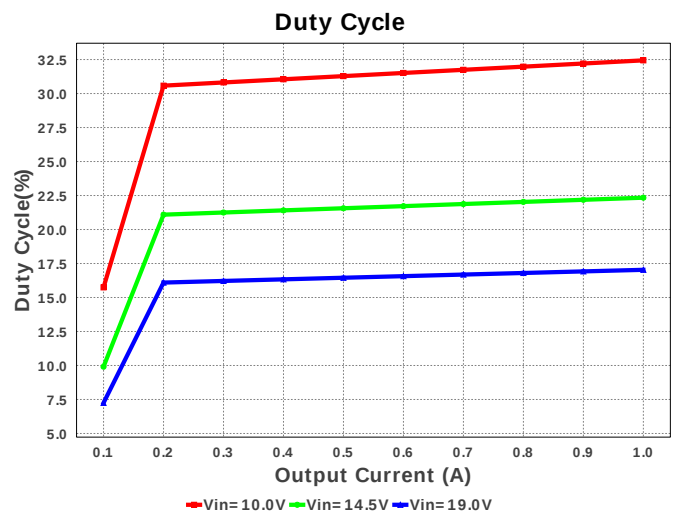
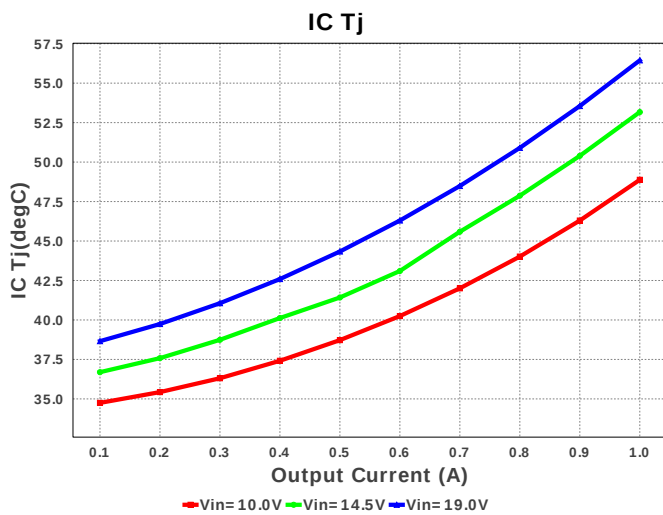
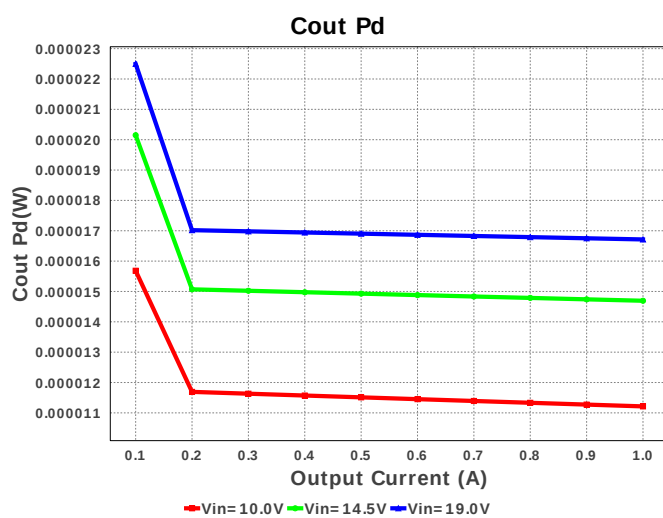
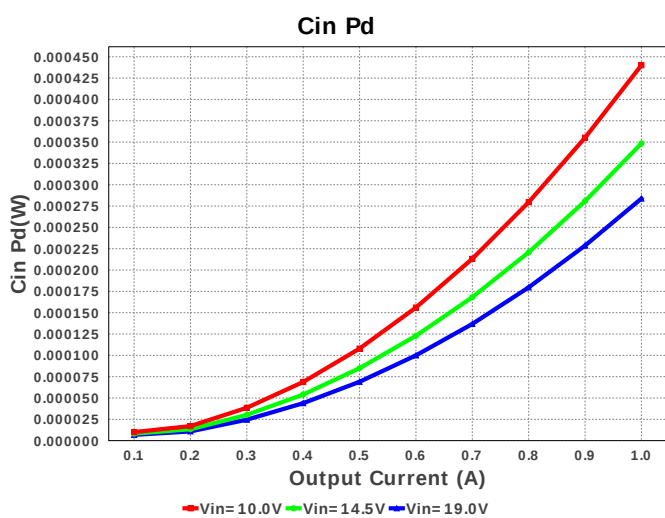
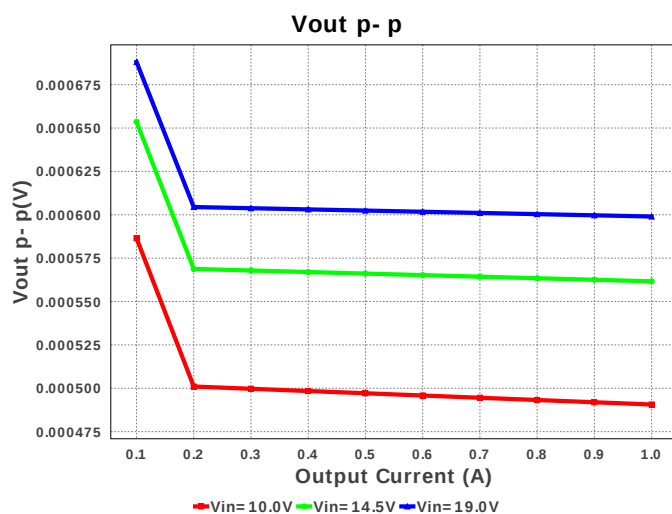







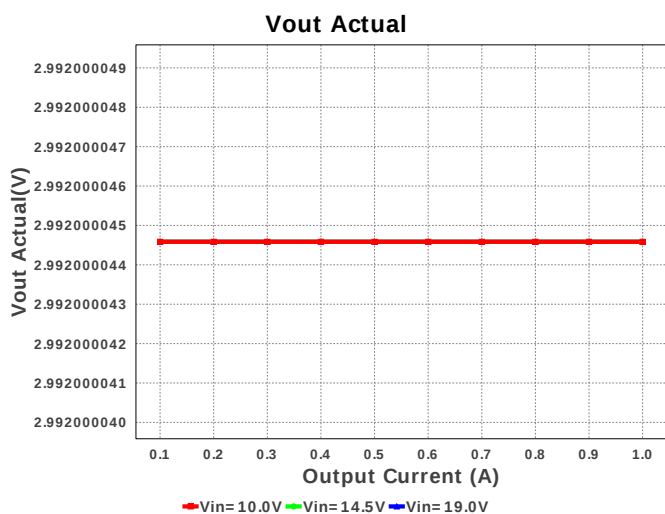



Device = LMR24210TL/NOPB
Topology = Buck
Created = 7/19/16 5:59:11 AM
BOM Cost = \$2.27
BOM Count = 13
Total Pd = 0.65W

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
8.	Ren	Vishay-Dale	CRCW0402100KFKED Series= CRCW..e3	Res= 100.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
9.	Rfbb	Vishay-Dale	CRCW04021K00FKED Series= CRCW..e3	Res= 1000.0 Ohm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
10.	Rfbt	Vishay-Dale	CRCW04022K74FKED Series= CRCW..e3	Res= 2.74 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
11.	Ron	Vishay-Dale	CRCW040246K4FKED Series= CRCW..e3	Res= 46.4 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
12.	U1	Texas Instruments	LMR24210TL/NOPB	Switcher	1	\$1.73	 TLC28VFA 16 mm ²

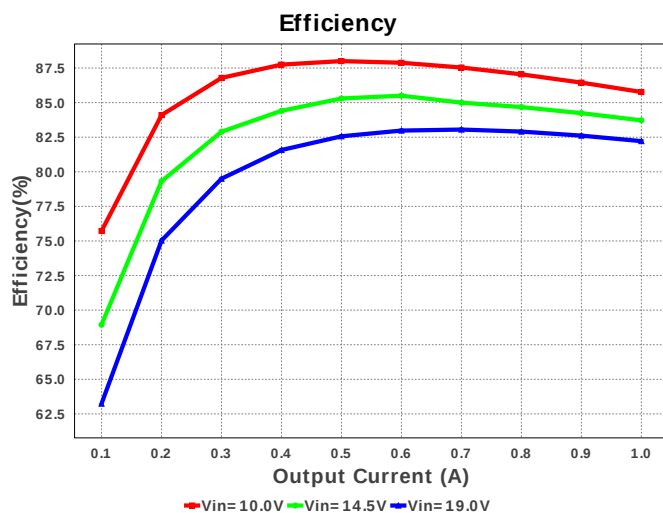

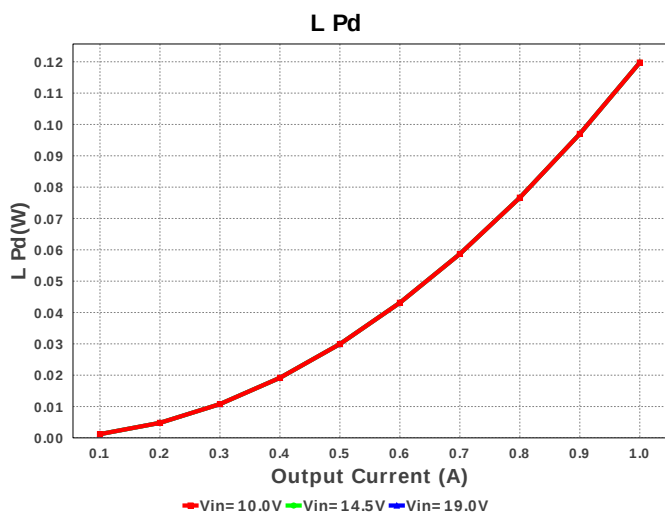

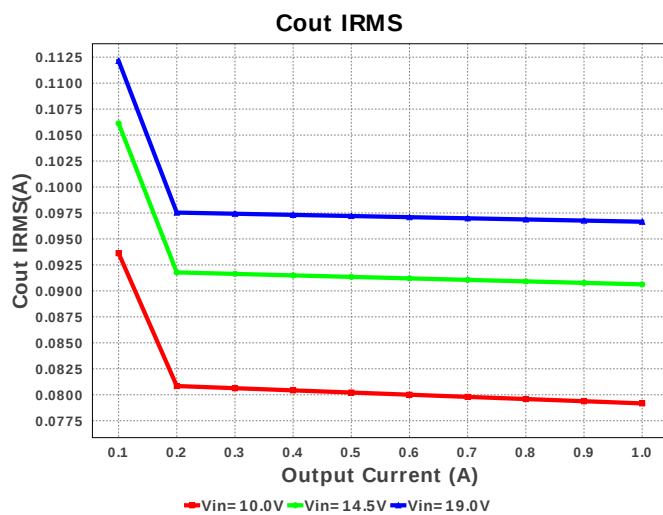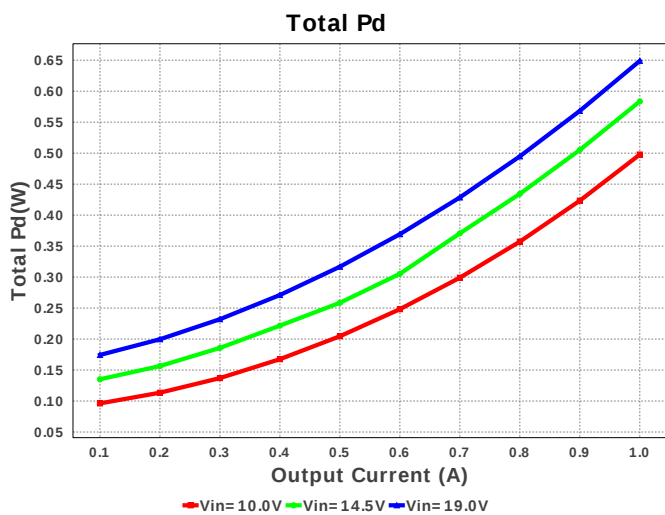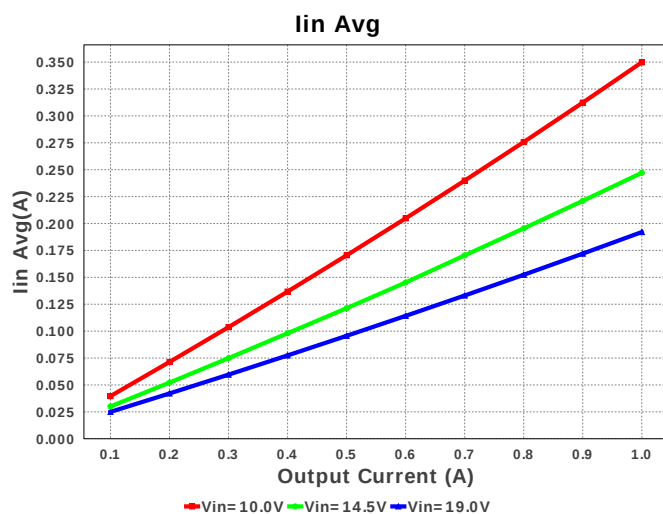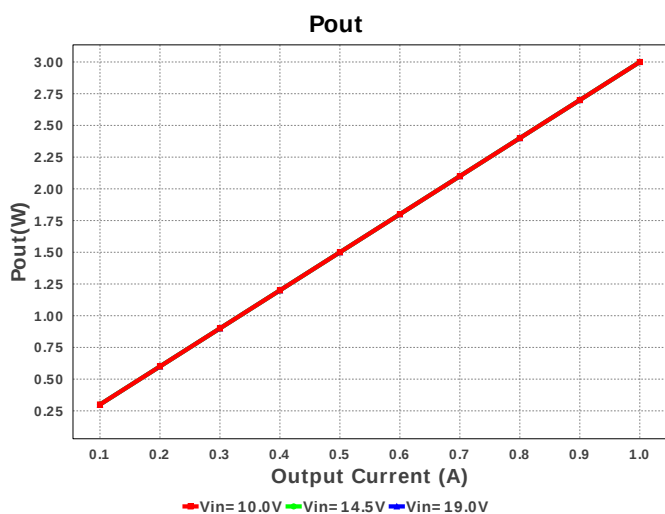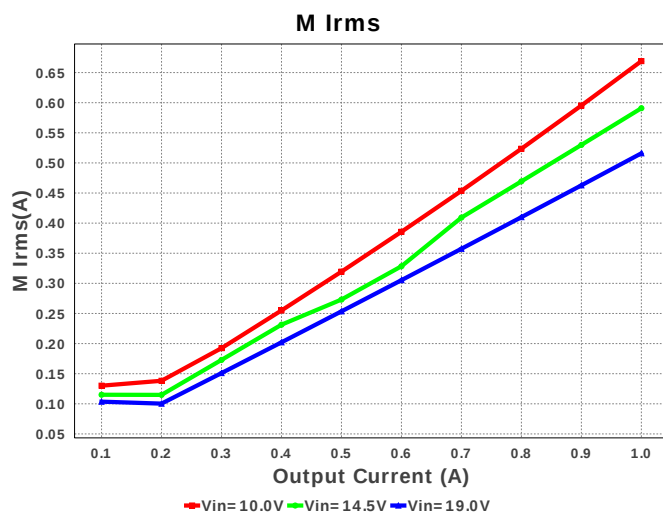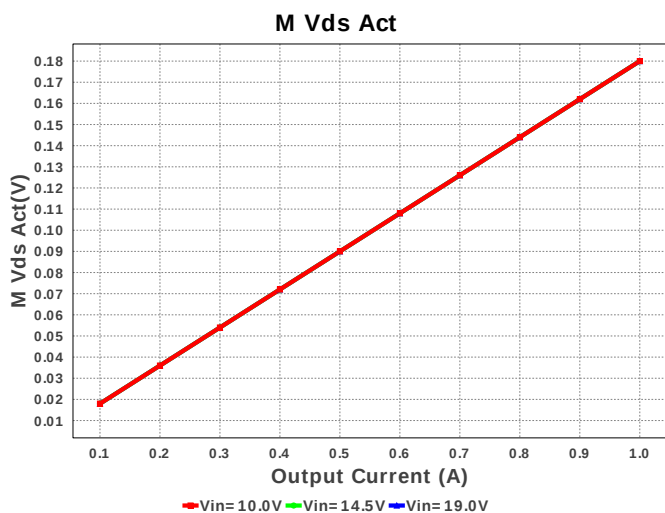

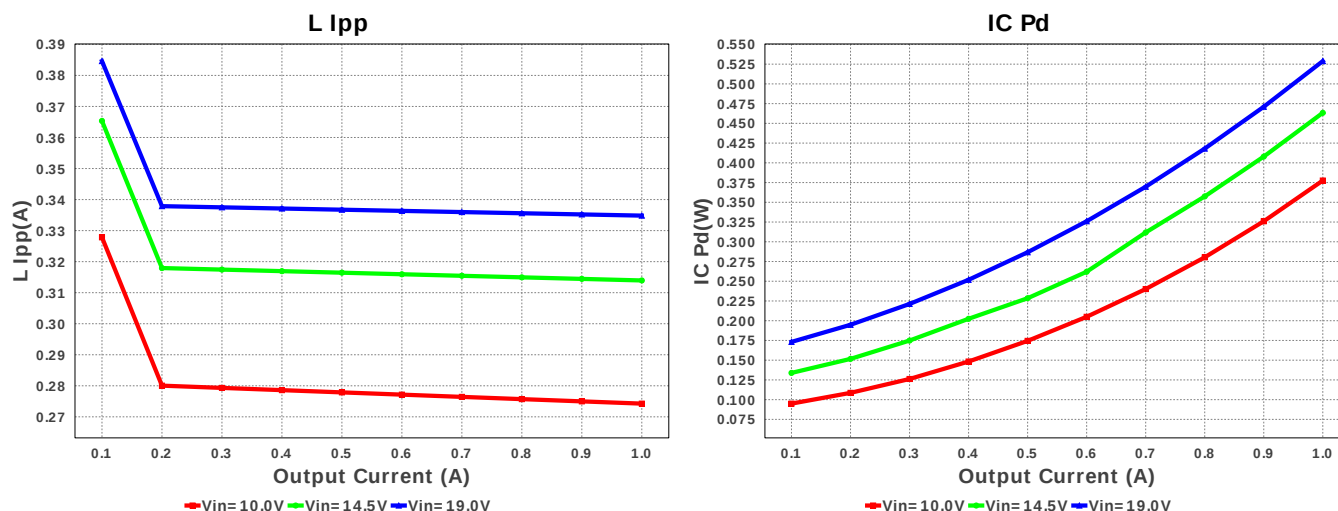

Operating Values

#	Name	Value	Category	Description
1.	Cin IRMS	375.947 mA	Current	Input capacitor RMS ripple current
2.	Cout IRMS	96.657 mA	Current	Output capacitor RMS ripple current
3.	IC Ipk	1.167 A	Current	Peak switch current in IC
4.	Iin Avg	192.05 mA	Current	Average input current
5.	L Ipp	334.83 mA	Current	Peak-to-peak inductor ripple current
6.	M Irms	515.931 mA	Current	MOSFET RMS current
7.	BOM Count	13	General	Total Design BOM count
8.	FootPrint	138.0 mm ²	General	Total Foot Print Area of BOM components
9.	Frequency	497.347 kHz	General	Switching frequency
10.	IC Tolerance	16.0 mV	General	IC Feedback Tolerance
11.	M Vds Act	180.0 mV	General	Voltage drop across the MosFET
12.	Pout	3.0 W	General	Total output power
13.	Total BOM	\$2.27	General	Total BOM Cost
14.	Vout Actual	2.992 V	Op_Point	Vout Actual calculated based on selected voltage divider resistors
15.	Vout OP	3.0 V	Op_Point	Operational Output Voltage
16.	Duty Cycle	17.036 %	Op_point	Duty cycle
17.	Efficiency	82.216 %	Op_point	Steady state efficiency
18.	IC Tj	56.443 degC	Op_point	IC junction temperature
19.	ICThetaJA	50.0 degC/W	Op_point	IC junction-to-ambient thermal resistance
20.	IOUT_OP	1.0 A	Op_point	Iout operating point
21.	VIN_OP	19.0 V	Op_point	Vin operating point
22.	Vout p-p	599.009 μV	Op_point	Peak-to-peak output ripple voltage
23.	Cin Pd	283.803 μW	Power	Input capacitor power dissipation
24.	Cout Pd	16.714 μW	Power	Output capacitor power dissipation
25.	IC Pd	528.87 mW	Power	IC power dissipation
26.	L Pd	119.75 mW	Power	Inductor power dissipation
27.	Total Pd	648.929 mW	Power	Total Power Dissipation
28.	Vout Tolerance	3.51 %		Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable

Design Inputs

#	Name	Value	Description
1.	Iout	1.0	Maximum Output Current
2.	VinMax	19.0	Maximum input voltage
3.	VinMin	10.0	Minimum input voltage
4.	Vout	3.0	Output Voltage
5.	base_pn	LMR24210	Texas Instruments Base Part Number
6.	source	DC	Input Source Type
7.	ta	30.0	Ambient temperature

Design Assistance

1. LMR24210 Product Folder : <http://www.ti.com/product/LMR24210> : contains the data sheet and other resources.

Texas Instruments' WEBENCH simulation tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Simulations are created using Texas Instruments' published specifications as well as the published specifications of other device manufacturers. While Texas Instruments does update this information periodically, this information may not be current at the time the simulation is built. Texas Instruments does not warrant the accuracy or completeness of the specifications or any information contained therein. Texas Instruments does not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. Texas Instruments does not warrant that the designs are production worthy.

You should completely validate and test your design implementation to confirm the system functionality for your application prior to production.

Use of Texas Instruments' WEBENCH simulation tools is subject to [Texas Instruments' Site Terms and Conditions of Use](#). Prototype boards based on WEBENCH created designs are provided AS IS without warranty of any kind for evaluation and testing purposes and are subject to the terms of the [Evaluation License Agreement](#).