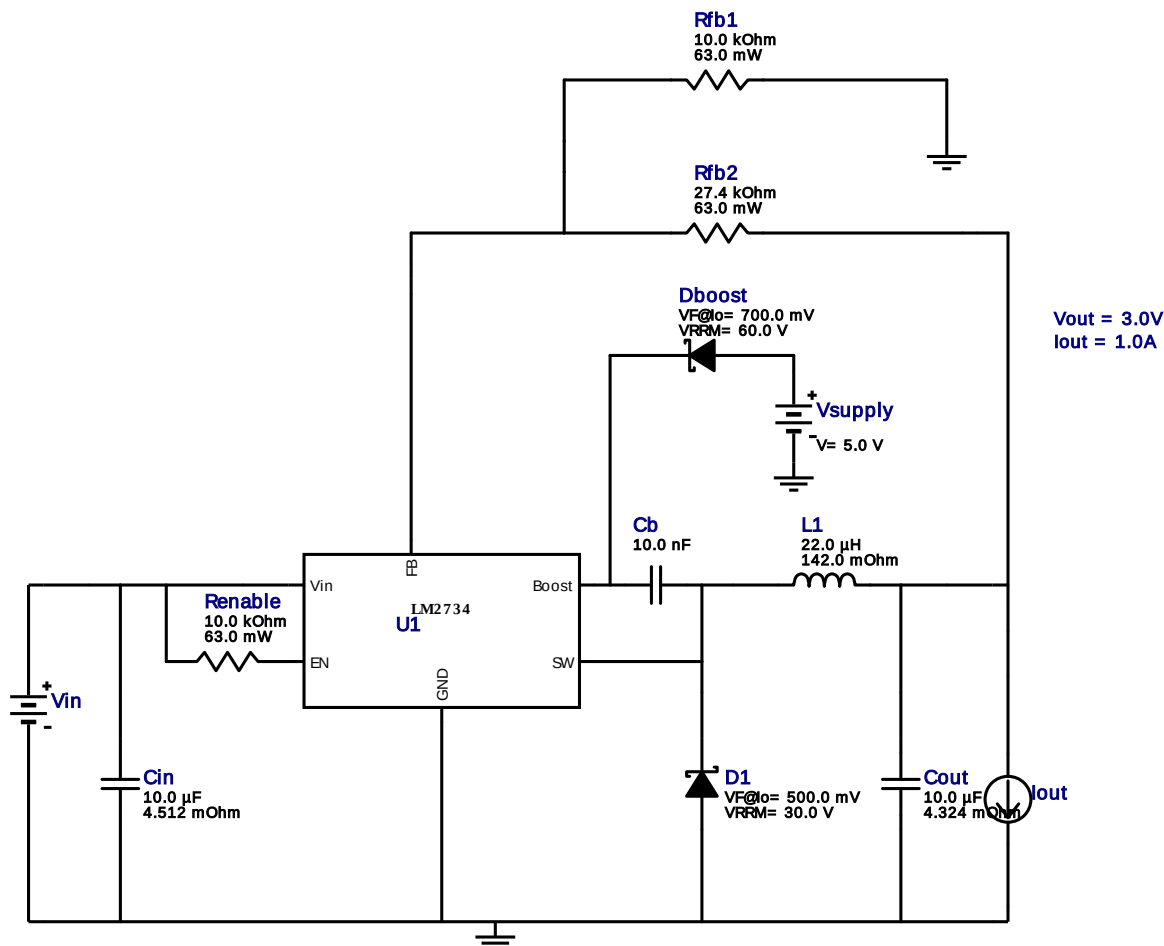














1. The Boost pin voltage must be supplied from a source of less than 5.5V. Recommended methods are described in the LM2734 datasheet Application Information.







Electrical BOM




#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	Cb	MuRata	GRM216R71H103KA01D Series= X7R	Cap= 10.0 nF VDC= 50.0 V IRMS= 0.0 A	1	\$0.01	0805 7 mm ²
2.	Cin	MuRata	GRM31CR61E106KA12L Series= X5R	Cap= 10.0 uF ESR= 4.512 mOhm VDC= 25.0 V IRMS= 2.447 A	1	\$0.05	1206_190 11 mm ²
3.	Cout	MuRata	GRM219R60J106KE19D Series= X5R	Cap= 10.0 uF ESR= 4.324 mOhm VDC= 6.3 V IRMS= 2.8728 A	1	\$0.02	0805 7 mm ²
4.	D1	Diodes Inc.	B230A-13-F	VF@Io= 500.0 mV VRRM= 30.0 V	1	\$0.09	SMA 37 mm ²
5.	Dboost	Diodes Inc.	B160-13-F	VF@Io= 700.0 mV VRRM= 60.0 V	1	\$0.06	SMA 37 mm ²

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
6.	L1	Bourns	SRN6045-220M	L= 22.0 μ H DCR= 142.0 mOhm	1	\$0.16	 SRN6045 64 mm ²
7.	Renale	Vishay-Dale	CRCW040210K0FKED Series= CRCW..e3	Res= 10.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
8.	Rfb1	Vishay-Dale	CRCW040210K0FKED Series= CRCW..e3	Res= 10.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
9.	Rfb2	Vishay-Dale	CRCW040227K4FKED Series= CRCW..e3	Res= 27.4 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
10.	U1	Texas Instruments	LM2734YMK/NOPB	Switcher	1	\$0.95	 MK06A 11 mm ²

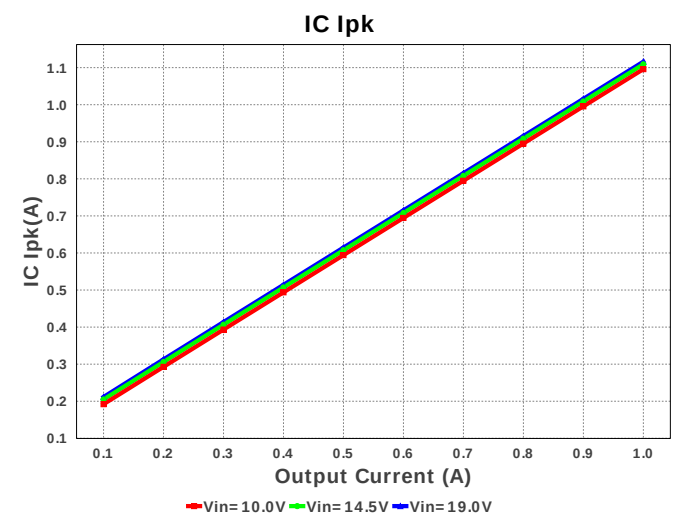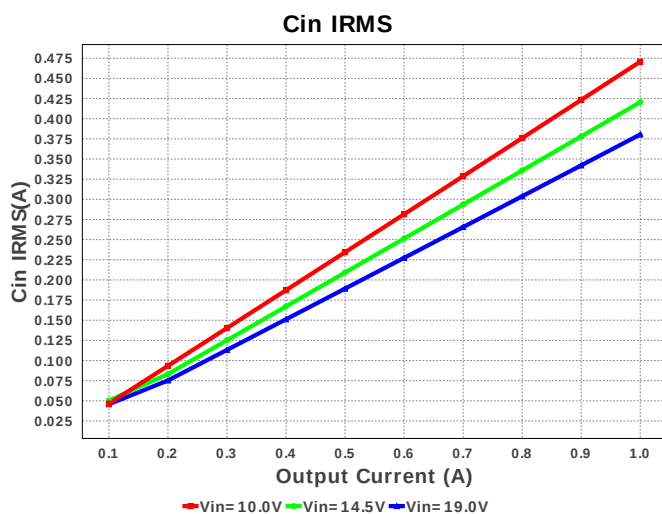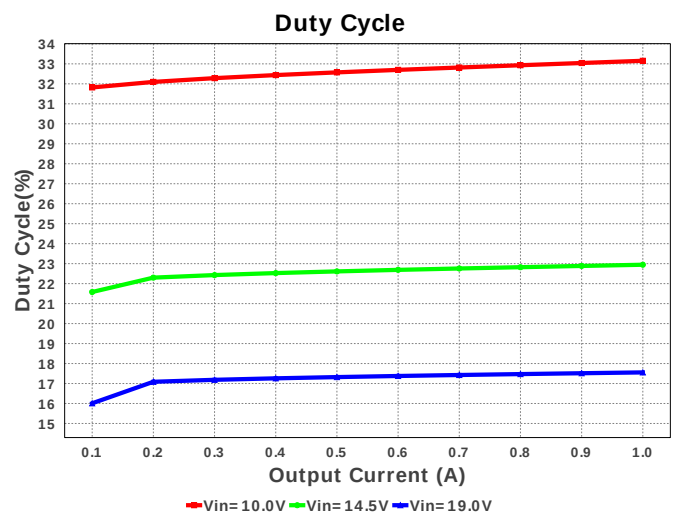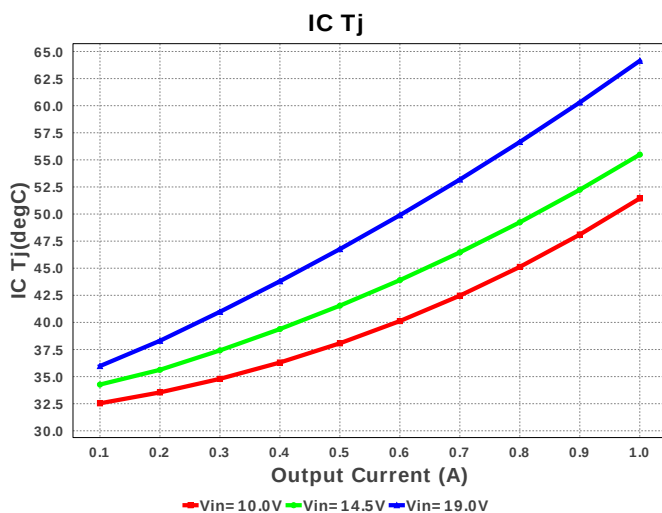

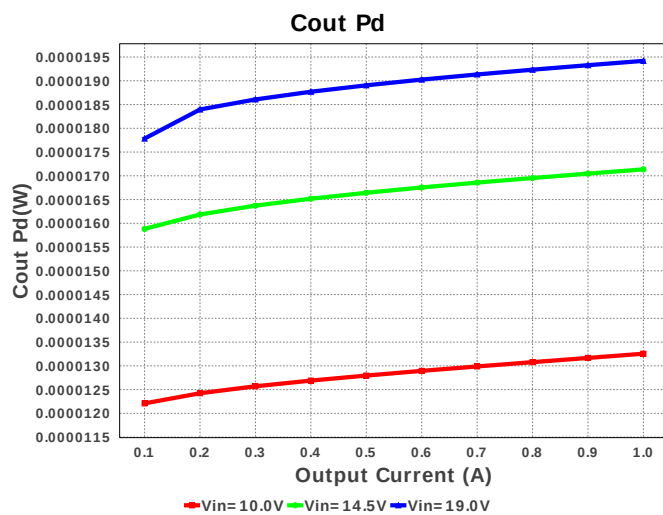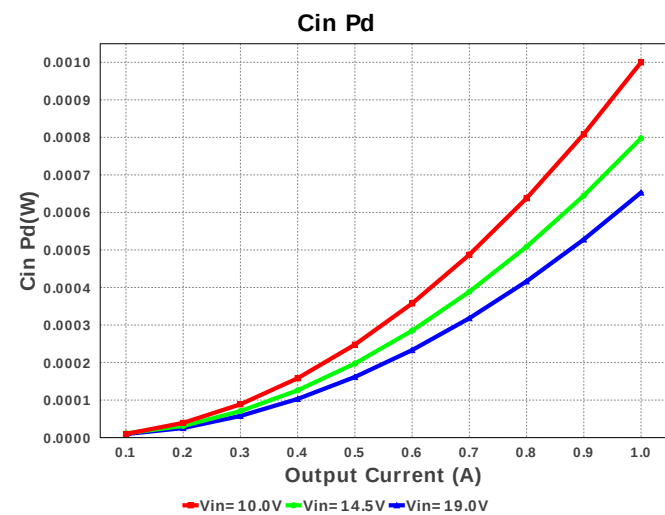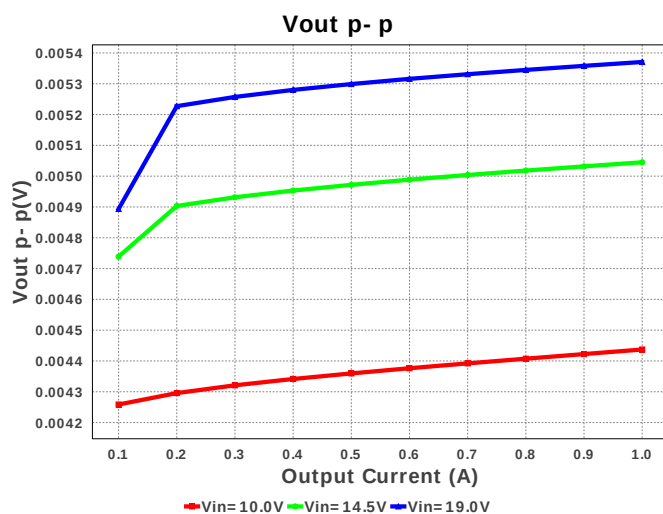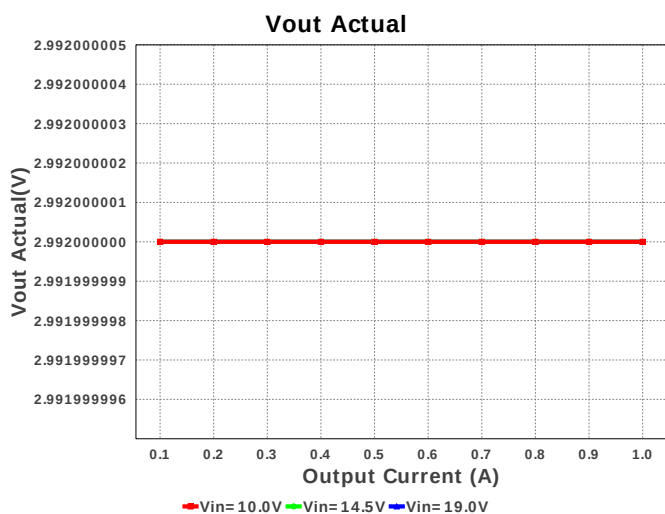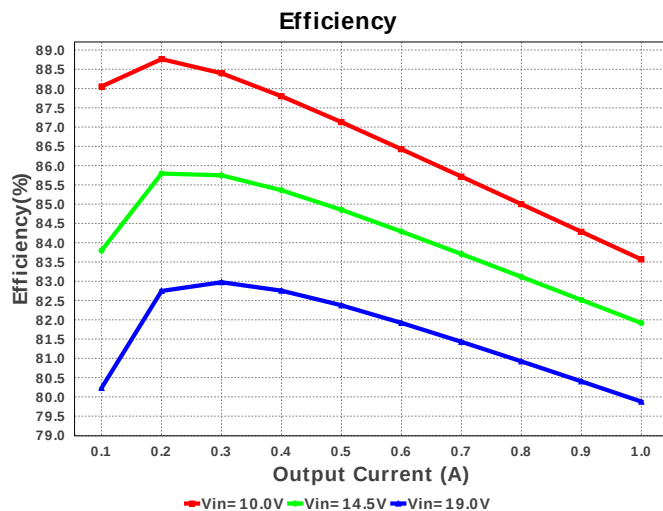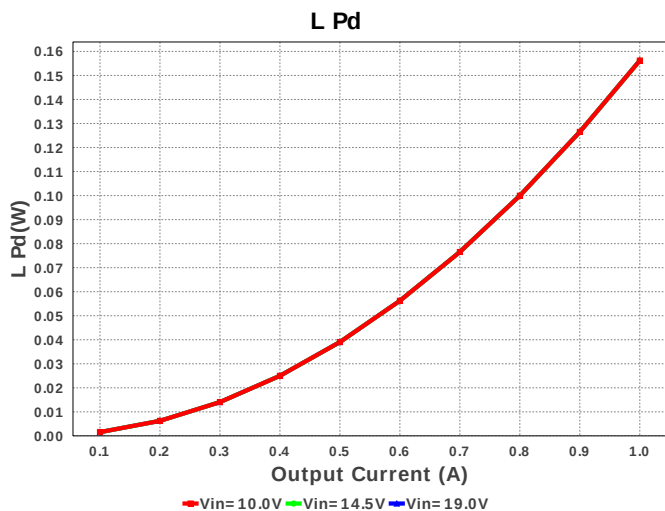

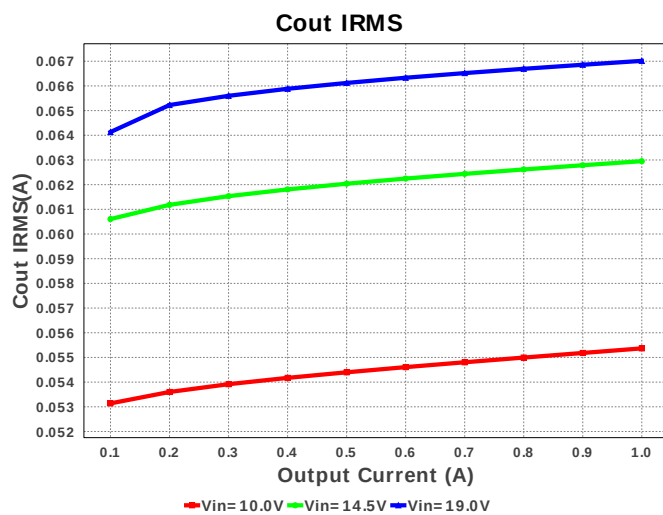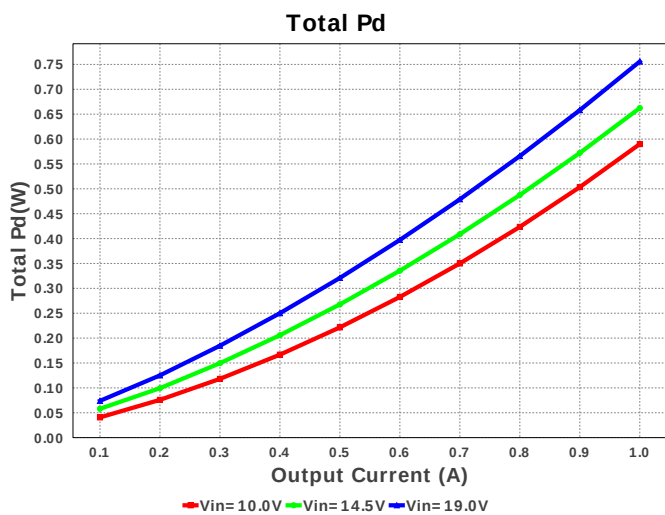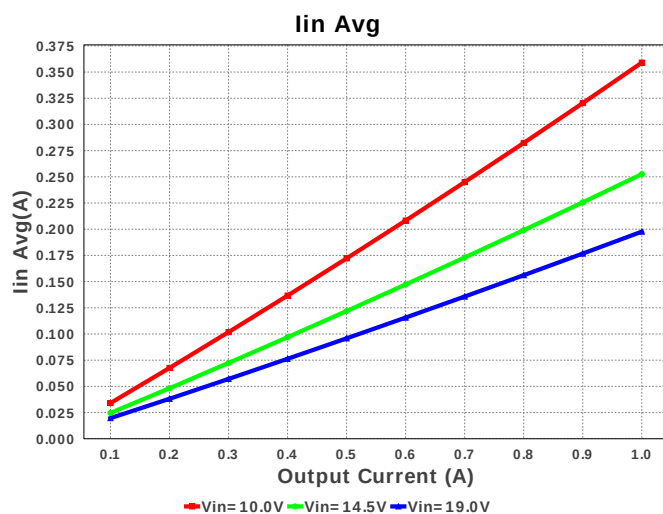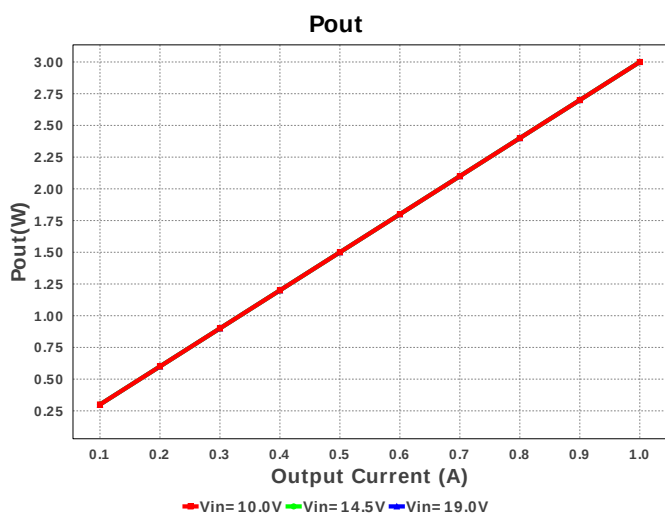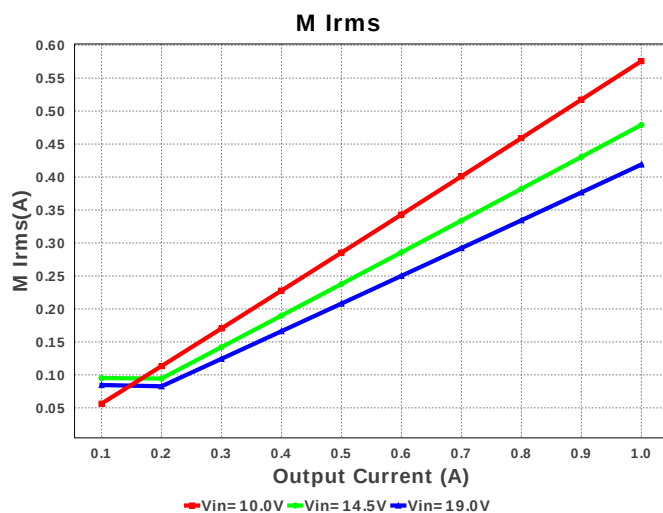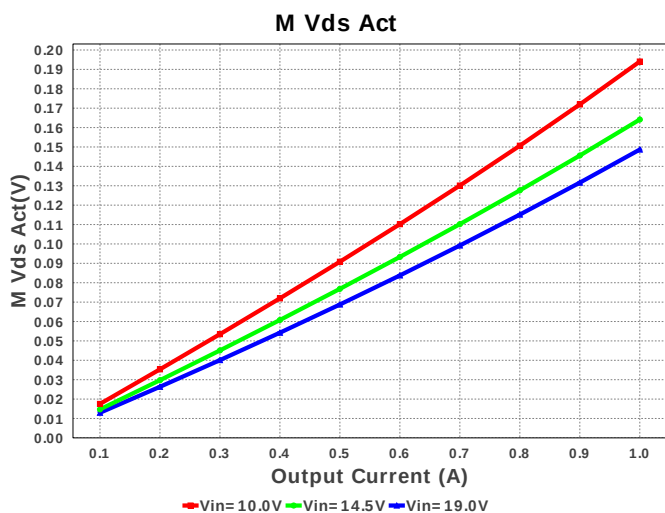

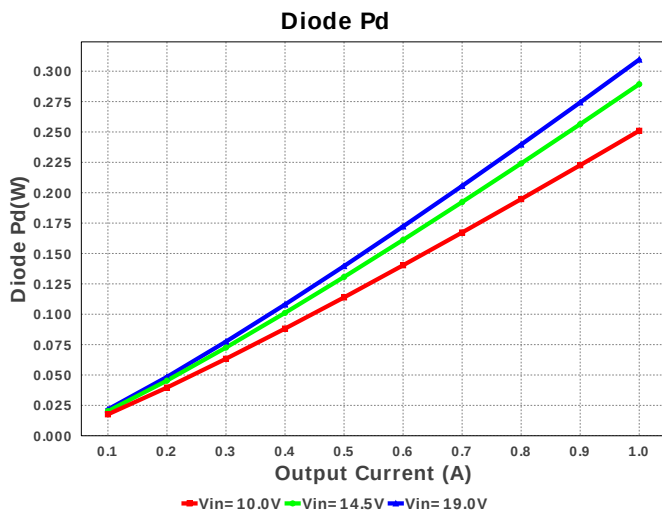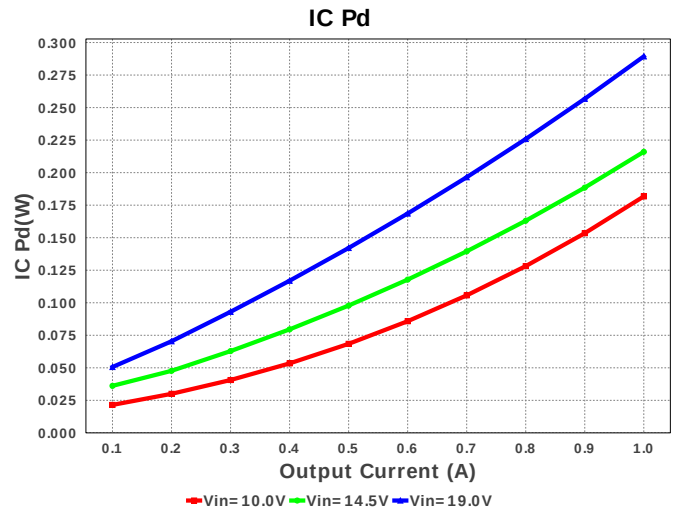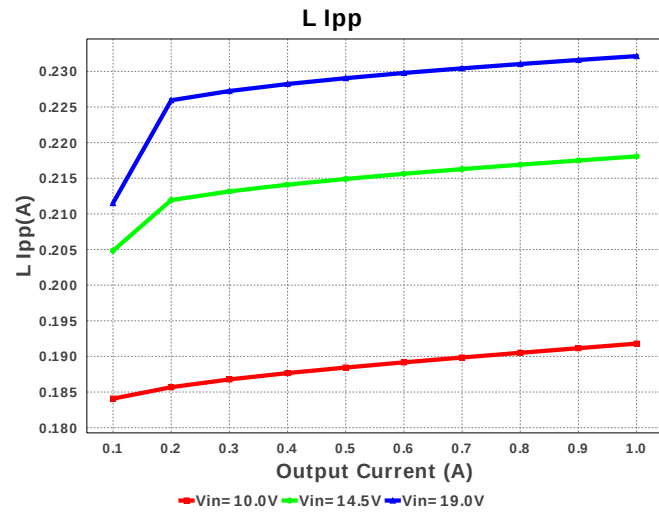

Operating Values

#	Name	Value	Category	Description
1.	Cin IRMS	380.555 mA	Current	Input capacitor RMS ripple current
2.	Cout IRMS	67.064 mA	Current	Output capacitor RMS ripple current
3.	IC Ipk	1.116 A	Current	Peak switch current in IC
4.	Iin Avg	197.8 mA	Current	Average input current
5.	L Ipp	232.32 mA	Current	Peak-to-peak inductor ripple current
6.	M Irms	419.153 mA	Current	MOSFET RMS current
7.	BOM Count	10	General	Total Design BOM count
8.	FootPrint	183.0 mm ²	General	Total Foot Print Area of BOM components
9.	Frequency	550.0 kHz	General	Switching frequency
10.	IC Tolerance	16.0 mV	General	IC Feedback Tolerance
11.	M Vds Act	148.718 mV	General	
12.	Pout	3.0 W	General	Total output power
13.	Total BOM	\$1.37	General	Total BOM Cost
14.	Vout Actual	2.992 V	Op_Point	Vout Actual calculated based on selected voltage divider resistors
15.	Duty Cycle	17.569 %	Op_point	Duty cycle
16.	Efficiency	79.825 %	Op_point	Steady state efficiency
17.	IC Tj	64.147 degC	Op_point	IC junction temperature
18.	ICThetaJA	118.0 degC/W	Op_point	IC junction-to-ambient thermal resistance
19.	IOUT_OP	1.0 A	Op_point	Iout operating point
20.	VIN_OP	19.0 V	Op_point	Vin operating point
21.	Vout p-p	5.375 mV	Op_point	Peak-to-peak output ripple voltage
22.	Cin Pd	653.438 μW	Power	Input capacitor power dissipation
23.	Cout Pd	19.447 μW	Power	Output capacitor power dissipation
24.	Diode Pd	311.962 mW	Power	Diode power dissipation
25.	IC Pd	289.386 mW	Power	IC power dissipation
26.	L Pd	156.2 mW	Power	Inductor power dissipation
27.	Total Pd	758.217 mW	Power	Total Power Dissipation
28.	Vout Tolerance	3.51 %		Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable

Design Inputs

#	Name	Value	Description
1.	Iout	1.0	Maximum Output Current
2.	VinMax	19.0	Maximum input voltage
3.	VinMin	10.0	Minimum input voltage
4.	Vout	3.0	Output Voltage
5.	base_pn	LM2734Y	Texas Instruments Base Part Number
6.	source	DC	Input Source Type
7.	ta	30.0	Ambient temperature

Design Assistance

1. LM2734Y Product Folder : <http://www.ti.com/product/LM2734> : contains the data sheet and other resources.

Texas Instruments' WEBENCH simulation tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Simulations are created using Texas Instruments' published specifications as well as the published specifications of other device manufacturers. While Texas Instruments does update this information periodically, this information may not be current at the time the simulation is built. Texas Instruments does not warrant the accuracy or completeness of the specifications or any information contained therein. Texas Instruments does not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. Texas Instruments does not warrant that the designs are production worthy.

You should completely validate and test your design implementation to confirm the system functionality for your application prior to production.

Use of Texas Instruments' WEBENCH simulation tools is subject to [Texas Instruments' Site Terms and Conditions of Use](#). Prototype boards based on WEBENCH created designs are provided AS IS without warranty of any kind for evaluation and testing purposes and are subject to the terms of the [Evaluation License Agreement](#).