
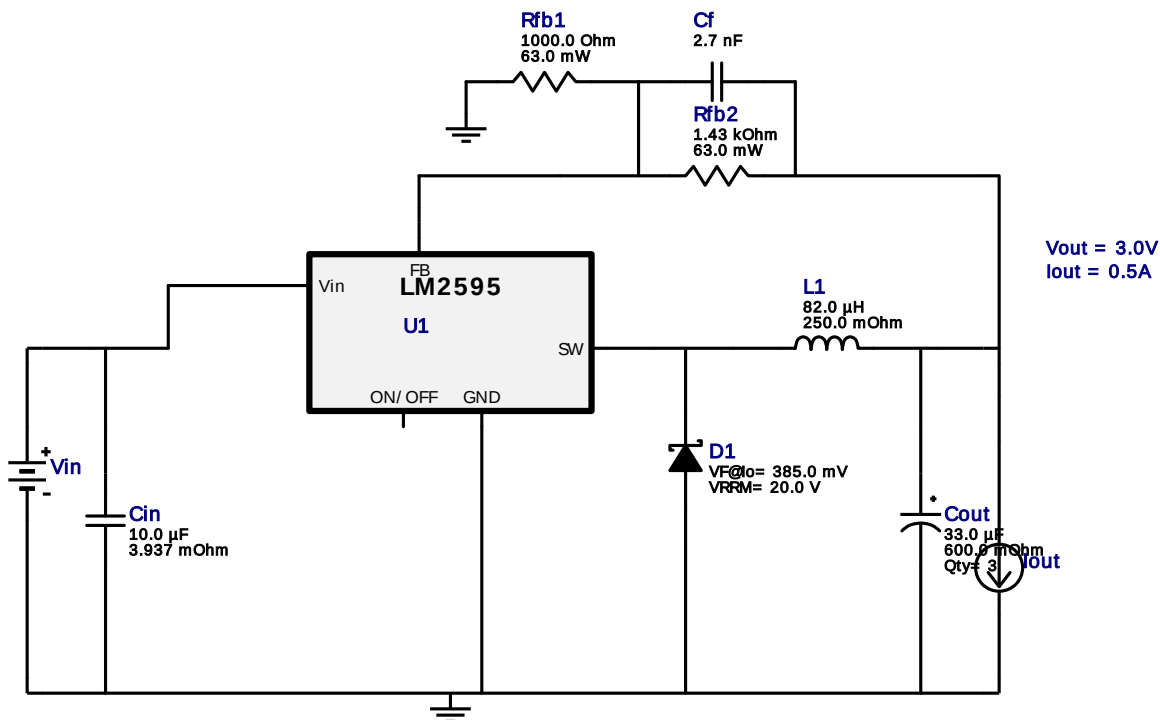



WEBENCH® Design Report




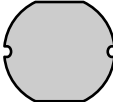
Design : 4742013/174 LM2595SX-ADJ/NOPB
LM2595SX-ADJ/NOPB 4.5V-5.5V to 3.00V @ 0.5A















Electrical BOM


#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	Cf	Yageo America	CC0805KRX7R9BB272 Series= X7R	Cap= 2.7 nF VDC= 50.0 V IRMS= 0.0 A	1	\$0.01	 0805 7 mm ²
2.	Cin	MuRata	GRM219R61A106KE44D Series= X5R	Cap= 10.0 uF ESR= 3.937 mOhm VDC= 10.0 V IRMS= 2.7713 A	1	\$0.03	 0805 7 mm ²
3.	Cout	AVX	TPSA336K006R0600 Series= TPS	Cap= 33.0 uF ESR= 600.0 mOhm VDC= 6.3 V IRMS= 318.0 mA	3	\$0.13	 3216-18 11 mm ²
4.	D1	ON Semiconductor	MBR0520LT1G	Vf@Io= 385.0 mV VRRM= 20.0 V	1	\$0.06	 SOD-123 13 mm ²
5.	L1	NIC Components	NPI105C820MTRF	L= 82.0 uH DCR= 250.0 mOhm	1	\$0.11	 IND_NPI105C 141 mm ²
6.	Rfb1	Vishay-Dale	CRCW04021K00FKED Series= CRCW..e3	Res= 1000.0 Ohm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
7.	Rfb2	Vishay-Dale	CRCW04021K43FKED Series= CRCW..e3	Res= 1.43 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
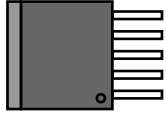
#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
8.	U1	Texas Instruments	LM2595SX-ADJ/NOPB	Switcher	1	\$1.60	 TS5B 199 mm ²

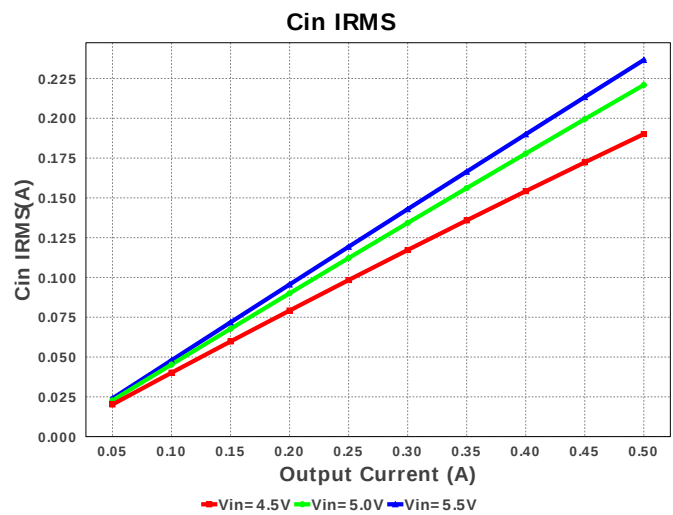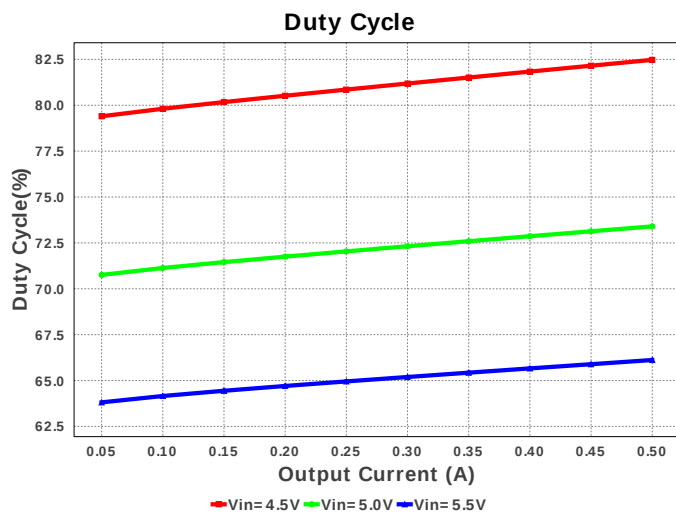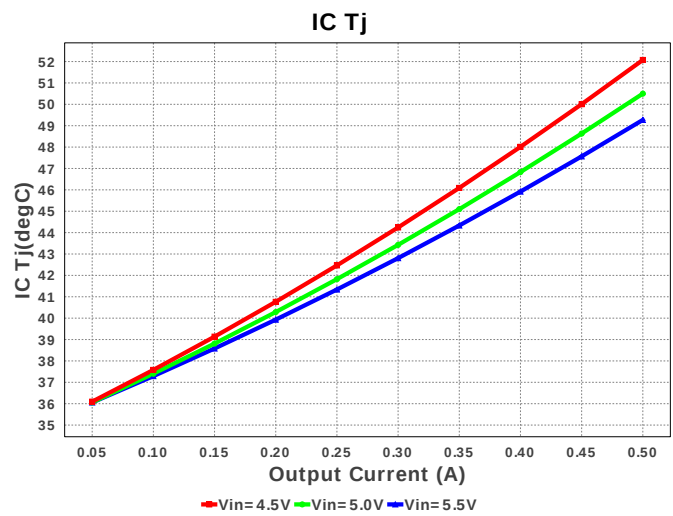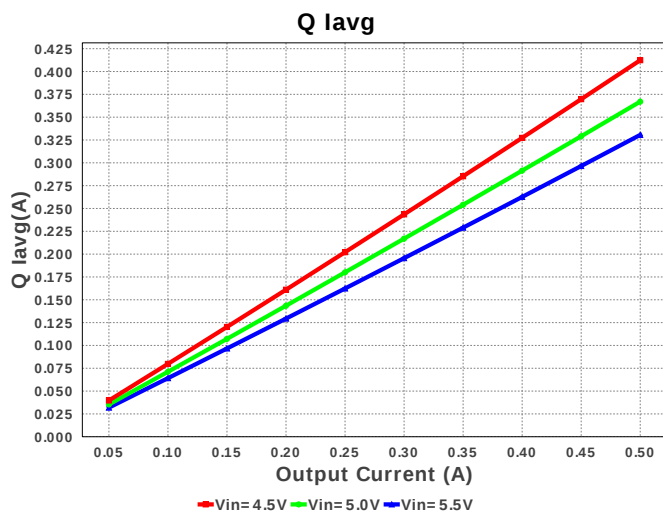

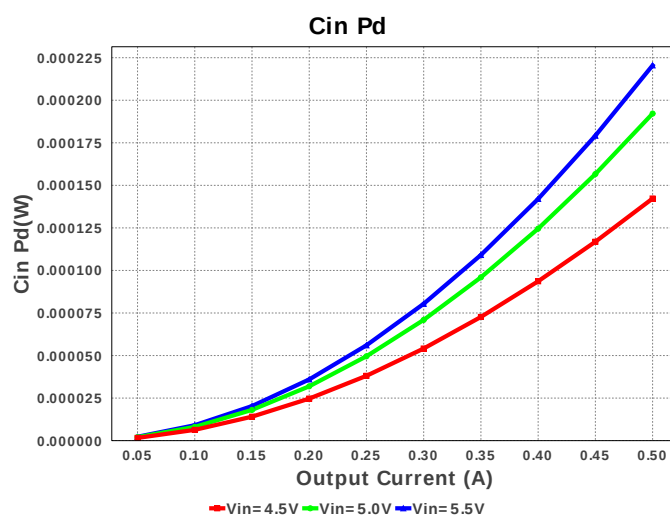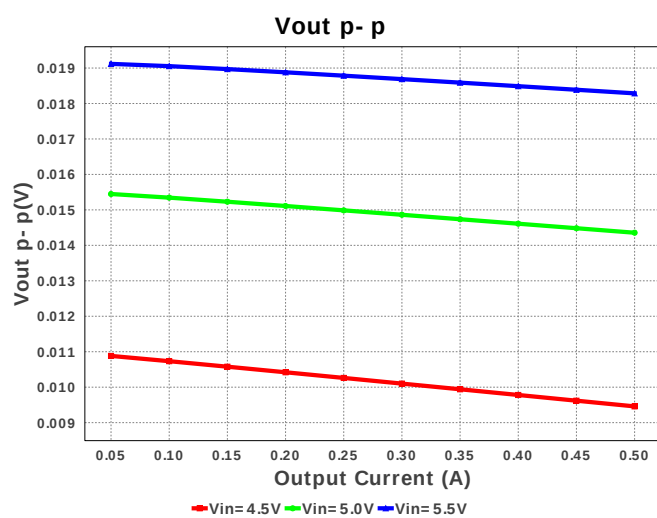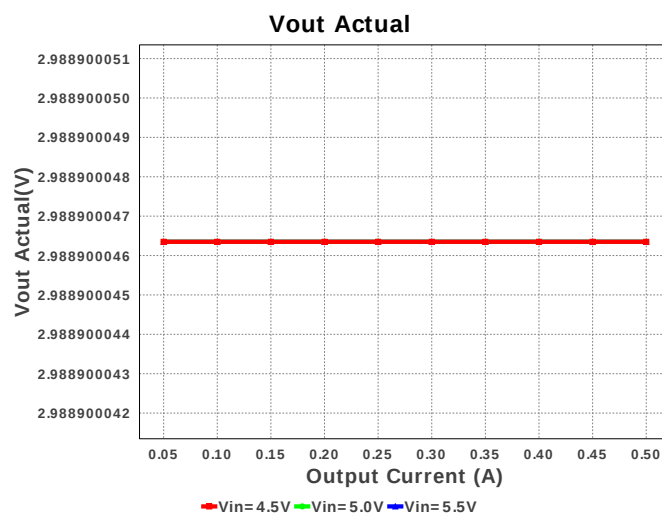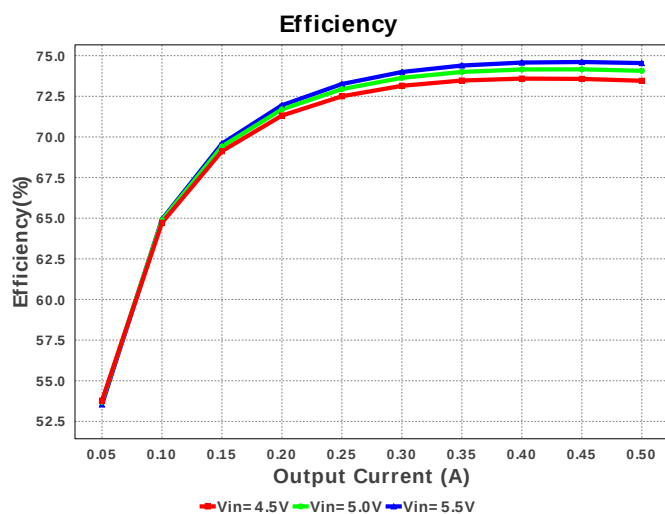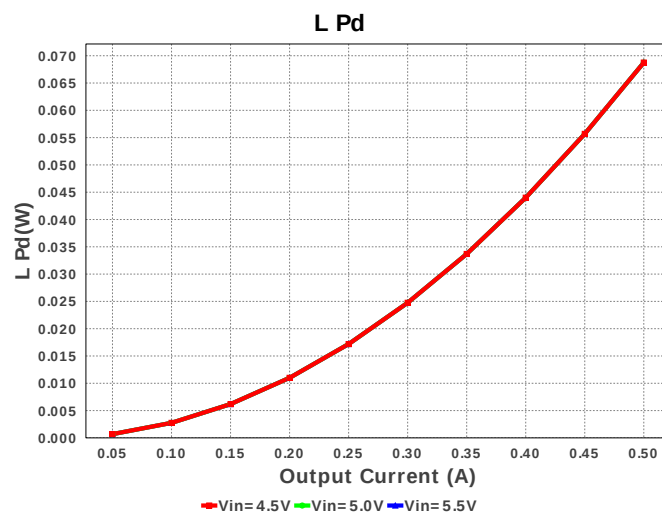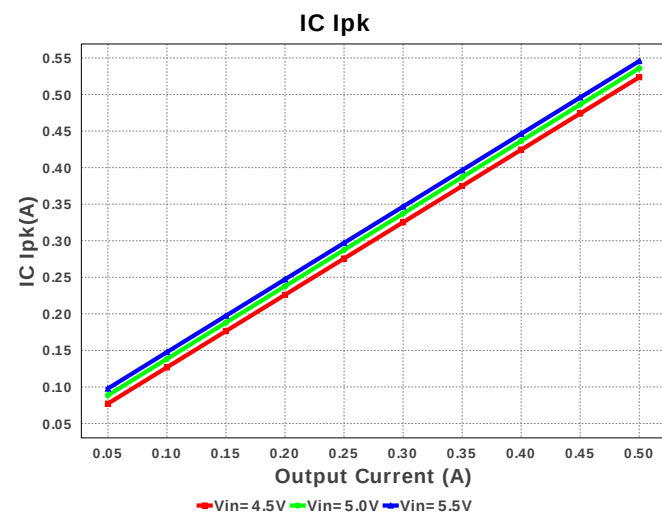

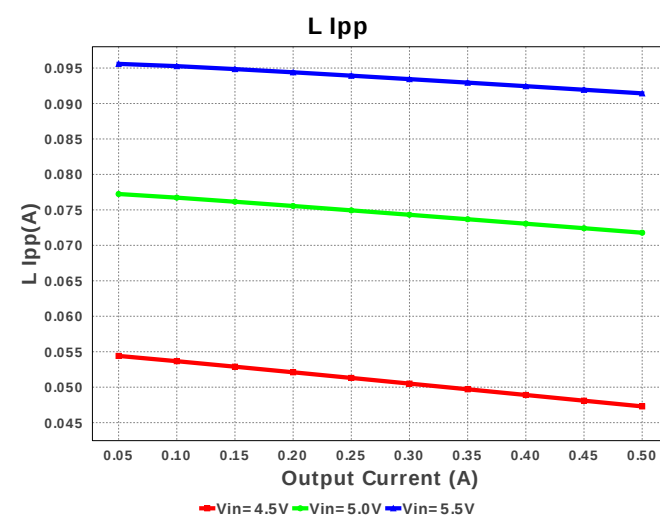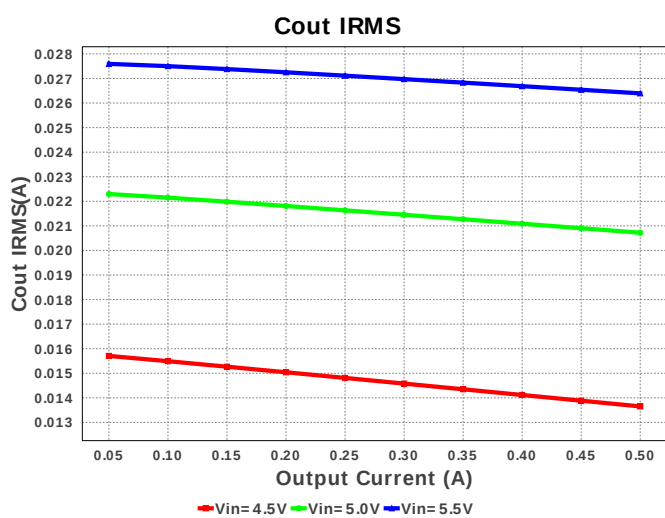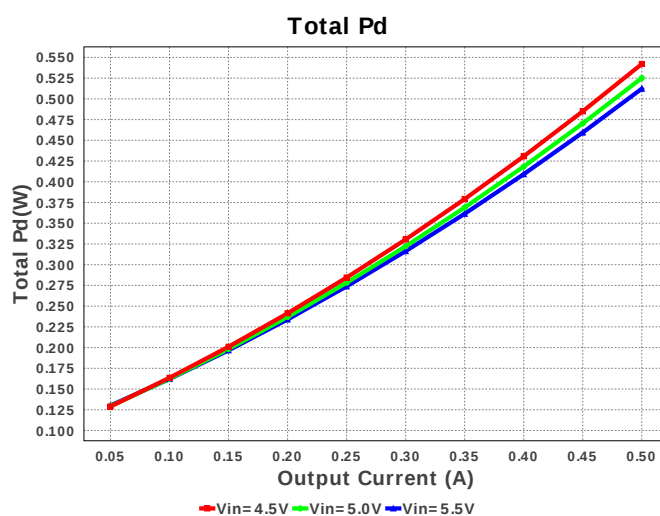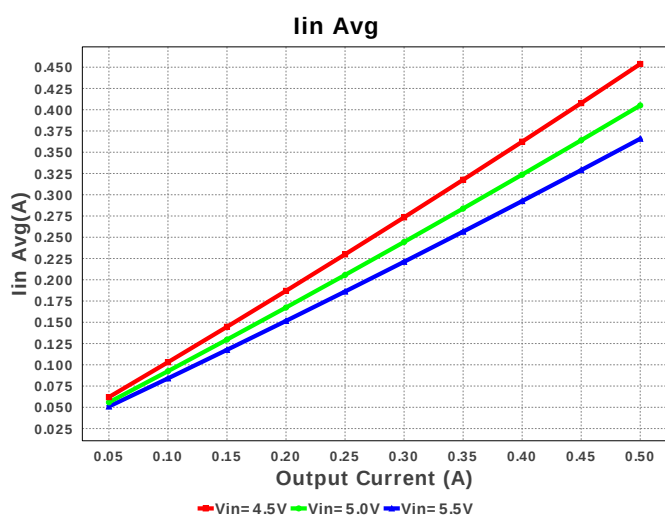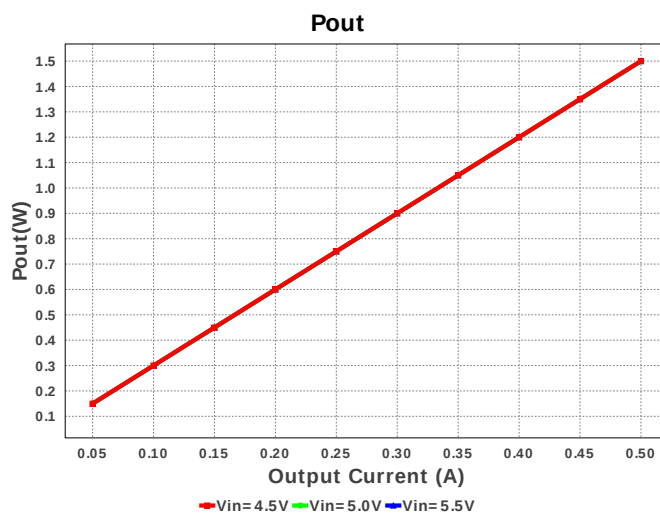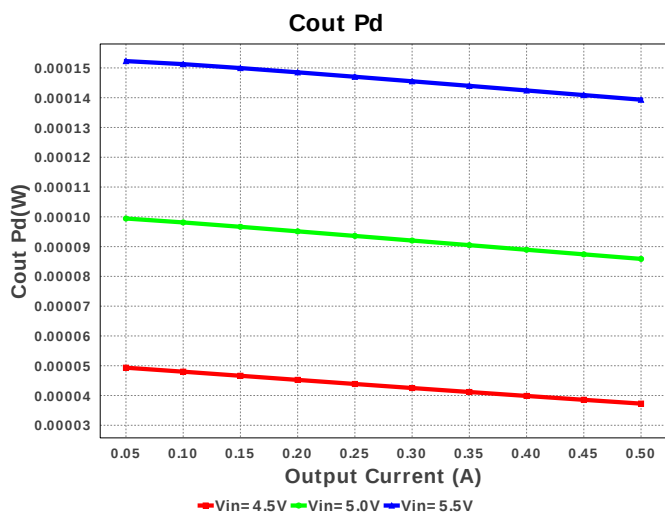

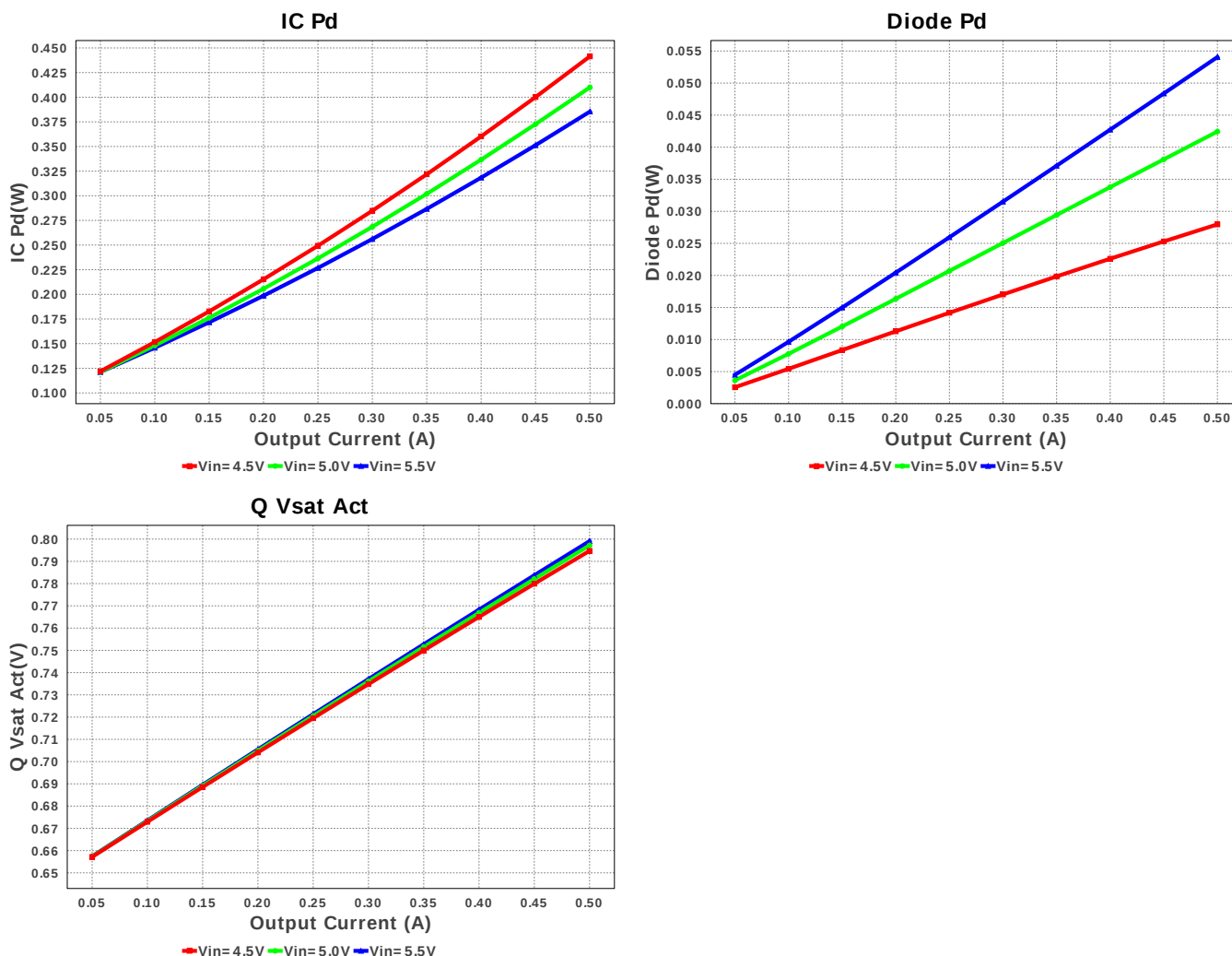

Operating Values

#	Name	Value	Category	Description
1.	Cin IRMS	235.902 mA	Current	Input capacitor RMS ripple current
2.	Cout IRMS	26.571 mA	Current	Output capacitor RMS ripple current
3.	IC Ipk	546.023 mA	Current	Peak switch current in IC
4.	Iin Avg	368.14 mA	Current	Average input current
5.	L Ipp	92.046 mA	Current	Peak-to-peak inductor ripple current
6.	Q Iavg	332.767 mA	Current	Q Iavg
7.	BOM Count	10	General	Total Design BOM count
8.	FootPrint	406.0 mm ²	General	Total Foot Print Area of BOM components
9.	Frequency	150.0 kHz	General	Switching frequency
10.	IC Tolerance	0.0 V	General	IC Feedback Tolerance
11.	Pout	1.5 W	General	Total output power
12.	Q Vsat Act	798.853 mV	General	Q Vsat
13.	Total BOM	\$2.22	General	Total BOM Cost
14.	Vout Actual	2.989 V	Op_Point	Vout Actual calculated based on selected voltage divider resistors
15.	Cross Freq	6.31 kHz	Op_point	Bode plot crossover frequency
16.	Duty Cycle	66.553 %	Op_point	Duty cycle
17.	Efficiency	74.083 %	Op_point	Steady state efficiency
18.	IC Tj	49.377 degC	Op_point	IC junction temperature
19.	ICThetaJA	50.0 degC/W	Op_point	IC junction-to-ambient thermal resistance
20.	IOUT_OP	500.0 mA	Op_point	Iout operating point
21.	Phase Marg	47.37 deg	Op_point	Bode Plot Phase Margin
22.	VIN_OP	5.5 V	Op_point	Vin operating point
23.	Vout p-p	18.409 mV	Op_point	Peak-to-peak output ripple voltage
24.	Cin Pd	219.093 μW	Power	Input capacitor power dissipation
25.	Cout Pd	141.209 μW	Power	Output capacitor power dissipation
26.	Diode Pd	64.385 mW	Power	Diode power dissipation
27.	IC Pd	387.545 mW	Power	IC power dissipation
28.	L Pd	68.75 mW	Power	Inductor power dissipation
29.	Total Pd	524.76 mW	Power	Total Power Dissipation
30.	Vout Tolerance	1.189 %		Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable

Design Inputs

#	Name	Value	Description
1.	Iout	500.0 m	Maximum Output Current
2.	VinMax	5.5	Maximum input voltage
3.	VinMin	4.5	Minimum input voltage
4.	Vout	3.0	Output Voltage
5.	base_pn	LM2595	Base Product Number
6.	source	DC	Input Source Type
7.	Ta	30.0	Ambient temperature

Design Assistance

1. **LM2595** Product Folder : <http://www.ti.com/product/LM2595> : contains the data sheet and other resources.

Texas Instruments' WEBENCH simulation tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Simulations are created using Texas Instruments' published specifications as well as the published specifications of other device manufacturers. While Texas Instruments does update this information periodically, this information may not be current at the time the simulation is built. Texas Instruments does not warrant the accuracy or completeness of the specifications or any information contained therein. Texas Instruments does not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. Texas Instruments does not warrant that the designs are production worthy.

You should completely validate and test your design implementation to confirm the system functionality for your application prior to production.

Use of Texas Instruments' WEBENCH simulation tools is subject to [Texas Instruments' Site Terms and Conditions of Use](#). Prototype boards based on WEBENCH created designs are provided AS IS without warranty of any kind for evaluation and testing purposes and are subject to the terms of the [Evaluation License Agreement](#).