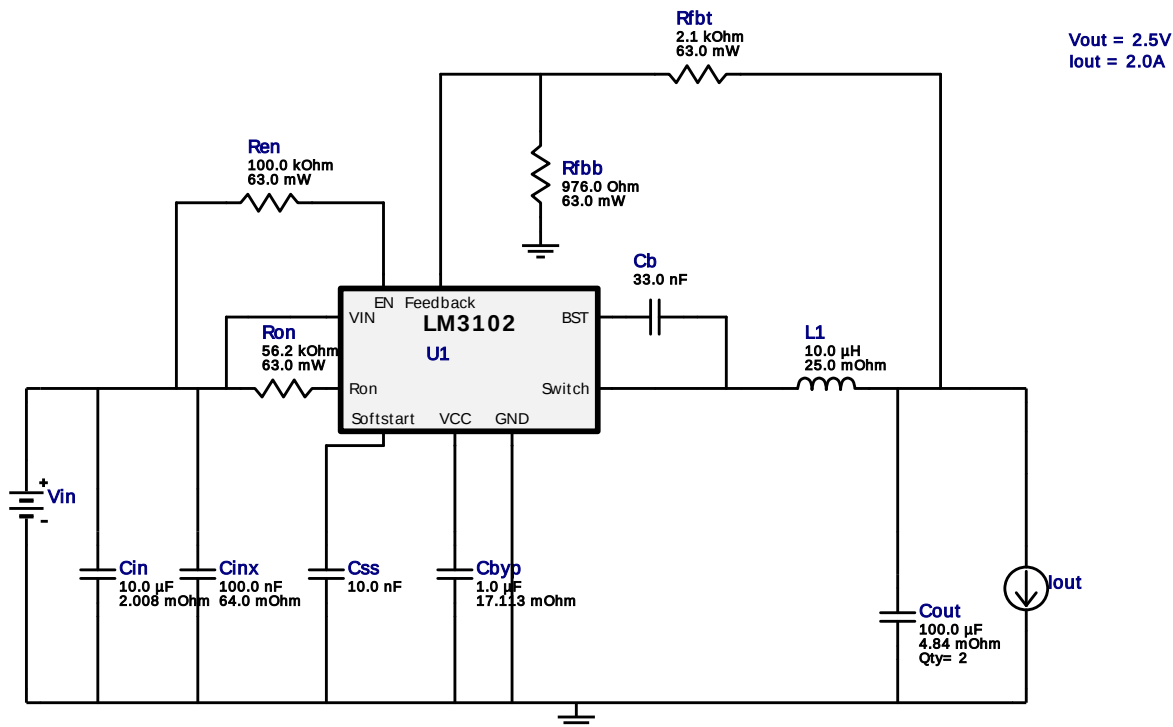


WEBENCH® Design Report


Design : 4742013/200 LM3102MHX/NOPB
LM3102MHX/NOPB 21.0V-25.0V to 2.50V @ 2.0A











1. This regulator device is qualified for Automotive applications. All passives and other components selected in this design may not be qualified for Automotive applications. The user is required to verify that all components in the design meet the qualification and safety requirements for their specific application. View WEBENCH(R) Disclaimer.







Electrical BOM


#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	Cb	MuRata	GRM155R71E333KA88D Series= X7R	Cap= 33.0 nF VDC= 25.0 V IRMS= 0.0 A	1	\$0.01	0402 3 mm ²
2.	Cbyp	MuRata	GRM188R61E105KA12D Series= X5R	Cap= 1.0 uF ESR= 17.113 mOhm VDC= 25.0 V IRMS= 979.39 mA	1	\$0.01	0603 5 mm ²
3.	Cin	MuRata	GRM32ER7YA106KA12L Series= X7R	Cap= 10.0 uF ESR= 2.008 mOhm VDC= 35.0 V IRMS= 4.6772 A	1	\$0.22	1210_280 15 mm ²
4.	Cinx	Kemet	C0805C104K5RACTU Series= X7R	Cap= 100.0 nF ESR= 64.0 mOhm VDC= 50.0 V IRMS= 1.64 A	1	\$0.01	0805 7 mm ²
5.	Cout	MuRata	GRM31CD80G107ME39L Series= X6T	Cap= 100.0 uF ESR= 4.84 mOhm VDC= 4.0 V IRMS= 4.3381 A	2	\$0.14	1206_190 11 mm ²
6.	Css	MuRata	GRM155R71E103KA01D Series= X7R	Cap= 10.0 nF VDC= 25.0 V IRMS= 0.0 A	1	\$0.01	0402 3 mm ²
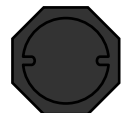
#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
7.	L1	Bourns	SRU1038-100Y	L= 10.0 μ H DCR= 25.0 mOhm	1	\$0.33	 SRU1038 144 mm ²
8.	Ren	Vishay-Dale	CRCW0402100KFKED Series= CRCW..e3	Res= 100.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
9.	Rfbb	Vishay-Dale	CRCW0402976RFKED Series= CRCW..e3	Res= 976.0 Ohm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
10.	Rfbt	Vishay-Dale	CRCW04022K10FKED Series= CRCW..e3	Res= 2.1 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
11.	Ron	Vishay-Dale	CRCW040256K2FKED Series= CRCW..e3	Res= 56.2 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
12.	U1	Texas Instruments	LM3102MHX/NOPB	Switcher	1	\$2.15	 MXA20A 71 mm ²

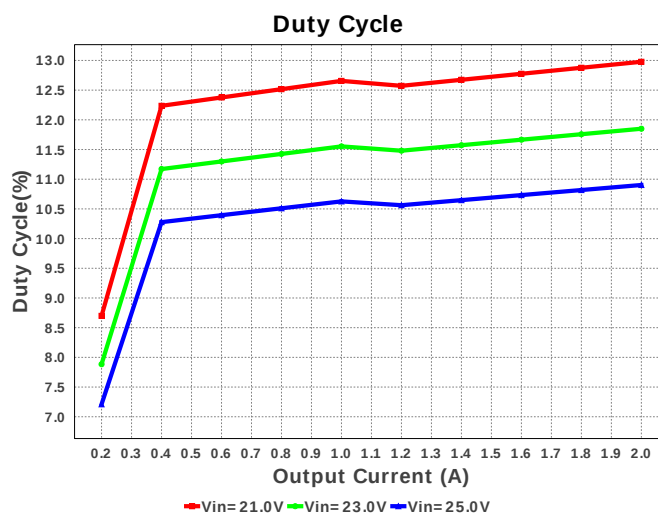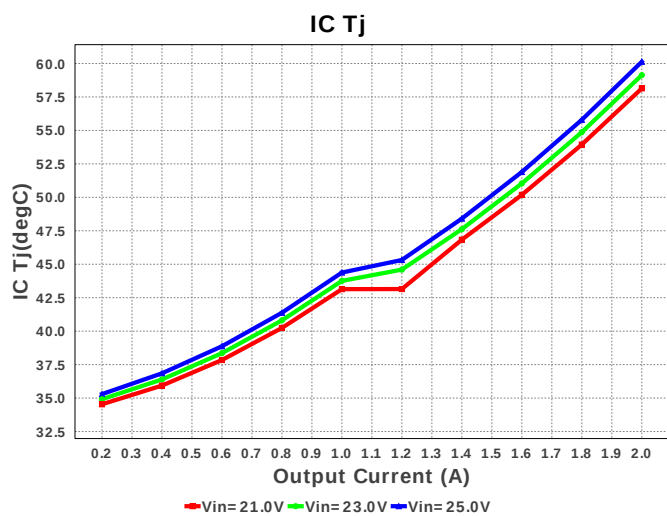

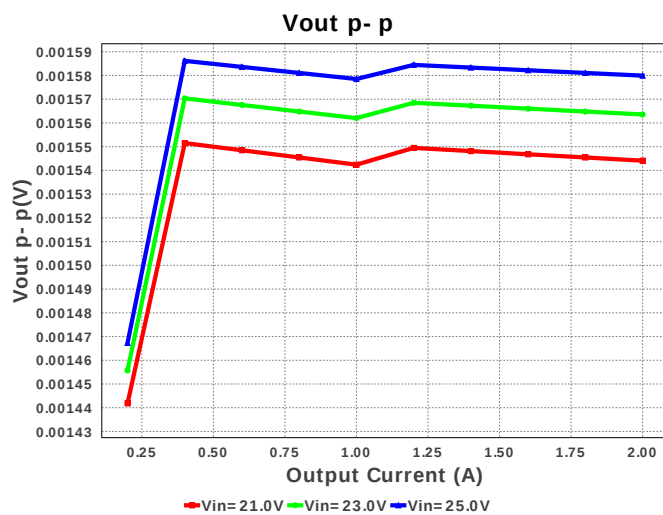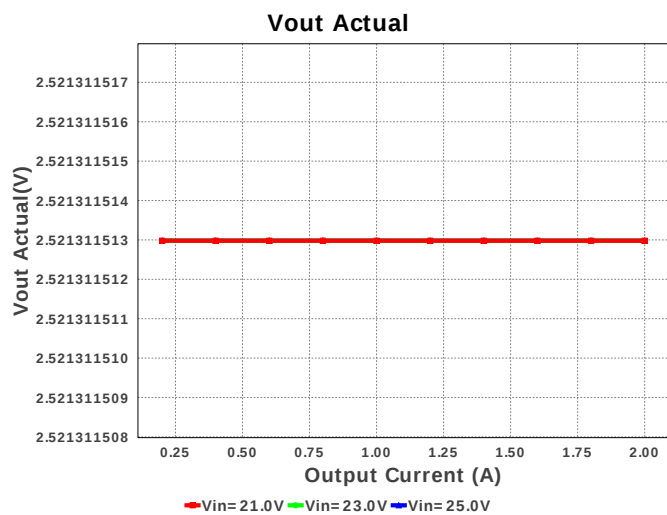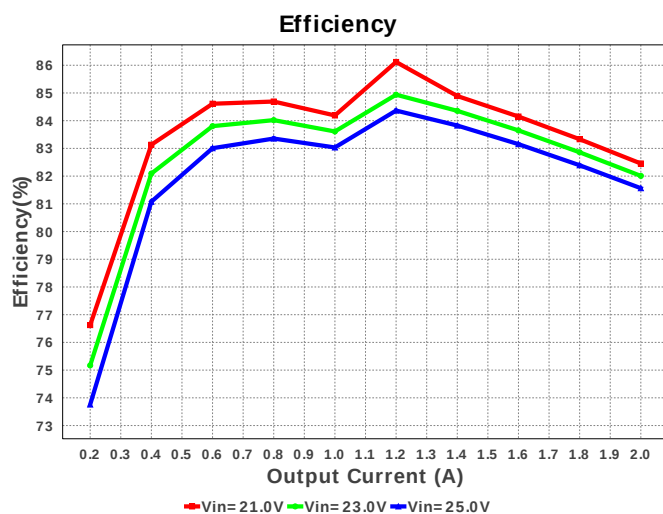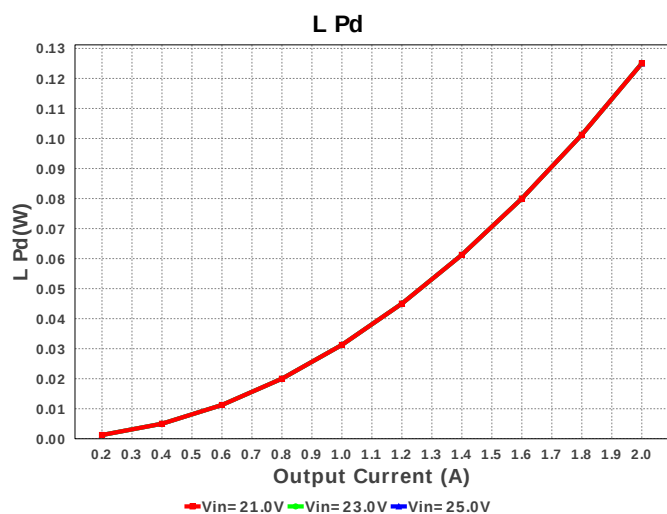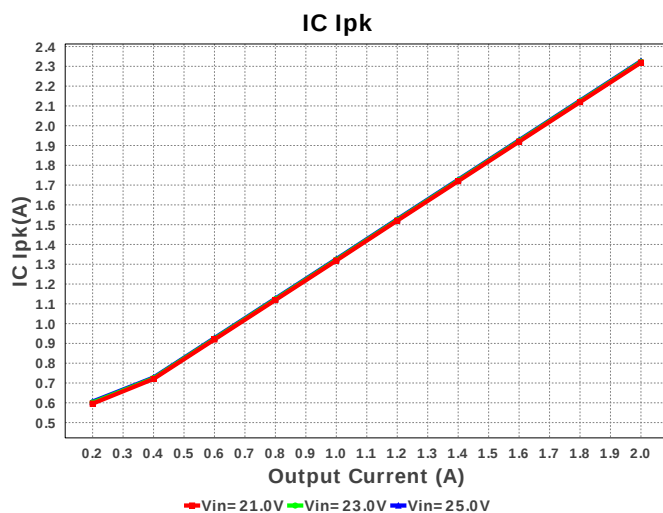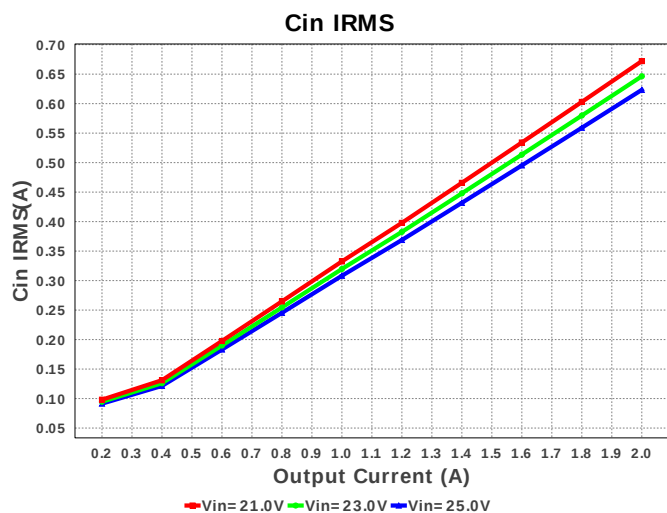

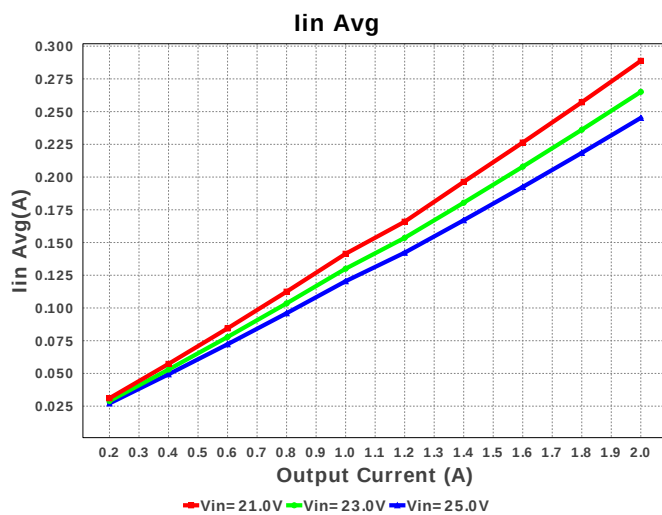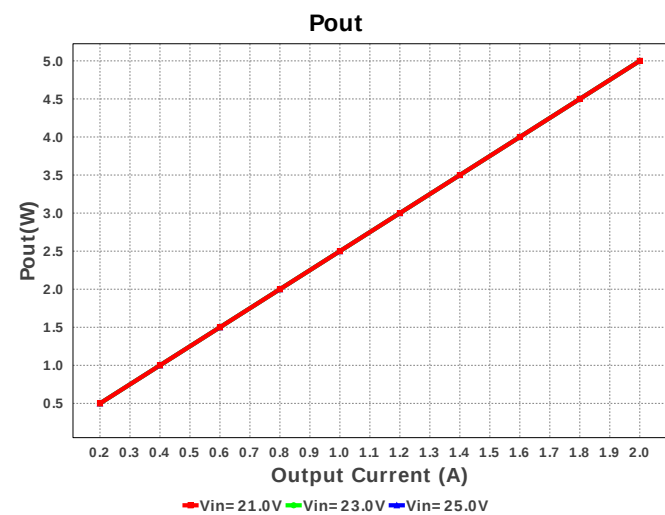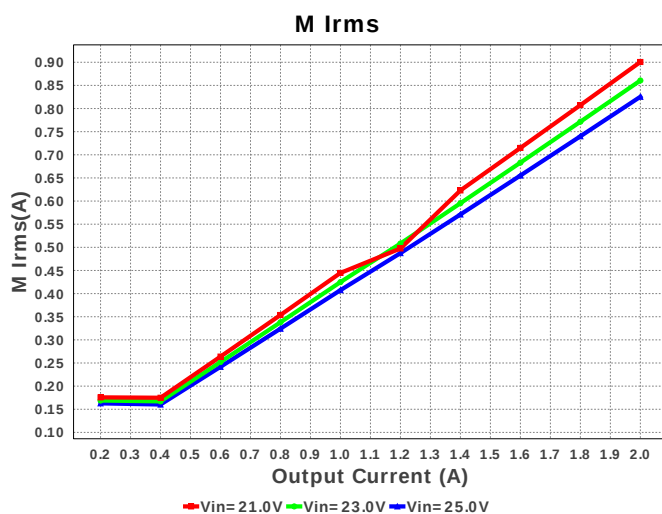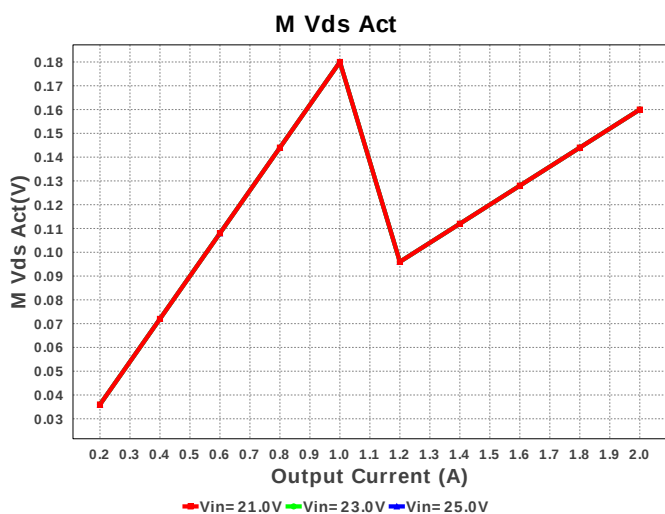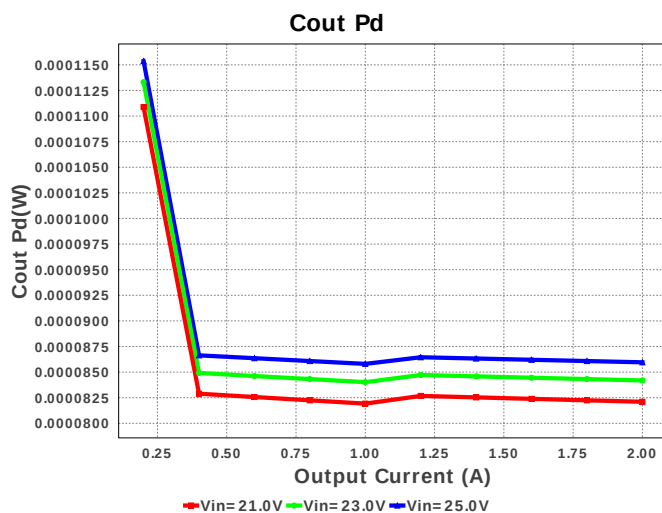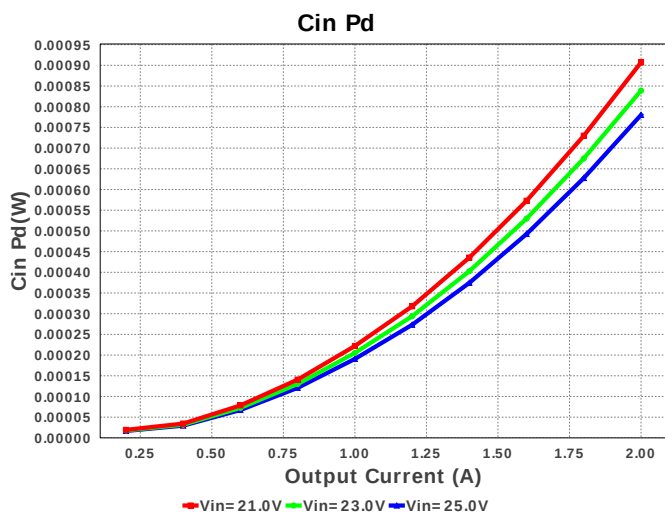

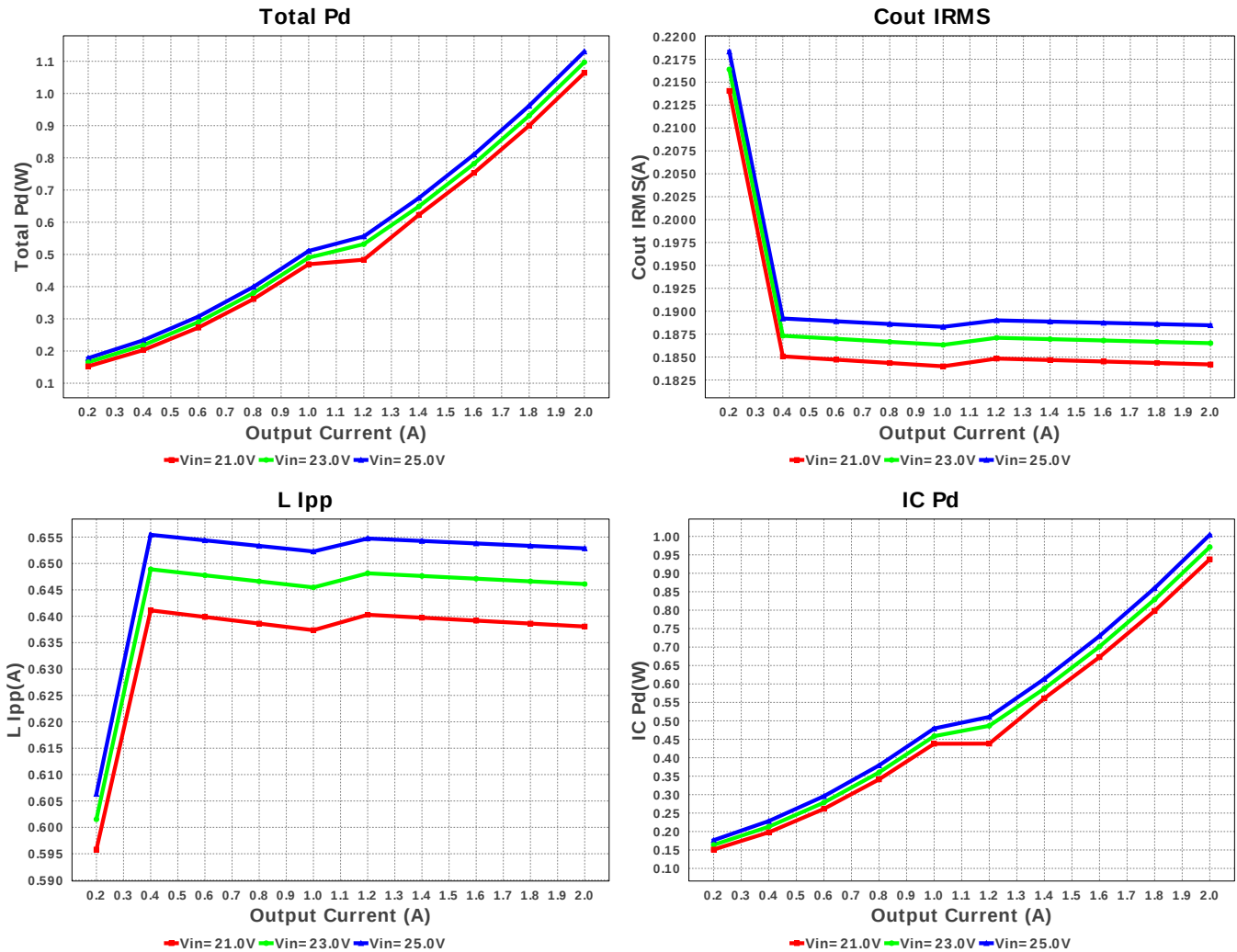

Operating Values

#	Name	Value	Category	Description
1.	Cin IRMS	623.342 mA	Current	Input capacitor RMS ripple current
2.	Cout IRMS	188.466 mA	Current	Output capacitor RMS ripple current
3.	IC Ipk	2.326 A	Current	Peak switch current in IC
4.	Iin Avg	246.05 mA	Current	Average input current
5.	L Ipp	652.86 mA	Current	Peak-to-peak inductor ripple current
6.	M Irms	825.475 mA	Current	MOSFET RMS current
7.	BOM Count	13	General	Total Design BOM count
8.	FootPrint	281.0 mm ²	General	Total Foot Print Area of BOM components
9.	Frequency	342.185 kHz	General	Switching frequency
10.	IC Tolerance	16.0 mV	General	IC Feedback Tolerance
11.	M Vds Act	160.0 mV	General	Voltage drop across the MosFET
12.	Pout	5.0 W	General	Total output power
13.	Total BOM	\$3.06	General	Total BOM Cost
14.	Vout Actual	2.521 V	Op_Point	Vout Actual calculated based on selected voltage divider resistors
15.	Vout OP	2.5 V	Op_Point	Operational Output Voltage
16.	Duty Cycle	10.903 %	Op_point	Duty cycle
17.	Efficiency	81.284 %	Op_point	Steady state efficiency
18.	IC Tj	71.015 degC	Op_point	IC junction temperature
19.	ICThetaJA	40.0 degC/W	Op_point	IC junction-to-ambient thermal resistance
20.	IOUT_OP	2.0 A	Op_point	Iout operating point
21.	VIN_OP	25.0 V	Op_point	Vin operating point
22.	Vout p-p	1.58 mV	Op_point	Peak-to-peak output ripple voltage
23.	Cin Pd	780.219 μW	Power	Input capacitor power dissipation
24.	Cout Pd	85.957 μW	Power	Output capacitor power dissipation
25.	IC Pd	1.025 W	Power	IC power dissipation
26.	L Pd	125.0 mW	Power	Inductor power dissipation
27.	Total Pd	1.151 W	Power	Total Power Dissipation
28.	Vout Tolerance	3.407 %		Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable

Design Inputs

#	Name	Value	Description
1.	Iout	2.0	Maximum Output Current
2.	VinMax	25.0	Maximum input voltage
3.	VinMin	21.0	Minimum input voltage
4.	Vout	2.5	Output Voltage
5.	base_pn	LM3102	Texas Instruments Base Part Number
6.	source	DC	Input Source Type
7.	ta	30.0	Ambient temperature

Design Assistance

1. LM3102 Product Folder : <http://www.ti.com/product/LM3102> : contains the data sheet and other resources.

Texas Instruments' WEBENCH simulation tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Simulations are created using Texas Instruments' published specifications as well as the published specifications of other device manufacturers. While Texas Instruments does update this information periodically, this information may not be current at the time the simulation is built. Texas Instruments does not warrant the accuracy or completeness of the specifications or any information contained therein. Texas Instruments does not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. Texas Instruments does not warrant that the designs are production worthy.

You should completely validate and test your design implementation to confirm the system functionality for your application prior to production.

Use of Texas Instruments' WEBENCH simulation tools is subject to [Texas Instruments' Site Terms and Conditions of Use](#). Prototype boards based on WEBENCH created designs are provided AS IS without warranty of any kind for evaluation and testing purposes and are subject to the terms of the [Evaluation License Agreement](#).