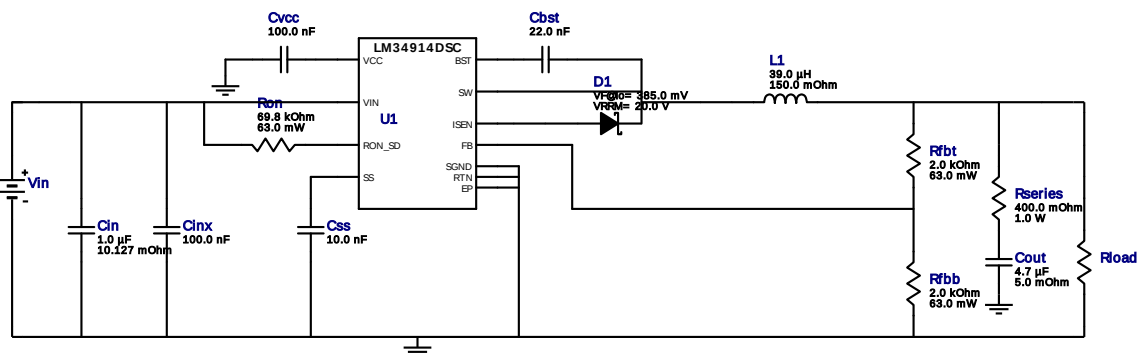














Device = LM34914SD/NOPB
Topology = Buck
Created = 7/24/16 5:36:24 PM
BOM Cost = \$1.89
BOM Count = 13
Total Pd = 0.23W













#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	Cbst	MuRata	GRM033C80J223KE01D Series= X6S	Cap= 22.0 nF VDC= 6.3 V IRMS= 0.0 A	1	\$0.01	 0201 2 mm ²
2.	Cin	MuRata	GRM188R61C105KA93D Series= X5R	Cap= 1.0 uF ESR= 10.127 mOhm VDC= 16.0 V IRMS= 994.63 mA	1	\$0.01	 0603 5 mm ²
3.	Cinx	MuRata	GRM21BR71E104KA01L Series= X7R	Cap= 100.0 nF VDC= 25.0 V IRMS= 0.0 A	1	\$0.01	 0805 7 mm ²
4.	Cout	MuRata	GRM188R60J475KE19D Series= X5R	Cap= 4.7 uF ESR= 5.0 mOhm VDC= 6.3 V IRMS= 2.0 A	1	\$0.01	 0603 5 mm ²
5.	Css	MuRata	GRM155R61C103KA01D Series= X5R	Cap= 10.0 nF VDC= 16.0 V IRMS= 0.0 A	1	\$0.01	 0402 3 mm ²
6.	Cvcc	MuRata	GRM21BR71E104KA01L Series= X7R	Cap= 100.0 nF VDC= 25.0 V IRMS= 0.0 A	1	\$0.01	 0805 7 mm ²
7.	D1	ON Semiconductor	MBR0520LT1G	VF@Io= 385.0 mV VRRM= 20.0 V	1	\$0.06	 SOD-123 13 mm ²
8.	L1	Panasonic	ELL-6UH390M	L= 39.0 uH DCR= 150.0 mOhm	1	\$0.28	 ELL6UH 67 mm ²
9.	Rfbb	Vishay-Dale	CRCW04022K00FKED Series= CRCW..e3	Res= 2.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
10.	Rfbt	Vishay-Dale	CRCW04022K00FKED Series= CRCW..e3	Res= 2.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
11.	Ron	Vishay-Dale	CRCW040269K8FKED Series= CRCW..e3	Res= 69.8 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
12.	Rseries	Stackpole Electronics Inc	CSRN2010FKR400 Series= ?	Res= 400.0 mOhm Power= 1.0 W Tolerance= 1.0%	1	\$0.11	 2010 32 mm ²
13.	U1	Texas Instruments	LM34914SD/NOPB	Switcher	1	\$1.35	 DSC0010B 16 mm ²

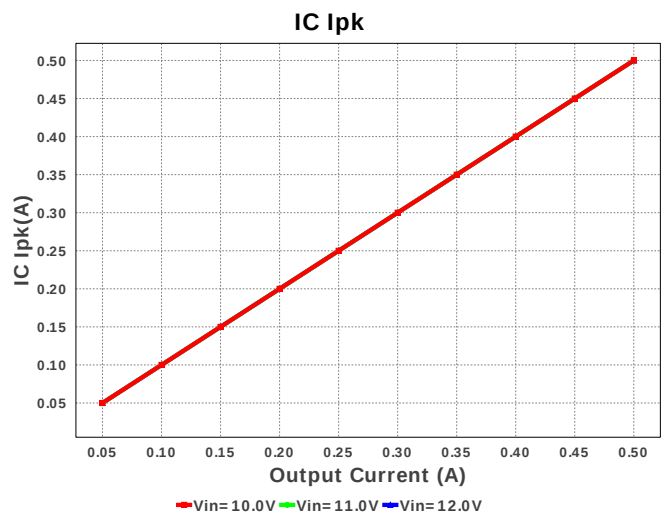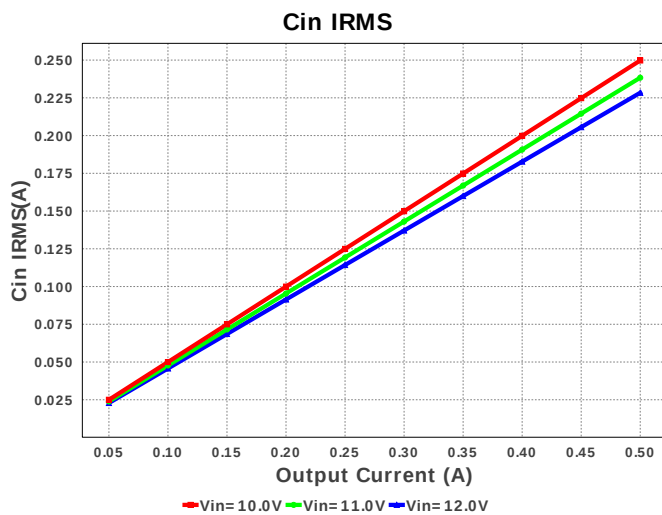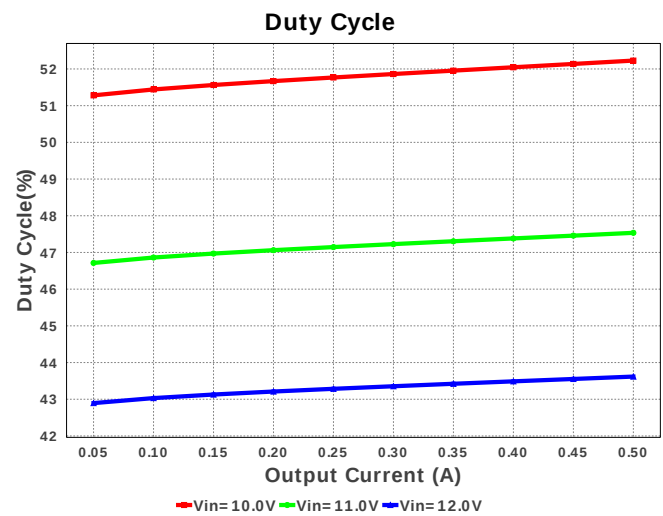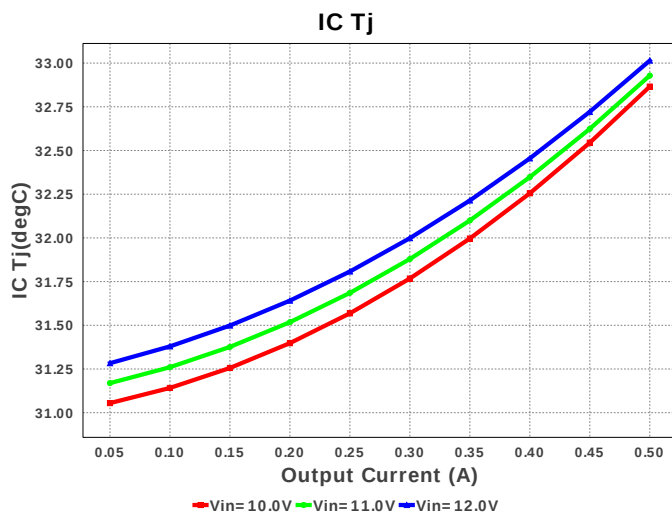

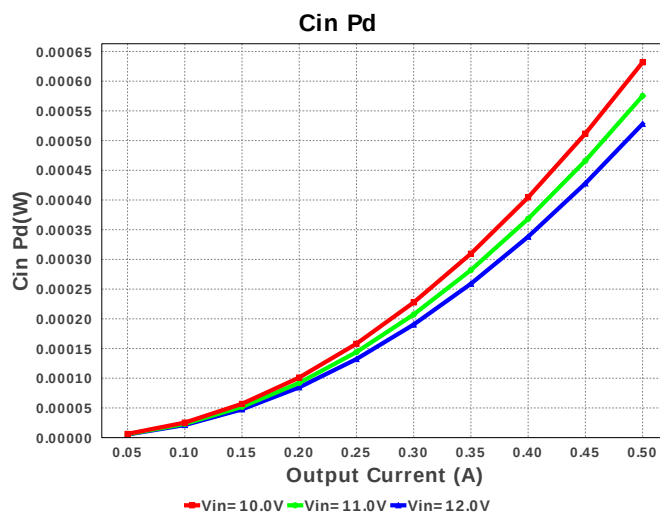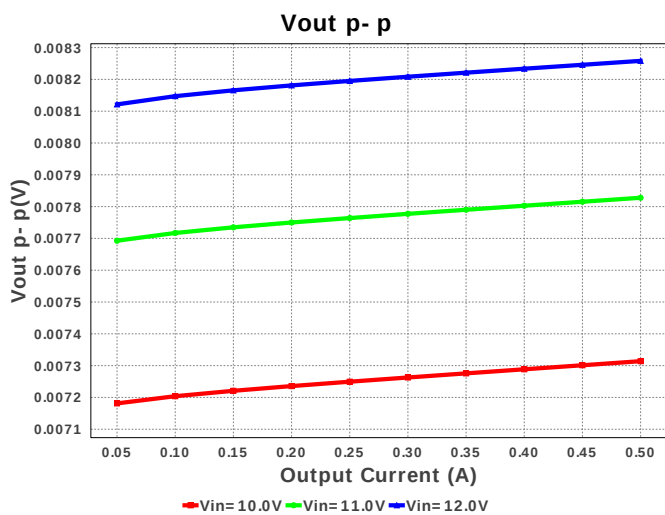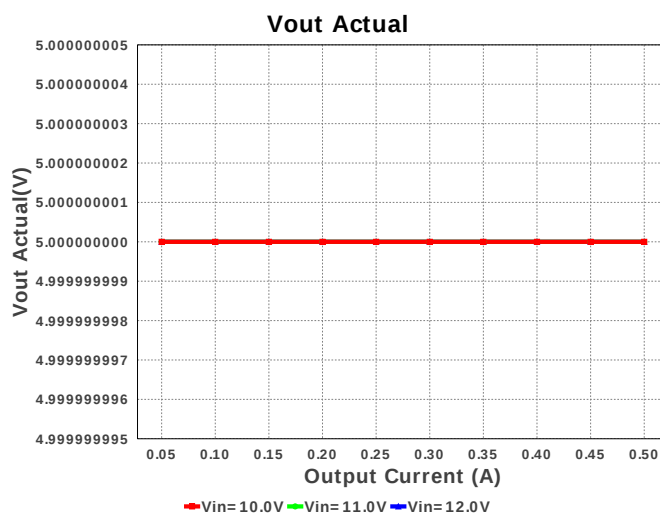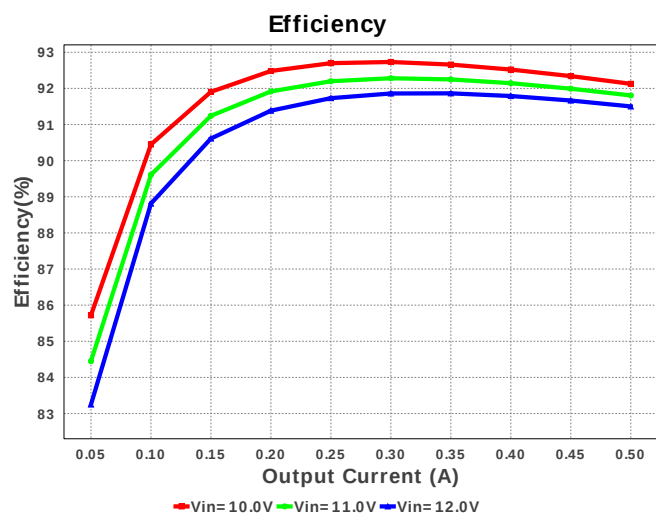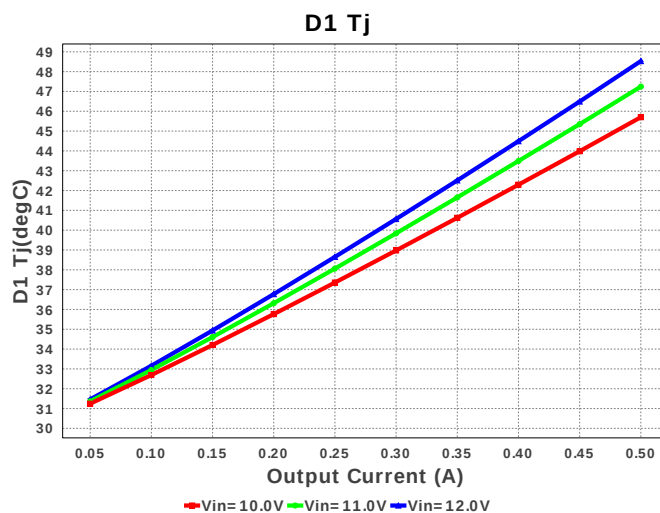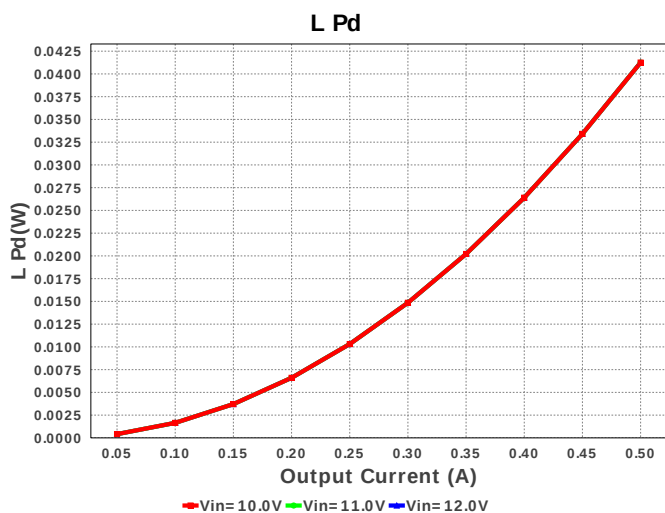

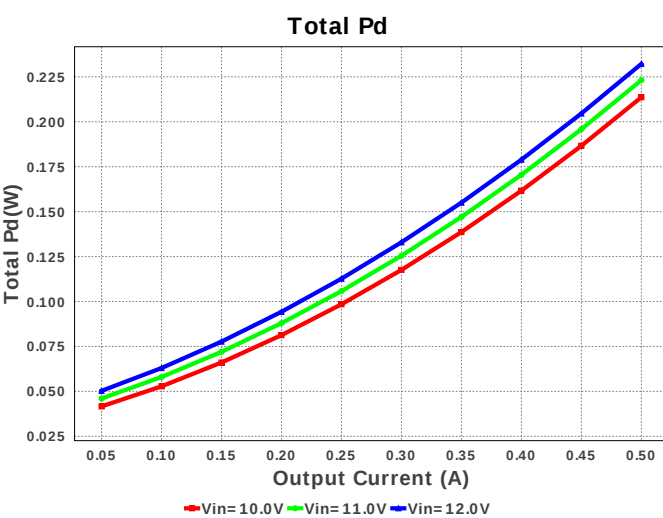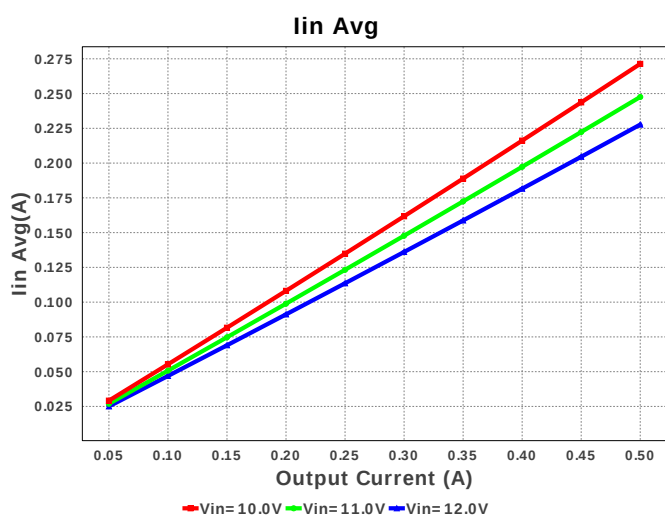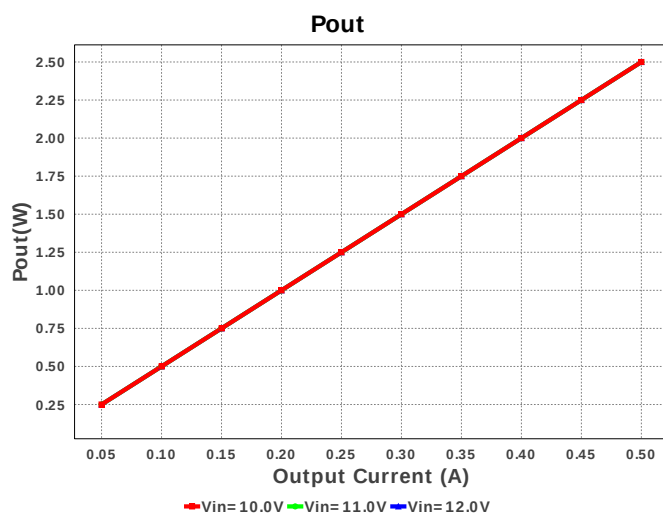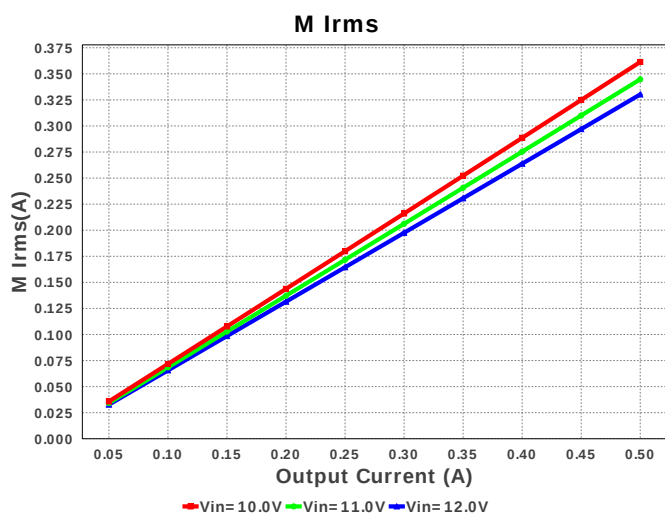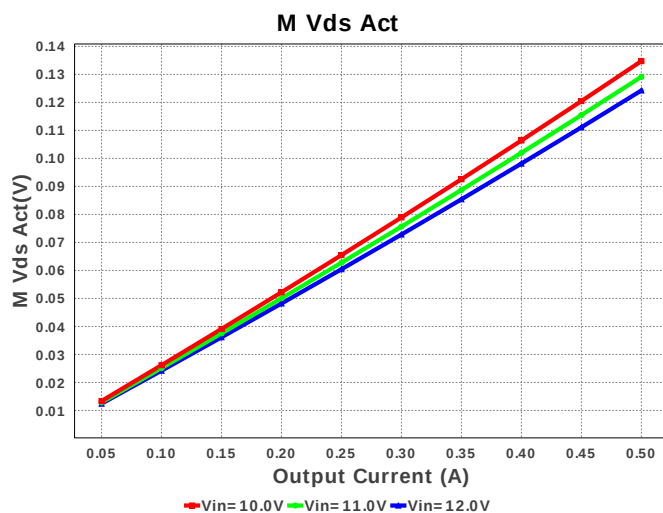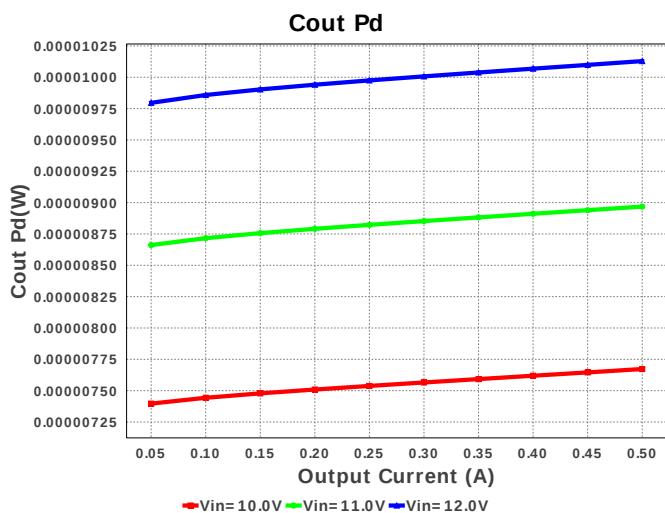

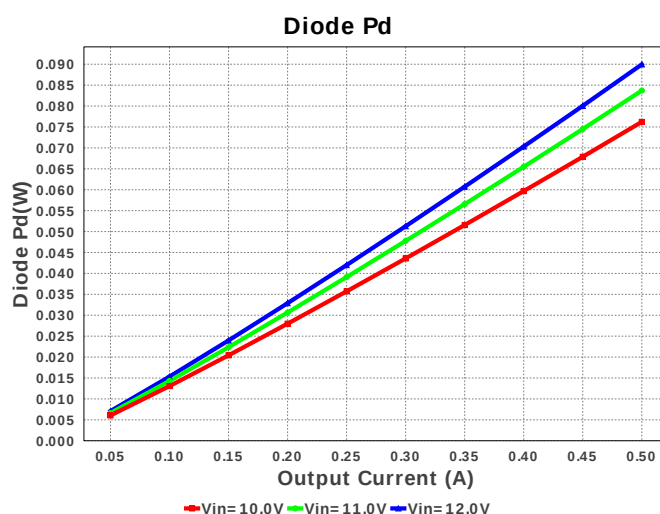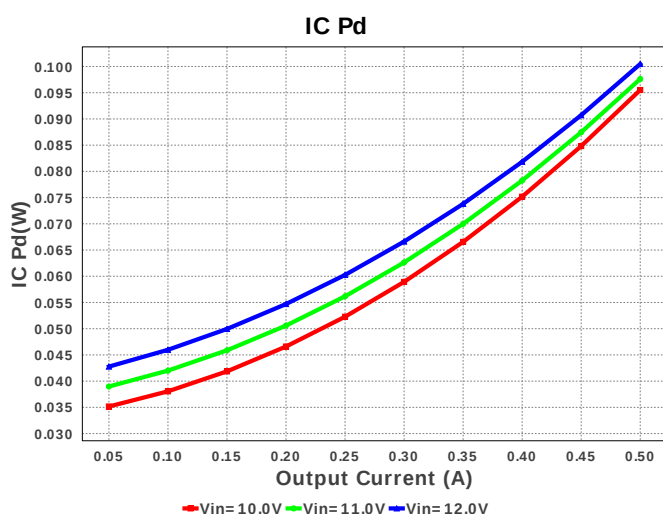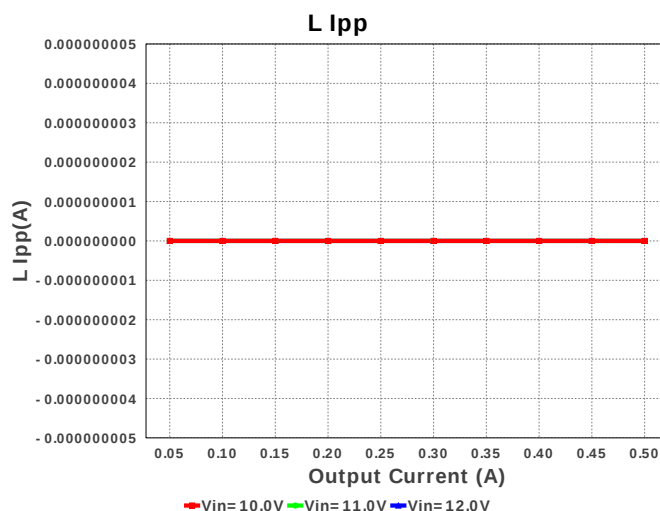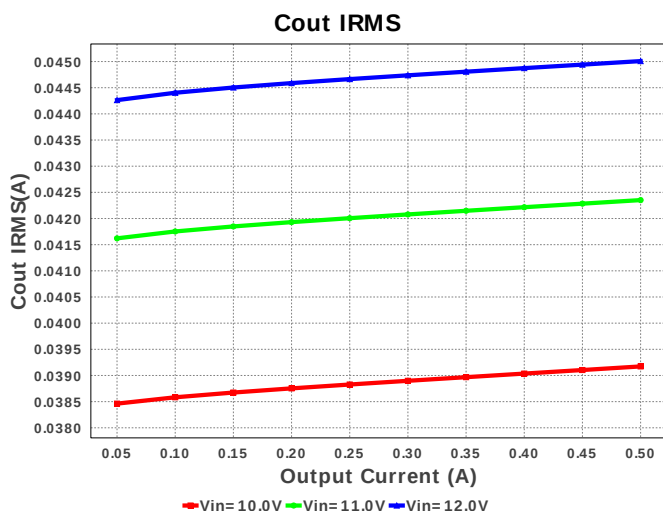

Operating Values

#	Name	Value	Category	Description
1.	Cin IRMS	228.366 mA	Current	Input capacitor RMS ripple current
2.	Cout IRMS	45.008 mA	Current	Output capacitor RMS ripple current
3.	IC Ipk	572.793 mA	Current	Peak switch current in IC
4.	Iin Avg	227.69 mA	Current	Average input current
5.	L Ipp	145.59 mA	Current	Peak-to-peak inductor ripple current
6.	M1 Irms	330.218 mA	Current	Q lavg
7.	BOM Count	13	General	Total Design BOM count
8.	FootPrint	165.0 mm ²	General	Total Foot Print Area of BOM components
9.	Frequency	502.123 kHz	General	Switching frequency
10.	IC Tolerance	5.0 mV	General	IC Feedback Tolerance
11.	M Vds Act	124.263 mV	General	Voltage drop across the MosFET
12.	Pout	2.5 W	General	Total output power
13.	Total BOM	\$1.89	General	Total BOM Cost
14.	D1 Tj	48.531 degC	Op_Point	D1 junction temperature
15.	Vout Actual	5.0 V	Op_Point	Vout Actual calculated based on selected voltage divider resistors
16.	Vout OP	5.0 V	Op_Point	Operational Output Voltage
17.	Duty Cycle	43.618 %	Op_point	Duty cycle
18.	Efficiency	91.501 %	Op_point	Steady state efficiency
19.	IC Tj	33.014 degC	Op_point	IC junction temperature
20.	ICThetaJA	30.0 degC/W	Op_point	IC junction-to-ambient thermal resistance
21.	IOUT_OP	500.0 mA	Op_point	Iout operating point
22.	VIN_OP	12.0 V	Op_point	Vin operating point
23.	Vout p-p	66.492 mV	Op_point	Peak-to-peak output ripple voltage
24.	Cin Pd	528.133 μW	Power	Input capacitor power dissipation
25.	Cout Pd	10.129 μW	Power	Output capacitor power dissipation
26.	Diode Pd	89.957 mW	Power	Diode power dissipation
27.	IC Pd	100.48 mW	Power	IC power dissipation
28.	L Pd	41.25 mW	Power	Inductor power dissipation
29.	Total Pd	232.216 mW	Power	Total Power Dissipation
30.	Vout Tolerance	1.212 %		Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable

Design Inputs

#	Name	Value	Description
1.	Iout	500.0 m	Maximum Output Current
2.	VinMax	12.0	Maximum input voltage
3.	VinMin	10.0	Minimum input voltage
4.	Vout	5.0	Output Voltage
5.	base_pn	LM34914	Base Product Number
6.	source	DC	Input Source Type
7.	Ta	30.0	Ambient temperature

Design Assistance

1. For a Constant On Time device to be stable, we need to provide a ripple at the feedback comparator. There are various methods to implement the ripple. Depending on the circuit complexity vs. the allowable ripple, we have three options to choose from. The simplest option, 'Low Complexity', would require only a high ESR cap at the output. This means that the BOM count will be small, but the output voltage ripple will be quite large. The 'Optimal Solution' would require a feed-forward cap in parallel with the upper feedback resistor to AC couple the ripple to the feedback node. This increases the BOM count slightly, but now we have more control over the output voltage ripple. If the output voltage requirement is very tight, then the best option is to go for the 'Low Output Ripple' solution. In this option we can go with very low ESR output caps and have very good control over the output voltage ripple.

2. **LM34914** Product Folder : <http://www.ti.com/product/LM34914> : contains the data sheet and other resources.

Texas Instruments' WEBENCH simulation tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Simulations are created using Texas Instruments' published specifications as well as the published specifications of other device manufacturers. While Texas Instruments does update this information periodically, this information may not be current at the time the simulation is built. Texas Instruments does not warrant the accuracy or completeness of the specifications or any information contained therein. Texas Instruments does not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. Texas Instruments does not warrant that the designs are production worthy.

You should completely validate and test your design implementation to confirm the system functionality for your application prior to production.

Use of Texas Instruments' WEBENCH simulation tools is subject to [Texas Instruments' Site Terms and Conditions of Use](#). Prototype boards based on WEBENCH created designs are provided AS IS without warranty of any kind for evaluation and testing purposes and are subject to the terms of the [Evaluation License Agreement](#).