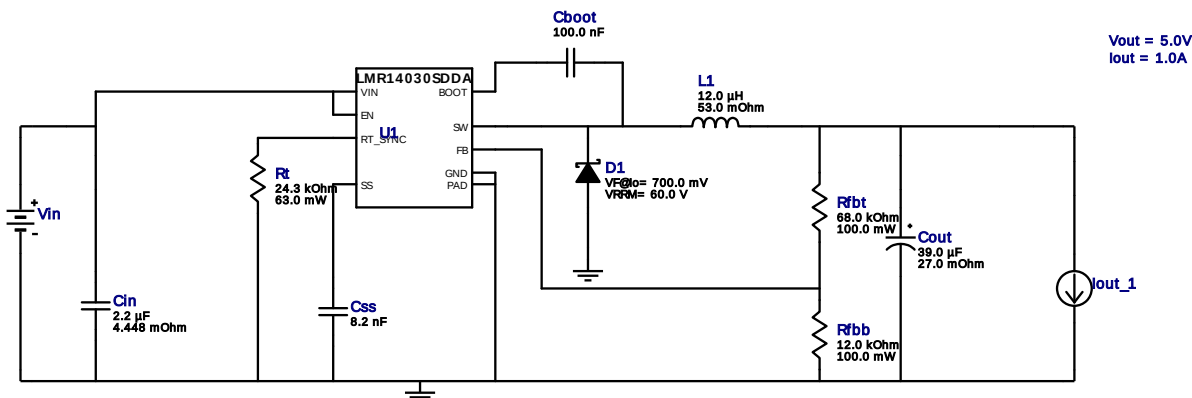


WEBENCH® Design Report





Design : 4742013/97 LMR14030SDDAR
LMR14030SDDAR 30.0V-37.0V to 5.00V @ 1.0001875000000002A















Electrical BOM






#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	Cboot	Taiyo Yuden	HMK212B7104KG-T Series= X7R	Cap= 100.0 nF VDC= 100.0 V IRMS= 0.0 A	1	\$0.03	 0805 7 mm ²
2.	Cin	MuRata	GRM31CR71H225KA88L Series= X7R	Cap= 2.2 uF ESR= 4.448 mOhm VDC= 50.0 V IRMS= 2.2252 A	1	\$0.05	 1206_190 11 mm ²
3.	Cout	Panasonic	16SVPC39MV Series= SVPC	Cap= 39.0 uF ESR= 27.0 mOhm VDC= 16.0 V IRMS= 2.35 A	1	\$0.28	 SM_RADIAL_5MM 58 mm ²
4.	Css	MuRata	GRM155R71C822KA01D Series= X7R	Cap= 8.2 nF VDC= 16.0 V IRMS= 0.0 A	1	\$0.01	 0402 3 mm ²
5.	D1	Diodes Inc.	B260A-13-F	VF@Io= 700.0 mV VRRM= 60.0 V	1	\$0.09	 SMA 37 mm ²
6.	L1	Bourns	SRR6038-120Y	L= 12.0 uH DCR= 53.0 mOhm	1	\$0.26	 SRR6038 77 mm ²
7.	Rfbb	Yageo America	RC0603FR-0712KL Series= ?	Res= 12.0 kOhm Power= 100.0 mW Tolerance= 1.0%	1	\$0.01	 0603 5 mm ²
8.	Rfbs	Yageo America	RC0603FR-0768KL Series= ?	Res= 68.0 kOhm Power= 100.0 mW Tolerance= 1.0%	1	\$0.01	 0603 5 mm ²
9.	Rt	Vishay-Dale	CRCW040224K3FKED Series= CRCW..e3	Res= 24.3 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
10. U1		Texas Instruments	LMR14030SDDAR	Switcher	1	\$1.68	 DDA0008E_N 57 mm ²

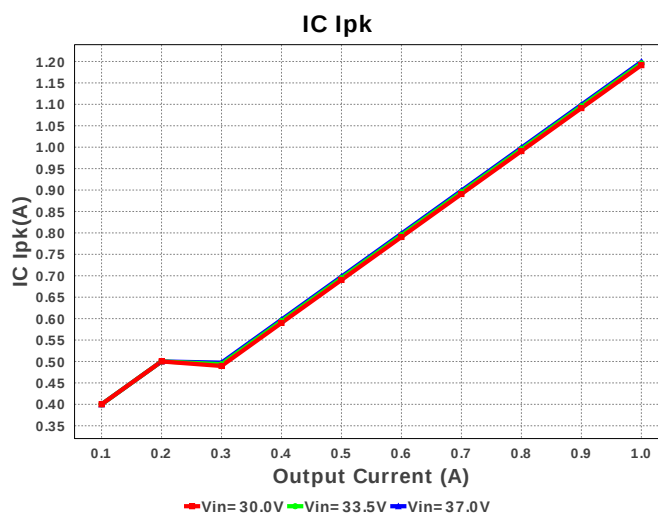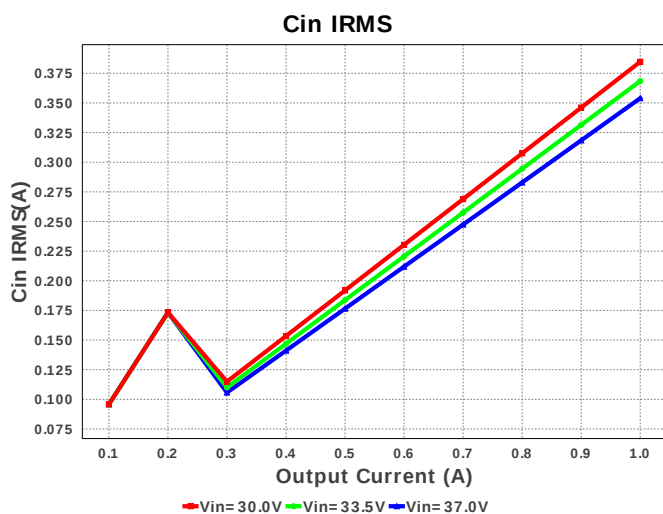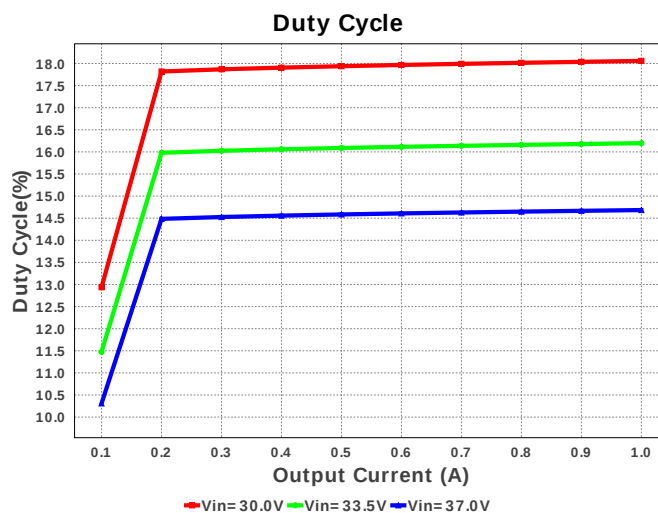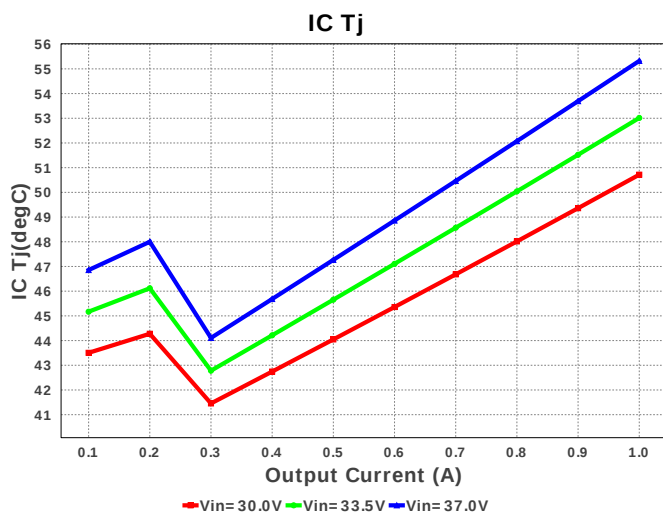

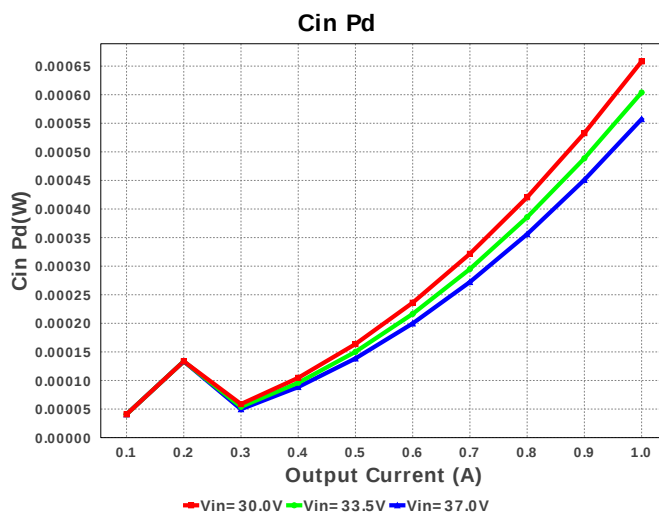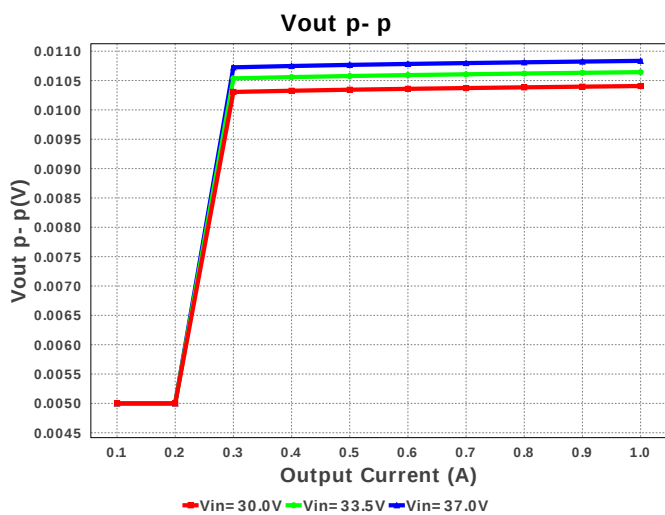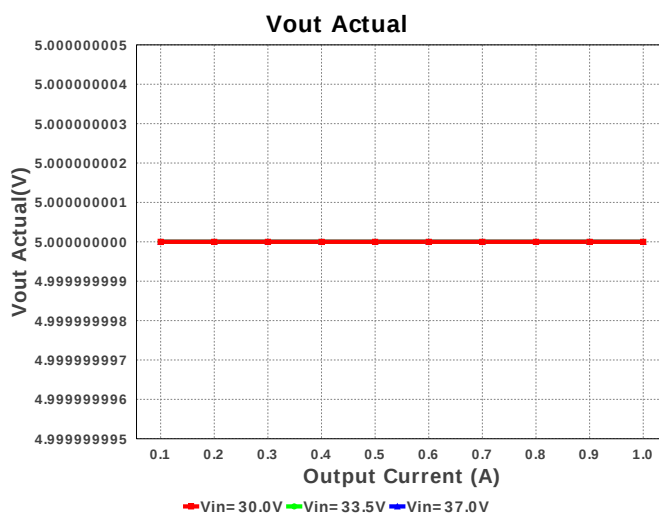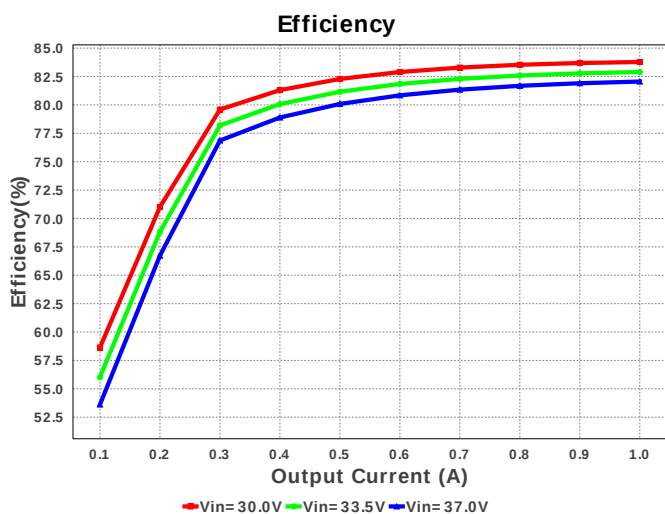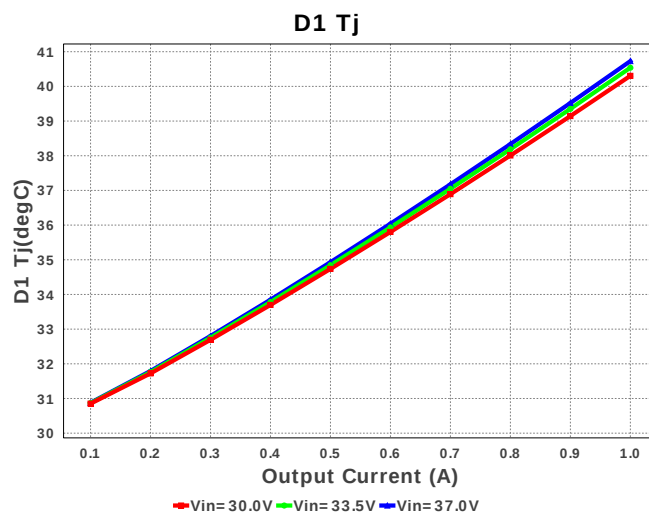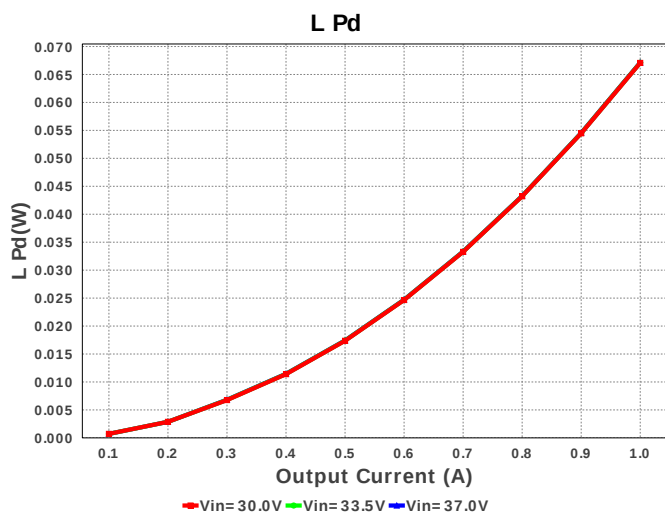

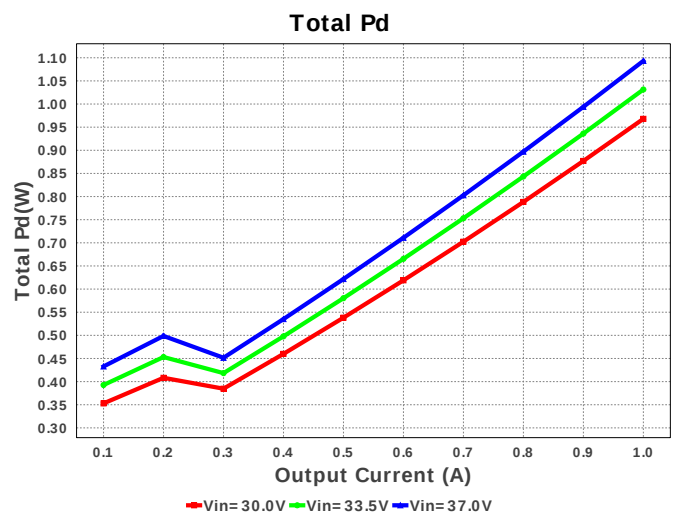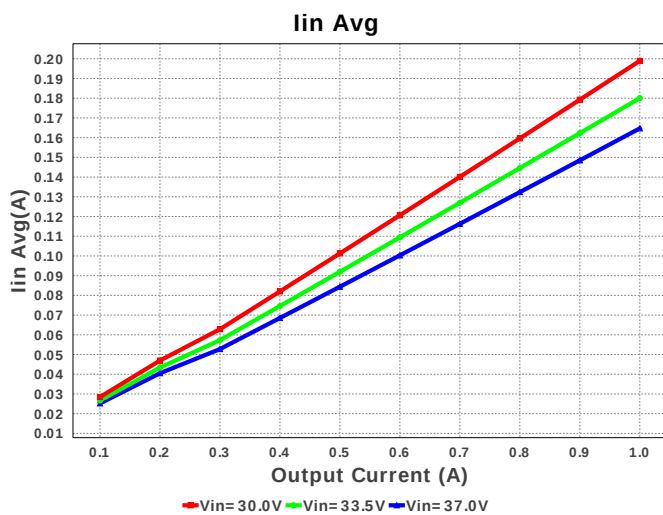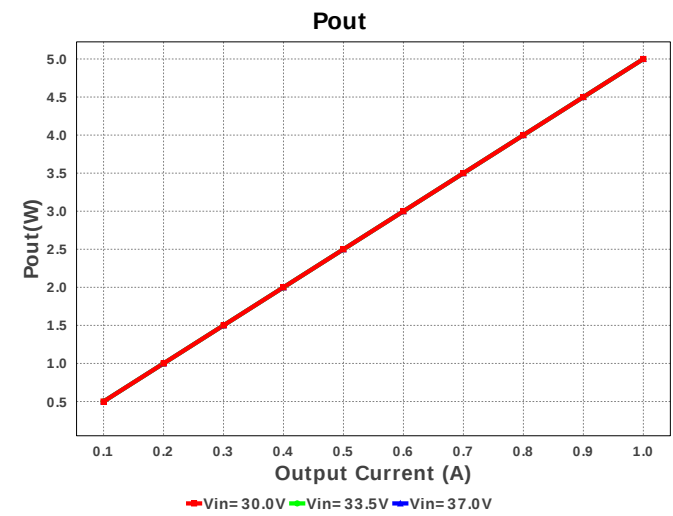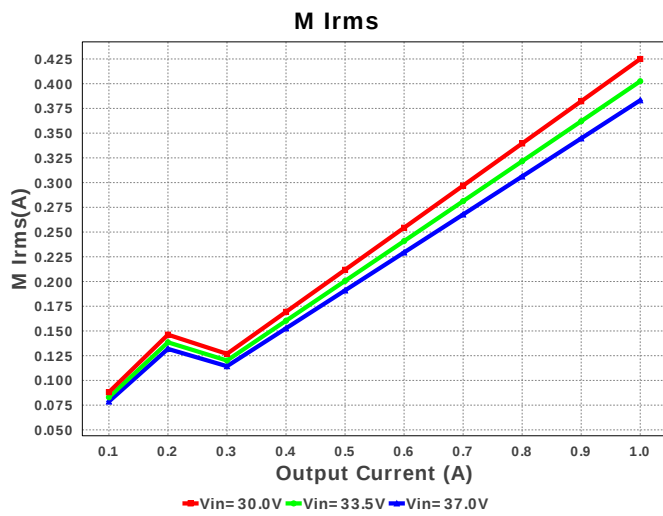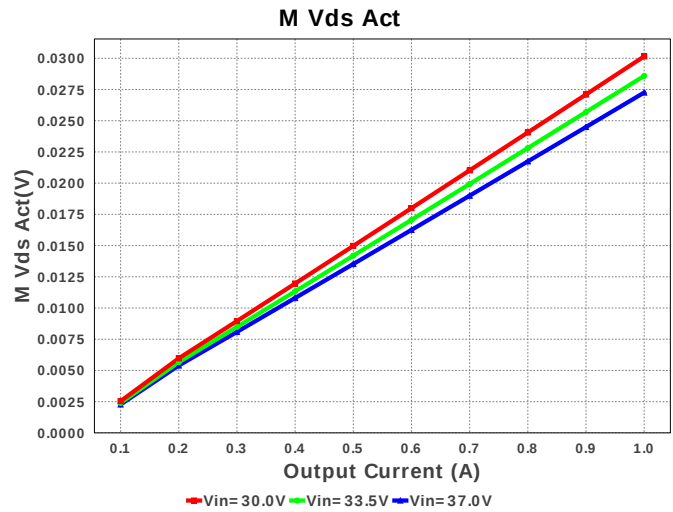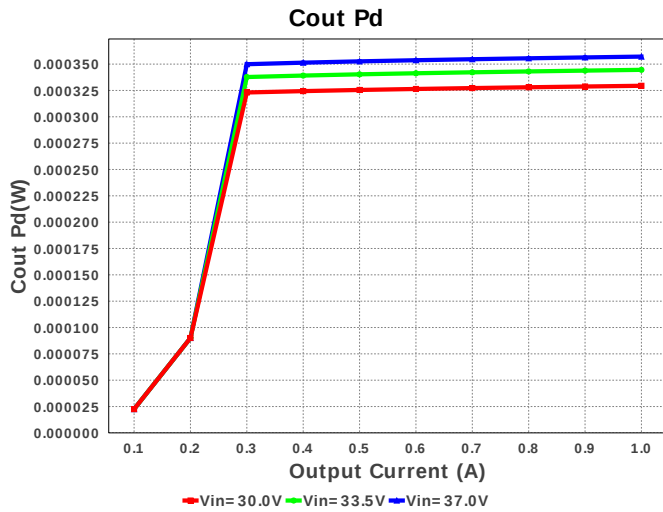

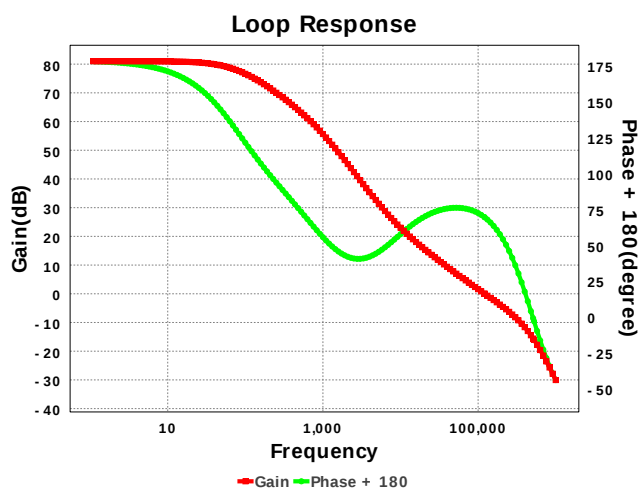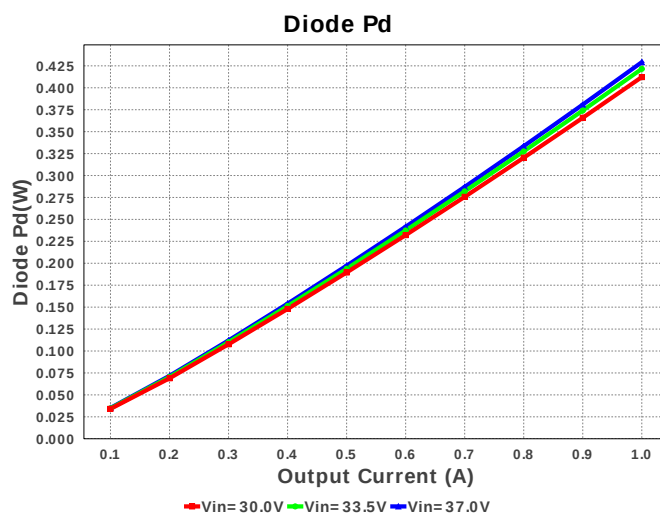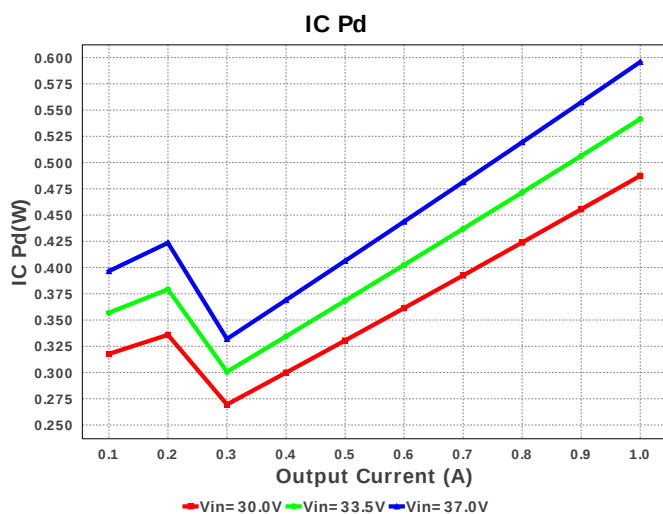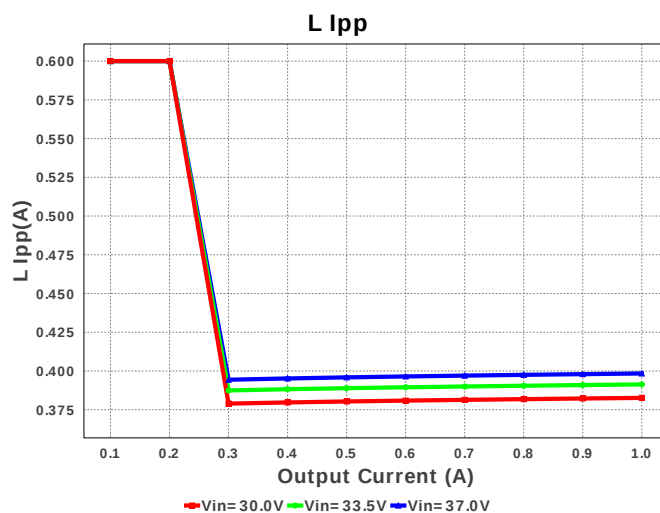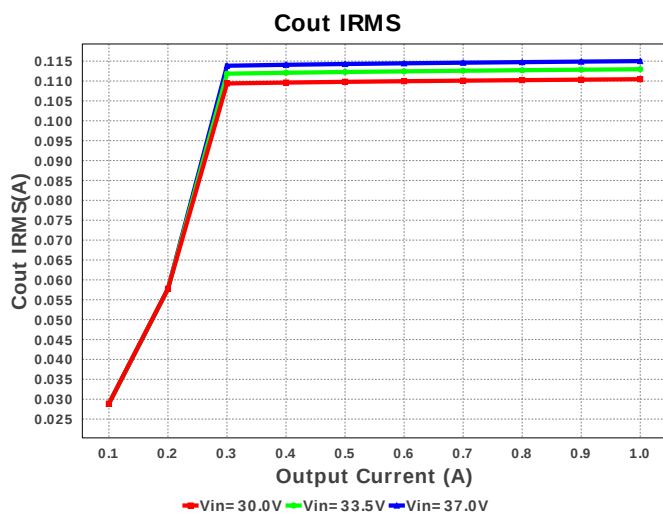

Operating Values

#	Name	Value	Category	Description
1.	Cin IRMS	353.97 mA	Current	Input capacitor RMS ripple current
2.	Cout IRMS	115.009 mA	Current	Output capacitor RMS ripple current
3.	IC Ipk	1.199 A	Current	Peak switch current in IC
4.	Iin Avg	164.69 mA	Current	Average input current
5.	L Ipp	398.4 mA	Current	Peak-to-peak inductor ripple current
6.	M1 Irms	383.223 mA	Current	Q lavg
7.	BOM Count	10	General	Total Design BOM count
8.	FootPrint	264.0 mm ²	General	Total Foot Print Area of BOM components
9.	Frequency	982.032 kHz	General	Switching frequency
10.	IC Tolerance	18.0 mV	General	IC Feedback Tolerance
11.	M Vds Act	27.251 mV	General	Voltage drop across the MosFET

#	Name	Value	Category	Description
12.	Pout	5.0 W	General	Total output power
13.	Total BOM	\$2.43	General	Total BOM Cost
14.	D1 Tj	40.729 degC	Op_Point	D1 junction temperature
15.	Vout Actual	5.0 V	Op_Point	Vout Actual calculated based on selected voltage divider resistors
16.	Vout OP	5.0 V	Op_Point	Operational Output Voltage
17.	Cross Freq	121.527 kHz	Op_point	Bode plot crossover frequency
18.	Duty Cycle	14.684 %	Op_point	Duty cycle
19.	Efficiency	82.058 %	Op_point	Steady state efficiency
20.	IC Tj	55.024 degC	Op_point	IC junction temperature
21.	ICThetaJA	42.0 degC/W	Op_point	IC junction-to-ambient thermal resistance
22.	IOUT_OP	1.0 A	Op_point	Iout operating point
23.	Phase Marg	70.337 deg	Op_point	Bode Plot Phase Margin
24.	VIN_OP	37.0 V	Op_point	Vin operating point
25.	Vout p-p	10.835 mV	Op_point	Peak-to-peak output ripple voltage
26.	Cin Pd	557.311 μW	Power	Input capacitor power dissipation
27.	Cout Pd	357.13 μW	Power	Output capacitor power dissipation
28.	Diode Pd	429.16 mW	Power	Diode power dissipation
29.	IC Pd	595.818 mW	Power	IC power dissipation
30.	L Pd	67.135 mW	Power	Inductor power dissipation
31.	Total Pd	1.093 W	Power	Total Power Dissipation
32.	Vout Tolerance	4.158 %		Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable

Design Inputs

#	Name	Value	Description
1.	Iout	1.0	Maximum Output Current
2.	VinMax	37.0	Maximum input voltage
3.	VinMin	30.0	Minimum input voltage
4.	Vout	5.0	Output Voltage
5.	base_pn	LMR14030S	Base Product Number
6.	source	DC	Input Source Type
7.	Ta	30.0	Ambient temperature

Design Assistance

1. **LMR14030S** Product Folder : <http://www.ti.com/product/LMR14030> : contains the data sheet and other resources.

Texas Instruments' WEBENCH simulation tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Simulations are created using Texas Instruments' published specifications as well as the published specifications of other device manufacturers. While Texas Instruments does update this information periodically, this information may not be current at the time the simulation is built. Texas Instruments does not warrant the accuracy or completeness of the specifications or any information contained therein. Texas Instruments does not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. Texas Instruments does not warrant that the designs are production worthy.

You should completely validate and test your design implementation to confirm the system functionality for your application prior to production.

Use of Texas Instruments' WEBENCH simulation tools is subject to [Texas Instruments' Site Terms and Conditions of Use](#). Prototype boards based on WEBENCH created designs are provided AS IS without warranty of any kind for evaluation and testing purposes and are subject to the terms of the [Evaluation License Agreement](#).