

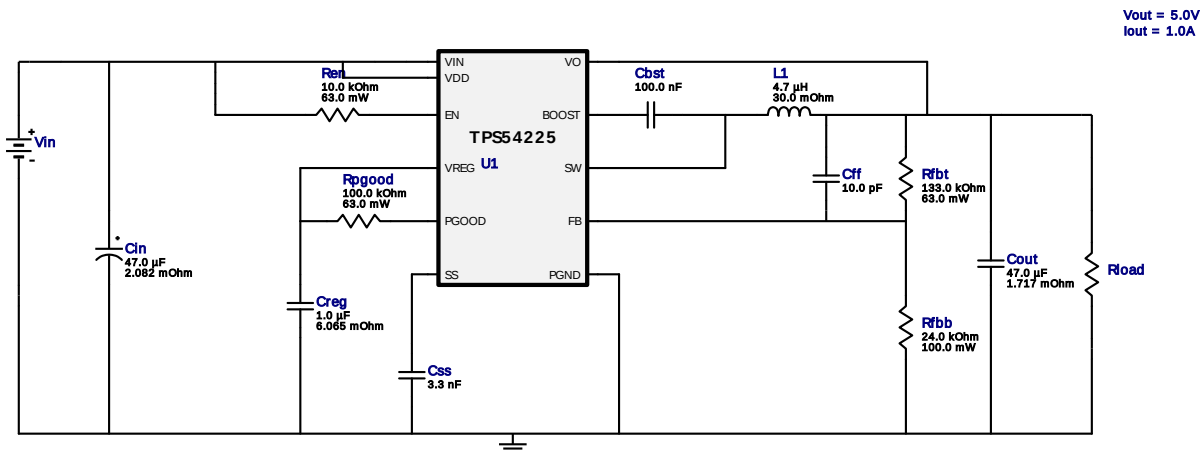
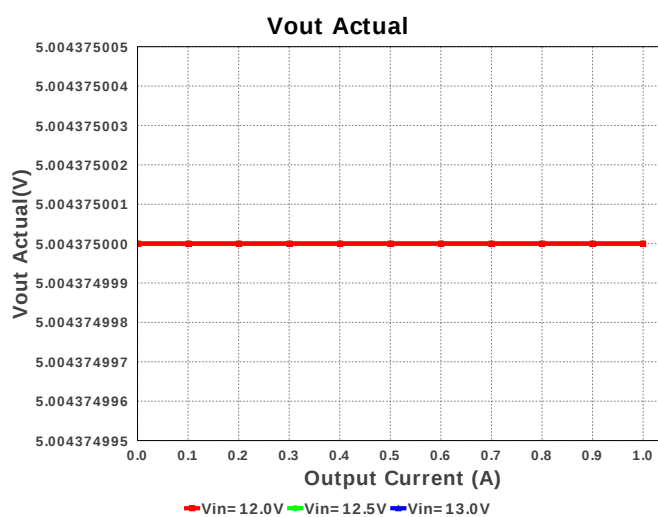
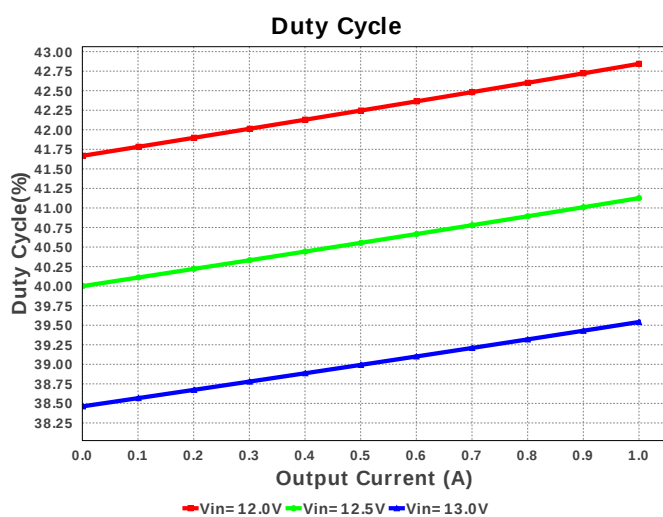







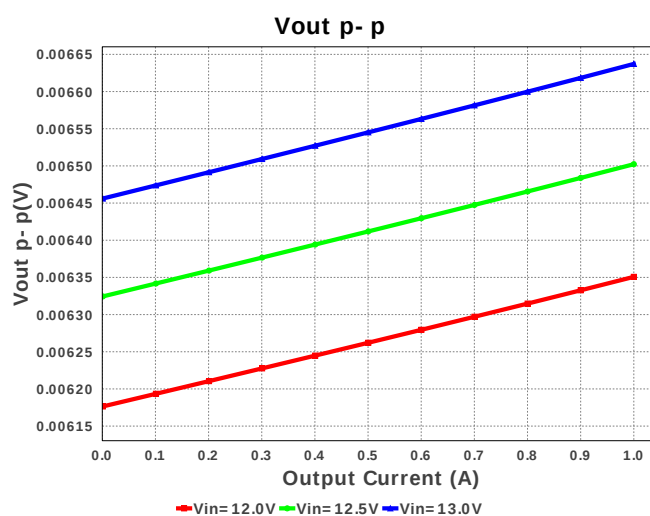








Electrical BOM


#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	Cbst	MuRata	GRM155R61A104KA01D Series= X5R	Cap= 100.0 nF VDC= 10.0 V IRMS= 0.0 A	1	\$0.01	 0402 3 mm ²
2.	Cff	Kemet	C0805C100M4GACTU Series= C0G/NP0	Cap= 10.0 pF VDC= 16.0 V IRMS= 0.0 A	1	\$0.01	 0805 7 mm ²
3.	Cin	TDK	C3216X5R1E476M160AC Series= X5R	Cap= 47.0 uF ESR= 2.082 mOhm VDC= 25.0 V IRMS= 5.0279 A	1	\$0.35	 1206 11 mm ²
4.	Cout	TDK	C3216JB1A476M Series= JB	Cap= 47.0 uF ESR= 1.717 mOhm VDC= 10.0 V IRMS= 0.0 A	1	\$0.34	 1206 11 mm ²
5.	Creg	MuRata	GRM188R61A105KA61D Series= X5R	Cap= 1.0 uF ESR= 6.065 mOhm VDC= 10.0 V IRMS= 1.30675 A	1	\$0.01	 0603 5 mm ²
6.	Css	MuRata	GRM216R71E332KA01D Series= X7R	Cap= 3.3 nF VDC= 25.0 V IRMS= 0.0 A	1	\$0.01	 0805 7 mm ²
7.	L1	TDK	CLF7045T-4R7N	L= 4.7 µH DCR= 30.0 mOhm	1	\$0.42	 CLF7045 86 mm ²
8.	Ren	Vishay-Dale	CRCW040210K0FKED Series= CRCW..e3	Res= 10.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
9.	Rfbb	Yageo America	RC0603FR-0724KL Series= ?	Res= 24.0 kOhm Power= 100.0 mW Tolerance= 1.0%	1	\$0.01	 0603 5 mm ²
10.	Rfbt	Vishay-Dale	CRCW0402133KFKED Series= CRCW..e3	Res= 133.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
11.	Rpgood	Vishay-Dale	CRCW0402100KFKED Series= CRCW..e3	Res= 100.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm²
12.	U1	Texas Instruments	TPS54225PWPR	Switcher	1	\$0.73	 R-PDSO-G14 61 mm²

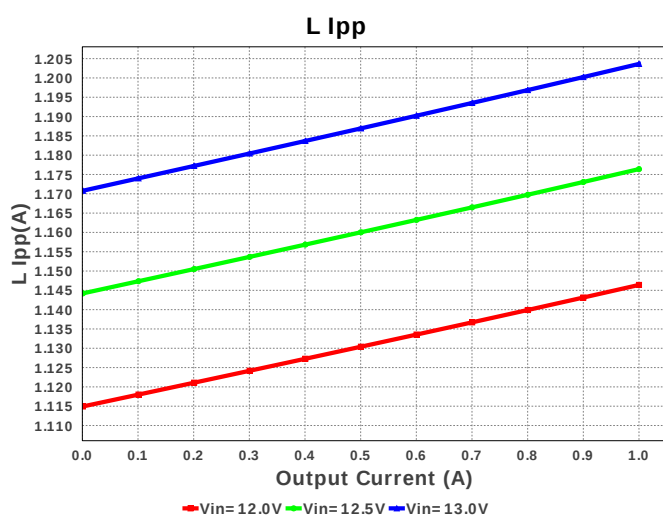

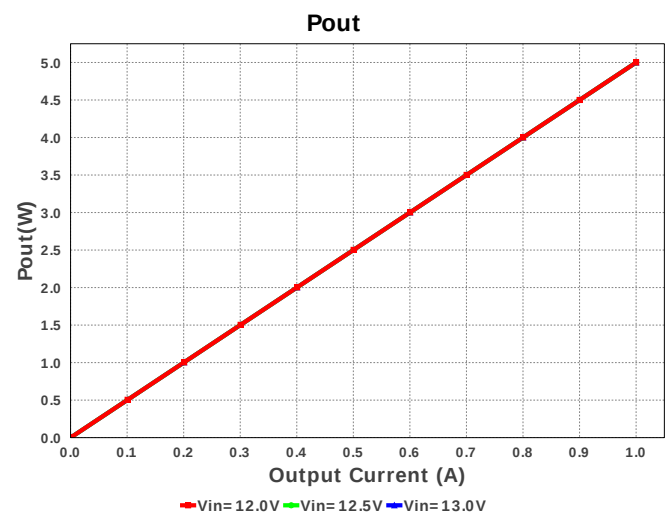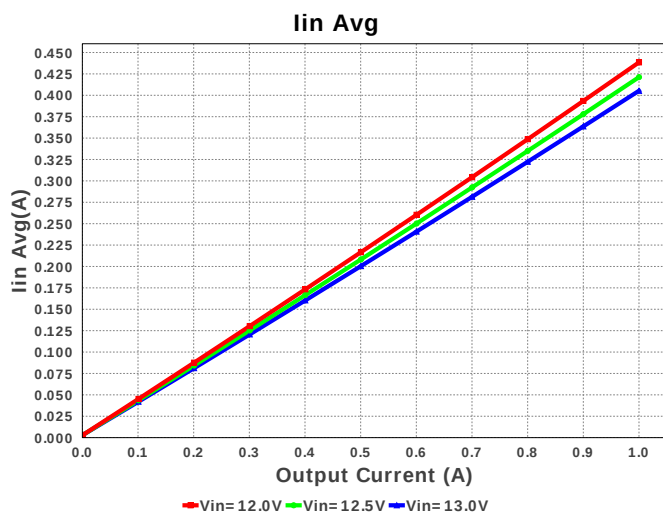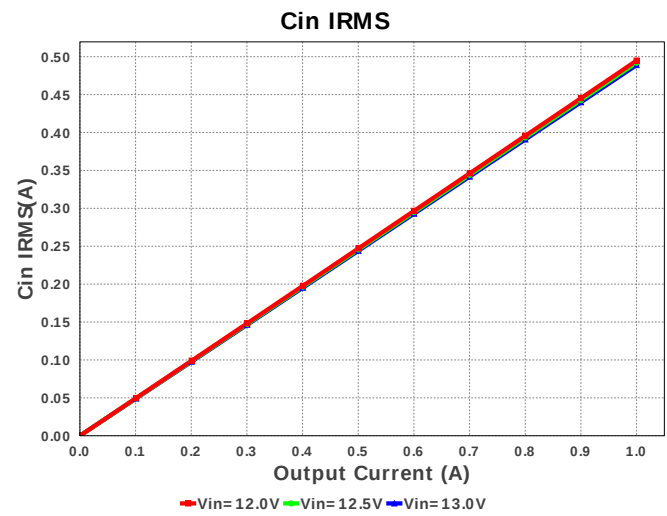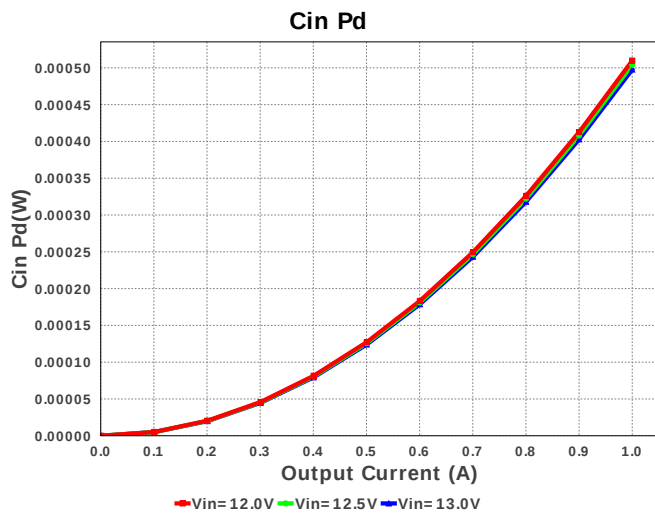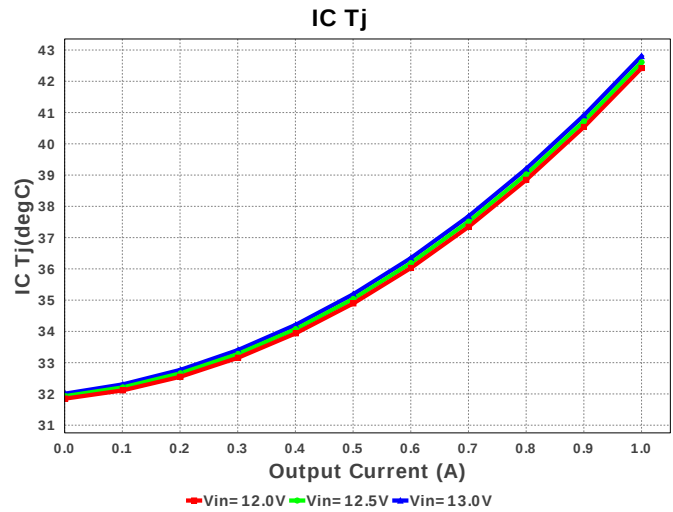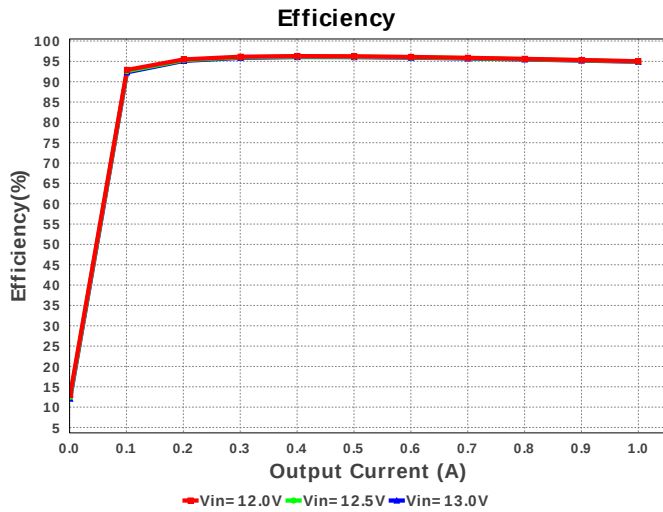

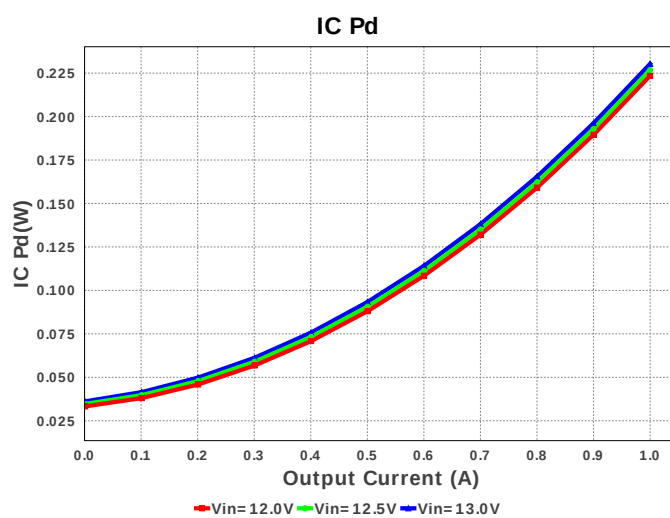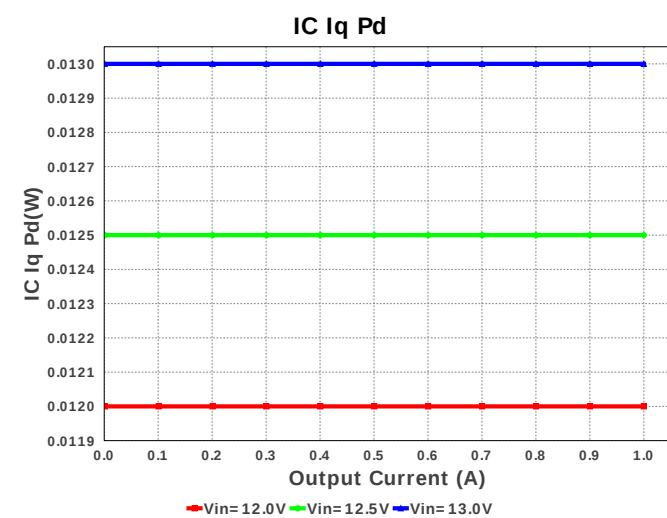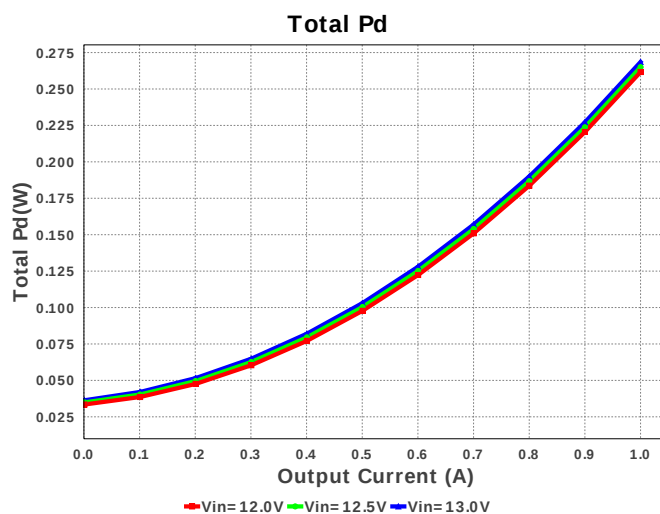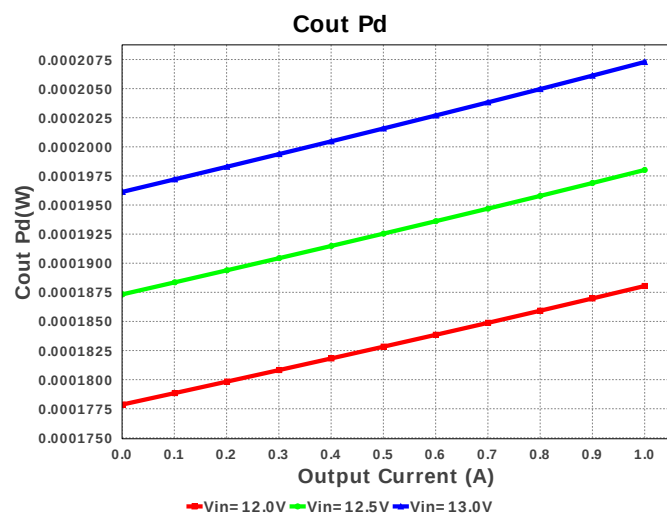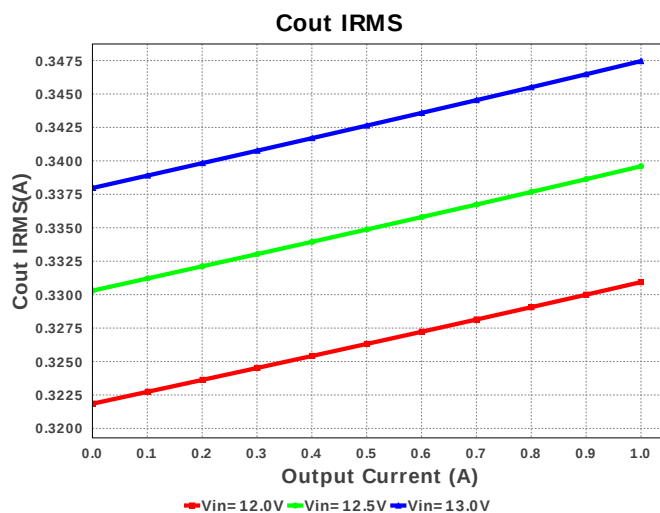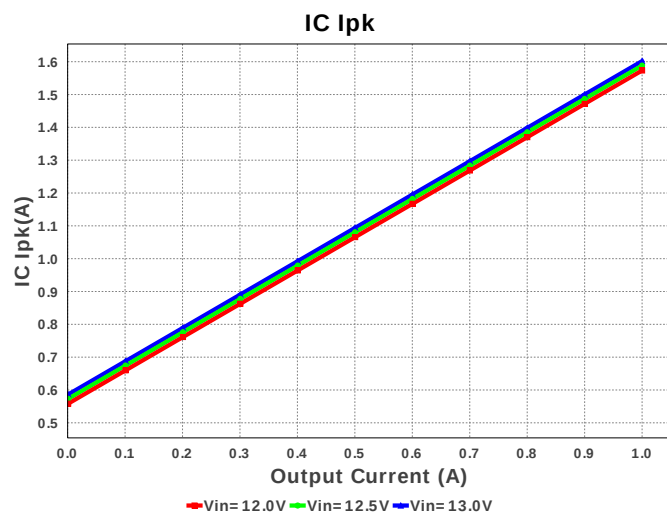

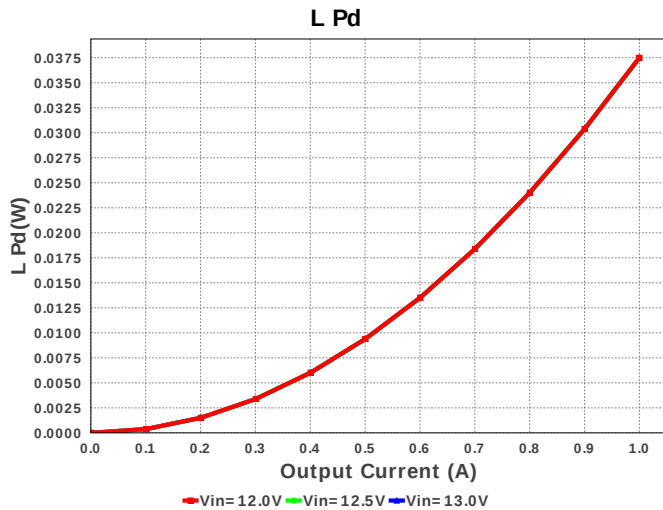

Operating Values

#	Name	Value	Category	Description
1.	Cin IRMS	488.94 mA	Current	Input capacitor RMS ripple current
2.	Cout IRMS	347.461 mA	Current	Output capacitor RMS ripple current
3.	IC Ipk	1.602 A	Current	Peak switch current in IC
4.	Iin Avg	405.51 mA	Current	Average input current
5.	L Ipp	1.204 A	Current	Peak-to-peak inductor ripple current
6.	BOM Count	12	General	Total Design BOM count
7.	FootPrint	203.0 mm ²	General	Total Foot Print Area of BOM components
8.	Frequency	559.178 kHz	General	Switching frequency
9.	Pout	5.0 W	General	Total output power
10.	Total BOM	\$1.92	General	Total BOM Cost
11.	Vout Actual	5.004 V	Op_Point	Vout Actual calculated based on selected voltage divider resistors
12.	Vout OP	5.0 V	Op_Point	Operational Output Voltage
13.	Duty Cycle	39.542 %	Op_point	Duty cycle
14.	Efficiency	94.847 %	Op_point	Steady state efficiency
15.	IC Tj	42.981 degC	Op_point	IC junction temperature
16.	ICThetaJA	55.6 degC/W	Op_point	IC junction-to-ambient thermal resistance
17.	IOUT_OP	1.0 A	Op_point	Iout operating point
18.	VIN_OP	13.0 V	Op_point	Vin operating point
19.	Vout p-p	6.637 mV	Op_point	Peak-to-peak output ripple voltage
20.	Cin Pd	497.728 μW	Power	Input capacitor power dissipation
21.	Cout Pd	207.292 μW	Power	Output capacitor power dissipation
22.	IC Iq Pd	13.0 mW	Power	IC Iq Pd
23.	IC Pd	233.464 mW	Power	IC power dissipation
24.	L Pd	37.5 mW	Power	Inductor power dissipation
25.	Total Pd	271.647 mW	Power	Total Power Dissipation
26.	Vout Tolerance	2.775 %		Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable

Design Inputs

#	Name	Value	Description
1.	Iout	1.0	Maximum Output Current
2.	VinMax	13.0	Maximum input voltage
3.	VinMin	12.0	Minimum input voltage
4.	Vout	5.0	Output Voltage
5.	base_pn	TPS54225	Base Product Number
6.	source	DC	Input Source Type
7.	Ta	30.0	Ambient temperature

Design Assistance

1. **TPS54225** Product Folder : <http://www.ti.com/product/TPS54225> : contains the data sheet and other resources.

Texas Instruments' WEBENCH simulation tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Simulations are created using Texas Instruments' published specifications as well as the published specifications of other device manufacturers. While Texas Instruments does update this information periodically, this information may not be current at the time the simulation is built. Texas Instruments does not warrant the accuracy or completeness of the specifications or any information contained therein. Texas Instruments does not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. Texas Instruments does not warrant that the designs are production worthy.

You should completely validate and test your design implementation to confirm the system functionality for your application prior to production.

Use of Texas Instruments' WEBENCH simulation tools is subject to [Texas Instruments' Site Terms and Conditions of Use](#). Prototype boards based on WEBENCH created designs are provided AS IS without warranty of any kind for evaluation and testing purposes and are subject to the terms of the [Evaluation License Agreement](#).