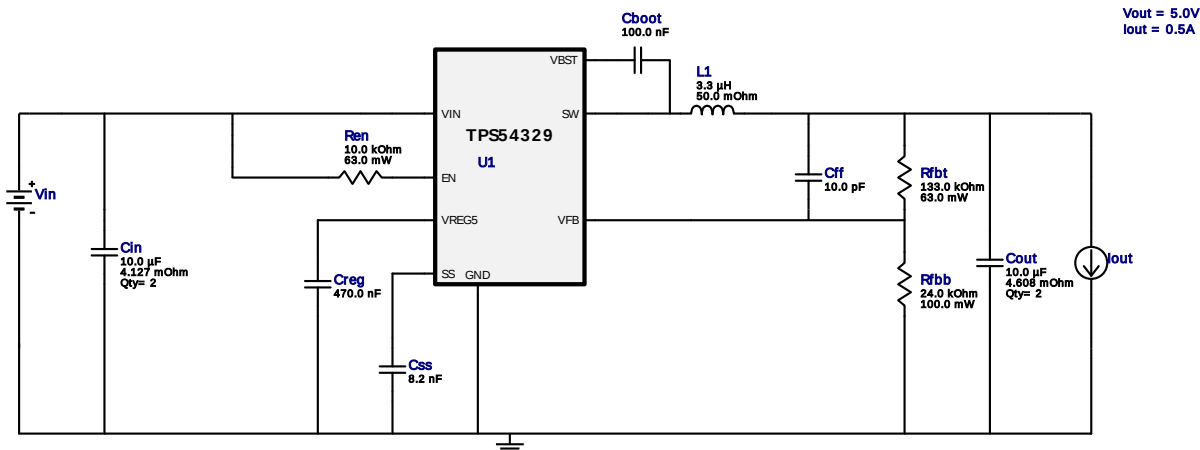


WEBENCH® Design Report





Design : 4742013/239 TPS54329DDAR
TPS54329DDAR 10.0V-12.0V to 5.00V @ 0.5A















Electrical BOM


#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	Cboot	MuRata	GRM155R61A104KA01D Series= X5R	Cap= 100.0 nF VDC= 10.0 V IRMS= 0.0 A	1	\$0.01	 0402 3 mm ²
2.	Cff	Kemet	C0805C100M4GACTU Series= C0G/NP0	Cap= 10.0 pF VDC= 16.0 V IRMS= 0.0 A	1	\$0.01	 0805 7 mm ²
3.	Cin	MuRata	GRM21BR61C106KE15L Series= X5R	Cap= 10.0 uF ESR= 4.127 mOhm VDC= 16.0 V IRMS= 2.46634 A	2	\$0.03	 0805 7 mm ²
4.	Cout	MuRata	GRM319R61C106KE15D Series= X5R	Cap= 10.0 uF ESR= 4.608 mOhm VDC= 16.0 V IRMS= 2.54841 A	2	\$0.04	 1206 11 mm ²
5.	Creg	MuRata	GRM155R61A474KE15D Series= X5R	Cap= 470.0 nF VDC= 10.0 V IRMS= 0.0 A	1	\$0.01	 0402 3 mm ²
6.	Css	MuRata	GRM033R61A822KA01D Series= X5R	Cap= 8.2 nF VDC= 10.0 V IRMS= 0.0 A	1	\$0.01	 0201 2 mm ²
7.	L1	Bourns	SDR0603-3R3ML	L= 3.3 uH DCR= 50.0 mOhm	1	\$0.18	 SDR0603 61 mm ²
8.	Ren	Vishay-Dale	CRCW040210K0FKED Series= CRCW..e3	Res= 10.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
9.	Rfbb	Yageo America	RC0603FR-0724KL Series= ?	Res= 24.0 kOhm Power= 100.0 mW Tolerance= 1.0%	1	\$0.01	 0603 5 mm ²
10.	Rfbt	Vishay-Dale	CRCW0402133KFKED Series= CRCW..e3	Res= 133.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
11.	U1	Texas Instruments	TPS54329DDAR	Switcher	1	\$0.73	 DDA0008E 57 mm ²

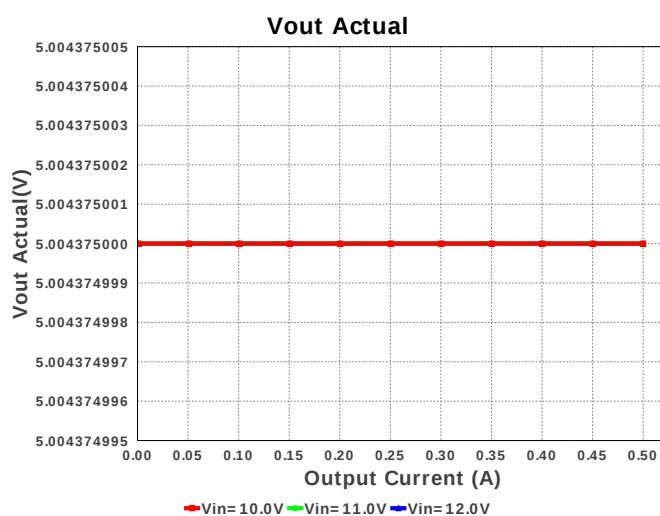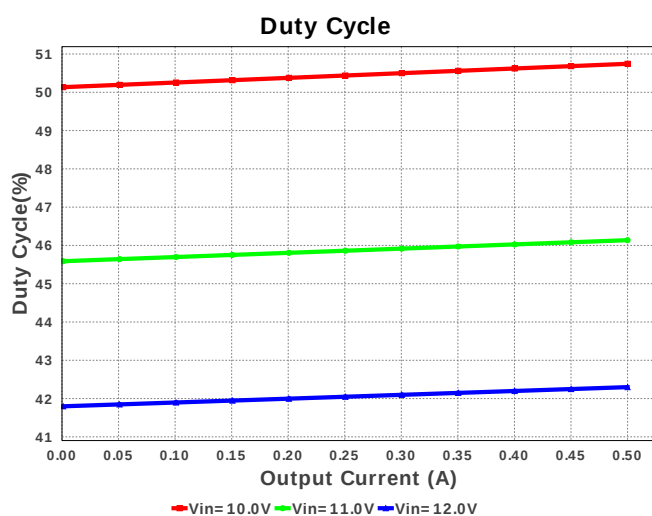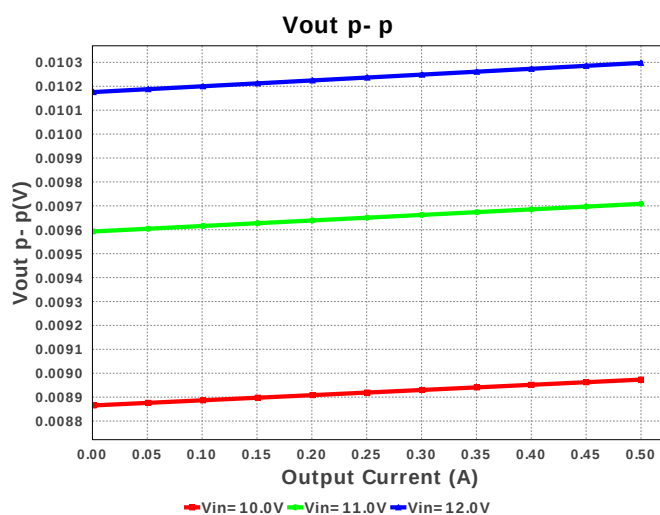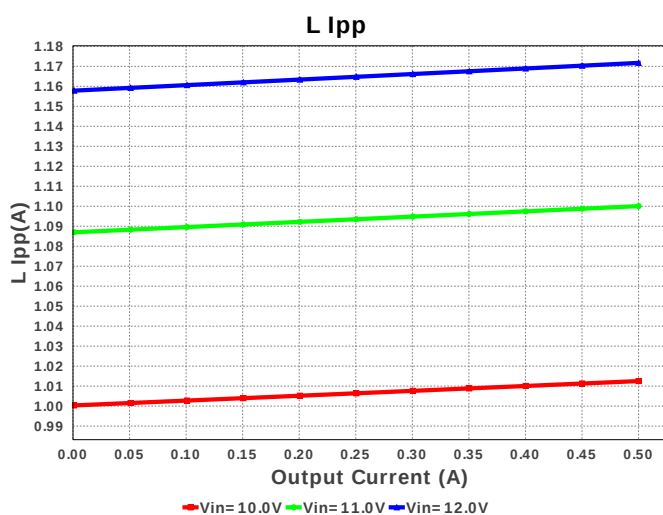

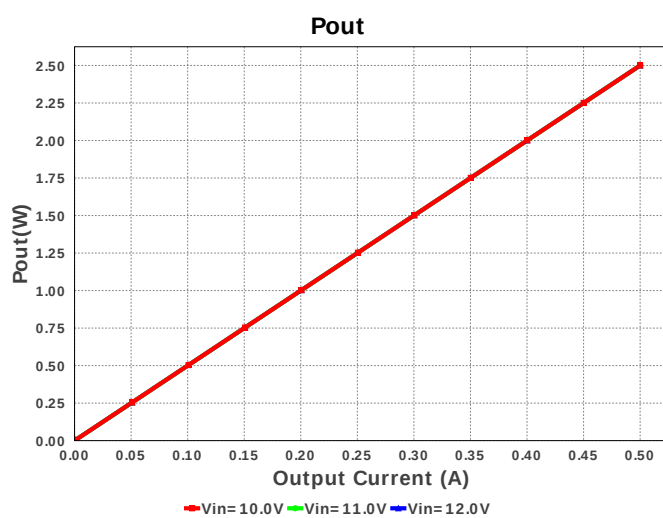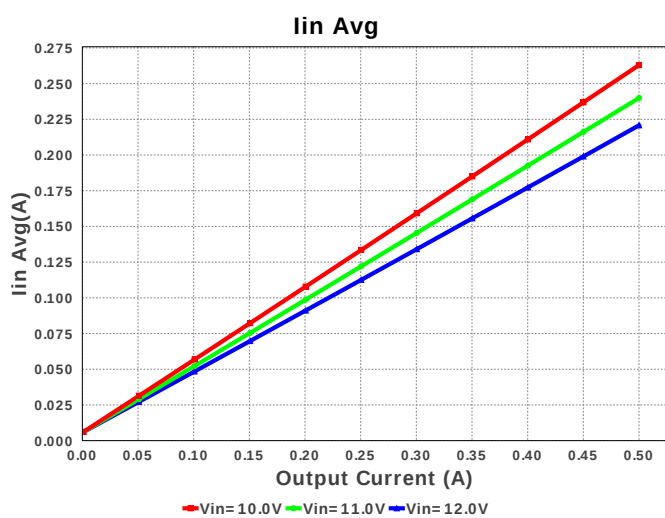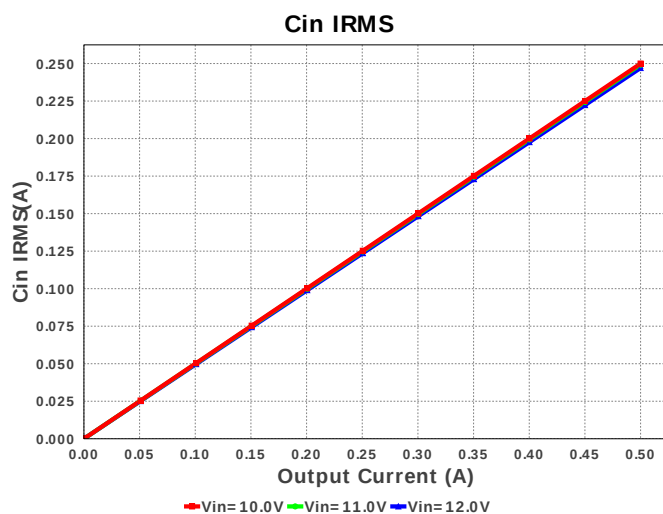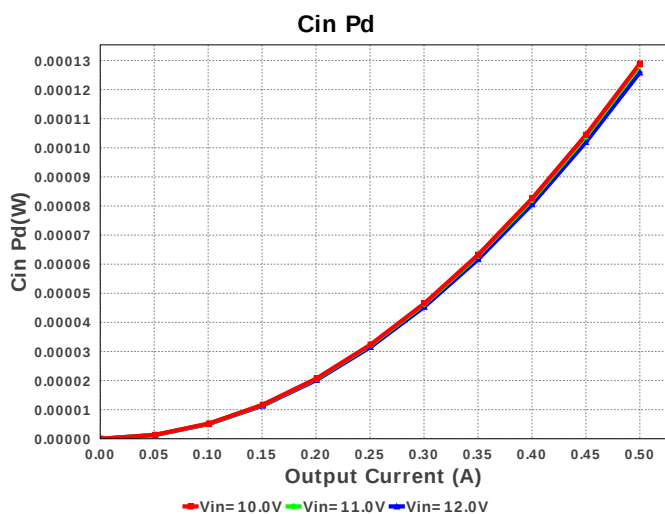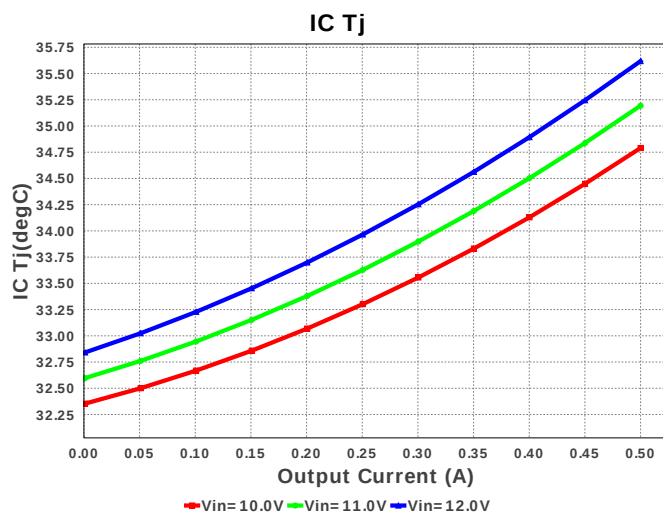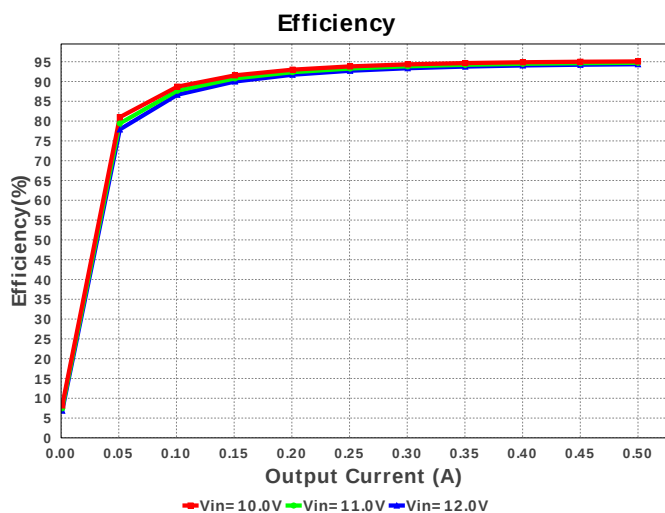

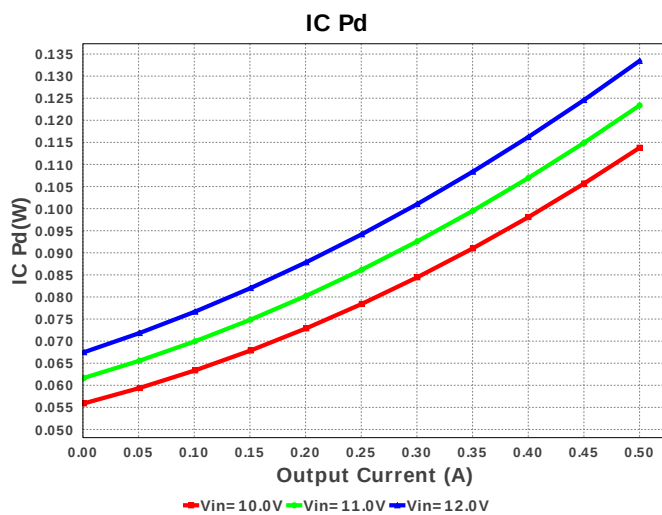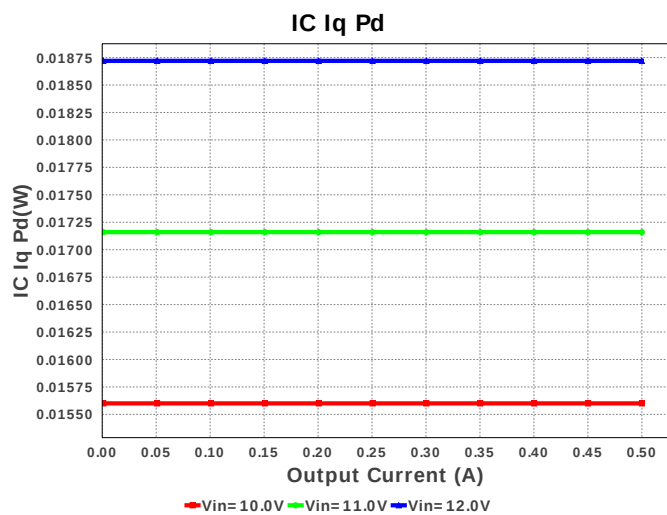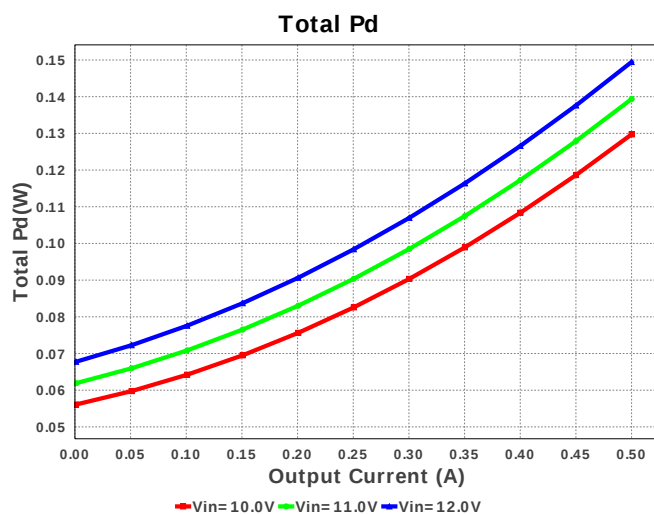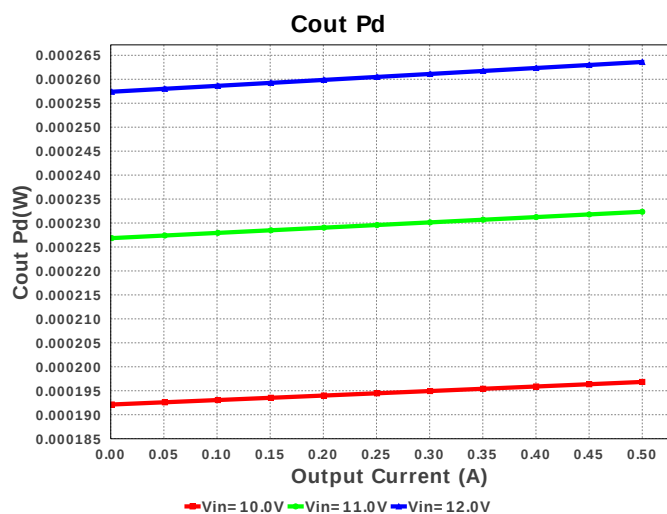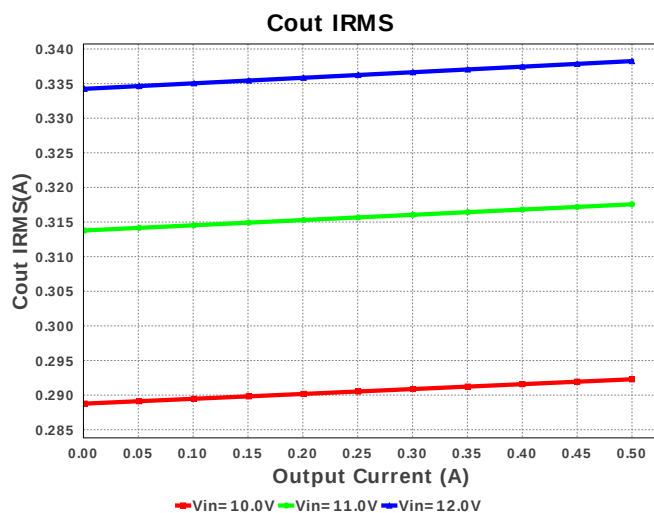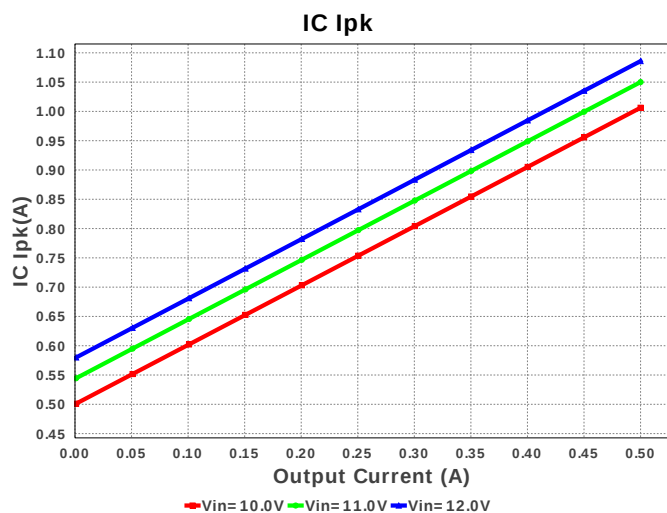

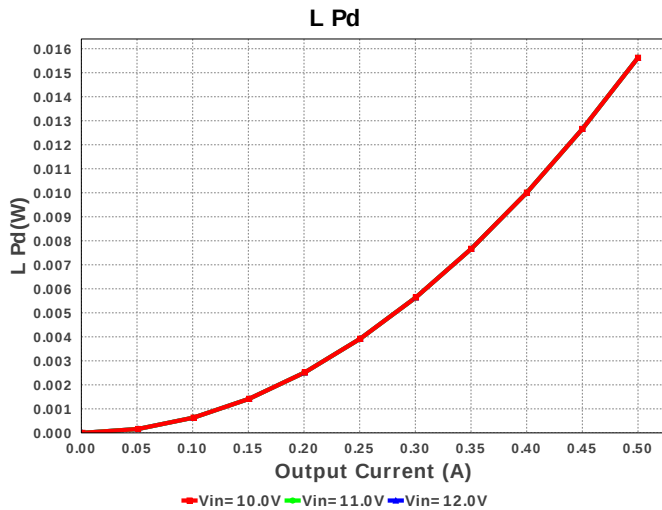

Operating Values

#	Name	Value	Category	Description
1.	Cin IRMS	247.017 mA	Current	Input capacitor RMS ripple current
2.	Cout IRMS	338.25 mA	Current	Output capacitor RMS ripple current
3.	IC Ipk	1.086 A	Current	Peak switch current in IC
4.	Iin Avg	220.79 mA	Current	Average input current
5.	L Ipp	1.172 A	Current	Peak-to-peak inductor ripple current
6.	BOM Count	13	General	Total Design BOM count
7.	FootPrint	179.0 mm ²	General	Total Foot Print Area of BOM components
8.	Frequency	765.742 kHz	General	Switching frequency
9.	Pout	2.5 W	General	Total output power
10.	Total BOM	\$1.12	General	Total BOM Cost
11.	Vout Actual	5.004 V	Op_Point	Vout Actual calculated based on selected voltage divider resistors
12.	Vout OP	5.0 V	Op_Point	Operational Output Voltage
13.	Duty Cycle	42.299 %	Op_point	Duty cycle
14.	Efficiency	94.359 %	Op_point	Steady state efficiency
15.	IC Tj	35.618 degC	Op_point	IC junction temperature
16.	ICThetaJA	42.1 degC/W	Op_point	IC junction-to-ambient thermal resistance
17.	IOUT_OP	500.0 mA	Op_point	Iout operating point
18.	VIN_OP	12.0 V	Op_point	Vin operating point
19.	Vout p-p	10.298 mV	Op_point	Peak-to-peak output ripple voltage
20.	Cin Pd	125.909 μW	Power	Input capacitor power dissipation
21.	Cout Pd	263.608 μW	Power	Output capacitor power dissipation
22.	IC Iq Pd	18.72 mW	Power	IC Iq Pd
23.	IC Pd	133.454 mW	Power	IC power dissipation
24.	L Pd	15.625 mW	Power	Inductor power dissipation
25.	Total Pd	149.457 mW	Power	Total Power Dissipation
26.	Vout Tolerance	3.573 %		Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable

Design Inputs

#	Name	Value	Description
1.	Iout	500.0 m	Maximum Output Current
2.	VinMax	12.0	Maximum input voltage
3.	VinMin	10.0	Minimum input voltage
4.	Vout	5.0	Output Voltage
5.	base_pn	TPS54329	Base Product Number
6.	source	DC	Input Source Type
7.	Ta	30.0	Ambient temperature

Design Assistance

1. **TPS54329** Product Folder : <http://www.ti.com/product/TPS54329> : contains the data sheet and other resources.

Texas Instruments' WEBENCH simulation tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Simulations are created using Texas Instruments' published specifications as well as the published specifications of other device manufacturers. While Texas Instruments does update this information periodically, this information may not be current at the time the simulation is built. Texas Instruments does not warrant the accuracy or completeness of the specifications or any information contained therein. Texas Instruments does not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. Texas Instruments does not warrant that the designs are production worthy.

You should completely validate and test your design implementation to confirm the system functionality for your application prior to production.

Use of Texas Instruments' WEBENCH simulation tools is subject to [Texas Instruments' Site Terms and Conditions of Use](#). Prototype boards based on WEBENCH created designs are provided AS IS without warranty of any kind for evaluation and testing purposes and are subject to the terms of the [Evaluation License Agreement](#).