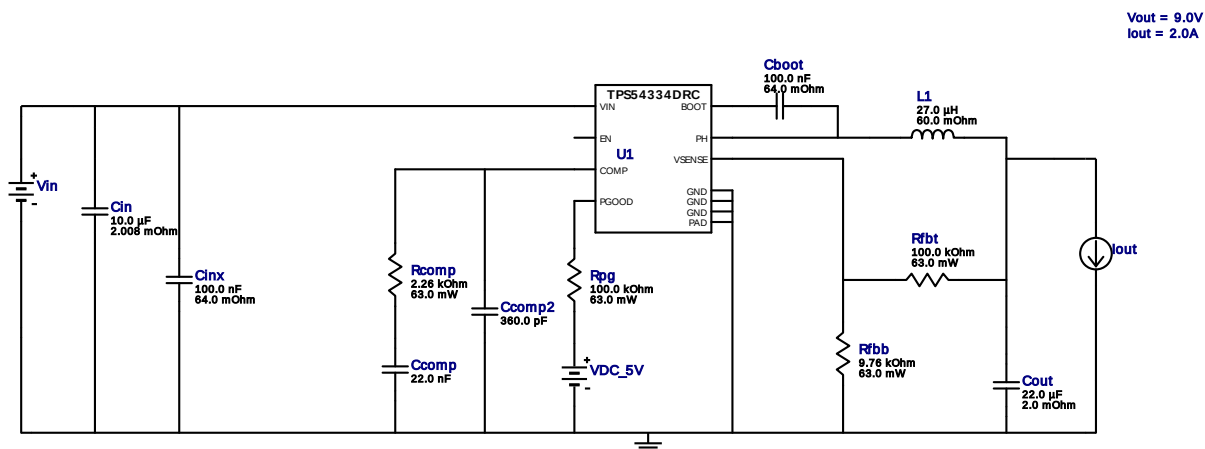


WEBENCH® Design Report





Design : 4742013/5 TPS54334DRCR
TPS54334DRCR 14.0V-25.0V to 9.00V @ 2.0A















Electrical BOM


#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	Cboot	Kemet	C0805C104K5RACTU Series= X7R	Cap= 100.0 nF ESR= 64.0 mOhm VDC= 50.0 V IRMS= 1.64 A	1	\$0.01	0805 7 mm ²
2.	Ccomp	Yageo America	CC0805KRX7R9BB223 Series= X7R	Cap= 22.0 nF VDC= 50.0 V IRMS= 0.0 A	1	\$0.01	0805 7 mm ²
3.	Ccomp2	MuRata	GRM1555C1H361JA01D Series= C0G/NP0	Cap= 360.0 pF VDC= 50.0 V IRMS= 0.0 A	1	\$0.01	0402 3 mm ²
4.	Cin	MuRata	GRM32ER7YA106KA12L Series= X7R	Cap= 10.0 uF ESR= 2.008 mOhm VDC= 35.0 V IRMS= 4.6772 A	1	\$0.22	1210_280 15 mm ²
5.	Cinx	Kemet	C0805C104K5RACTU Series= X7R	Cap= 100.0 nF ESR= 64.0 mOhm VDC= 50.0 V IRMS= 1.64 A	1	\$0.01	0805 7 mm ²
6.	Cout	MuRata	GRM32ER61C226ME20L Series= X5R	Cap= 22.0 uF ESR= 2.0 mOhm VDC= 16.0 V IRMS= 3.68 A	1	\$0.12	1210 15 mm ²
7.	L1	Bourns	SDR1307-270ML	L= 27.0 uH DCR= 60.0 mOhm	1	\$0.35	SDR1307 227 mm ²
8.	Rcomp	Vishay-Dale	CRCW04022K26FKED Series= CRCW..e3	Res= 2.26 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²
9.	Rfbb	Vishay-Dale	CRCW04029K76FKED Series= CRCW..e3	Res= 9.76 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
10.	Rfbt	Vishay-Dale	CRCW0402100KFKED Series= CRCW..e3	Res= 100.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm²
11.	Rpg	Vishay-Dale	CRCW0402100KFKED Series= CRCW..e3	Res= 100.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm²
12.	U1	Texas Instruments	TPS54334DRCR	Switcher	1	\$0.95	 DR0010J 16 mm²

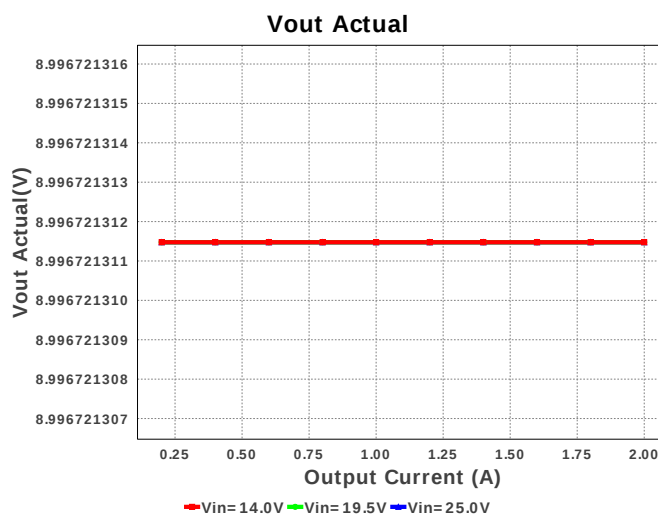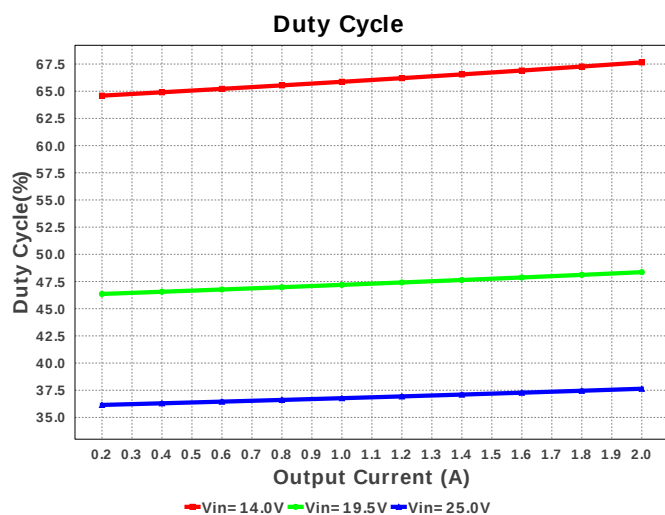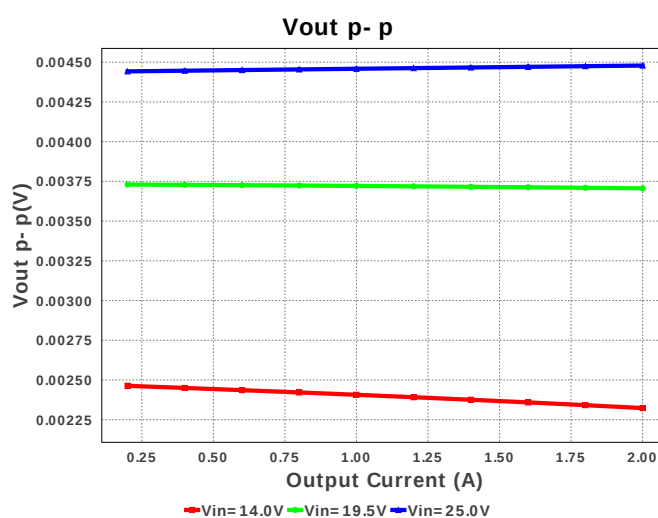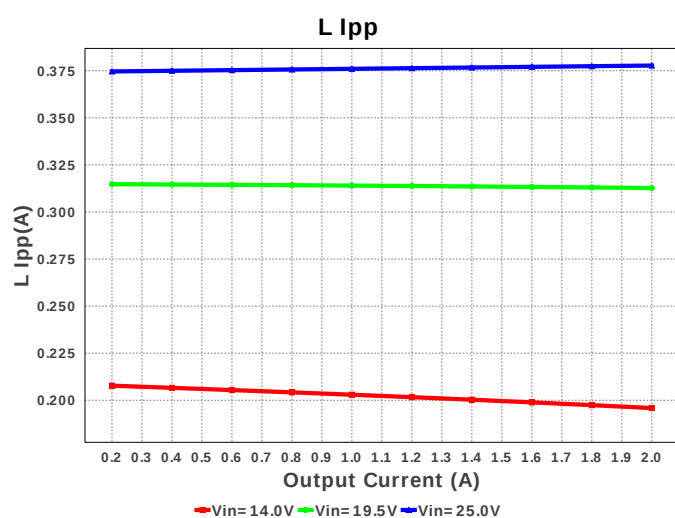

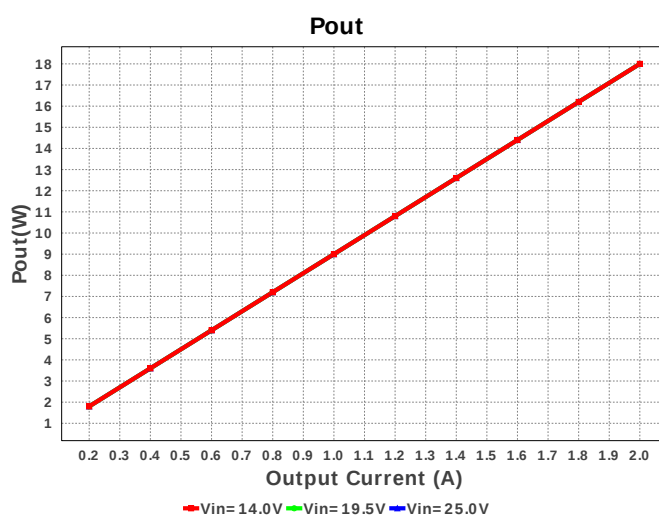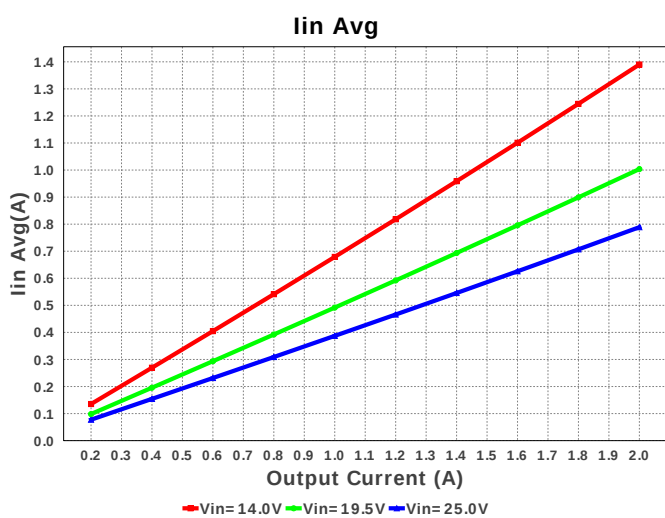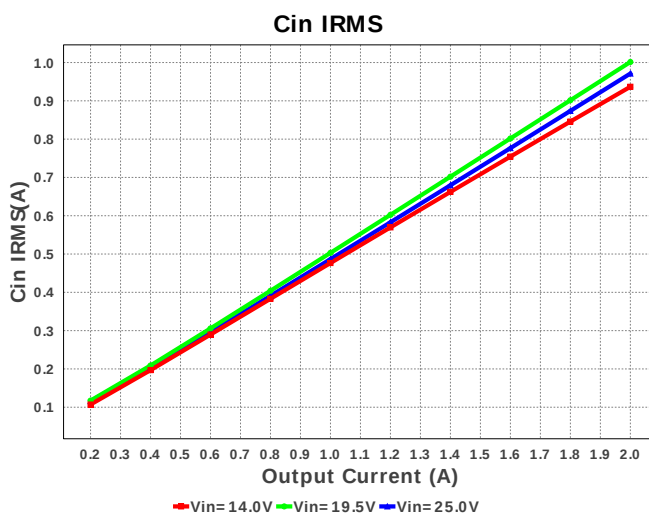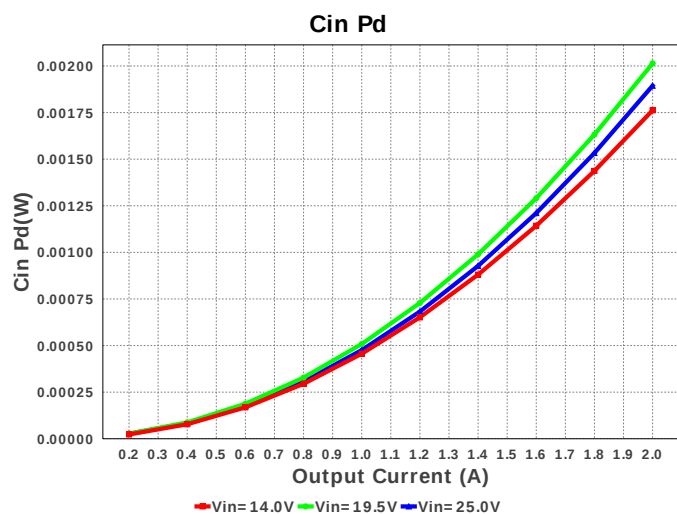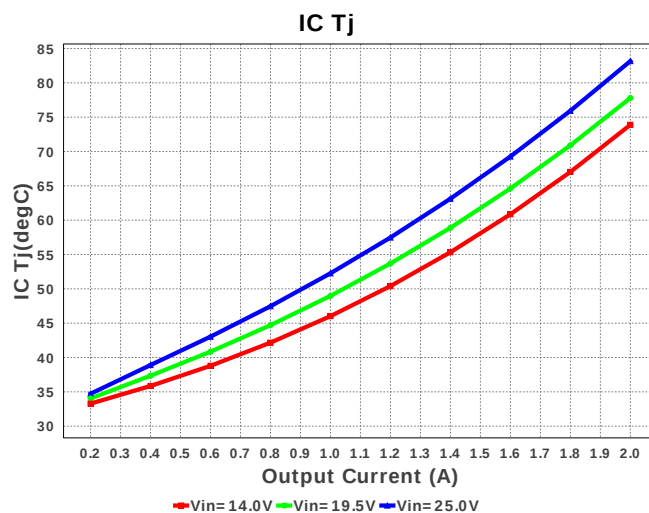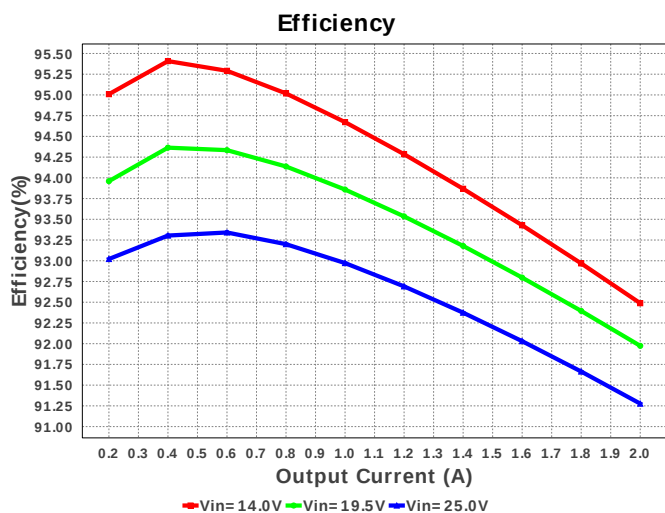

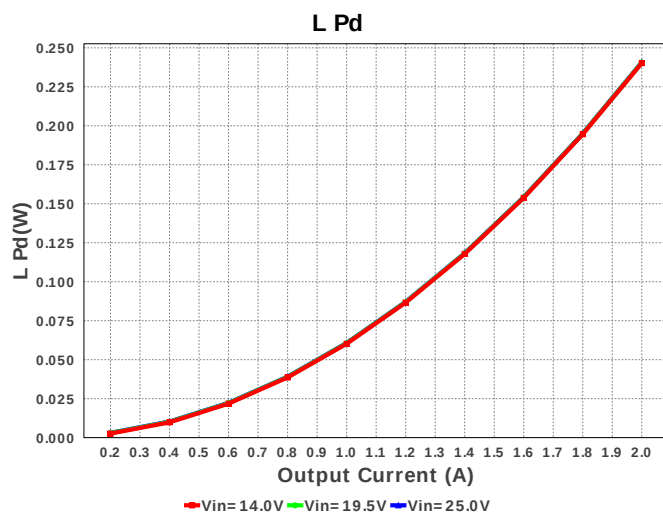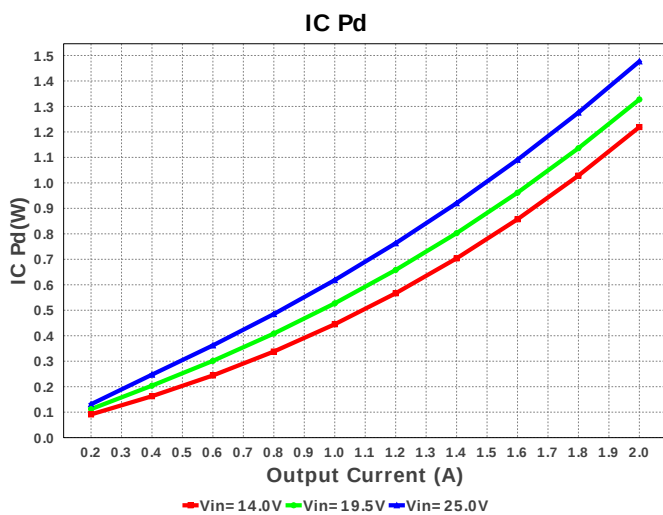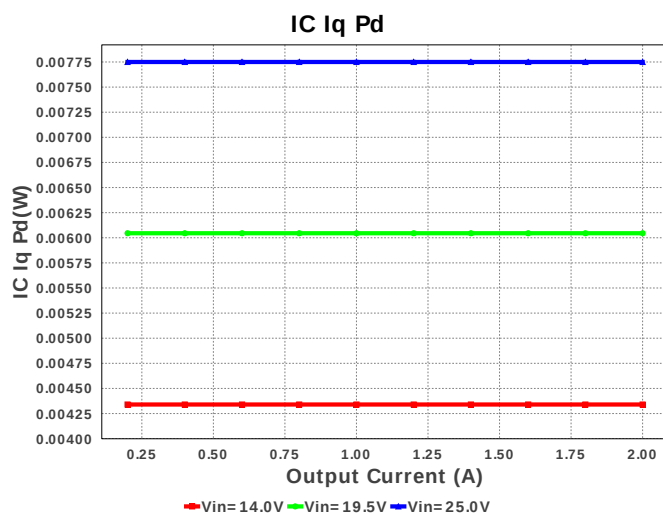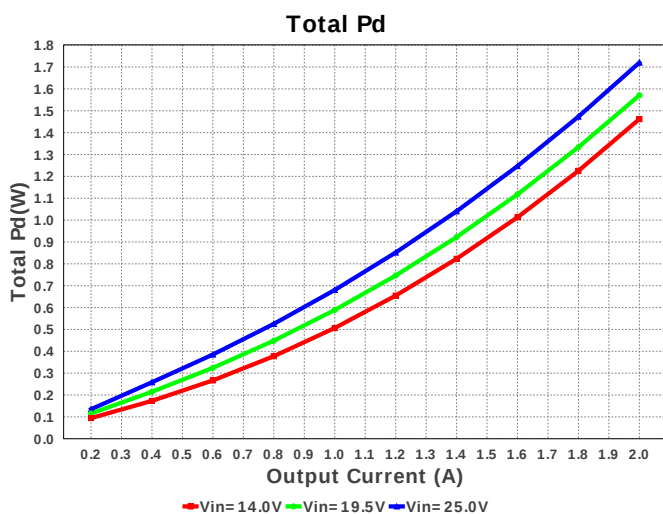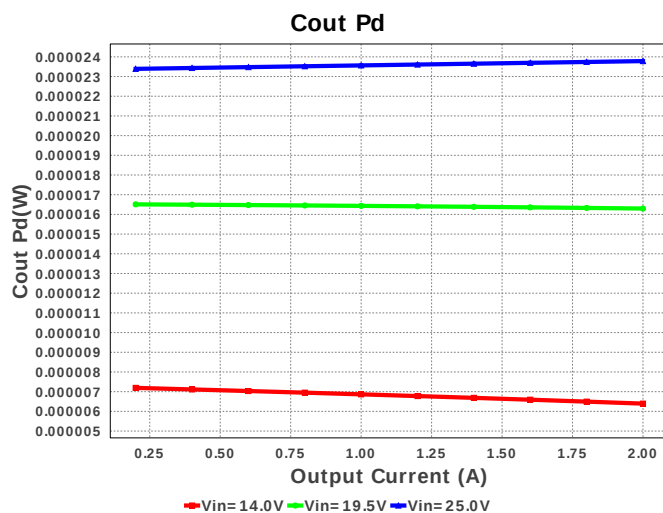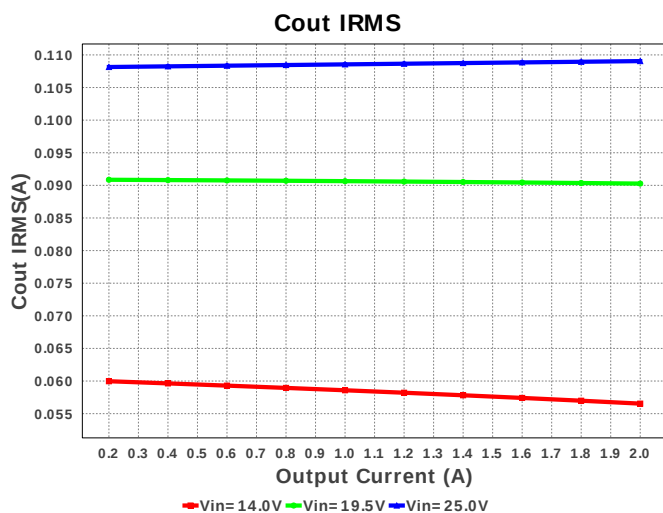

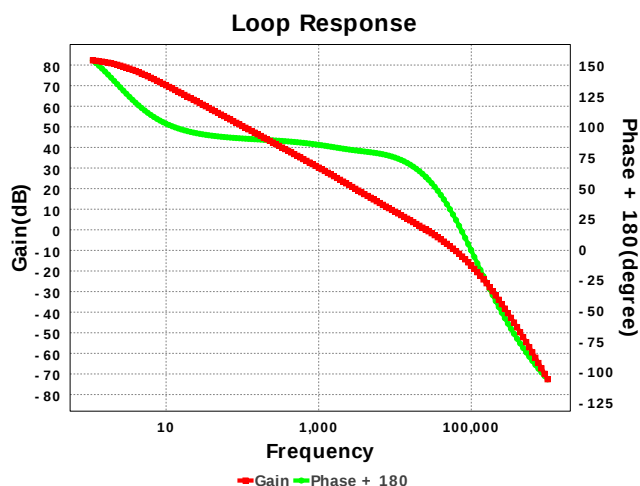

Operating Values

#	Name	Value	Category	Description
1.	Cin IRMS	971.264 mA	Current	Input capacitor RMS ripple current
2.	Cout IRMS	109.05 mA	Current	Output capacitor RMS ripple current
3.	Iin Avg	788.81 mA	Current	Average input current
4.	L Ipp	377.76 mA	Current	Peak-to-peak inductor ripple current
5.	BOM Count	12	General	Total Design BOM count
6.	FootPrint	307.0 mm ²	General	Total Foot Print Area of BOM components
7.	Frequency	570.0 kHz	General	Switching frequency
8.	IC Tolerance	10.0 mV	General	IC Feedback Tolerance
9.	Pout	18.0 W	General	Total output power
10.	Total BOM	\$1.72	General	Total BOM Cost
11.	ICThetaJA Effective	36.0 degC/W	Op_Point	Effective IC Junction-to-Ambient Thermal Resistance
12.	Low Freq Gain	82.243 dB	Op_Point	Gain at 10Hz
13.	Vout Actual	8.997 V	Op_Point	Vout Actual calculated based on selected voltage divider resistors
14.	Vout OP	9.0 V	Op_Point	Operational Output Voltage
15.	Cross Freq	25.605 kHz	Op_point	Bode plot crossover frequency
16.	Duty Cycle	37.638 %	Op_point	Duty cycle
17.	Efficiency	91.277 %	Op_point	Steady state efficiency
18.	Gain Marg	-17.171 dB	Op_point	Bode Plot Gain Margin
19.	IC Tj	83.167 degC	Op_point	IC junction temperature
20.	IOUT_OP	2.0 A	Op_point	Iout operating point
21.	Phase Marg	59.147 deg	Op_point	Bode Plot Phase Margin
22.	VIN_OP	25.0 V	Op_point	Vin operating point
23.	Vout p-p	4.479 mV	Op_point	Peak-to-peak output ripple voltage
24.	Cin Pd	1.894 mW	Power	Input capacitor power dissipation
25.	Cout Pd	23.784 μ W	Power	Output capacitor power dissipation
26.	IC Iq Pd	7.75 mW	Power	IC Iq Pd
27.	IC Pd	1.477 W	Power	IC power dissipation
28.	L Pd	240.714 mW	Power	Inductor power dissipation
29.	Total Pd	1.72 W	Power	Total Power Dissipation
30.	Vout Tolerance	3.114 %		Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable

Design Inputs

#	Name	Value	Description
1.	Iout	2.0	Maximum Output Current
2.	VinMax	25.0	Maximum input voltage
3.	VinMin	14.0	Minimum input voltage
4.	Vout	9.0	Output Voltage
5.	base_pn	TPS54334	Base Product Number
6.	source	DC	Input Source Type
7.	Ta	30.0	Ambient temperature

Design Assistance

1. **TPS54334** Product Folder : <http://www.ti.com/product/TPS54334> : contains the data sheet and other resources.

Texas Instruments' WEBENCH simulation tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Simulations are created using Texas Instruments' published specifications as well as the published specifications of other device manufacturers. While Texas Instruments does update this information periodically, this information may not be current at the time the simulation is built. Texas Instruments does not warrant the accuracy or completeness of the specifications or any information contained therein. Texas Instruments does not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. Texas Instruments does not warrant that the designs are production worthy.

You should completely validate and test your design implementation to confirm the system functionality for your application prior to production.

Use of Texas Instruments' WEBENCH simulation tools is subject to [Texas Instruments' Site Terms and Conditions of Use](#). Prototype boards based on WEBENCH created designs are provided AS IS without warranty of any kind for evaluation and testing purposes and are subject to the terms of the [Evaluation License Agreement](#).