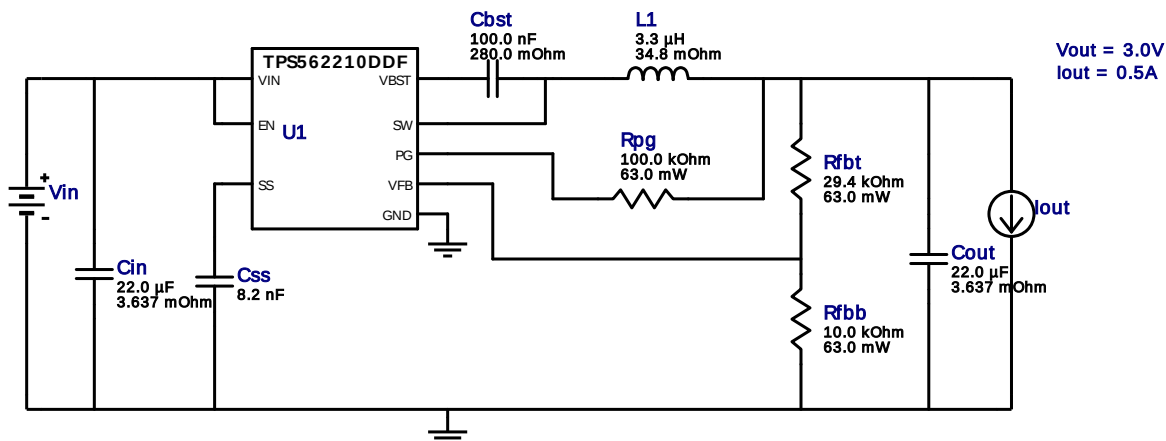


WEBENCH® Design Report





Design : 4742013/139 TPS562210DDFR
TPS562210DDFR 4.5V-5.5V to 3.00V @ 0.5A















Electrical BOM


#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	Cbst	AVX	08053C104KAT2A Series= X7R	Cap= 100.0 nF ESR= 280.0 mOhm VDC= 25.0 V IRMS= 0.0 A	1	\$0.01	0805 7 mm ²
2.	Cin	MuRata	GRM31CR61A226KE19L Series= X5R	Cap= 22.0 uF ESR= 3.637 mOhm VDC= 10.0 V IRMS= 3.56456 A	1	\$0.07	1206_190 11 mm ²
3.	Cout	MuRata	GRM31CR61A226KE19L Series= X5R	Cap= 22.0 uF ESR= 3.637 mOhm VDC= 10.0 V IRMS= 3.56456 A	1	\$0.07	1206_190 11 mm ²
4.	Css	MuRata	GRM033R61A822KA01D Series= X5R	Cap= 8.2 nF VDC= 10.0 V IRMS= 0.0 A	1	\$0.01	0201 2 mm ²
5.	L1	Coilcraft	XFL4020-332MEB	L= 3.3 uH DCR= 34.8 mOhm	1	\$0.55	XFL4020 25 mm ²
6.	Rfbb	Vishay-Dale	CRCW040210K0FKED Series= CRCW..e3	Res= 10.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²
7.	Rfbs	Vishay-Dale	CRCW040229K4FKED Series= CRCW..e3	Res= 29.4 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²
8.	Rpg	Vishay-Dale	CRCW0402100KFKED Series= CRCW..e3	Res= 100.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
9.	U1	Texas Instruments	TPS562210DDFR	Switcher	1	\$0.60	 DDF0008A 10 mm ²

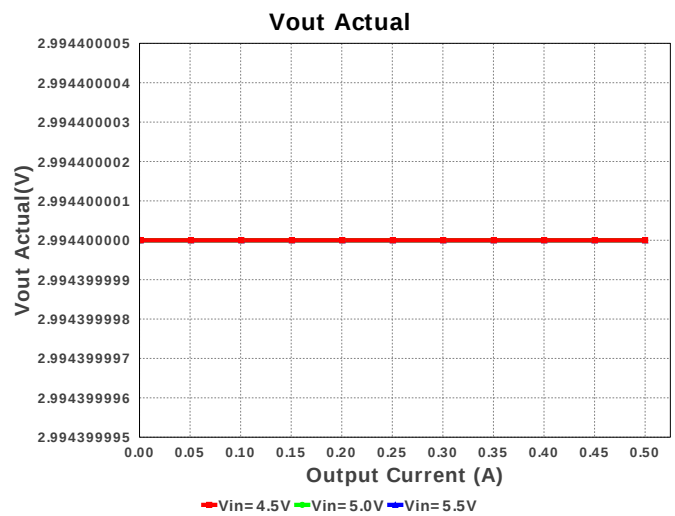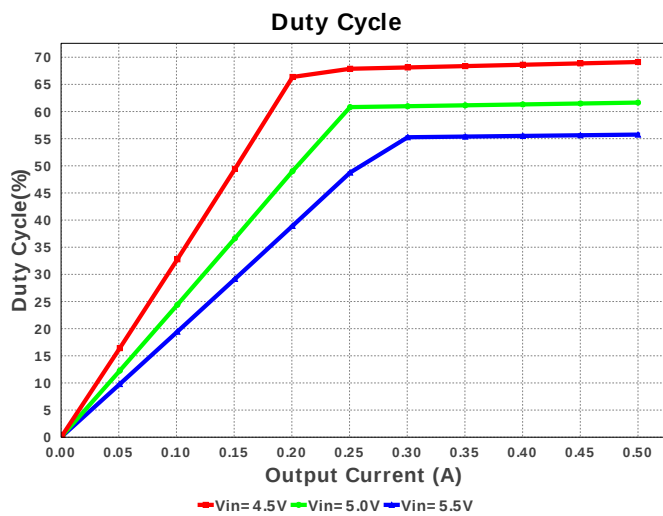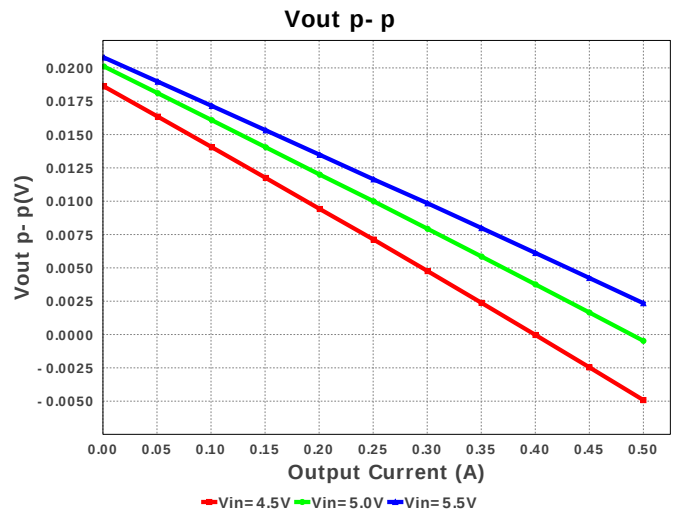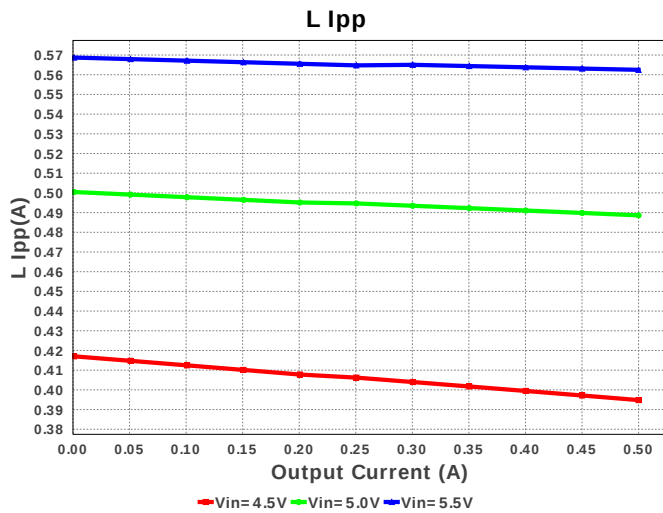

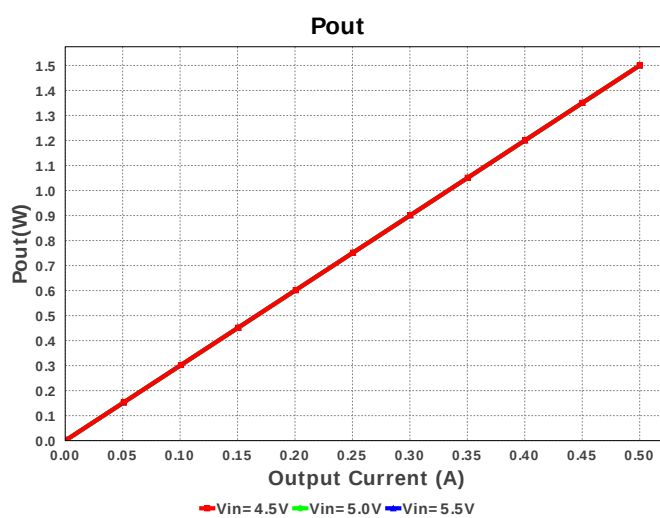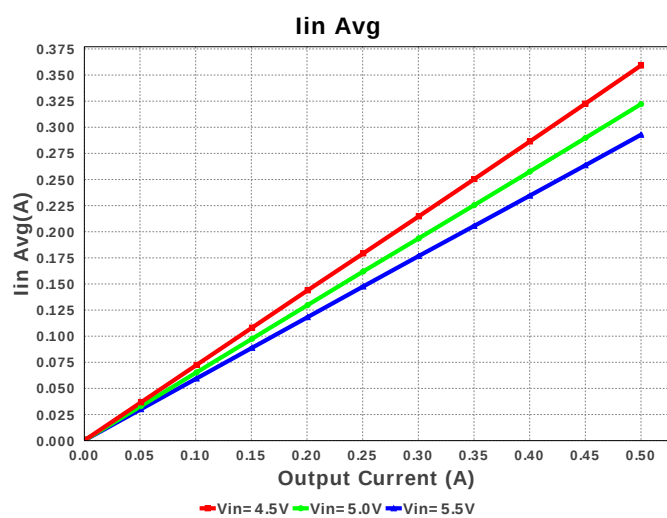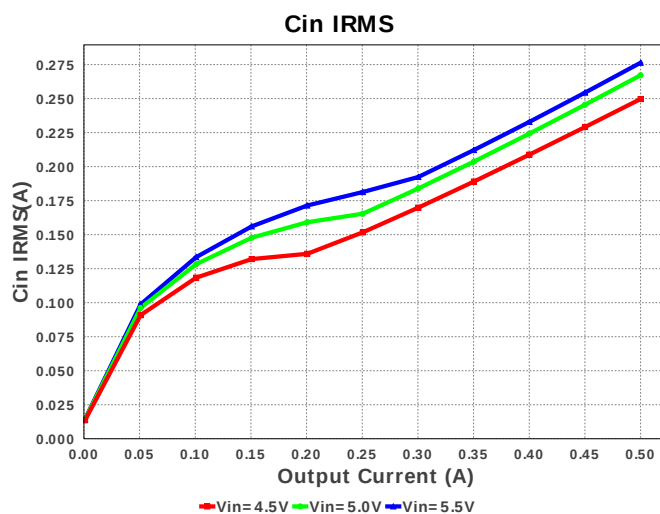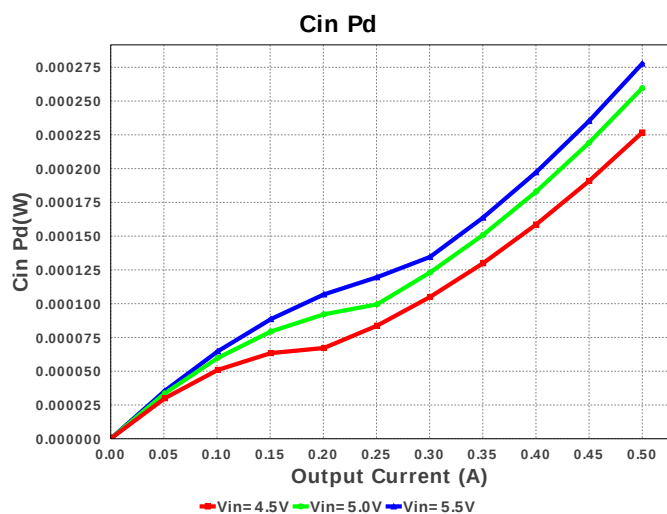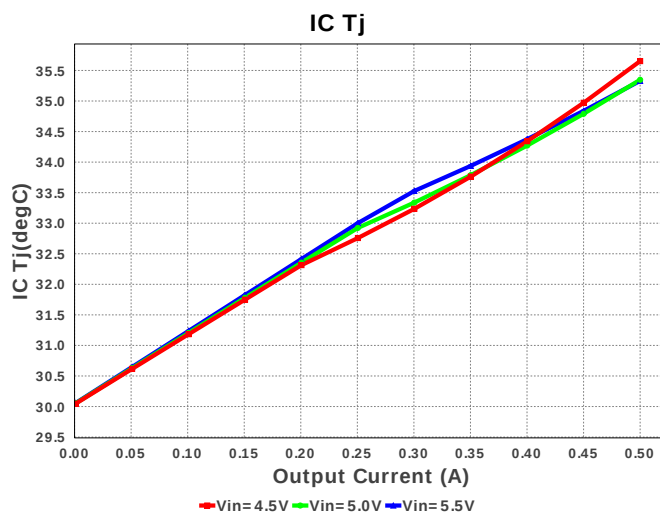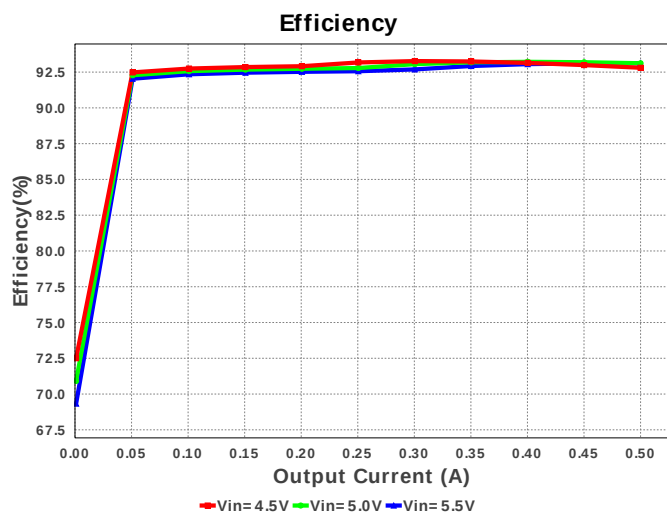

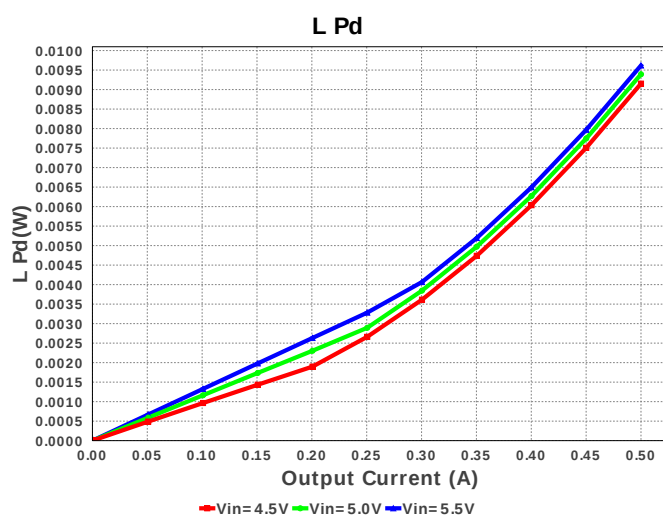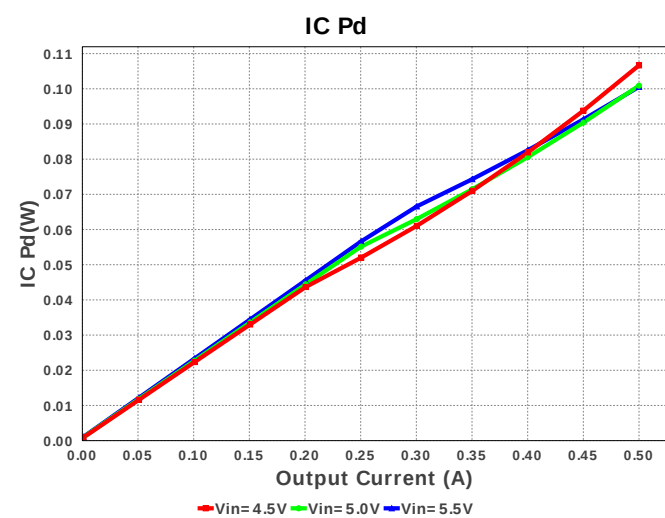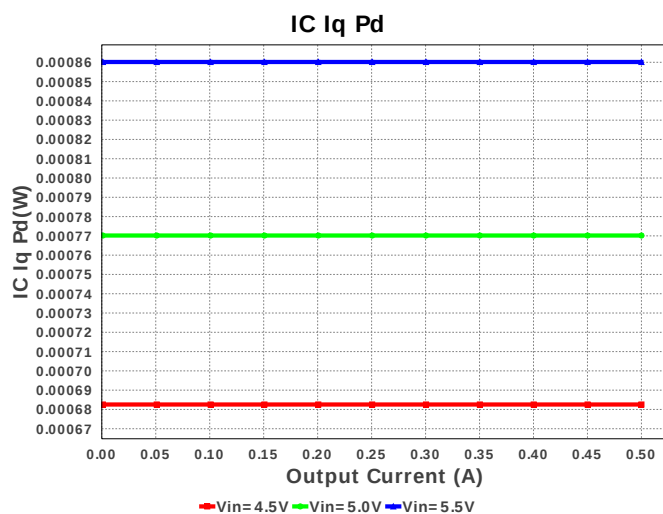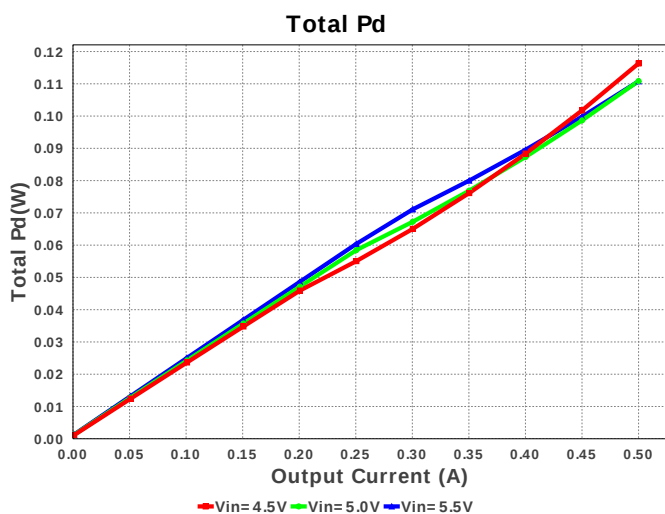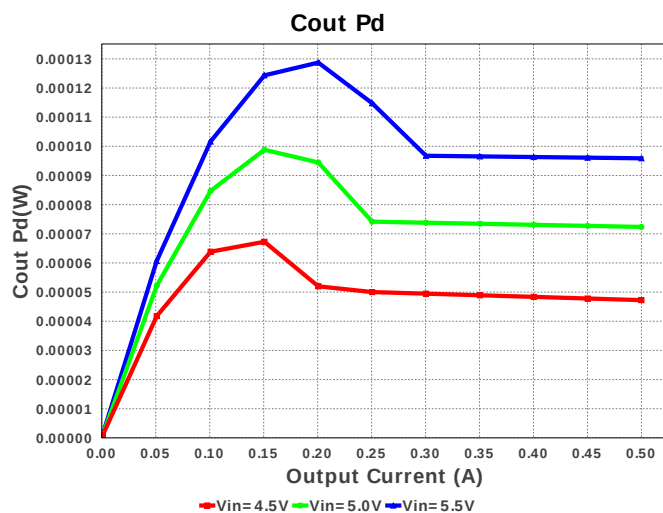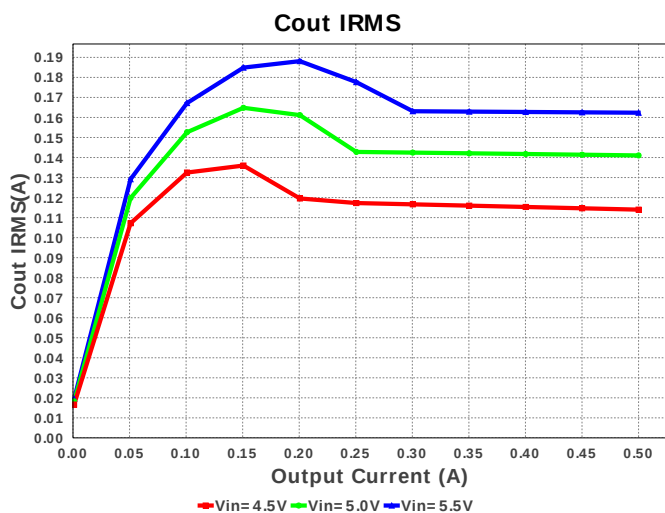

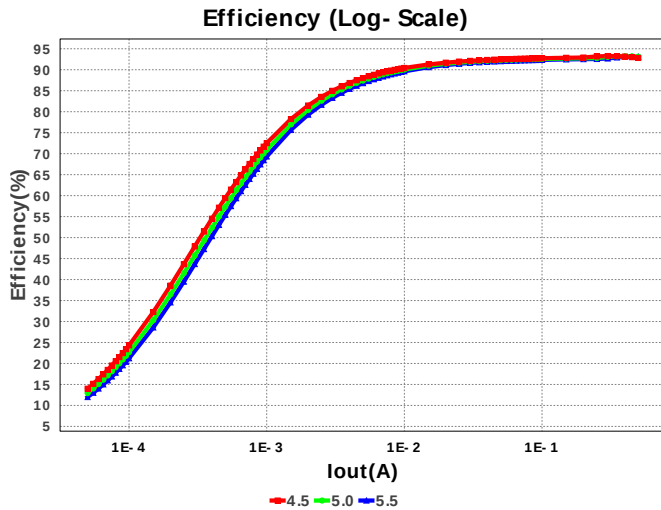

Operating Values

#	Name	Value	Category	Description
1.	Cin IRMS	276.355 mA	Current	Input capacitor RMS ripple current
2.	Cout IRMS	162.374 mA	Current	Output capacitor RMS ripple current
3.	Iin Avg	292.87 mA	Current	Average input current
4.	L Ipp	562.48 mA	Current	Peak-to-peak inductor ripple current
5.	BOM Count	9	General	Total Design BOM count
6.	FootPrint	75.0 mm ²	General	Total Foot Print Area of BOM components
7.	Frequency	722.789 kHz	General	Switching frequency
8.	Pout	1.5 W	General	Total output power
9.	Total BOM	\$1.34	General	Total BOM Cost
10.	Vout Actual	2.994 V	Op_Point	Vout Actual calculated based on selected voltage divider resistors
11.	Vout OP	3.0 V	Op_Point	Operational Output Voltage
12.	Duty Cycle	55.75 %	Op_point	Duty cycle
13.	Efficiency	93.123 %	Op_point	Steady state efficiency
14.	IC Tj	35.33 degC	Op_point	IC junction temperature
15.	ICThetaJA	53.0 degC/W	Op_point	IC junction-to-ambient thermal resistance
16.	IOUT_OP	500.0 mA	Op_point	Iout operating point
17.	VIN_OP	5.5 V	Op_point	Vin operating point
18.	Vout p-p	4.965 mV	Op_point	Peak-to-peak output ripple voltage
19.	Cin Pd	277.765 μ W	Power	Input capacitor power dissipation
20.	Cout Pd	95.89 μ W	Power	Output capacitor power dissipation
21.	IC Iq Pd	860.16 μ W	Power	IC Iq Pd
22.	IC Pd	100.56 mW	Power	IC power dissipation
23.	L Pd	9.618 mW	Power	Inductor power dissipation
24.	Total Pd	110.774 mW	Power	Total Power Dissipation
25.	Vout Tolerance	2.843 %		Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable

Design Inputs

#	Name	Value	Description
1.	Iout	500.0 m	Maximum Output Current
2.	VinMax	5.5	Maximum input voltage
3.	VinMin	4.5	Minimum input voltage
4.	Vout	3.0	Output Voltage
5.	base_pn	TPS562210	Base Product Number
6.	source	DC	Input Source Type
7.	Ta	30.0	Ambient temperature

Design Assistance

1. **TPS562210** Product Folder : <http://www.ti.com/product/TPS562210> : contains the data sheet and other resources.

Texas Instruments' WEBENCH simulation tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Simulations are created using Texas Instruments' published specifications as well as the published specifications of other device manufacturers. While Texas Instruments does update this information periodically, this information may not be current at the time the simulation is built. Texas Instruments does not warrant the accuracy or completeness of the specifications or any information contained therein. Texas Instruments does not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. Texas Instruments does not warrant that the designs are production worthy.

You should completely validate and test your design implementation to confirm the system functionality for your application prior to production.

Use of Texas Instruments' WEBENCH simulation tools is subject to [Texas Instruments' Site Terms and Conditions of Use](#). Prototype boards based on WEBENCH created designs are provided AS IS without warranty of any kind for evaluation and testing purposes and are subject to the terms of the [Evaluation License Agreement](#).