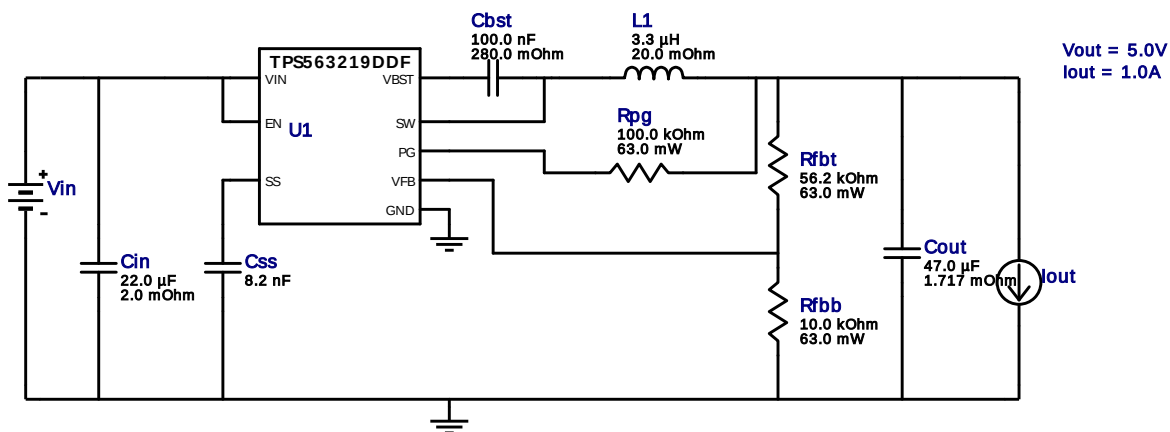


WEBENCH® Design Report





Design : 4742013/64 TPS563219DDFR
TPS563219DDFR 12.0V-13.0V to 5.00V @ 1.0A















Electrical BOM

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	Cbst	AVX	08053C104KAT2A Series= X7R	Cap= 100.0 nF ESR= 280.0 mOhm VDC= 25.0 V IRMS= 0.0 A	1	\$0.01	 0805 7 mm²
2.	Cin	MuRata	GRM32ER61E226KE15L Series= X5R	Cap= 22.0 uF ESR= 2.0 mOhm VDC= 25.0 V IRMS= 3.67 A	1	\$0.16	 1210 15 mm²
3.	Cout	TDK	C3216JB1A476M Series= JB	Cap= 47.0 uF ESR= 1.717 mOhm VDC= 10.0 V IRMS= 0.0 A	1	\$0.34	 1206 11 mm²
4.	Css	MuRata	GRM033R61A822KA01D Series= X5R	Cap= 8.2 nF VDC= 10.0 V IRMS= 0.0 A	1	\$0.01	 0201 2 mm²
5.	L1	Bourns	SRR6038-3R3Y	L= 3.3 uH DCR= 20.0 mOhm	1	\$0.26	 SRR6038 77 mm²
6.	Rfbb	Vishay-Dale	CRCW040210K0FKED Series= CRCW..e3	Res= 10.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm²
7.	Rfbt	Vishay-Dale	CRCW040256K2FKED Series= CRCW..e3	Res= 56.2 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm²
8.	Rpg	Vishay-Dale	CRCW0402100KFKED Series= CRCW..e3	Res= 100.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm²

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
9.	U1	Texas Instruments	TPS563219DDFR	Switcher	1	\$0.80	 DDF0008A 10 mm ²

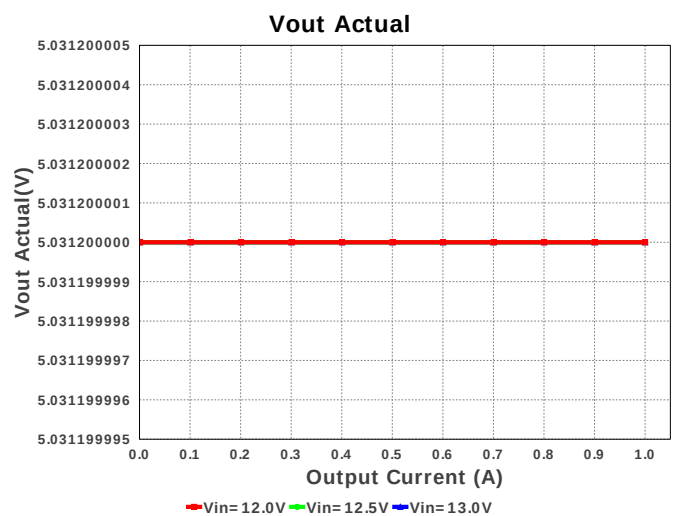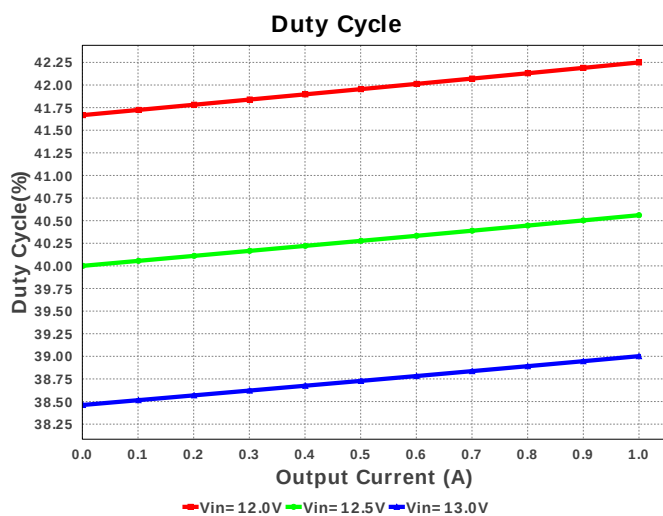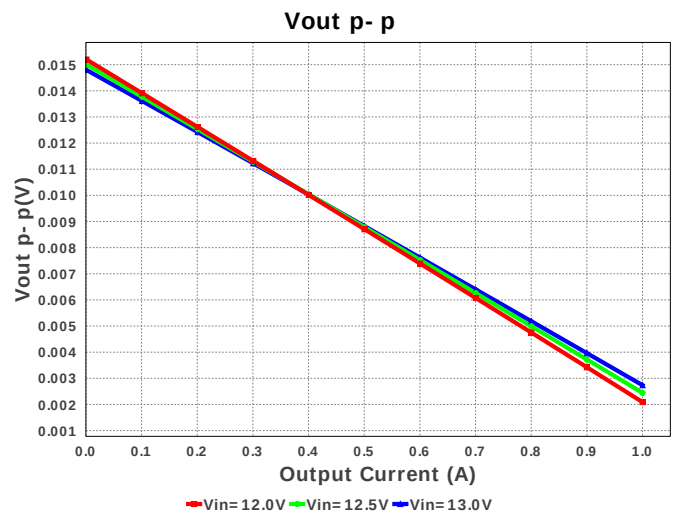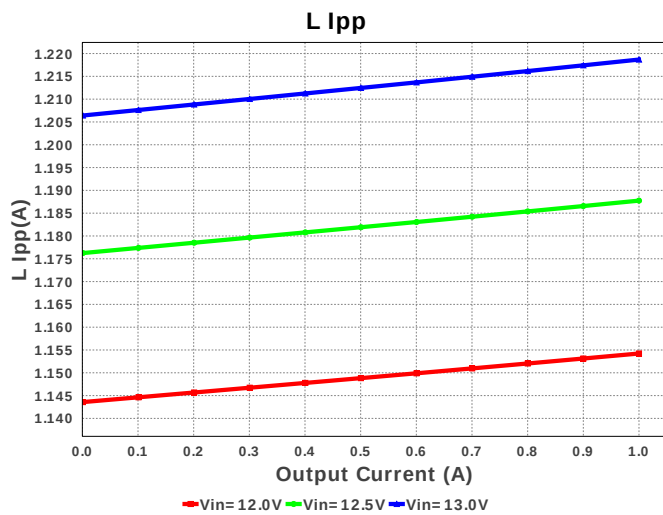

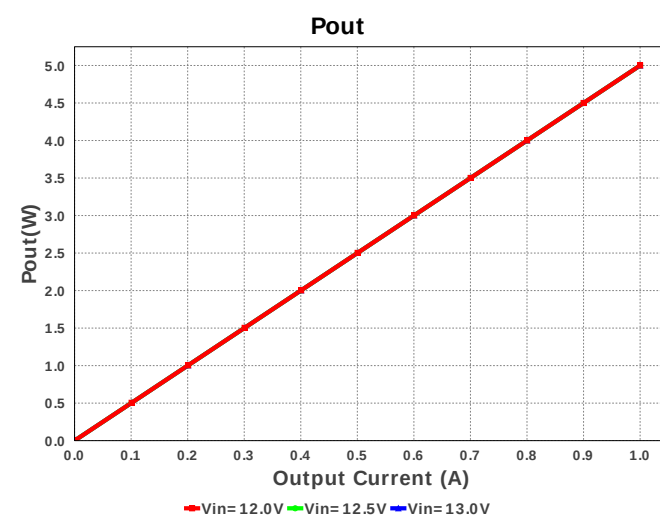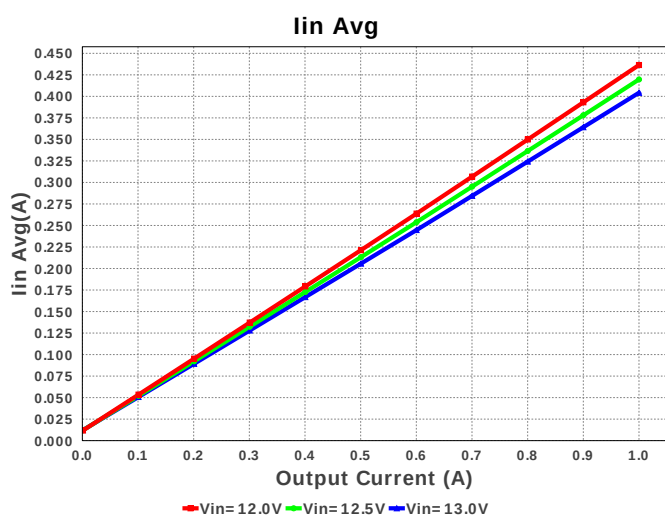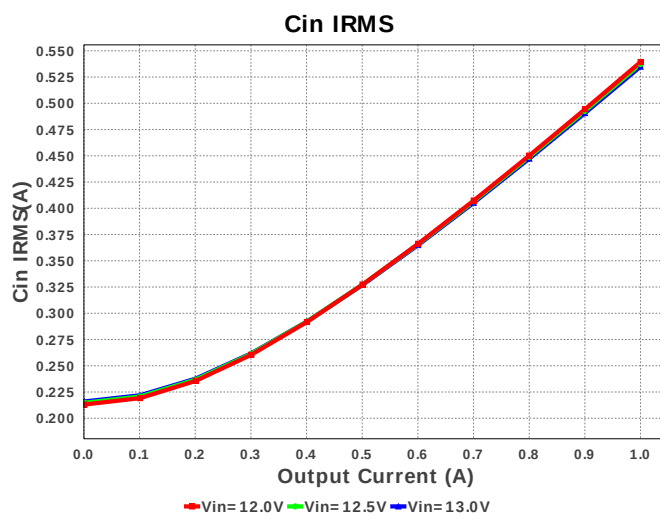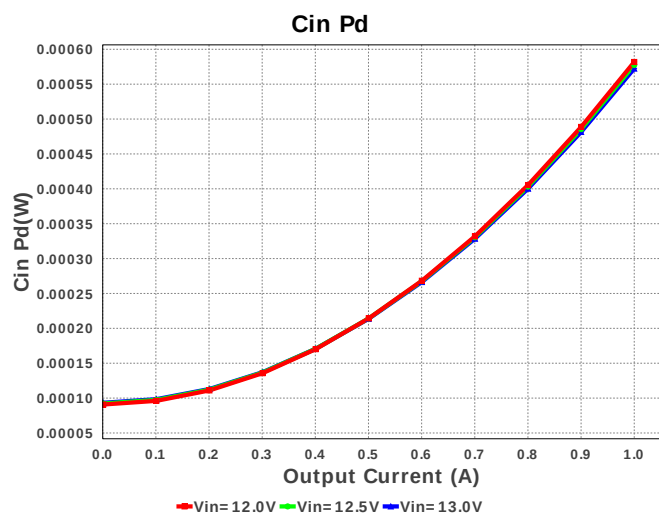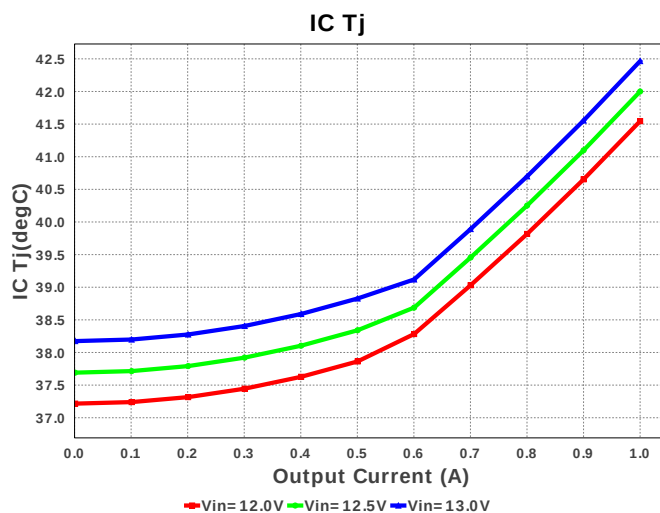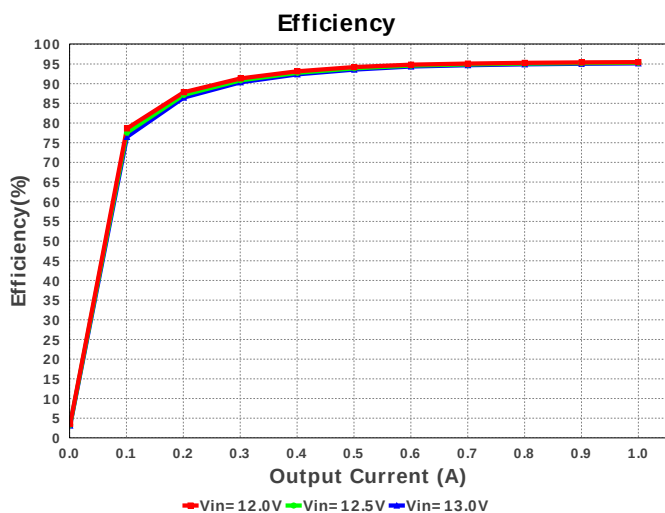

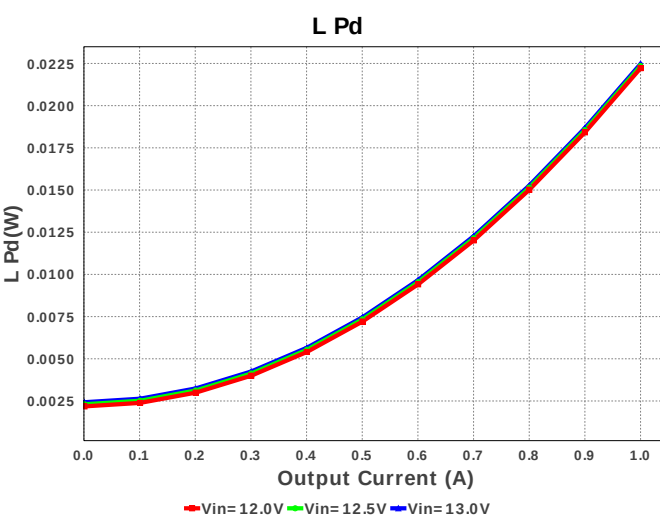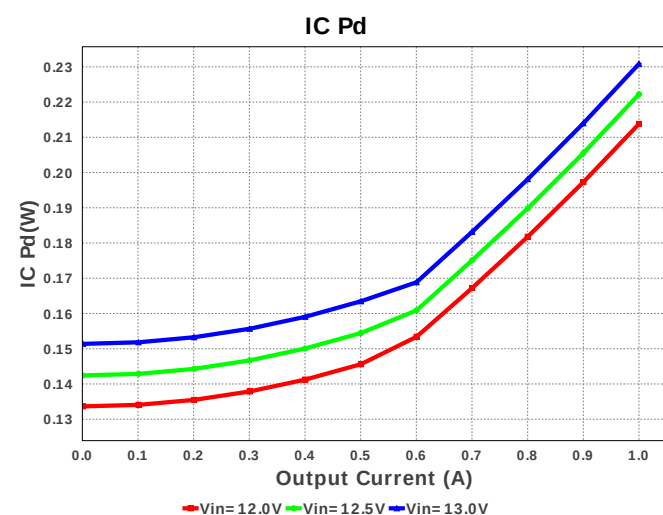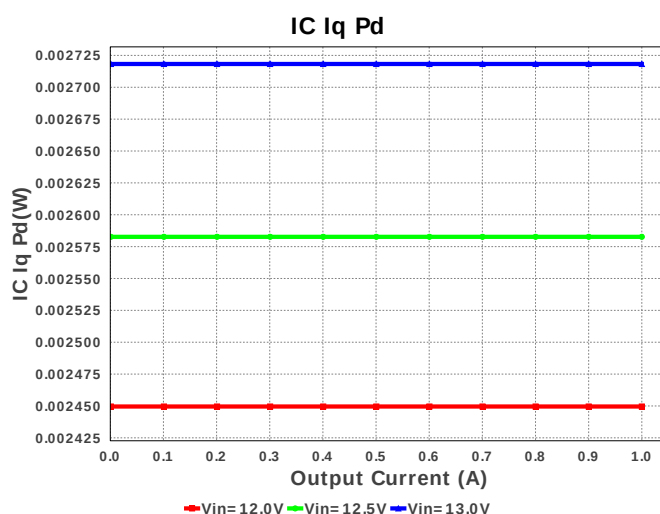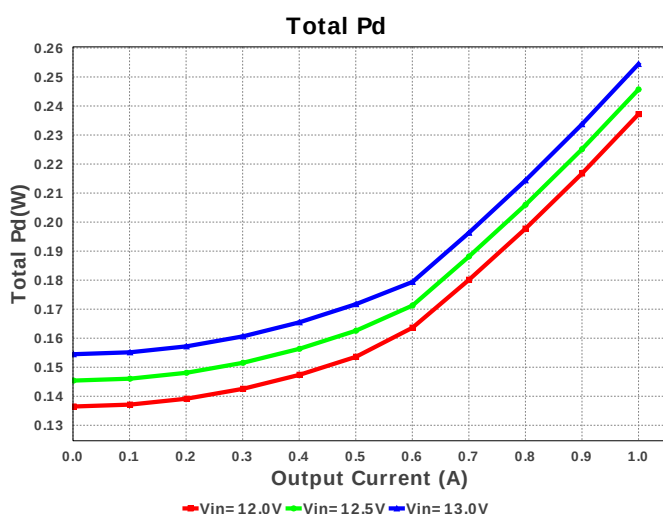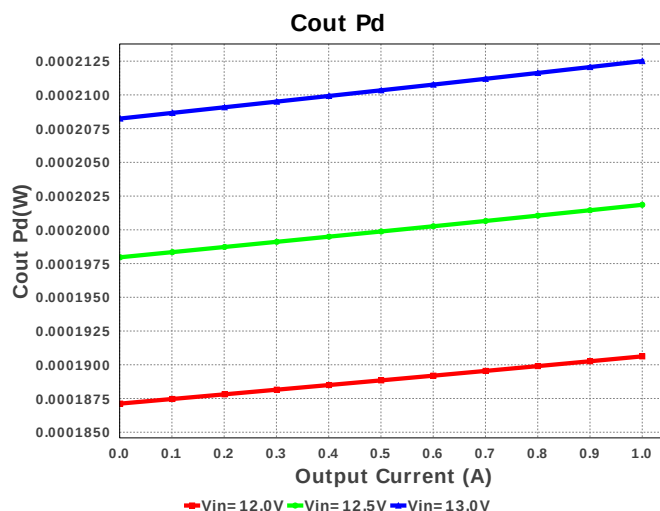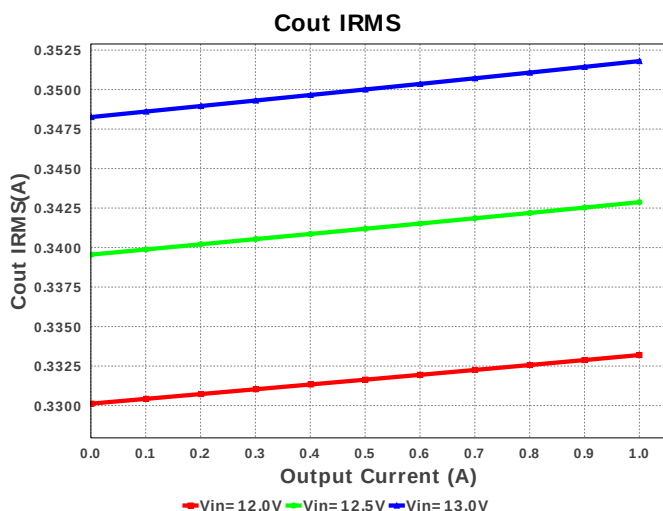

Operating Values

#	Name	Value	Category	Description
1.	Cin IRMS	534.952 mA	Current	Input capacitor RMS ripple current
2.	Cout IRMS	351.802 mA	Current	Output capacitor RMS ripple current
3.	Iin Avg	404.19 mA	Current	Average input current
4.	L Ipp	1.219 A	Current	Peak-to-peak inductor ripple current
5.	BOM Count	9	General	Total Design BOM count
6.	FootPrint	131.0 mm ²	General	Total Foot Print Area of BOM components
7.	Frequency	769.091 kHz	General	Switching frequency
8.	Pout	5.0 W	General	Total output power
9.	Total BOM	\$1.61	General	Total BOM Cost
10.	Vout Actual	5.031 V	Op_Point	Vout Actual calculated based on selected voltage divider resistors
11.	Vout OP	5.0 V	Op_Point	Operational Output Voltage

#	Name	Value	Category	Description
12.	Duty Cycle	39.002 %	Op_point	Duty cycle
13.	Efficiency	95.157 %	Op_point	Steady state efficiency
14.	IC Tj	42.465 degC	Op_point	IC junction temperature
15.	ICThetaJA	54.0 degC/W	Op_point	IC junction-to-ambient thermal resistance
16.	IOUT_OP	1.0 A	Op_point	Iout operating point
17.	VIN_OP	13.0 V	Op_point	Vin operating point
18.	Vout p-p	5.121 mV	Op_point	Peak-to-peak output ripple voltage
19.	Cin Pd	572.348 μ W	Power	Input capacitor power dissipation
20.	Cout Pd	212.504 μ W	Power	Output capacitor power dissipation
21.	IC Iq Pd	2.718 mW	Power	IC Iq Pd
22.	IC Pd	230.842 mW	Power	IC power dissipation
23.	L Pd	22.475 mW	Power	Inductor power dissipation
24.	Total Pd	254.474 mW	Power	Total Power Dissipation
25.	Vout Tolerance	3.053 %		Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable

Design Inputs

#	Name	Value	Description
1.	Iout	1.0	Maximum Output Current
2.	VinMax	13.0	Maximum input voltage
3.	VinMin	12.0	Minimum input voltage
4.	Vout	5.0	Output Voltage
5.	base_pn	TPS563219	Base Product Number
6.	source	DC	Input Source Type
7.	Ta	30.0	Ambient temperature

Design Assistance

1. **TPS563219** Product Folder : <http://www.ti.com/product/TPS563219> : contains the data sheet and other resources.

Texas Instruments' WEBENCH simulation tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Simulations are created using Texas Instruments' published specifications as well as the published specifications of other device manufacturers. While Texas Instruments does update this information periodically, this information may not be current at the time the simulation is built. Texas Instruments does not warrant the accuracy or completeness of the specifications or any information contained therein. Texas Instruments does not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. Texas Instruments does not warrant that the designs are production worthy.

You should completely validate and test your design implementation to confirm the system functionality for your application prior to production.

Use of Texas Instruments' WEBENCH simulation tools is subject to [Texas Instruments' Site Terms and Conditions of Use](#). Prototype boards based on WEBENCH created designs are provided AS IS without warranty of any kind for evaluation and testing purposes and are subject to the terms of the [Evaluation License Agreement](#).