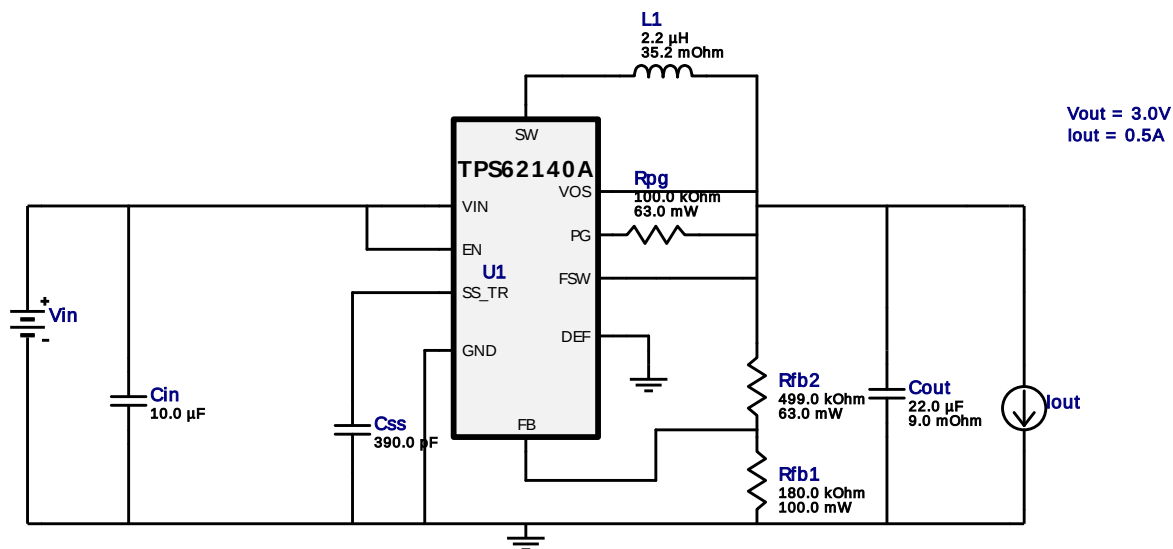








WEBENCH® Design Report







Design : 4742013/143 TPS62140ARGTR
TPS62140ARGTR 4.5V-5.5V to 3.00V @ 0.5A




Electrical BOM

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	Cin	Taiyo Yuden	LMK212BJ106KG-T Series= X5R	Cap= 10.0 uF VDC= 10.0 V IRMS= 0.0 A	1	\$0.03	0805 7 mm ²
2.	Cout	MuRata	GRM21BR60J226ME39L Series= X5R	Cap= 22.0 uF ESR= 9.0 mOhm VDC= 6.3 V IRMS= 3.5 A	1	\$0.04	0805 7 mm ²
3.	Css	MuRata	GRM033R71C391KA01D Series= X7R	Cap= 390.0 pF VDC= 16.0 V IRMS= 0.0 A	1	\$0.01	0201 2 mm ²
4.	L1	Coilcraft	XAL4020-222MEB	L= 2.2 µH DCR= 35.2 mOhm	1	\$0.60	XAL4020 28 mm ²
5.	Rfb1	Yageo America	RC0603FR-07180KL Series= ?	Res= 180.0 kOhm Power= 100.0 mW Tolerance= 1.0%	1	\$0.01	0603 5 mm ²
6.	Rfb2	Vishay-Dale	CRCW0402499KFKED Series= CRCW..e3	Res= 499.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²
7.	Rpg	Vishay-Dale	CRCW0402100KFKED Series= CRCW..e3	Res= 100.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²
8.	U1	Texas Instruments	TPS62140ARGTR	Switcher	1	\$0.88	S-PVQFN-N16 17 mm ²

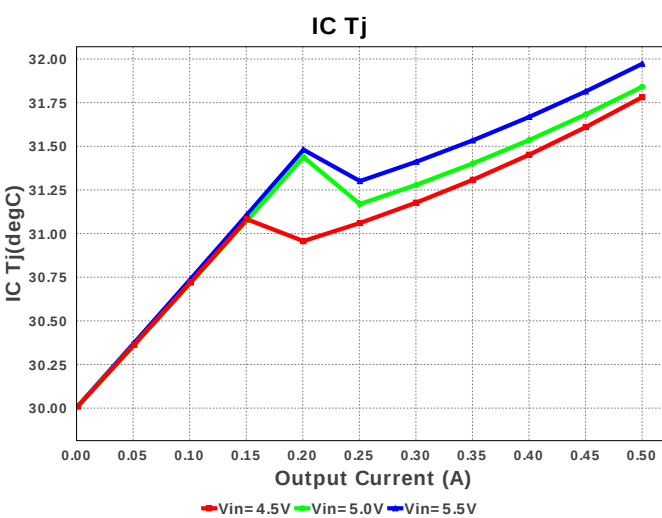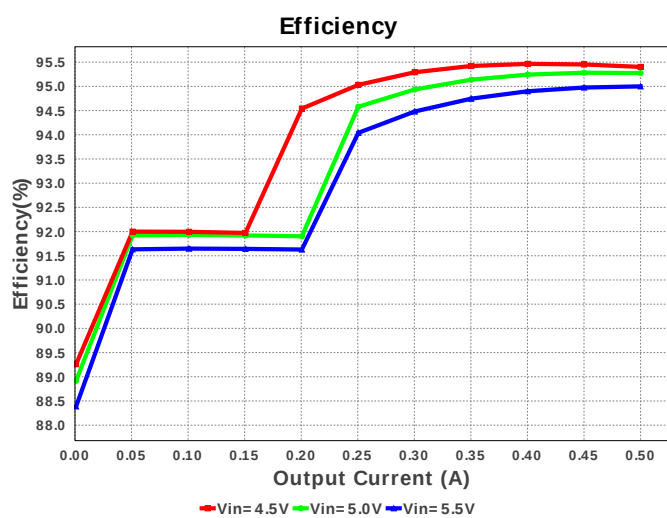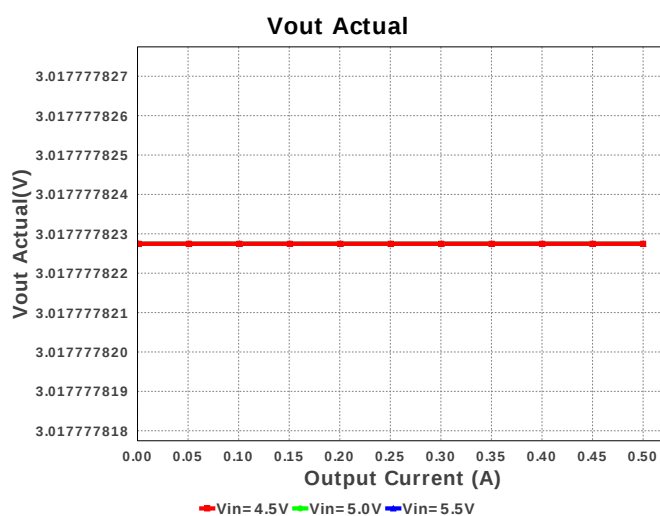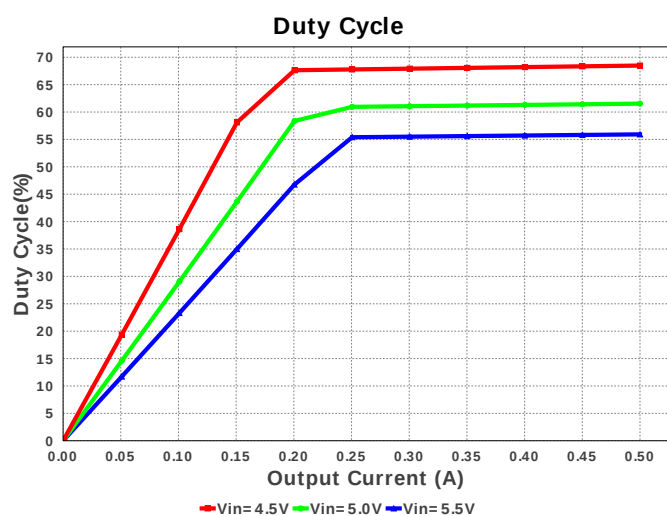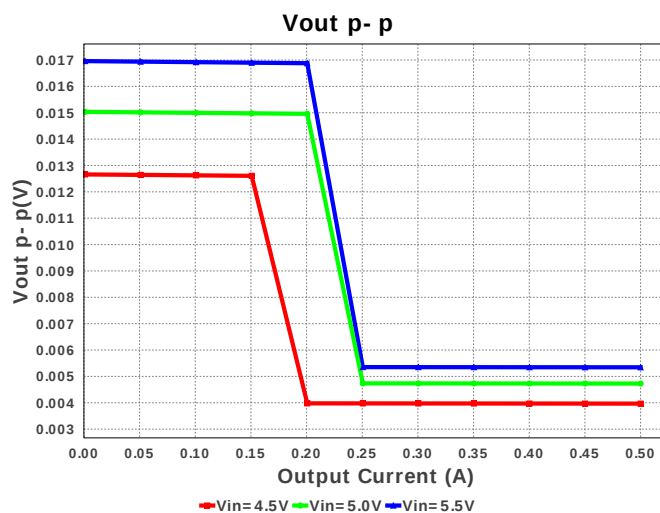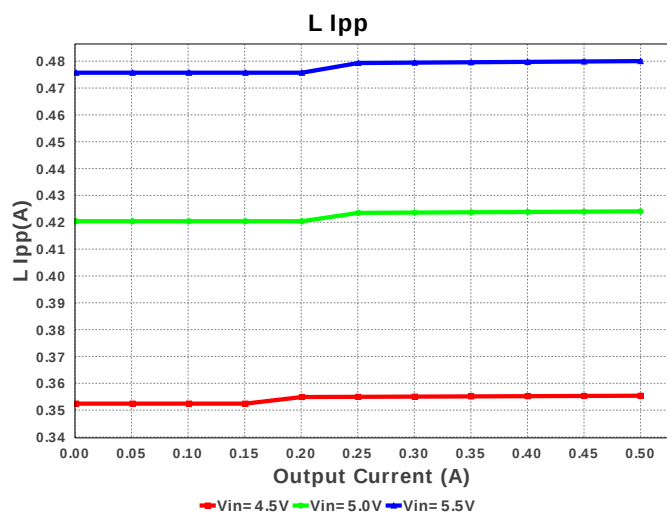

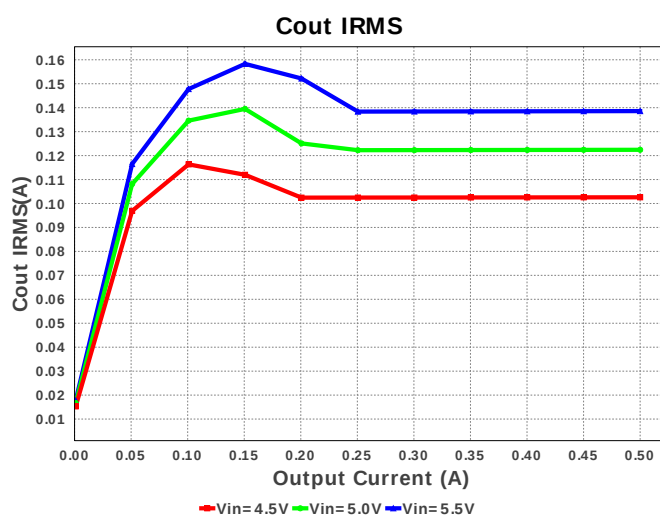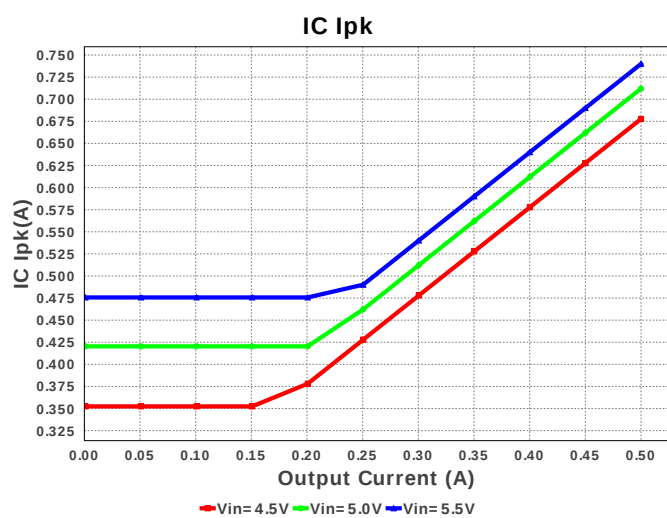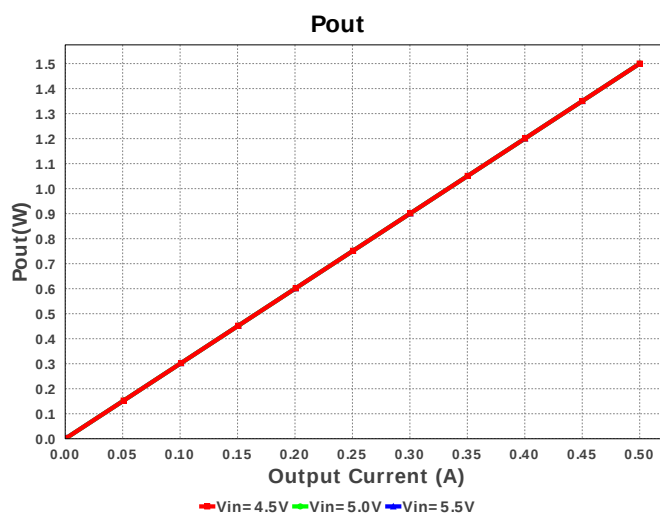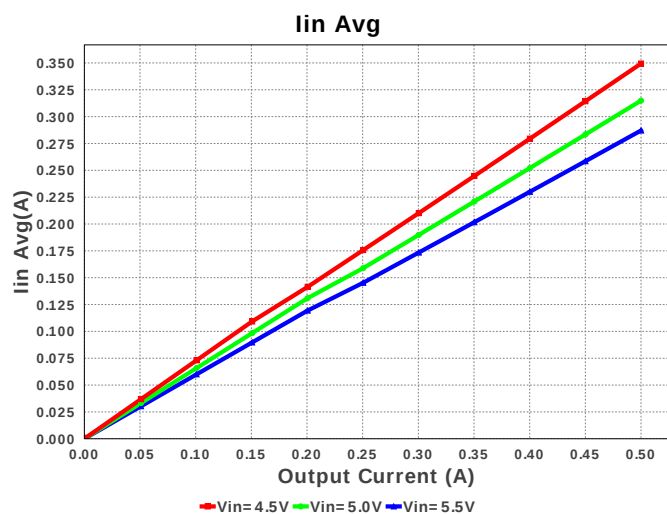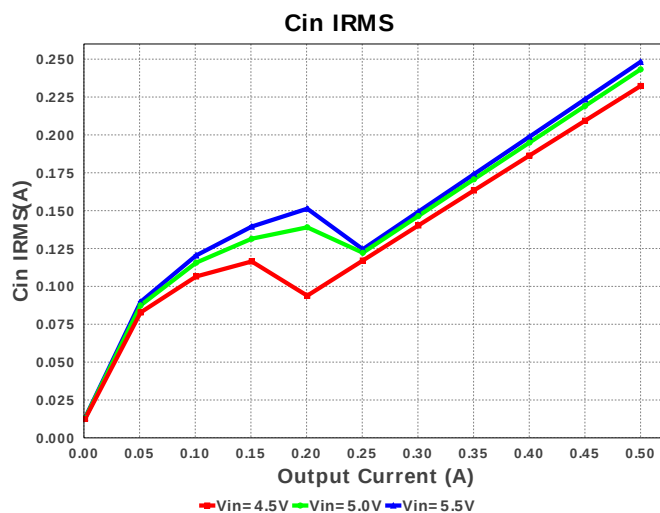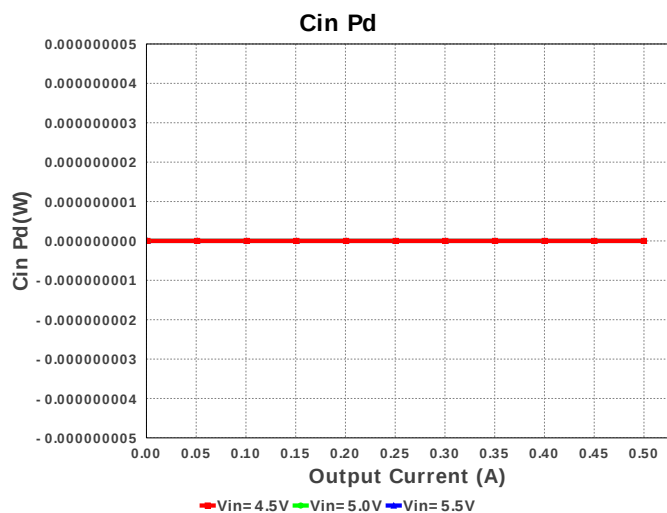

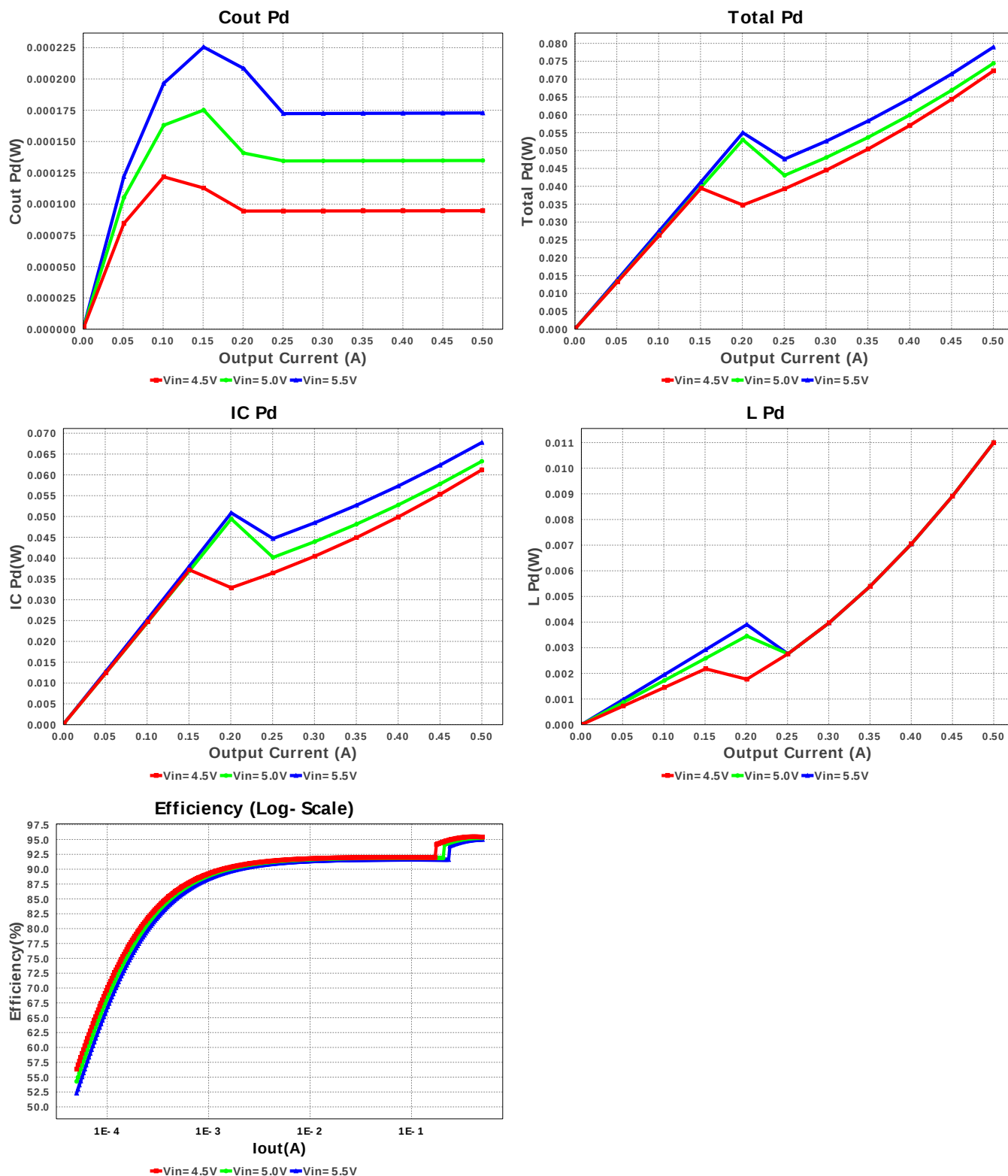

Operating Values

#	Name	Value	Category	Description
1.	Cin IRMS	248.239 mA	Current	Input capacitor RMS ripple current
2.	Cout IRMS	138.575 mA	Current	Output capacitor RMS ripple current
3.	IC IpK	740.018 mA	Current	Peak switch current in IC
4.	Iin Avg	287.08 mA	Current	Average input current
5.	L Ipp	480.04 mA	Current	Peak-to-peak inductor ripple current
6.	BOM Count	8	General	Total Design BOM count
7.	FootPrint	71.0 mm ²	General	Total Foot Print Area of BOM components
8.	Frequency	1.324 MHz	General	Switching frequency
9.	Pout	1.5 W	General	Total output power
10.	Total BOM	\$1.59	General	Total BOM Cost
11.	Vout Actual	3.018 V	Op_Point	Vout Actual calculated based on selected voltage divider resistors

#	Name	Value	Category	Description
12.	Vout OP	3.0 V	Op_Point	Operational Output Voltage
13.	Duty Cycle	55.923 %	Op_point	Duty cycle
14.	Efficiency	95.0 %	Op_point	Steady state efficiency
15.	IC Tj	31.972 degC	Op_point	IC junction temperature
16.	ICThetaJA	29.1 degC/W	Op_point	IC junction-to-ambient thermal resistance
17.	IOUT_OP	500.0 mA	Op_point	Iout operating point
18.	VIN_OP	5.5 V	Op_point	Vin operating point
19.	Vout p-p	5.345 mV	Op_point	Peak-to-peak output ripple voltage
20.	Cin Pd	0.0 W	Power	Input capacitor power dissipation
21.	Cout Pd	172.827 μ W	Power	Output capacitor power dissipation
22.	IC Pd	67.767 mW	Power	IC power dissipation
23.	L Pd	11.0 mW	Power	Inductor power dissipation
24.	Total Pd	78.947 mW	Power	Total Power Dissipation
25.	Vout Tolerance	3.311 %		Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable

Design Inputs

#	Name	Value	Description
1.	Iout	500.0 m	Maximum Output Current
2.	VinMax	5.5	Maximum input voltage
3.	VinMin	4.5	Minimum input voltage
4.	Vout	3.0	Output Voltage
5.	base_pn	TPS62140A	Base Product Number
6.	source	DC	Input Source Type
7.	Ta	30.0	Ambient temperature

Design Assistance

1. Feature Highlights: DCS-Control(TM) Architecture with upto 2A output current, 3V to 17V Input Voltage Range, Adjustable output voltage from 0.9V to 6V Selectable operating frequency, Optional Softstart Capacitor for slow startup, Tracking, Pin selectable output voltage (nominal, +5%) Seamless Power Save Mode for Light Load Efficiency, Power Good Output, 100% Duty Cycle mode, Short Circuit Protection, PG=Low when device is in shutdown through EN, UVLO or Thermal Shutdown

2. **TPS62140A** Product Folder : <http://www.ti.com/product/TPS62140A> : contains the data sheet and other resources.

Texas Instruments' WEBENCH simulation tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Simulations are created using Texas Instruments' published specifications as well as the published specifications of other device manufacturers. While Texas Instruments does update this information periodically, this information may not be current at the time the simulation is built. Texas Instruments does not warrant the accuracy or completeness of the specifications or any information contained therein. Texas Instruments does not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. Texas Instruments does not warrant that the designs are production worthy.

You should completely validate and test your design implementation to confirm the system functionality for your application prior to production.

Use of Texas Instruments' WEBENCH simulation tools is subject to [Texas Instruments' Site Terms and Conditions of Use](#). Prototype boards based on WEBENCH created designs are provided AS IS without warranty of any kind for evaluation and testing purposes and are subject to the terms of the [Evaluation License Agreement](#).