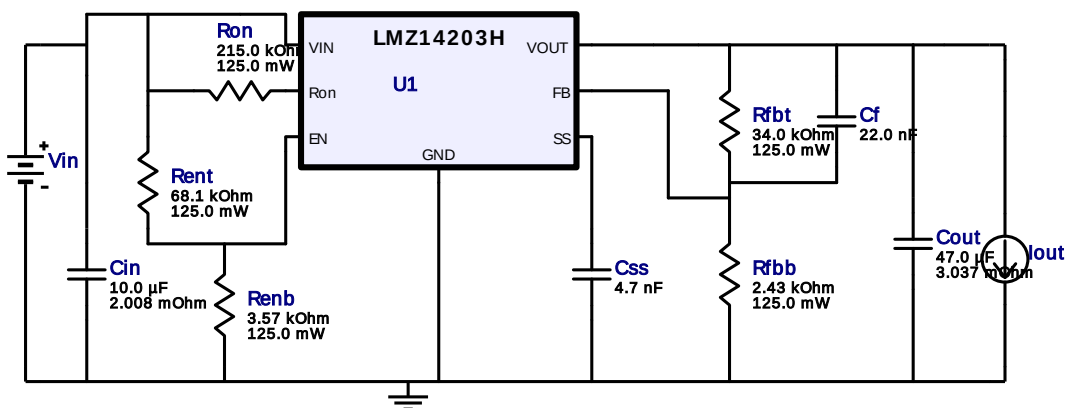


WEBENCH® Design Report


Design : 4077713/29 LMZ14203HTZ/NOPB
LMZ14203HTZ/NOPB 24.0V-26.0V to 12.00V @ 2.0A





Vout = 12.0V
Iout = 2.0A















Electrical BOM

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	Cf	Yageo America	CC0805KRX7R9BB223 Series= X7R	Cap= 22.0 nF VDC= 50.0 V IRMS= 0.0 A	1	\$0.01	0805 7 mm ²
2.	Cin	MuRata	GRM32ER7YA106KA12L Series= X7R	Cap= 10.0 uF ESR= 2.008 mOhm VDC= 35.0 V IRMS= 4.6772 A	1	\$0.22	1210_280 15 mm ²
3.	Cout	MuRata	GRM32ER61C476ME15L Series= X5R	Cap= 47.0 uF ESR= 3.037 mOhm VDC= 16.0 V IRMS= 4.59346 A	1	\$0.24	1210_280 15 mm ²
4.	Css	Yageo America	CC0805KRX7R9BB472 Series= X7R	Cap= 4.7 nF VDC= 50.0 V IRMS= 0.0 A	1	\$0.01	0805 7 mm ²
5.	Renb	Panasonic	ERJ-6ENF3571V Series= ERJ-6E	Res= 3.57 kOhm Power= 125.0 mW Tolerance= 1.0%	1	\$0.01	0805 7 mm ²
6.	Rent	Panasonic	ERJ-6ENF6812V Series= ERJ-6E	Res= 68.1 kOhm Power= 125.0 mW Tolerance= 1.0%	1	\$0.01	0805 7 mm ²
7.	Rfbb	Panasonic	ERJ-6ENF2431V Series= ERJ-6E	Res= 2.43 kOhm Power= 125.0 mW Tolerance= 1.0%	1	\$0.01	0805 7 mm ²
8.	Rfbt	Panasonic	ERJ-6ENF3402V Series= ERJ-6E	Res= 34.0 kOhm Power= 125.0 mW Tolerance= 1.0%	1	\$0.01	0805 7 mm ²
9.	Ron	Panasonic	ERJ-6ENF2153V Series= ERJ-6E	Res= 215.0 kOhm Power= 125.0 mW Tolerance= 1.0%	1	\$0.01	0805 7 mm ²
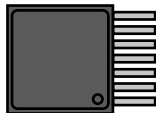
#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
10.	U1	Texas Instruments	LMZ14203HTZ/NOPB	Switcher	1	\$9.78	

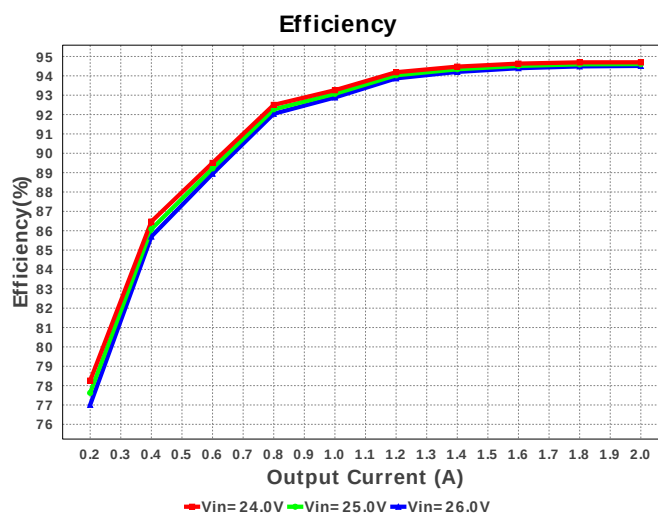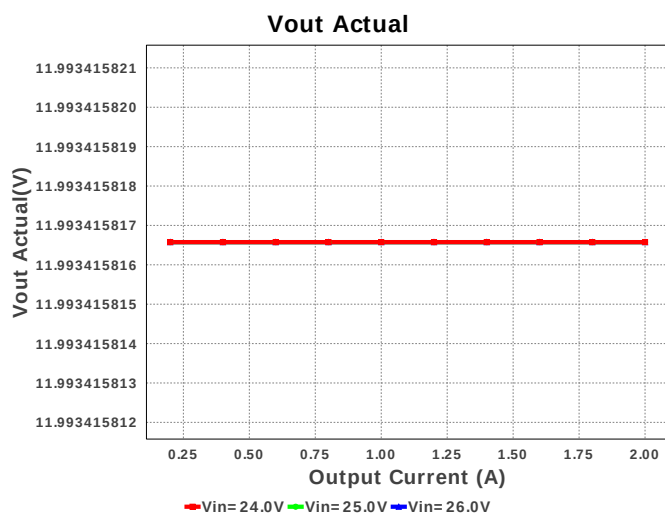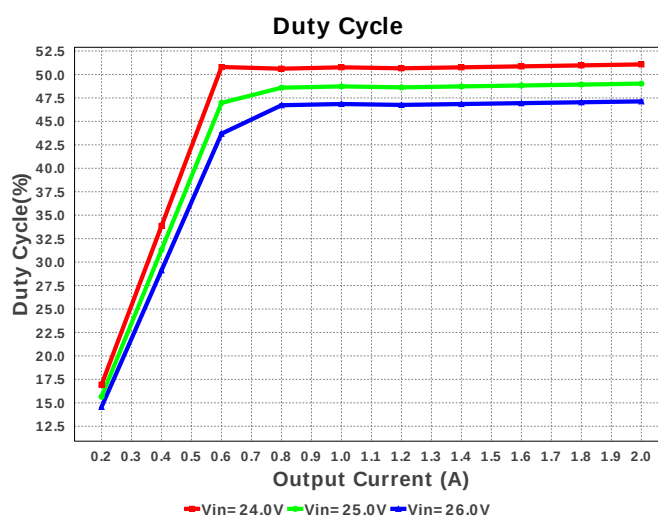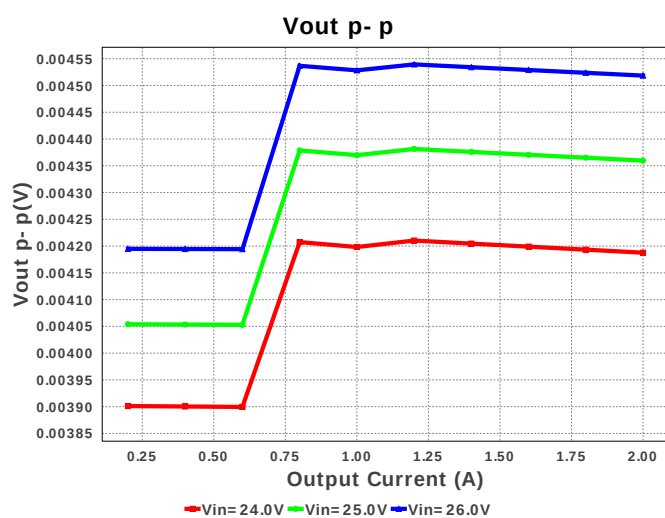TZA07A 199 mm²

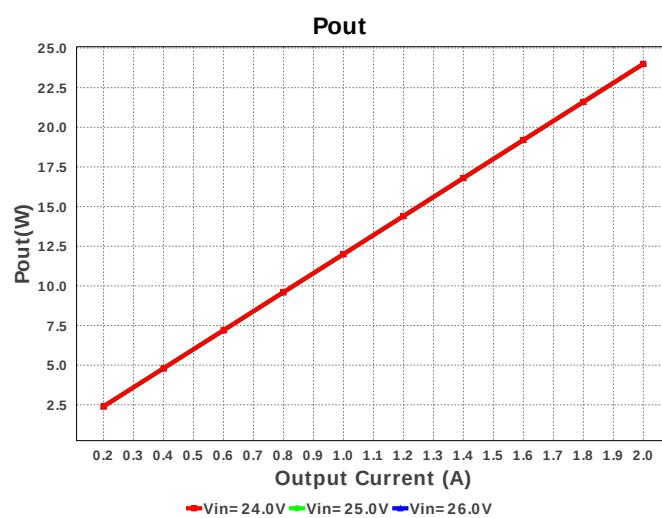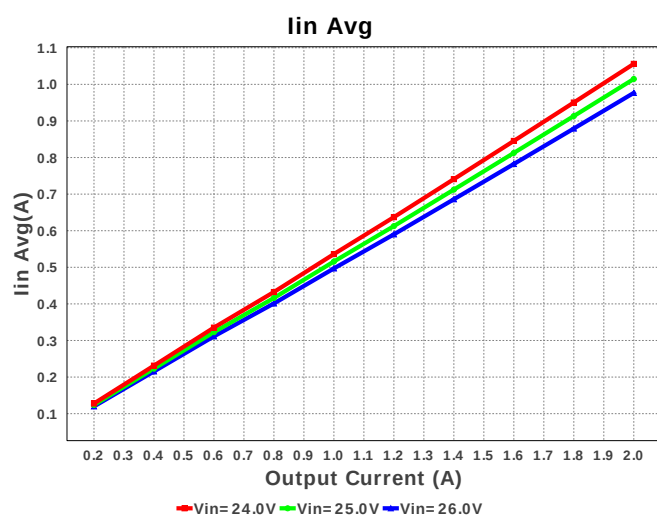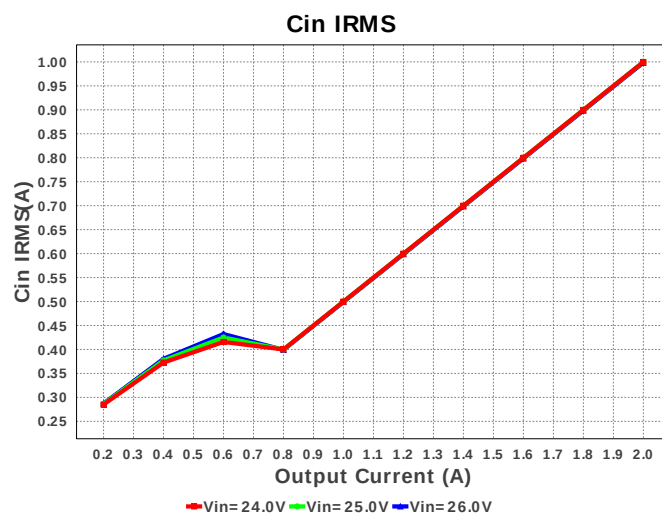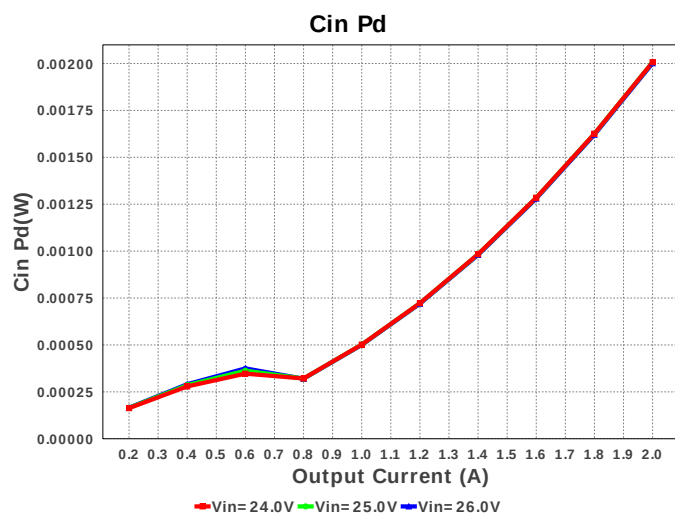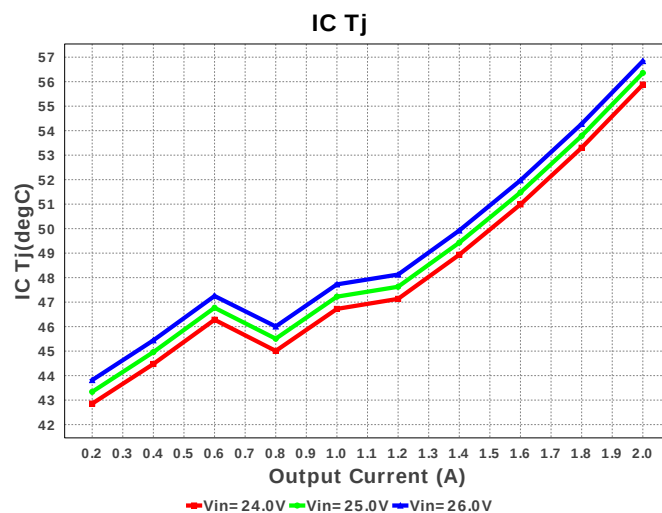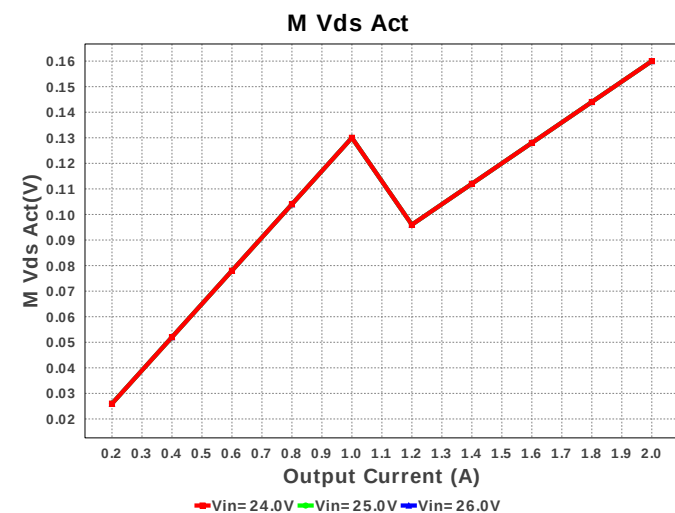

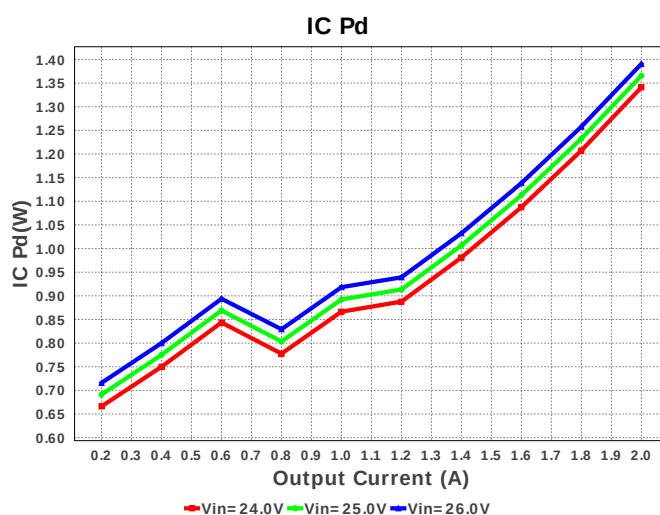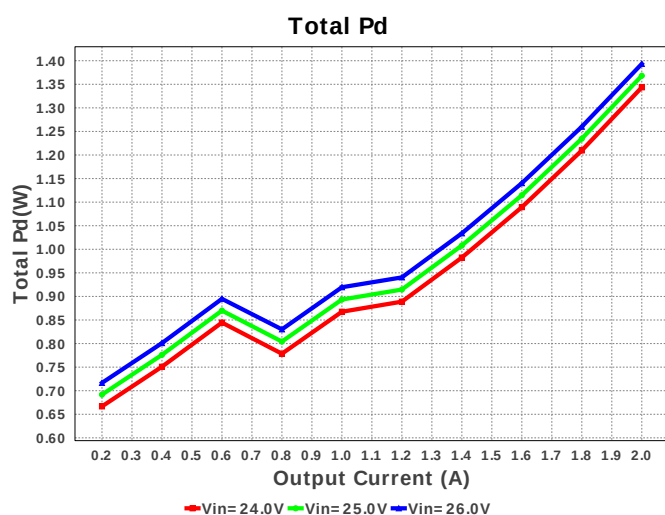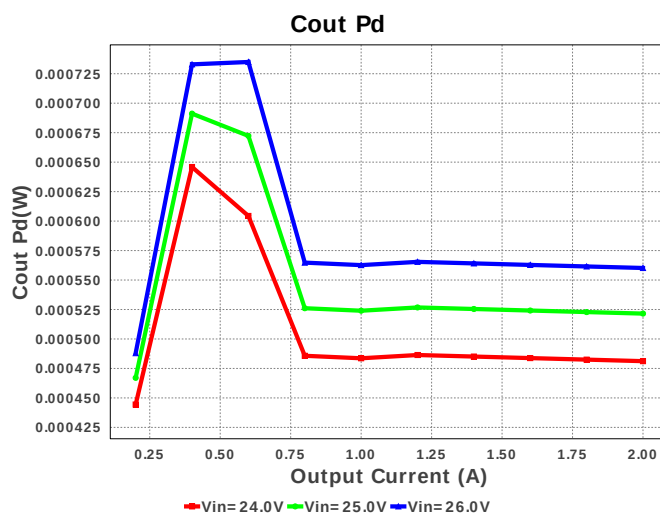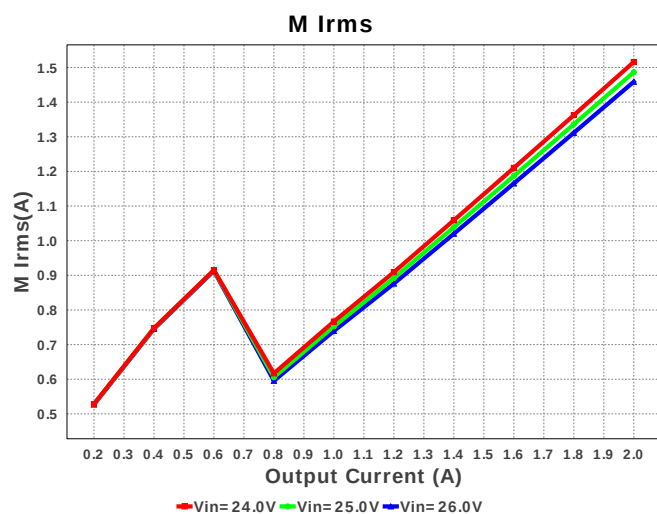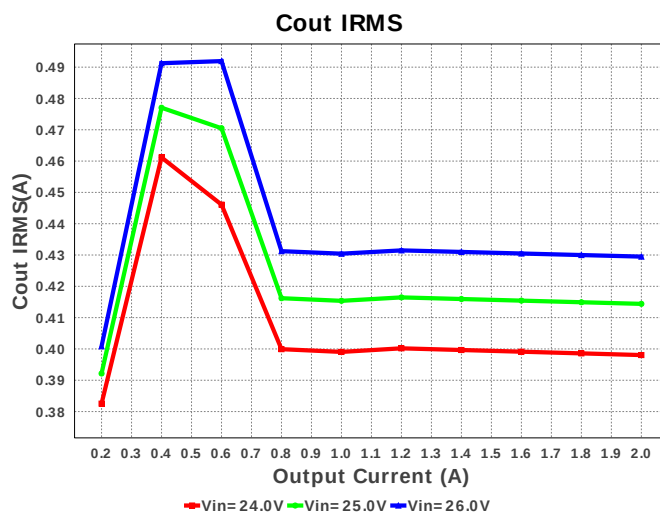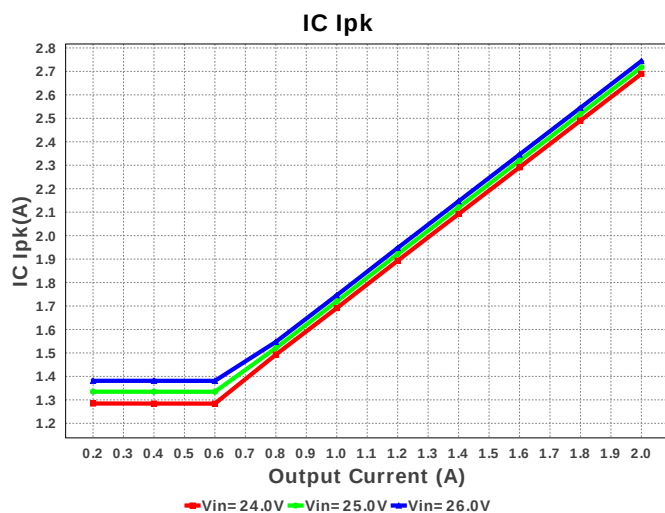

Operating Values

#	Name	Value	Category	Description
1.	Cin IRMS	998.352 mA	Current	Input capacitor RMS ripple current
2.	Cout IRMS	429.491 mA	Current	Output capacitor RMS ripple current
3.	IC Ip _k	2.744 A	Current	Peak switch current in IC
4.	Iin Avg	973.14 mA	Current	Average input current
5.	M1 Irms	1.454 A	Current	Q ₁ I _{avg}
6.	BOM Count	10	General	Total Design BOM count
7.	FootPrint	275.0 mm ²	General	Total Foot Print Area of BOM components
8.	Frequency	429.338 kHz	General	Switching frequency
9.	IC Tolerance	20.0 mV	General	IC Feedback Tolerance
10.	M V _{ds} Act	160.0 mV	General	Voltage drop across the MosFET
11.	Pout	24.0 W	General	Total output power

#	Name	Value	Category	Description
12.	Total BOM	\$10.31	General	Total BOM Cost
13.	Vout Actual	11.993 V	Op_Point	Vout Actual calculated based on selected voltage divider resistors
14.	Vout OP	12.0 V	Op_Point	Operational Output Voltage
15.	Duty Cycle	47.131 %	Op_point	Duty cycle
16.	Efficiency	94.856 %	Op_point	Steady state efficiency
17.	IC Tj	55.072 degC	Op_point	IC junction temperature
18.	ICThetaJA	19.3 degC/W	Op_point	IC junction-to-ambient thermal resistance
19.	IOUT_OP	2.0 A	Op_point	Iout operating point
20.	VIN_OP	26.0 V	Op_point	Vin operating point
21.	Vout p-p	4.518 mV	Op_point	Peak-to-peak output ripple voltage
22.	Cin Pd	2.001 mW	Power	Input capacitor power dissipation
23.	Cout Pd	560.212 μ W	Power	Output capacitor power dissipation
24.	IC Pd	1.299 W	Power	IC power dissipation
25.	Total Pd	1.302 W	Power	Total Power Dissipation
26.	Vout Tolerance	4.433 %		Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable

Design Inputs

#	Name	Value	Description
1.	Iout	2.0	Maximum Output Current
2.	VinMax	26.0	Maximum input voltage
3.	VinMin	24.0	Minimum input voltage
4.	Vout	12.0	Output Voltage
5.	base_pn	LMZ14203H	Base Product Number
6.	source	DC	Input Source Type
7.	Ta	30.0	Ambient temperature

Design Assistance

1. **LMZ14203H** Product Folder : <http://www.ti.com/product/LMZ14203H> : contains the data sheet and other resources.

Texas Instruments' WEBENCH simulation tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Simulations are created using Texas Instruments' published specifications as well as the published specifications of other device manufacturers. While Texas Instruments does update this information periodically, this information may not be current at the time the simulation is built. Texas Instruments does not warrant the accuracy or completeness of the specifications or any information contained therein. Texas Instruments does not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. Texas Instruments does not warrant that the designs are production worthy.

You should completely validate and test your design implementation to confirm the system functionality for your application prior to production.

Use of Texas Instruments' WEBENCH simulation tools is subject to [Texas Instruments' Site Terms and Conditions of Use](#). Prototype boards based on WEBENCH created designs are provided AS IS without warranty of any kind for evaluation and testing purposes and are subject to the terms of the [Evaluation License Agreement](#).