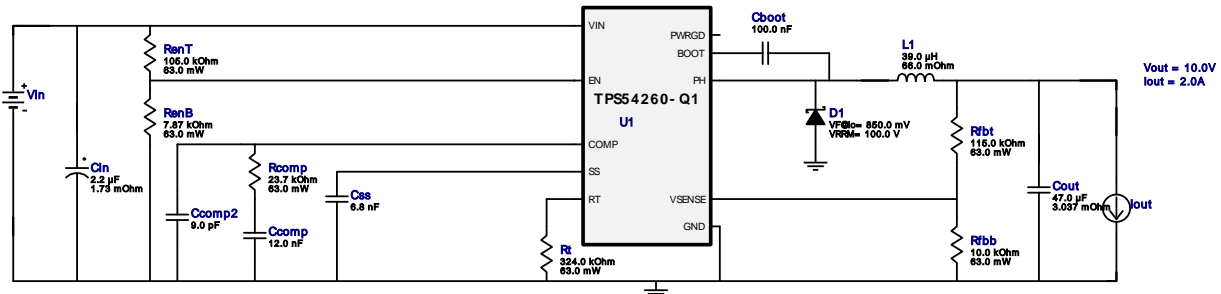


WEBENCH® Design Report

Design : 4352199/67 TPS54260QDGQRQ1
TPS54260QDGQRQ1 20.0V-40.0V to 10.00V @ 2.0A













1. This regulator device is qualified for Automotive applications. All passives and other components selected in this design may not be qualified for Automotive applications. The user is required to verify that all components in the design meet the qualification and safety requirements for their specific application. View WEBENCH(R) Disclaimer.







Electrical BOM




#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	Cboot	MuRata	GRM155R61A104KA01D Series= X5R	Cap= 100.0 nF VDC= 10.0 V IRMS= 0.0 A	1	\$0.01	 0402 3 mm ²
2.	Ccomp	MuRata	GRM033C80J123KE01D Series= X6S	Cap= 12.0 nF VDC= 6.3 V IRMS= 0.0 A	1	\$0.01	 0201 2 mm ²
3.	Ccomp2	MuRata	GQM2195C2A9R0CB01D Series= C0G/NP0	Cap= 9.0 pF VDC= 100.0 V IRMS= 0.0 A	1	\$0.17	 0805 7 mm ²
4.	Cin	TDK	C3225X7R2A225K230AB Series= X7R	Cap= 2.2 uF ESR= 1.73 mOhm VDC= 100.0 V IRMS= 5.5932 A	1	\$0.19	 1210_250 15 mm ²
5.	Cout	MuRata	GRM32ER61C476ME15L Series= X5R	Cap= 47.0 uF ESR= 3.037 mOhm VDC= 16.0 V IRMS= 4.59346 A	1	\$0.24	 1210_280 15 mm ²
6.	Css	Yageo America	CC0805KRX7R9BB682 Series= X7R	Cap= 6.8 nF VDC= 50.0 V IRMS= 0.0 A	1	\$0.01	 0805 7 mm ²
7.	D1	Micro Commercial Components	SK310A-TP	VF@Io= 850.0 mV VRRM= 100.0 V	1	\$0.10	 SMA 37 mm ²
8.	L1	Bourns	SRR1210-390M	L= 39.0 uH DCR= 66.0 mOhm	1	\$0.44	 SRR1210 196 mm ²
9.	Rcomp	Vishay-Dale	CRCW040223K7FKED Series= CRCW..e3	Res= 23.7 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
10.	RenB	Vishay-Dale	CRCW04027K87FKED Series= CRCW..e3	Res= 7.87 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
11.	RenT	Vishay-Dale	CRCW0402105KFKED Series= CRCW..e3	Res= 105.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm²
12.	Rfbb	Vishay-Dale	CRCW040210K0FKED Series= CRCW..e3	Res= 10.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm²
13.	Rfbt	Vishay-Dale	CRCW0402115KFKED Series= CRCW..e3	Res= 115.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm²
14.	Rt	Vishay-Dale	CRCW0402324KFKED Series= CRCW..e3	Res= 324.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm²
15.	U1	Texas Instruments	TPS54260QDGQRQ1	Switcher	1	\$2.12	 S-PDSO-G10 24 mm²

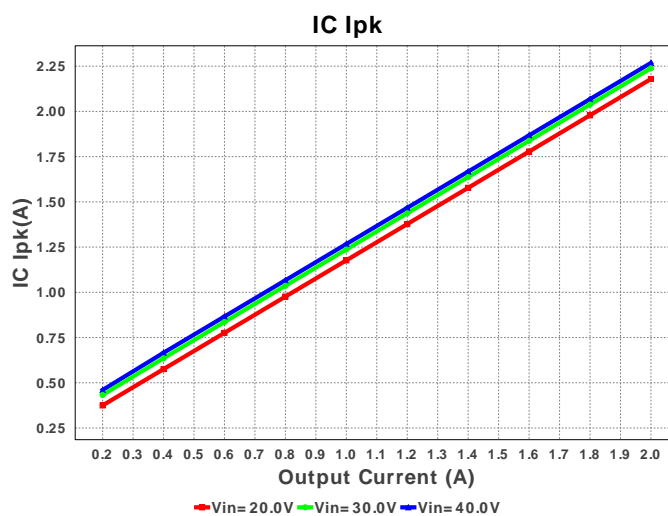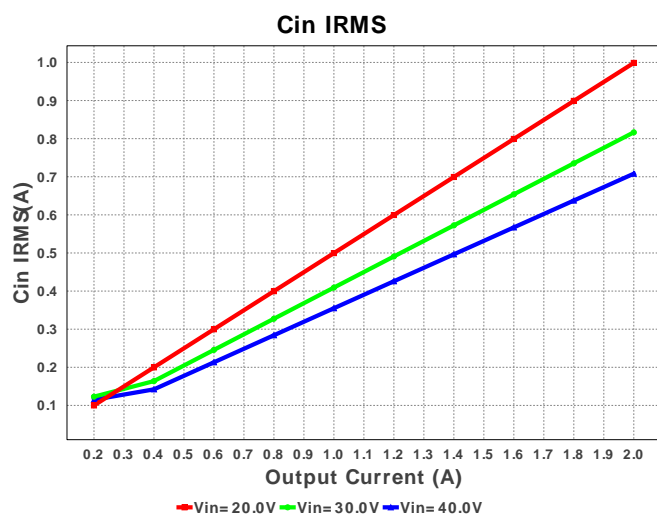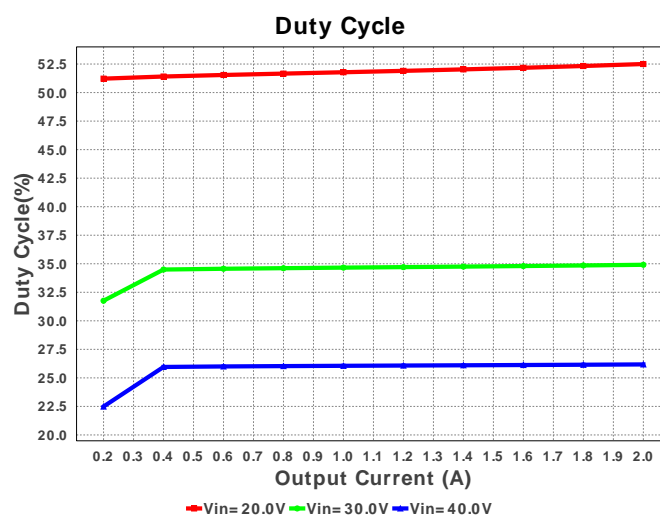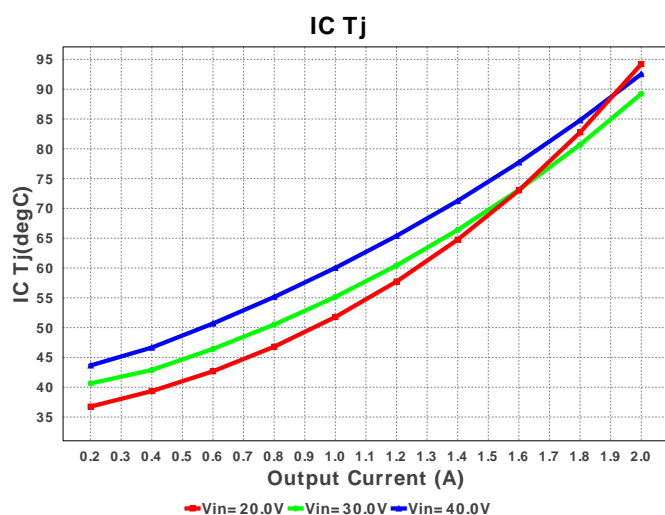

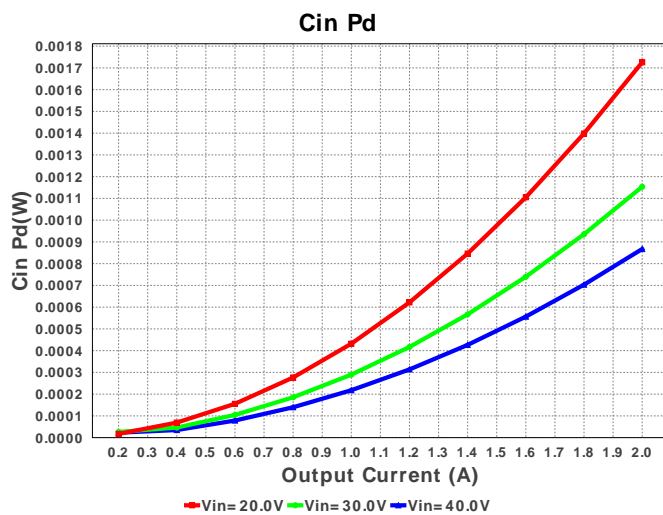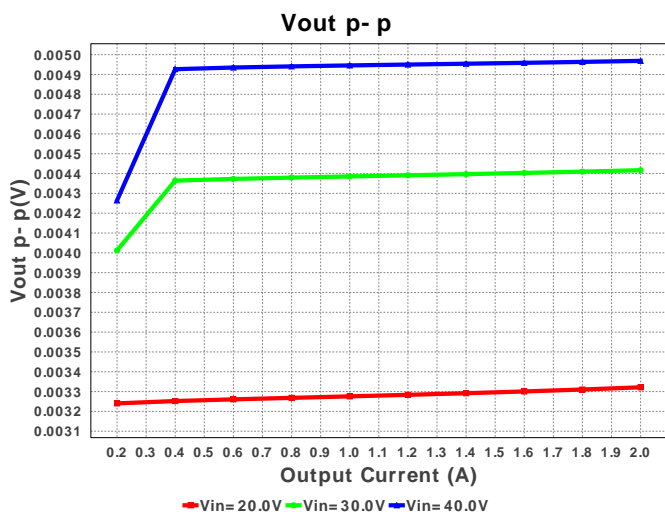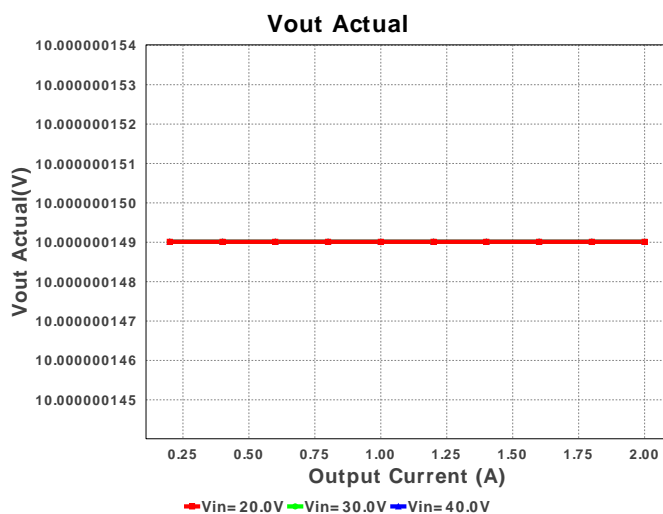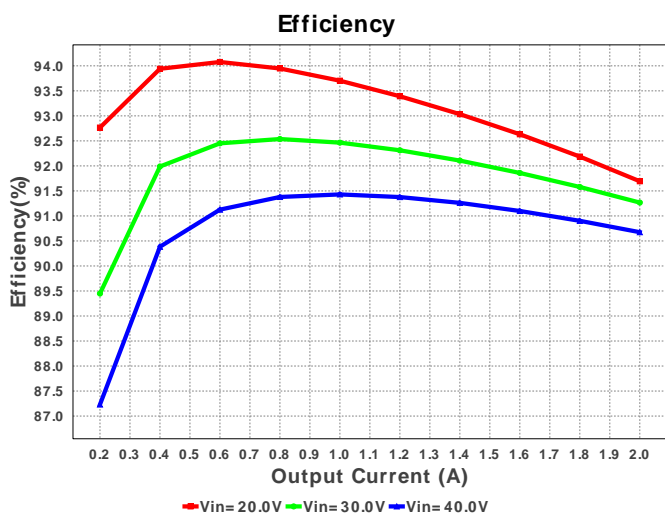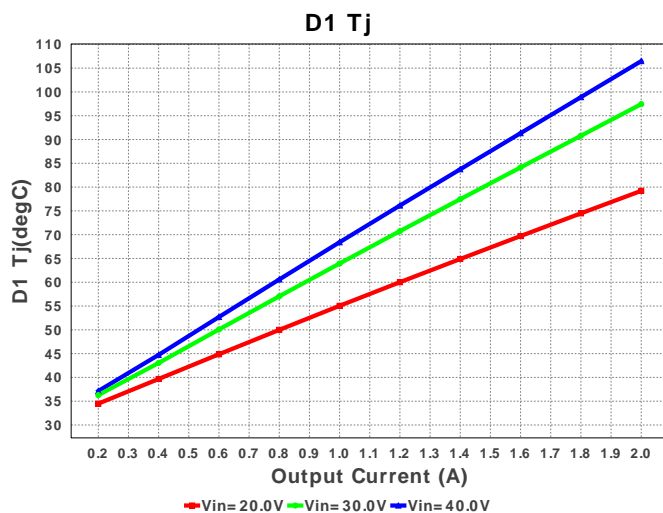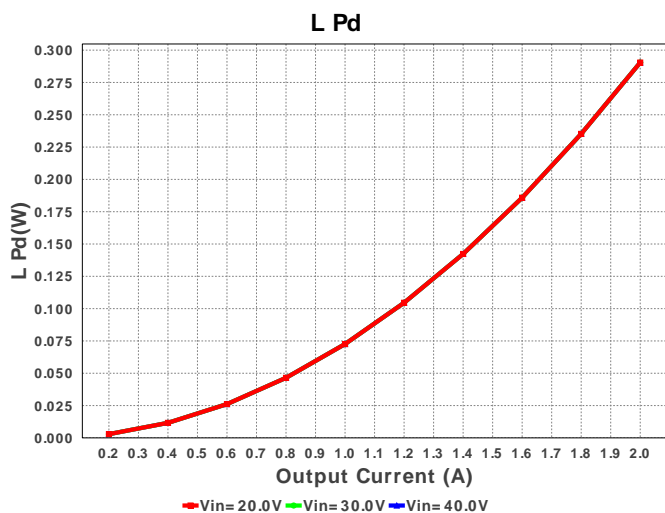

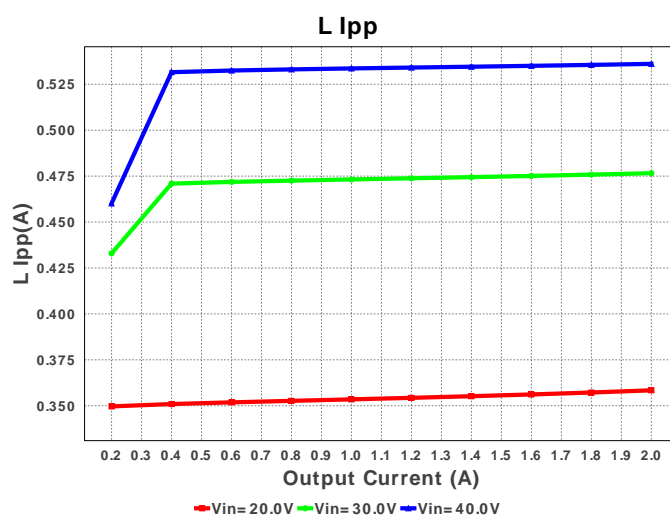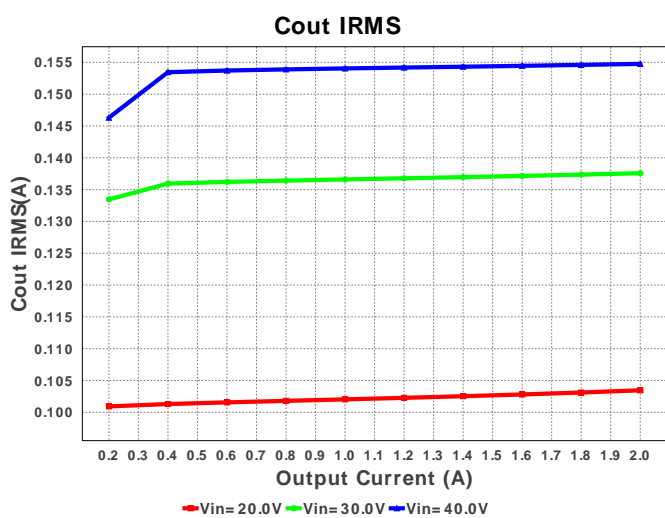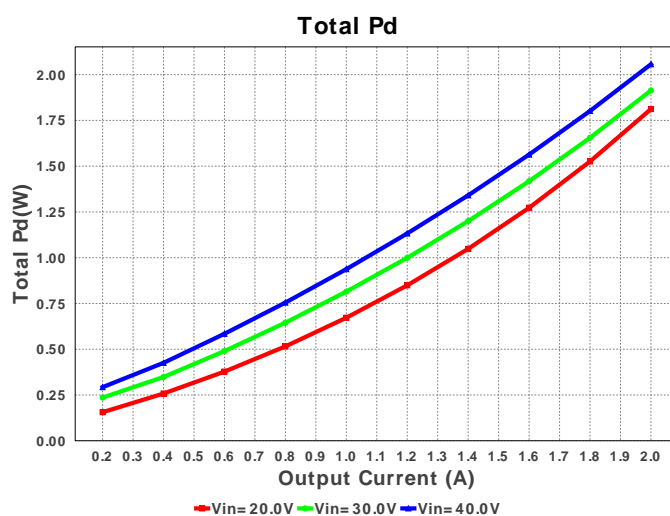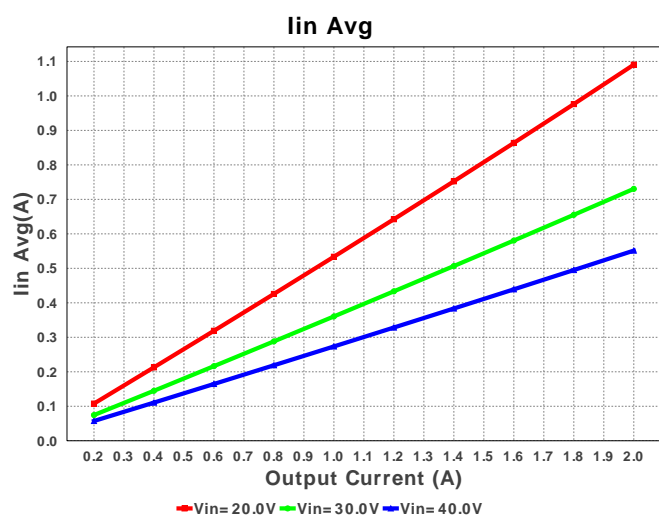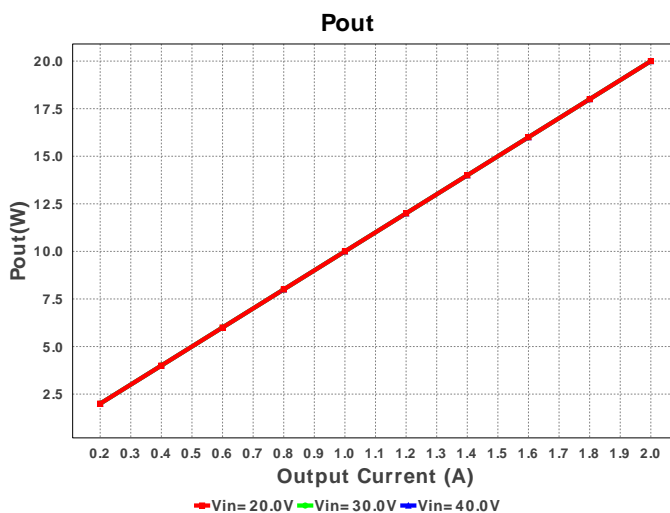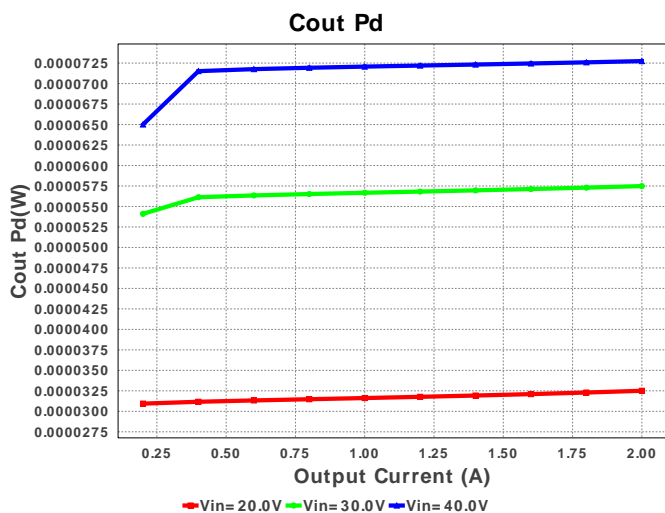

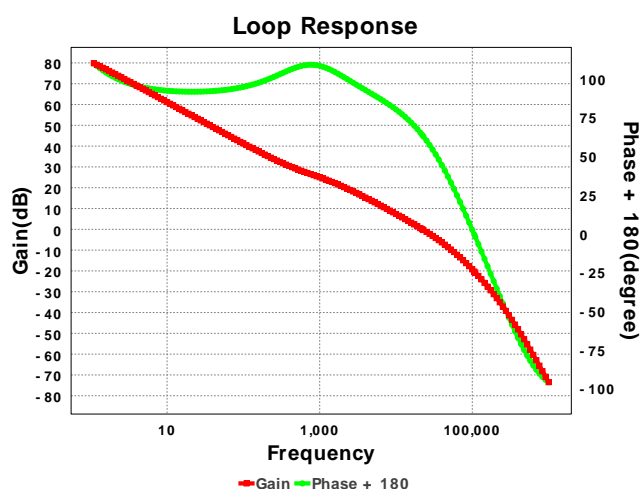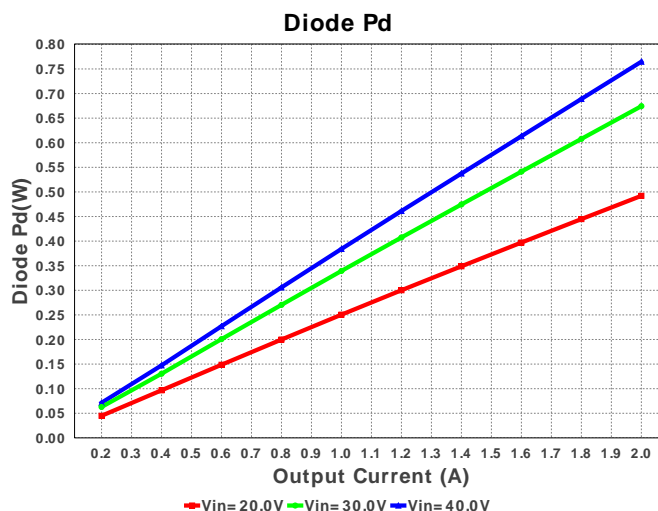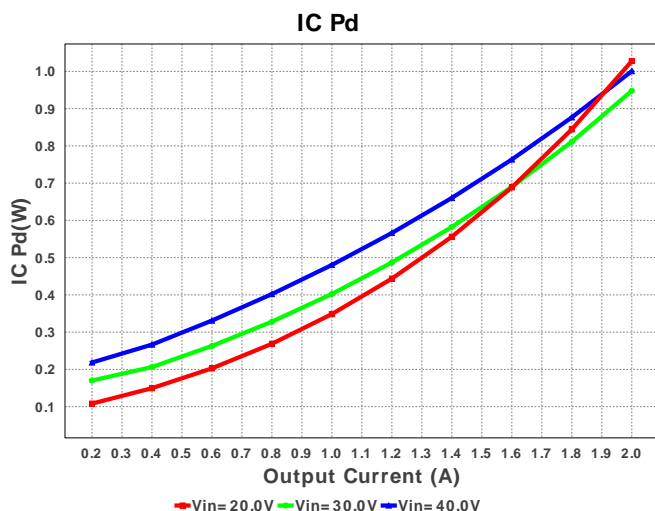

Operating Values

#	Name	Value	Category	Description
1.	Cin IRMS	710.284 mA	Current	Input capacitor RMS ripple current
2.	Cout IRMS	158.358 mA	Current	Output capacitor RMS ripple current
3.	IC Ipk	2.0 A	Current	Peak switch current in IC
4.	Iin Avg	563.63 mA	Current	Average input current
5.	L Ipp	548.57 mA	Current	Peak-to-peak inductor ripple current
6.	BOM Count	15	General	Total Design BOM count
7.	FootPrint	323.0 mm ²	General	Total Foot Print Area of BOM components
8.	Frequency	375.624 kHz	General	Switching frequency
9.	Pout	20.0 W	General	Total output power
10.	Total BOM	\$3.35	General	Total BOM Cost
11.	D1 Tj	154.462 degC	Op_Point	D1 junction temperature
12.	Low Freq Gain	79.744 dB	Op_Point	Gain at 10Hz
13.	Vout Actual	10.0 V	Op_Point	Vout Actual calculated based on selected voltage divider resistors
14.	Vout OP	10.0 V	Op_Point	Operational Output Voltage
15.	Cross Freq	22.1 kHz	Op_point	Bode plot crossover frequency
16.	Duty Cycle	26.787 %	Op_point	Duty cycle
17.	Efficiency	88.71 %	Op_point	Steady state efficiency
18.	Gain Marg	-20.334 dB	Op_point	Bode Plot Gain Margin
19.	IC Tj	93.089 degC	Op_point	IC junction temperature
20.	ICThetaJA	62.5 degC/W	Op_point	IC junction-to-ambient thermal resistance
21.	IOUT_OP	2.0 A	Op_point	Iout operating point
22.	Phase Marg	63.811 deg	Op_point	Bode Plot Phase Margin
23.	VIN_OP	40.0 V	Op_point	Vin operating point
24.	Vout p-p	5.084 mV	Op_point	Peak-to-peak output ripple voltage
25.	Cin Pd	872.792 μW	Power	Input capacitor power dissipation
26.	Cout Pd	76.16 μW	Power	Output capacitor power dissipation
27.	Diode Pd	1.245 W	Power	Diode power dissipation
28.	IC Pd	1.009 W	Power	IC power dissipation
29.	L Pd	290.4 mW	Power	Inductor power dissipation
30.	Total Pd	2.545 W	Power	Total Power Dissipation

#	Name	Value	Category	Description
31.	Vout Tolerance	2.877 %		Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable

Design Inputs

#	Name	Value	Description
1.	Iout	2.0	Maximum Output Current
2.	VinMax	40.0	Maximum input voltage
3.	VinMin	20.0	Minimum input voltage
4.	Vout	10.0	Output Voltage
5.	base_pn	TPS54260-Q1	Texas Instruments Base Part Number
6.	source	DC	Input Source Type
7.	ta	30.0	Ambient temperature

Design Assistance

1. The TPS54260-Q1 is qualified for Automotive applications. All passives and other components selected in this design may not be qualified for Automotive applications. The user is required to verify that all components in the design meet the qualification and safety requirements for their specific application

2. TPS54260-Q1 Product Folder : <http://www.ti.com/product/TPS54260%2DQ1> : contains the data sheet and other resources.

Texas Instruments' WEBENCH simulation tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Simulations are created using Texas Instruments' published specifications as well as the published specifications of other device manufacturers. While Texas Instruments does update this information periodically, this information may not be current at the time the simulation is built. Texas Instruments does not warrant the accuracy or completeness of the specifications or any information contained therein. Texas Instruments does not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. Texas Instruments does not warrant that the designs are production worthy.

You should completely validate and test your design implementation to confirm the system functionality for your application prior to production.

Use of Texas Instruments' WEBENCH simulation tools is subject to [Texas Instruments' Site Terms and Conditions of Use](#). Prototype boards based on WEBENCH created designs are provided AS IS without warranty of any kind for evaluation and testing purposes and are subject to the terms of the [Evaluation License Agreement](#).