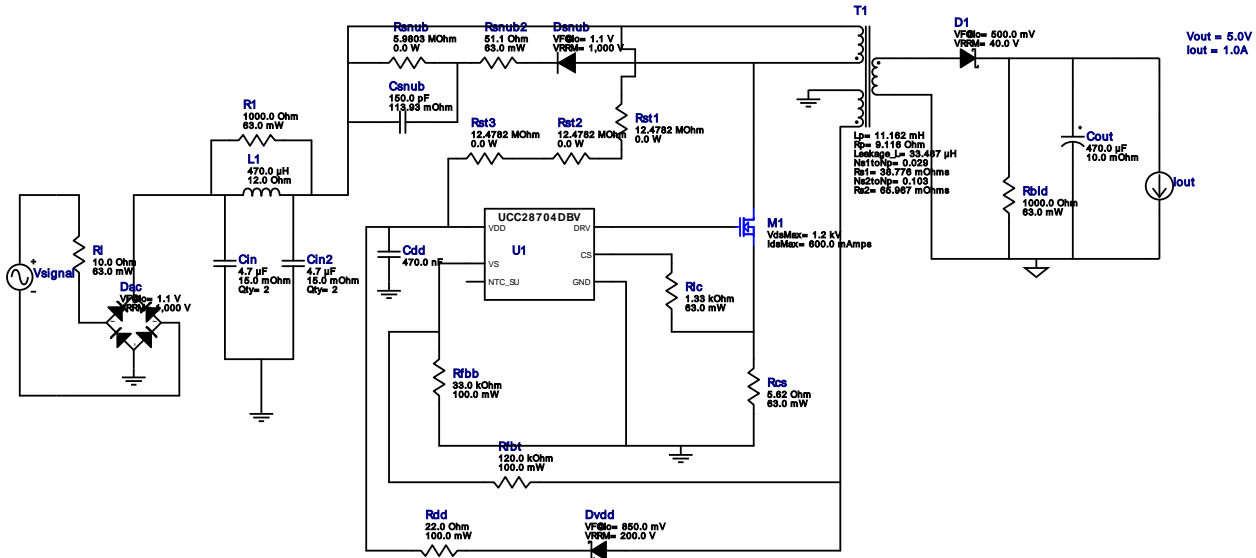


WEBENCH® Design Report














 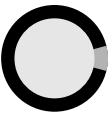

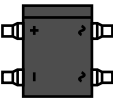Design : 4352199/81 UCC28704DBVR-1
UCC28704DBVR-1 220.0V-330.0V to 5.66V @ 1.0A





1. Rbld is a starting point, but may need to be experimented with in order to get minimum current needed to hold Vout at no load. Rlc and the feedback resistors may also need adjustment based on the actual transformer used. For more information please click the design assistance button.







Electrical BOM







#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	Cdd	Taiyo Yuden	TMK212BJ474KD-T Series= X5R	Cap= 470.0 nF VDC= 20.0 V IRMS= 0.0 A	1	\$0.02	0805 7 mm ²
2.	Cin	TDK	B32924C3475M Series= B32924	Cap= 4.7 uF ESR= 15.0 mOhm VDC= 630.0 V IRMS= 457.0 mA	2	\$1.11	B32924_33mm 670 mm ²







#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
3.	Cin2	TDK	B32924C3475M Series= B32924	Cap= 4.7 uF ESR= 15.0 mOhm VDC= 630.0 V IRMS= 457.0 mA	2	\$1.11	 B32924_33mm 670 mm²
4.	Cout	Nichicon	RNU1C471MDN1PH Series= ?	Cap= 470.0 uF ESR= 10.0 mOhm VDC= 16.0 V IRMS= 6.1 A	1	\$0.52	 NU_1000x1250 144 mm²
5.	Csnub	TDK	C3216CH2J151J Series= CH	Cap= 150.0 pF ESR= 113.93 mOhm VDC= 630.0 V IRMS= 0.0 A	1	\$0.03	 1206 11 mm²
6.	D1	Diodes Inc.	B340A-13-F	VF@Io= 500.0 mV VRRM= 40.0 V	1	\$0.11	 SMA 37 mm²
7.	Dac	Vishay-Semiconductor	DF10SA	VF@Io= 1.1 V VRRM= 1,000.0 V	1	\$0.24	 DF-S 99 mm²
8.	Dsnub	Fairchild Semiconductor	1N4007	VF@Io= 1.1 V VRRM= 1,000.0 V	1	\$0.03	 DO-41 43 mm²
9.	Dvdd	Diodes Inc.	DFLS1200-7	VF@Io= 850.0 mV VRRM= 200.0 V	1	\$0.21	 PowerDI123 13 mm²
10.	L1	NIC Components	NPI32C471MTRF	L= 470.0 uH DCR= 12.0 Ohm	1	\$0.08	 IND_NPI32C 21 mm²
11.	M1	IXYS	IXTA06N120P	VdsMax= 1.2 kV IdsMax= 600.0 mAmps	1	\$1.43	 DDPAK 210 mm²
12.	R1	Vishay-Dale	CRCW04021K00FKED Series= CRCW..e3	Res= 1000.0 Ohm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm²
13.	Rbld	Vishay-Dale	CRCW04021K00FKED Series= CRCW..e3	Res= 1000.0 Ohm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm²
14.	Rcs	Vishay-Dale	CRCW04025R62FKED Series= CRCW..e3	Res= 5.62 Ohm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm²
15.	Rdd	Yageo America	RC0603FR-0722RL Series= ?	Res= 22.0 Ohm Power= 100.0 mW Tolerance= 1.0%	1	\$0.01	 0603 5 mm²
16.	Rfbb	Yageo America	RC0603FR-0733KL Series= ?	Res= 33.0 kOhm Power= 100.0 mW Tolerance= 1.0%	1	\$0.01	 0603 5 mm²
17.	Rfbt	Yageo America	RC0603FR-07120KL Series= ?	Res= 120.0 kOhm Power= 100.0 mW Tolerance= 1.0%	1	\$0.01	 0603 5 mm²







#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
18.	RI	Vishay-Dale	CRCW040210R0FKED Series= CRCW..e3	Res= 10.0 Ohm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
19.	RIc	Vishay-Dale	CRCW04021K33FKED Series= CRCW..e3	Res= 1.33 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
20.	Rsnub	CUSTOM	CUSTOM Series= ?	Res= 5.9803 MOhm Power= 0.0 W Tolerance= 0.0%	1	NA	CUSTOM 0 mm ²
21.	Rsnub2	Vishay-Dale	CRCW040251R1FKED Series= CRCW..e3	Res= 51.1 Ohm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
22.	Rst1	CUSTOM	CUSTOM Series= ?	Res= 12.4782 MOhm Power= 0.0 W Tolerance= 0.0%	1	NA	CUSTOM 0 mm ²
23.	Rst2	CUSTOM	CUSTOM Series= ?	Res= 12.4782 MOhm Power= 0.0 W Tolerance= 0.0%	1	NA	CUSTOM 0 mm ²
24.	Rst3	CUSTOM	CUSTOM Series= ?	Res= 12.4782 MOhm Power= 0.0 W Tolerance= 0.0%	1	NA	CUSTOM 0 mm ²
25.	T1	CUSTOM	CUSTOM	Lp= 11.162 mH Rp= 9.116 Ohm Leakage_L= 33.487 μH Ns1toNp= 0.029 Rs1= 38.776 mOhms Ns2toNp= 0.103 Rs2= 65.967 mOhms	1	NA	CUSTOM 0 mm ²
26.	U1	Texas Instruments	UCC28704DBVR-1	Switcher	1	\$0.30	 SOT-23-6 15 mm ²

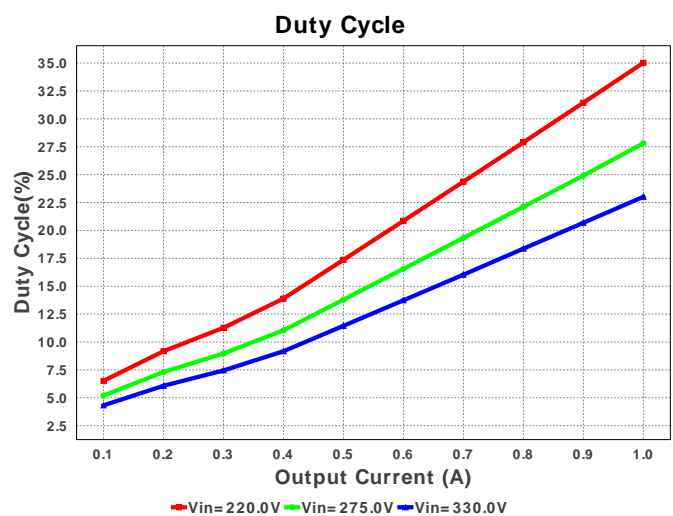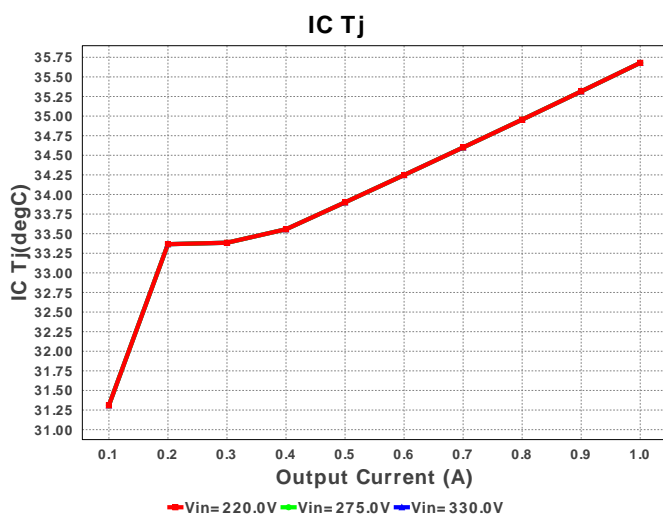


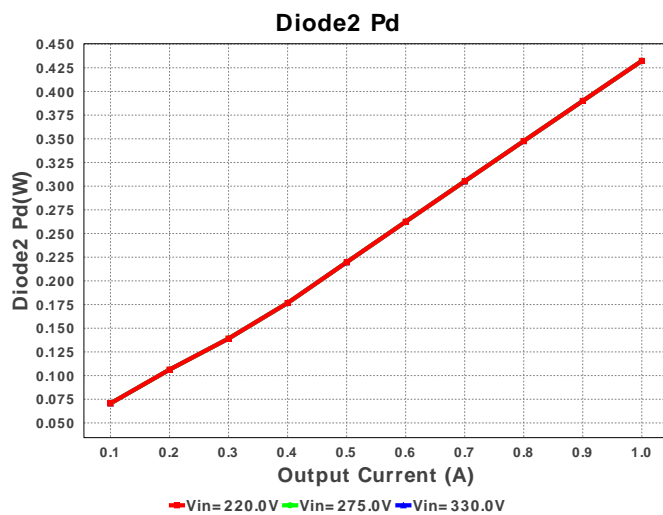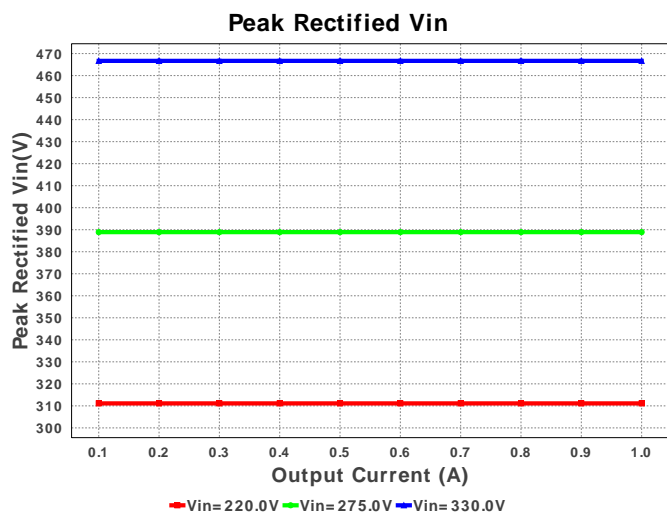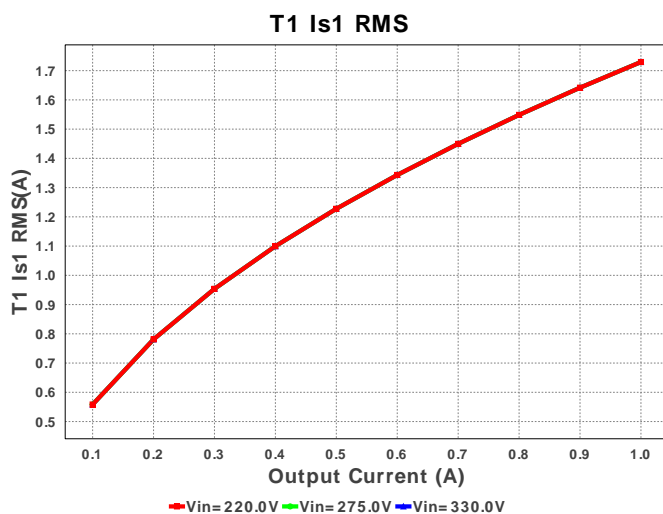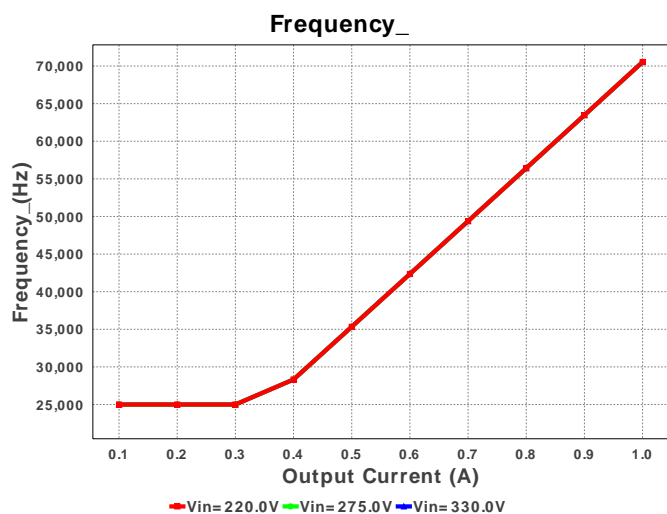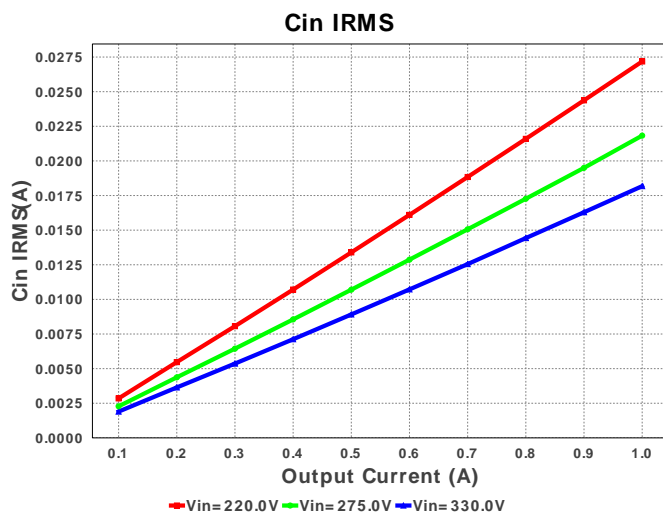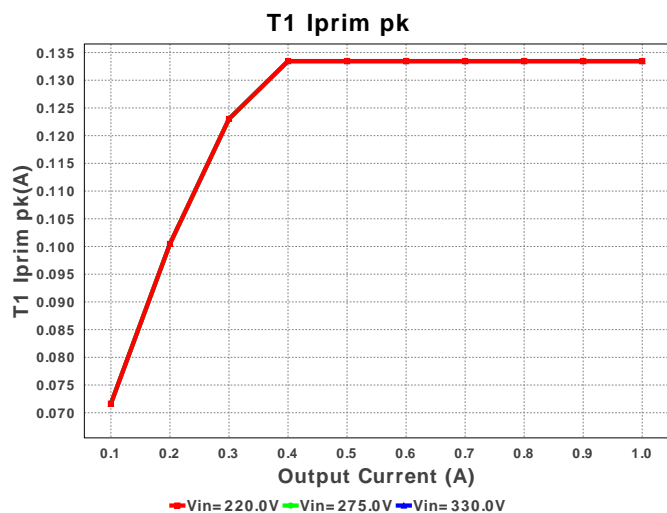

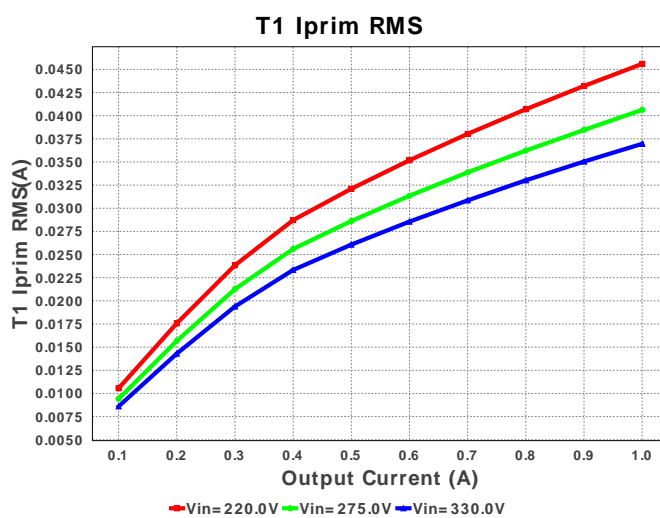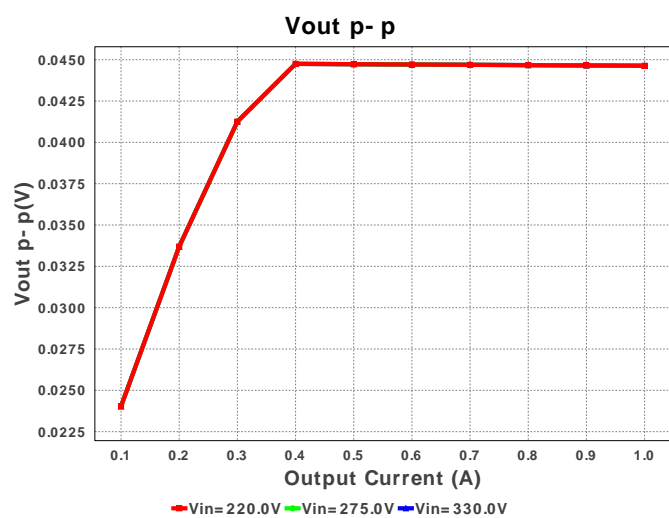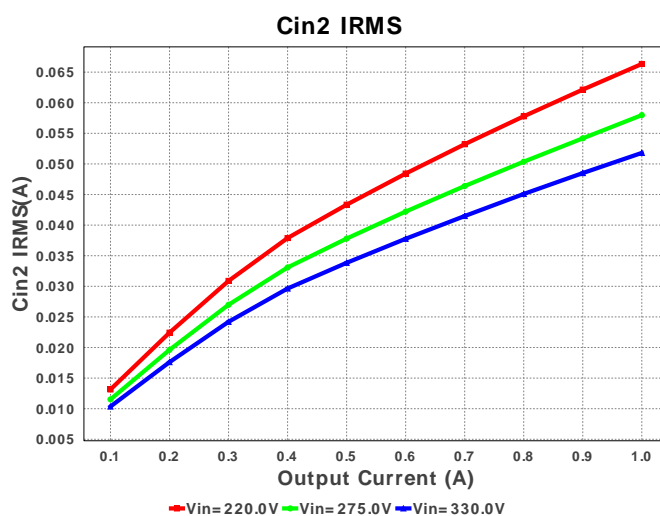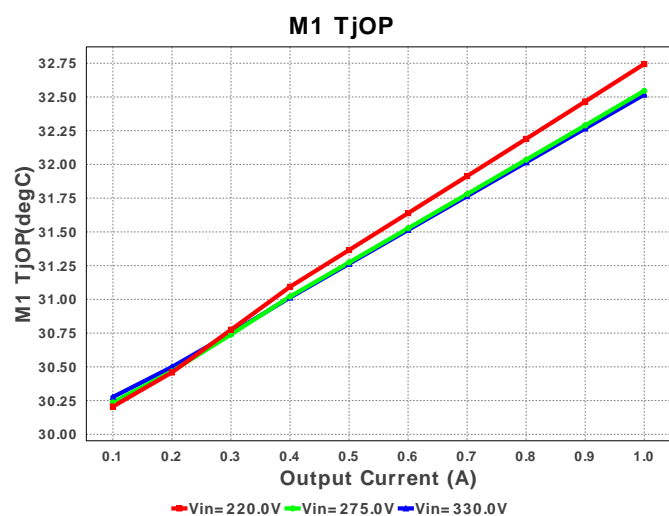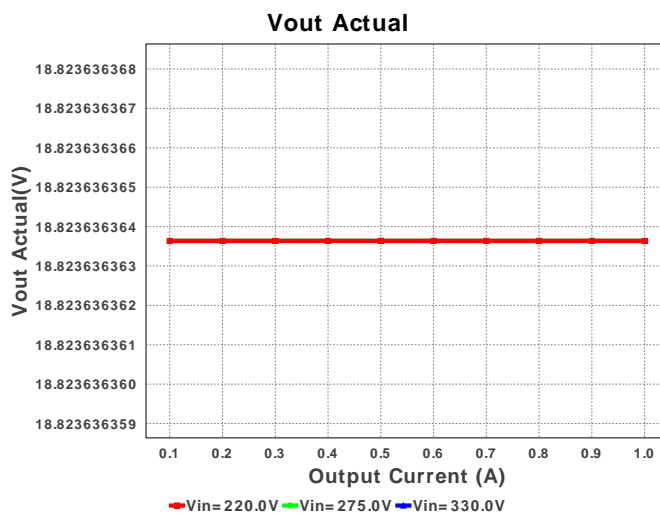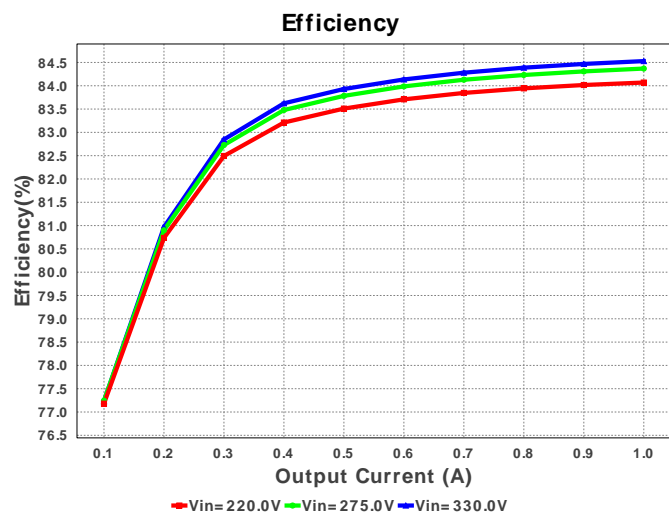

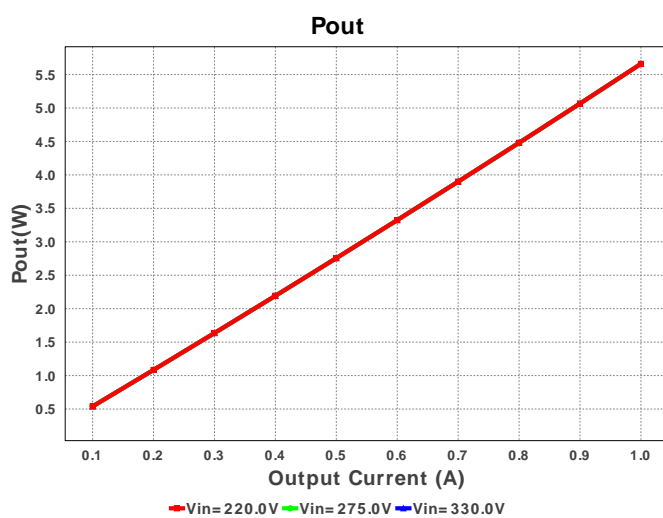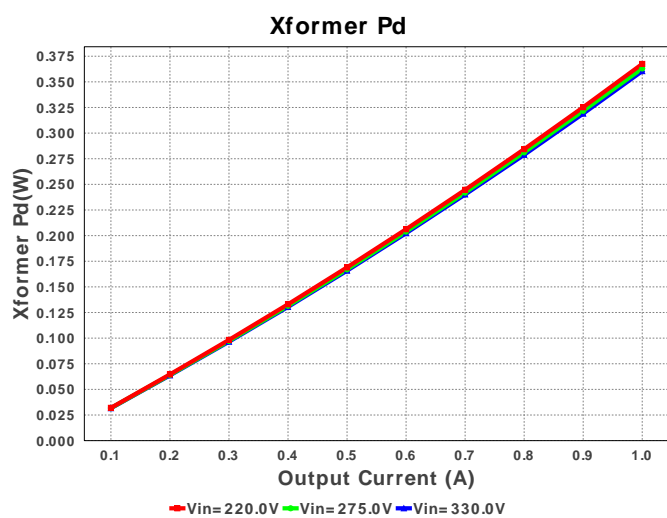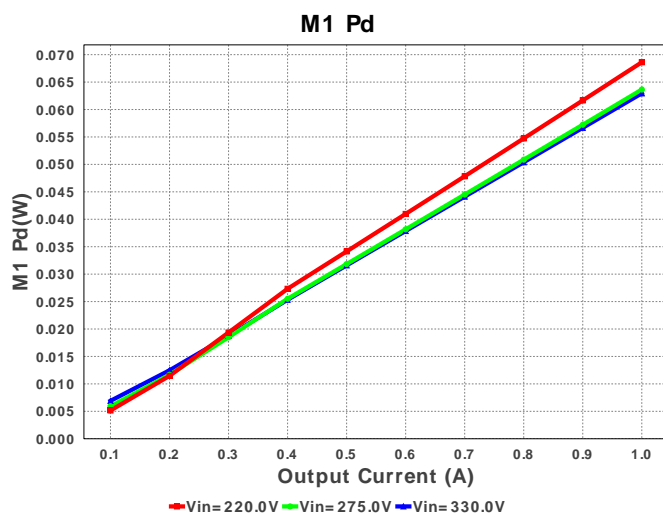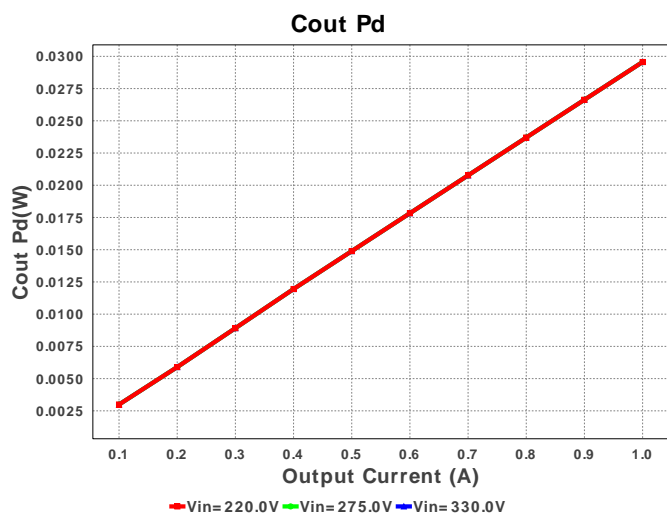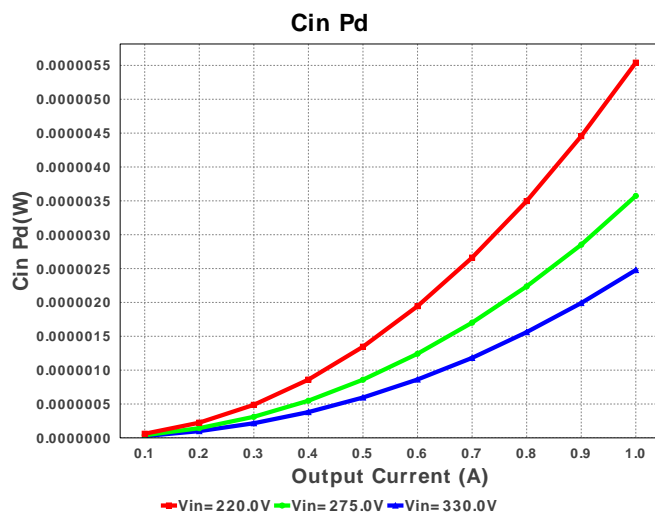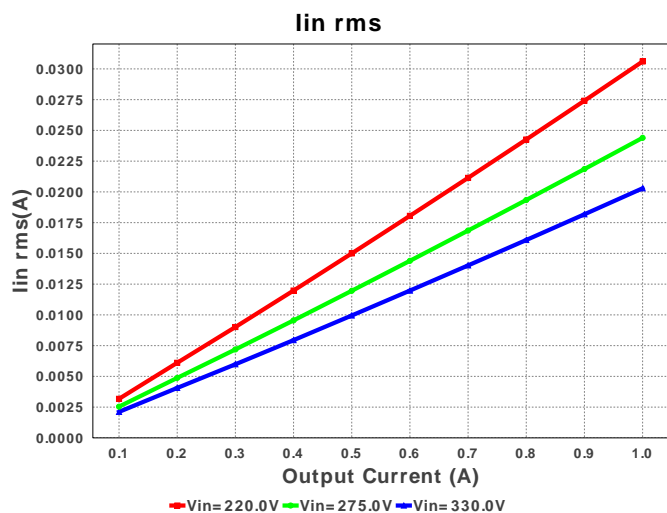

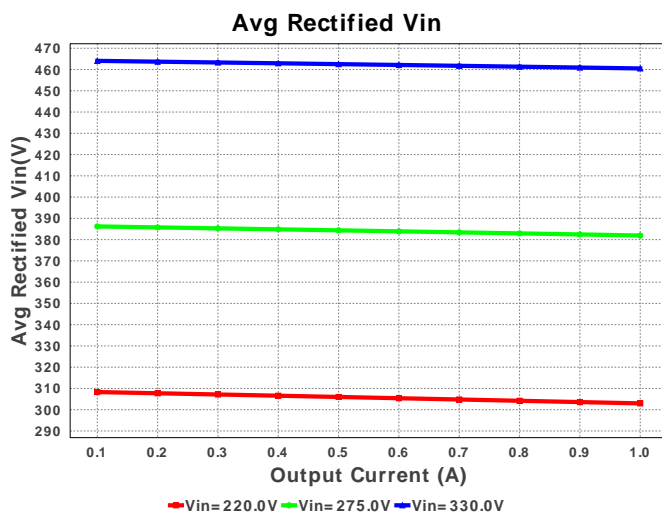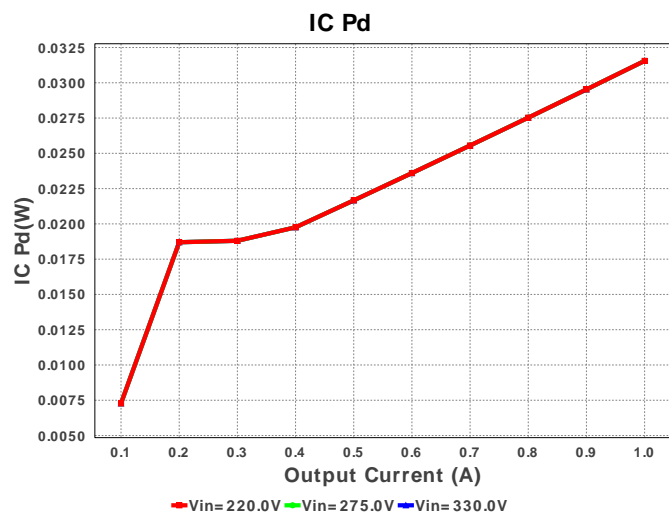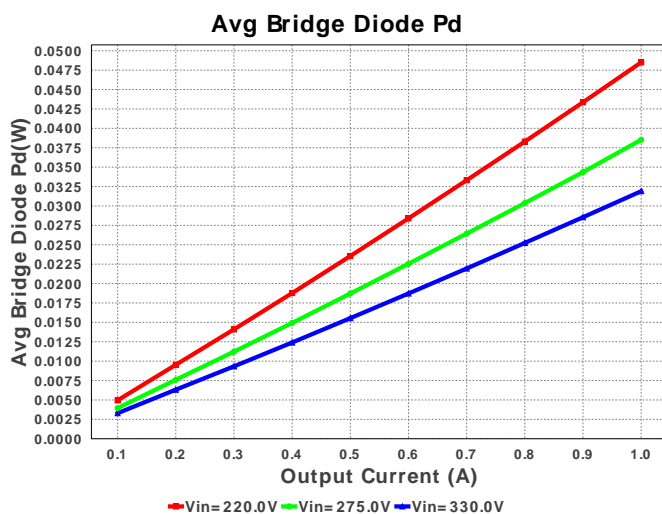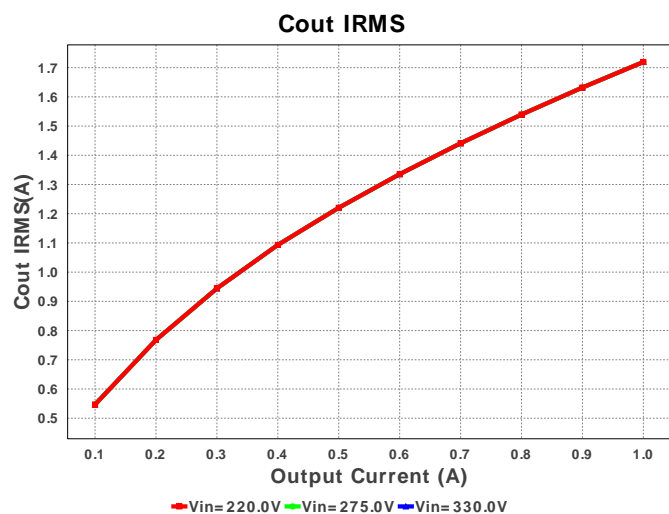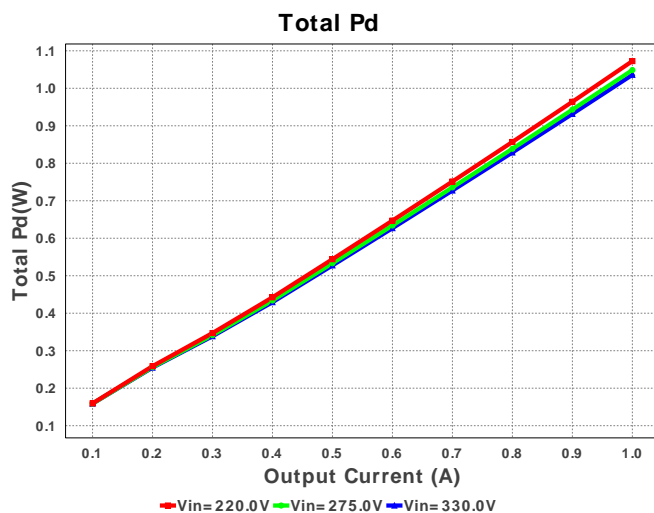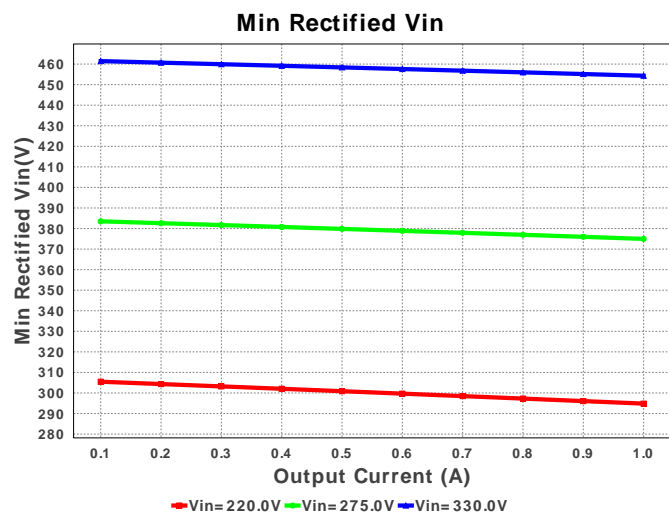

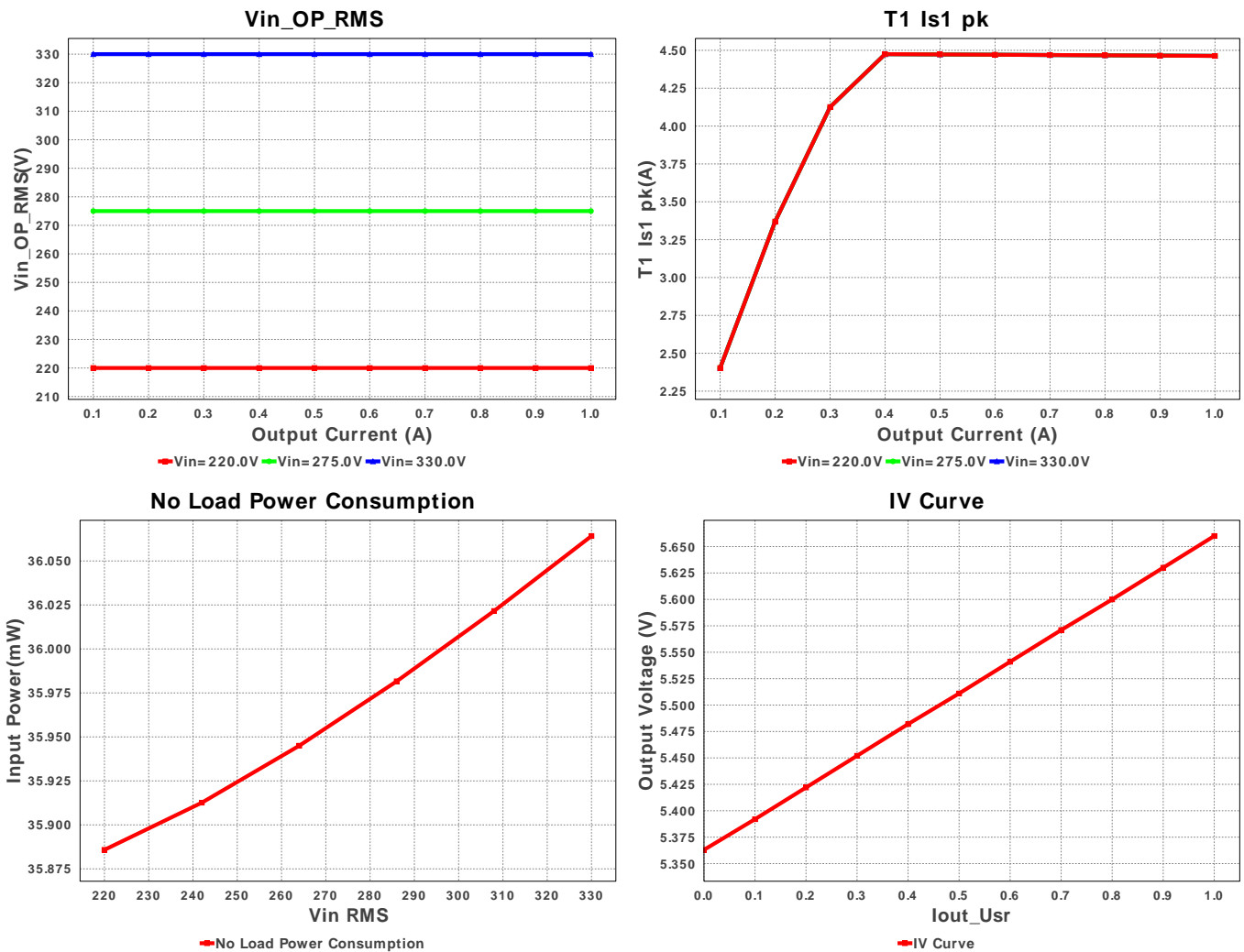

Operating Values

#	Name	Value	Category	Description
1.	Cin IRMS	18.172 mA	Current	Input capacitor RMS ripple current
2.	Cin2 IRMS	51.755 mA	Current	Input Capacitor Cin2 RMS Ripple Current
3.	Cout IRMS	1.719 A	Current	Output capacitor RMS ripple current
4.	Iin rms	20.254 mA	Current	RMS Input Current
5.	T1 Iprim RMS	36.909 mA	Current	Transformer Primary RMS Current
6.	T1 Iprim pk	133.452 mA	Current	Transformer Primary Peak Current
7.	T1 Is1 RMS	1.73 A	Current	Transformer Secondary1 RMS Current
8.	T1 Is1 pk	4.463 A	Current	Transformer Secondary1 Peak Current
9.	Avg Rectified Vin	461.759 V	General	Average Rectified Voltage for the AC Line Period
10.	BOM Count	28	General	Total Design BOM count
11.	FootPrint	3.336 k mm ²	General	Total Foot Print Area of BOM components
12.	Pout	5.66 W	General	Total output power
13.	Total BOM	\$0.0	General	Total BOM Cost
14.	Vout Actual	18.824 V	Op_Point	Vout Actual calculated based on selected voltage divider resistors
15.	Duty Cycle	22.947 %	Op_point	Duty cycle
16.	Efficiency	84.681 %	Op_point	Steady state efficiency
17.	Frequency_	70.531 kHz	Op_point	Switching frequency
18.	IC Tj	32.209 degC	Op_point	IC junction temperature
19.	ICThetaJA	70.0 degC/W	Op_point	IC junction-to-ambient thermal resistance
20.	IOUT_OP	1.0 A	Op_point	Iout operating point
21.	M1 TJOP	32.518 degC	Op_point	M1 MOSFET junction temperature
22.	Min Rectified Vin	456.832 V	Op_point	Minimum voltage seen at rectified input
23.	Peak Rectified Vin	466.686 V	Op_point	Peak voltage seen at rectified input
24.	Vin_OP_RMS	330.0 V	Op_point	AC Input RMS Voltage
25.	Vout p-p	44.634 mV	Op_point	Peak-to-peak output ripple voltage
26.	Avg Bridge Diode Pd	17.956 mW	Power	Average Power Dissipation in the Bridge Diode over the AC Line Period
27.	Cin Pd	2.477 μ W	Power	Input capacitor power dissipation
28.	Cout Pd	29.563 mW	Power	Output capacitor power dissipation
29.	Diode2 Pd	432.302 mW	Power	Diode2 power dissipation
30.	IC Pd	31.551 mW	Power	IC power dissipation
31.	M1 Pd	62.958 mW	Power	M1 MOSFET total power dissipation

#	Name	Value	Category	Description
32.	Total Pd	1.024 W	Power	Total Power Dissipation
33.	Xformer Pd	360.424 mW	Power	Transformer power dissipation
34.	Vout Tolerance	1.785 %		Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable

Design Inputs

#	Name	Value	Description
1.	Iout	1.0	Maximum Output Current
2.	VinMax	330.0	Maximum input voltage
3.	VinMin	220.0	Minimum input voltage
4.	Vout	5.0	Output Voltage
5.	acFrequency	60.0	Light Output in Lumen
6.	base_pn	UCC28704	Texas Instruments Base Part Number
7.	source	AC	Input Source Type
8.	ta	30.0	Ambient temperature

Design Assistance

1. Application Hints: T1: The transformer parameters assume that an RM6 core is used, and the DCR values are assumed values used only for efficiency estimates. Rbld: Rbld is used to set a minimum load for the circuit, so that in standby the output voltage does not float up. The value chosen by WEBENCH should be a good starting point but may need to be adjusted to achieve minimum power dissipation at standby as well. Rlc: Rlc provides the function of feed-forward line compensation to eliminate change in IPP due to change in di/dt and the propagation delay of the internal comparator and MOSFET turn-off time. For best results the chosen value may need to be adjusted based on board, FET and transformer parasitics. Rfbb: The feedback resistors will set the output voltage of the circuit. The values chosen may need to be fine tuned based on the final Transformer turns ratios and the voltage across the output diode at close to zero current. Cdd: Cdd supplies the device operating current until the output of the converter reaches the target minimum operating voltage. The value calculated by WEBENCH for Cdd is a good starting point since it assumes that the output current of the Flyback is available to charge the output capacitance until the minimum output voltage is achieved, but may need to be adjusted. Part Description: The UCC28704 Flyback power supply controller provides Constant-Voltage (CV) and Constant-Current (CC) output regulation. Primary-Side Regulation (PSR) eliminates the use of an Opto-Coupler. Please see the datasheet for further design guidance. <http://www.ti.com/lit/ds/symlink/ucc28704.pdf>

2. UCC28704 Product Folder : <http://www.ti.com/product/UCC28704> : contains the data sheet and other resources.

Texas Instruments' WEBENCH simulation tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Simulations are created using Texas Instruments' published specifications as well as the published specifications of other device manufacturers. While Texas Instruments does update this information periodically, this information may not be current at the time the simulation is built. Texas Instruments does not warrant the accuracy or completeness of the specifications or any information contained therein. Texas Instruments does not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. Texas Instruments does not warrant that the designs are production worthy.

You should completely validate and test your design implementation to confirm the system functionality for your application prior to production.

Use of Texas Instruments' WEBENCH simulation tools is subject to [Texas Instruments' Site Terms and Conditions of Use](#). Prototype boards based on WEBENCH created designs are provided AS IS without warranty of any kind for evaluation and testing purposes and are subject to the terms of the [Evaluation License Agreement](#).