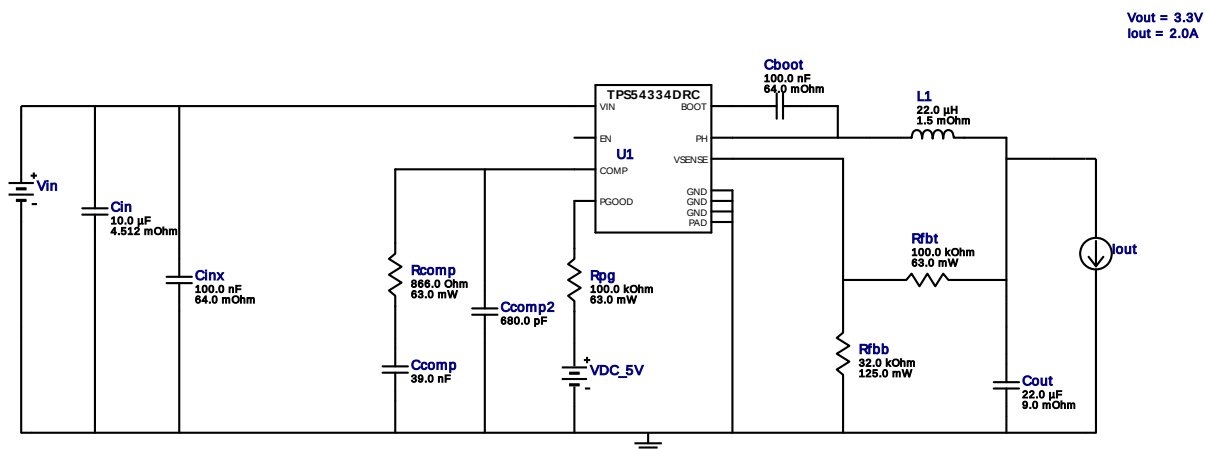



WEBENCH® Design Report

Design : 4331192/24 TPS54334DRCR
TPS54334DRCR 14.0V-22.0V to 3.30V @ 2.0A












Electrical BOM







#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	Cboot	Kemet	C0805C104K5RACTU Series= X7R	Cap= 100.0 nF ESR= 64.0 mOhm VDC= 50.0 V IRMS= 1.64 A	1	\$0.01	0805 7 mm ²
2.	Ccomp	MuRata	GRM155R61A393KA01D Series= X5R	Cap= 39.0 nF VDC= 10.0 V IRMS= 0.0 A	1	\$0.01	0402 3 mm ²
3.	Ccomp2	Yageo America	CC0805KRX7R9BB681 Series= X7R	Cap= 680.0 pF VDC= 50.0 V IRMS= 0.0 A	1	\$0.01	0805 7 mm ²
4.	Cin	MuRata	GRM31CR61E106KA12L Series= X5R	Cap= 10.0 uF ESR= 4.512 mOhm VDC= 25.0 V IRMS= 2.447 A	1	\$0.05	1206_190 11 mm ²
5.	Cinx	Kemet	C0805C104K5RACTU Series= X7R	Cap= 100.0 nF ESR= 64.0 mOhm VDC= 50.0 V IRMS= 1.64 A	1	\$0.01	0805 7 mm ²
6.	Cout	MuRata	GRM21BR60J226ME39L Series= X5R	Cap= 22.0 uF ESR= 9.0 mOhm VDC= 6.3 V IRMS= 3.5 A	1	\$0.04	0805 7 mm ²
7.	L1	Coilcraft	SER2915L-223KL	L= 22.0 uH DCR= 1.5 mOhm	1	\$1.88	SER2915L 652 mm ²
8.	Rcomp	Vishay-Dale	CRCW0402866RFKED Series= CRCW..e3	Res= 866.0 Ohm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²

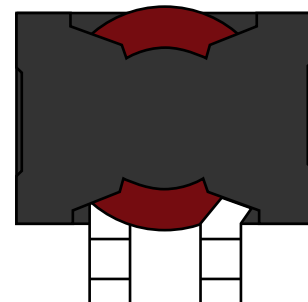


#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
9.	Rfbb	Yageo America	RT0805BRD0732KL Series= ?	Res= 32.0 kOhm Power= 125.0 mW Tolerance= 0.1%	1	\$0.05	0805 7 mm ²
10.	Rfbt	Vishay-Dale	CRCW0402100KFKED Series= CRCW..e3	Res= 100.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²
11.	Rpg	Vishay-Dale	CRCW0402100KFKED Series= CRCW..e3	Res= 100.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²
12.	U1	Texas Instruments	TPS54334DRCR	Switcher	1	\$0.95	DRC0010J 16 mm ²

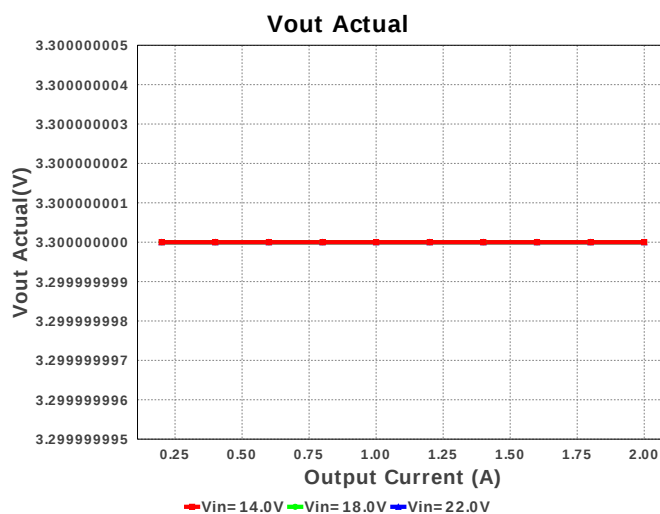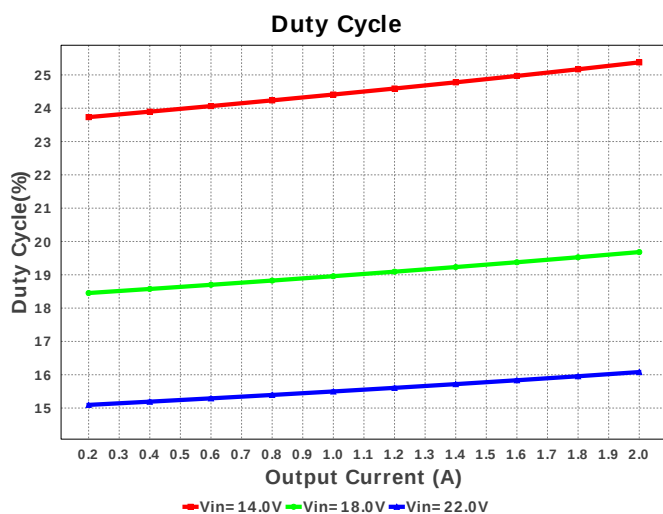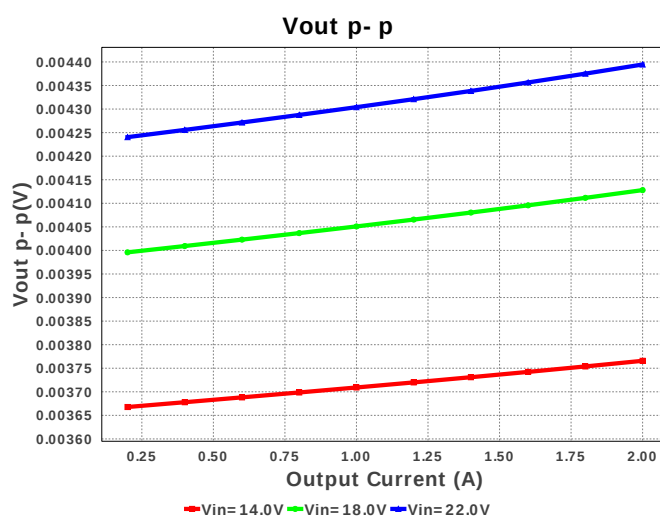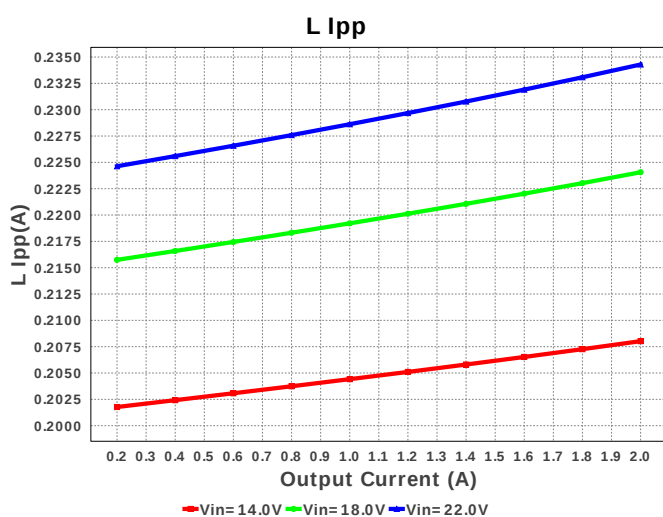

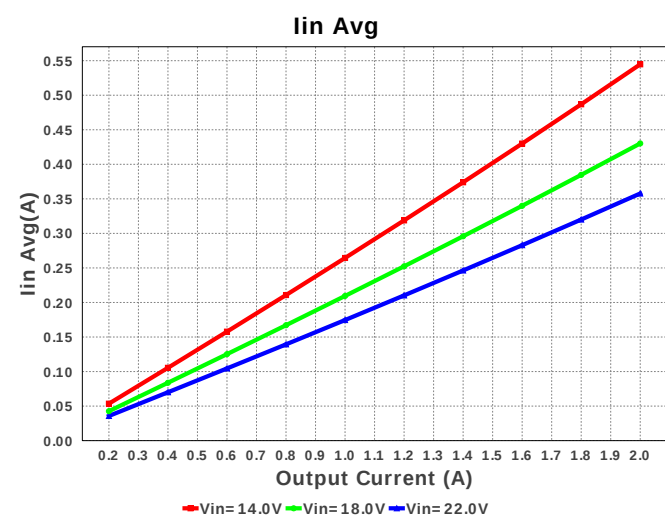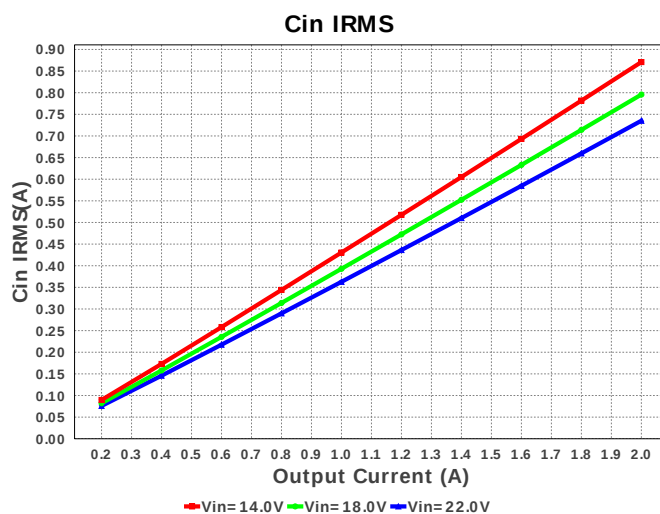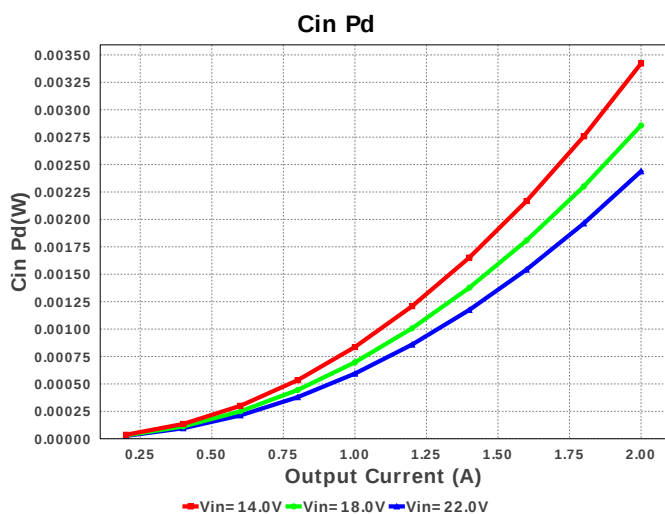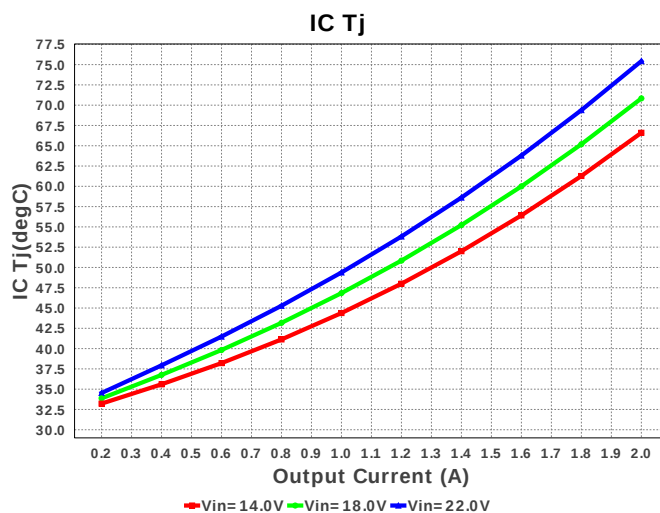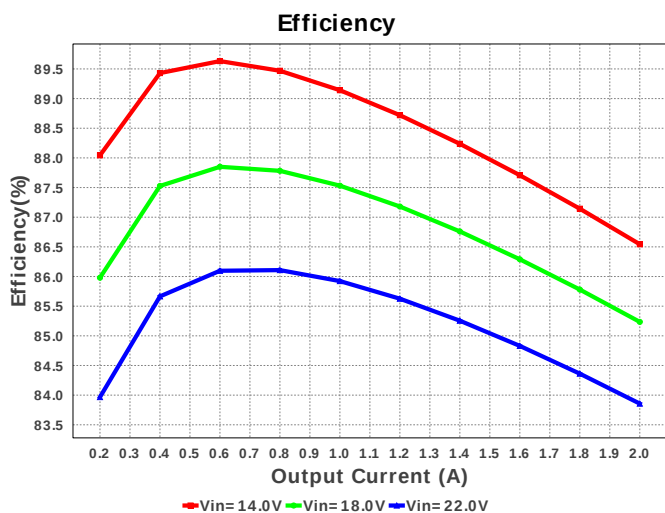

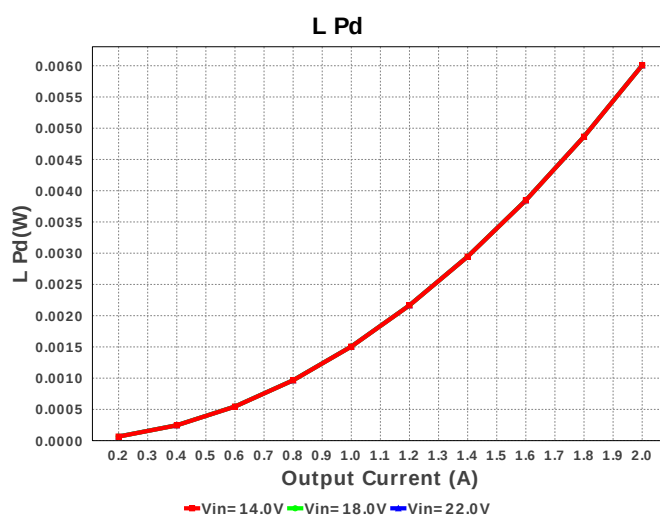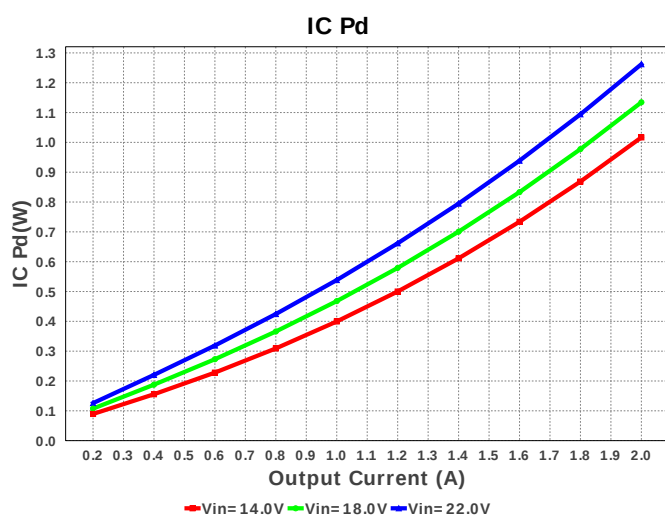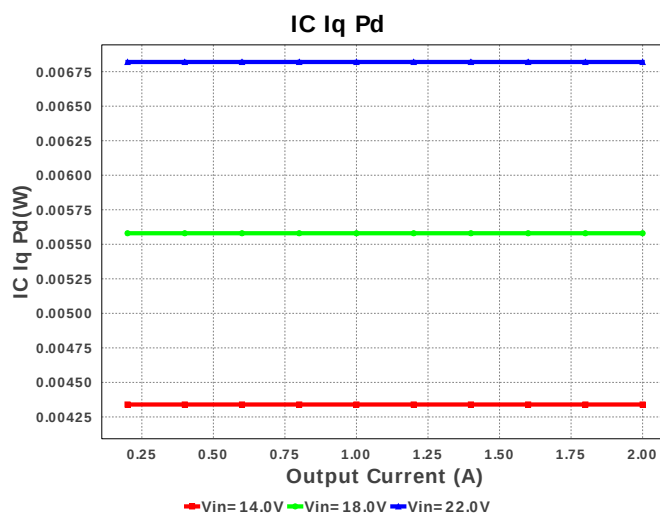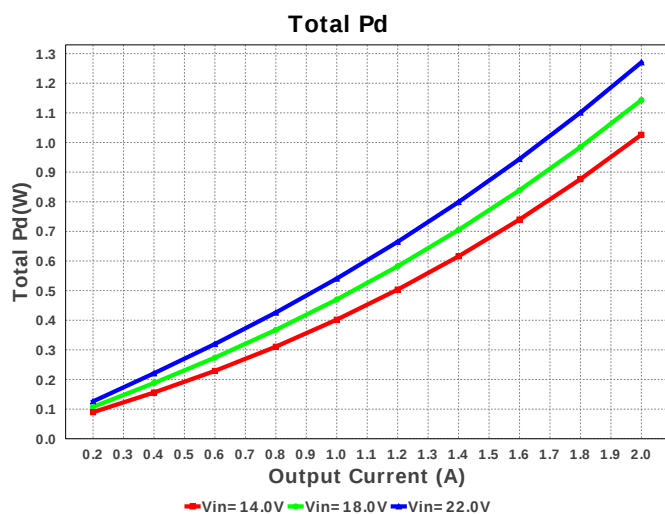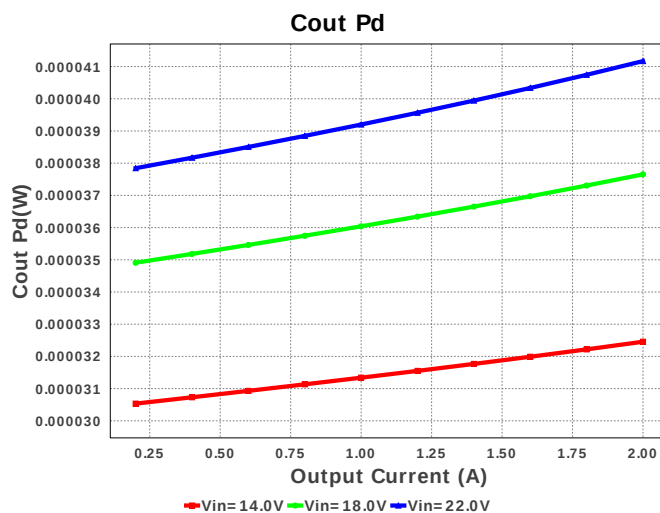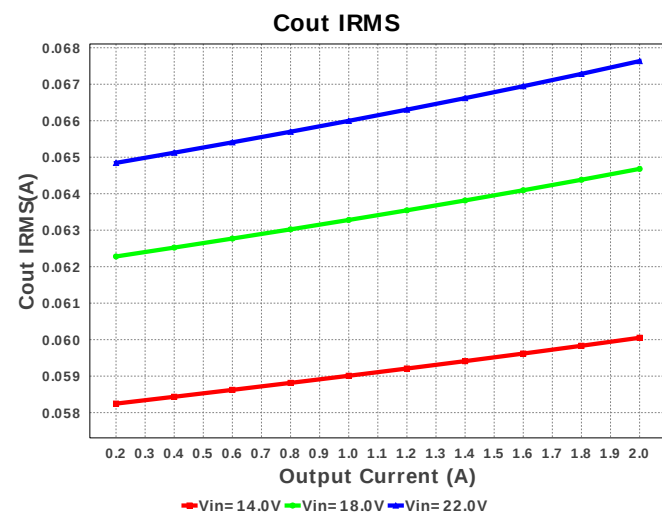

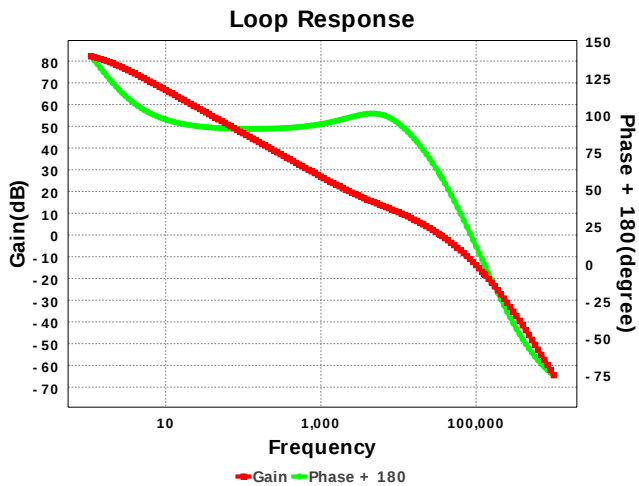

Operating Values

#	Name	Value	Category	Description
1.	Cin IRMS	735.198 mA	Current	Input capacitor RMS ripple current
2.	Cout IRMS	67.634 mA	Current	Output capacitor RMS ripple current
3.	Iin Avg	357.75 mA	Current	Average input current
4.	L Ipp	234.29 mA	Current	Peak-to-peak inductor ripple current
5.	BOM Count	12	General	Total Design BOM count
6.	FootPrint	724.0 mm ²	General	Total Foot Print Area of BOM components
7.	Frequency	570.0 kHz	General	Switching frequency
8.	IC Tolerance	10.0 mV	General	IC Feedback Tolerance
9.	Mode	CCM	General	Conduction Mode
10.	Pout	6.6 W	General	Total output power
11.	Total BOM	\$3.04	General	Total BOM Cost
12.	ICThetaJA Effective	36.0 degC/W	Op_Point	Effective IC Junction-to-Ambient Thermal Resistance
13.	Low Freq Gain	82.143 dB	Op_Point	Gain at 10Hz
14.	Vout Actual	3.3 V	Op_Point	Vout Actual calculated based on selected voltage divider resistors
15.	Vout OP	3.3 V	Op_Point	Operational Output Voltage
16.	Cross Freq	34.7 kHz	Op_point	Bode plot crossover frequency
17.	Duty Cycle	16.08 %	Op_point	Duty cycle
18.	Efficiency	83.857 %	Op_point	Steady state efficiency
19.	Gain Marg	-18.042 dB	Op_point	Bode Plot Gain Margin
20.	IC Tj	75.432 degC	Op_point	IC junction temperature
21.	IOUT_OP	2.0 A	Op_point	Iout operating point
22.	Phase Marg	59.731 deg	Op_point	Bode Plot Phase Margin
23.	VIN_OP	22.0 V	Op_point	Vin operating point
24.	Vout p-p	4.395 mV	Op_point	Peak-to-peak output ripple voltage
25.	Cin Pd	2.439 mW	Power	Input capacitor power dissipation
26.	Cout Pd	41.17 μW	Power	Output capacitor power dissipation
27.	IC Iq Pd	6.82 mW	Power	IC Iq Pd
28.	IC Pd	1.262 W	Power	IC power dissipation
29.	L Pd	6.007 mW	Power	Inductor power dissipation
30.	Total Pd	1.271 W	Power	Total Power Dissipation
31.	Vout Tolerance	2.095 %		Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable

Design Inputs

#	Name	Value	Description
1.	Iout	2.0	Maximum Output Current
2.	VinMax	22.0	Maximum input voltage
3.	VinMin	14.0	Minimum input voltage
4.	Vout	3.3	Output Voltage
5.	base_pn	TPS54334	Base Product Number
6.	source	DC	Input Source Type
7.	Ta	30.0	Ambient temperature

Design Assistance

1. **TPS54334** Product Folder : <http://www.ti.com/product/TPS54334> : contains the data sheet and other resources.

Texas Instruments' WEBENCH simulation tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Simulations are created using Texas Instruments' published specifications as well as the published specifications of other device manufacturers. While Texas Instruments does update this information periodically, this information may not be current at the time the simulation is built. Texas Instruments does not warrant the accuracy or completeness of the specifications or any information contained therein. Texas Instruments does not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. Texas Instruments does not warrant that the designs are production worthy.

You should completely validate and test your design implementation to confirm the system functionality for your application prior to production.

Use of Texas Instruments' WEBENCH simulation tools is subject to [Texas Instruments' Site Terms and Conditions of Use](#). Prototype boards based on WEBENCH created designs are provided AS IS without warranty of any kind for evaluation and testing purposes and are subject to the terms of the [Evaluation License Agreement](#).