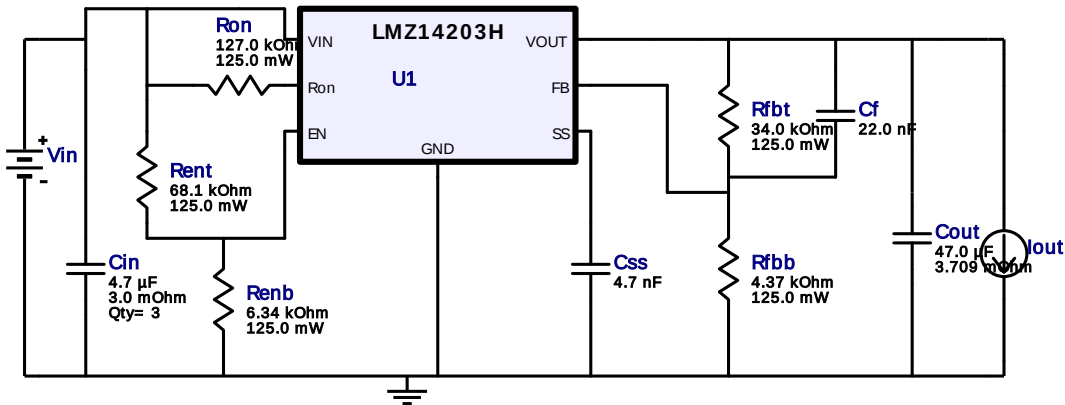


WEBENCH® Design Report

Design : 4740075/9 LMZ14203HTZ/NOPB
LMZ14203HTZ/NOPB 14.0V-36.0V to 7.00V @ 2.0A

Vout = 7.0V
Iout = 2.0A








My Comments







No comments







Electrical BOM

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	Cf	Yageo America	CC0805KRX7R9BB223 Series= X7R	Cap= 22.0 nF VDC= 50.0 V IRMS= 0.0 A	1	\$0.01	0805 7 mm ²
2.	Cin	MuRata	GRM31CR71H475KA12L Series= X7R	Cap= 4.7 uF ESR= 3.0 mOhm VDC= 50.0 V IRMS= 4.98 A	3	\$0.07	1206 11 mm ²
3.	Cout	MuRata	GRM31CR61A476KE15L Series= X5R	Cap= 47.0 uF ESR= 3.709 mOhm VDC= 10.0 V IRMS= 4.2862 A	1	\$0.15	1206_190 11 mm ²
4.	Css	Yageo America	CC0805KRX7R9BB472 Series= X7R	Cap= 4.7 nF VDC= 50.0 V IRMS= 0.0 A	1	\$0.01	0805 7 mm ²
5.	Renb	Panasonic	ERJ-6ENF6341V Series= ERJ-6E	Res= 6.34 kOhm Power= 125.0 mW Tolerance= 1.0%	1	\$0.01	0805 7 mm ²
6.	Rent	Panasonic	ERJ-6ENF6812V Series= ERJ-6E	Res= 68.1 kOhm Power= 125.0 mW Tolerance= 1.0%	1	\$0.01	0805 7 mm ²
7.	Rfbb	Yageo America	RT0805BRD074K37L Series= RT0805	Res= 4.37 kOhm Power= 125.0 mW Tolerance= 0.1%	1	\$0.05	0805 7 mm ²
8.	Rfbb	Panasonic	ERJ-6ENF3402V Series= ERJ-6E	Res= 34.0 kOhm Power= 125.0 mW Tolerance= 1.0%	1	\$0.01	0805 7 mm ²
9.	Ron	Panasonic	ERJ-6ENF1273V Series= ERJ-6E	Res= 127.0 kOhm Power= 125.0 mW Tolerance= 1.0%	1	\$0.01	0805 7 mm ²

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
10.	U1	Texas Instruments	LMZ14203HTZ/NOPB	Switcher	1	\$9.78	

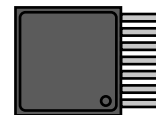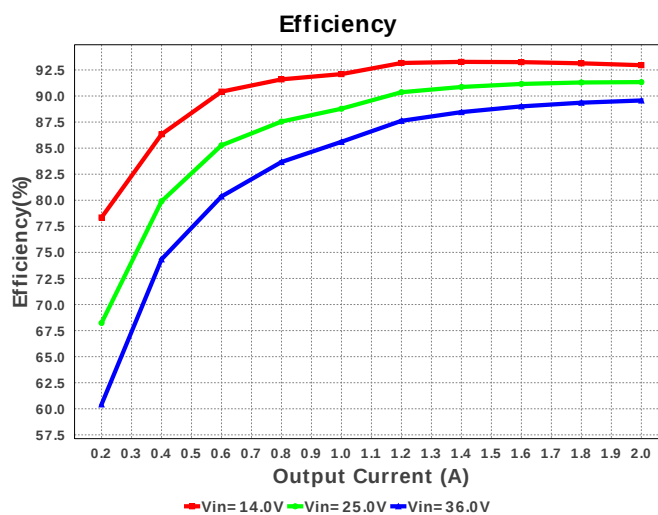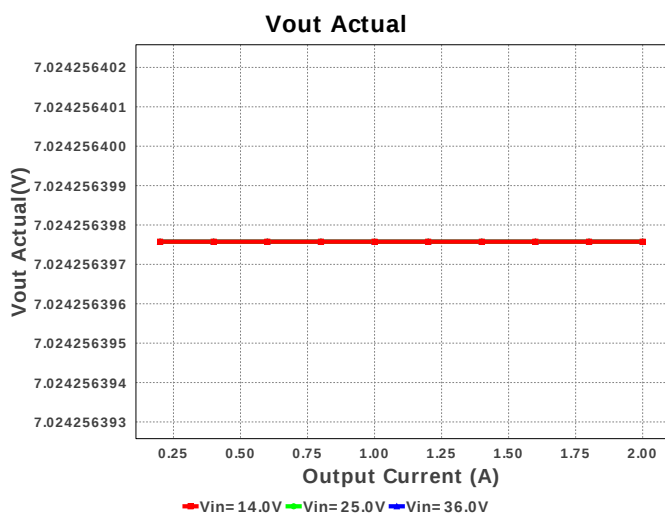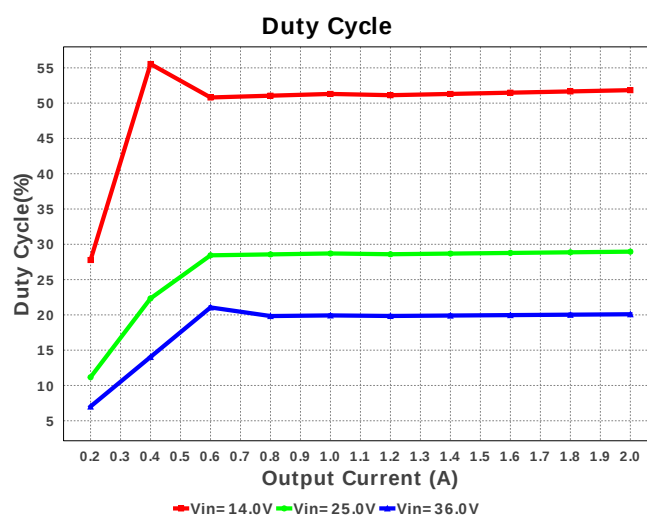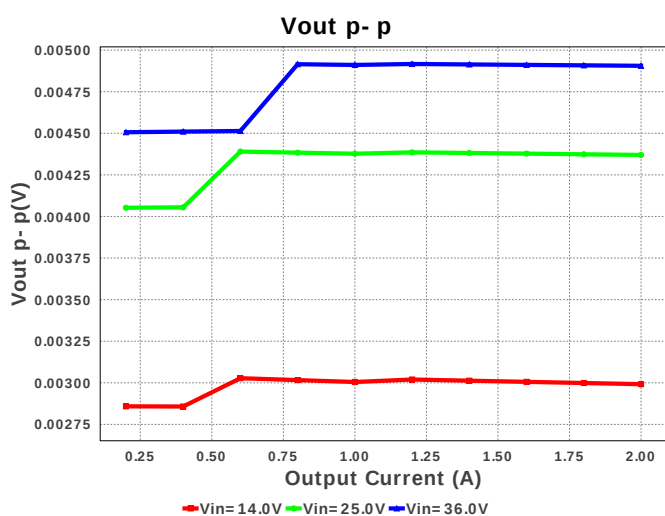TZA07A 199 mm²

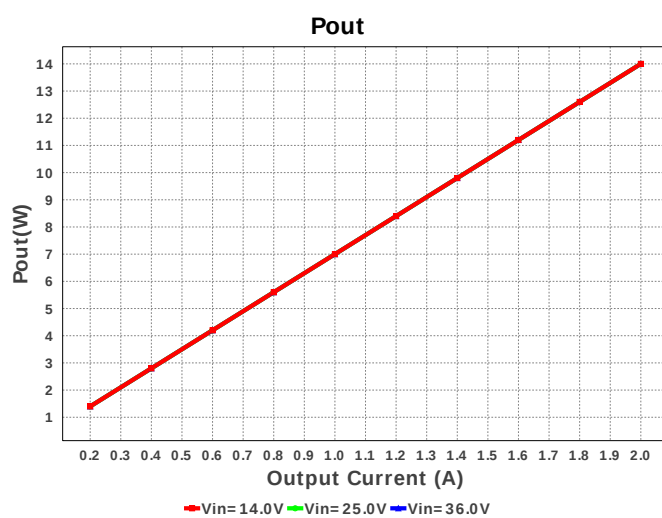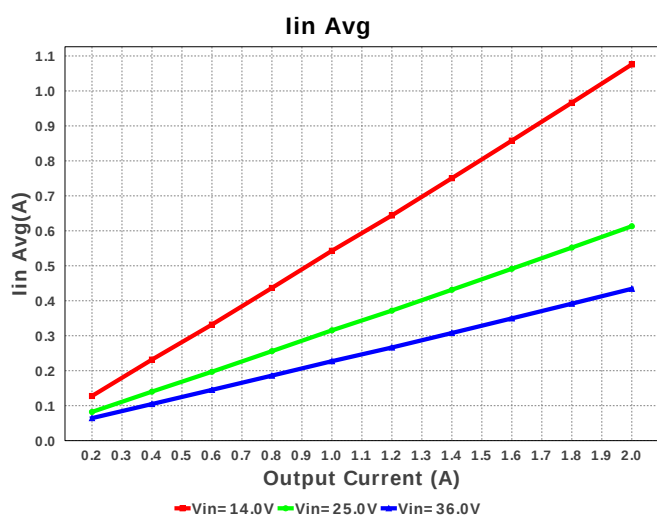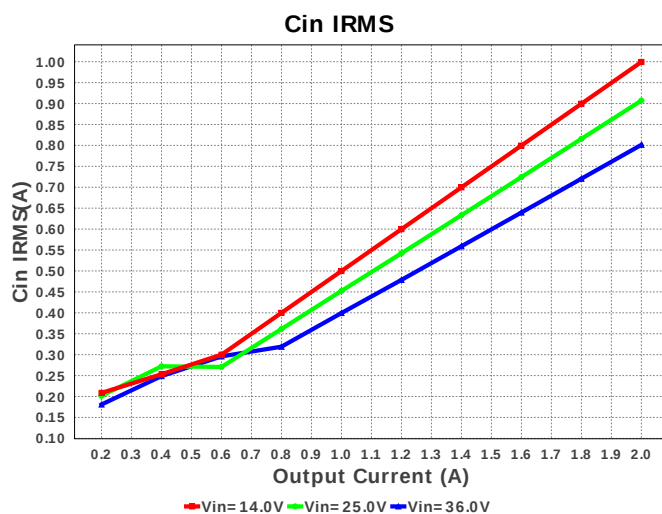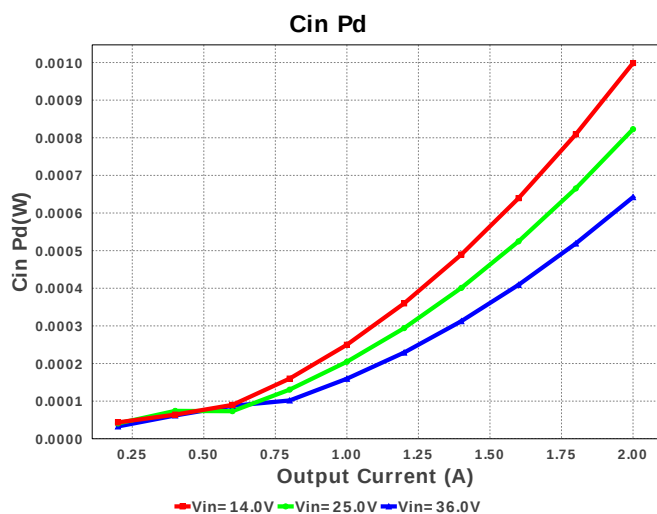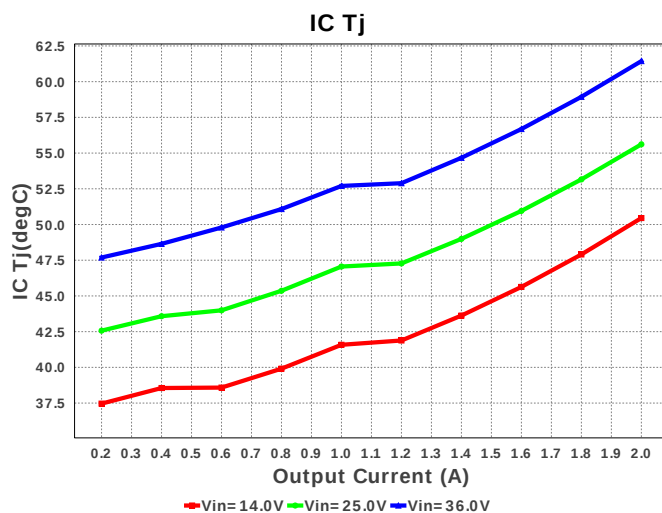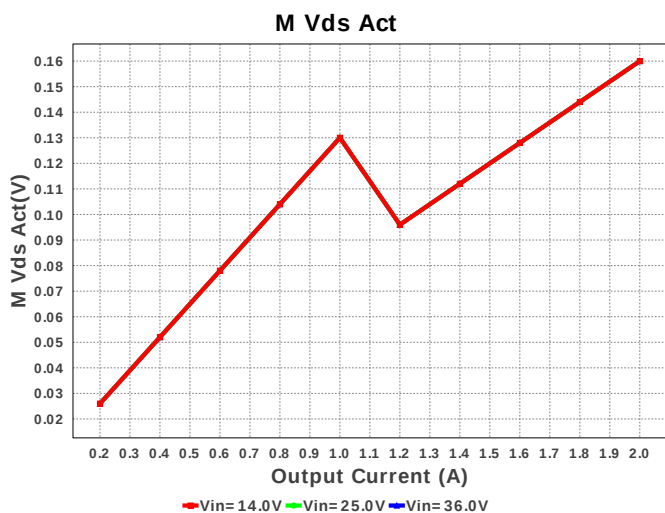

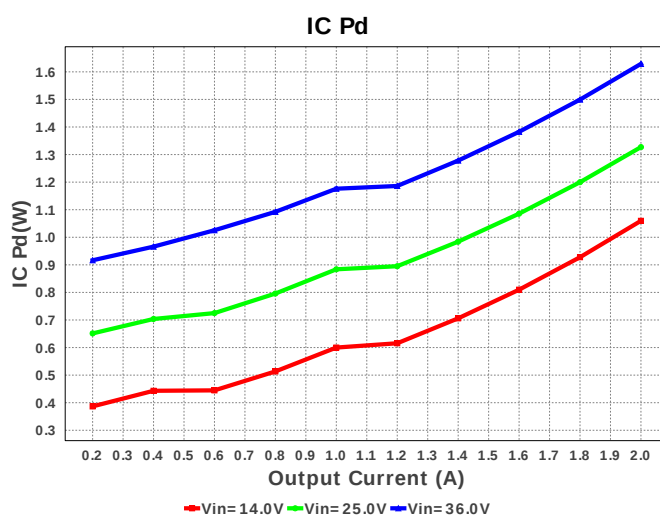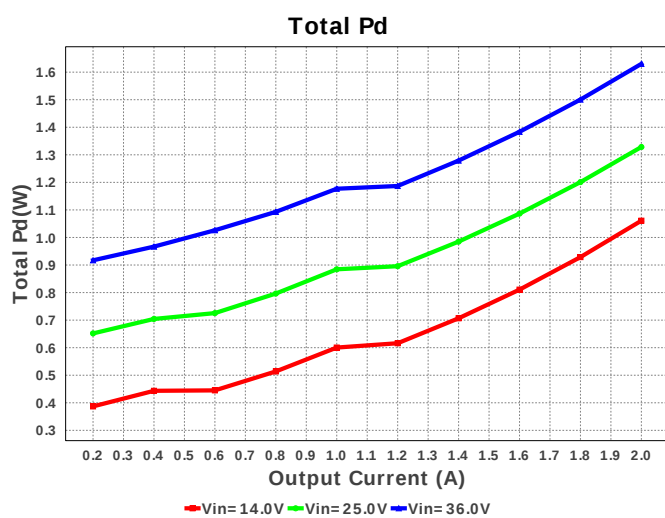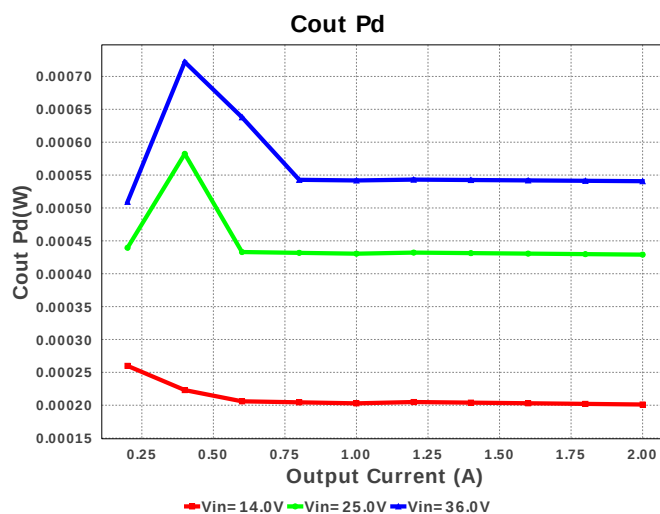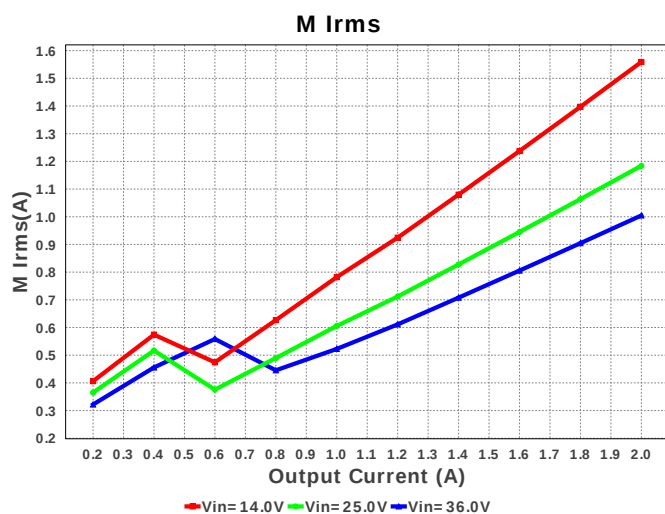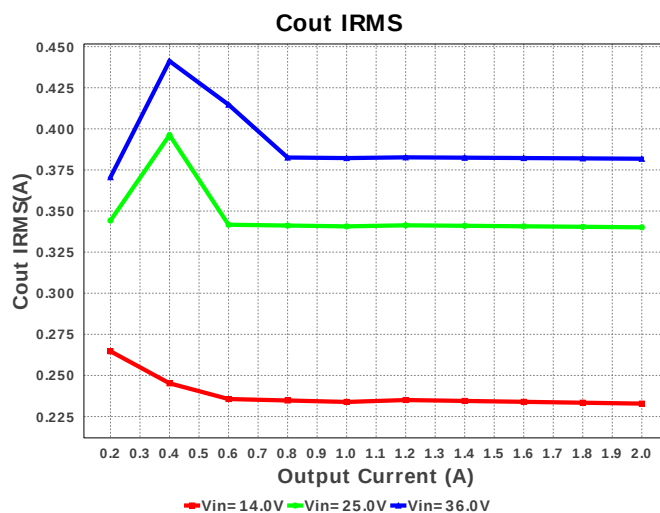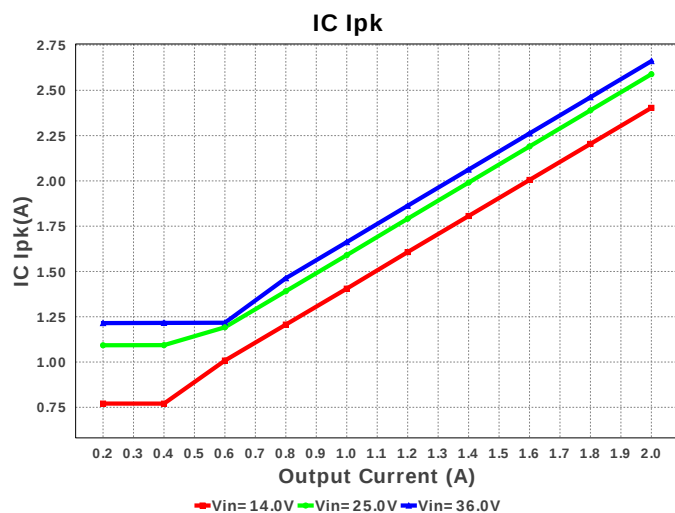

Operating Values

#	Name	Value	Category	Description
1.	Cin IRMS	801.352 mA	Current	Input capacitor RMS ripple current
2.	Cout IRMS	381.812 mA	Current	Output capacitor RMS ripple current
3.	IC Ipk	2.661 A	Current	Peak switch current in IC
4.	Iin Avg	430.65 mA	Current	Average input current
5.	M Irms	996.782 mA	Current	MOSFET RMS current
6.	BOM Count	12	General	Total Design BOM count
7.	FootPrint	290.0 mm ²	General	Total Foot Print Area of BOM components
8.	Frequency	423.985 kHz	General	Switching frequency
9.	IC Tolerance	20.0 mV	General	IC Feedback Tolerance
10.	M Vds Act	160.0 mV	General	Voltage drop across the MosFET
11.	Mode	CCM	General	Conduction Mode

#	Name	Value	Category	Description
12.	Pout	14.0 W	General	Total output power
13.	Total BOM	\$10.25	General	Total BOM Cost
14.	Vout Actual	7.024 V	Op_Point	Vout Actual calculated based on selected voltage divider resistors
15.	Vout OP	7.0 V	Op_Point	Operational Output Voltage
16.	Duty Cycle	20.09 %	Op_point	Duty cycle
17.	Efficiency	90.303 %	Op_point	Steady state efficiency
18.	IC Tj	58.991 degC	Op_point	IC junction temperature
19.	ICThetaJA	19.3 degC/W	Op_point	IC junction-to-ambient thermal resistance
20.	IOUT_OP	2.0 A	Op_point	Iout operating point
21.	VIN_OP	36.0 V	Op_point	Vin operating point
22.	Vout p-p	4.906 mV	Op_point	Peak-to-peak output ripple voltage
23.	Cin Pd	642.165 μ W	Power	Input capacitor power dissipation
24.	Cout Pd	540.699 μ W	Power	Output capacitor power dissipation
25.	IC Pd	1.502 W	Power	IC power dissipation
26.	Total Pd	1.503 W	Power	Total Power Dissipation
27.	Vout Tolerance	3.5 %		Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable

Design Inputs

#	Name	Value	Description
1.	Iout	2.0	Maximum Output Current
2.	Iout1	2.0	Output Current #1
3.	VinMax	36.0	Maximum input voltage
4.	VinMin	14.0	Minimum input voltage
5.	Vout	7.0	Output Voltage
6.	Vout1	7.0	Output Voltage #1
7.	Vout2	6.0	Output Voltage #2
8.	base_pn	LMZ14203H	Texas Instruments Base Part Number
9.	source	DC	Input Source Type
10.	ta	30.0	Ambient temperature

Design Assistance

1. LMZ14203H Product Folder : <http://www.ti.com/product/LMZ14203H> : contains the data sheet and other resources.

Texas Instruments' WEBENCH simulation tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Simulations are created using Texas Instruments' published specifications as well as the published specifications of other device manufacturers. While Texas Instruments does update this information periodically, this information may not be current at the time the simulation is built. Texas Instruments does not warrant the accuracy or completeness of the specifications or any information contained therein. Texas Instruments does not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. Texas Instruments does not warrant that the designs are production worthy.

You should completely validate and test your design implementation to confirm the system functionality for your application prior to production.

Use of Texas Instruments' WEBENCH simulation tools is subject to [Texas Instruments' Site Terms and Conditions of Use](#). Prototype boards based on WEBENCH created designs are provided AS IS without warranty of any kind for evaluation and testing purposes and are subject to the terms of the [Evaluation License Agreement](#).