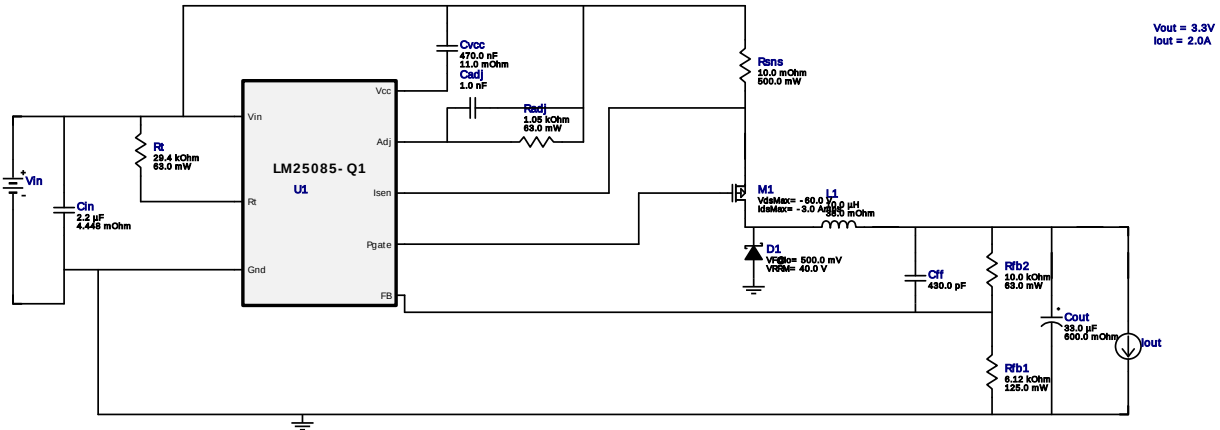


## WEBENCH® Design Report

Design : 4766239/4 LM25085QMY/NOPB  
LM25085QMY/NOPB 14.0V-22.0V to 3.30V @ 2.0A













1. This regulator device is qualified for Automotive applications. All passives and other components selected in this design may not be qualified for Automotive applications. The user is required to verify that all components in the design meet the qualification and safety requirements for their specific application. View WEBENCH(R) Disclaimer.







## Electrical BOM







| #  | Name | Manufacturer              | Part Number                           | Properties                                                      | Qty | Price  | Footprint                                                                                                            |
|----|------|---------------------------|---------------------------------------|-----------------------------------------------------------------|-----|--------|----------------------------------------------------------------------------------------------------------------------|
| 1. | Cadj | Samsung Electro-Mechanics | CL21C102JBCNFNC<br>Series= C0G/NP0    | Cap= 1.0 nF<br>VDC= 50.0 V<br>IRMS= 0.0 A                       | 1   | \$0.01 | <br>0805 7 mm <sup>2</sup>      |
| 2. | Cff  | MuRata                    | GRM1555C1H431GA01D<br>Series= C0G/NP0 | Cap= 430.0 pF<br>VDC= 50.0 V<br>IRMS= 0.0 A                     | 1   | \$0.02 | <br>0402 3 mm <sup>2</sup>      |
| 3. | Cin  | MuRata                    | GRM31CR71H225KA88L<br>Series= X7R     | Cap= 2.2 µF<br>ESR= 4.448 mOhm<br>VDC= 50.0 V<br>IRMS= 2.2252 A | 1   | \$0.05 | <br>1206_190 11 mm <sup>2</sup> |
| 4. | Cout | AVX                       | TPSA336K006R0600<br>Series= TPS       | Cap= 33.0 µF<br>ESR= 600.0 mOhm<br>VDC= 6.3 V<br>IRMS= 318.0 mA | 1   | \$0.13 | <br>3216-18 11 mm <sup>2</sup>  |
| 5. | Cvcc | AVX                       | 0805YC474KAT2A<br>Series= X7R         | Cap= 470.0 nF<br>ESR= 11.0 mOhm<br>VDC= 16.0 V<br>IRMS= 0.0 A   | 1   | \$0.02 | <br>0805 7 mm <sup>2</sup>      |
| 6. | D1   | Diodes Inc.               | B340A-13-F                            | VF@Io= 500.0 mV<br>VRRM= 40.0 V                                 | 1   | \$0.11 | <br>SMA 37 mm <sup>2</sup>      |
| 7. | L1   | TDK                       | VLP8040T-100M                         | L= 10.0 µH<br>DCR= 38.0 mOhm                                    | 1   | \$0.22 | <br>VLP8040 113 mm <sup>2</sup> |
| 8. | M1   | Fairchild Semiconductor   | FDC5614P                              | VdsMax= -60.0 V<br>IdsMax= -3.0 Amps                            | 1   | \$0.23 | <br>SOT-23-6 15 mm <sup>2</sup> |
| 9. | Radj | Vishay-Dale               | CRCW04021K05FKED<br>Series= CRCW..e3  | Res= 1.05 kOhm<br>Power= 63.0 mW<br>Tolerance= 1.0%             | 1   | \$0.01 | <br>0402 3 mm <sup>2</sup>      |

| #   | Name | Manufacturer              | Part Number                          | Properties                                           | Qty | Price  | Footprint                                                                                                     |
|-----|------|---------------------------|--------------------------------------|------------------------------------------------------|-----|--------|---------------------------------------------------------------------------------------------------------------|
| 10. | Rfb1 | Yageo America             | RT0805BRD076K12L<br>Series= RT0805   | Res= 6.12 kOhm<br>Power= 125.0 mW<br>Tolerance= 0.1% | 1   | \$0.05 |  0805 7 mm <sup>2</sup>    |
| 11. | Rfb2 | Vishay-Dale               | CRCW040210K0FKED<br>Series= CRCW..e3 | Res= 10.0 kOhm<br>Power= 63.0 mW<br>Tolerance= 1.0%  | 1   | \$0.01 |  0402 3 mm <sup>2</sup>    |
| 12. | Rsns | Stackpole Electronics Inc | CSR1206FK10L0<br>Series= ?           | Res= 10.0 mOhm<br>Power= 500.0 mW<br>Tolerance= 1.0% | 1   | \$0.11 |  1206 11 mm <sup>2</sup>   |
| 13. | Rt   | Vishay-Dale               | CRCW040229K4FKED<br>Series= CRCW..e3 | Res= 29.4 kOhm<br>Power= 63.0 mW<br>Tolerance= 1.0%  | 1   | \$0.01 |  0402 3 mm <sup>2</sup>    |
| 14. | U1   | Texas Instruments         | LM25085QMY/NOPB                      | Switcher                                             | 1   | \$0.79 |  MUY08A 24 mm <sup>2</sup> |

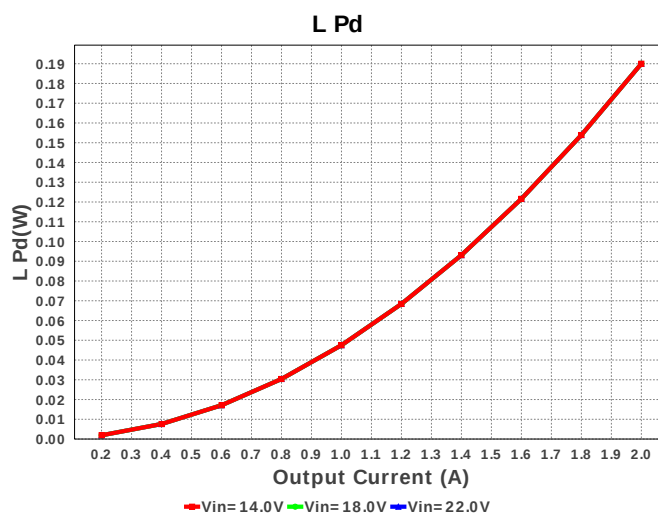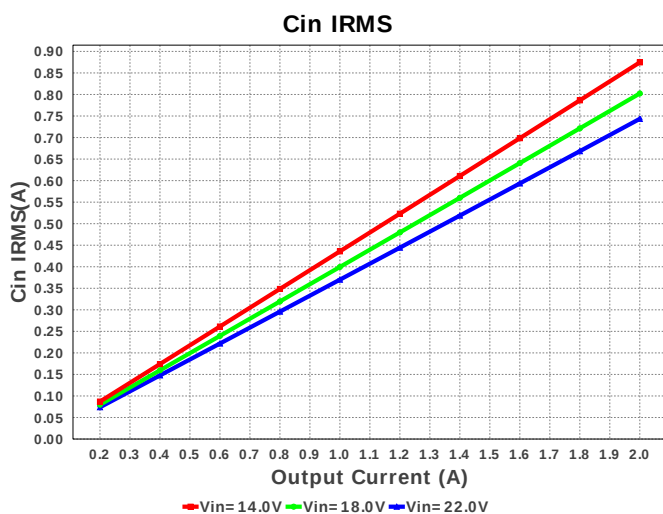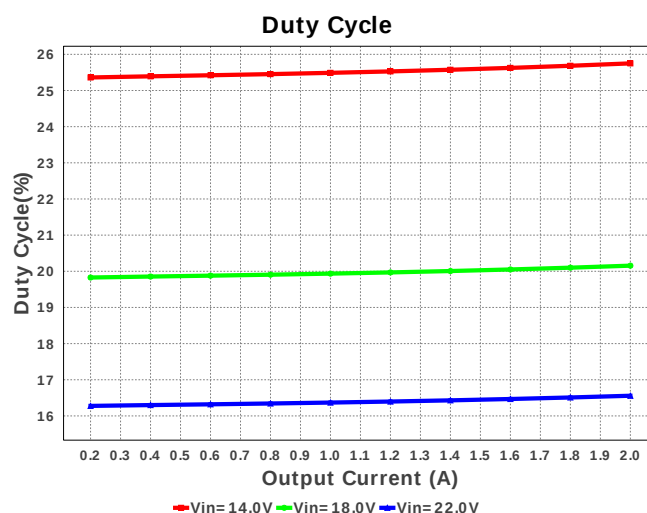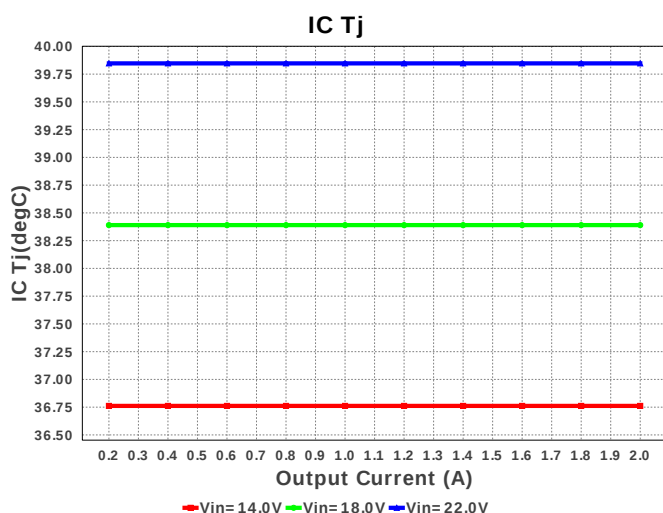

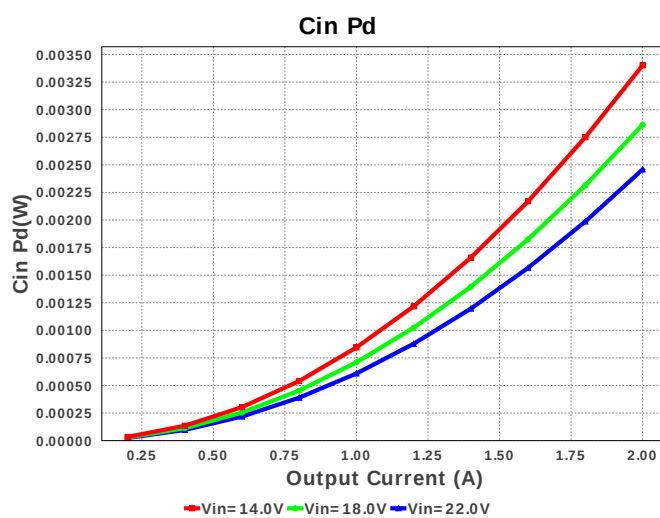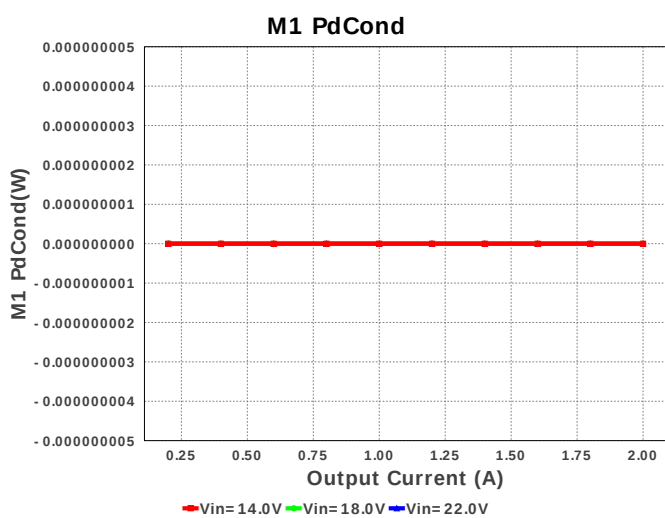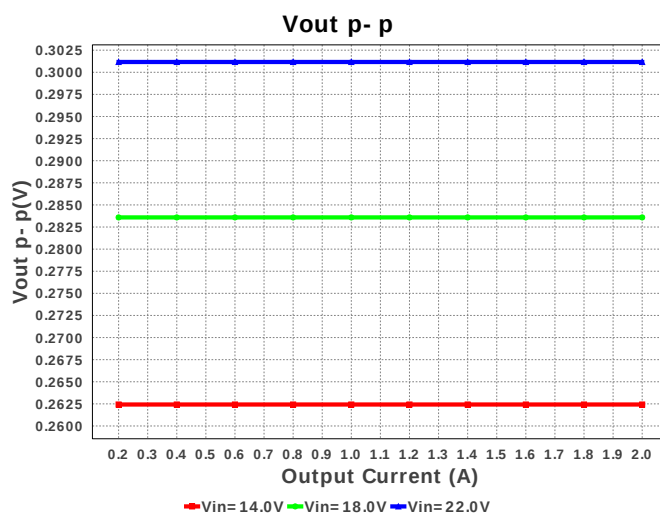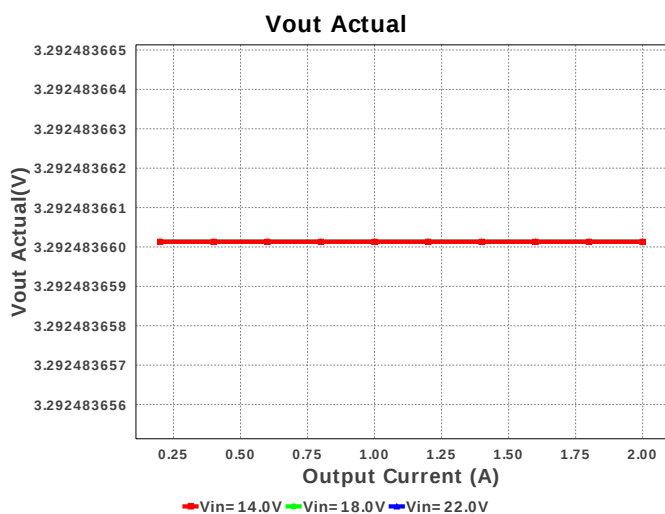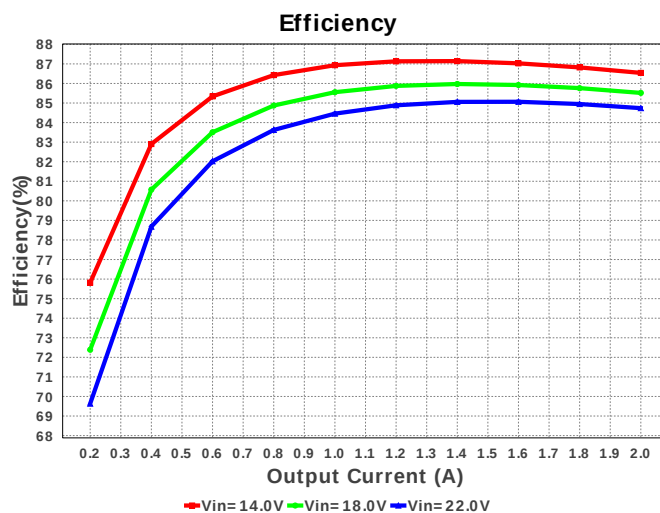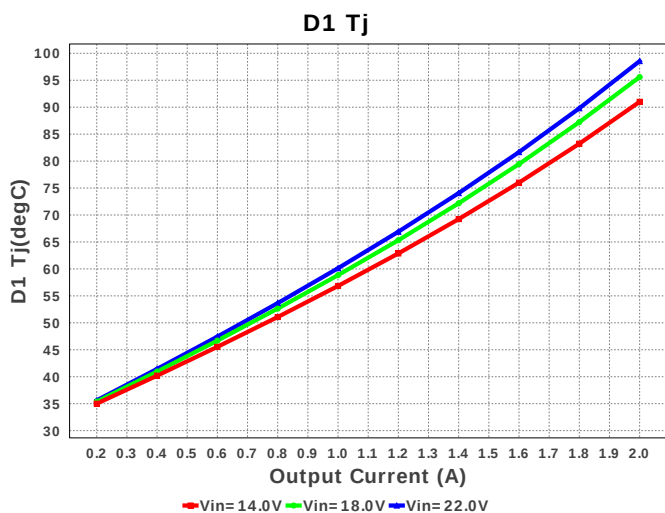

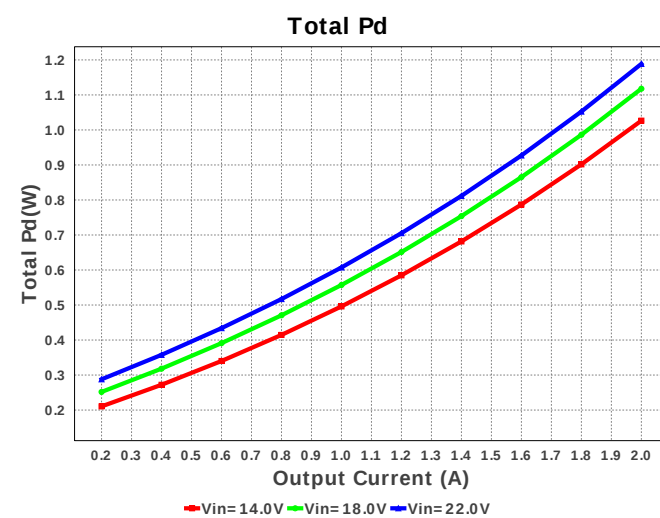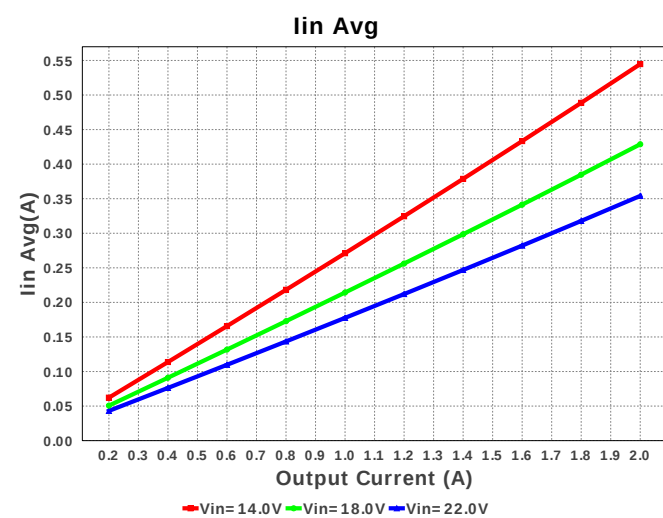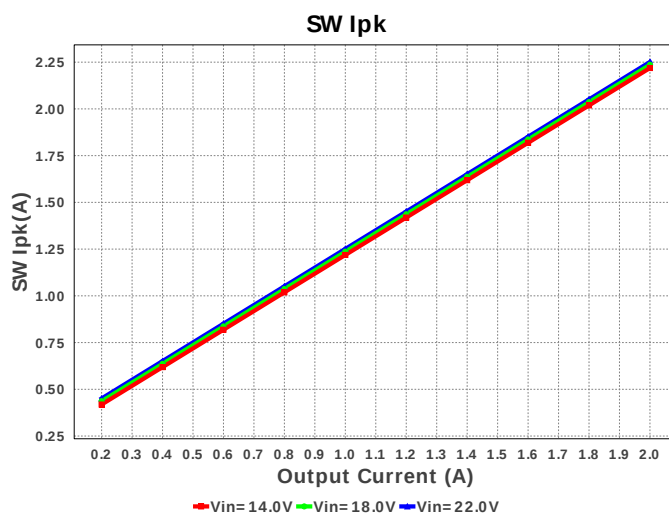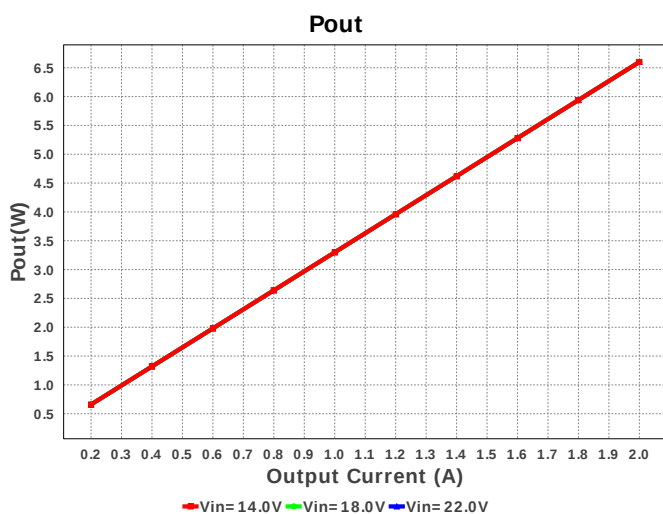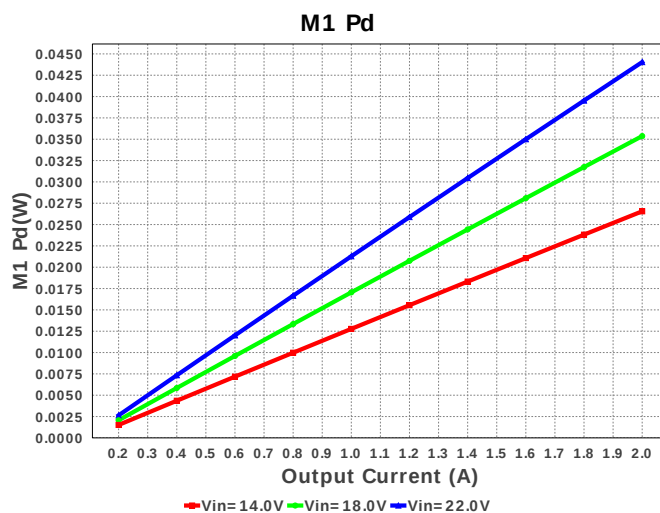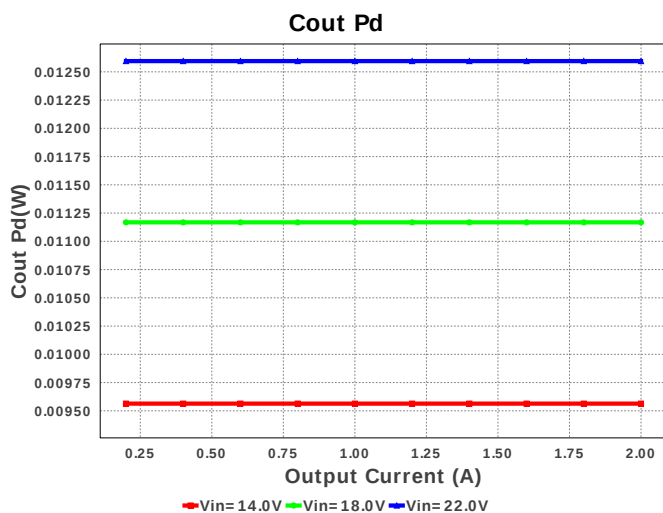

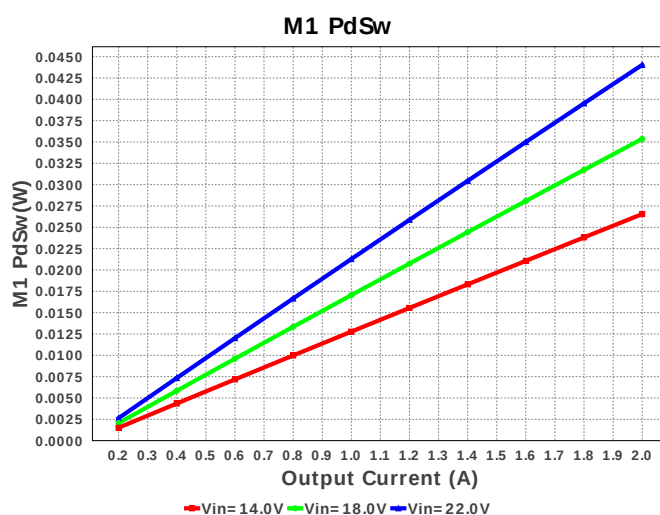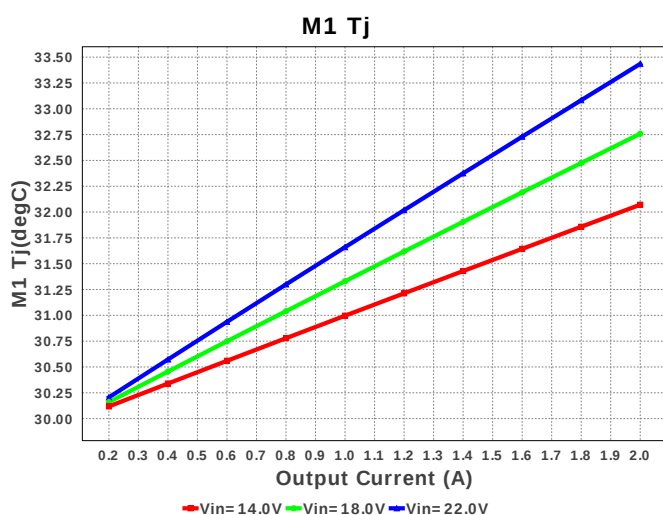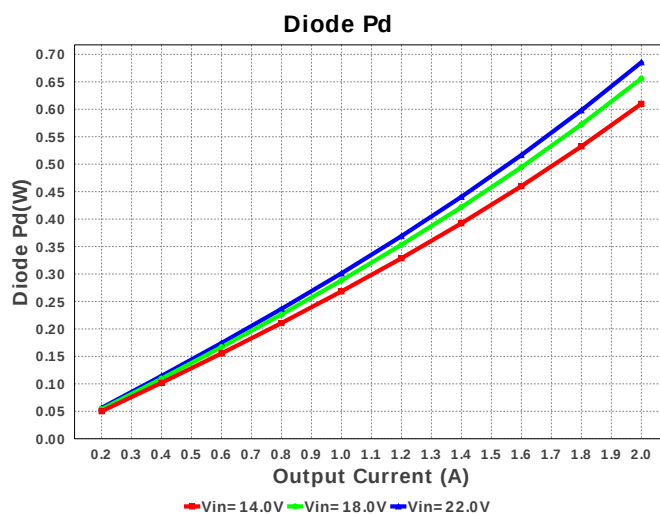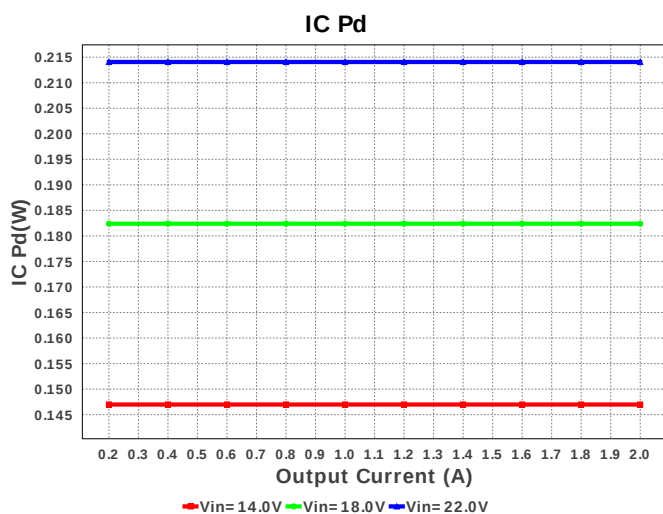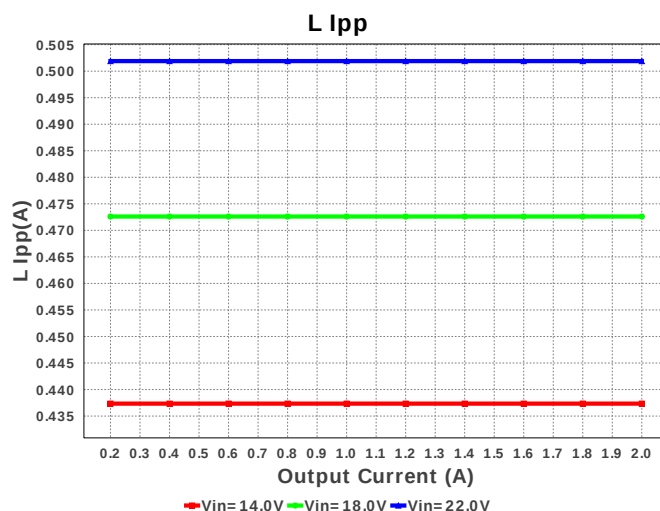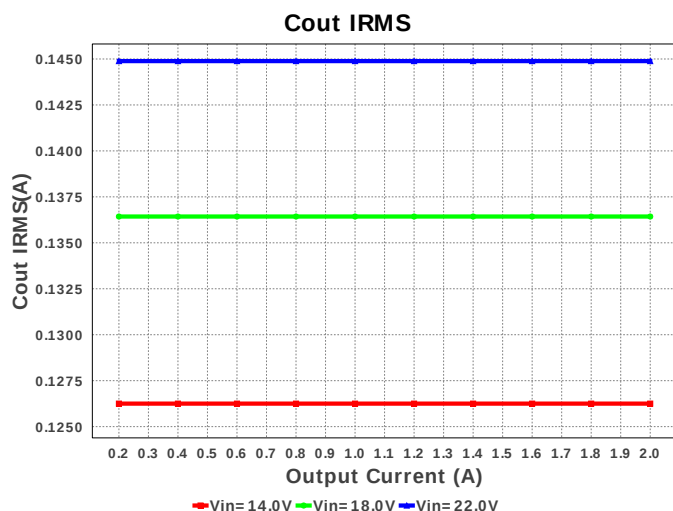

## Operating Values

| #   | Name         | Value                 | Category | Description                             |
|-----|--------------|-----------------------|----------|-----------------------------------------|
| 1.  | Cin IRMS     | 743.406 mA            | Current  | Input capacitor RMS ripple current      |
| 2.  | Cout IRMS    | 144.885 mA            | Current  | Output capacitor RMS ripple current     |
| 3.  | Iin Avg      | 354.03 mA             | Current  | Average input current                   |
| 4.  | L Ipp        | 501.9 mA              | Current  | Peak-to-peak inductor ripple current    |
| 5.  | SW Ipk       | 2.251 A               | Current  | Peak switch current                     |
| 6.  | BOM Count    | 14                    | General  | Total Design BOM count                  |
| 7.  | FootPrint    | 254.0 mm <sup>2</sup> | General  | Total Foot Print Area of BOM components |
| 8.  | Frequency    | 471.114 kHz           | General  | Switching frequency                     |
| 9.  | IC Tolerance | 25.0 mV               | General  | IC Feedback Tolerance                   |
| 10. | Mode         | CCM                   | General  | Conduction Mode                         |
| 11. | Pout         | 6.6 W                 | General  | Total output power                      |

| #   | Name           | Value       | Category | Description                                                                                |
|-----|----------------|-------------|----------|--------------------------------------------------------------------------------------------|
| 12. | Total BOM      | \$1.77      | General  | Total BOM Cost                                                                             |
| 13. | D1 Tj          | 98.552 degC | Op_Point | D1 junction temperature                                                                    |
| 14. | Vout Actual    | 3.292 V     | Op_Point | Vout Actual calculated based on selected voltage divider resistors                         |
| 15. | Vout OP        | 3.3 V       | Op_Point | Operational Output Voltage                                                                 |
| 16. | Duty Cycle     | 16.558 %    | Op_point | Duty cycle                                                                                 |
| 17. | Efficiency     | 84.738 %    | Op_point | Steady state efficiency                                                                    |
| 18. | IC Tj          | 39.847 degC | Op_point | IC junction temperature                                                                    |
| 19. | ICThetaJA      | 46.0 degC/W | Op_point | IC junction-to-ambient thermal resistance                                                  |
| 20. | IOUT_OP        | 2.0 A       | Op_point | Iout operating point                                                                       |
| 21. | M1 Tj          | 33.435 degC | Op_point | M1 MOSFET junction temperature                                                             |
| 22. | VIN_OP         | 22.0 V      | Op_point | Vin operating point                                                                        |
| 23. | Vout p-p       | 301.165 mV  | Op_point | Peak-to-peak output ripple voltage                                                         |
| 24. | Cin Pd         | 2.458 mW    | Power    | Input capacitor power dissipation                                                          |
| 25. | Cout Pd        | 12.595 mW   | Power    | Output capacitor power dissipation                                                         |
| 26. | Diode Pd       | 685.519 mW  | Power    | Diode power dissipation                                                                    |
| 27. | IC Pd          | 214.061 mW  | Power    | IC power dissipation                                                                       |
| 28. | L Pd           | 190.0 mW    | Power    | Inductor power dissipation                                                                 |
| 29. | M1 Pd          | 44.037 mW   | Power    | M1 MOSFET total power dissipation                                                          |
| 30. | M1 PdCond      | 0.0 W       | Power    | M1 MOSFET conduction losses                                                                |
| 31. | M1 PdSw        | 44.037 mW   | Power    | M1 MOSFET switching losses                                                                 |
| 32. | Total Pd       | 1.189 W     | Power    | Total Power Dissipation                                                                    |
| 33. | Vout Tolerance | 2.697 %     |          | Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable |

## Design Inputs

| #  | Name    | Value      | Description            |
|----|---------|------------|------------------------|
| 1. | Iout    | 2.0        | Maximum Output Current |
| 2. | VinMax  | 22.0       | Maximum input voltage  |
| 3. | VinMin  | 14.0       | Minimum input voltage  |
| 4. | Vout    | 3.3        | Output Voltage         |
| 5. | base_pn | LM25085-Q1 | Base Product Number    |
| 6. | source  | DC         | Input Source Type      |
| 7. | Ta      | 30.0       | Ambient temperature    |

## Design Assistance

1. For a Constant On Time device to be stable, we need to provide a ripple at the feedback comparator. There are various methods to implement the ripple. Depending on the circuit complexity vs. the allowable ripple, we have three options to choose from. The simplest option, 'Low Complexity', would require only a high ESR cap at the output. This means that the BOM count will be small, but the output voltage ripple will be quite large. The 'optimal solution' would require a feed-forward cap in parallel with the upper feedback resistor to AC couple the ripple to the feedback node. This increases the BOM count slightly, but now we have more control over the output voltage ripple. If the output voltage requirement is very tight, then the best option is to go for the 'Low Output Ripple' solution. In this option we can go with very low ESR output caps and have very good control over the output voltage ripple

2. Feature Highlights: Automotive Qualified 75V Wide Vin Constant On-Time PFET Buck Switching Controller

3. The LM25085-Q1 is qualified for Automotive applications. All passives and other components selected in this design may not be qualified for Automotive applications. The user is required to verify that all components in the design meet the qualification and safety requirements for their specific application

4. **LM25085-Q1 Product Folder** : <http://www.ti.com/product/LM25085%2DQ1> : contains the data sheet and other resources.

Texas Instruments' WEBENCH simulation tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Simulations are created using Texas Instruments' published specifications as well as the published specifications of other device manufacturers. While Texas Instruments does update this information periodically, this information may not be current at the time the simulation is built. Texas Instruments does not warrant the accuracy or completeness of the specifications or any information contained therein. Texas Instruments does not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. Texas Instruments does not warrant that the designs are production worthy.

**You should completely validate and test your design implementation to confirm the system functionality for your application prior to production.**

Use of Texas Instruments' WEBENCH simulation tools is subject to [Texas Instruments' Site Terms and Conditions of Use](#). Prototype boards based on WEBENCH created designs are provided AS IS without warranty of any kind for evaluation and testing purposes and are subject to the terms of the [Evaluation License Agreement](#).