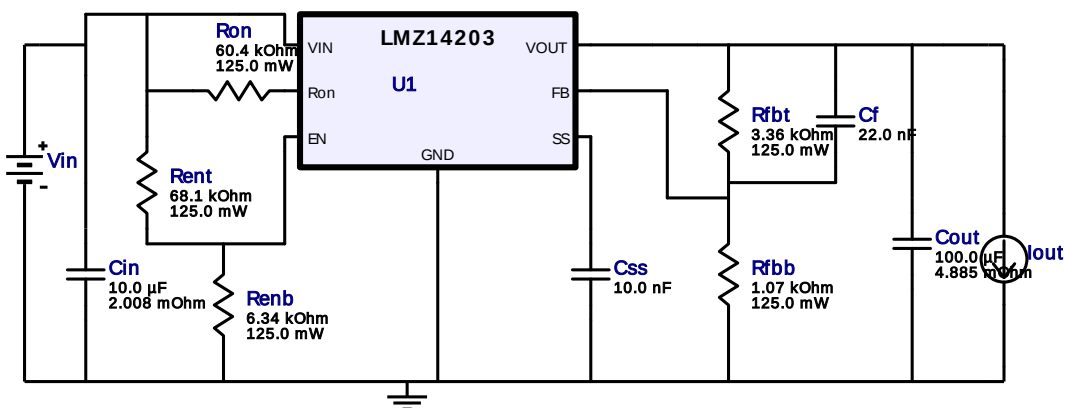


WEBENCH® Design Report

Design : 4770440/2 LMZ14203TZ-ADJ/NOPB
LMZ14203TZ-ADJ/NOPB 14.0V-25.0V to 3.30V @ 2.0A





Vout = 3.3V
Iout = 2.0A















Electrical BOM

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	Cf	Yageo America	CC0805KRX7R9BB223 Series= X7R	Cap= 22.0 nF VDC= 50.0 V IRMS= 0.0 A	1	\$0.01	0805 7 mm ²
2.	Cin	MuRata	GRM32ER7YA106KA12L Series= X7R	Cap= 10.0 uF ESR= 2.008 mOhm VDC= 35.0 V IRMS= 4.6772 A	1	\$0.22	1210_280 15 mm ²
3.	Cout	MuRata	GRM31CR60J107ME39L Series= X5R	Cap= 100.0 uF ESR= 4.885 mOhm VDC= 6.3 V IRMS= 4.4118 A	1	\$0.14	1206_190 11 mm ²
4.	Css	MuRata	GRM216R71H103KA01D Series= X7R	Cap= 10.0 nF VDC= 50.0 V IRMS= 0.0 A	1	\$0.01	0805 7 mm ²
5.	Renb	Panasonic	ERJ-6ENF6341V Series= ERJ-6E	Res= 6.34 kOhm Power= 125.0 mW Tolerance= 1.0%	1	\$0.01	0805 7 mm ²
6.	Rent	Panasonic	ERJ-6ENF6812V Series= ERJ-6E	Res= 68.1 kOhm Power= 125.0 mW Tolerance= 1.0%	1	\$0.01	0805 7 mm ²
7.	Rfbb	Panasonic	ERJ-6ENF1071V Series= ERJ-6E	Res= 1.07 kOhm Power= 125.0 mW Tolerance= 1.0%	1	\$0.01	0805 7 mm ²
8.	Rfbt	Yageo America	RT0805BRD073K36L Series= RT0805	Res= 3.36 kOhm Power= 125.0 mW Tolerance= 0.1%	1	\$0.05	0805 7 mm ²
9.	Ron	Panasonic	ERJ-6ENF6042V Series= ERJ-6E	Res= 60.4 kOhm Power= 125.0 mW Tolerance= 1.0%	1	\$0.01	0805 7 mm ²

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
10.	U1	Texas Instruments	LMZ14203TZ-ADJ/NOPB	Switcher	1	\$9.78	 TZA07A 199 mm ²

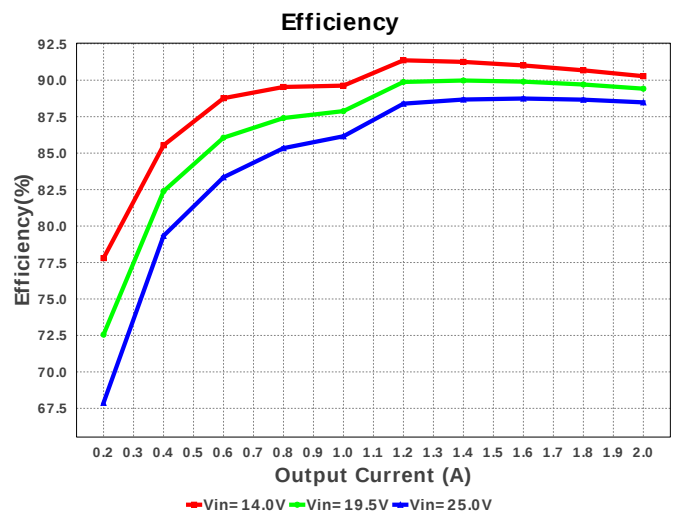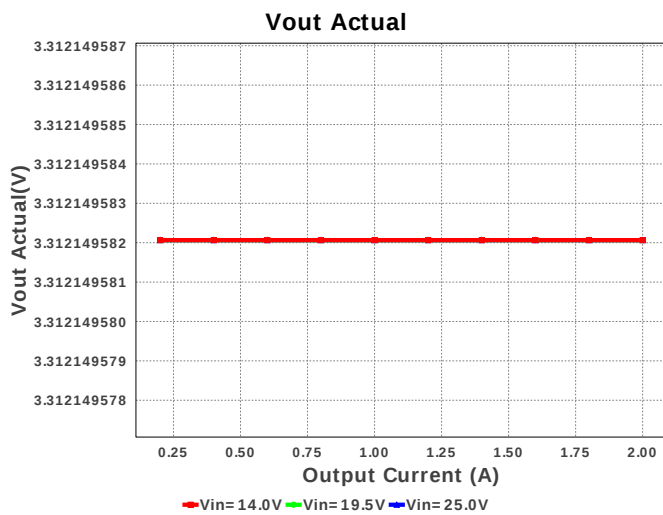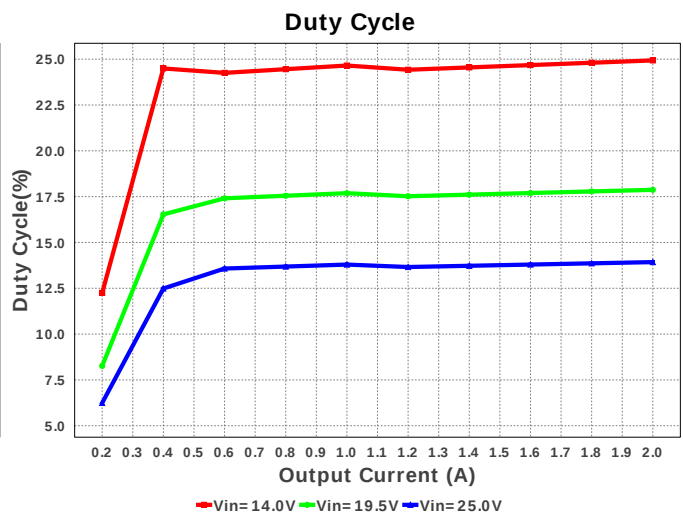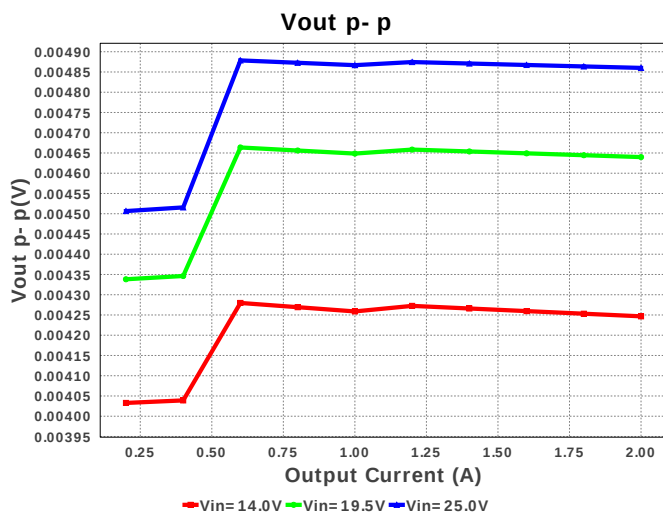

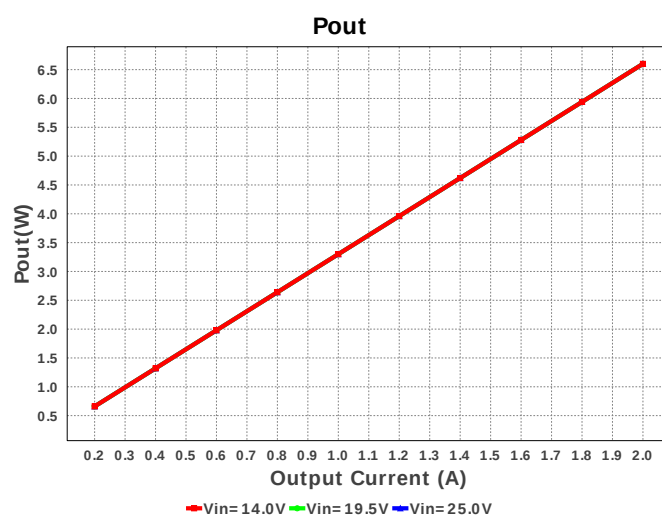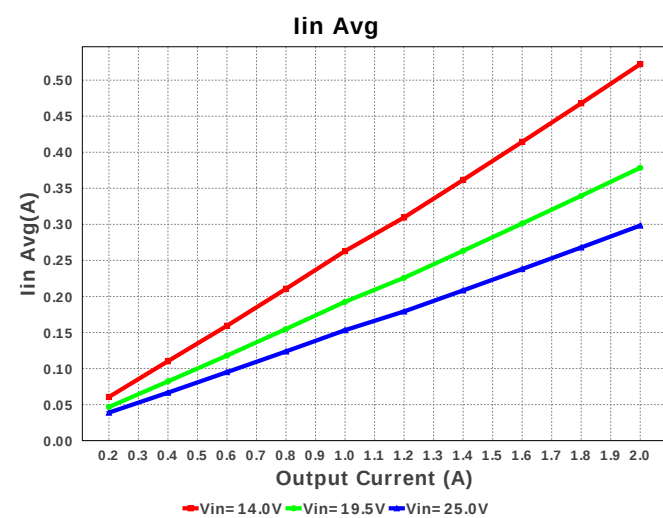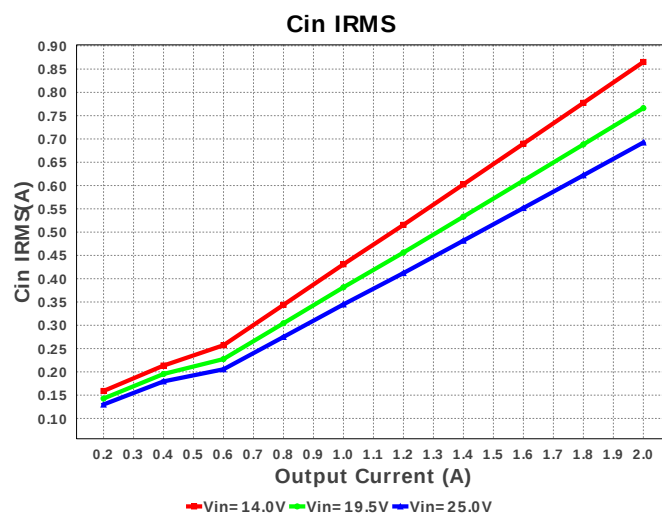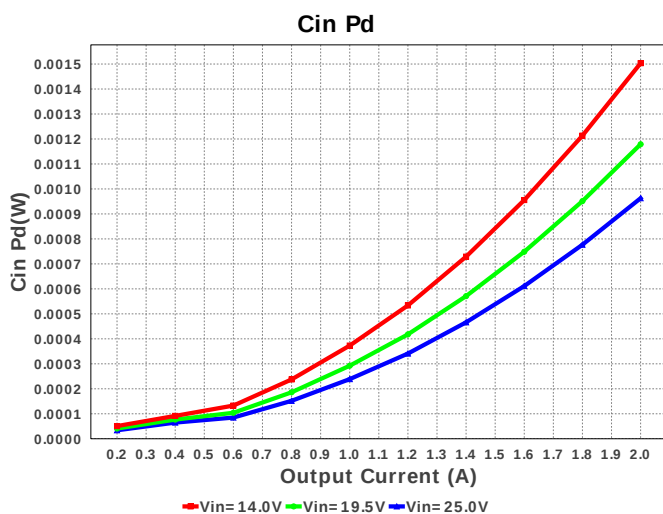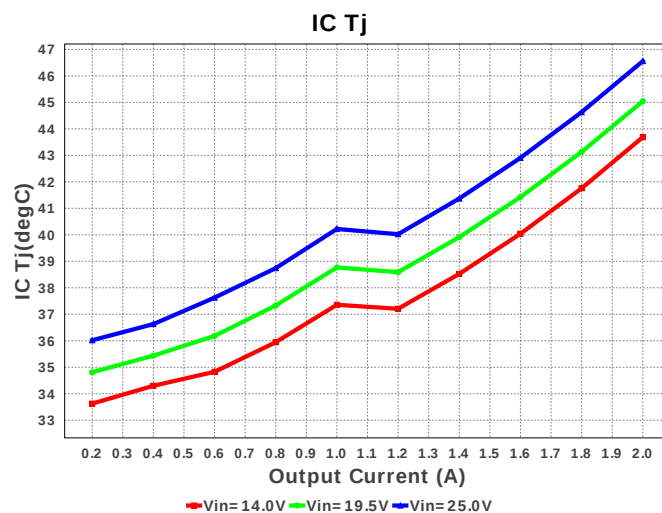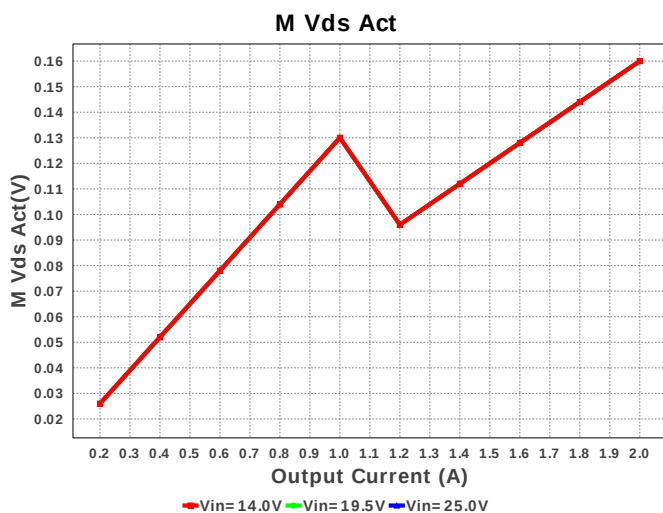

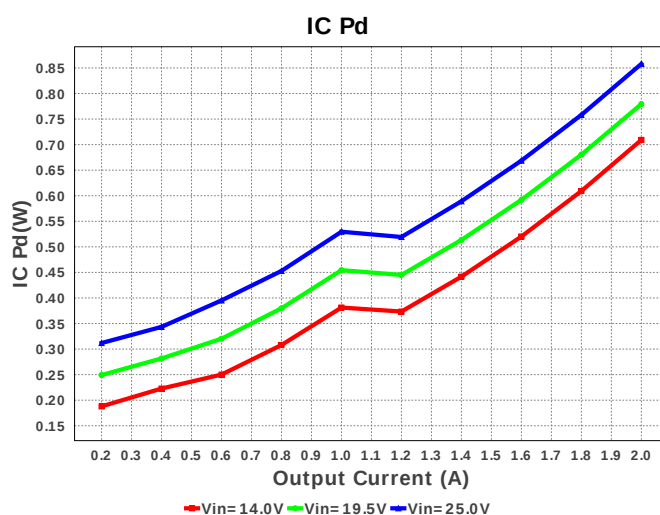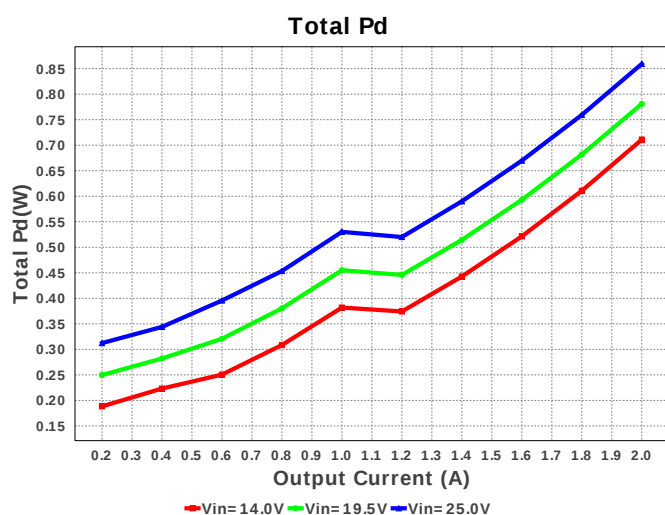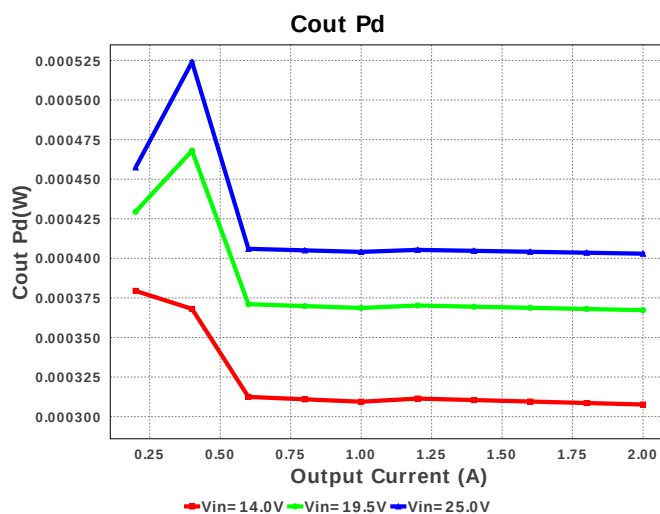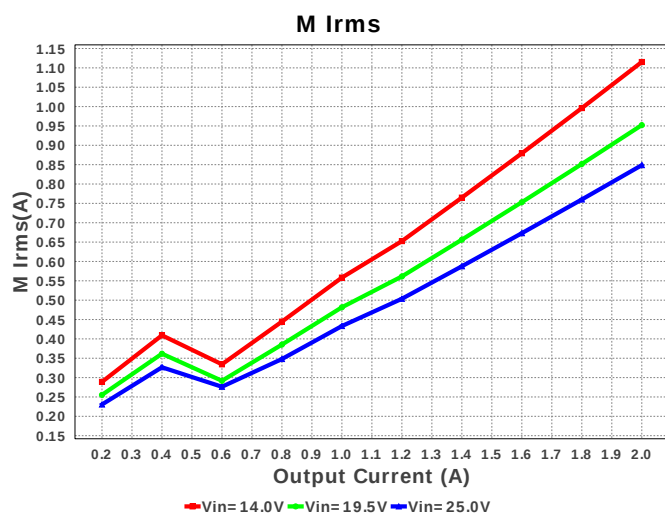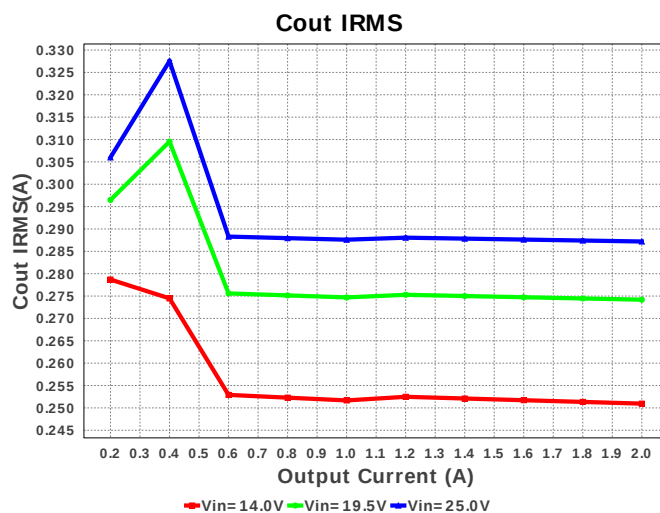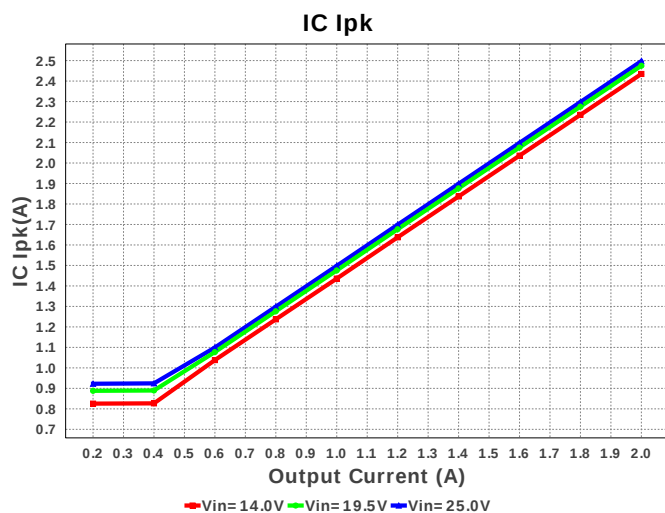

Operating Values

#	Name	Value	Category	Description
1.	Cin IRMS	692.469 mA	Current	Input capacitor RMS ripple current
2.	Cout IRMS	287.201 mA	Current	Output capacitor RMS ripple current
3.	IC Ipk	2.497 A	Current	Peak switch current in IC
4.	Iin Avg	294.79 mA	Current	Average input current
5.	M1 Irms	839.089 mA	Current	Q lavg
6.	BOM Count	10	General	Total Design BOM count
7.	FootPrint	272.0 mm ²	General	Total Foot Print Area of BOM components
8.	Frequency	420.275 kHz	General	Switching frequency
9.	IC Tolerance	20.0 mV	General	IC Feedback Tolerance
10.	M Vds Act	160.0 mV	General	Voltage drop across the MosFET
11.	Mode	CCM	General	Conduction Mode

#	Name	Value	Category	Description
12.	Pout	6.6 W	General	Total output power
13.	Total BOM	\$10.25	General	Total BOM Cost
14.	Vout Actual	3.312 V	Op_Point	Vout Actual calculated based on selected voltage divider resistors
15.	Vout OP	3.3 V	Op_Point	Operational Output Voltage
16.	Duty Cycle	13.928 %	Op_point	Duty cycle
17.	Efficiency	89.556 %	Op_point	Steady state efficiency
18.	IC Tj	44.829 degC	Op_point	IC junction temperature
19.	ICThetaJA	19.3 degC/W	Op_point	IC junction-to-ambient thermal resistance
20.	IOUT_OP	2.0 A	Op_point	Iout operating point
21.	VIN_OP	25.0 V	Op_point	Vin operating point
22.	Vout p-p	4.86 mV	Op_point	Peak-to-peak output ripple voltage
23.	Cin Pd	962.862 μ W	Power	Input capacitor power dissipation
24.	Cout Pd	402.937 μ W	Power	Output capacitor power dissipation
25.	IC Pd	768.354 mW	Power	IC power dissipation
26.	Total Pd	769.697 mW	Power	Total Power Dissipation
27.	Vout Tolerance	3.364 %		Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable

Design Inputs

#	Name	Value	Description
1.	Iout	2.0	Maximum Output Current
2.	VinMax	25.0	Maximum input voltage
3.	VinMin	14.0	Minimum input voltage
4.	Vout	3.3	Output Voltage
5.	base_pn	LMZ14203	Base Product Number
6.	source	DC	Input Source Type
7.	Ta	30.0	Ambient temperature

Design Assistance

1. **LMZ14203** Product Folder : <http://www.ti.com/product/LMZ14203> : contains the data sheet and other resources.

Texas Instruments' WEBENCH simulation tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Simulations are created using Texas Instruments' published specifications as well as the published specifications of other device manufacturers. While Texas Instruments does update this information periodically, this information may not be current at the time the simulation is built. Texas Instruments does not warrant the accuracy or completeness of the specifications or any information contained therein. Texas Instruments does not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. Texas Instruments does not warrant that the designs are production worthy.

You should completely validate and test your design implementation to confirm the system functionality for your application prior to production.

Use of Texas Instruments' WEBENCH simulation tools is subject to [Texas Instruments' Site Terms and Conditions of Use](#). Prototype boards based on WEBENCH created designs are provided AS IS without warranty of any kind for evaluation and testing purposes and are subject to the terms of the [Evaluation License Agreement](#).