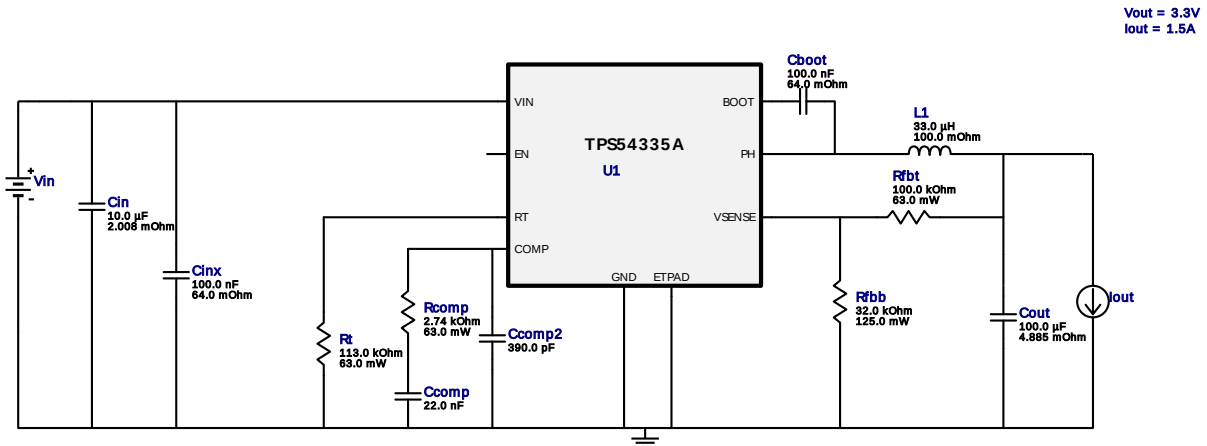
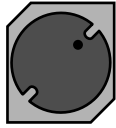







WEBENCH® Design Report







Design : 4774498/24 TPS54335ADDAR
TPS54335ADDAR 20.0V-28.0V to 3.30V @ 1.5A

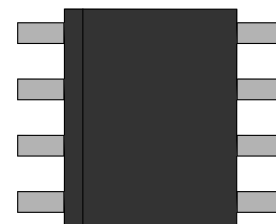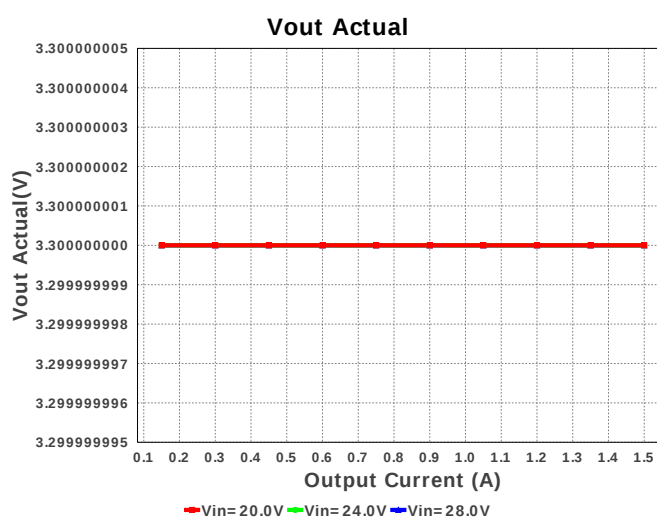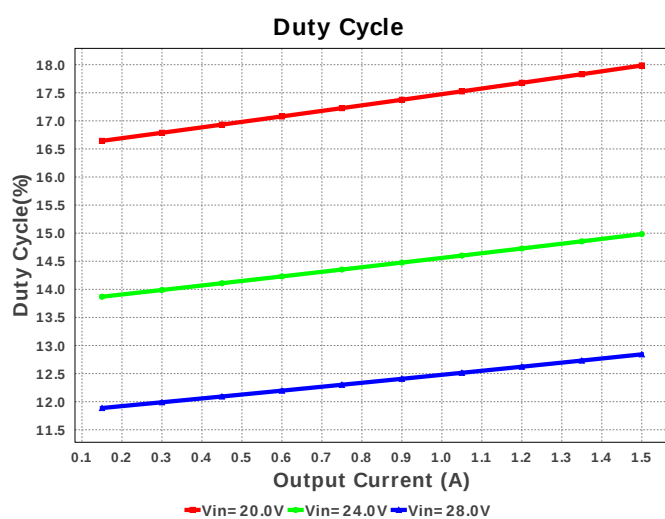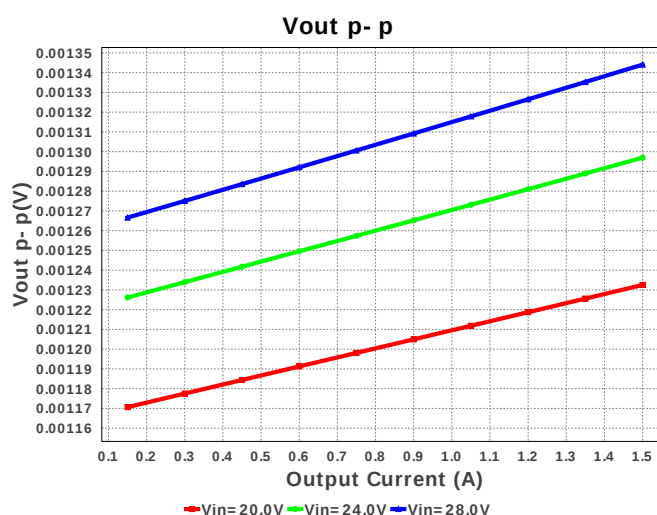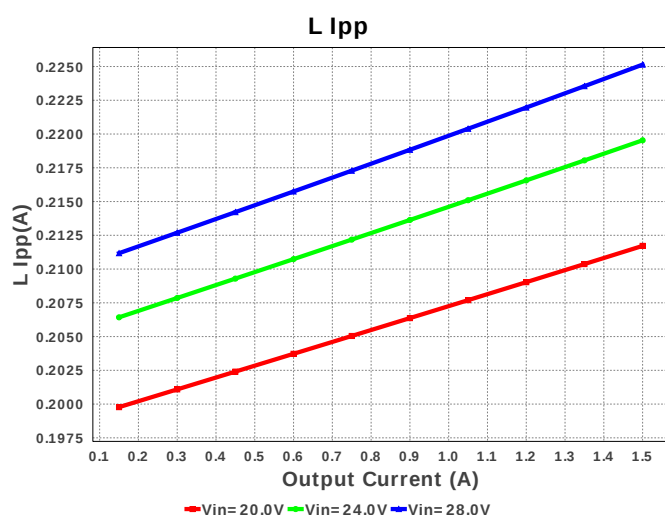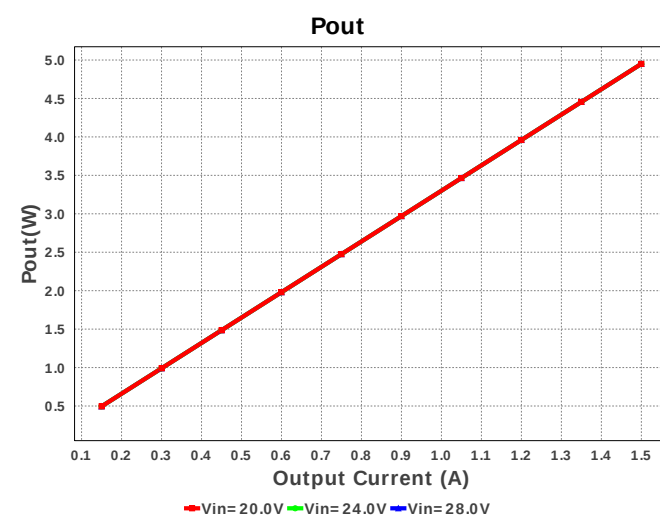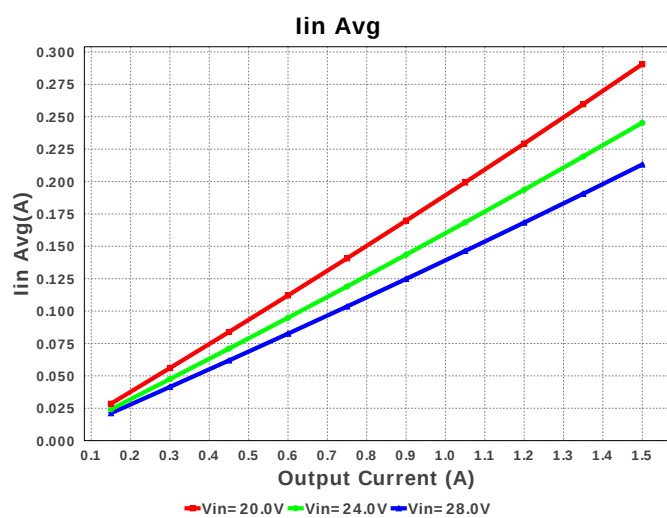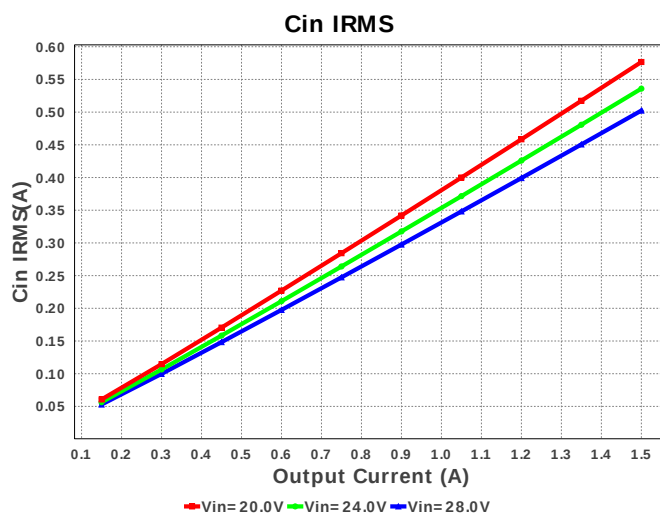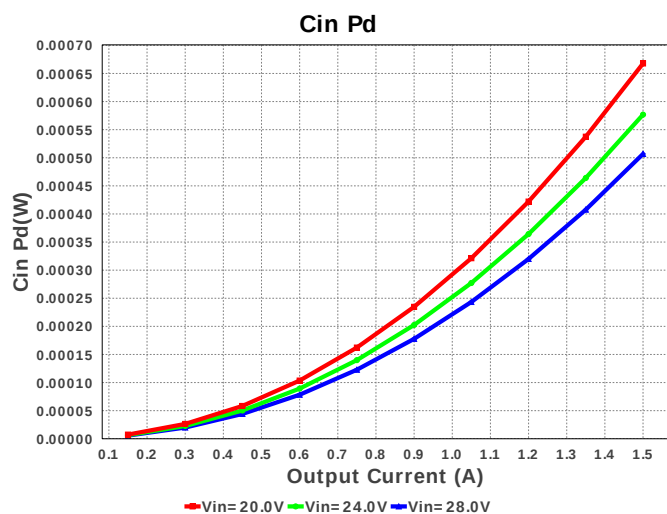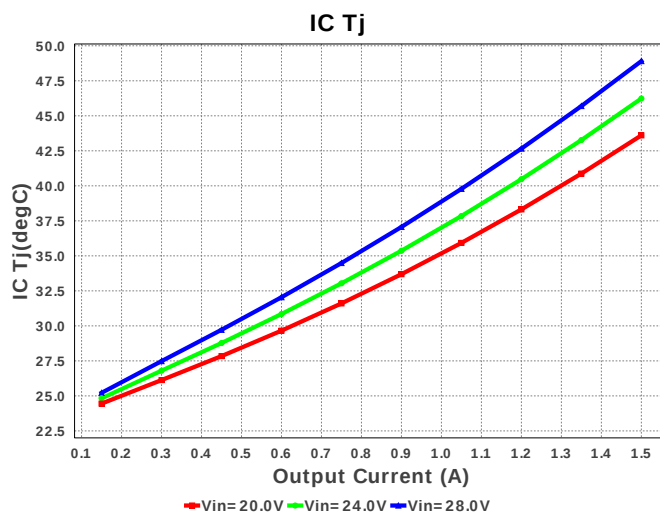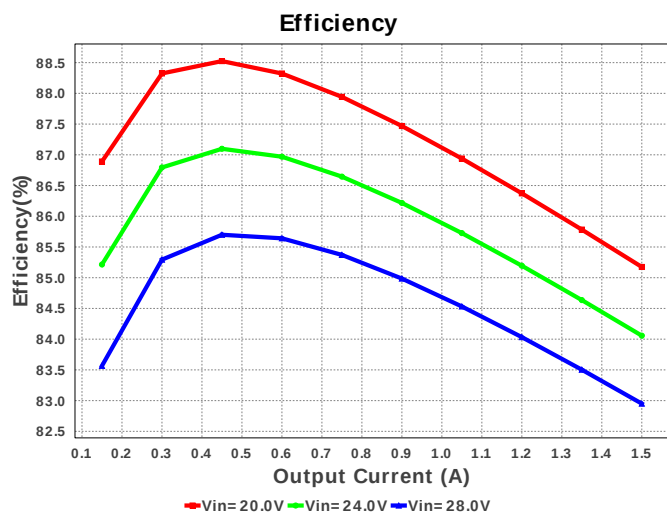
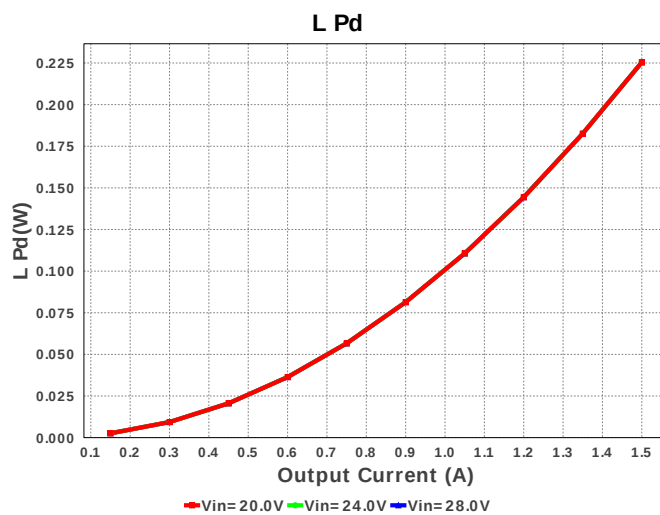
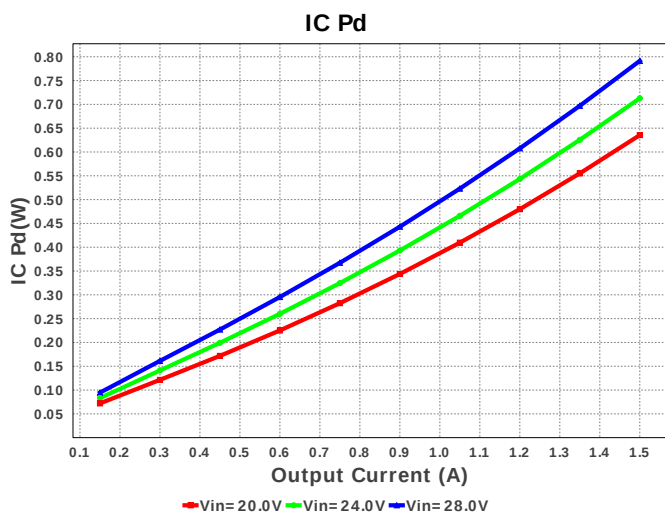
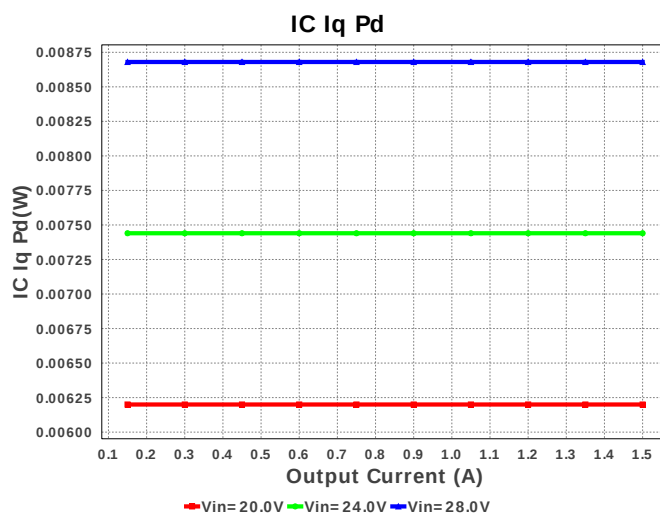
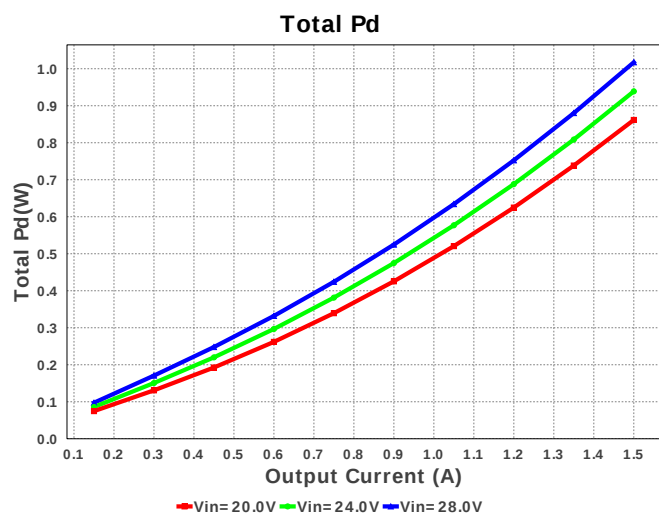
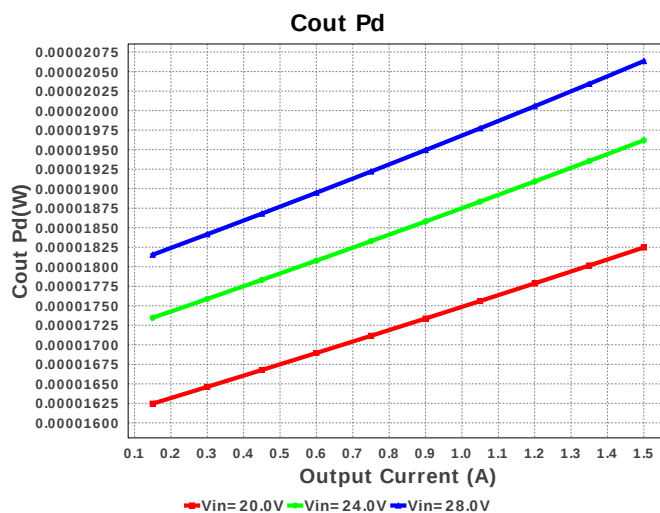
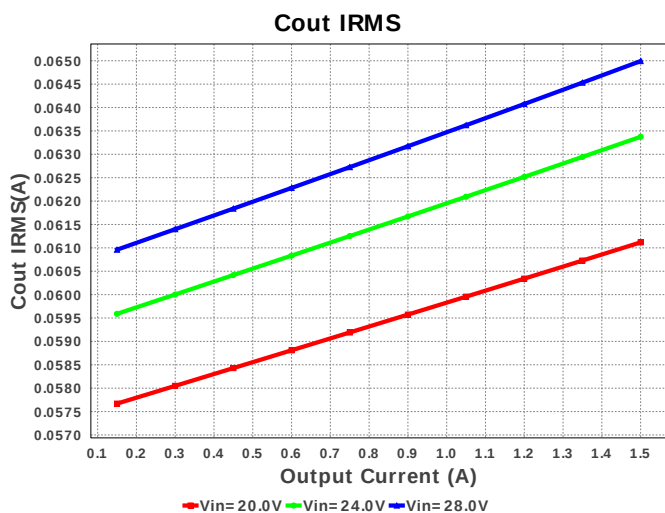
Electrical BOM


#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	Cboot	Kemet	C0805C104K5RACTU Series= X7R	Cap= 100.0 nF ESR= 64.0 mOhm VDC= 50.0 V IRMS= 1.64 A	1	\$0.01	0805 7 mm ²
2.	Ccomp	Yageo America	CC0805KRX7R9BB223 Series= X7R	Cap= 22.0 nF VDC= 50.0 V IRMS= 0.0 A	1	\$0.01	0805 7 mm ²
3.	Ccomp2	Yageo America	CC0805KRX7R9BB391 Series= X7R	Cap= 390.0 pF VDC= 50.0 V IRMS= 0.0 A	1	\$0.01	0805 7 mm ²
4.	Cin	MuRata	GRM32ER7YA106KA12L Series= X7R	Cap= 10.0 uF ESR= 2.008 mOhm VDC= 35.0 V IRMS= 4.6772 A	1	\$0.22	1210_280 15 mm ²
5.	Cinx	Kemet	C0805C104K5RACTU Series= X7R	Cap= 100.0 nF ESR= 64.0 mOhm VDC= 50.0 V IRMS= 1.64 A	1	\$0.01	0805 7 mm ²
6.	Cout	MuRata	GRM31CR60J107ME39L Series= X5R	Cap= 100.0 uF ESR= 4.885 mOhm VDC= 6.3 V IRMS= 4.4118 A	1	\$0.14	1206_190 11 mm ²
7.	L1	Bourns	SDR1105-330KL	L= 33.0 uH DCR= 100.0 mOhm	1	\$0.29	 SDR1105 157 mm ²
8.	Rcomp	Vishay-Dale	CRCW04022K74FKED Series= CRCW..e3	Res= 2.74 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²
9.	Rfbb	Yageo America	RT0805BRD0732KL Series= ?	Res= 32.0 kOhm Power= 125.0 mW Tolerance= 0.1%	1	\$0.05	0805 7 mm ²
10.	Rfht	Vishay-Dale	CRCW0402100KFKED Series= CRCW..e3	Res= 100.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
11.	Rt	Vishay-Dale	CRCW0402113KFKED Series= CRCW..e3	Res= 113.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²
12.	U1	Texas Instruments	TPS54335ADDAR	Switcher	1	\$0.90	

R-PDSO-G8 55 mm²





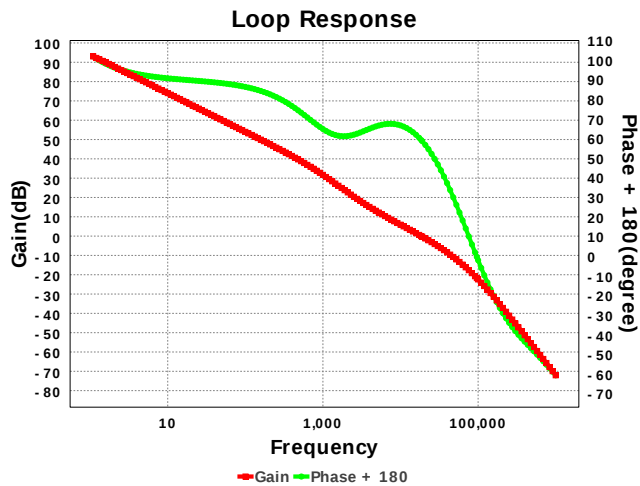

Operating Values

#	Name	Value	Category	Description
1.	Cin IRMS	502.388 mA	Current	Input capacitor RMS ripple current
2.	Cout IRMS	64.993 mA	Current	Output capacitor RMS ripple current
3.	Iin Avg	213.12 mA	Current	Average input current
4.	L Ipp	225.14 mA	Current	Peak-to-peak inductor ripple current
5.	BOM Count	12	General	Total Design BOM count
6.	FootPrint	281.0 mm ²	General	Total Foot Print Area of BOM components
7.	Frequency	420.74 kHz	General	Switching frequency
8.	IC Tolerance	12.0 mV	General	IC Feedback Tolerance
9.	Mode	CCM	General	Conduction Mode
10.	Pout	4.95 W	General	Total output power
11.	Total BOM	\$1.67	General	Total BOM Cost
12.	ICThetaJA Effective	34.0 degC/W	Op_Point	Effective IC Junction-to-Ambient Thermal Resistance
13.	Low Freq Gain	93.02 dB	Op_Point	Gain at 10Hz
14.	Vout Actual	3.3 V	Op_Point	Vout Actual calculated based on selected voltage divider resistors
15.	Vout OP	3.3 V	Op_Point	Operational Output Voltage
16.	Cross Freq	18.502 kHz	Op_point	Bode plot crossover frequency
17.	Duty Cycle	12.843 %	Op_point	Duty cycle
18.	Efficiency	82.951 %	Op_point	Steady state efficiency
19.	Gain Marg	-21.742 dB	Op_point	Bode Plot Gain Margin
20.	IC Tj	48.907 degC	Op_point	IC junction temperature
21.	IOUT_OP	1.5 A	Op_point	Iout operating point
22.	Phase Marg	59.536 deg	Op_point	Bode Plot Phase Margin
23.	VIN_OP	28.0 V	Op_point	Vin operating point
24.	Vout p-p	1.344 mV	Op_point	Peak-to-peak output ripple voltage
25.	Cin Pd	506.807 μ W	Power	Input capacitor power dissipation
26.	Cout Pd	20.634 μ W	Power	Output capacitor power dissipation
27.	IC Iq Pd	8.68 mW	Power	IC Iq Pd
28.	IC Pd	791.371 mW	Power	IC power dissipation
29.	L Pd	225.422 mW	Power	Inductor power dissipation
30.	Total Pd	1.017 W	Power	Total Power Dissipation
31.	Vout Tolerance	2.347 %		Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable

Design Inputs

#	Name	Value	Description
1.	Iout	1.5	Maximum Output Current
2.	VinMax	28.0	Maximum input voltage
3.	VinMin	20.0	Minimum input voltage
4.	Vout	3.3	Output Voltage
5.	base_pn	TPS54335A	Base Product Number
6.	source	DC	Input Source Type
7.	Ta	22.0	Ambient temperature

Design Assistance

1. **TPS54335A** Product Folder : <http://www.ti.com/product/TPS54335A> : contains the data sheet and other resources.

Texas Instruments' WEBENCH simulation tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Simulations are created using Texas Instruments' published specifications as well as the published specifications of other device manufacturers. While Texas Instruments does update this information periodically, this information may not be current at the time the simulation is built. Texas Instruments does not warrant the accuracy or completeness of the specifications or any information contained therein. Texas Instruments does not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. Texas Instruments does not warrant that the designs are production worthy.

You should completely validate and test your design implementation to confirm the system functionality for your application prior to production.

Use of Texas Instruments' WEBENCH simulation tools is subject to [Texas Instruments' Site Terms and Conditions of Use](#). Prototype boards based on WEBENCH created designs are provided AS IS without warranty of any kind for evaluation and testing purposes and are subject to the terms of the [Evaluation License Agreement](#).