


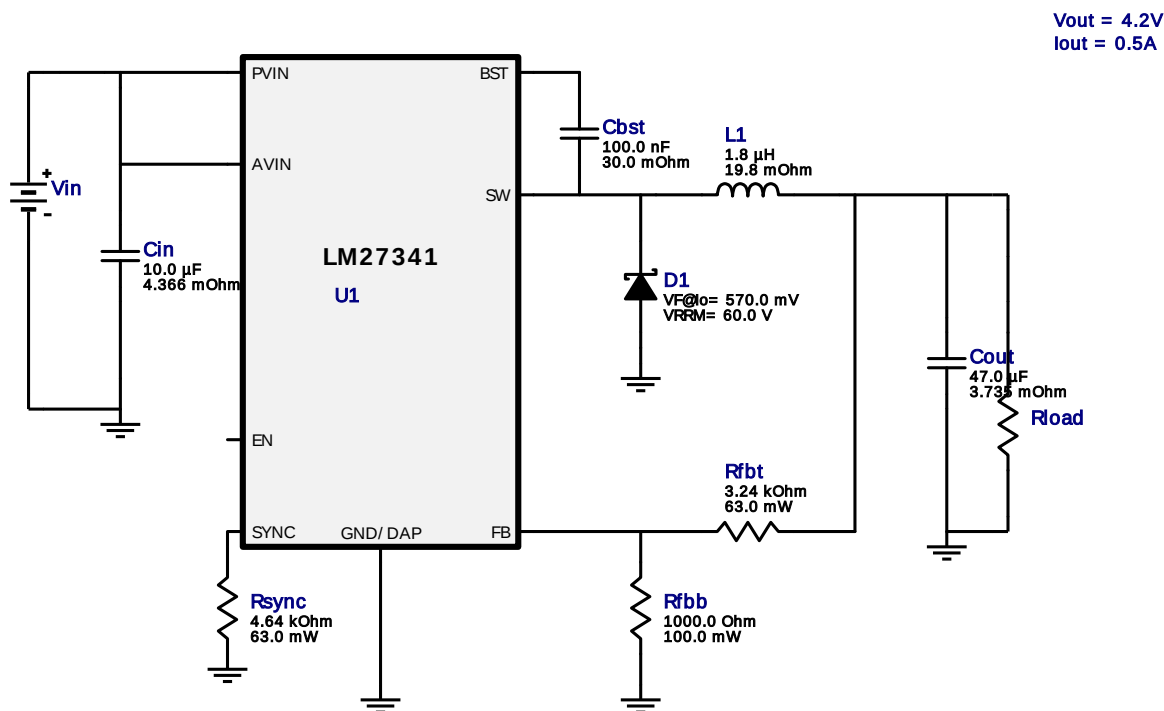
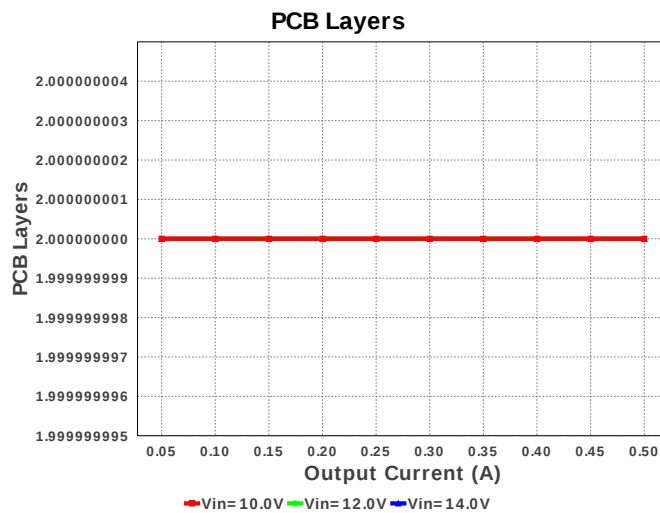







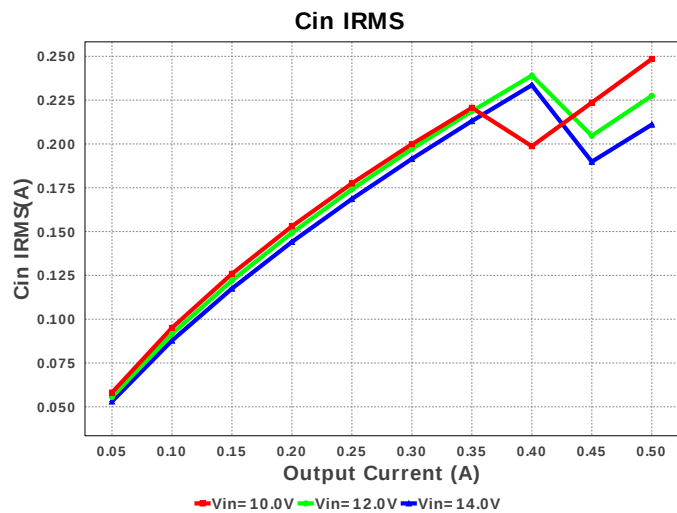







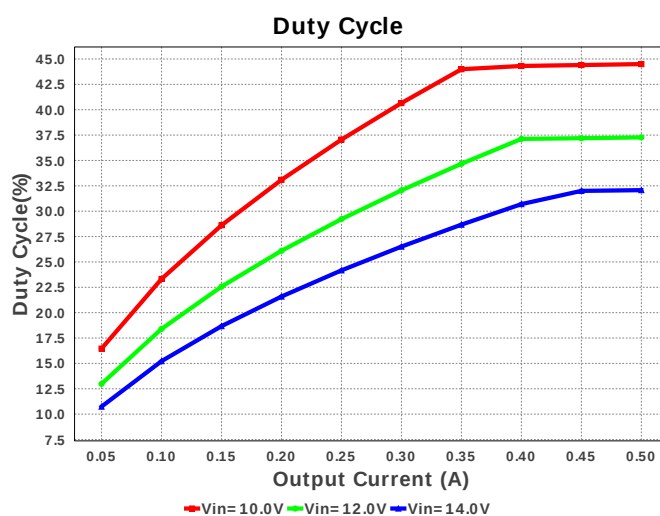
Device = LM27341MY/NOPB
Topology = Buck
Created = 9/4/16 8:00:45 AM
BOM Cost = \$1.49
BOM Count = 9
Total Pd = 0.44W










#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
8.	Rsync	Vishay-Dale	CRCW04024K64FKED Series= CRCW..e3	Res= 4.64 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm²
9.	U1	Texas Instruments	LM27341MY/NOPB	Switcher	1	\$1.10	 MUC10A 24 mm²

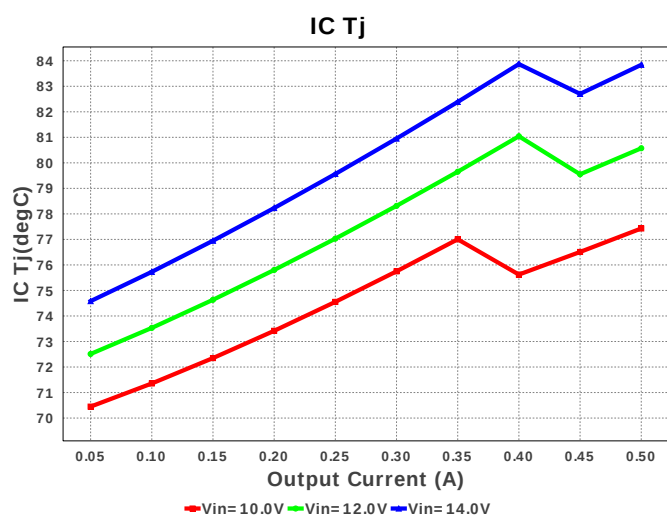

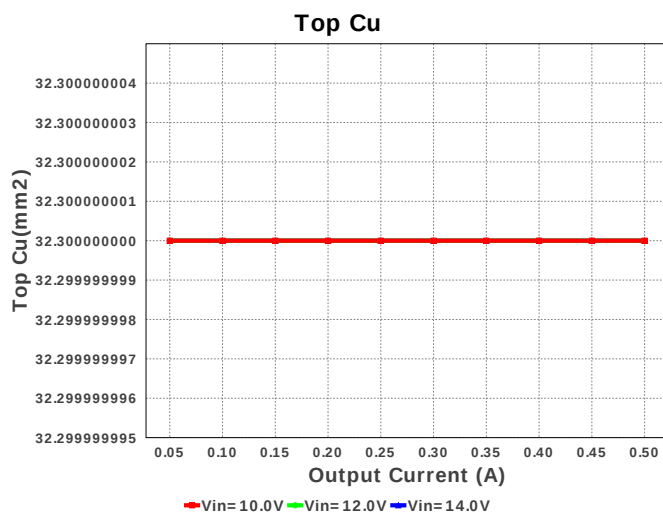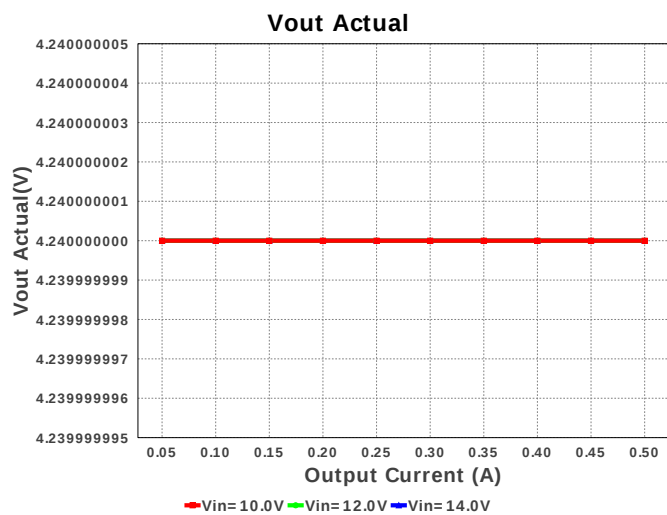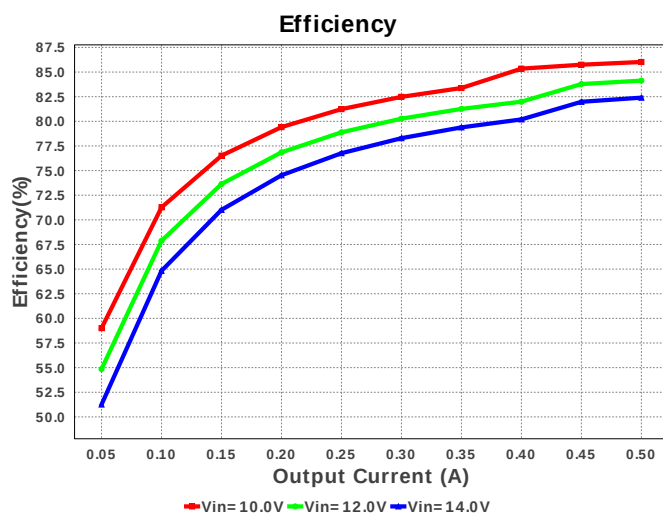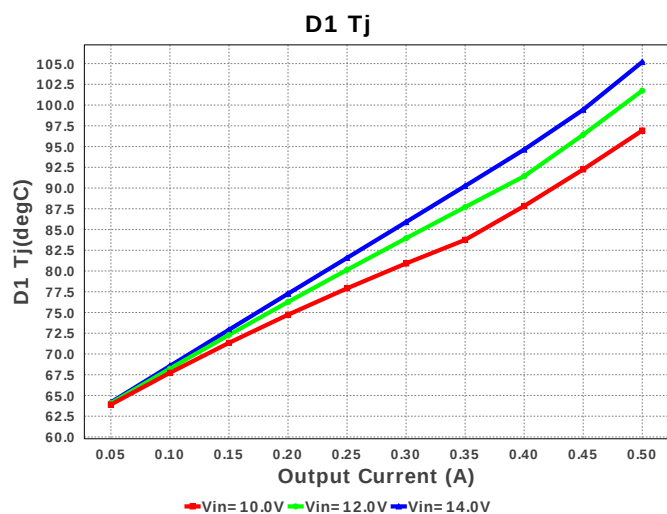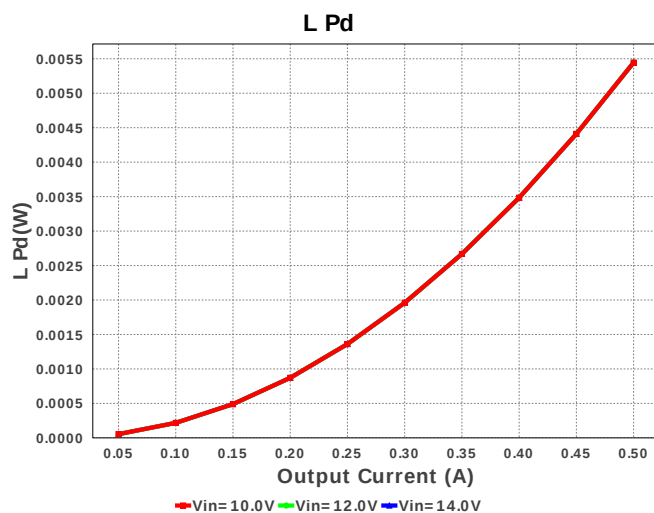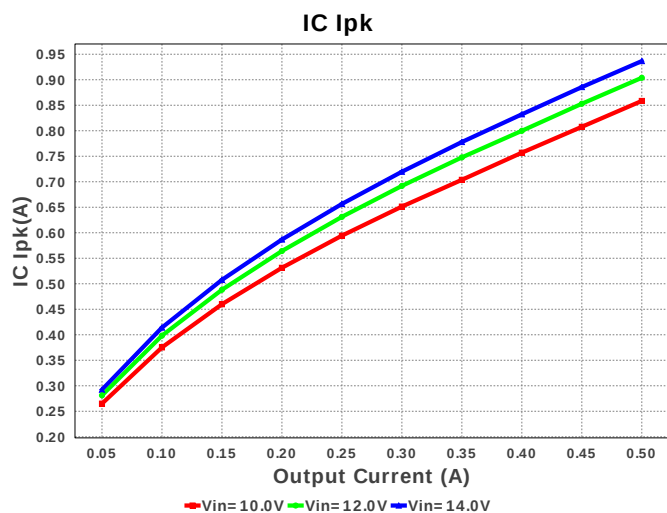

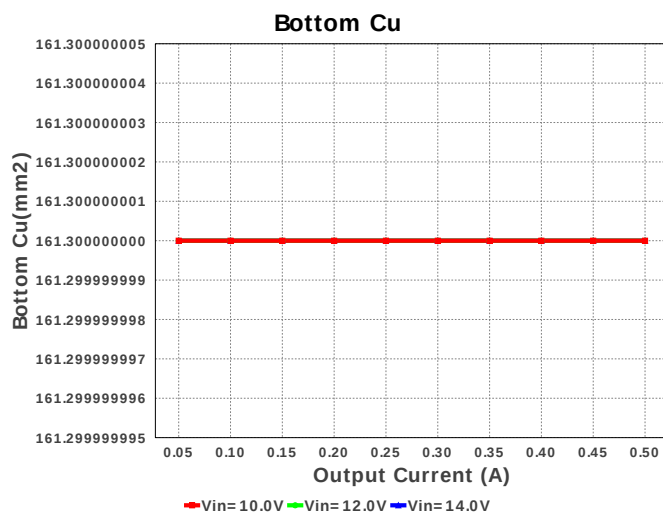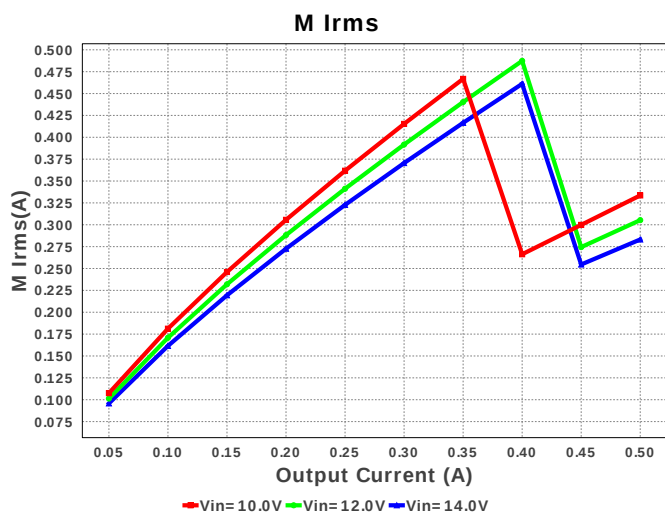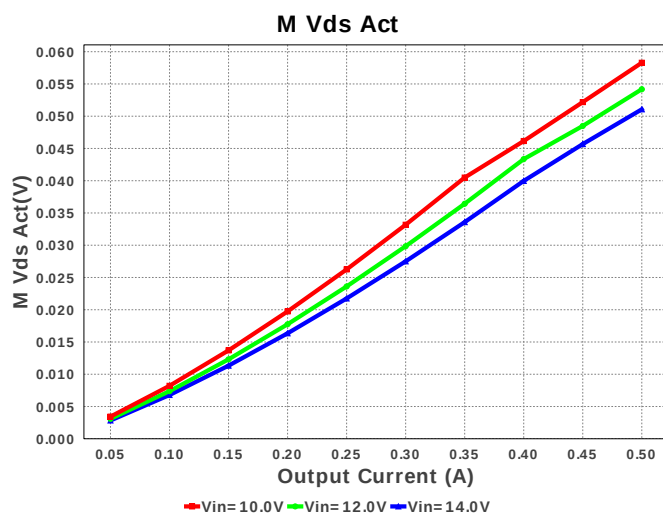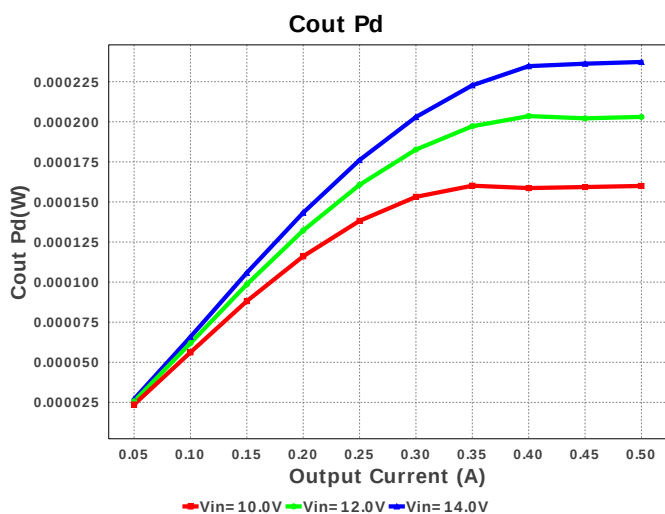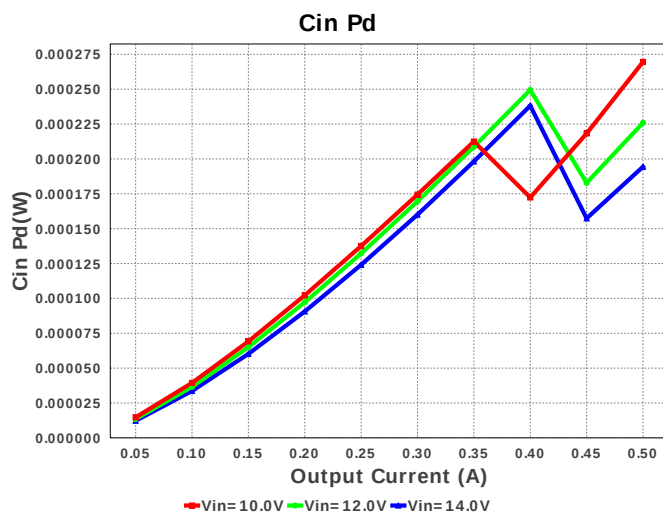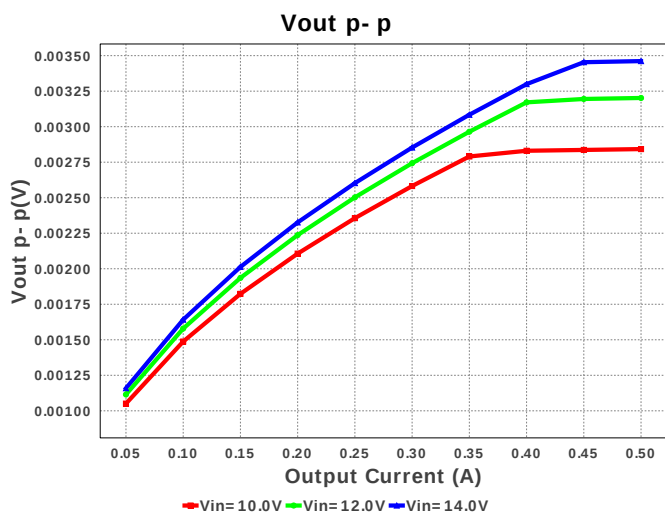

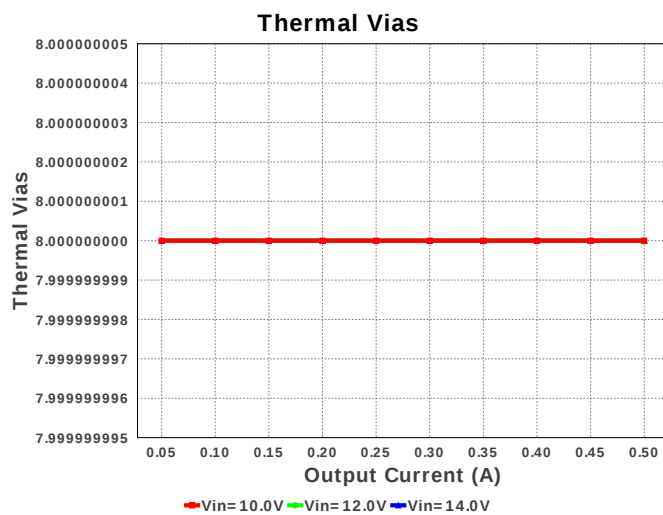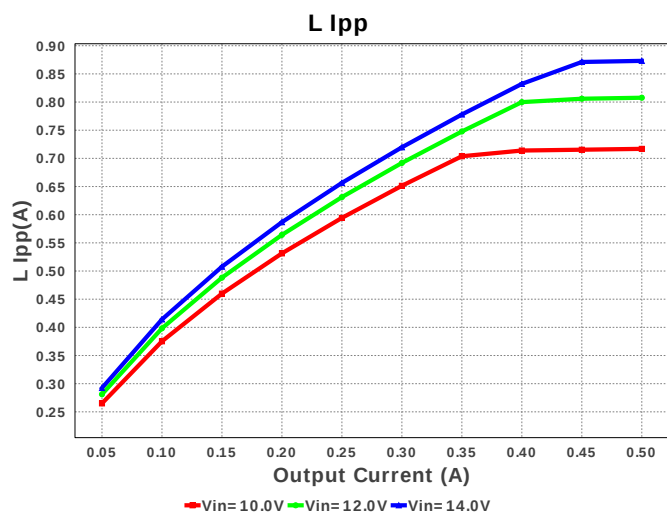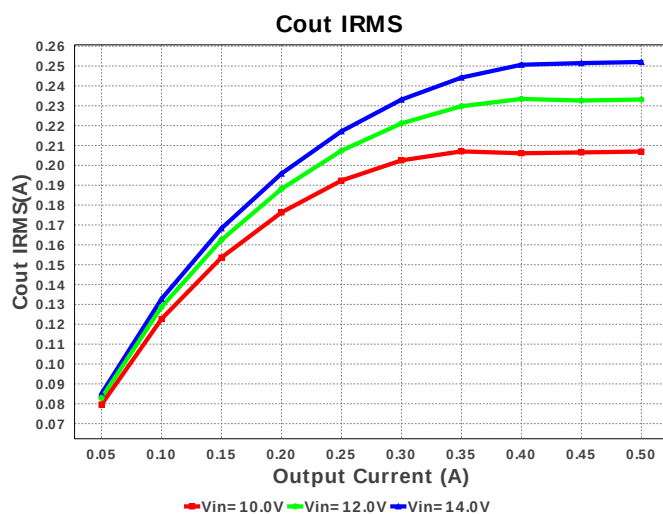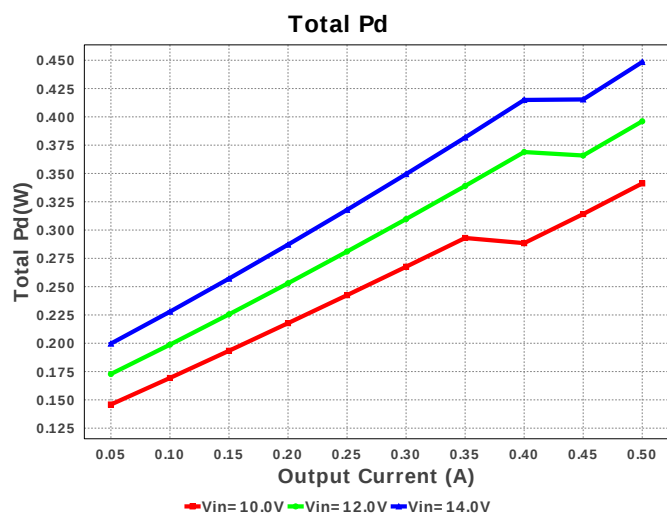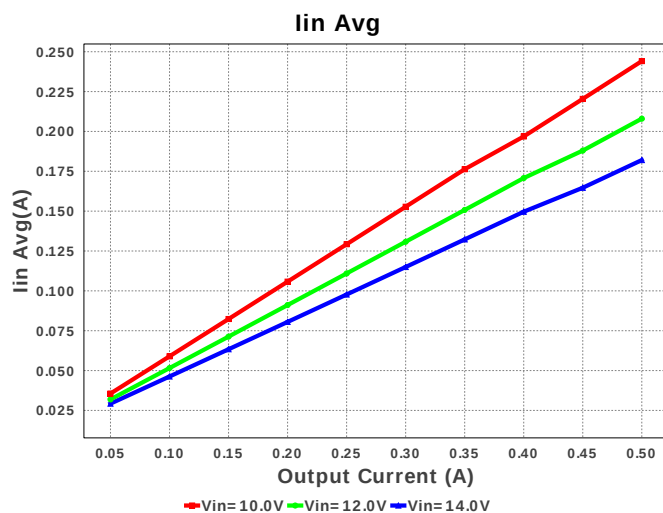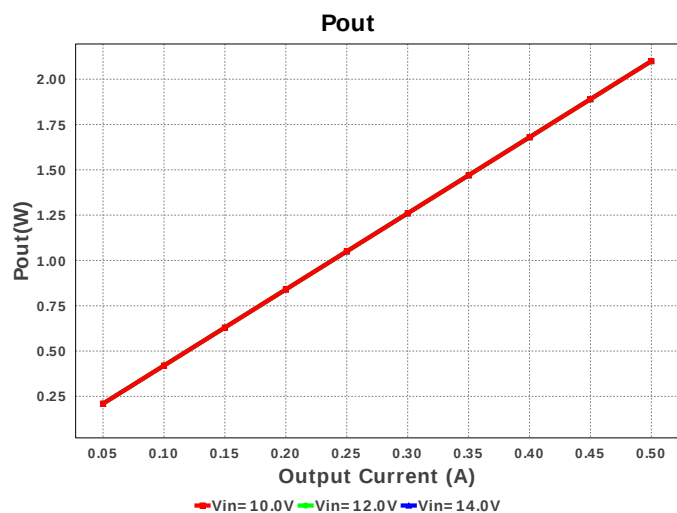

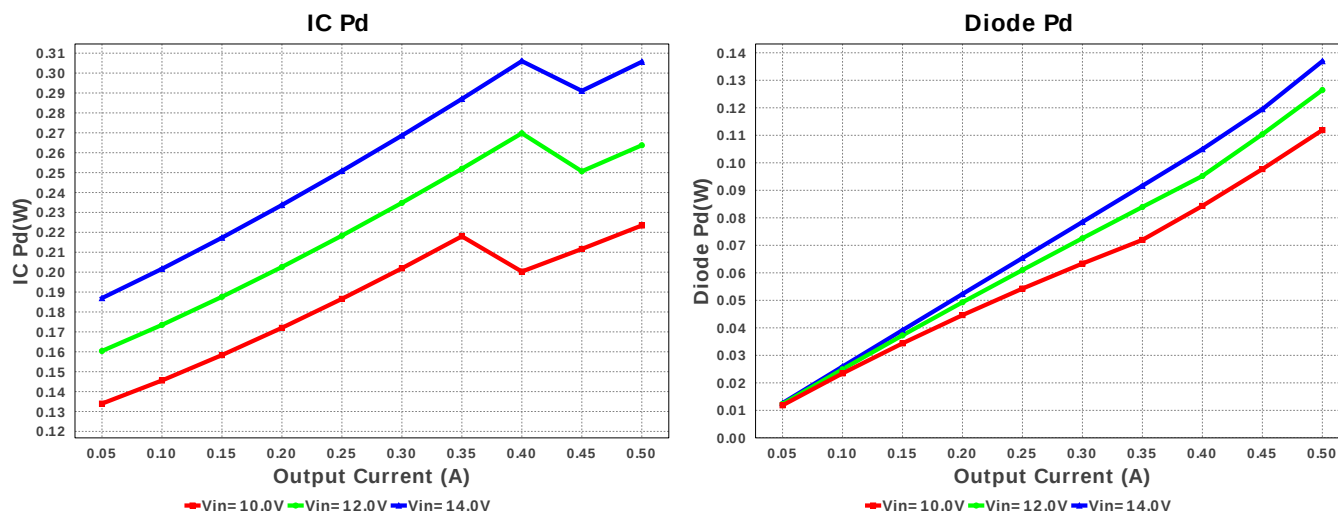

Operating Values

#	Name	Value	Category	Description
1.	Bottom Cu	161.3 mm ²	Board_Layout	Recommended minimum area of bottom layer copper connected to DAP
2.	PCB Layers	2.0	Board_Layout	Recommended number of PCB layers for the necessary IC Thermal Resistance
3.	Thermal Vias	8.0	Board_Layout	Recommended number of 10 mil thermal vias under the IC
4.	Top Cu	32.3 mm ²	Board_Layout	Recommended minimum area of top layer copper connected to DAP
5.	Cin IRMS	210.975 mA	Current	Input capacitor RMS ripple current
6.	Cout IRMS	251.683 mA	Current	Output capacitor RMS ripple current
7.	IC Ipk	935.928 mA	Current	Peak switch current in IC
8.	Iin Avg	181.78 mA	Current	Average input current
9.	L Ipp	871.86 mA	Current	Peak-to-peak inductor ripple current
10.	M Irms	282.964 mA	Current	MOSFET RMS current
11.	BOM Count	9	General	Total Design BOM count
12.	FootPrint	137.0 mm ²	General	Total Foot Print Area of BOM components
13.	Frequency	2.0 MHz	General	Switching frequency
14.	IC Tolerance	10.0 mV	General	IC Feedback Tolerance
15.	M Vds Act	48.553 mV	General	Voltage drop across the MosFET
16.	Mode	CCM	General	Conduction Mode
17.	Pout	2.1 W	General	Total output power
18.	Total BOM	\$1.49	General	Total BOM Cost
19.	D1 Tj	104.266 degC	Op_Point	D1 junction temperature
20.	Vout Actual	4.24 V	Op_Point	Vout Actual calculated based on selected voltage divider resistors
21.	Vout OP	4.2 V	Op_Point	Operational Output Voltage
22.	Duty Cycle	32.027 %	Op_point	Duty cycle
23.	Efficiency	82.516 %	Op_point	Steady state efficiency
24.	IC Tj	73.722 degC	Op_point	IC junction temperature
25.	ICThetaJA	45.0 degC/W	Op_point	IC junction-to-ambient thermal resistance
26.	IOUT_OP	500.0 mA	Op_point	Iout operating point
27.	VIN_OP	14.0 V	Op_point	Vin operating point
28.	Vout Act	4.24 V	Op_point	Achieved Vout with feedback resistor pair
29.	Vout p-p	3.457 mV	Op_point	Peak-to-peak output ripple voltage
30.	Cin Pd	194.332 μW	Power	Input capacitor power dissipation
31.	Cout Pd	236.591 μW	Power	Output capacitor power dissipation
32.	Diode Pd	134.14 mW	Power	Diode power dissipation
33.	IC Pd	304.939 mW	Power	IC power dissipation
34.	L Pd	5.445 mW	Power	Inductor power dissipation
35.	Total Pd	444.954 mW	Power	Total Power Dissipation
36.	Vout Tolerance	2.559 %		Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable

Design Inputs

#	Name	Value	Description
1.	Iout	500.0 m	Maximum Output Current
2.	VinMax	14.0	Maximum input voltage
3.	VinMin	10.0	Minimum input voltage
4.	Vout	4.2	Output Voltage
5.	base_pn	LM27341	Texas Instruments Base Part Number
6.	source	DC	Input Source Type
7.	ta	60.0	Ambient temperature

Design Assistance

1. LM27341 Product Folder : <http://www.ti.com/product/LM27341> : contains the data sheet and other resources.

Texas Instruments' WEBENCH simulation tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Simulations are created using Texas Instruments' published specifications as well as the published specifications of other device manufacturers. While Texas Instruments does update this information periodically, this information may not be current at the time the simulation is built. Texas Instruments does not warrant the accuracy or completeness of the specifications or any information contained therein. Texas Instruments does not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. Texas Instruments does not warrant that the designs are production worthy.

You should completely validate and test your design implementation to confirm the system functionality for your application prior to production.

Use of Texas Instruments' WEBENCH simulation tools is subject to [Texas Instruments' Site Terms and Conditions of Use](#). Prototype boards based on WEBENCH created designs are provided AS IS without warranty of any kind for evaluation and testing purposes and are subject to the terms of the [Evaluation License Agreement](#).