
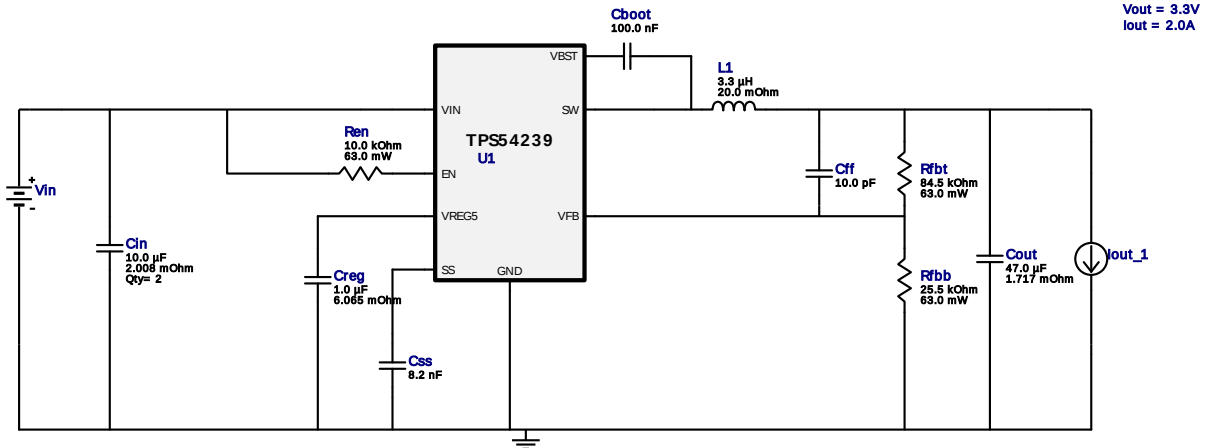


WEBENCH® Design Report




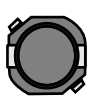
Design : 4766239/7 TPS54239DDAR
TPS54239DDAR 14.0V-22.0V to 3.30V @ 2.0A















Electrical BOM


#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	Cboot	MuRata	GRM155R61A104KA01D Series= X5R	Cap= 100.0 nF VDC= 10.0 V IRMS= 0.0 A	1	\$0.01	 0402 3 mm ²
2.	Cff	Kemet	C0805C100M4GACTU Series= C0G/NP0	Cap= 10.0 pF VDC= 16.0 V IRMS= 0.0 A	1	\$0.01	 0805 7 mm ²
3.	Cin	MuRata	GRM32ER7YA106KA12L Series= X7R	Cap= 10.0 uF ESR= 2.008 mOhm VDC= 35.0 V IRMS= 4.6772 A	2	\$0.22	 1210_280 15 mm ²
4.	Cout	TDK	C3216JB1A476M Series= JB	Cap= 47.0 uF ESR= 1.717 mOhm VDC= 10.0 V IRMS= 0.0 A	1	\$0.34	 1206 11 mm ²
5.	Creg	MuRata	GRM188R61A105KA61D Series= X5R	Cap= 1.0 uF ESR= 6.065 mOhm VDC= 10.0 V IRMS= 1.30675 A	1	\$0.01	 0603 5 mm ²
6.	Css	MuRata	GRM033R61A822KA01D Series= X5R	Cap= 8.2 nF VDC= 10.0 V IRMS= 0.0 A	1	\$0.01	 0201 2 mm ²
7.	L1	TDK	CLF7045T-3R3N	L= 3.3 uH DCR= 20.0 mOhm	1	\$0.42	 CLF7045 86 mm ²
8.	Ren	Vishay-Dale	CRCW040210K0FKED Series= CRCW..e3	Res= 10.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
9.	Rfbb	Vishay-Dale	CRCW040225K5FKED Series= CRCW..e3	Res= 25.5 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
10.	Rfbt	Vishay-Dale	CRCW040284K5FKED Series= CRCW..e3	Res= 84.5 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
11. U1		Texas Instruments	TPS54239DDAR	Switcher	1	\$0.73	 DDA0008E 57 mm ²

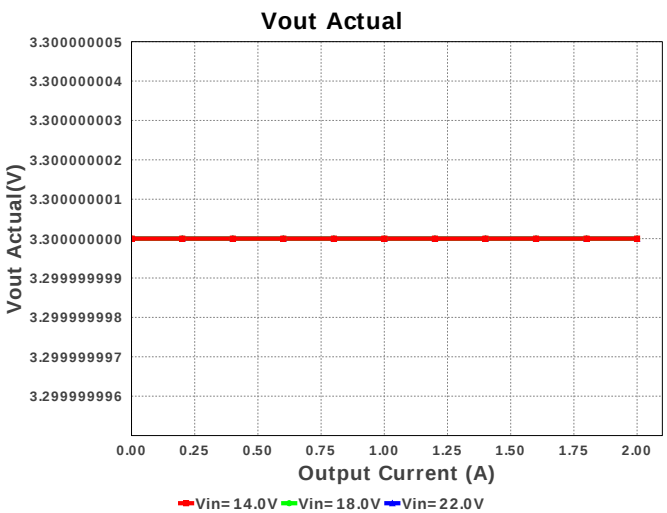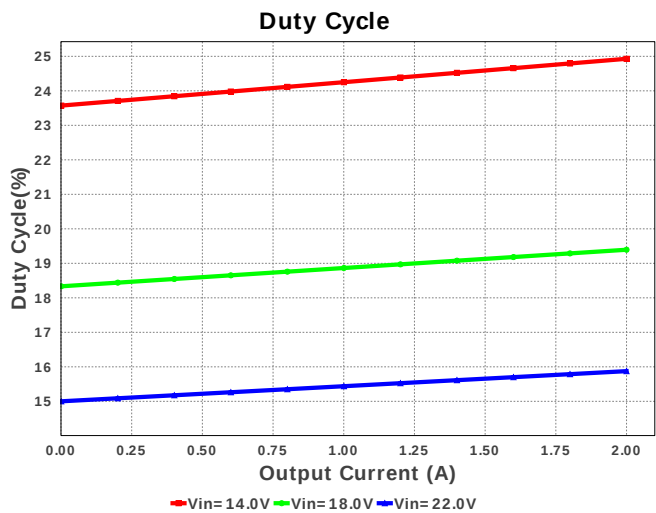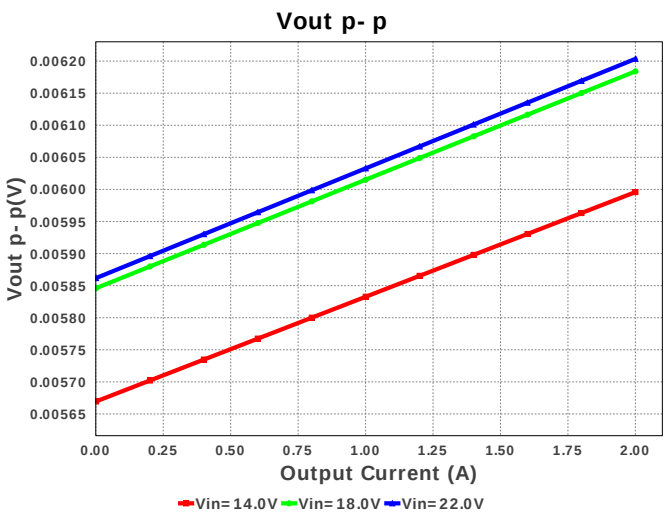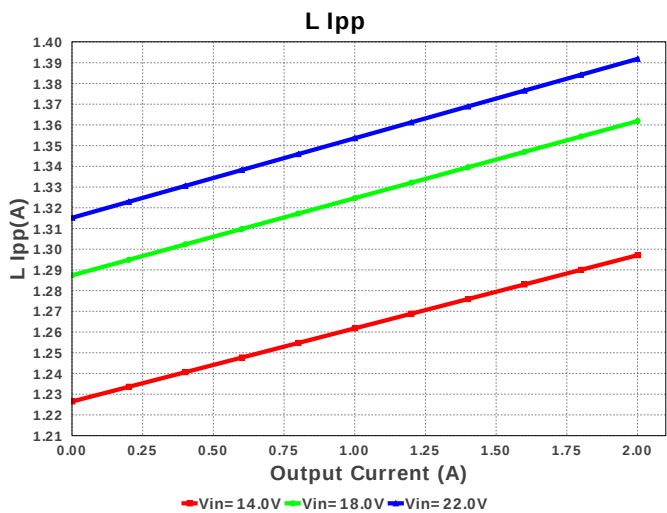

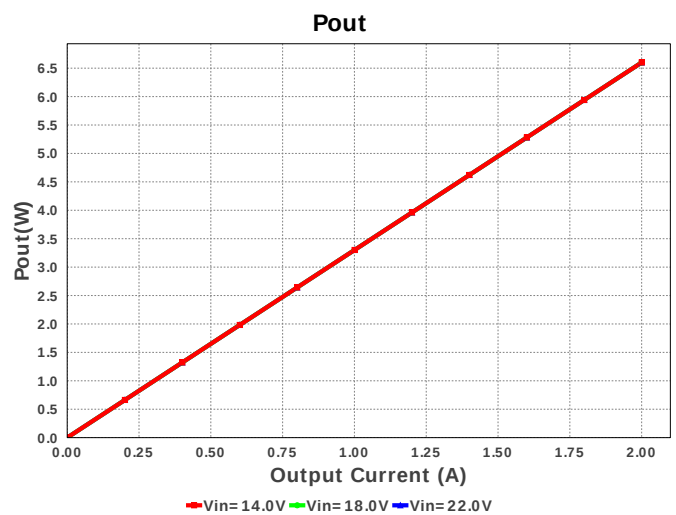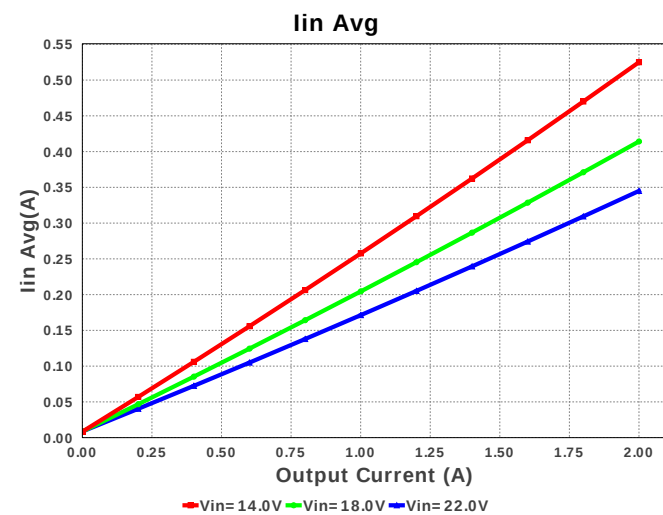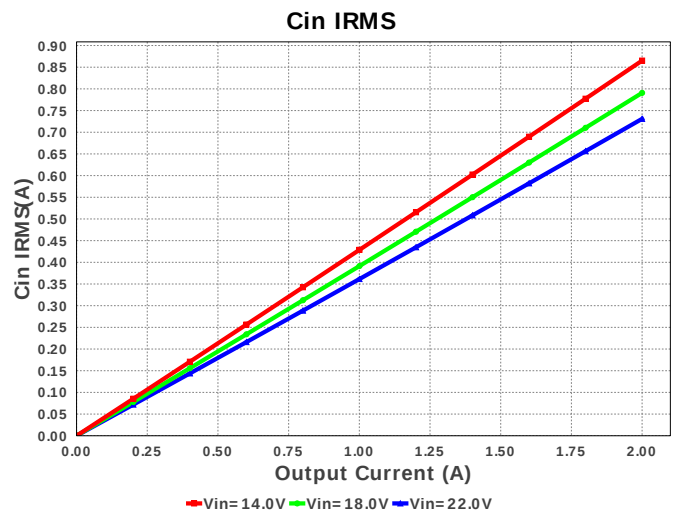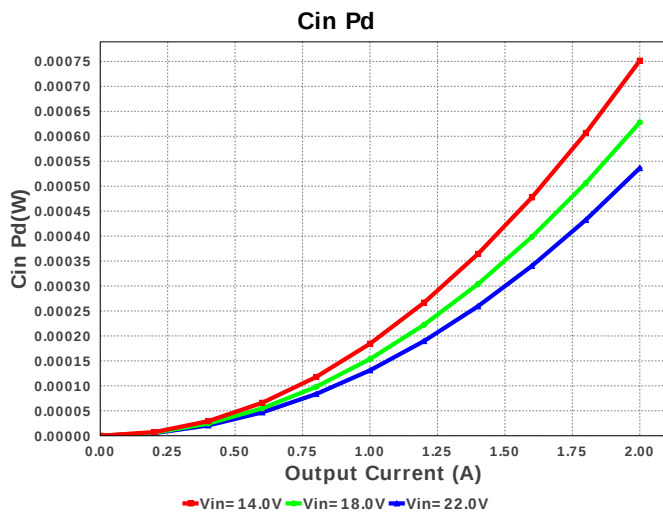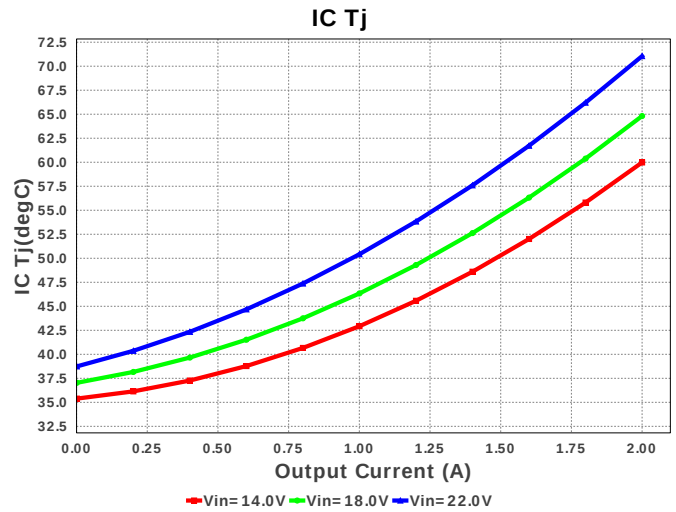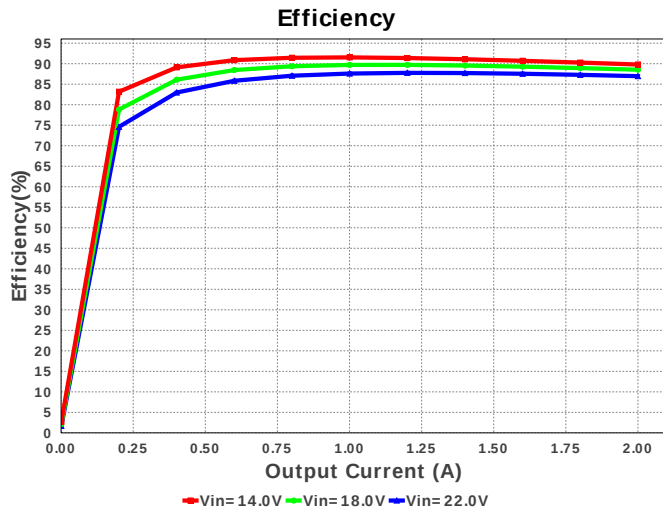

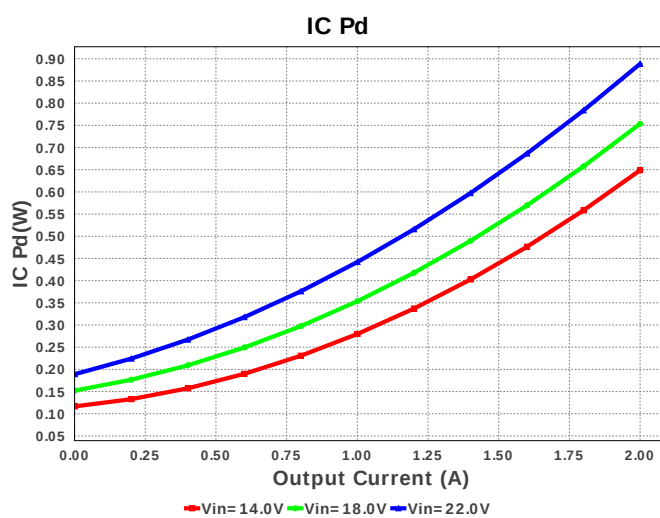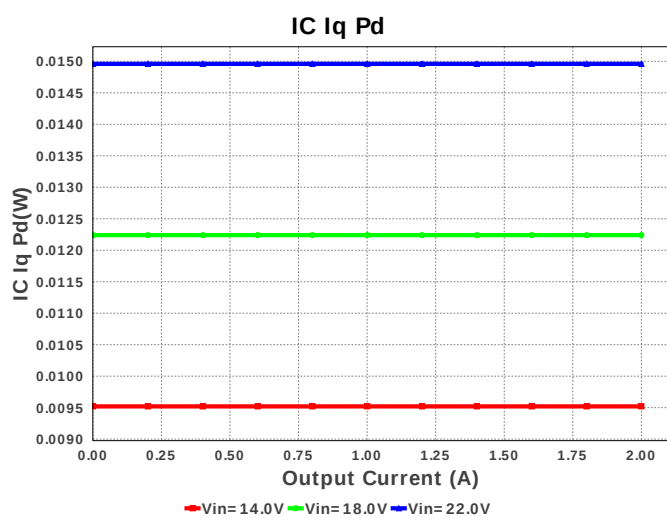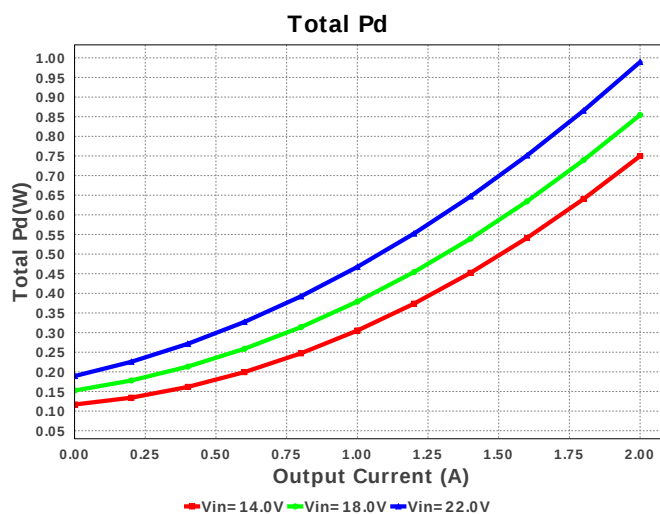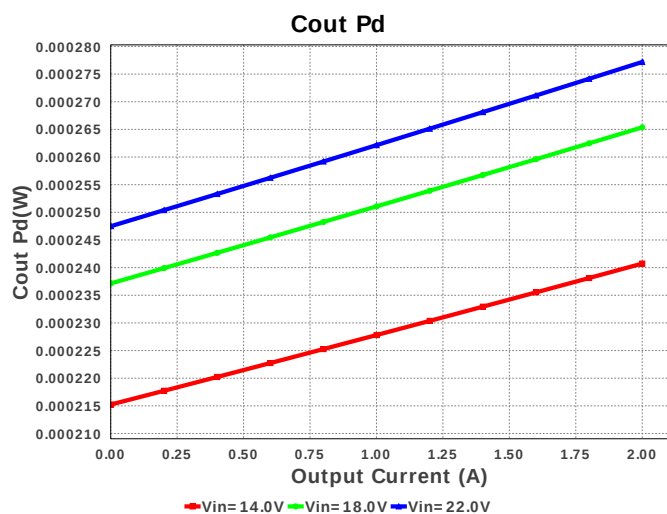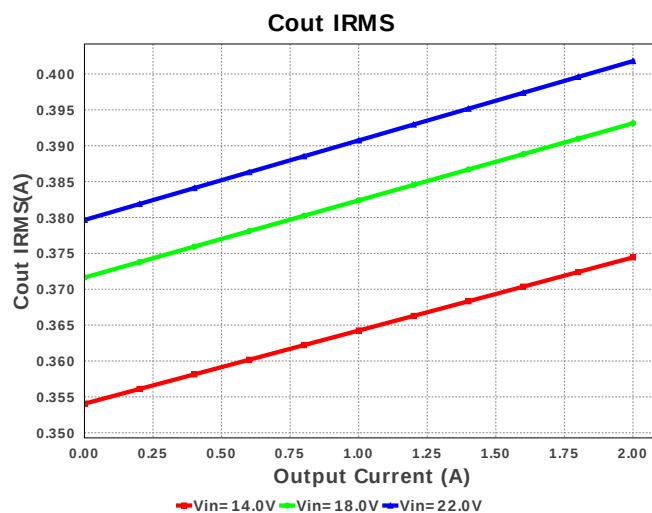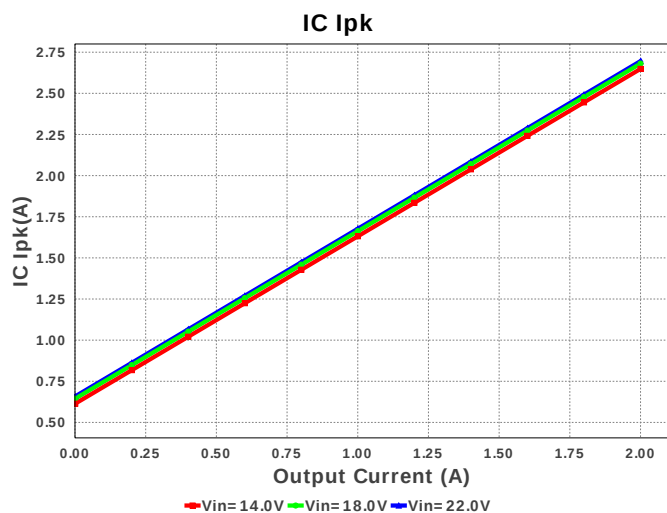

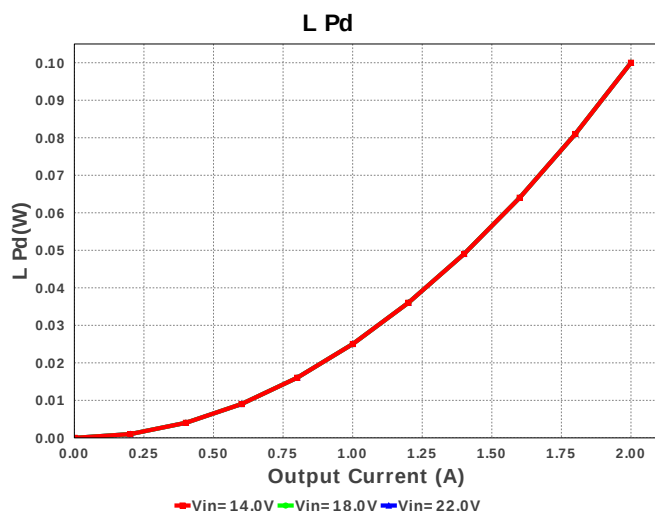

Operating Values

#	Name	Value	Category	Description
1.	Cin IRMS	730.882 mA	Current	Input capacitor RMS ripple current
2.	Cout IRMS	401.796 mA	Current	Output capacitor RMS ripple current
3.	IC Ipk	2.696 A	Current	Peak switch current in IC
4.	Iin Avg	344.97 mA	Current	Average input current
5.	L Ipp	1.392 A	Current	Peak-to-peak inductor ripple current
6.	BOM Count	12	General	Total Design BOM count
7.	FootPrint	209.0 mm ²	General	Total Foot Print Area of BOM components
8.	Frequency	646.308 kHz	General	Switching frequency
9.	Mode	CCM	General	Conduction Mode
10.	Pout	6.6 W	General	Total output power
11.	Total BOM	\$2.0	General	Total BOM Cost
12.	Vout Actual	3.3 V	Op_Point	Vout Actual calculated based on selected voltage divider resistors
13.	Vout OP	3.3 V	Op_Point	Operational Output Voltage
14.	Duty Cycle	15.875 %	Op_point	Duty cycle
15.	Efficiency	86.963 %	Op_point	Steady state efficiency
16.	IC Tj	71.053 degC	Op_point	IC junction temperature
17.	ICThetaJA	46.2 degC/W	Op_point	IC junction-to-ambient thermal resistance
18.	IOUT_OP	2.0 A	Op_point	Iout operating point
19.	VIN_OP	22.0 V	Op_point	Vin operating point
20.	Vout p-p	6.203 mV	Op_point	Peak-to-peak output ripple voltage
21.	Cin Pd	536.325 μ W	Power	Input capacitor power dissipation
22.	Cout Pd	277.193 μ W	Power	Output capacitor power dissipation
23.	IC Iq Pd	14.96 mW	Power	IC Iq Pd
24.	IC Pd	888.586 mW	Power	IC power dissipation
25.	L Pd	100.0 mW	Power	Inductor power dissipation
26.	Total Pd	989.422 mW	Power	Total Power Dissipation
27.	Vout Tolerance	3.41 %		Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable

Design Inputs

#	Name	Value	Description
1.	Iout	2.0	Maximum Output Current
2.	VinMax	22.0	Maximum input voltage
3.	VinMin	14.0	Minimum input voltage
4.	Vout	3.3	Output Voltage
5.	base_pn	TPS54239	Base Product Number
6.	source	DC	Input Source Type
7.	Ta	30.0	Ambient temperature

Design Assistance

1. **TPS54239** Product Folder : <http://www.ti.com/product/TPS54239> : contains the data sheet and other resources.

Texas Instruments' WEBENCH simulation tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Simulations are created using Texas Instruments' published specifications as well as the published specifications of other device manufacturers. While Texas Instruments does update this information periodically, this information may not be current at the time the simulation is built. Texas Instruments does not warrant the accuracy or completeness of the specifications or any information contained therein. Texas Instruments does not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. Texas Instruments does not warrant that the designs are production worthy.

You should completely validate and test your design implementation to confirm the system functionality for your application prior to production.

Use of Texas Instruments' WEBENCH simulation tools is subject to [Texas Instruments' Site Terms and Conditions of Use](#). Prototype boards based on WEBENCH created designs are provided AS IS without warranty of any kind for evaluation and testing purposes and are subject to the terms of the [Evaluation License Agreement](#).