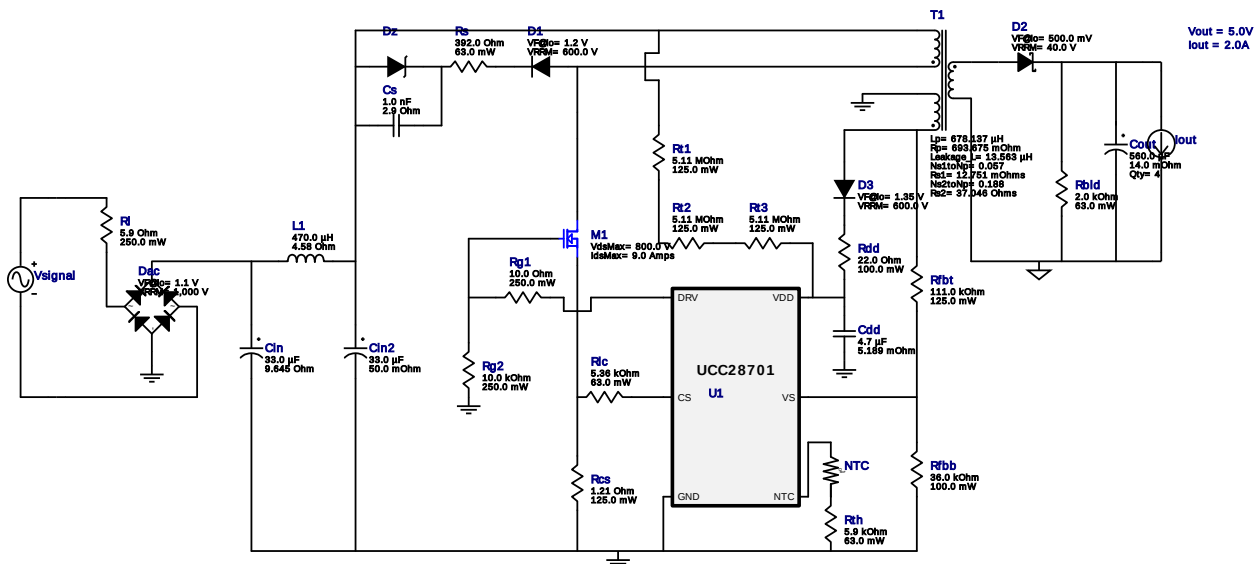



VinMin = 110.0V  
VinMax = 265.0V  
Vout = 5.0V  
Iout = 2.0A


Device = UCC28701DBVR  
Topology = Flyback  
Created = 9/6/16 10:24:33 PM  
BOM Cost = \$0.00  
BOM Count = 32  
Total Pd = 2.3W







1. R<sub>l</sub>bd is a starting point, but may need to be experimented with in order to get minimum current needed to hold V<sub>out</sub> at no load. R<sub>l</sub>c and the feedback resistors may also need adjustment based on the actual transformer used. For more information please click the design assistance button.







## Electrical BOM
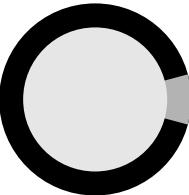
| #  | Name | Manufacturer | Part Number                       | Properties                                                       | Qty | Price  | Footprint                                                                                                                   |
|----|------|--------------|-----------------------------------|------------------------------------------------------------------|-----|--------|-----------------------------------------------------------------------------------------------------------------------------|
| 1. | Cdd  | MuRata       | GRM21BR61E475KA12L<br>Series= X5R | Cap= 4.7 uF<br>ESR= 5.189 mOhm<br>VDC= 25.0 V<br>IRMS= 2.03531 A | 1   | \$0.02 | <br>0805 7 mm <sup>2</sup>             |
| 2. | Cin  | Nichicon     | UCS2W330MHD6<br>Series= 2234      | Cap= 33.0 uF<br>ESR= 9.645 Ohm<br>VDC= 450.0 V<br>IRMS= 490.0 mA | 1   | \$0.58 | UCS_1800x2000 0 mm <sup>2</sup>                                                                                             |
| 3. | Cin2 | Nichicon     | UPW2W330MHD<br>Series= PW         | Cap= 33.0 uF<br>ESR= 50.0 mOhm<br>VDC= 450.0 V<br>IRMS= 145.0 mA | 1   | \$0.80 | <br>CAPPR7.5-18X40 400 mm <sup>2</sup> |
| 4. | Cout | Panasonic    | 16SVPF560M<br>Series= ?           | Cap= 560.0 uF<br>ESR= 14.0 mOhm<br>VDC= 16.0 V<br>IRMS= 4.95 A   | 4   | \$0.61 | <br>CAPSMT_62_E12 106 mm <sup>2</sup>  |
| 5. | Cs   | MuRata       | GRM188R72E102KW07D<br>Series= X7R | Cap= 1.0 nF<br>ESR= 2.9 Ohm<br>VDC= 250.0 V<br>IRMS= 90.0 mA     | 1   | \$0.01 | <br>0603 5 mm <sup>2</sup>             |
| 6. | D1   | Bourns       | CD214B-F3600                      | VF@Io= 1.2 V<br>VRRM= 600.0 V                                    | 1   | \$0.14 | <br>SMB 44 mm <sup>2</sup>             |

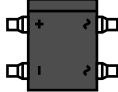
| #   | Name | Manufacturer                | Part Number                          | Properties                                            | Qty | Price  | Footprint                                                                                              |
|-----|------|-----------------------------|--------------------------------------|-------------------------------------------------------|-----|--------|--------------------------------------------------------------------------------------------------------|
| 7.  | D2   | Diodes Inc.                 | B340A-13-F                           | VF@Io= 500.0 mV<br>VRRM= 40.0 V                       | 1   | \$0.11 | <br>SMA 37 mm²      |
| 8.  | D3   | Micro Commercial Components | ES1J-TP                              | VF@Io= 1.35 V<br>VRRM= 600.0 V                        | 1   | \$0.08 | <br>SMA 37 mm²      |
| 9.  | Dac  | Vishay-Semiconductor        | DF10SA                               | VF@Io= 1.1 V<br>VRRM= 1,000.0 V                       | 1   | \$0.24 | <br>DF-S 99 mm²     |
| 10. | Dz   | ON Semiconductor            | 1SMB5949BT3G                         | Zener                                                 | 1   | \$0.10 | <br>SMB 44 mm²      |
| 11. | L1   | TDK                         | VLCF4028T-471MR14-2                  | L= 470.0 µH<br>DCR= 4.58 Ohm                          | 1   | \$0.36 | <br>VLCF4028 25 mm² |
| 12. | M1   | STMicroelectronics          | STF10N80K5                           | VdsMax= 800.0 V<br>IdsMax= 9.0 Amps                   | 1   | \$2.52 | <br>TO-220FP 79 mm² |
| 13. | Rbld | Vishay-Dale                 | CRCW04022K00FKED<br>Series= CRCW..e3 | Res= 2.0 kOhm<br>Power= 63.0 mW<br>Tolerance= 1.0%    | 1   | \$0.01 | <br>0402 3 mm²      |
| 14. | Rcs  | Vishay-Dale                 | CRCW08051R21FKEA<br>Series= CRCW..e3 | Res= 1.21 Ohm<br>Power= 125.0 mW<br>Tolerance= 1.0%   | 1   | \$0.01 | <br>0805 7 mm²      |
| 15. | Rdd  | Yageo America               | RC0603FR-0722RL<br>Series= ?         | Res= 22.0 Ohm<br>Power= 100.0 mW<br>Tolerance= 1.0%   | 1   | \$0.01 | <br>0603 5 mm²      |
| 16. | Rfbb | Yageo America               | RC0603FR-0736KL<br>Series= ?         | Res= 36.0 kOhm<br>Power= 100.0 mW<br>Tolerance= 1.0%  | 1   | \$0.01 | <br>0603 5 mm²    |
| 17. | Rfbt | Yageo America               | RT0805BRD07111KL<br>Series= RT0805   | Res= 111.0 kOhm<br>Power= 125.0 mW<br>Tolerance= 0.1% | 1   | \$0.05 | <br>0805 7 mm²    |
| 18. | Rg1  | Panasonic                   | ERJ-8ENF10R0V<br>Series= ERJ-8E      | Res= 10.0 Ohm<br>Power= 250.0 mW<br>Tolerance= 1.0%   | 1   | \$0.01 | <br>1206 11 mm²   |
| 19. | Rg2  | Panasonic                   | ERJ-8ENF1002V<br>Series= ERJ-8E      | Res= 10.0 kOhm<br>Power= 250.0 mW<br>Tolerance= 1.0%  | 1   | \$0.01 | <br>1206 11 mm²   |
| 20. | RI   | Vishay-Dale                 | CRCW12065R90FKEA<br>Series= CRCW..e3 | Res= 5.9 Ohm<br>Power= 250.0 mW<br>Tolerance= 1.0%    | 1   | \$0.01 | <br>1206 11 mm²   |
| 21. | Rlc  | Vishay-Dale                 | CRCW04025K36FKED<br>Series= CRCW..e3 | Res= 5.36 kOhm<br>Power= 63.0 mW<br>Tolerance= 1.0%   | 1   | \$0.01 | <br>0402 3 mm²    |
| 22. | Rs   | Vishay-Dale                 | CRCW0402392RFKED<br>Series= CRCW..e3 | Res= 392.0 Ohm<br>Power= 63.0 mW<br>Tolerance= 1.0%   | 1   | \$0.01 | <br>0402 3 mm²    |
| 23. | Rt1  | Vishay-Dale                 | CRCW08055M11FKEA<br>Series= CRCW..e3 | Res= 5.11 MOhm<br>Power= 125.0 mW<br>Tolerance= 1.0%  | 1   | \$0.01 | <br>0805 7 mm²    |
| 24. | Rt2  | Vishay-Dale                 | CRCW08055M11FKEA<br>Series= CRCW..e3 | Res= 5.11 MOhm<br>Power= 125.0 mW<br>Tolerance= 1.0%  | 1   | \$0.01 | <br>0805 7 mm²    |
| 25. | Rt3  | Vishay-Dale                 | CRCW08055M11FKEA<br>Series= CRCW..e3 | Res= 5.11 MOhm<br>Power= 125.0 mW<br>Tolerance= 1.0%  | 1   | \$0.01 | <br>0805 7 mm²    |
| 26. | Rth  | Vishay-Dale                 | CRCW04025K90FKED<br>Series= CRCW..e3 | Res= 5.9 kOhm<br>Power= 63.0 mW<br>Tolerance= 1.0%    | 1   | \$0.01 | <br>0402 3 mm²    |

| #   | Name | Manufacturer      | Part Number  | Properties                                                                                                                                        | Qty | Price  | Footprint                                                                                                       |
|-----|------|-------------------|--------------|---------------------------------------------------------------------------------------------------------------------------------------------------|-----|--------|-----------------------------------------------------------------------------------------------------------------|
| 27. | T1   | CUSTOM            | CUSTOM       | Lp= 678.137 $\mu$ H<br>Rp= 693.675 mOhm<br>Leakage_L= 13.563 $\mu$ H<br>Ns1toNp= 0.057<br>Rs1= 12.751 mOhms<br>Ns2toNp= 0.188<br>Rs2= 37.046 Ohms | 1   | NA     | CUSTOM 0 mm <sup>2</sup>                                                                                        |
| 28. | U1   | Texas Instruments | UCC28701DBVR | Switcher                                                                                                                                          | 1   | \$0.35 |  SOT-23-6 15 mm <sup>2</sup> |

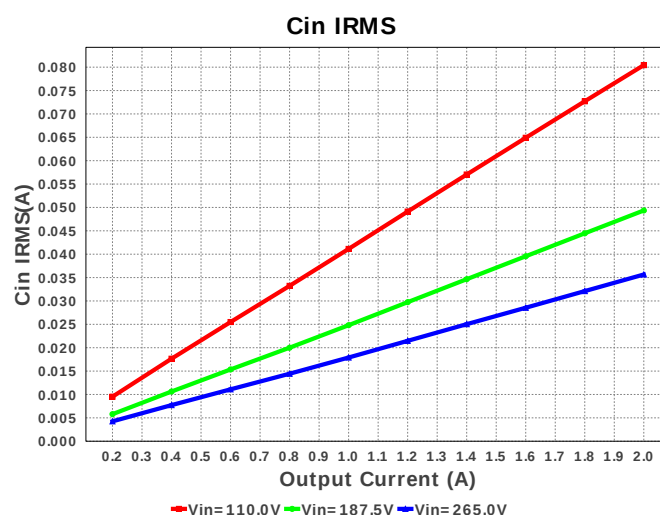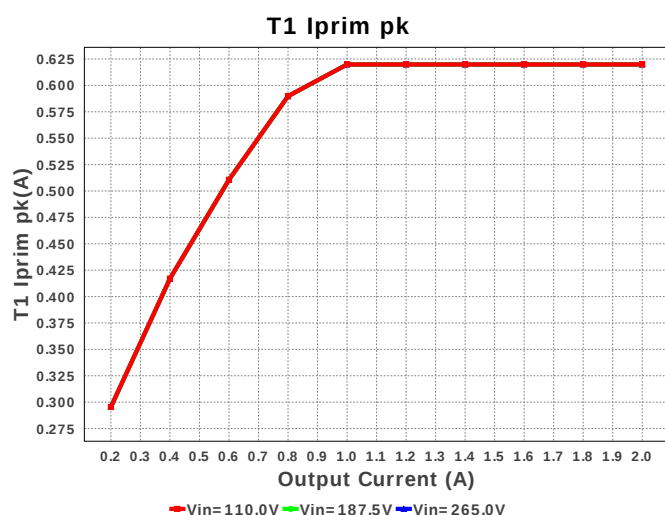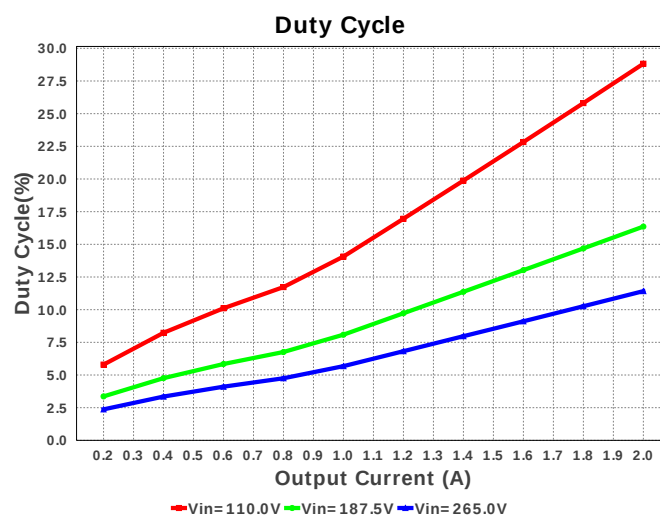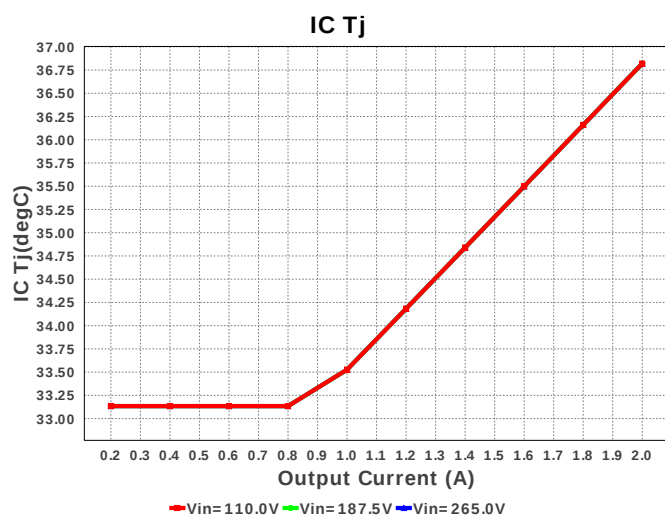


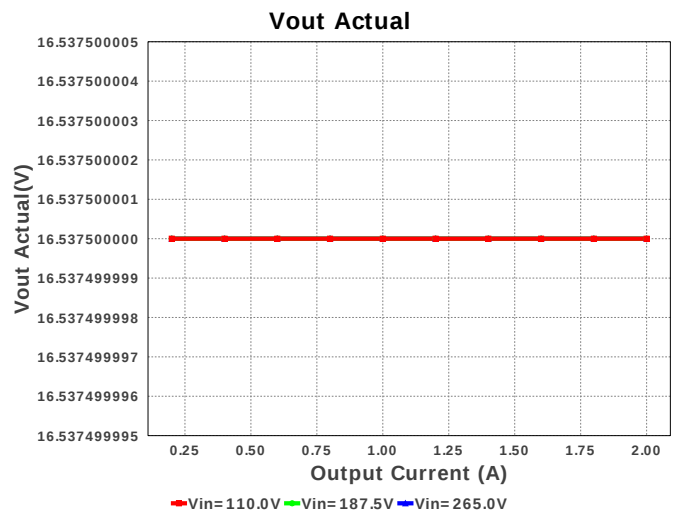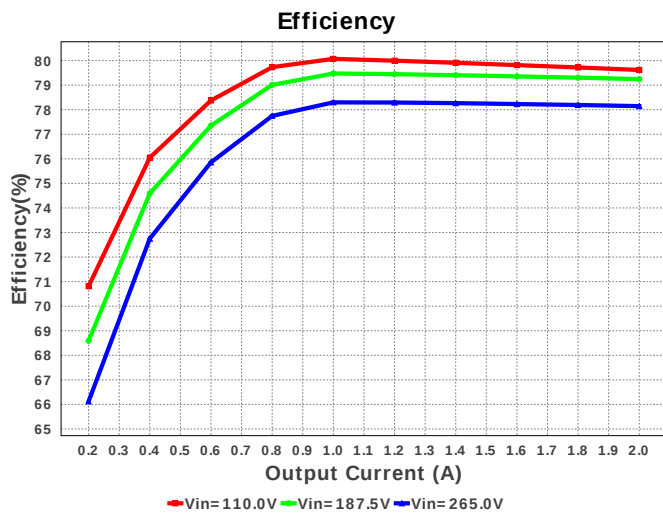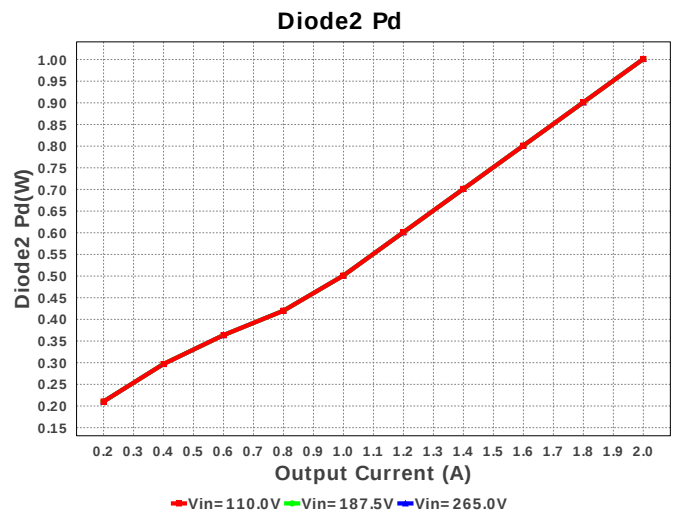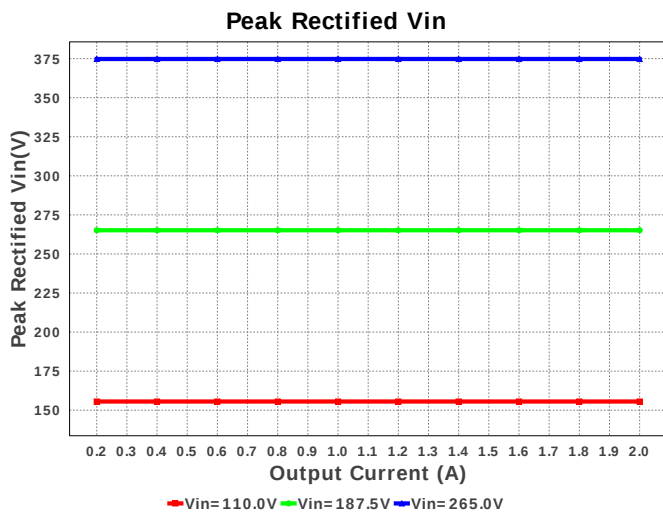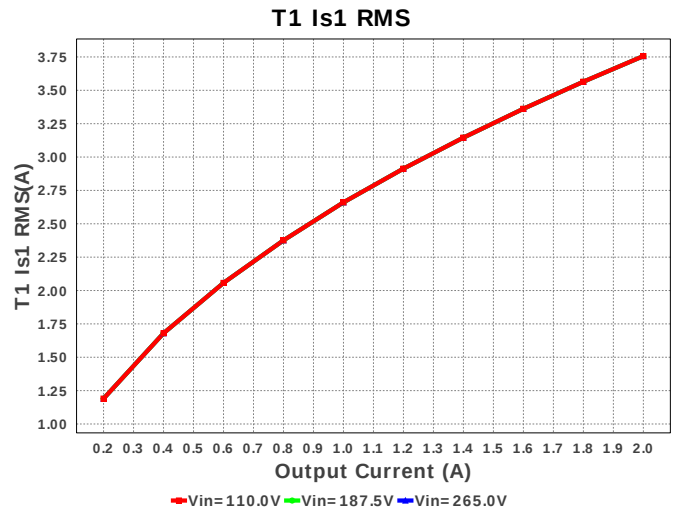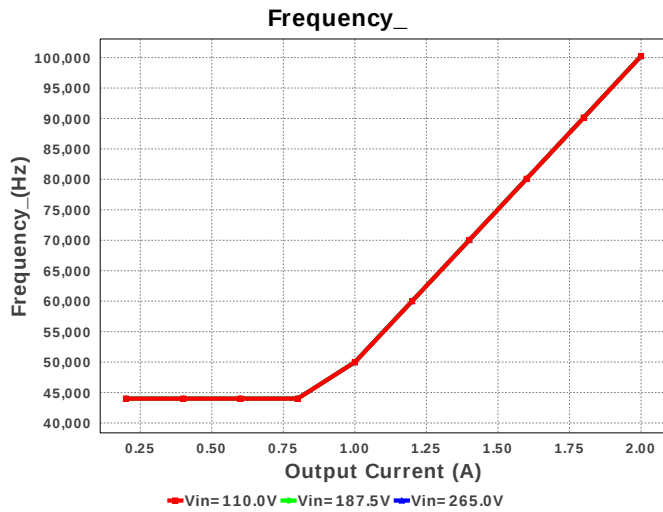


M1 TjOP

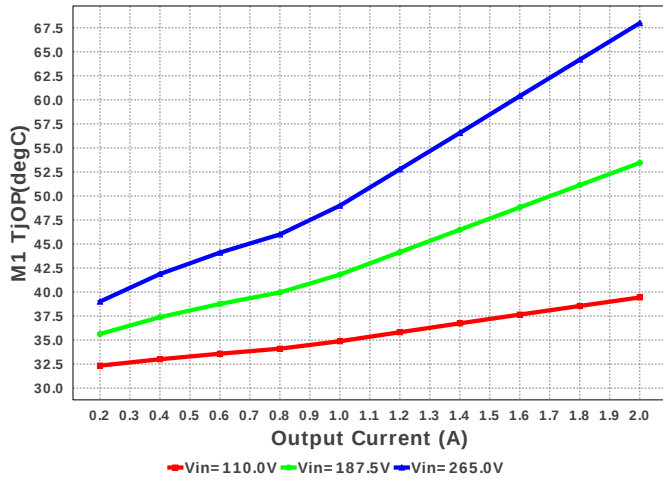


Cin2 IRMS

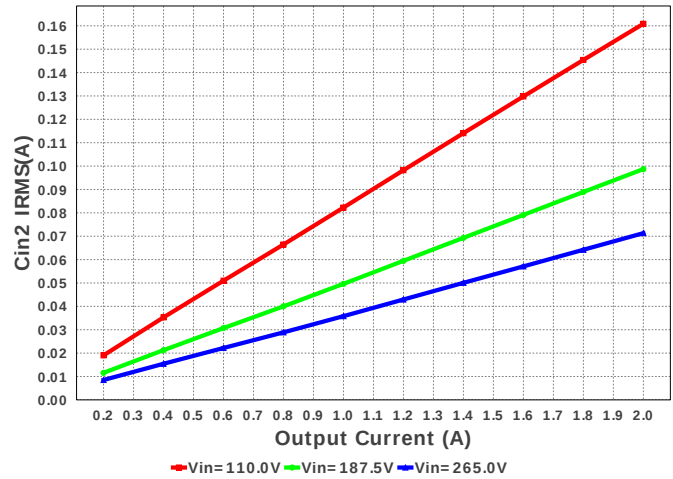


Vout p- p

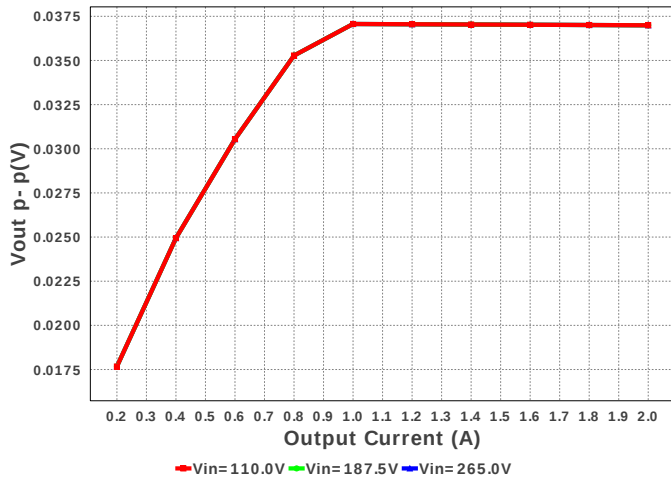


T1 Iprim RMS






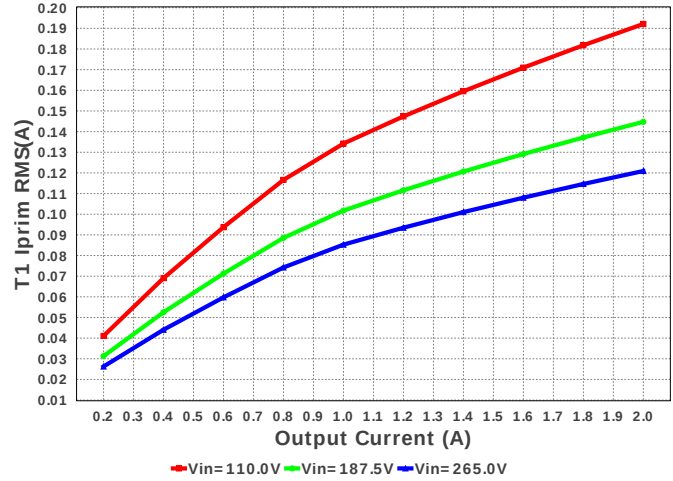








Zener Pd



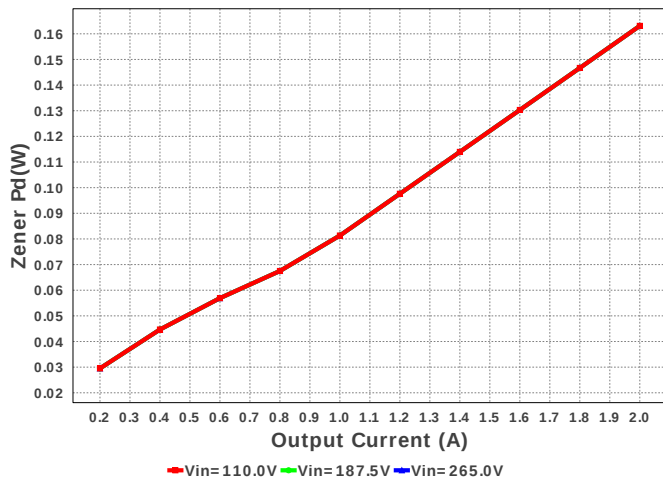


lin rms

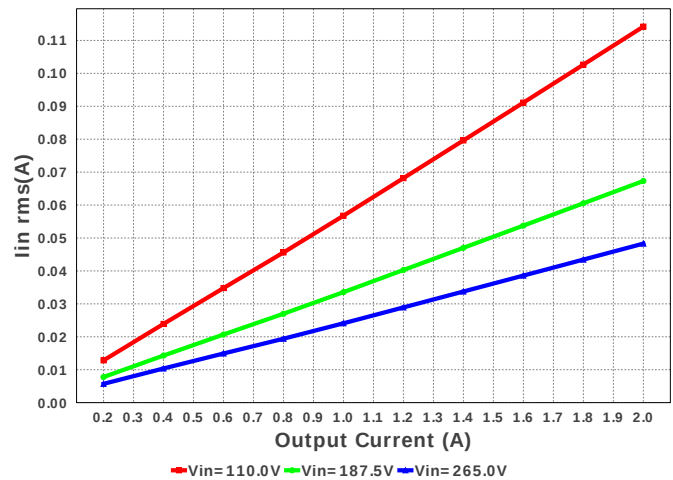

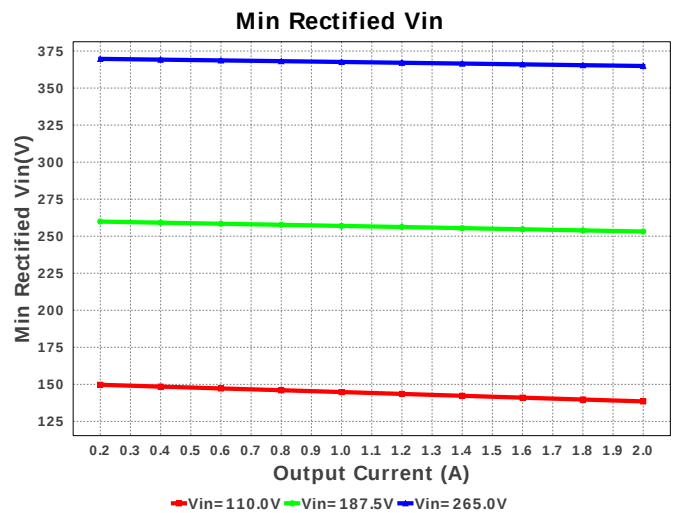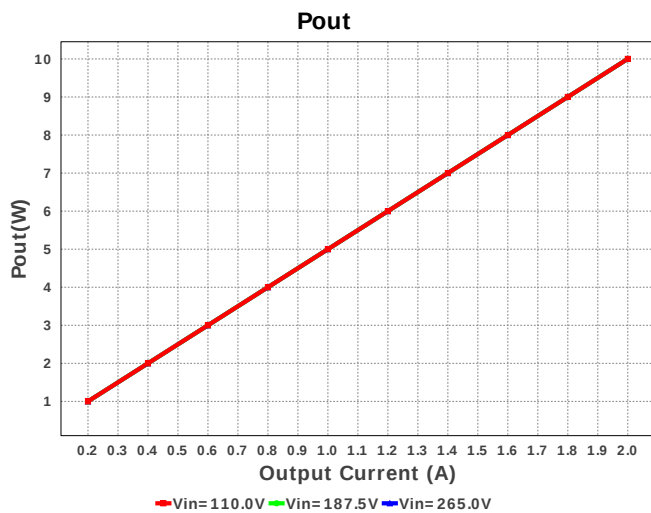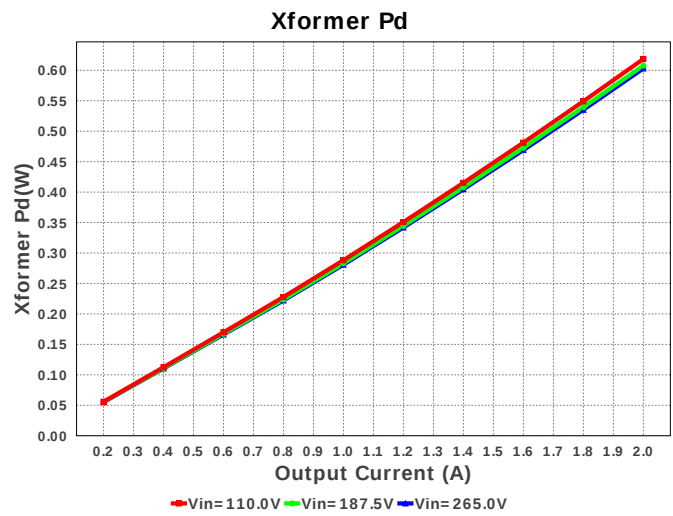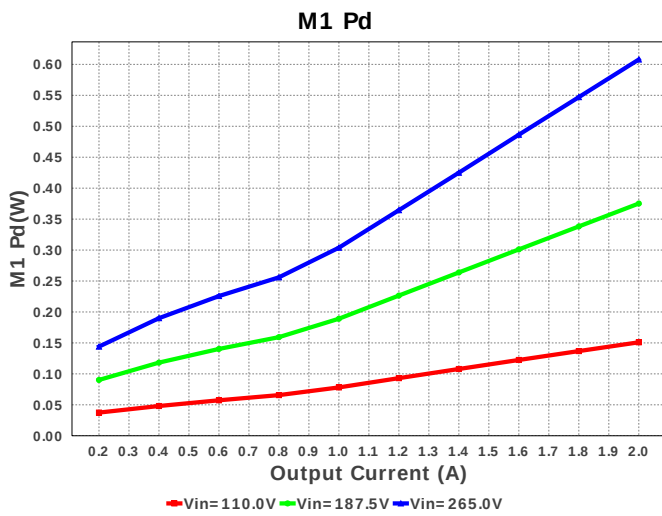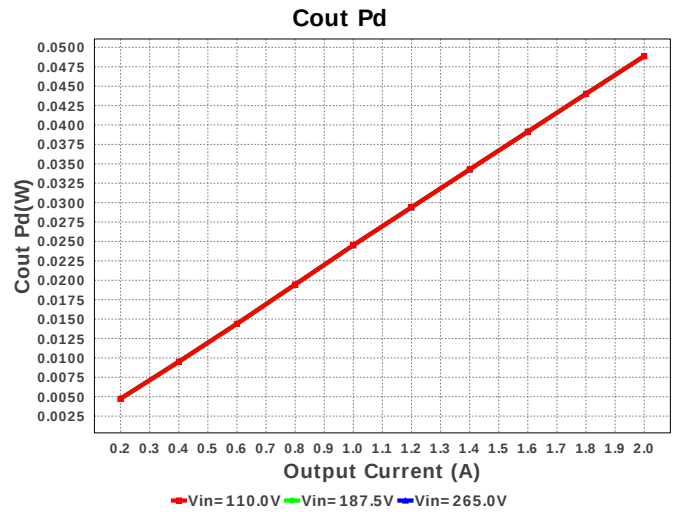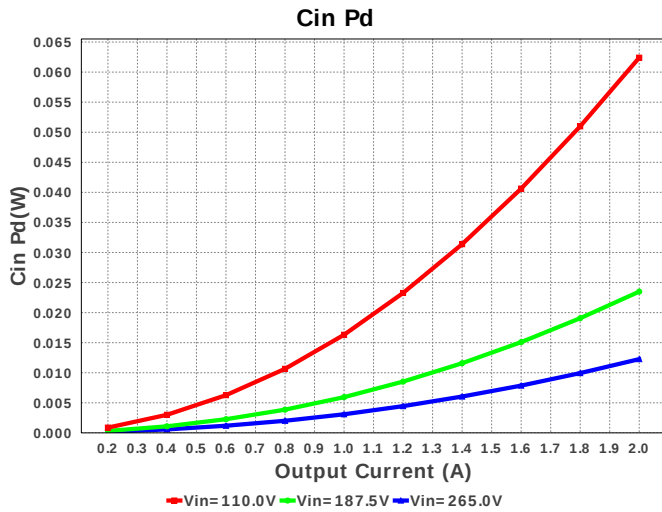

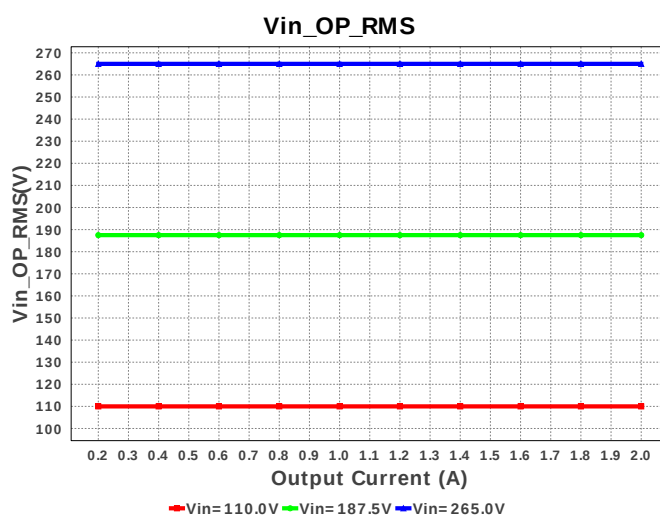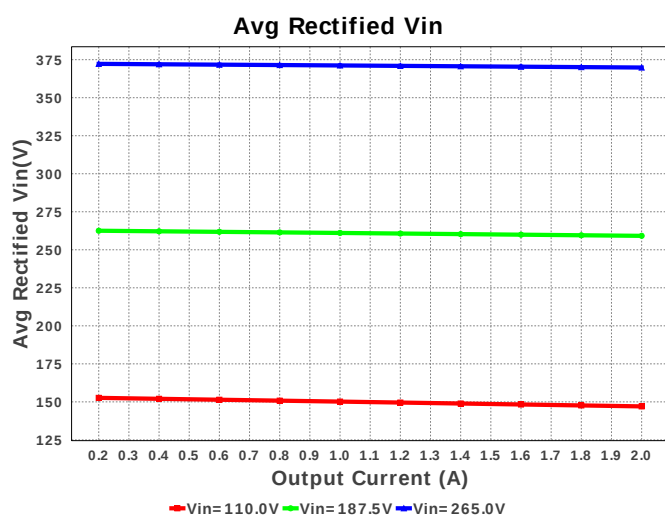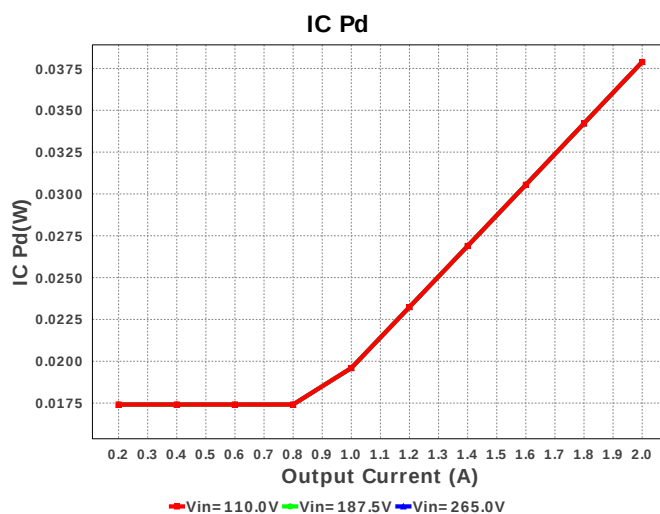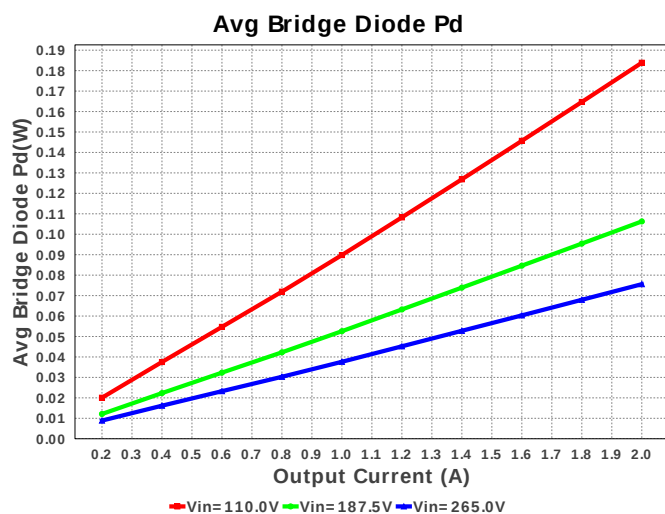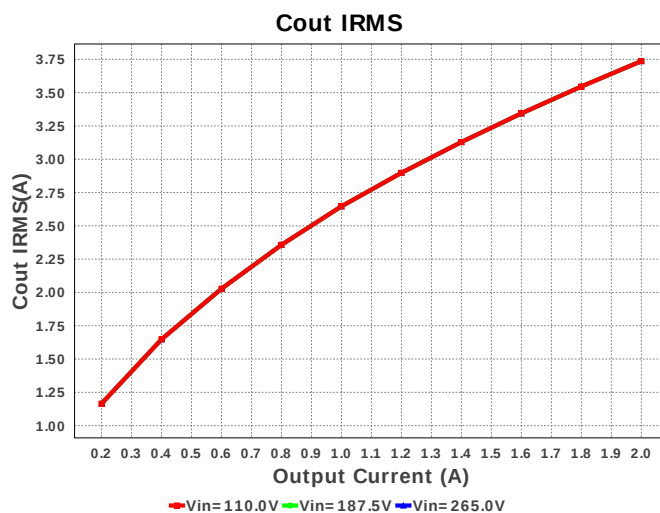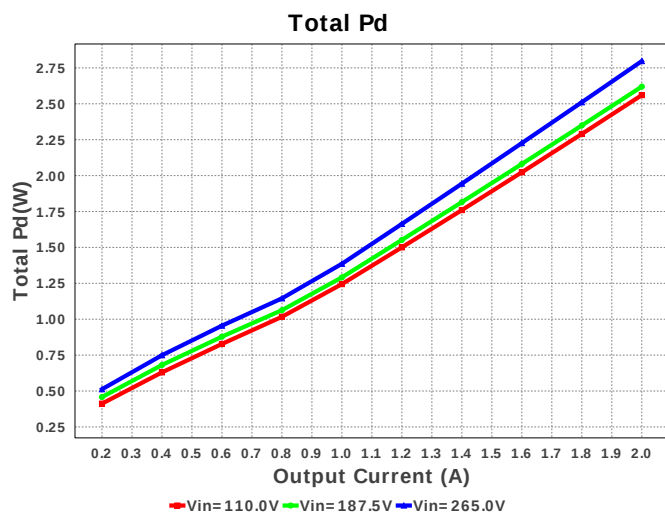

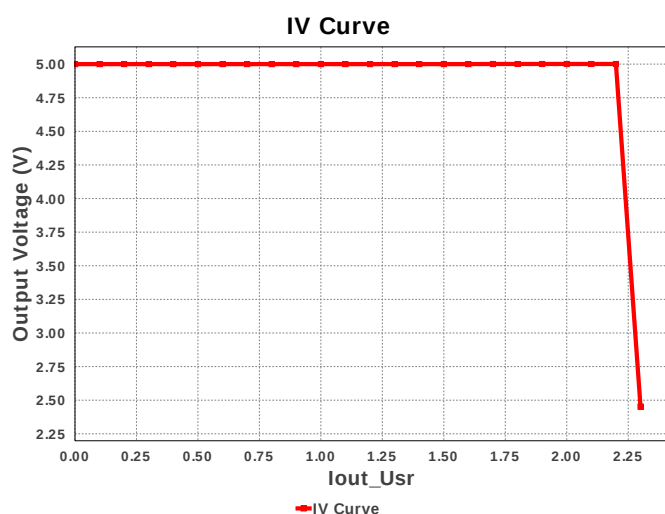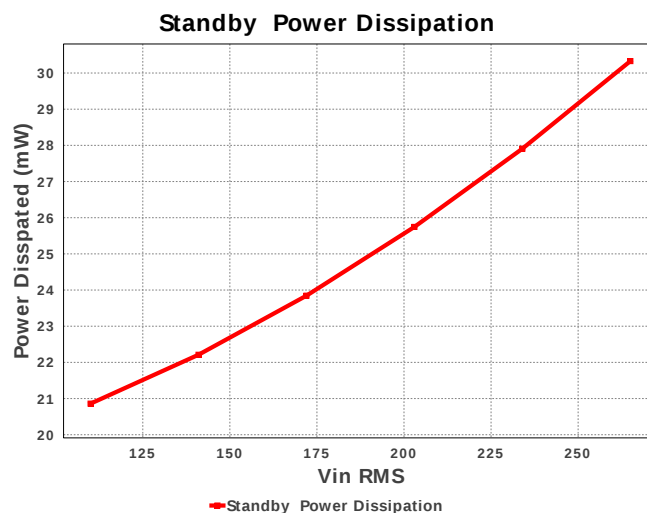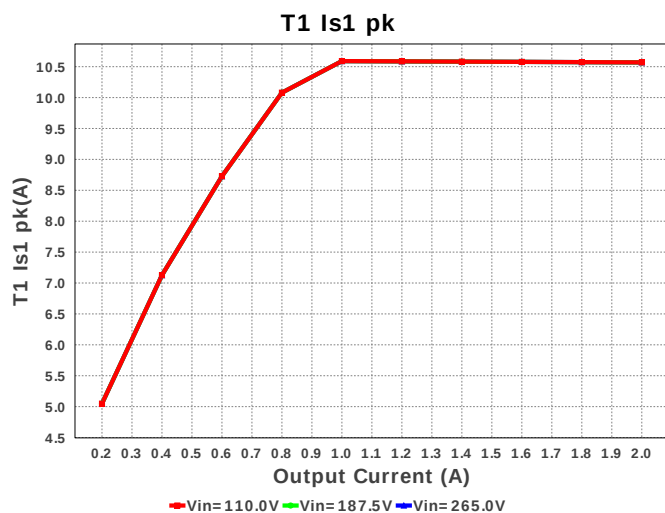

## Operating Values

| #   | Name                | Value                   | Category | Description                                                           |
|-----|---------------------|-------------------------|----------|-----------------------------------------------------------------------|
| 1.  | Cin IRMS            | 34.362 mA               | Current  | Input capacitor RMS ripple current                                    |
| 2.  | Cin2 IRMS           | 234.747 mA              | Current  | Input Capacitor Cin2 RMS Ripple Current                               |
| 3.  | Cout IRMS           | 3.752 A                 | Current  | Output capacitor RMS ripple current                                   |
| 4.  | Iin rms             | 46.441 mA               | Current  | RMS Input Current                                                     |
| 5.  | T1 Iprim RMS        | 118.934 mA              | Current  | Transformer Primary RMS Current                                       |
| 6.  | T1 Iprim pk         | 619.835 mA              | Current  | Transformer Primary Peak Current                                      |
| 7.  | T1 Is1 RMS          | 3.772 A                 | Current  | Transformer Secondary1 RMS Current                                    |
| 8.  | T1 Is1 pk           | 10.656 A                | Current  | Transformer Secondary1 Peak Current                                   |
| 9.  | Avg Rectified Vin   | 370.137 V               | General  | Average Rectified Voltage for the AC Line Period                      |
| 10. | BOM Count           | 32                      | General  | Total Design BOM count                                                |
| 11. | FootPrint           | 1.347 k mm <sup>2</sup> | General  | Total Foot Print Area of BOM components                               |
| 12. | Mode                | DCM                     | General  | Conduction Mode                                                       |
| 13. | Pout                | 10.002 W                | General  | Total output power                                                    |
| 14. | Total BOM           | \$0.0                   | General  | Total BOM Cost                                                        |
| 15. | Vout Actual         | 16.538 V                | Op_Point | Vout Actual calculated based on selected voltage divider resistors    |
| 16. | Vout OP             | 5.001 V                 | Op_Point | Operational Output Voltage                                            |
| 17. | Duty Cycle          | 11.045 %                | Op_point | Duty cycle                                                            |
| 18. | Efficiency          | 81.272 %                | Op_point | Steady state efficiency                                               |
| 19. | Frequency           | 97.048 kHz              | Op_point | Switching frequency                                                   |
| 20. | IC Tj               | 32.571 degC             | Op_point | IC junction temperature                                               |
| 21. | ICThetaJA           | 70.0 degC/W             | Op_point | IC junction-to-ambient thermal resistance                             |
| 22. | IOUT_OP             | 2.0 A                   | Op_point | Iout operating point                                                  |
| 23. | M1 TJOP             | 67.004 degC             | Op_point | M1 MOSFET junction temperature                                        |
| 24. | Min Rectified Vin   | 365.512 V               | Op_point | Minimum voltage seen at rectified input                               |
| 25. | Peak Rectified Vin  | 374.763 V               | Op_point | Peak voltage seen at rectified input                                  |
| 26. | Vin_OP_RMS          | 265.0 V                 | Op_point | AC Input RMS Voltage                                                  |
| 27. | Vout p-p            | 37.297 mV               | Op_point | Peak-to-peak output ripple voltage                                    |
| 28. | Avg Bridge Diode Pd | 47.146 mW               | Power    | Average Power Dissipation in the Bridge Diode over the AC Line Period |
| 29. | Cin Pd              | 11.388 mW               | Power    | Input capacitor power dissipation                                     |
| 30. | Cout Pd             | 49.277 mW               | Power    | Output capacitor power dissipation                                    |
| 31. | Diode2 Pd           | 822.579 mW              | Power    | Diode2 power dissipation                                              |

| #   | Name           | Value      | Category | Description                                                                                |
|-----|----------------|------------|----------|--------------------------------------------------------------------------------------------|
| 32. | IC Pd          | 36.724 mW  | Power    | IC power dissipation                                                                       |
| 33. | M1 Pd          | 592.065 mW | Power    | M1 MOSFET total power dissipation                                                          |
| 34. | Total Pd       | 2.305 W    | Power    | Total Power Dissipation                                                                    |
| 35. | Xformer Pd     | 594.868 mW | Power    | Transformer power dissipation                                                              |
| 36. | Zener Pd       | 43.148 mW  | Power    | Zener power dissipation                                                                    |
| 37. | Vout Tolerance | 1.038 %    |          | Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable |

## Design Inputs

| #  | Name     | Value    | Description            |
|----|----------|----------|------------------------|
| 1. | Iout     | 2.0      | Maximum Output Current |
| 2. | VinMax   | 265.0    | Maximum input voltage  |
| 3. | VinMin   | 110.0    | Minimum input voltage  |
| 4. | Vout     | 5.0      | Output Voltage         |
| 5. | line_fsw | 50.0     | Light Output in Lumen  |
| 6. | base_pn  | UCC28701 | Base Product Number    |
| 7. | source   | AC       | Input Source Type      |
| 8. | Ta       | 30.0     | Ambient temperature    |

## Design Assistance

1. Application Hints Rbld Rbld is used to to set a minimum load for the circuit, so that in standby the output voltage does not float up. The value chosen by WEBENCH should be a good starting point but may need to be adjusted to achieve minimum power dissipation at standby as well. Rlc Rlc provides the function of feed-forward line compensation to eliminate change in IPP due to change in di/dt and the propagation delay of the internal comparator and MOSFET turn-off time. For best results the chosen value may need to be adjusted based on board, FET and transformer parasitics. Rfbl & Rfbb The feedback resistors will set the output voltage of the circuit. The values chosen may need to be finely tuned based on the final Transformer turns ratios and the voltage across the output diode at close to zero current. Cdd Cdd supplies the device operating current until the output of the converter reaches the target minimum operating voltage. The value calculated by WEBENCH for Cdd is a good starting point since it assumes that the output current of the Flyback is available to charge the output capacitance until the minimum output voltage is achieved, but may need to be adjusted. Part Description The UCC28700 family of flyback power supply controllers provides Constant-Voltage (CV) and Constant-Current (CC) output regulation. Primary-Side Regulation (PSR) eliminates the use of an Opto-Coupler. Please see the datasheet for further design guidance. <http://www.ti.com/lit/ds/symlink/ucc28700.pdf>

2. **UCC28701** Product Folder : <http://www.ti.com/product/UCC28701> : contains the data sheet and other resources.

Texas Instruments' WEBENCH simulation tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Simulations are created using Texas Instruments' published specifications as well as the published specifications of other device manufacturers. While Texas Instruments does update this information periodically, this information may not be current at the time the simulation is built. Texas Instruments does not warrant the accuracy or completeness of the specifications or any information contained therein. Texas Instruments does not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. Texas Instruments does not warrant that the designs are production worthy.

**You should completely validate and test your design implementation to confirm the system functionality for your application prior to production.**

Use of Texas Instruments' WEBENCH simulation tools is subject to [Texas Instruments' Site Terms and Conditions of Use](#). Prototype boards based on WEBENCH created designs are provided AS IS without warranty of any kind for evaluation and testing purposes and are subject to the terms of the [Evaluation License Agreement](#).