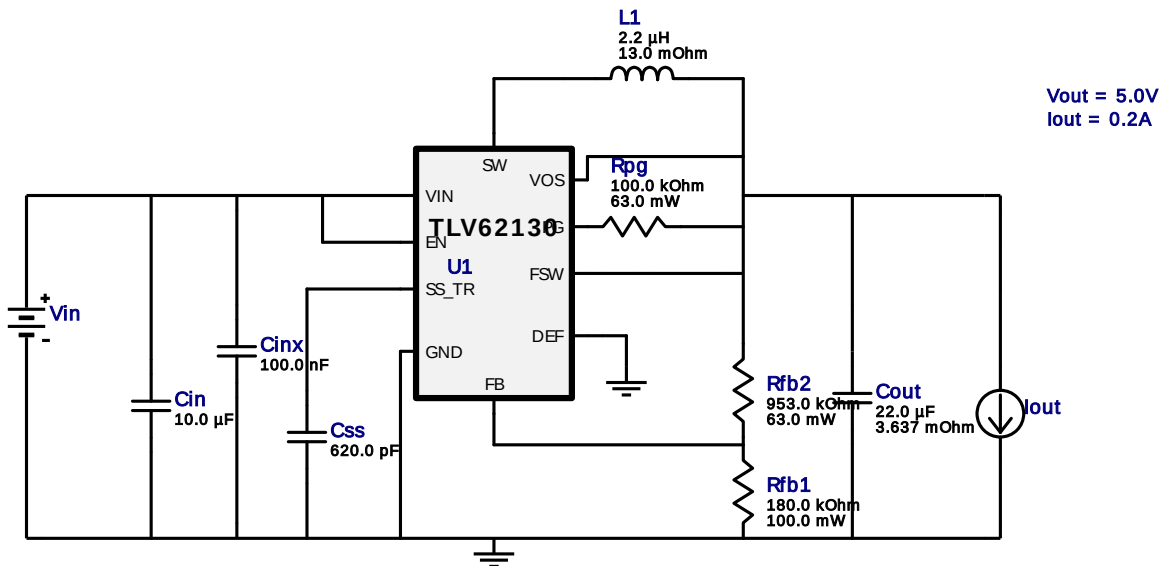


WEBENCH® Design Report





Design : 2425056/76 TLV62130RGTR
TLV62130RGTR 6.0V-15.0V to 5.00V @ 0.2A















Electrical BOM


#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	Cin	Taiyo Yuden	TMK316BJ106KL-T Series= X5R	Cap= 10.0 uF VDC= 25.0 V IRMS= 0.0 A	1	\$0.05	 1206 11 mm ²
2.	Cinx	Kemet	C0603C104K3RACTU Series= X7R	Cap= 100.0 nF VDC= 25.0 V IRMS= 0.0 A	1	\$0.01	 0603 5 mm ²
3.	Cout	MuRata	GRM31CR61A226ME19L Series= X5R	Cap= 22.0 uF ESR= 3.637 mOhm VDC= 10.0 V IRMS= 3.56456 A	1	\$0.08	 1206_190 11 mm ²
4.	Css	Samsung Electro-Mechanics	CL21C621JBCNNNC Series= C0G/NP0	Cap= 620.0 pF VDC= 50.0 V IRMS= 0.0 A	1	\$0.01	 0805 7 mm ²
5.	L1	Bourns	SRN8040-2R2Y	L= 2.2 uH DCR= 13.0 mOhm	1	\$0.22	 SRN8040 100 mm ²
6.	Rfb1	Yageo America	RC0603FR-07180KL Series= ?	Res= 180.0 kOhm Power= 100.0 mW Tolerance= 1.0%	1	\$0.01	 0603 5 mm ²
7.	Rfb2	Vishay-Dale	CRCW0402953KFKED Series= CRCW..e3	Res= 953.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
8.	Rpg	Vishay-Dale	CRCW0402100KFKED Series= CRCW..e3	Res= 100.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
9.	U1	Texas Instruments	TLV62130RGTR	Switcher	1	\$0.72	 S-PVQFN-N16 17 mm ²

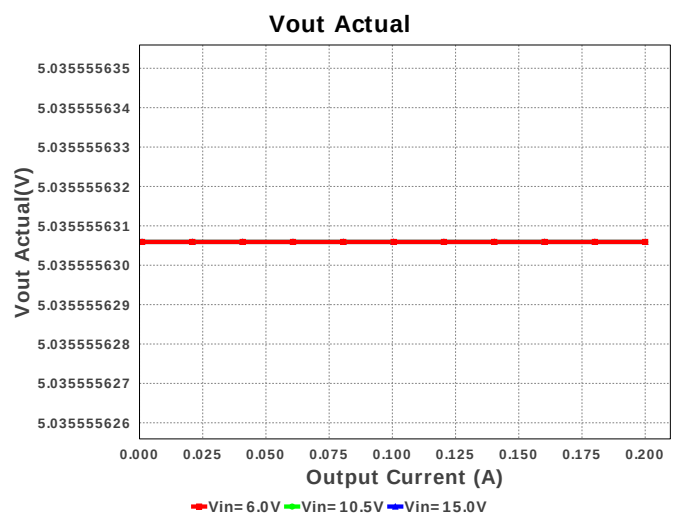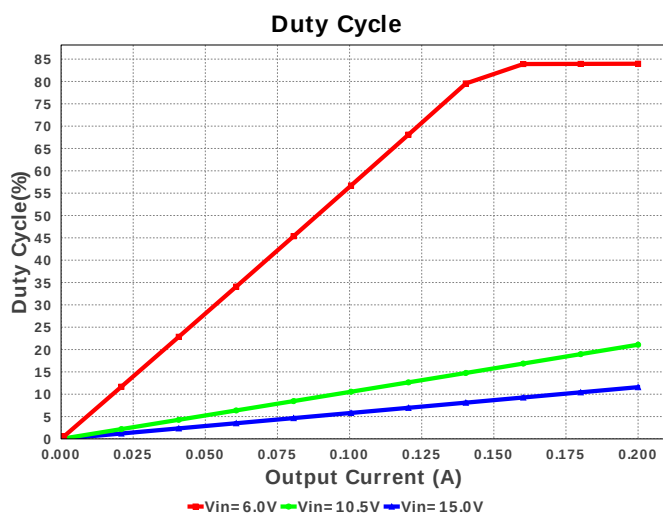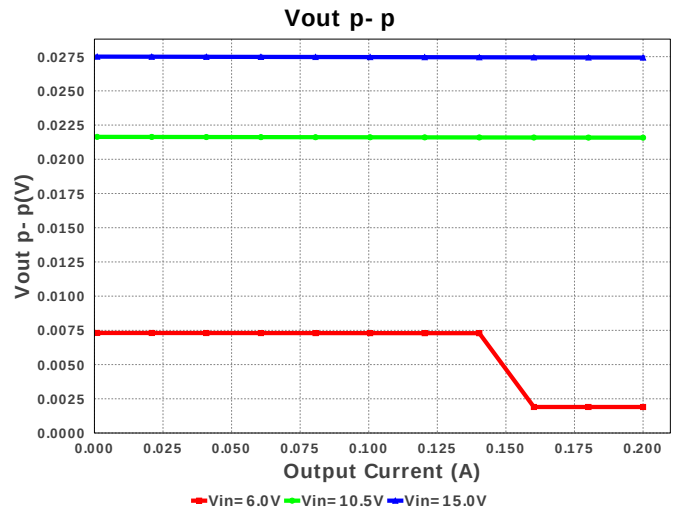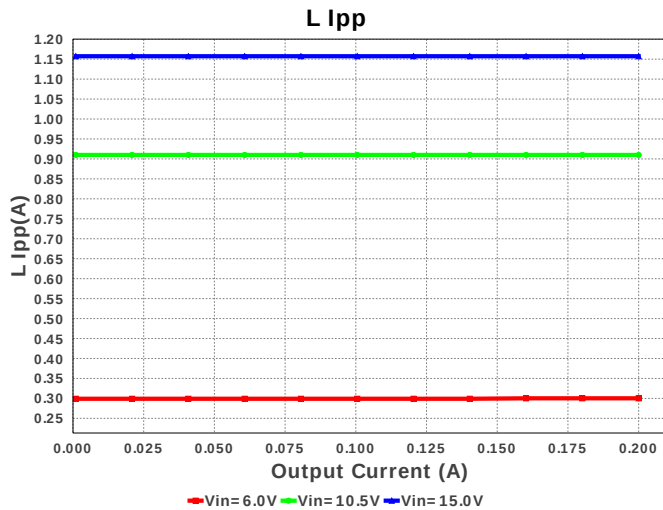

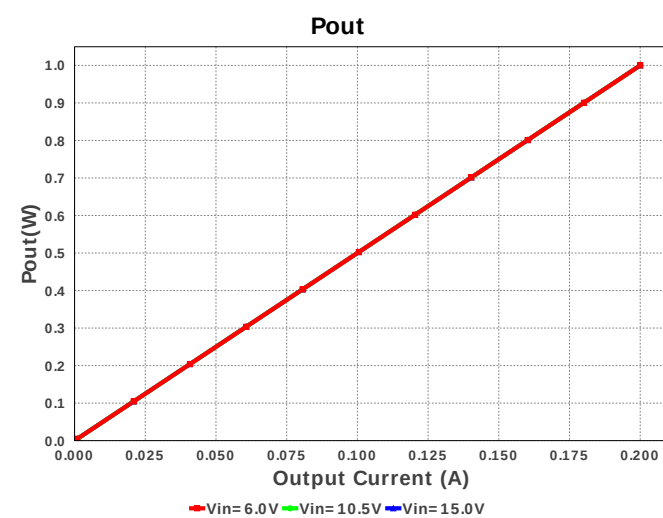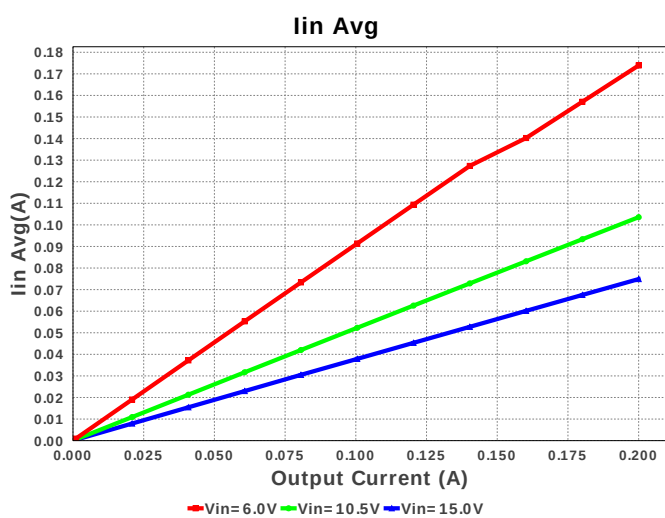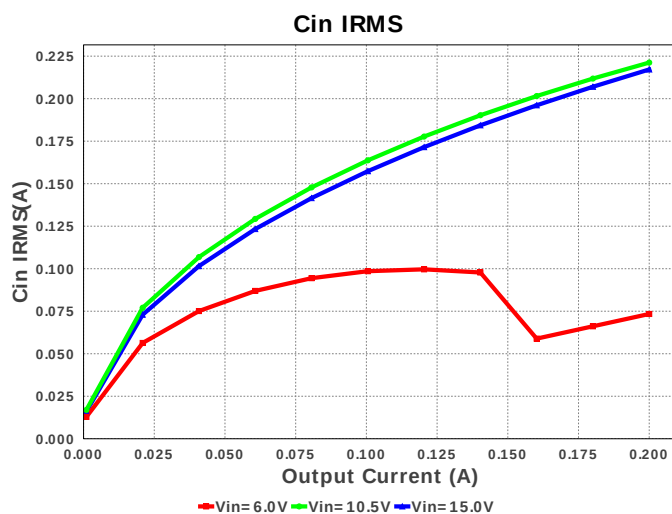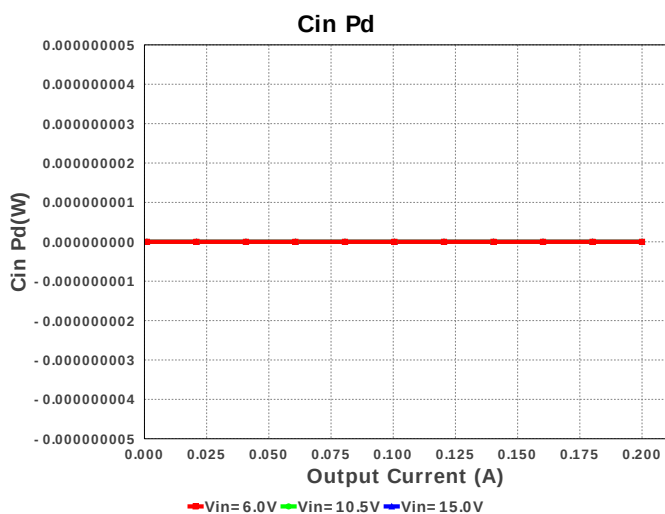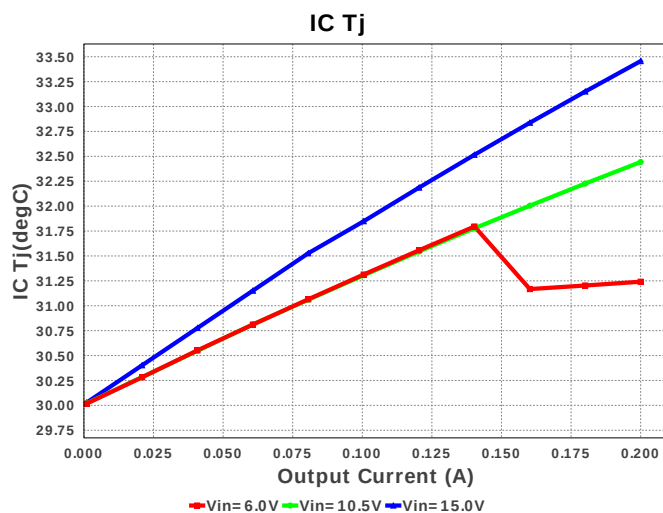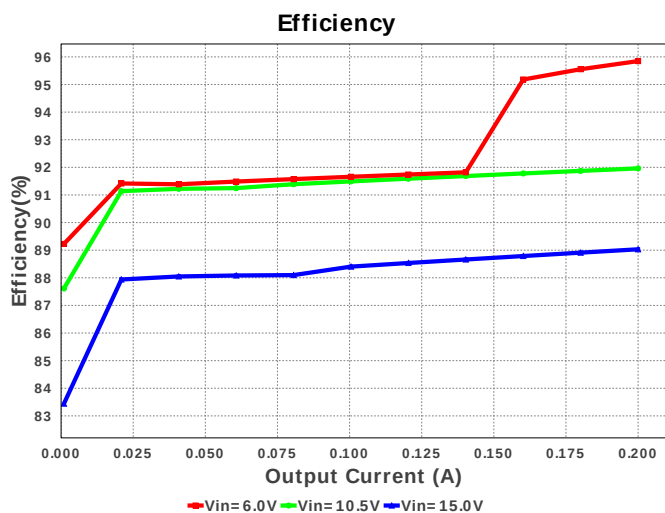

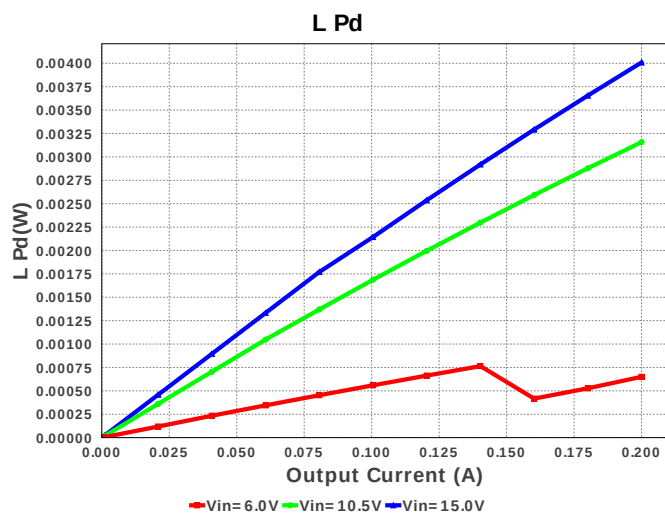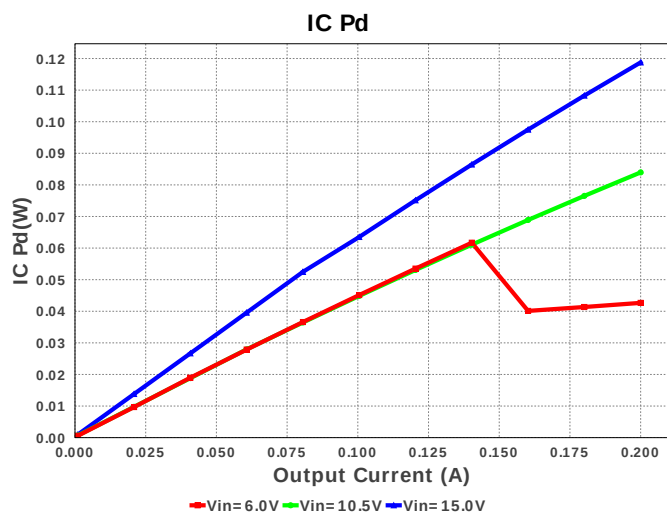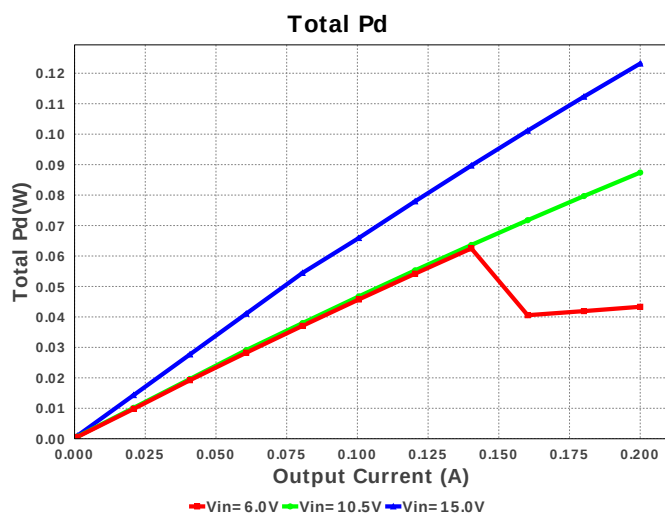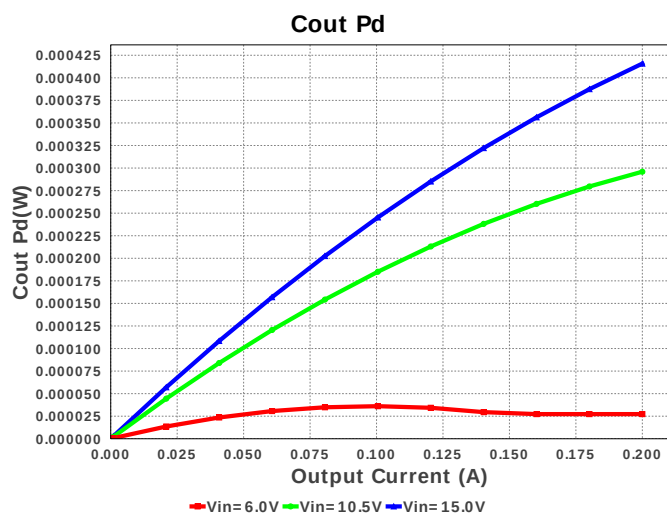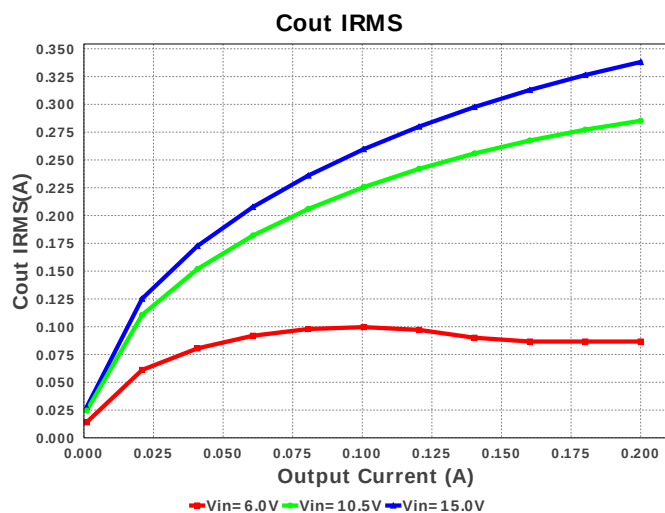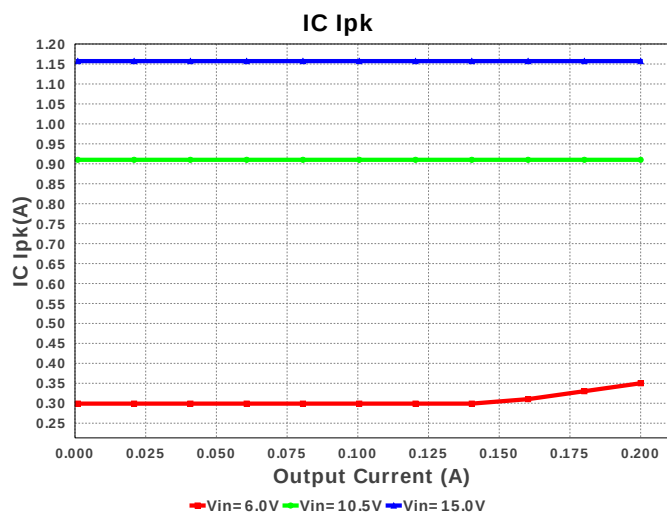

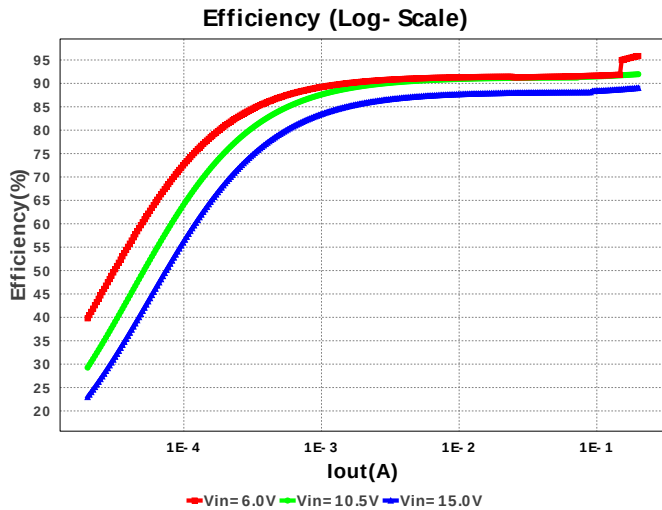

Operating Values

#	Name	Value	Category	Description
1.	Cin IRMS	217.169 mA	Current	Input capacitor RMS ripple current
2.	Cout IRMS	338.112 mA	Current	Output capacitor RMS ripple current
3.	IC Ipk	1.157 A	Current	Peak switch current in IC
4.	Iin Avg	74.88 mA	Current	Average input current
5.	L Ipp	1.157 A	Current	Peak-to-peak inductor ripple current
6.	BOM Count	9	General	Total Design BOM count
7.	FootPrint	161.0 mm ²	General	Total Foot Print Area of BOM components
8.	Frequency	454.788 kHz	General	Switching frequency
9.	Mode	DCM	General	Conduction Mode
10.	Pout	1.0 W	General	Total output power
11.	Total BOM	\$1.12	General	Total BOM Cost
12.	Vout Actual	5.036 V	Op_Point	Vout Actual calculated based on selected voltage divider resistors
13.	Vout OP	5.0 V	Op_Point	Operational Output Voltage
14.	Duty Cycle	11.579 %	Op_point	Duty cycle
15.	Efficiency	89.032 %	Op_point	Steady state efficiency
16.	IC Tj	33.456 degC	Op_point	IC junction temperature
17.	ICThetaJA	29.1 degC/W	Op_point	IC junction-to-ambient thermal resistance
18.	IOUT_OP	200.0 mA	Op_point	Iout operating point
19.	VIN_OP	15.0 V	Op_point	Vin operating point
20.	Vout p-p	27.432 mV	Op_point	Peak-to-peak output ripple voltage
21.	Cin Pd	0.0 W	Power	Input capacitor power dissipation
22.	Cout Pd	415.781 μ W	Power	Output capacitor power dissipation
23.	IC Pd	118.769 mW	Power	IC power dissipation
24.	L Pd	4.009 mW	Power	Inductor power dissipation
25.	Total Pd	123.193 mW	Power	Total Power Dissipation
26.	Vout Tolerance	4.242 %		Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable

Design Inputs

#	Name	Value	Description
1.	Iout	200.0 m	Maximum Output Current
2.	VinMax	15.0	Maximum input voltage
3.	VinMin	6.0	Minimum input voltage
4.	Vout	5.0	Output Voltage
5.	base_pn	TLV62130	Base Product Number
6.	source	DC	Input Source Type
7.	Ta	30.0	Ambient temperature

Design Assistance

1. Feature Highlights: DCS-Control(TM) Architecture with upto 3A output current, 4V to 17V Input Voltage Range, Adjustable output voltage from 0.9V to 6V>Selectable operating frequency, Optional Softstart Capacitor for slow startup, Tracking, Pin selectable output voltage (nominal, +5%) Seamless Power Save Mode for Light Load Efficiency, Power Good Output, 100% Duty Cycle mode, Short Circuit Protection, Thermal Shutdown

2. **TLV62130** Product Folder : <http://www.ti.com/product/TLV62130> : contains the data sheet and other resources.

Texas Instruments' WEBENCH simulation tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Simulations are created using Texas Instruments' published specifications as well as the published specifications of other device manufacturers. While Texas Instruments does update this information periodically, this information may not be current at the time the simulation is built. Texas Instruments does not warrant the accuracy or completeness of the specifications or any information contained therein. Texas Instruments does not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. Texas Instruments does not warrant that the designs are production worthy.

You should completely validate and test your design implementation to confirm the system functionality for your application prior to production.

Use of Texas Instruments' WEBENCH simulation tools is subject to [Texas Instruments' Site Terms and Conditions of Use](#). Prototype boards based on WEBENCH created designs are provided AS IS without warranty of any kind for evaluation and testing purposes and are subject to the terms of the [Evaluation License Agreement](#).