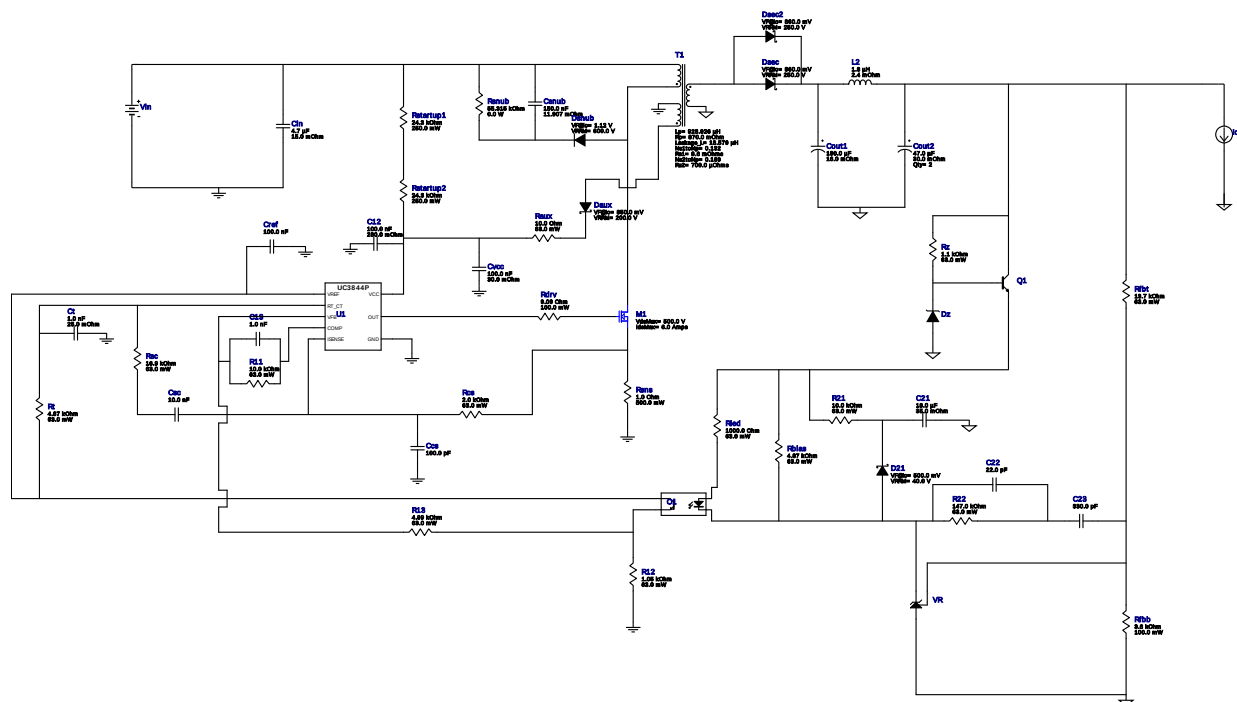



WEBENCH® Design Report



Design : 4354914/3 UC3844N
UC3844N 150.0V-280.0V to 12.00V @ 2.0A






Electrical BOM







#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	C12	AVX	08053C104KAT2A Series= X7R	Cap= 100.0 nF ESR= 280.0 mOhm VDC= 25.0 V IRMS= 0.0 A	1	\$0.01	 0805 7 mm²
2.	C13	MuRata	GRM033R71C102KA01D Series= X7R	Cap= 1.0 nF VDC= 16.0 V IRMS= 0.0 A	1	\$0.01	 0201 2 mm²
3.	C21	Panasonic	50SVPF18M Series= ?	Cap= 18.0 uF ESR= 35.0 mOhm VDC= 50.0 V IRMS= 2.7 A	1	\$0.53	 CAPSMT_62_E7 106 mm²
4.	C22	Kemet	C0805C220K3GACTU Series= C0G/NP0	Cap= 22.0 pF VDC= 25.0 V IRMS= 0.0 A	1	\$0.01	 0805 7 mm²
5.	C23	MuRata	GRM033R71C331KA01D Series= X7R	Cap= 330.0 pF VDC= 16.0 V IRMS= 0.0 A	1	\$0.01	 0201 2 mm²
6.	Ccs	Kemet	C0201C101J3GACTU Series= C0G/NP0	Cap= 100.0 pF VDC= 5.0 V IRMS= 0.0 A	1	\$0.01	 0201 2 mm²






 
#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
7.	Cin	TDK	B32924D3475K Series= B32924	Cap= 4.7 uF ESR= 15.0 mOhm VDC= 630.0 V IRMS= 457.0 mA	1	\$1.68	 B32924_31mm 770 mm ²
8.	Cout1	Panasonic	25SVPF180M Series= ?	Cap= 180.0 uF ESR= 16.0 mOhm VDC= 25.0 V IRMS= 4.65 A	1	\$0.61	 CAPSMT_62_E12 106 mm ²
9.	Cout2	Panasonic	25SVPF47M Series= ?	Cap= 47.0 uF ESR= 30.0 mOhm VDC= 25.0 V IRMS= 2.8 A	2	\$0.43	 CAPSMT_62_F61 74 mm ²
10.	Cref	MuRata	GRM155R61C104KA88D Series= X5R	Cap= 100.0 nF VDC= 16.0 V IRMS= 0.0 A	1	\$0.01	 0402 3 mm ²
11.	Csc	MuRata	GRM033R60J103KA01D Series= X5R	Cap= 10.0 nF VDC= 6.3 V IRMS= 0.0 A	1	\$0.01	 0201 2 mm ²
12.	Csnub	TDK	C3225X7T2J154K Series= X7T	Cap= 150.0 nF ESR= 11.907 mOhm VDC= 630.0 V IRMS= 0.0 A	1	\$0.19	 1210 15 mm ²
13.	Ct	Kemet	C0805C102J5GACTU Series= C0G/NP0	Cap= 1.0 nF ESR= 25.0 mOhm VDC= 50.0 V IRMS= 1.71 A	1	\$0.01	 0805 7 mm ²
14.	Cvcc	MuRata	GRM188R71E104KA01D Series= X7R	Cap= 100.0 nF ESR= 30.0 mOhm VDC= 25.0 V IRMS= 1.51 A	1	\$0.01	 0603 5 mm ²
15.	D21	Vishay-Semiconductor	SS14-E3/61T	VF@Io= 500.0 mV VRRM= 40.0 V	1	\$0.08	 SMA 37 mm ²
16.	Daux	Diodes Inc.	DFLS1200-7	VF@Io= 850.0 mV VRRM= 200.0 V	1	\$0.21	 PowerDI123 13 mm ²
17.	Dsec	ON Semiconductor	MBRB40250TG	VF@Io= 860.0 mV VRRM= 250.0 V	1	\$0.94	 DDPAK 210 mm ²
18.	Dsec2	ON Semiconductor	MBRB40250TG	VF@Io= 860.0 mV VRRM= 250.0 V	1	\$0.94	 DDPAK 210 mm ²
19.	Dsnub	Bourns	CD214C-F3600	VF@Io= 1.12 V VRRM= 600.0 V	1	\$0.18	 SMC 83 mm ²
20.	Dz	ON Semiconductor	BZX84C9V1LT1G	Zener	1	\$0.02	 SOT-23 14 mm ²





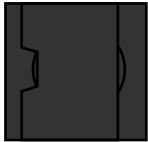
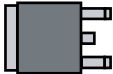
#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
21.	L2	Coilcraft	SER1360-182KLB	L= 1.8 μ H DCR= 2.4 mOhm	1	\$0.72	 SER1360 225 mm ²
22.	M1	Fairchild Semiconductor	FDD6N50TM	VdsMax= 500.0 V IdsMax= 6.0 Amps	1	\$0.47	 DPAK 102 mm ²
23.	O1	Vishay-Semiconductor	TCMT1107	Optocoupler	1	\$0.21	 SOP-4 44 mm ²
24.	Q1	ON Semiconductor	BC846BLT1G	Bipolar Transistor	1	\$0.02	 SOT-23 14 mm ²
25.	R11	Vishay-Dale	CRCW040210K0FKED Series= CRCW..e3	Res= 10.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
26.	R12	Vishay-Dale	CRCW04021K05FKED Series= CRCW..e3	Res= 1.05 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
27.	R13	Vishay-Dale	CRCW04024K99FKED Series= CRCW..e3	Res= 4.99 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
28.	R21	Vishay-Dale	CRCW040210K0FKED Series= CRCW..e3	Res= 10.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
29.	R22	Vishay-Dale	CRCW0402147KFKED Series= CRCW..e3	Res= 147.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
30.	Raux	Vishay-Dale	CRCW040210R0FKED Series= CRCW..e3	Res= 10.0 Ohm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
31.	Rbias	Vishay-Dale	CRCW04024K87FKED Series= CRCW..e3	Res= 4.87 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
32.	Rcs	Vishay-Dale	CRCW04022K00FKED Series= CRCW..e3	Res= 2.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
33.	Rdrv	Vishay-Dale	CRCW06039R09FKEA Series= CRCW..e3	Res= 9.09 Ohm Power= 100.0 mW Tolerance= 1.0%	1	\$0.01	 0603 5 mm ²
34.	Rfbb	Yageo America	RC0603FR-073K6L Series= ?	Res= 3.6 kOhm Power= 100.0 mW Tolerance= 1.0%	1	\$0.01	 0603 5 mm ²
35.	Rfbt	Vishay-Dale	CRCW040213K7FKED Series= CRCW..e3	Res= 13.7 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
36.	Rled	Vishay-Dale	CRCW04021K00FKED Series= CRCW..e3	Res= 1000.0 Ohm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
37.	Rsc	Vishay-Dale	CRCW040216K9FKED Series= CRCW..e3	Res= 16.9 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
38.	Rsns	Stackpole Electronics Inc	CSR1206FT1R00 Series= ?	Res= 1.0 Ohm Power= 500.0 mW Tolerance= 1.0%	1	\$0.04	 1206 11 mm ²
39.	Rsns	CUSTOM	CUSTOM Series= ?	Res= 55.315 kOhm Power= 0.0 W Tolerance= 0.0%	1	NA	CUSTOM 0 mm ²






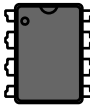
#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
40.	Rstartup1	Panasonic	ERJ-8ENF2432V Series= ERJ-8E	Res= 24.3 kOhm Power= 250.0 mW Tolerance= 1.0%	1	\$0.01	 1206 11 mm ²
41.	Rstartup2	Panasonic	ERJ-8ENF2432V Series= ERJ-8E	Res= 24.3 kOhm Power= 250.0 mW Tolerance= 1.0%	1	\$0.01	 1206 11 mm ²
42.	Rt	Vishay-Dale	CRCW04024K87FKED Series= CRCW..e3	Res= 4.87 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
43.	Rz	Vishay-Dale	CRCW04021K10FKED Series= CRCW..e3	Res= 1.1 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
44.	T1	CUSTOM	CUSTOM	Lp= 928.926 μ H Rp= 870.0 mOhm Leakage_L= 18.579 μ H Ns1toNp= 0.132 Rs1= 8.6 mOhms Ns2toNp= 0.169 Rs2= 700.0 μ Ohms	1	NA	CUSTOM 0 mm ²
45.	U1	Texas Instruments	UC3844N	Switcher	1	\$0.56	 P0008A 116 mm ²
46.	VR	Texas Instruments	TL431AIDBVR	Voltage References	1	\$0.07	 R-PDSO-G3 16 mm ²

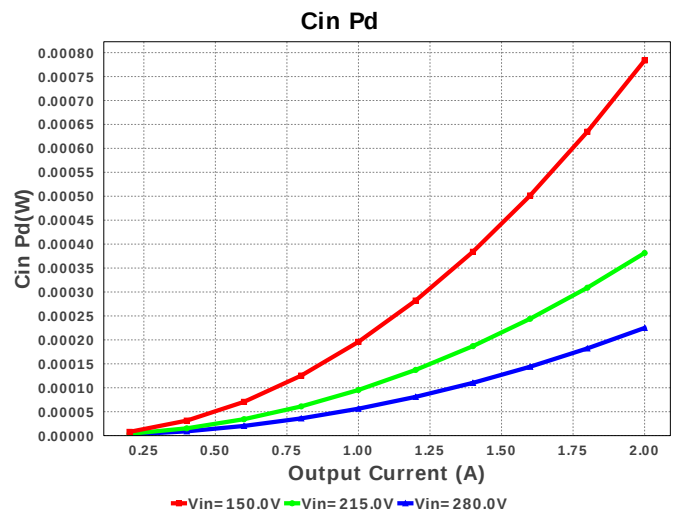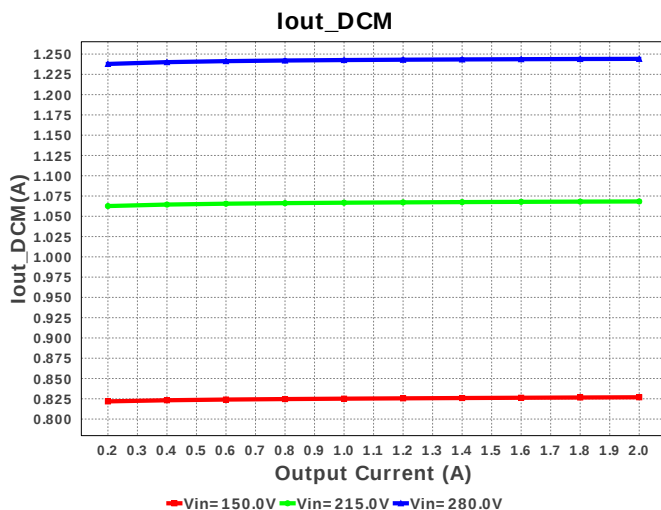

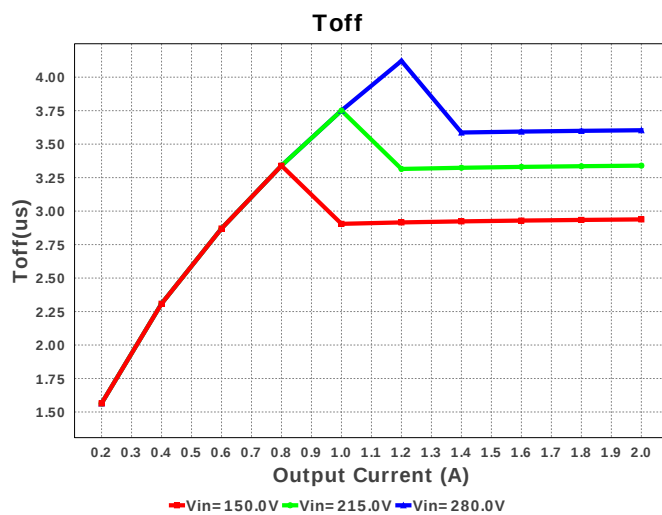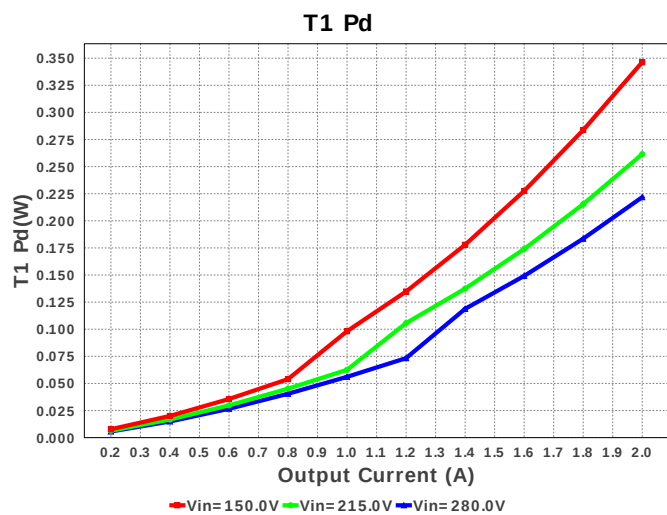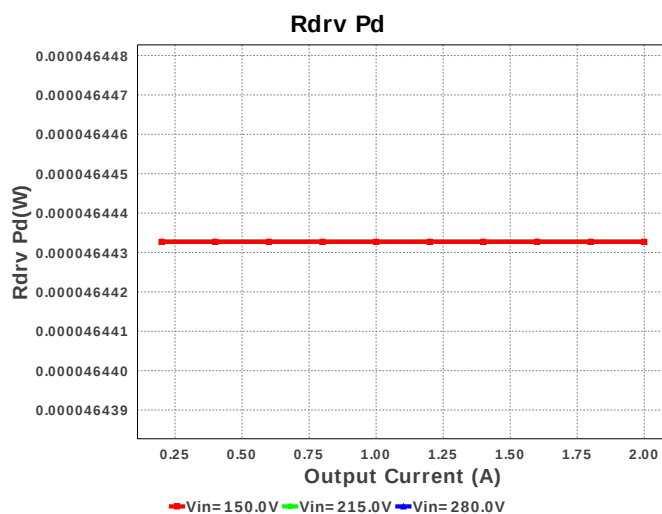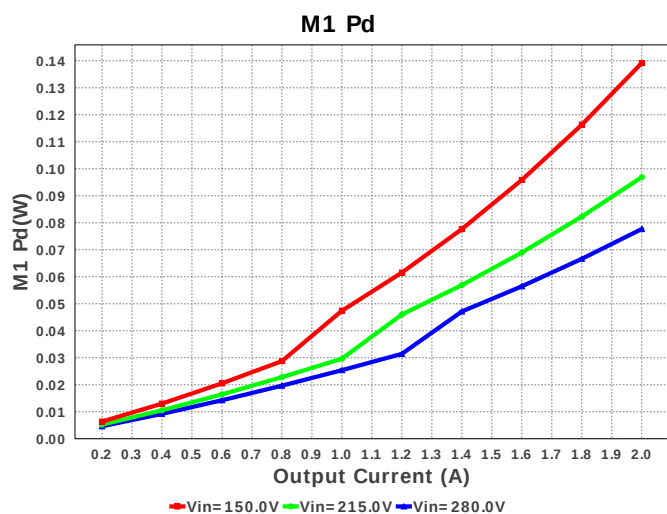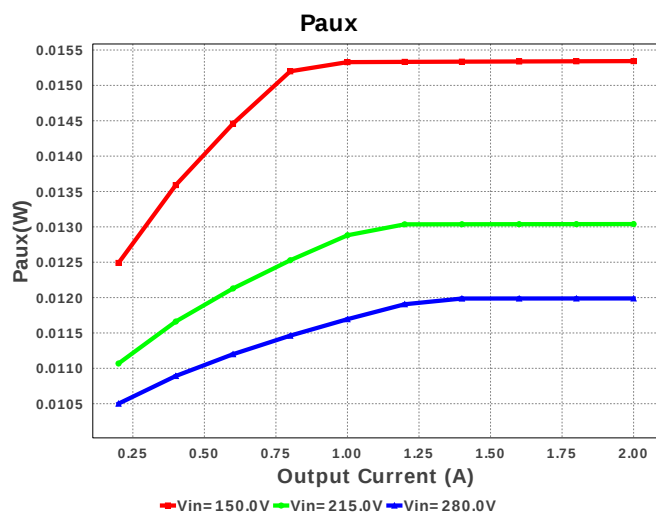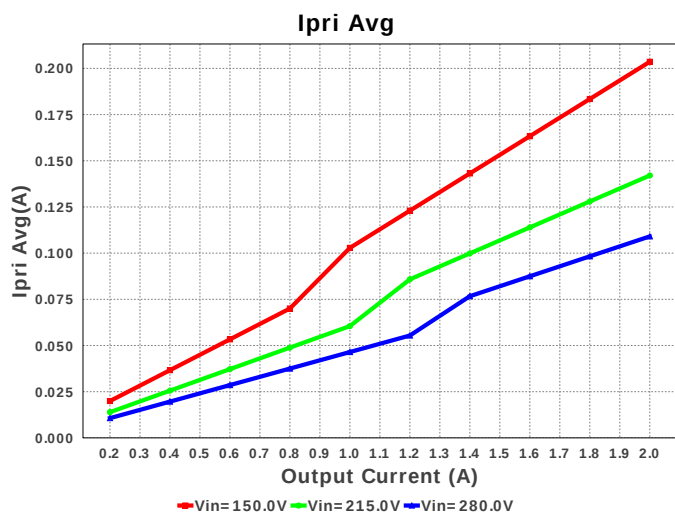


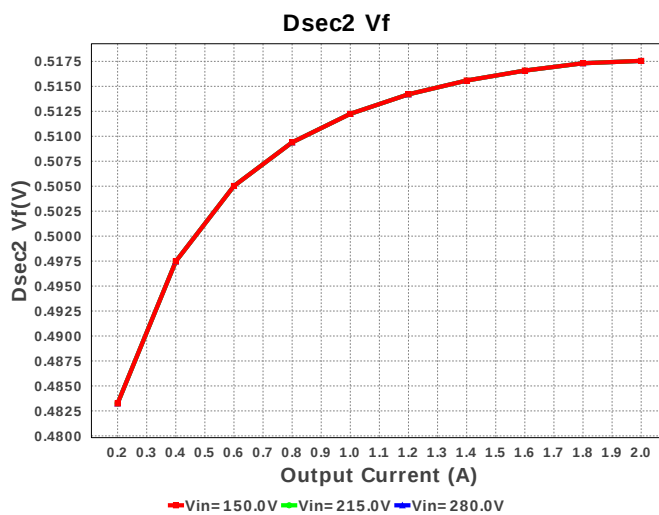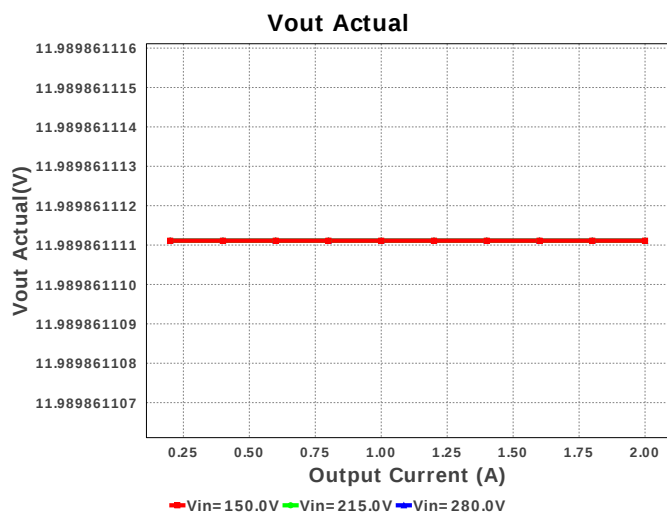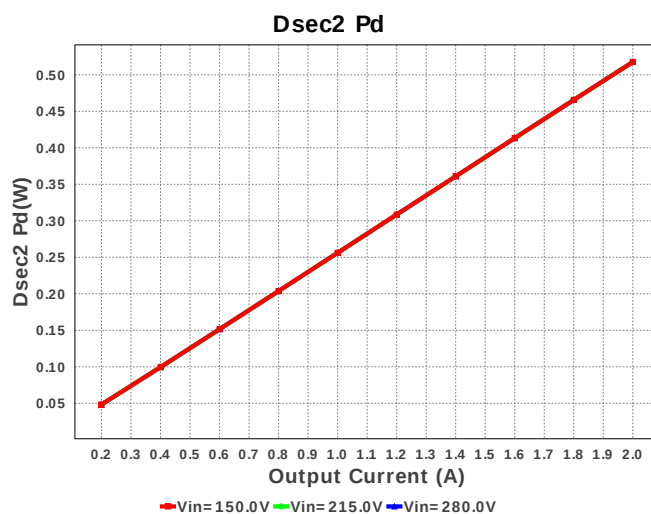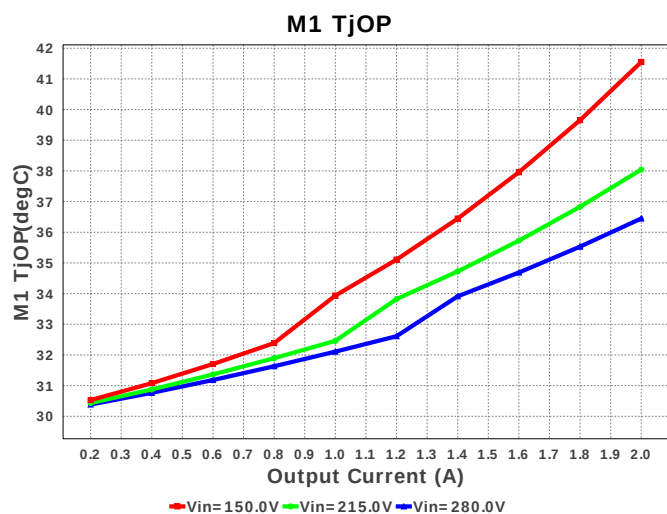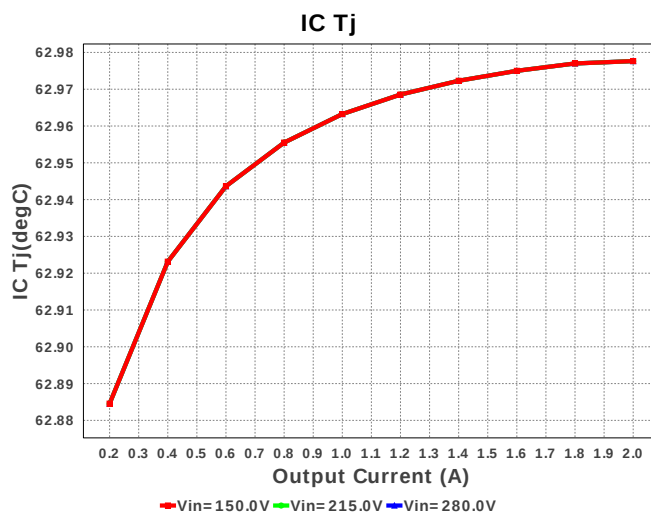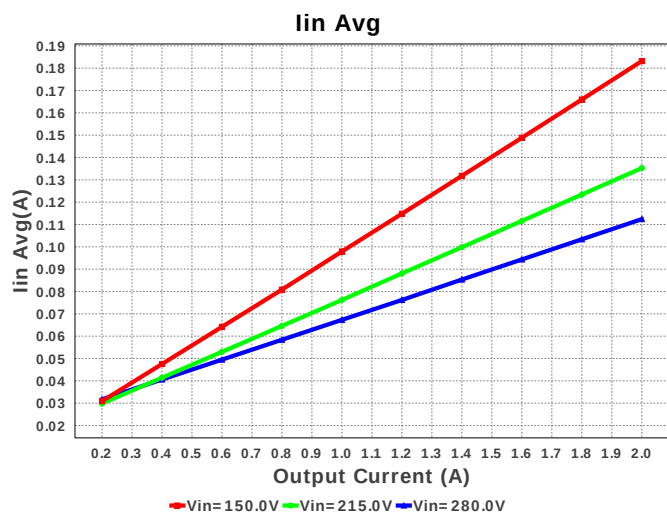

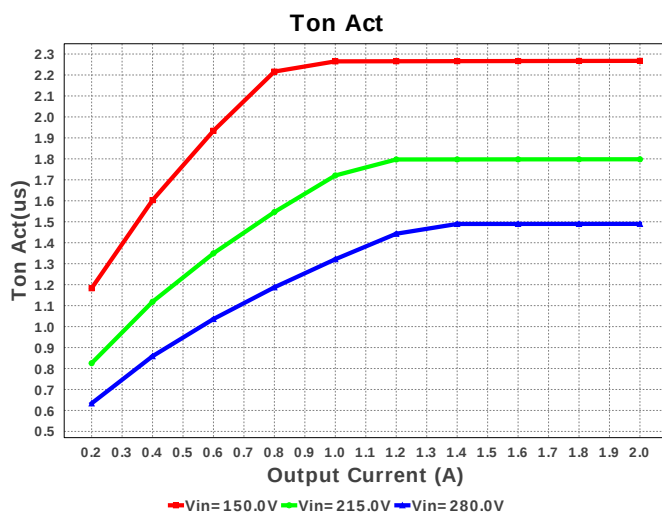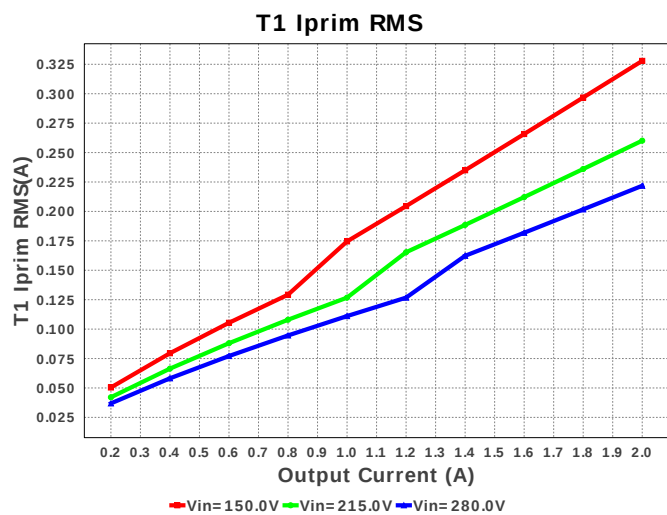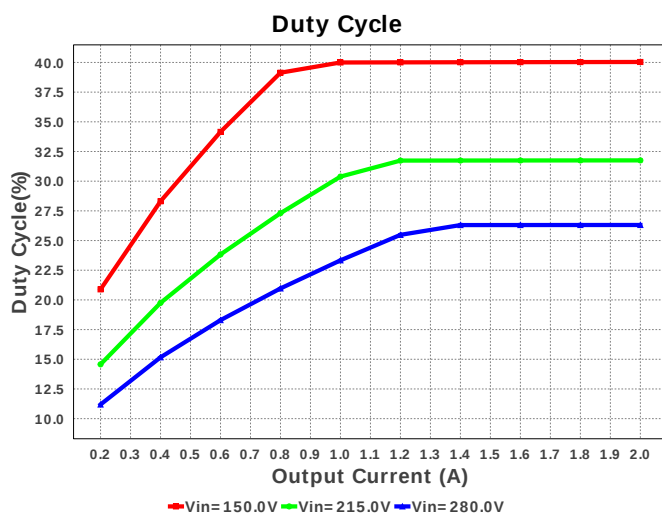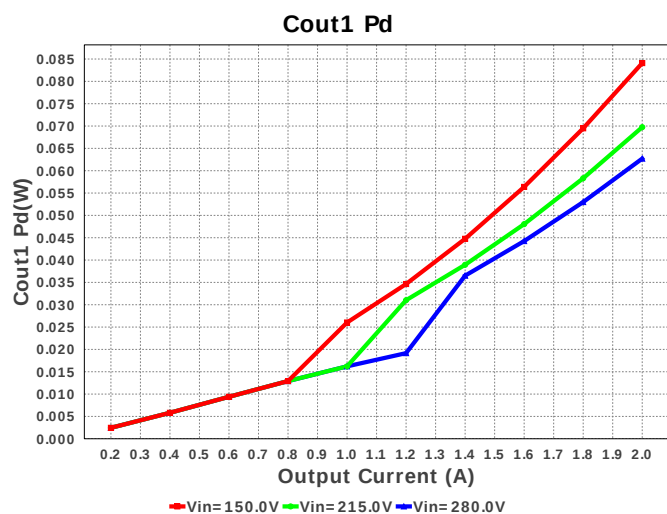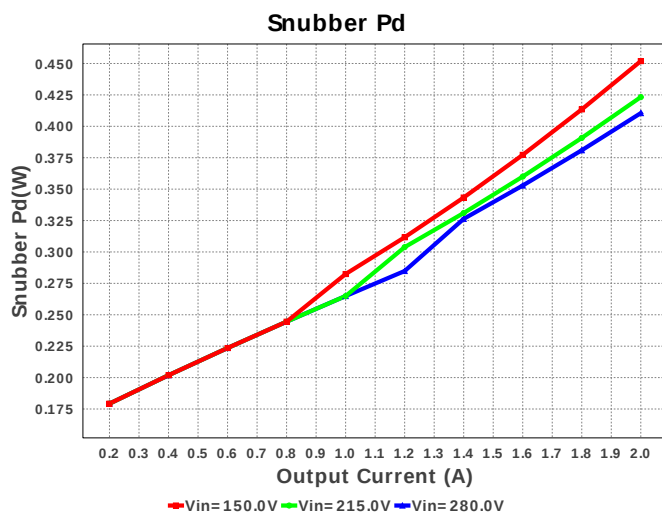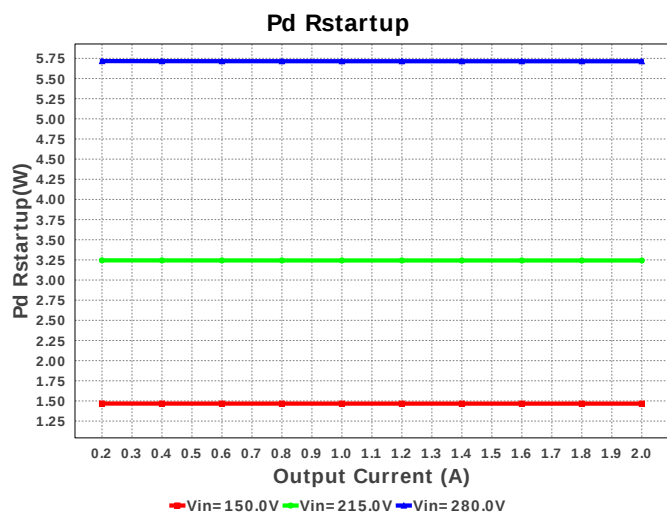


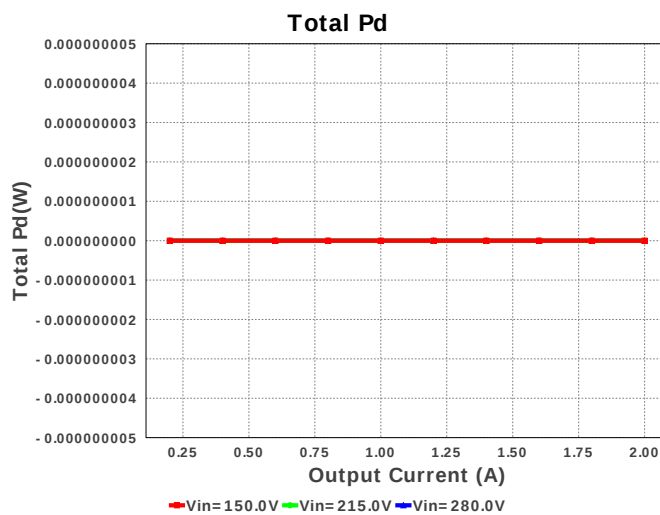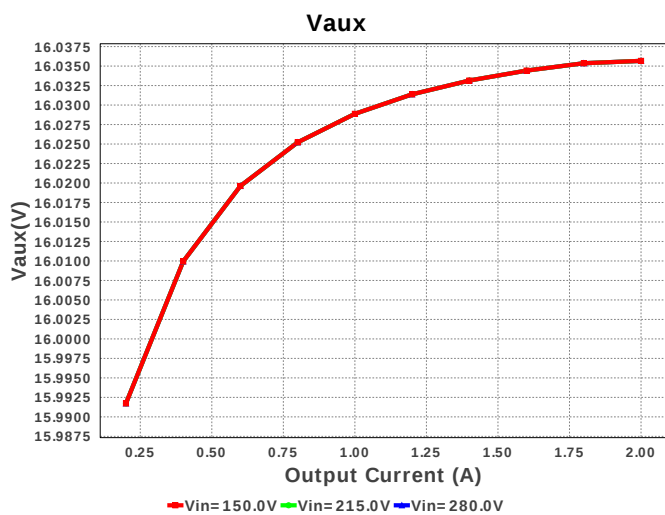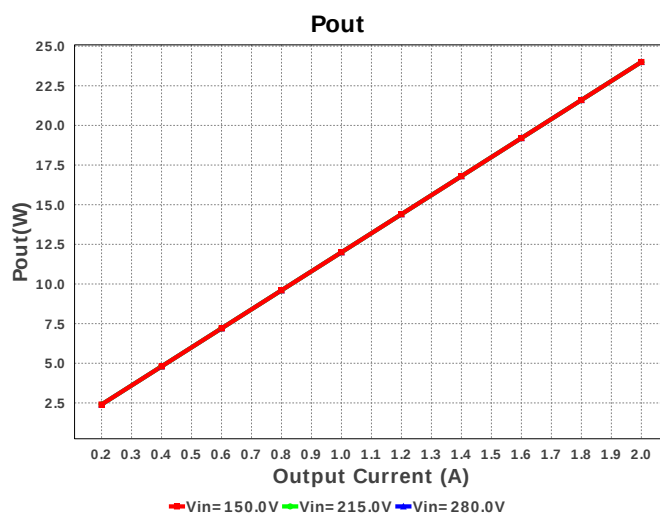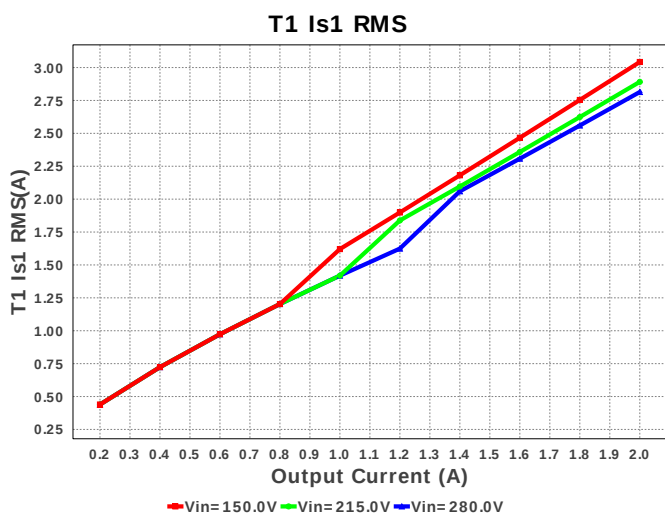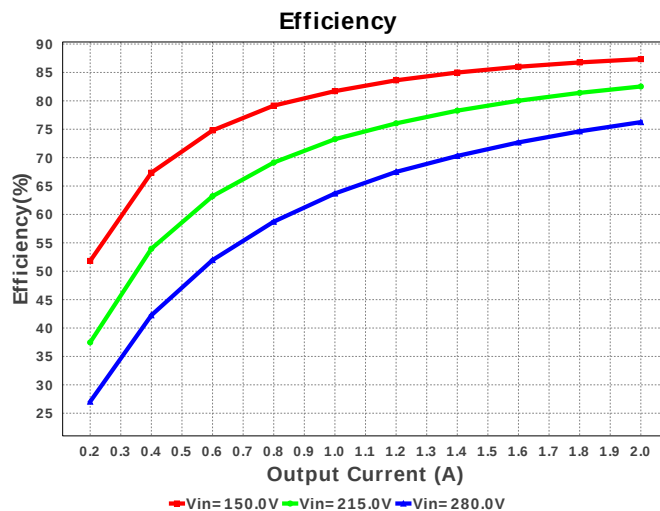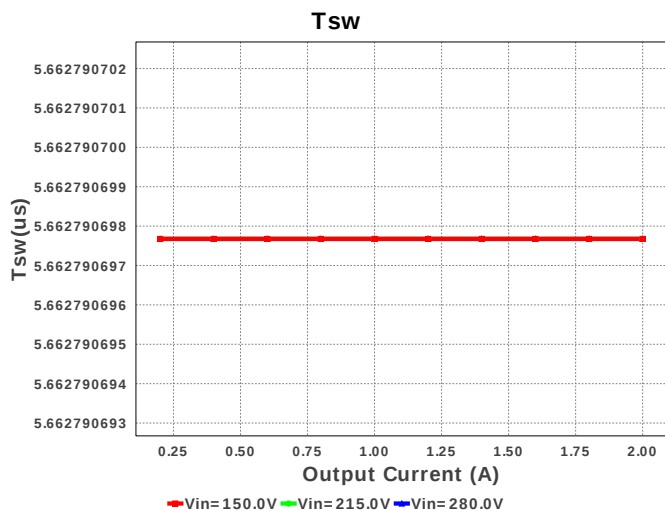


T1 Is1 pk

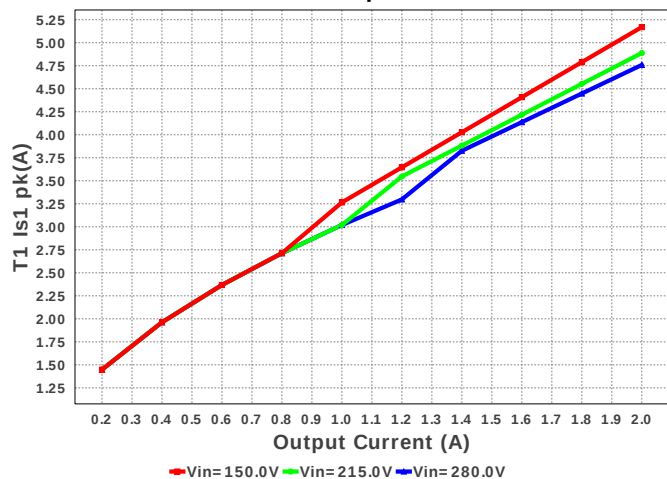


Dsec Pd

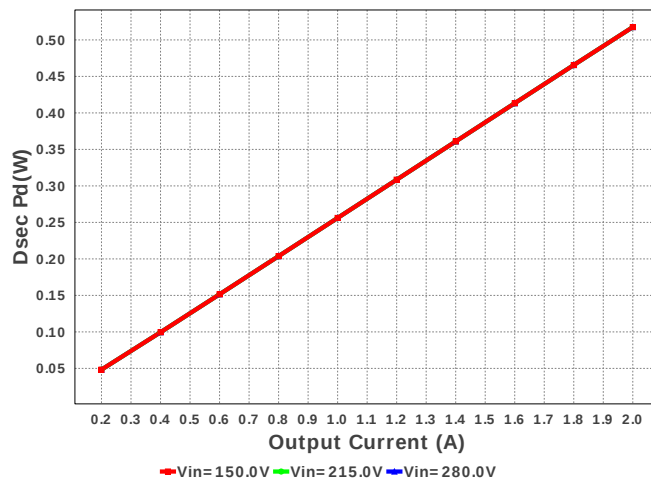


Tdead

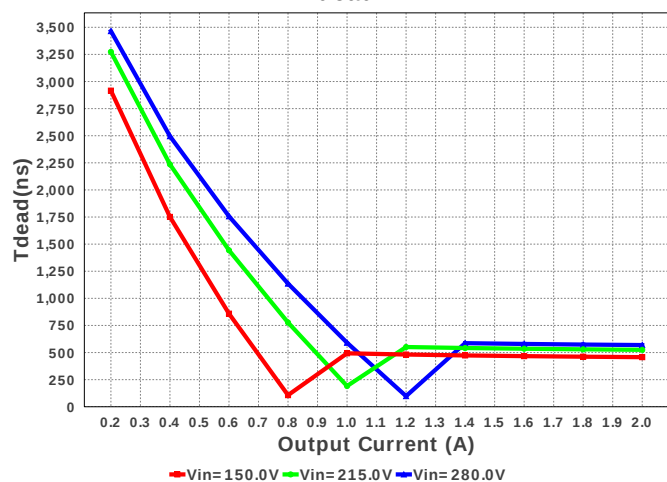


IC Pd






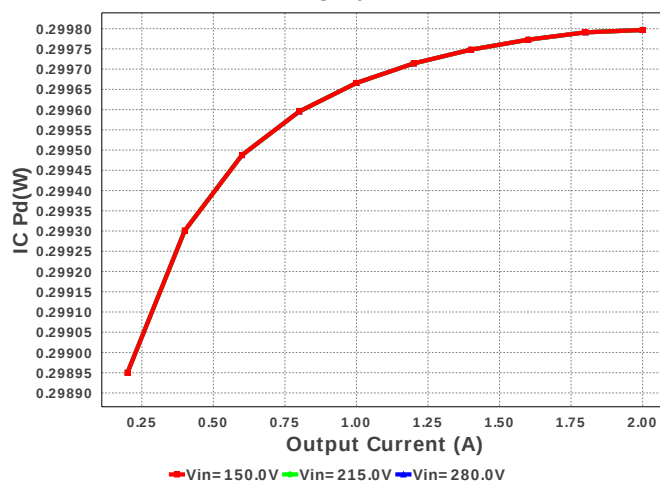



Cout1 IRMS

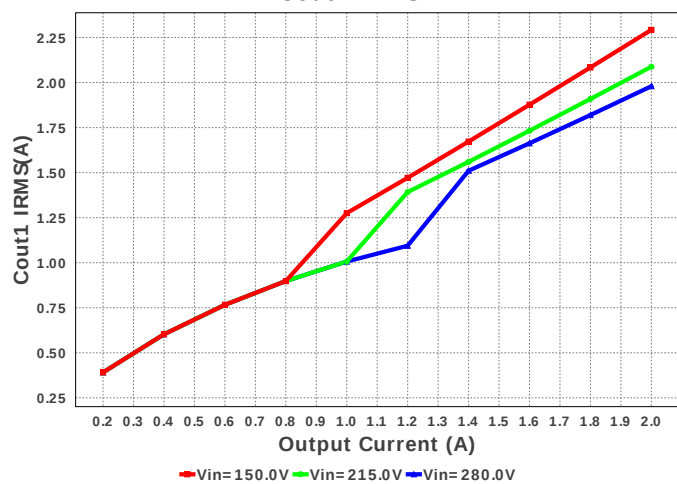

Dsec Vf

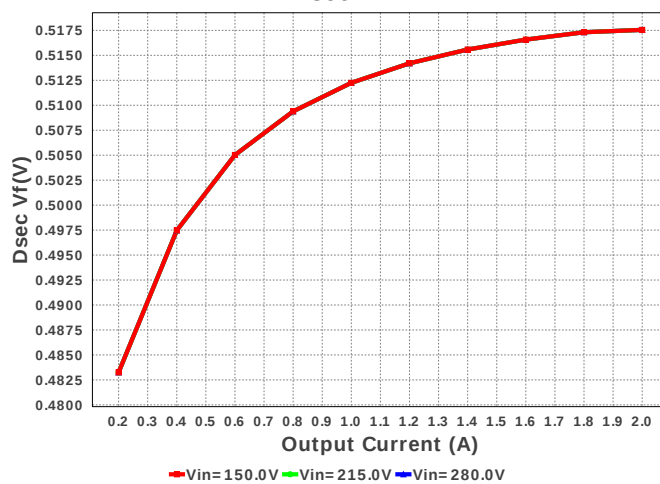

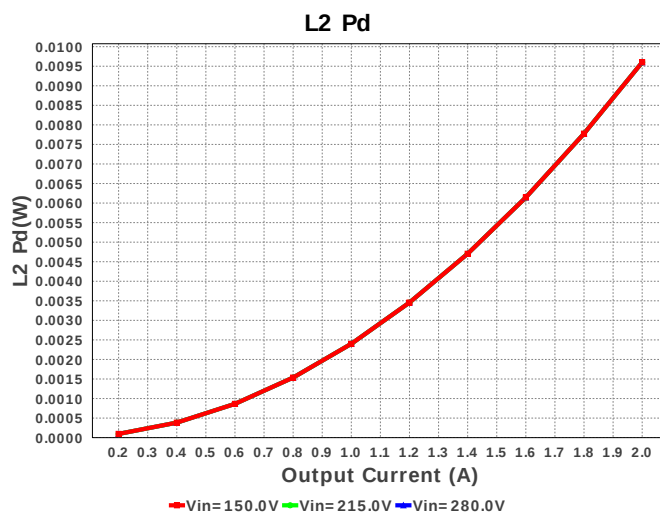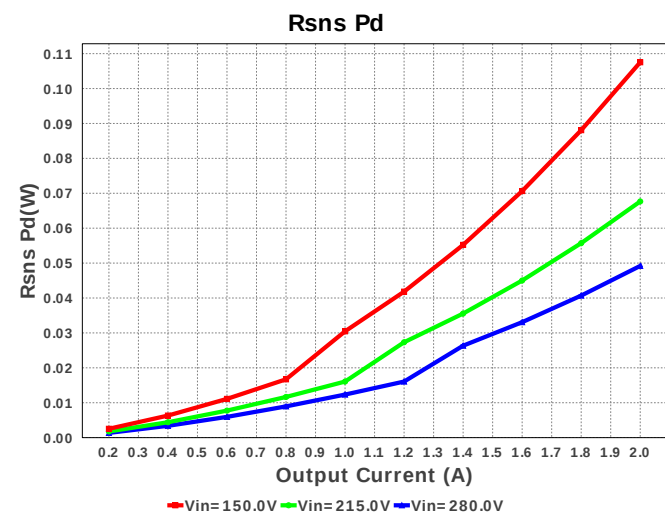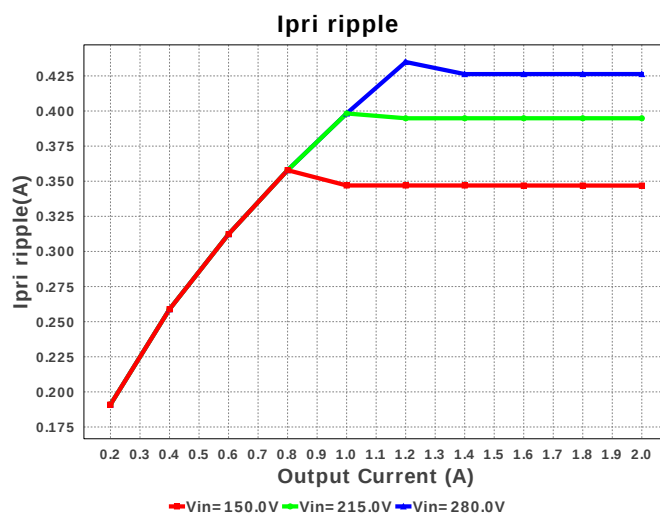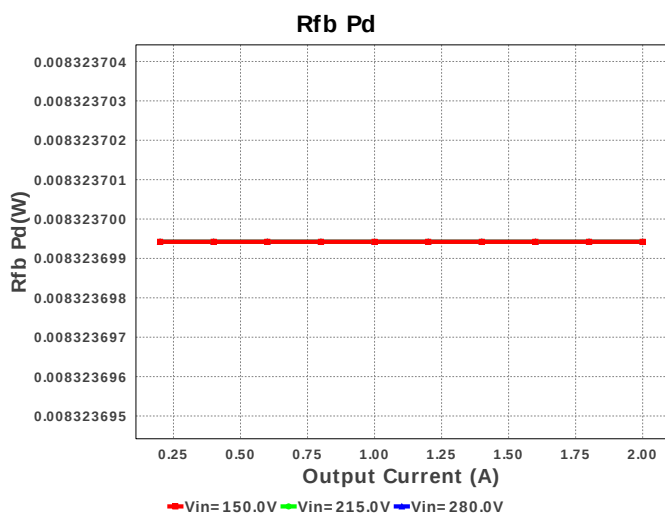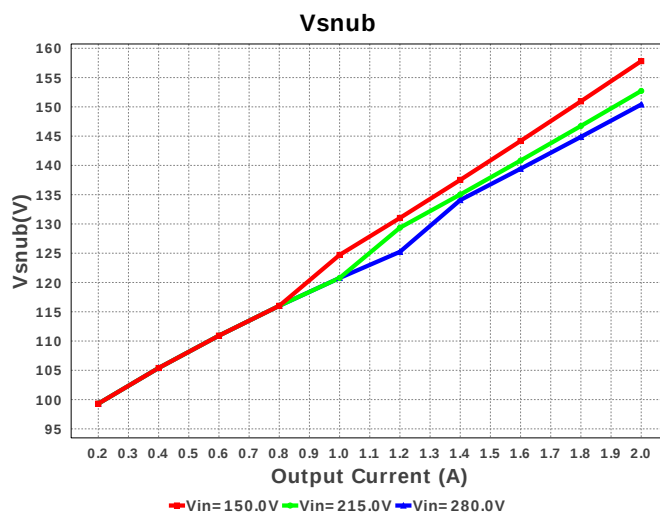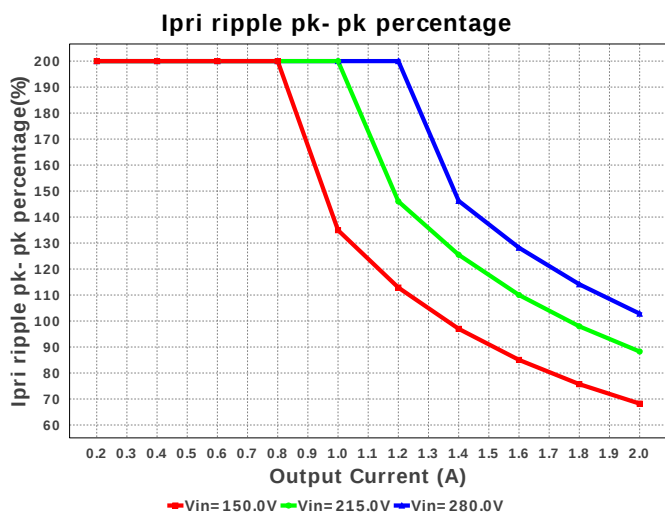

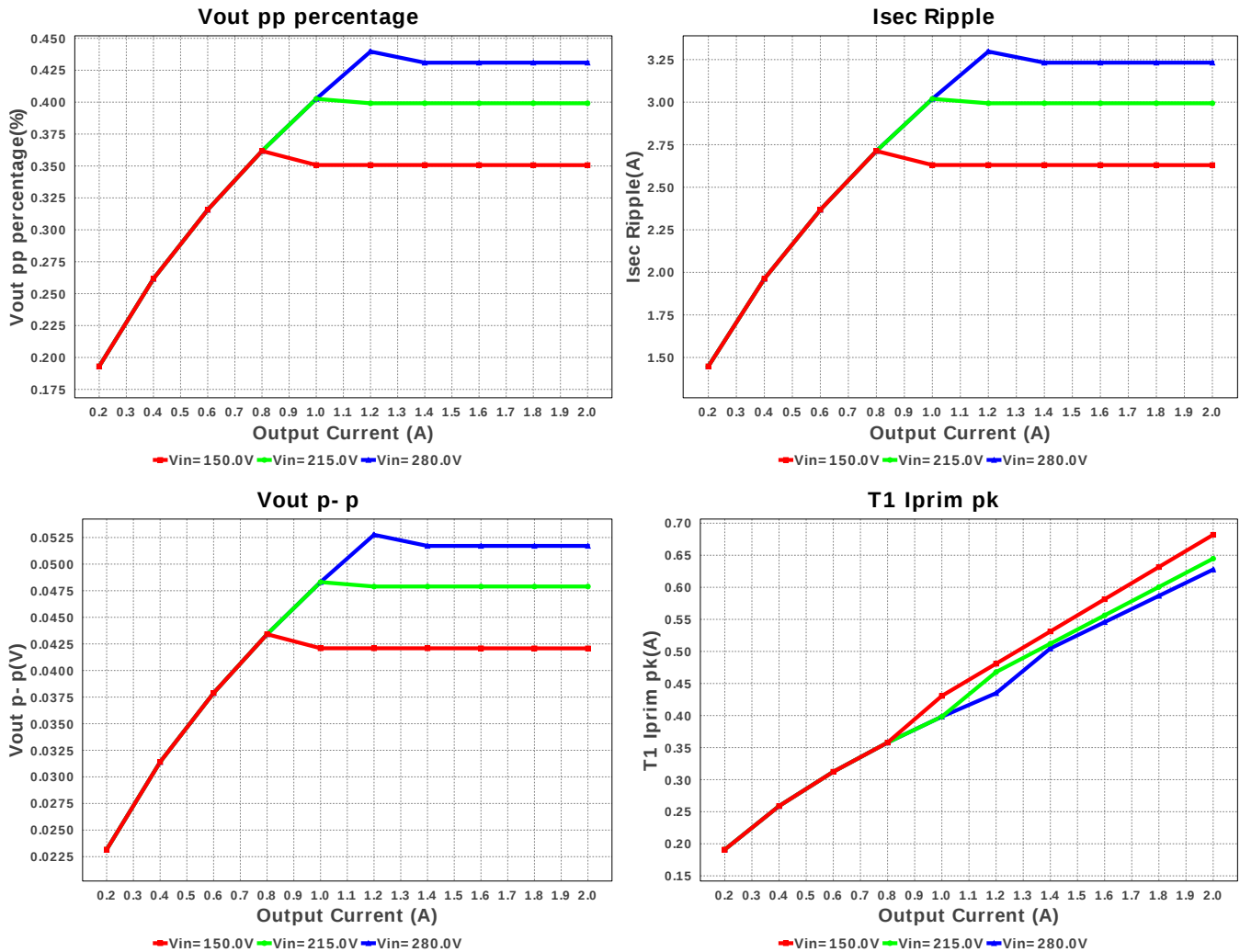

Operating Values

#	Name	Value	Category	Description
1.	Cout1 IRMS	2.293 A	Current	Output capacitor1 RMS ripple current
2.	Iin Avg	183.172 mA	Current	Average input current
3.	Iout_DCM	826.873 mA	Current	Approximate Current below which DCM mode of operation will begin
4.	Ipri Avg	203.581 mA	Current	Average Current in Primary Winding over the complete Switching Period
5.	Ipri ripple	346.887 mA	Current	Ripple Current in the Primary Winding
6.	Ipri ripple pk-pk percentage	68.224 %	Current	Primary Current pk-pk ripple percentage(of Ipri avg during ton only)
7.	Isec Ripple	2.63 A	Current	Ripple Current in the Secondary Winding
8.	T1 Iprim RMS	327.913 mA	Current	Transformer Primary RMS Current
9.	T1 Iprim pk	681.899 mA	Current	Transformer Primary Peak Current
10.	T1 Is1 RMS	3.042 A	Current	Transformer Secondary1 RMS Current
11.	T1 Is1 pk	5.17 A	Current	Transformer Secondary1 Peak Current
12.	BOM Count	47	General	Total Design BOM count
13.	Daux trr	0.0 ns	General	Auxiliary Diode Reverse Recovery Time
14.	Dsec Vf	517.55 mV	General	Effective Forward Voltage Drop at the Operating Current
15.	Dsec trr	0.0 ns	General	Output Diode Reverse Recovery Time
16.	Dsec2 Vf	517.55 mV	General	Effective Forward Voltage Drop at the Operating Current
17.	Dsnub trr	30.0 ns	General	Snubber Diode Reverse Recovery Time
18.	FootPrint	2.356 k mm ²	General	Total Foot Print Area of BOM components
19.	Frequency	176.591 kHz	General	Switching frequency
20.	Pout	24.0 W	General	Total output power
21.	Tdead	457.425 ns	General	Approximate Dead Time of the Regulator
22.	Toff	2.938 us	General	Approximate Converter Off Time
23.	Ton Act	2.267 us	General	Approximate Converter On Time
24.	Total BOM	\$0.0	General	Total BOM Cost
25.	Tsw	5.663 us	General	Switching Time Period
26.	Vaux	16.036 V	General	Auxiliary Voltage
27.	Vsnub	157.816 V	General	Voltage Across the Snubber
28.	Vout Actual	11.99 V	Op_Point	Vout Actual calculated based on selected voltage divider resistors
29.	Vout OP	12.0 V	Op_Point	Operational Output Voltage

#	Name	Value	Category	Description
30.	Duty Cycle	40.039 %	Op_point	Duty cycle
31.	Efficiency	87.35 %	Op_point	Steady state efficiency
32.	IC Tj	62.978 degC	Op_point	IC junction temperature
33.	ICThetaJA	110.0 degC/W	Op_point	IC junction-to-ambient thermal resistance
34.	IOUT_OP	2.0 A	Op_point	Iout operating point
35.	M1 TjOP	41.552 degC	Op_point	M1 MOSFET junction temperature
36.	Vout p-p	42.078 mV	Op_point	Peak-to-peak output ripple voltage
37.	Cin Pd	783.673 μ W	Power	Input capacitor power dissipation
38.	Cout1 Pd	84.089 mW	Power	Output capacitor1 power dissipation
39.	Dsec Pd	517.55 mW	Power	Secondary Diode Power Dissipation
40.	Dsec2 Pd	517.55 mW	Power	Secondary Diode Power Dissipation
41.	IC Pd	299.797 mW	Power	IC power dissipation
42.	L2 Pd	9.6 mW	Power	Average Power Dissipation in the Inductor Over the AC Line Period
43.	M1 Pd	139.181 mW	Power	M1 MOSFET total power dissipation
44.	Paux	15.343 mW	Power	Power Dissipation in Raux and Daux
45.	Pd Rstartup	1.467 W	Power	Power Dissipation in Rstartup1 and Rstartup2
46.	Rdrv Pd	46.443 μ W	Power	Power Dissipation in Gate Drive Resistor
47.	Rfb Pd	8.324 mW	Power	Rfb Power Dissipation
48.	Rsns Pd	107.527 mW	Power	Current Limit Sense Resistor Power Dissipation
49.	Snubber Pd	451.903 mW	Power	Snubber Power Dissipation
50.	T1 Pd	346.293 mW	Power	Estimated Losses in Transformer
51.	Total Pd	0.0 W	Power	Total Power Dissipation
52.	Vout Tolerance	1.926 %		Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable
53.	Vout pp percentage	350.654 m%		Output Voltage ripple percentage

Design Inputs

#	Name	Value	Description
1.	Iout	2.0	Maximum Output Current
2.	VinMax	280.0	Maximum input voltage
3.	VinMin	150.0	Minimum input voltage
4.	Vout	12.0	Output Voltage
5.	base_pn	UC3844	Texas Instruments Base Part Number
6.	source	DC	Input Source Type
7.	ta	30.0	Ambient temperature

Design Assistance

1. UC3844 Product Folder : <http://www.ti.com/product/UC3844> : contains the data sheet and other resources.

Texas Instruments' WEBENCH simulation tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Simulations are created using Texas Instruments' published specifications as well as the published specifications of other device manufacturers. While Texas Instruments does update this information periodically, this information may not be current at the time the simulation is built. Texas Instruments does not warrant the accuracy or completeness of the specifications or any information contained therein. Texas Instruments does not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. Texas Instruments does not warrant that the designs are production worthy.

You should completely validate and test your design implementation to confirm the system functionality for your application prior to production.

Use of Texas Instruments' WEBENCH simulation tools is subject to [Texas Instruments' Site Terms and Conditions of Use](#). Prototype boards based on WEBENCH created designs are provided AS IS without warranty of any kind for evaluation and testing purposes and are subject to the terms of the [Evaluation License Agreement](#).