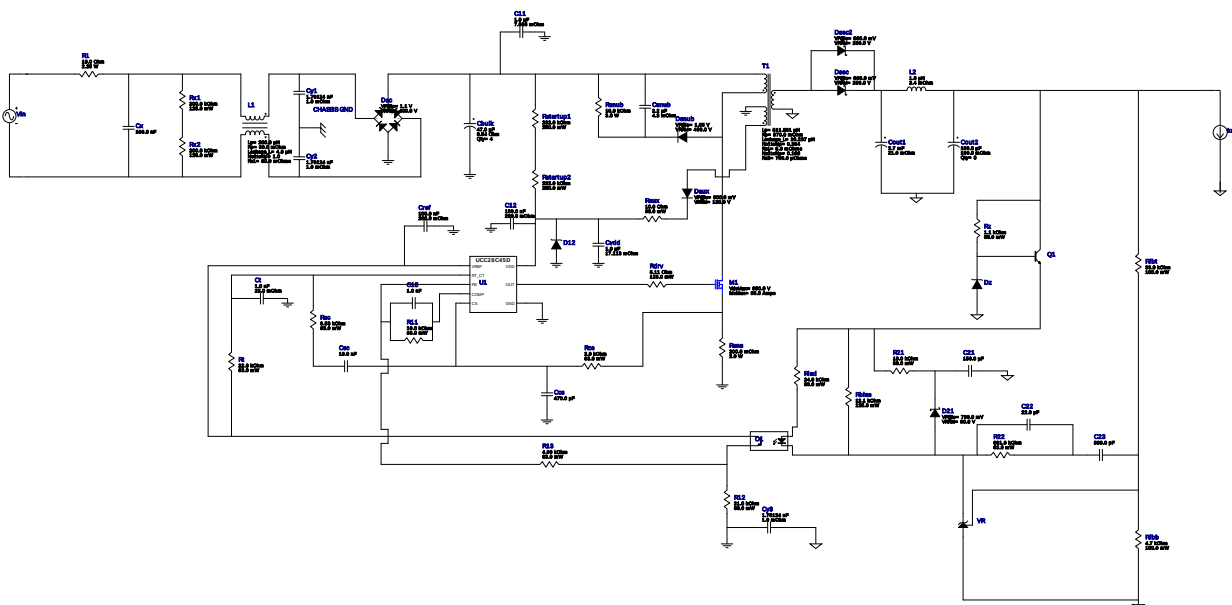


WEBENCH® Design Report



Design : 4737466/9 UCC28C45DR
UCC28C45DR 110.0V-130.0V to 20.00V @ 5.0A




1. The EMI filter selected here contains the estimated values. The real numbers will depend on the attenuation needed at a particular frequency.

Electrical BOM





#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	C11	MuRata	GRM55DR72E105KW01L Series= X7R	Cap= 1.0 uF ESR= 7.086 mOhm VDC= 250.0 V IRMS= 2.0605 A	1	\$0.26	 2220_200 54 mm ²
2.	C12	AVX	08053C104KAT2A Series= X7R	Cap= 100.0 nF ESR= 280.0 mOhm VDC= 25.0 V IRMS= 0.0 A	1	\$0.01	 0805 7 mm ²
3.	C13	Samsung Electro-Mechanics	CL21C102JBCNFNC Series= C0G/NP0	Cap= 1.0 nF VDC= 50.0 V IRMS= 0.0 A	1	\$0.01	 0805 7 mm ²
4.	C21	CUSTOM	CUSTOM Series= ?	Cap= 156.0 uF VDC= 36.0 V IRMS= 0.0 A	1	NA	CUSTOM 0 mm ²
5.	C22	Kemet	C0805C220K3GACTU Series= C0G/NP0	Cap= 22.0 pF VDC= 25.0 V IRMS= 0.0 A	1	\$0.01	 0805 7 mm ²
6.	C23	Samsung Electro-Mechanics	CL21C331JBANFNC Series= C0G/NP0	Cap= 330.0 pF VDC= 50.0 V IRMS= 0.0 A	1	\$0.01	 0805 7 mm ²
7.	Cbulk	Vishay-Bccomponents	MAL215759479E3 Series= 2239	Cap= 47.0 uF ESR= 3.54 Ohm VDC= 500.0 V IRMS= 680.0 mA	4	\$2.68	157PUM-SI_2200x2500 576 mm ²
8.	Ccs	Yageo America	CC0805KRX7R9BB471 Series= X7R	Cap= 470.0 pF VDC= 50.0 V IRMS= 0.0 A	1	\$0.01	 0805 7 mm ²





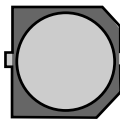
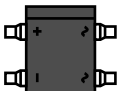
#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
9.	Cout1	TDK	B41605A8278M009 Series= 2385	Cap= 2.7 mF ESR= 21.0 mOhm VDC= 63.0 V IRMS= 5.3 A	1	\$12.37	B41605_2500x4000_9 729 mm ²
10.	Cout2	Nichicon	UUD1H151MNL1GS Series= uD	Cap= 150.0 uF ESR= 180.0 mOhm VDC= 50.0 V IRMS= 670.0 mA	8	\$0.26	 SM_RADIAL_10BMM 160 mm ²
11.	Cref	AVX	08053C104KAT2A Series= X7R	Cap= 100.0 nF ESR= 280.0 mOhm VDC= 25.0 V IRMS= 0.0 A	1	\$0.01	 0805 7 mm ²
12.	Csc	MuRata	GRM216R71H103KA01D Series= X7R	Cap= 10.0 nF VDC= 50.0 V IRMS= 0.0 A	1	\$0.01	 0805 7 mm ²
13.	Csnub	TDK	C5750X6S2W225K Series= X6S	Cap= 2.2 uF ESR= 4.3 mOhm VDC= 400.0 V IRMS= 0.0 A	1	NA	 2220 54 mm ²
14.	Ct	Kemet	C0805C102J5GACTU Series= C0G/NP0	Cap= 1.0 nF ESR= 25.0 mOhm VDC= 50.0 V IRMS= 1.71 A	1	\$0.01	 0805 7 mm ²
15.	Cvdd	MuRata	GRM188R61E105KA12D Series= X5R	Cap= 1.0 uF ESR= 17.113 mOhm VDC= 25.0 V IRMS= 979.39 mA	1	\$0.01	 0603 5 mm ²
16.	Cx	TDK	B32913A5104M000 Series= 2231	Cap= 100.0 nF VDC= 1000.0 V IRMS= 0.0 A	1	\$0.46	 B32913_2650x600x1500 228 mm ²
17.	Cy1	CUSTOM	CUSTOM Series= ?	Cap= 1.70124 nF ESR= 1.0 mOhm VDC= 220.62 V IRMS= 500.0 uA	1	NA	CUSTOM 0 mm ²
18.	Cy2	CUSTOM	CUSTOM Series= ?	Cap= 1.70124 nF ESR= 1.0 mOhm VDC= 220.62 V IRMS= 500.0 uA	1	NA	CUSTOM 0 mm ²
19.	Cy3	CUSTOM	CUSTOM Series= ?	Cap= 1.70124 nF ESR= 1.0 mOhm VDC= 220.62 V IRMS= 500.0 uA	1	NA	CUSTOM 0 mm ²
20.	D12	Diodes Inc.	MMSZ5248B-7-F	Zener	1	\$0.04	 SOD-123 13 mm ²
21.	D21	Diodes Inc.	B260A-13-F	VF@Io= 700.0 mV VRRM= 60.0 V	1	\$0.09	 SMA 37 mm ²
22.	Dac	Diodes Inc.	DF1504S-T	VF@Io= 1.1 V VRRM= 400.0 V	1	\$0.20	 DF-S 99 mm ²
23.	Daux	Vishay-Semiconductor	V12P12-M3/86A	VF@Io= 800.0 mV VRRM= 120.0 V	1	\$0.40	 TO-277A 56 mm ²






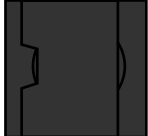
#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
24.	Dsec	ON Semiconductor	MBRB40250TG	VF@Io= 860.0 mV VRRM= 250.0 V	1	\$0.94	 DDPAK 210 mm ²
25.	Dsec2	ON Semiconductor	MBRB40250TG	VF@Io= 860.0 mV VRRM= 250.0 V	1	\$0.94	 DDPAK 210 mm ²
26.	Dsnub	Bourns	CD1408-FU1400	VF@Io= 1.05 V VRRM= 400.0 V	1	\$0.13	 Diode_1408 13 mm ²
27.	Dz	Diodes Inc.	MMSZ5248B-7-F	Zener	1	\$0.04	 SOD-123 13 mm ²
28.	L1	CUSTOM	CUSTOM	Lp= 200.0 µH Rp= 60.0 mOhm Leakage_L= 4.0 µH Ns1toNp= 1.0 Rs1= 60.0 mOhms	1	NA	CUSTOM 0 mm ²
29.	L2	Coilcraft	SER1360-182KLB	L= 1.8 µH DCR= 2.4 mOhm	1	\$0.72	 SER1360 225 mm ²
30.	M1	STMicroelectronics	STP45N65M5	VdsMax= 650.0 V IdsMax= 35.0 Amps	1	\$3.85	 TO-220AB 397 mm ²
31.	O1	Vishay-Semiconductor	TCMT1107	Optocoupler	1	\$0.21	 SOP-4 44 mm ²
32.	Q1	ON Semiconductor	BC846BLT1G	Bipolar Transistor	1	\$0.02	 SOT-23 14 mm ²
33.	R1	Vishay-Dale	AC03000001009JACCS Series= F_RES	Res= 10.0 Ohm Power= 2.25 W Tolerance= 5.0%	1	\$0.30	 AC03 158 mm ²
34.	R11	Vishay-Dale	CRCW040210K0FKED Series= CRCW..e3	Res= 10.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
35.	R12	Vishay-Dale	CRCW040221K0FKED Series= CRCW..e3	Res= 21.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
36.	R13	Vishay-Dale	CRCW04024K99FKED Series= CRCW..e3	Res= 4.99 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
37.	R21	Vishay-Dale	CRCW040210K0FKED Series= CRCW..e3	Res= 10.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
38.	R22	Vishay-Dale	CRCW0402681KFKED Series= CRCW..e3	Res= 681.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
39.	Raux	Vishay-Dale	CRCW040210R0FKED Series= CRCW..e3	Res= 10.0 Ohm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
40.	Rbias	Panasonic	ERJ-6ENF1212V Series= ERJ-6E	Res= 12.1 kOhm Power= 125.0 mW Tolerance= 1.0%	1	\$0.01	 0805 7 mm ²







#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
41.	Rcs	Vishay-Dale	CRCW04022K00FKED Series= CRCW..e3	Res= 2.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
42.	Rdrv	Vishay-Dale	CRCW08055R11FKEA Series= CRCW..e3	Res= 5.11 Ohm Power= 125.0 mW Tolerance= 1.0%	1	\$0.01	 0805 7 mm ²
43.	Rfbb	Yageo America	RC0603FR-074K7L Series= ?	Res= 4.7 kOhm Power= 100.0 mW Tolerance= 1.0%	1	\$0.01	 0603 5 mm ²
44.	Rfbt	Yageo America	RC0603FR-0733KL Series= ?	Res= 33.0 kOhm Power= 100.0 mW Tolerance= 1.0%	1	\$0.01	 0603 5 mm ²
45.	Rled	Vishay-Dale	CRCW040224K9FKED Series= CRCW..e3	Res= 24.9 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
46.	Rsc	Vishay-Dale	CRCW04029K53FKED Series= CRCW..e3	Res= 9.53 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
47.	Rsns	Stackpole Electronics Inc	CSRN2512FKR200 Series= ?	Res= 200.0 mOhm Power= 2.0 W Tolerance= 1.0%	1	\$0.13	 2512 43 mm ²
48.	Rsnsb	Vishay-Bccomponents	PR03000201002JAC00 Series= ?	Res= 10.0 kOhm Power= 3.0 W Tolerance= 5.0%	1	\$0.19	 PR03 0 mm ²
49.	Rstartup1	Panasonic	ERJ-8ENF2323V Series= ERJ-8E	Res= 232.0 kOhm Power= 250.0 mW Tolerance= 1.0%	1	\$0.01	 1206 11 mm ²
50.	Rstartup2	Panasonic	ERJ-8ENF2323V Series= ERJ-8E	Res= 232.0 kOhm Power= 250.0 mW Tolerance= 1.0%	1	\$0.01	 1206 11 mm ²
51.	Rt	Vishay-Dale	CRCW040222K6FKED Series= CRCW..e3	Res= 22.6 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
52.	Rx1	Panasonic	ERJ-6ENF2003V Series= ERJ-6E	Res= 200.0 kOhm Power= 125.0 mW Tolerance= 1.0%	1	\$0.01	 0805 7 mm ²
53.	Rx2	Panasonic	ERJ-6ENF2003V Series= ERJ-6E	Res= 200.0 kOhm Power= 125.0 mW Tolerance= 1.0%	1	\$0.01	 0805 7 mm ²
54.	Rz	Vishay-Dale	CRCW04021K10FKED Series= CRCW..e3	Res= 1.1 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
55.	T1	CUSTOM	CUSTOM	Lp= 511.851 µH Rp= 870.0 mOhm Leakage_L= 10.237 µH Ns1toNp= 0.284 Rs1= 8.6 mOhms Ns2toNp= 0.166 Rs2= 700.0 µOhms	1	NA	CUSTOM 0 mm ²
56.	U1	Texas Instruments	UCC28C45DR	Switcher	1	\$0.60	 D0008A 57 mm ²







#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
57.	VR	Texas Instruments	TL431AIDBVR	Voltage References	1	\$0.07	 R-PDSO-G3 16 mm ²



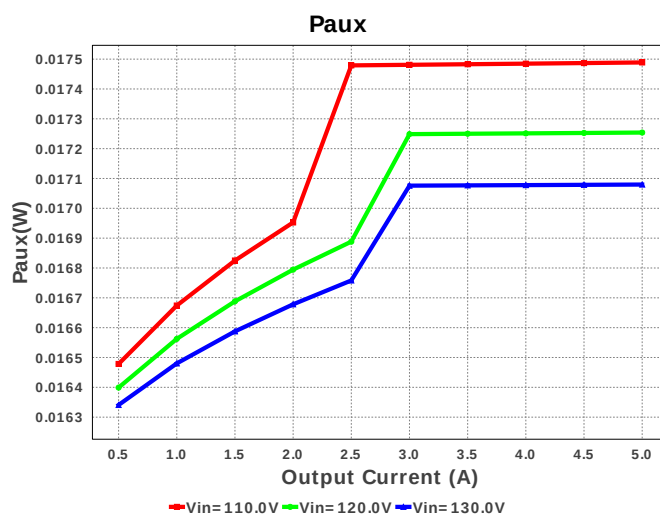
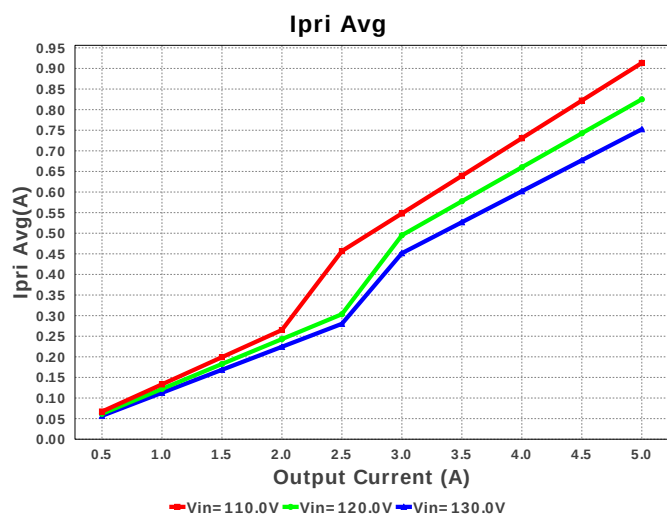
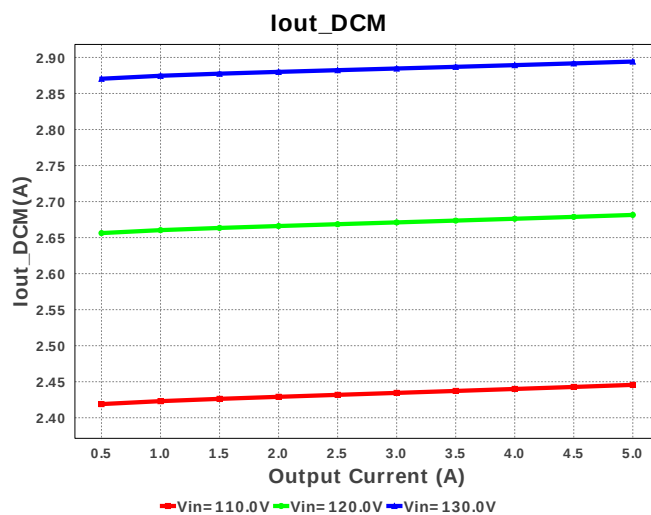
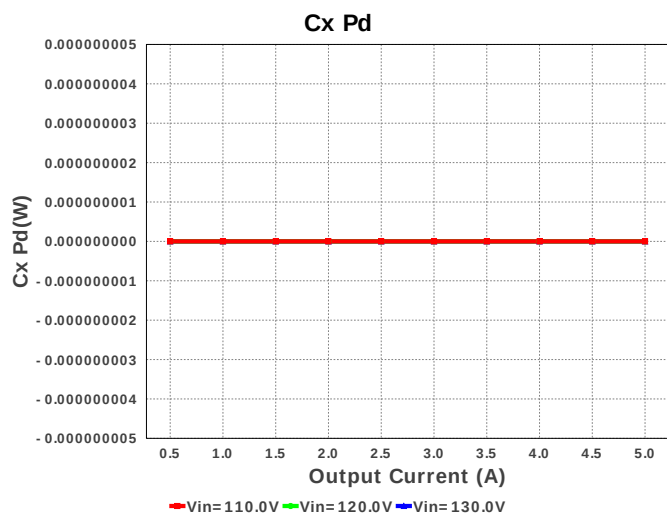


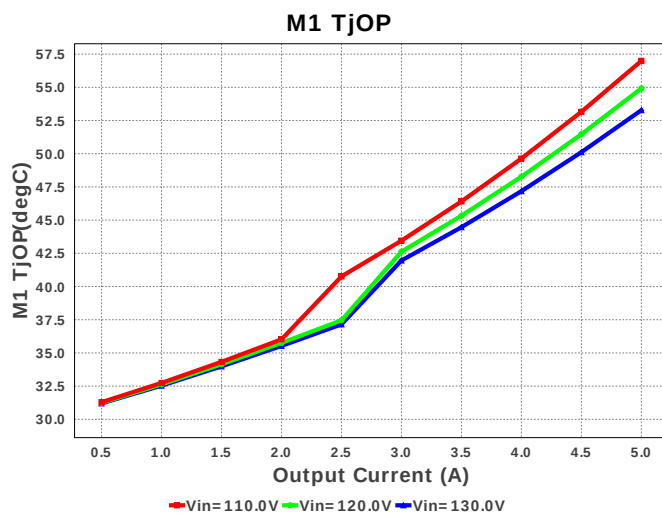
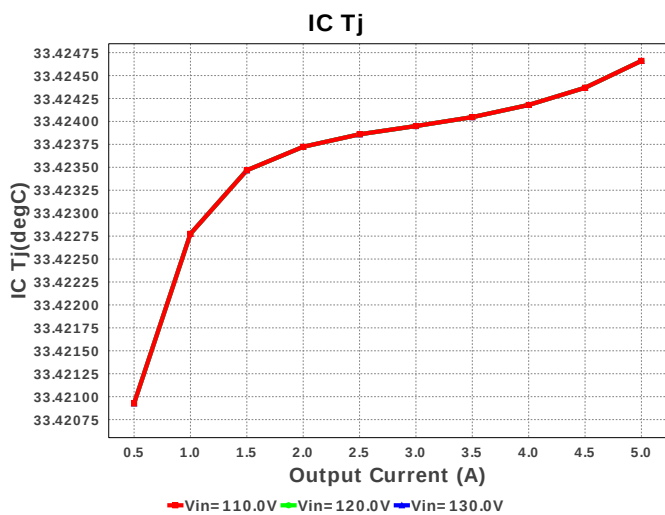
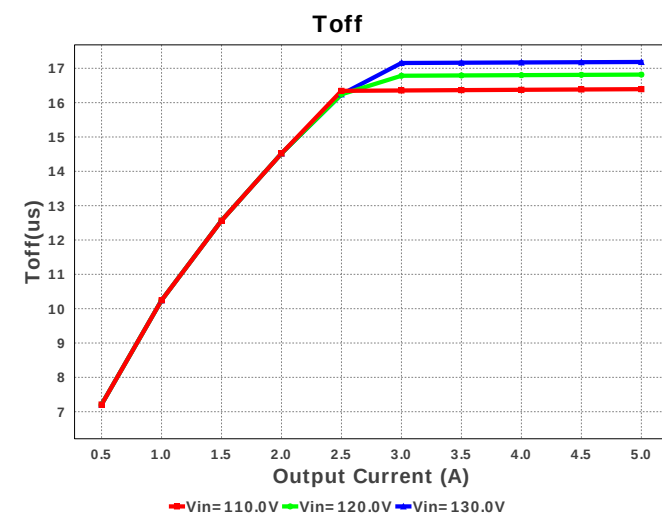
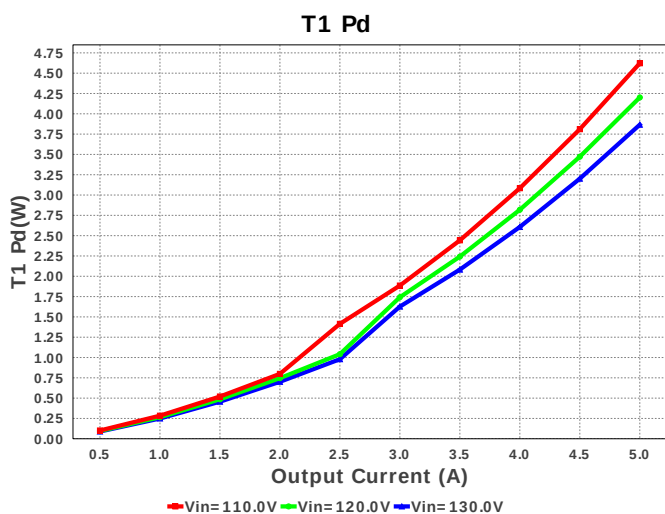
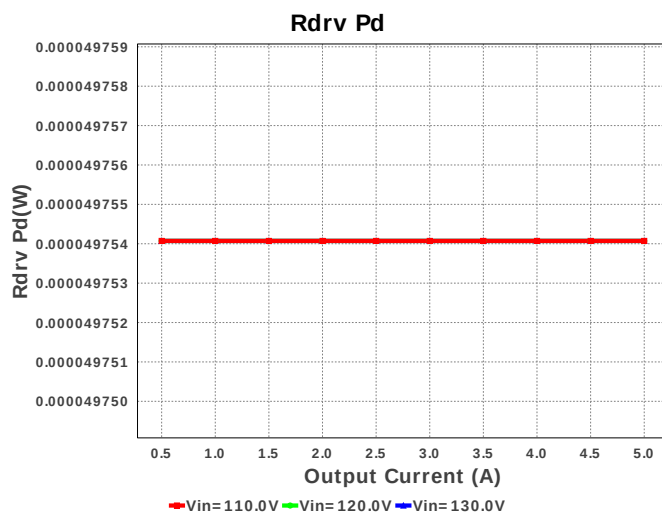
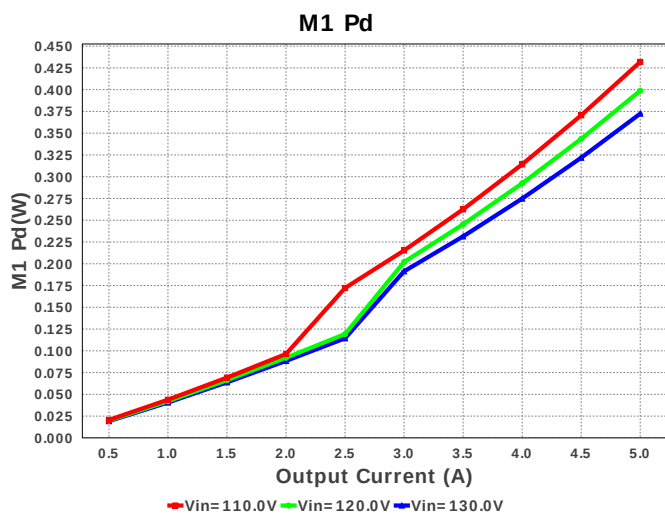


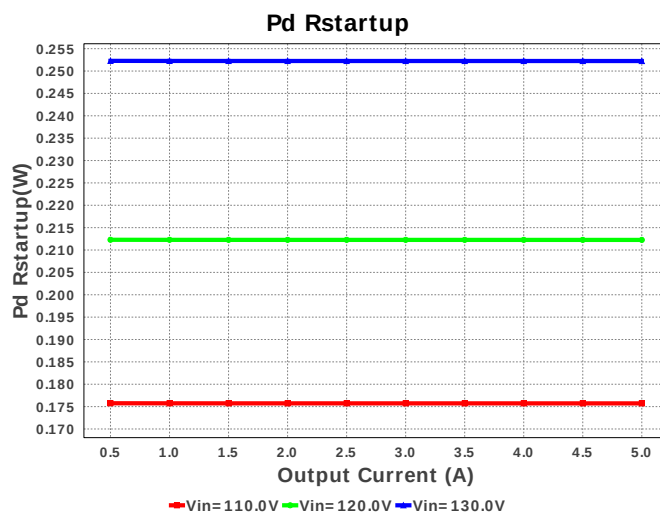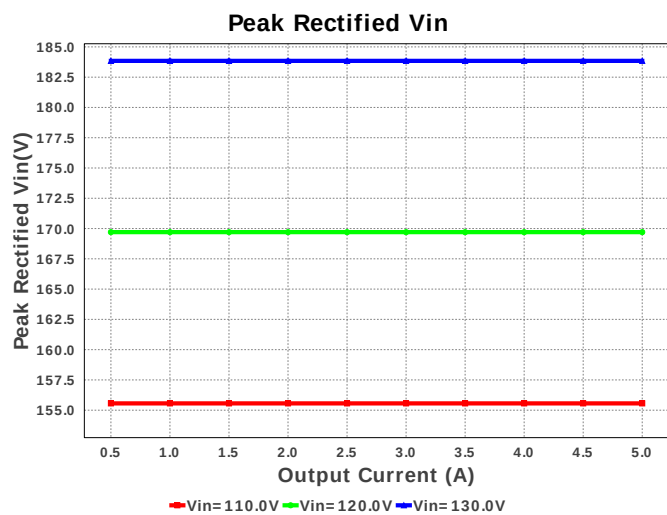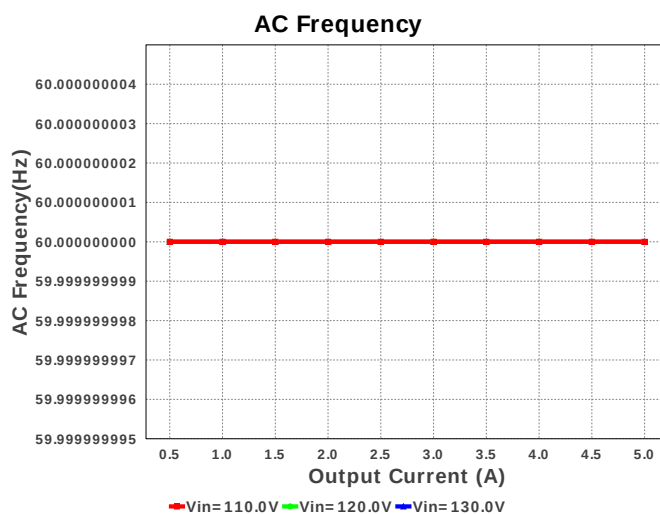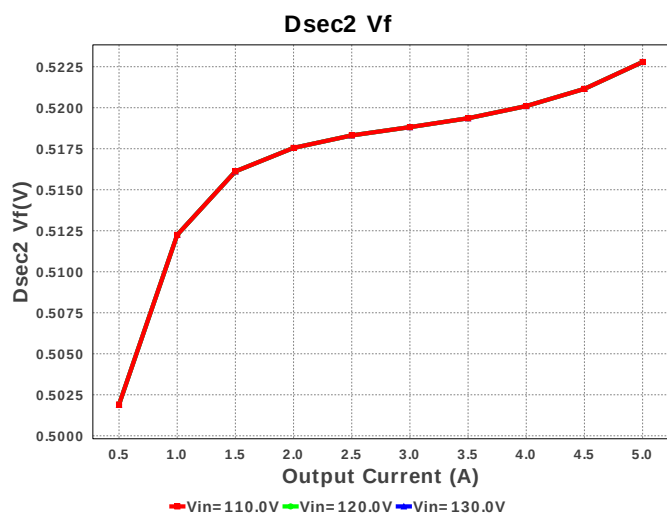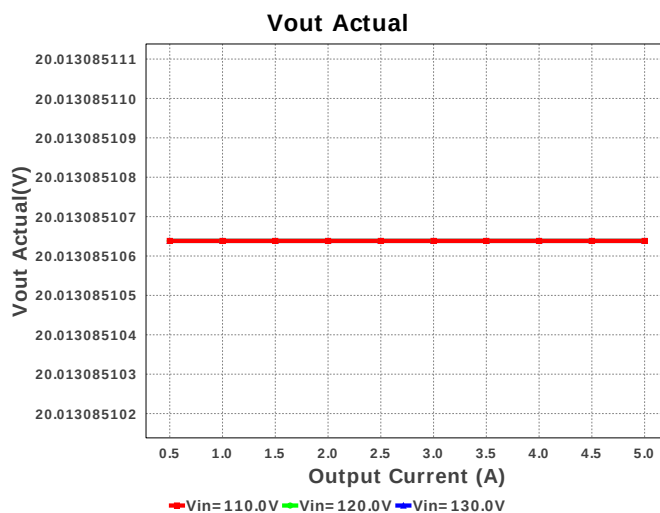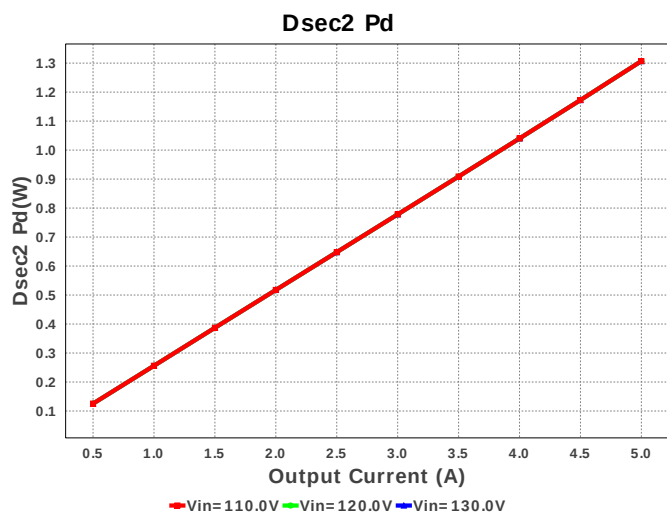


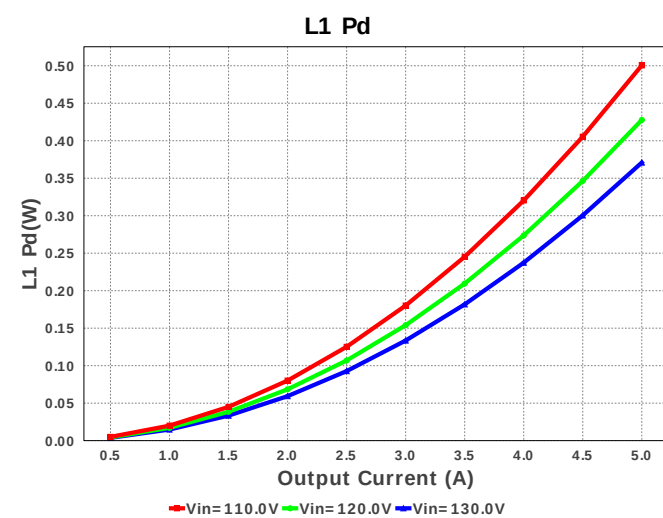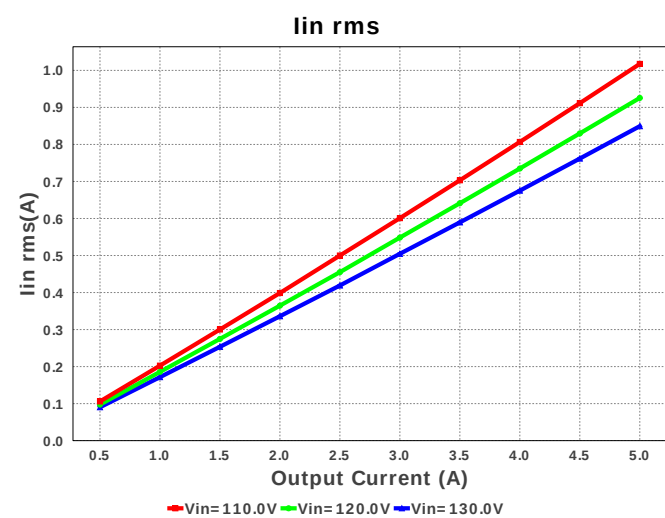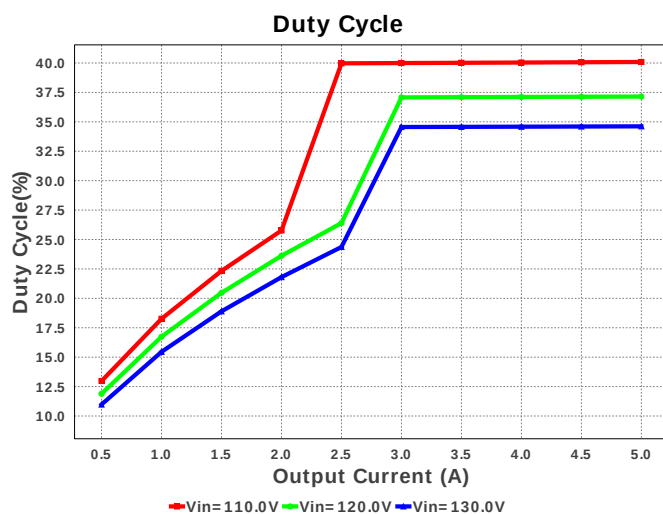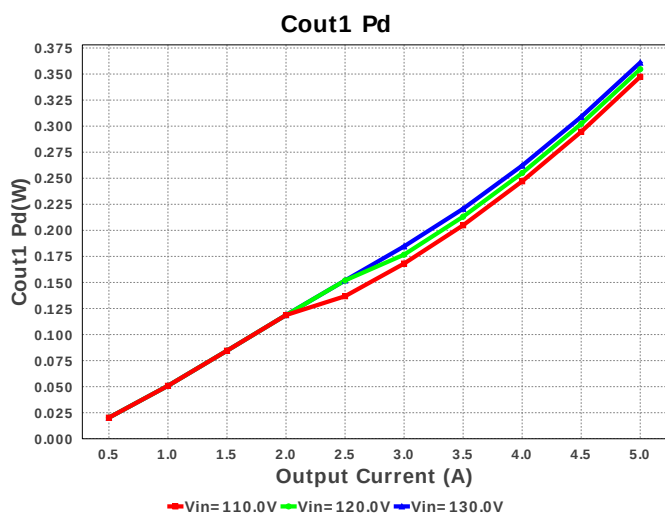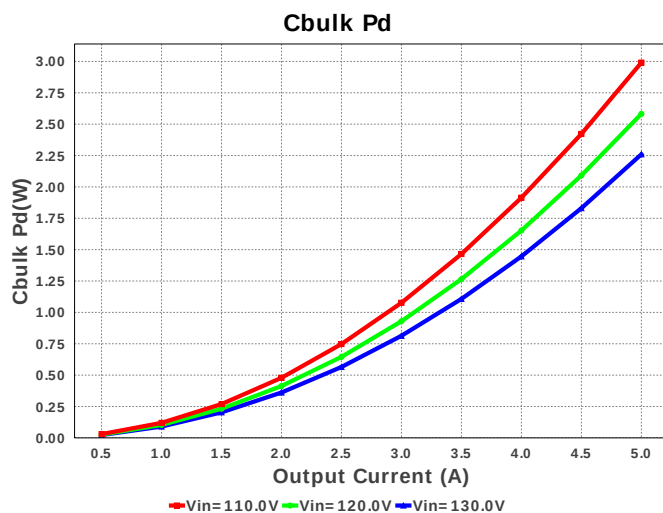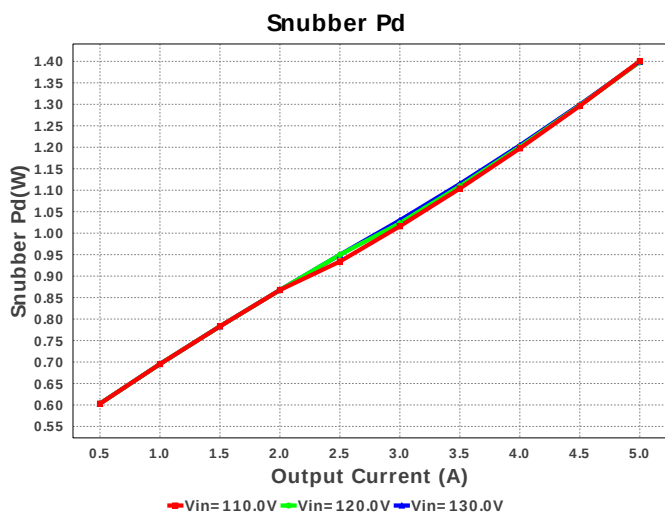


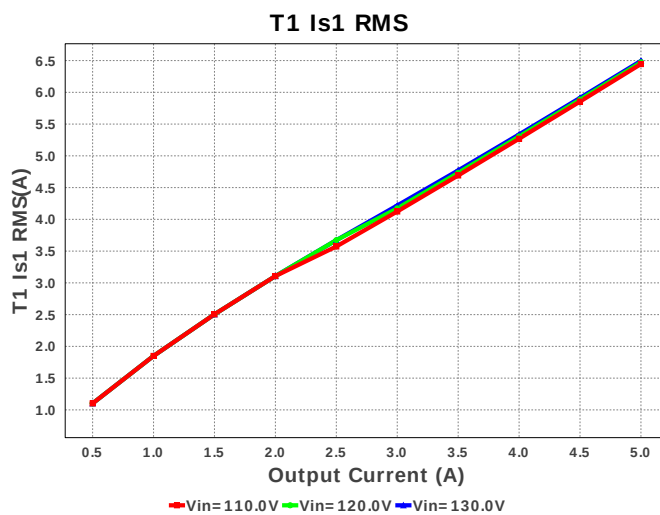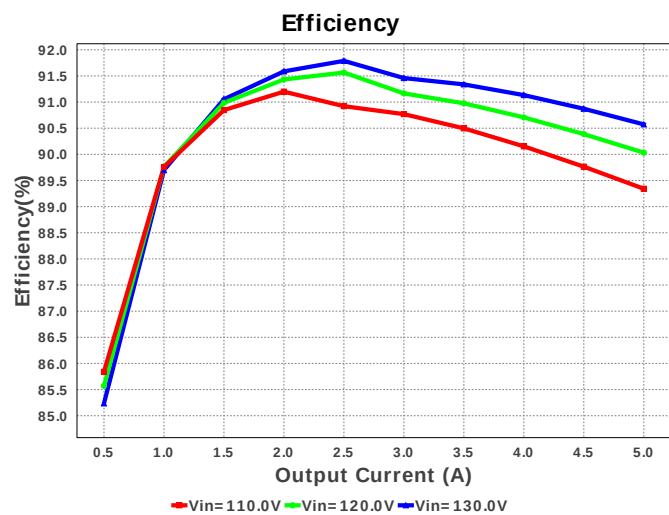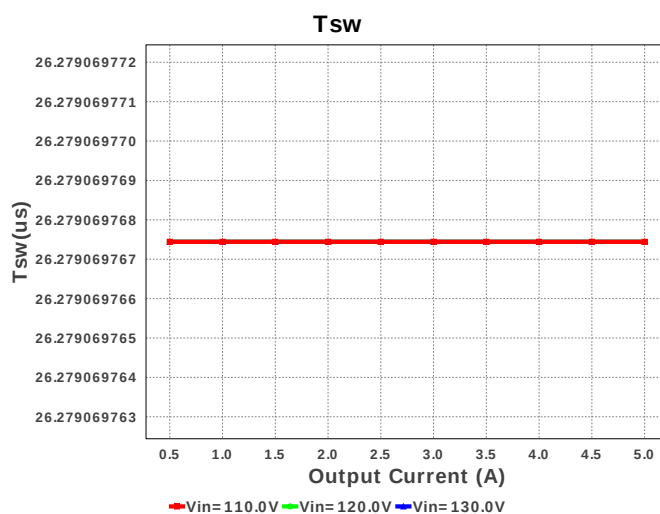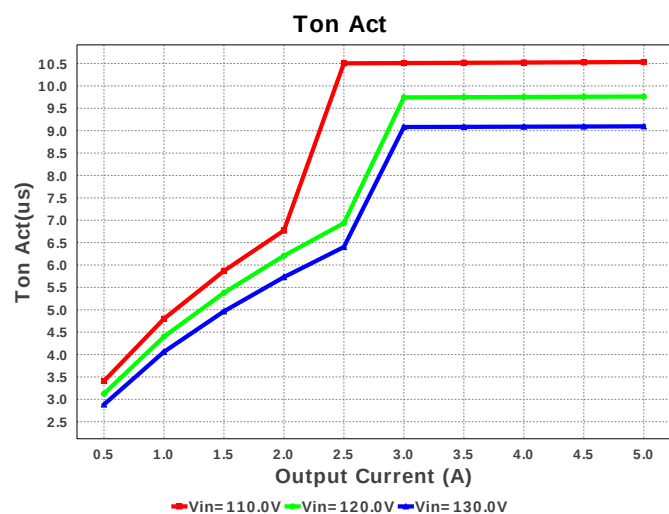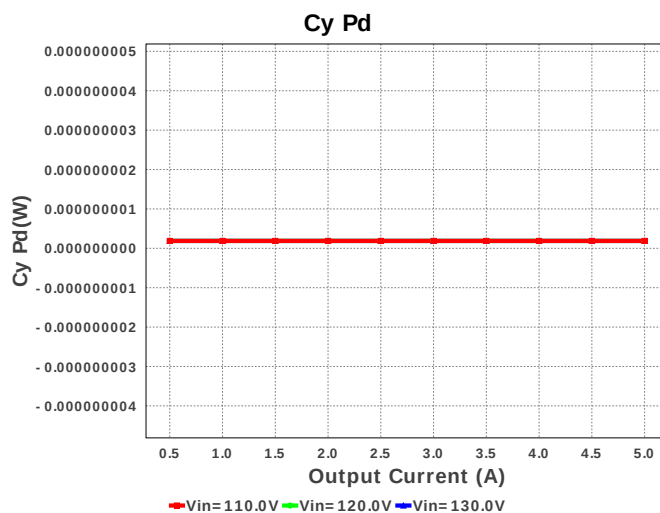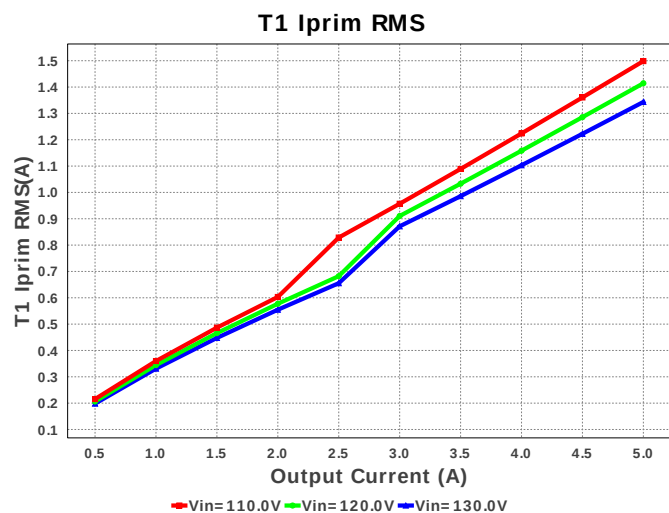

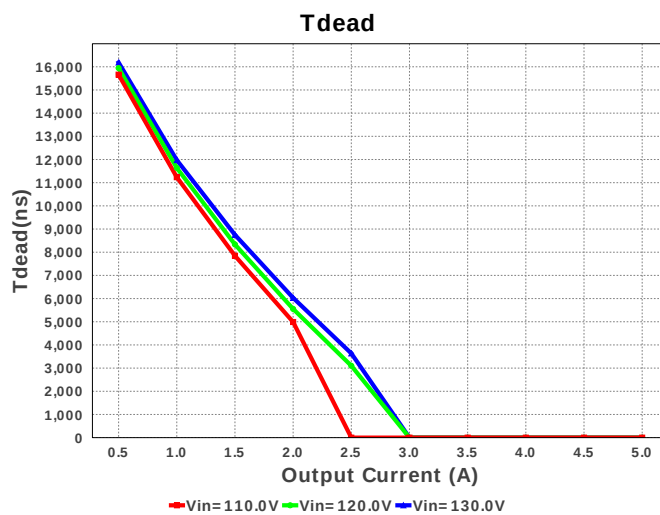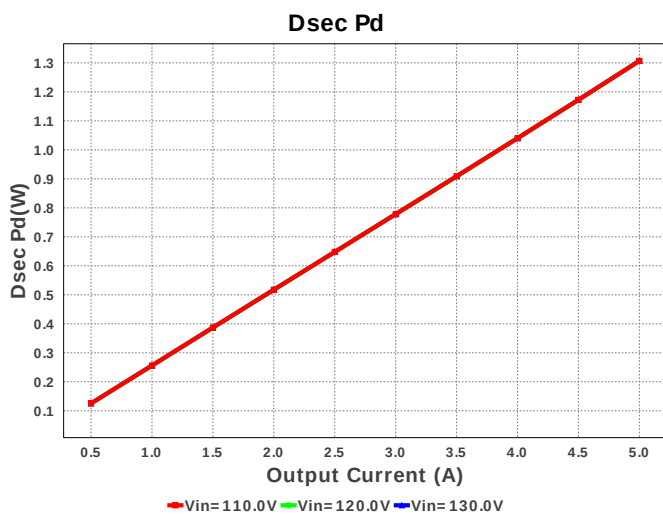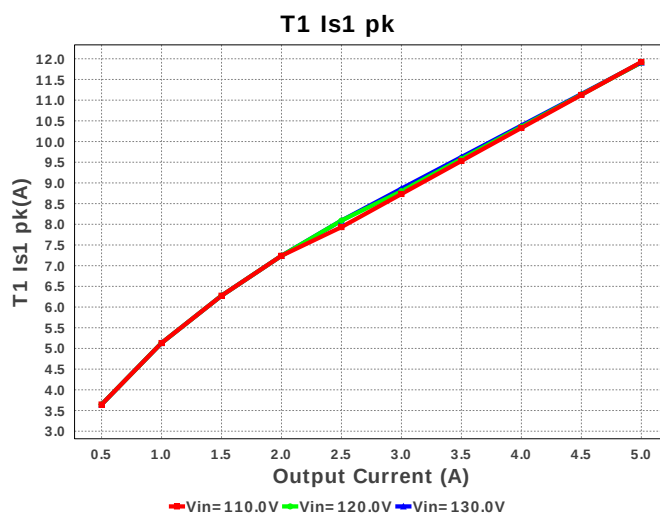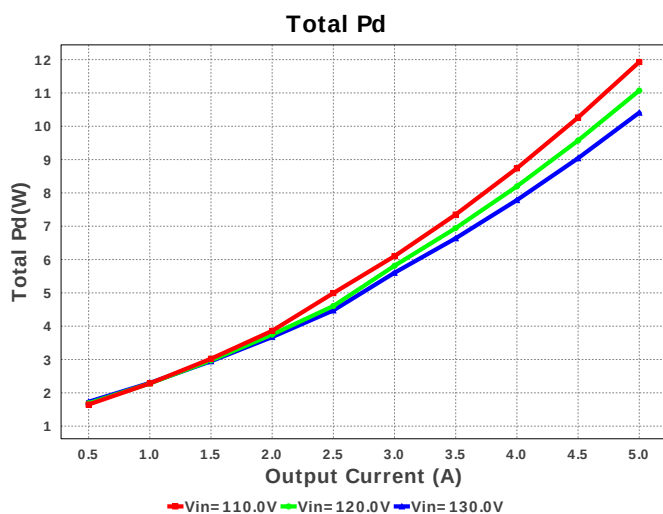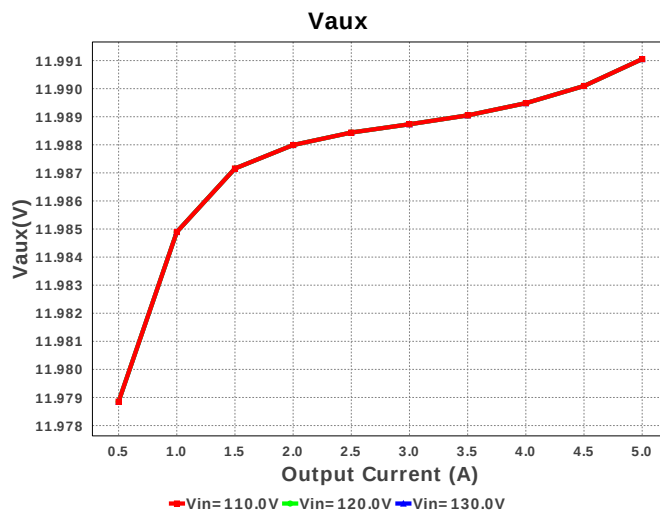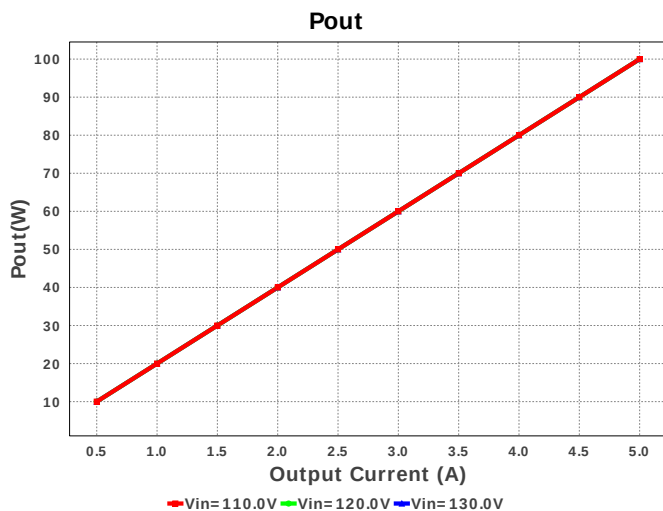

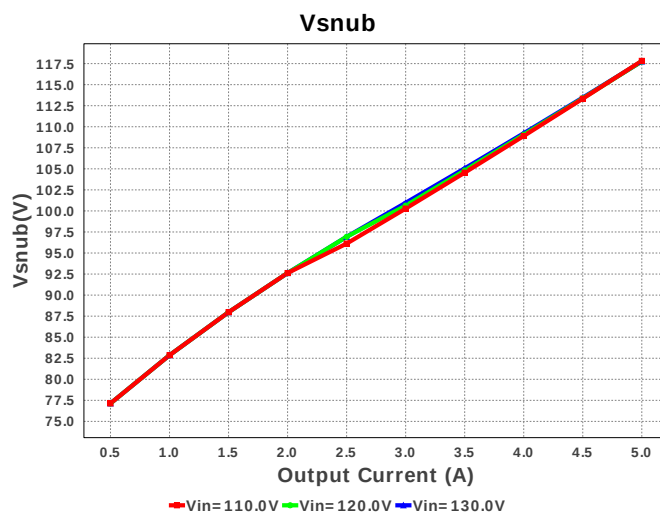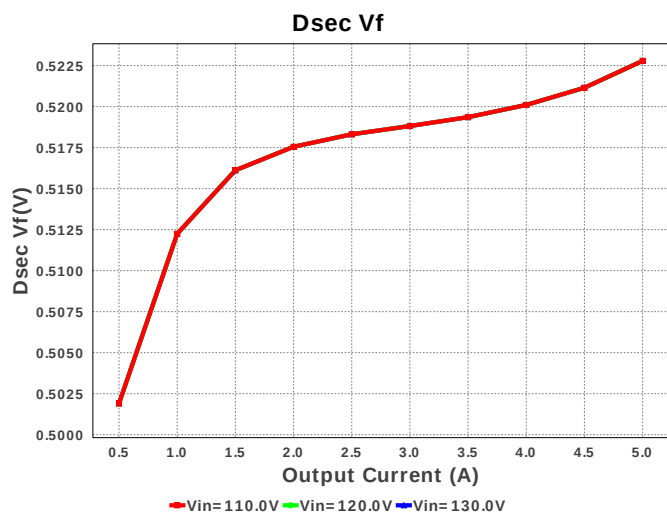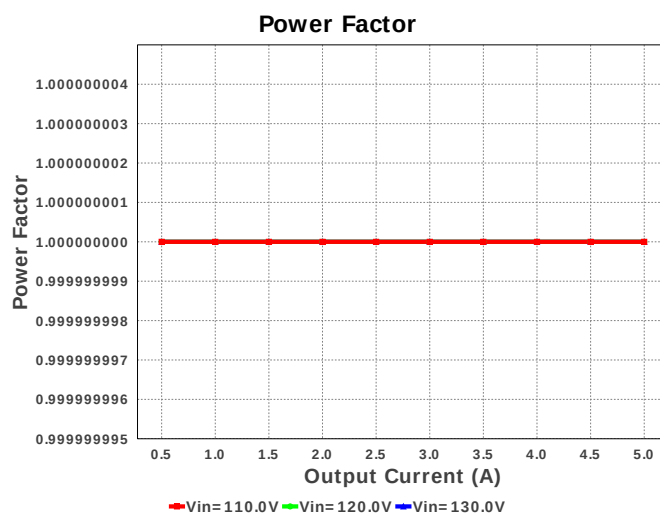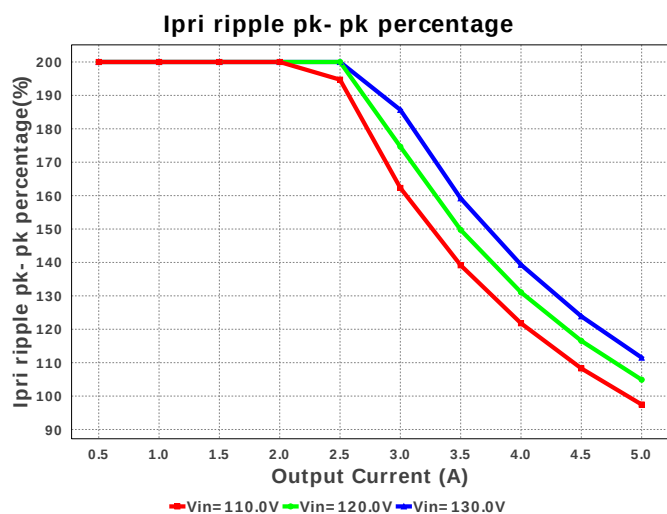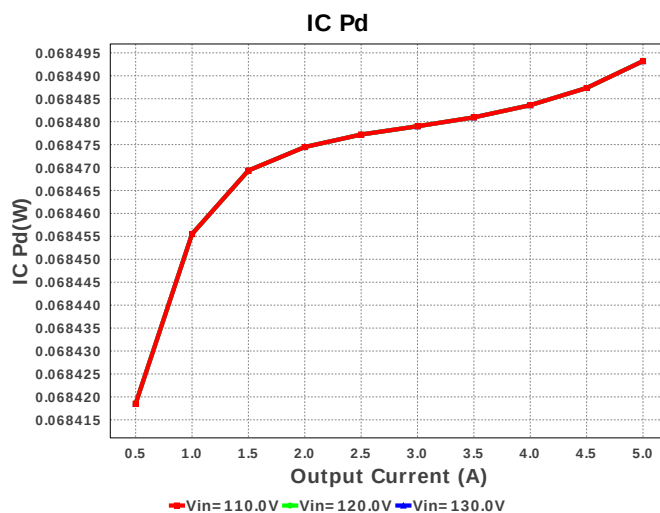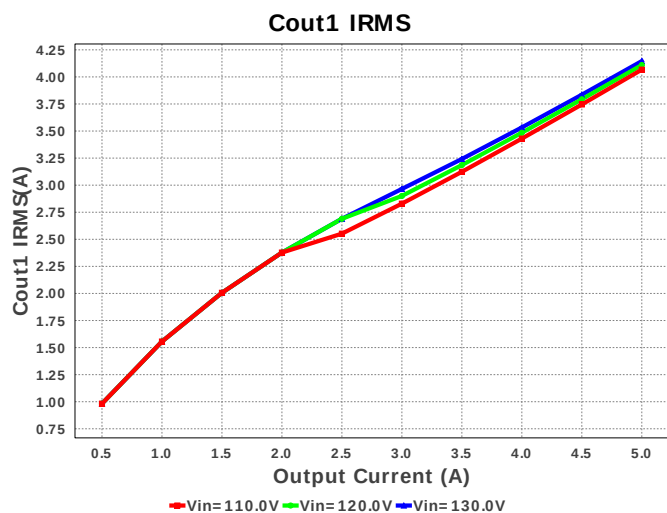

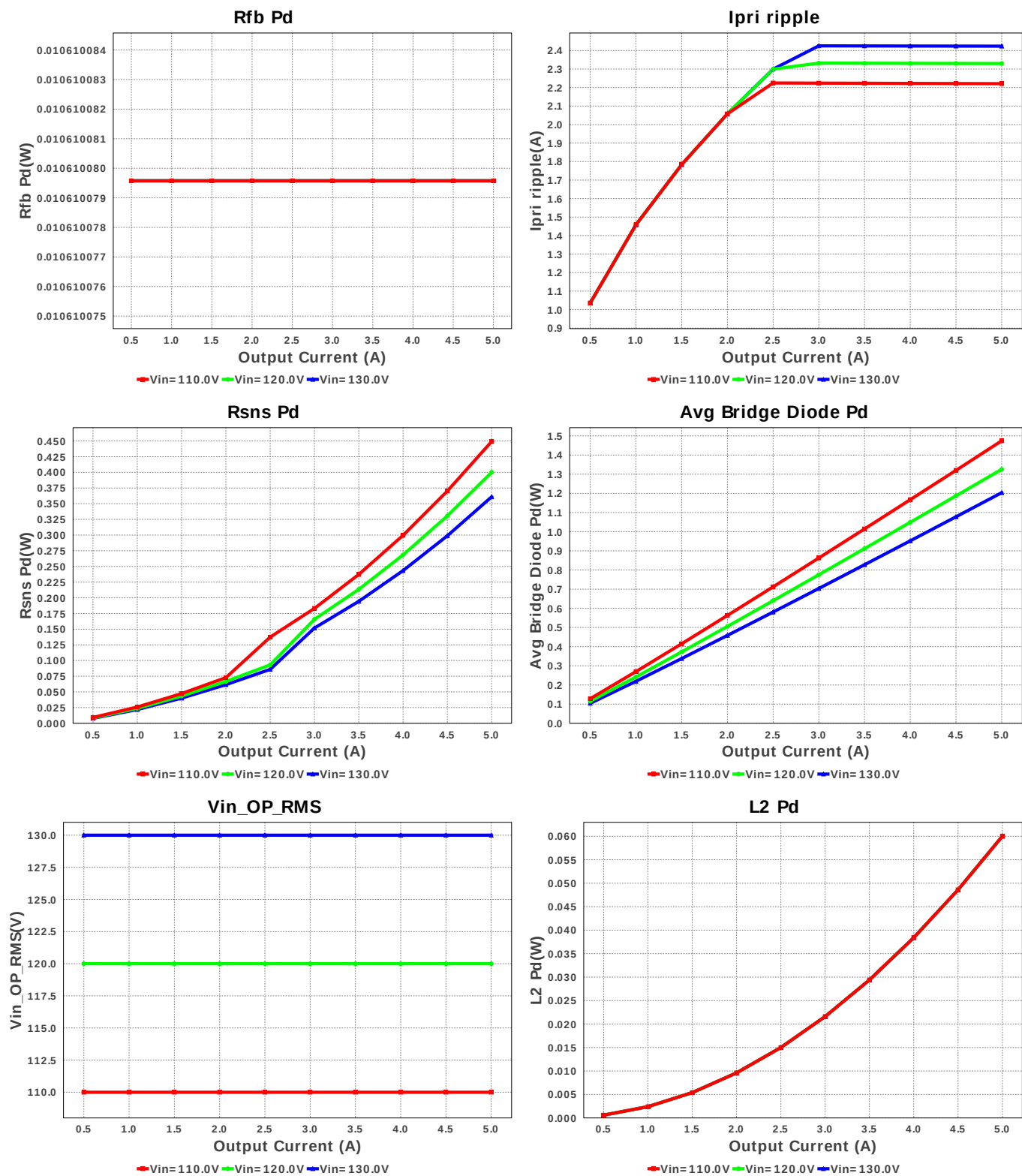

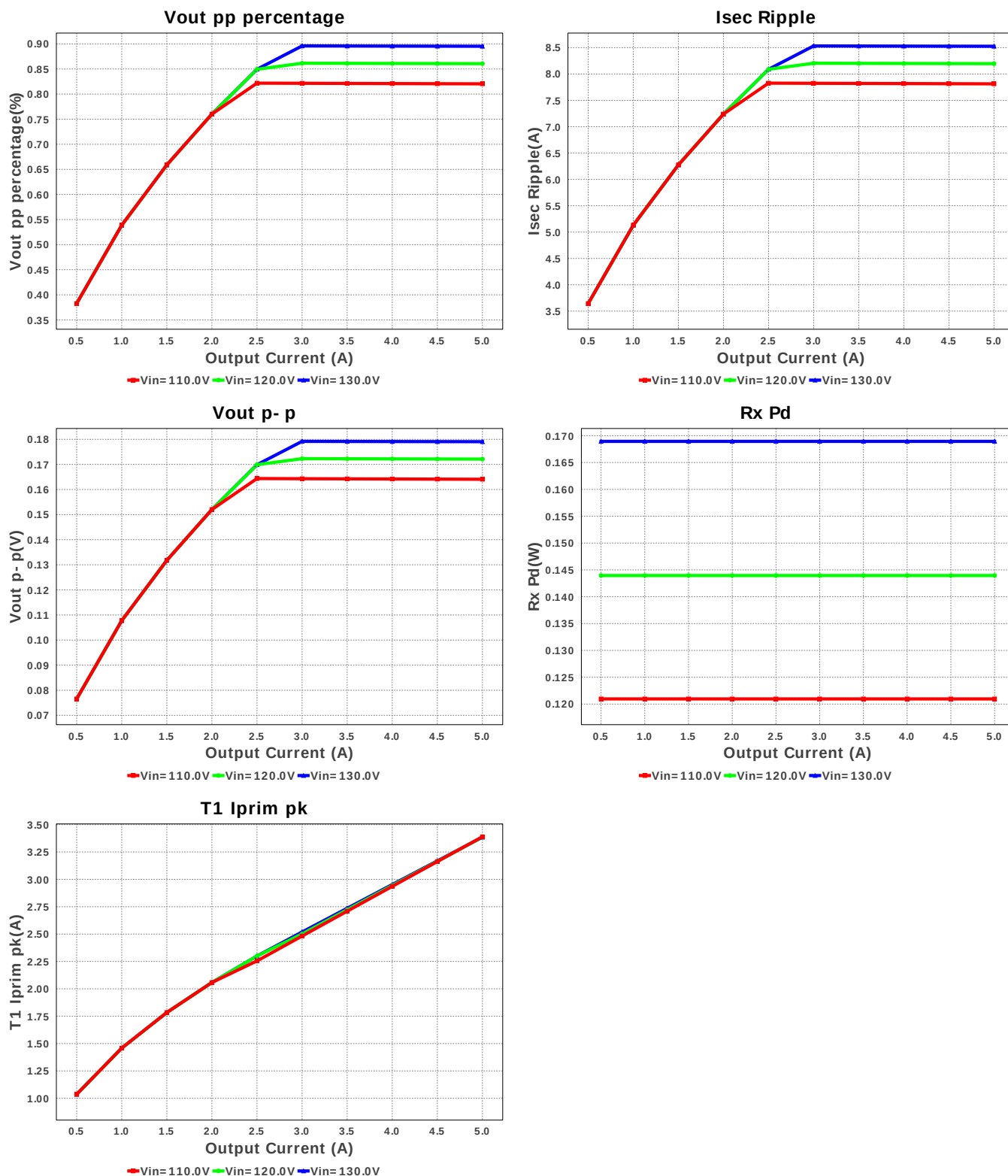

Operating Values

#	Name	Value	Category	Description
1.	Cout1 IRMS	4.067 A	Current	Output capacitor1 RMS ripple current
2.	Iin rms	1.018 A	Current	RMS Input Current
3.	Iout_DCM	2.446 A	Current	Approximate Current below which DCM mode of operation will begin
4.	Ipri Avg	913.308 mA	Current	Average Current in Primary Winding over the complete Switching Period
5.	Ipri ripple	2.221 A	Current	Ripple Current in the Primary Winding
6.	Ipri ripple pk-pk percentage	97.48 %	Current	Primary Current pk-pk ripple percentage(of Ipri avg during ton only)
7.	Isec Ripple	7.814 A	Current	Ripple Current in the Secondary Winding
8.	T1 Iprim RMS	1.499 A	Current	Transformer Primary RMS Current
9.	T1 Iprim pk	3.389 A	Current	Transformer Primary Peak Current

#	Name	Value	Category	Description
10.	T1 Is1 RMS	6.445 A	Current	Transformer Secondary1 RMS Current
11.	T1 Is1 pk	11.922 A	Current	Transformer Secondary1 Peak Current
12.	AC Frequency	60.0 Hz	General	Input AC frequency
13.	BOM Count	67	General	Total Design BOM count
14.	Daux trr	0.0 ns	General	Auxiliary Diode Reverse Recovery Time
15.	Dsec Vf	522.788 mV	General	Effective Forward Voltage Drop at the Operating Current
16.	Dsec trr	0.0 ns	General	Output Diode Reverse Recovery Time
17.	Dsec2 Vf	522.788 mV	General	Effective Forward Voltage Drop at the Operating Current
18.	Dsnub trr	35.0 ns	General	Snubber Diode Reverse Recovery Time
19.	FootPrint	6.632 k mm ²	General	Total Foot Print Area of BOM components
20.	Frequency	38.053 kHz	General	Switching frequency
21.	Pout	100.0 W	General	Total output power
22.	Power Factor	1.0	General	Assumed Power Factor for the Application
23.	Tdead	0.0 ns	General	Approximate Dead Time of the Regulator
24.	Toff	16.392 us	General	Approximate Converter Off Time
25.	Ton Act	10.534 us	General	Approximate Converter On Time
26.	Total BOM	\$0.0	General	Total BOM Cost
27.	Tsw	26.279 us	General	Switching Time Period
28.	Vaux	11.991 V	General	Auxiliary Voltage
29.	Vsnub	117.824 V	General	Voltage Across the Snubber
30.	Vout Actual	20.013 V	Op_Point	Vout Actual calculated based on selected voltage divider resistors
31.	Vout OP	20.0 V	Op_Point	Operational Output Voltage
32.	Duty Cycle	40.086 %	Op_point	Duty cycle
33.	Efficiency	89.342 %	Op_point	Steady state efficiency
34.	IC Tj	33.425 degC	Op_point	IC junction temperature
35.	ICThetaJA	50.0 degC/W	Op_point	IC junction-to-ambient thermal resistance
36.	IOUT_OP	5.0 A	Op_point	Iout operating point
37.	M1 TJOP	56.991 degC	Op_point	M1 MOSFET junction temperature
38.	Peak Rectified Vin	155.562 V	Op_point	Peak voltage seen at rectified input
39.	Vin_OP_RMS	110.0 V	Op_point	AC Input RMS Voltage
40.	Vout p-p	164.085 mV	Op_point	Peak-to-peak output ripple voltage
41.	Avg Bridge Diode Pd	1.474 W	Power	Average Power Dissipation in the Bridge Diode over the AC Line Period
42.	Cbulk Pd	2.991 W	Power	Bulk capacitor power dissipation
43.	Cout1 Pd	347.407 mW	Power	Output capacitor1 power dissipation
44.	Cx Pd	0.0 W	Power	X-cap Power Dissipation
45.	Cy Pd	187.5 pW	Power	Y-caps Power Dissipation
46.	Dsec Pd	1.307 W	Power	Secondary Diode Power Dissipation
47.	Dsec2 Pd	1.307 W	Power	Secondary Diode Power Dissipation
48.	IC Pd	68.493 mW	Power	IC power dissipation
49.	L1 Pd	500.515 mW	Power	Power Dissipation in the Inductor
50.	L2 Pd	60.0 mW	Power	Average Power Dissipation in the Inductor Over the AC Line Period
51.	M1 Pd	431.851 mW	Power	M1 MOSFET total power dissipation
52.	Paux	17.489 mW	Power	Power Dissipation in Raux and Daux
53.	Pd Rstartup	175.72 mW	Power	Power Dissipation in Rstartup1 and Rstartup2
54.	Rdrv Pd	49.754 μW	Power	Power Dissipation in Gate Drive Resistor
55.	Rfb Pd	10.61 mW	Power	Rfb Power Dissipation
56.	Rsns Pd	449.129 mW	Power	Current Limit Sense Resistor Power Dissipation
57.	Rx Pd	120.961 mW	Power	Total Power Dissipation in Rx1 and Rx2
58.	Snubber Pd	1.401 W	Power	Snubber Power Dissipation
59.	T1 Pd	4.622 W	Power	Estimated Losses in Transformer
60.	Total Pd	11.929 W	Power	Total Power Dissipation
61.	Vout Tolerance	2.095 %		Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable
62.	Vout pp percentage	820.426 m%		Output Voltage ripple percentage

Design Inputs

#	Name	Value	Description
1.	Iout	5.0	Maximum Output Current
2.	VinMax	130.0	Maximum input voltage
3.	VinMin	110.0	Minimum input voltage
4.	Vout	20.0	Output Voltage
5.	acFrequency	60.0	Light Output in Lumen
6.	base_pn	UCC28C45	Texas Instruments Base Part Number
7.	source	AC	Input Source Type
8.	ta	30.0	Ambient temperature

Design Assistance

1. UCC28C45 Product Folder : <http://www.ti.com/product/UCC28C45> : contains the data sheet and other resources.

Texas Instruments' WEBENCH simulation tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Simulations are created using Texas Instruments' published specifications as well as the published specifications of other device manufacturers. While Texas Instruments does update this information periodically, this information may not be current at the time the simulation is built. Texas Instruments does not warrant the accuracy or completeness of the specifications or any information contained therein. Texas Instruments does not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. Texas Instruments does not warrant that the designs are production worthy.

You should completely validate and test your design implementation to confirm the system functionality for your application prior to production.

Use of Texas Instruments' WEBENCH simulation tools is subject to [Texas Instruments' Site Terms and Conditions of Use](#). Prototype boards based on WEBENCH created designs are provided AS IS without warranty of any kind for evaluation and testing purposes and are subject to the terms of the [Evaluation License Agreement](#).