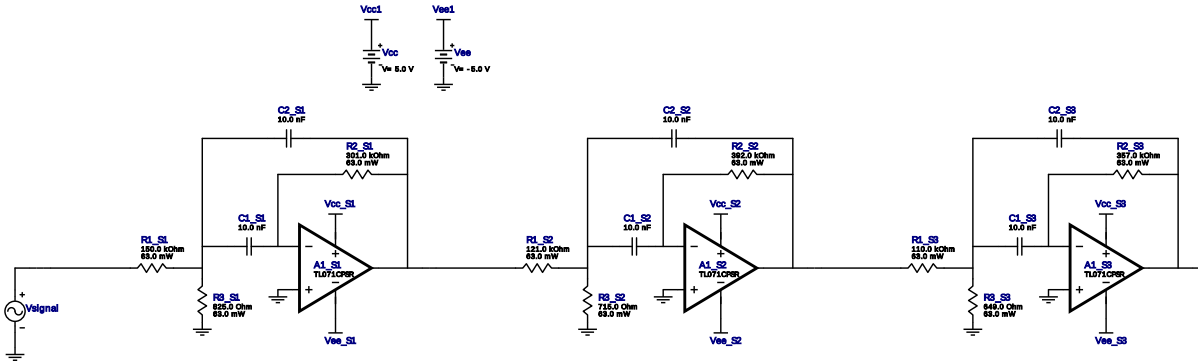


WEBENCH® Design Report

Design : 4354344/52 TL071CPSR
Bandpass, Multiple Feedback, Linear Phase 0.05deg



My Comments

No comments

Electrical BOM

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	A1_S1	Texas Instruments, Inc.	TL071CPSR	GbwTyp= 3.0MHz VccMin= 10.0 V VccMax= 36.0 V	1	\$0.13	 PS0008A 80 mm ²
2.	A1_S2	Texas Instruments, Inc.	TL071CPSR	GbwTyp= 3.0MHz VccMin= 10.0 V VccMax= 36.0 V	1	\$0.13	 PS0008A 80 mm ²
3.	A1_S3	Texas Instruments, Inc.	TL071CPSR	GbwTyp= 3.0MHz VccMin= 10.0 V VccMax= 36.0 V	1	\$0.13	 PS0008A 80 mm ²
4.	C1_S1	Kemet	C0603C103J5RACTU Series= X7R	Cap= 10.0 nF VDC= 50.0 V Tolerance= 5.0 %	1	\$0.01	 0603 5 mm ²
5.	C1_S2	Kemet	C0603C103J5RACTU Series= X7R	Cap= 10.0 nF VDC= 50.0 V Tolerance= 5.0 %	1	\$0.01	 0603 5 mm ²
6.	C1_S3	Kemet	C0603C103J5RACTU Series= X7R	Cap= 10.0 nF VDC= 50.0 V Tolerance= 5.0 %	1	\$0.01	 0603 5 mm ²
7.	C2_S1	Kemet	C0603C103J5RACTU Series= X7R	Cap= 10.0 nF VDC= 50.0 V Tolerance= 5.0 %	1	\$0.01	 0603 5 mm ²
8.	C2_S2	Kemet	C0603C103J5RACTU Series= X7R	Cap= 10.0 nF VDC= 50.0 V Tolerance= 5.0 %	1	\$0.01	 0603 5 mm ²
9.	C2_S3	Kemet	C0603C103J5RACTU Series= X7R	Cap= 10.0 nF VDC= 50.0 V Tolerance= 5.0 %	1	\$0.01	 0603 5 mm ²
10.	R1_S1	Vishay-Dale	CRCW0402150KFKED Series= CRCW..e3	Res= 150.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
11.	R1_S2	Vishay-Dale	CRCW0402121KFKED Series= CRCW..e3	Res= 121.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
12.	R1_S3	Vishay-Dale	CRCW0402110KFKED Series= CRCW..e3	Res= 110.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²
13.	R2_S1	Vishay-Dale	CRCW0402301KFKED Series= CRCW..e3	Res= 301.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²
14.	R2_S2	Vishay-Dale	CRCW0402392KFKED Series= CRCW..e3	Res= 392.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²
15.	R2_S3	Vishay-Dale	CRCW0402357KFKED Series= CRCW..e3	Res= 357.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²
16.	R3_S1	Vishay-Dale	CRCW0402825RFKED Series= CRCW..e3	Res= 825.0 Ohm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²
17.	R3_S2	Vishay-Dale	CRCW0402715RFKED Series= CRCW..e3	Res= 715.0 Ohm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²
18.	R3_S3	Vishay-Dale	CRCW0402649RFKED Series= CRCW..e3	Res= 649.0 Ohm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²

Design Inputs


#	Name	Value	Description
1.	FilterType	Bandpass	
2.	FilterResponse	Linear_Phase_005	
3.	FilterOrder	6.0	
4.	FilterTopology	Multiple_Feedback	
5.	NumberOfStages	3.0	
6.	CenterFrequency	1,000.0	
7.	StopbandAttenuation	-45.0	
8.	PassbandBandwidth	100.0	
9.	StopbandBandwidth	1,000.0	
10.	Gain	1.0	
11.	DualSupply	+/-5.0 V	Power supply(s) to active chips
12.	ResistorTolerance	E96	Resistor series - 1% Passive resistor tolerance
13.	CapacitorTolerance	E24	Capacitor series - 5% Passive capacitance tolerance
14.	SeedCapacitance	10.0 n	Seed Capacitance to start design of filter

Design Assistance

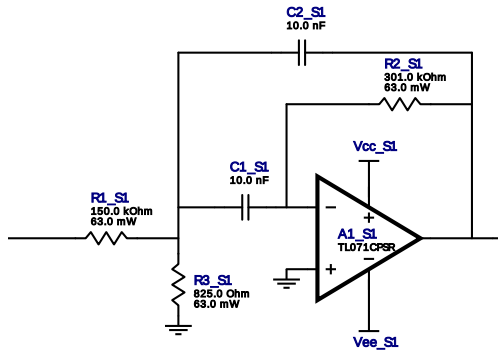1. **TL071CPSR** Product Folder : <http://www.ti.com//product/TL071> : contains the data sheet and other resources.

Filter Stage :1

Cutoff Frequency 1,000.0 Hz
 Min GBW Req'd 956.1 kHz
 Stage Gain 1.0 V/V
 Stage Q 9.561
 Stage Topology Multiple_Feedback




Electrical BOM

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	A1_S1	Texas Instruments, Inc.	TL071CPSR	GbwTyp= 3.0MHz VccMin= 10.0 V VccMax= 36.0 V	1	\$0.13	 PS0008A 80 mm ²
2.	C1_S1	Kemet	C0603C103J5RACTU Series= X7R	Cap= 10.0 nF VDC= 50.0 V Tolerance= 5.0 %	1	\$0.01	 0603 5 mm ²
3.	C2_S1	Kemet	C0603C103J5RACTU Series= X7R	Cap= 10.0 nF VDC= 50.0 V Tolerance= 5.0 %	1	\$0.01	 0603 5 mm ²
4.	R1_S1	Vishay-Dale	CRCW0402150KFKED Series= CRCW..e3	Res= 150.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
5.	R2_S1	Vishay-Dale	CRCW0402301KFKED Series= CRCW..e3	Res= 301.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
6.	R3_S1	Vishay-Dale	CRCW0402825RFKED Series= CRCW..e3	Res= 825.0 Ohm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²

Filter Stage :2

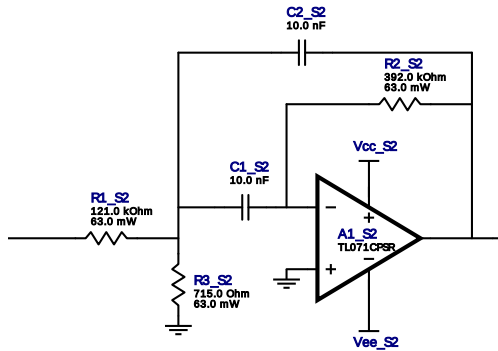Cutoff Frequency 947.766 Hz
 Min GBW Req'd 1.111 MHz
 Stage Gain 1.0 V/V
 Stage Q 11.725
 Stage Topology Multiple_Feedback




Electrical BOM

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	A1_S2	Texas Instruments, Inc.	TL071CPSR	GbwTyp= 3.0MHz VccMin= 10.0 V VccMax= 36.0 V	1	\$0.13	 PS0008A 80 mm ²
2.	C1_S2	Kemet	C0603C103J5RACTU Series= X7R	Cap= 10.0 nF VDC= 50.0 V Tolerance= 5.0 %	1	\$0.01	 0603 5 mm ²
3.	C2_S2	Kemet	C0603C103J5RACTU Series= X7R	Cap= 10.0 nF VDC= 50.0 V Tolerance= 5.0 %	1	\$0.01	 0603 5 mm ²
4.	R1_S2	Vishay-Dale	CRCW0402121KFKED Series= CRCW..e3	Res= 121.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
5.	R2_S2	Vishay-Dale	CRCW0402392KFKED Series= CRCW..e3	Res= 392.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
6.	R3_S2	Vishay-Dale	CRCW0402715RFKED Series= CRCW..e3	Res= 715.0 Ohm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²

Filter Stage :3

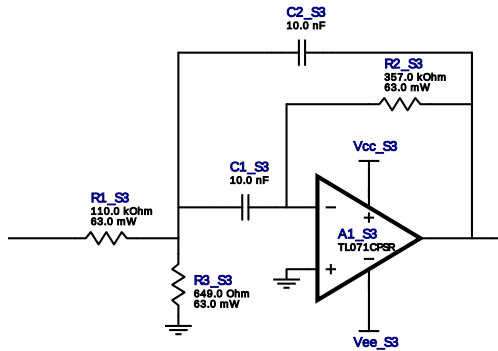Cutoff Frequency 1.055 kHz
 Min GBW Req'd 1.237 MHz
 Stage Gain 1.0 V/V
 Stage Q 11.725
 Stage Topology Multiple_Feedback



Electrical BOM

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	A1_S3	Texas Instruments, Inc.	TL071CPSR	GbwTyp= 3.0MHz VccMin= 10.0 V VccMax= 36.0 V	1	\$0.13	 PS0008A 80 mm ²
2.	C1_S3	Kemet	C0603C103J5RACTU Series= X7R	Cap= 10.0 nF VDC= 50.0 V Tolerance= 5.0 %	1	\$0.01	 0603 5 mm ²
3.	C2_S3	Kemet	C0603C103J5RACTU Series= X7R	Cap= 10.0 nF VDC= 50.0 V Tolerance= 5.0 %	1	\$0.01	 0603 5 mm ²
4.	R1_S3	Vishay-Dale	CRCW0402110KFKED Series= CRCW..e3	Res= 110.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
5.	R2_S3	Vishay-Dale	CRCW0402357KFKED Series= CRCW..e3	Res= 357.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
6.	R3_S3	Vishay-Dale	CRCW0402649RFKED Series= CRCW..e3	Res= 649.0 Ohm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²

Texas Instruments' WEBENCH simulation tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Simulations are created using Texas Instruments' published specifications as well as the published specifications of other device manufacturers. While Texas Instruments does update this information periodically, this information may not be current at the time the simulation is built. Texas Instruments does not warrant the accuracy or completeness of the specifications or any information contained therein. Texas Instruments does not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. Texas Instruments does not warrant that the designs are production worthy.

You should completely validate and test your design implementation to confirm the system functionality for your application prior to production.

Use of Texas Instruments' WEBENCH simulation tools is subject to [Texas Instruments' Site Terms and Conditions of Use](#). Prototype boards based on WEBENCH created designs are provided AS IS without warranty of any kind for evaluation and testing purposes and are subject to the terms of the [Evaluation License Agreement](#).