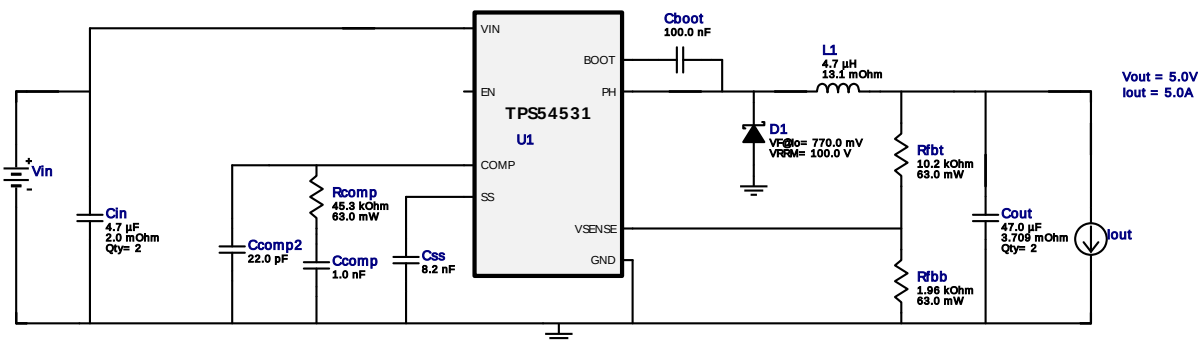


WEBENCH® Design Report





Design : 4739804/7 TPS54531DDAR
TPS54531DDAR 14.0V-22.0V to 5.00V @ 5.0A















Electrical BOM






#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	Cboot	MuRata	GRM155R61A104KA01D Series= X5R	Cap= 100.0 nF VDC= 10.0 V IRMS= 0.0 A	1	\$0.01	0402 3 mm ²
2.	Ccomp	Samsung Electro-Mechanics	CL21C102JBCNFNC Series= C0G/NP0	Cap= 1.0 nF VDC= 50.0 V IRMS= 0.0 A	1	\$0.01	0805 7 mm ²
3.	Ccomp2	Kemet	C0805C220K3GACTU Series= C0G/NP0	Cap= 22.0 pF VDC= 25.0 V IRMS= 0.0 A	1	\$0.01	0805 7 mm ²
4.	Cin	MuRata	GRM32ER71H475KA88L Series= X7R	Cap= 4.7 uF ESR= 2.0 mOhm VDC= 50.0 V IRMS= 5.35 A	2	\$0.19	1210 15 mm ²
5.	Cout	MuRata	GRM31CR61A476KE15L Series= X5R	Cap= 47.0 uF ESR= 3.709 mOhm VDC= 10.0 V IRMS= 4.2862 A	2	\$0.15	1206_190 11 mm ²
6.	Css	MuRata	GRM033R61A822KA01D Series= X5R	Cap= 8.2 nF VDC= 10.0 V IRMS= 0.0 A	1	\$0.01	0201 2 mm ²
7.	D1	Vishay-Semiconductor	50WQ10FNPBF	VF@Io= 770.0 mV VRRM= 100.0 V	1	\$0.74	DPAK 102 mm ²
8.	L1	Coilcraft	XAL6060-472MEB	L= 4.7 uH DCR= 13.1 mOhm	1	\$0.82	XAL6060 72 mm ²
9.	Rcomp	Vishay-Dale	CRCW040245K3FKED Series= CRCW..e3	Res= 45.3 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²
10.	Rfbb	Vishay-Dale	CRCW04021K96FKED Series= CRCW..e3	Res= 1.96 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²
11.	Rfht	Vishay-Dale	CRCW040210K2FKED Series= CRCW..e3	Res= 10.2 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
12.	U1	Texas Instruments	TPS54531DDAR	Switcher	1	\$0.75	 DDA0008E 57 mm ²

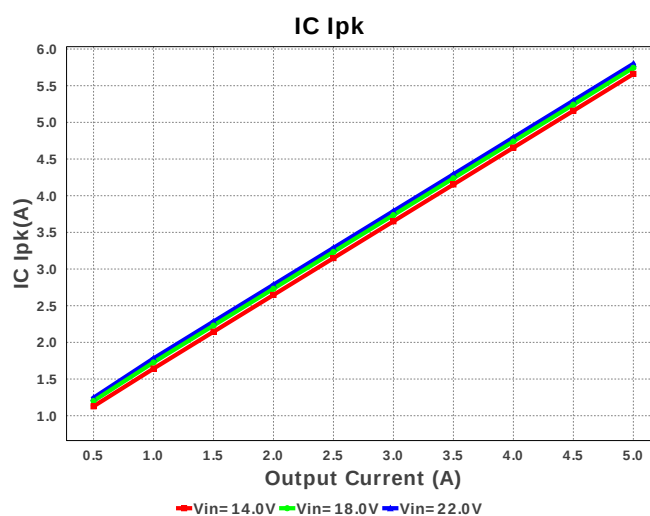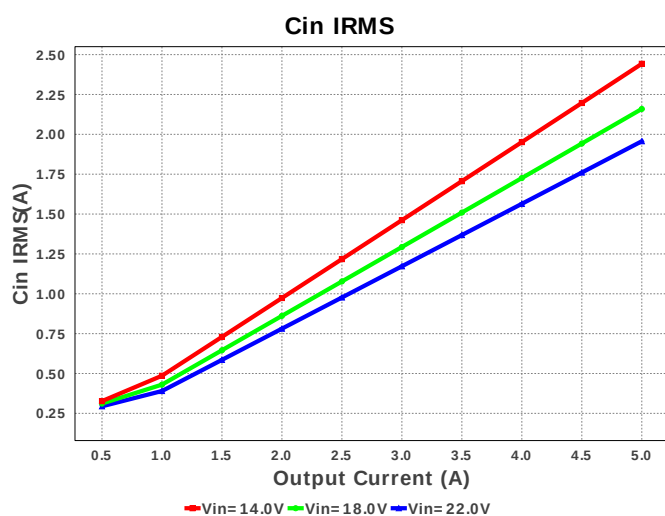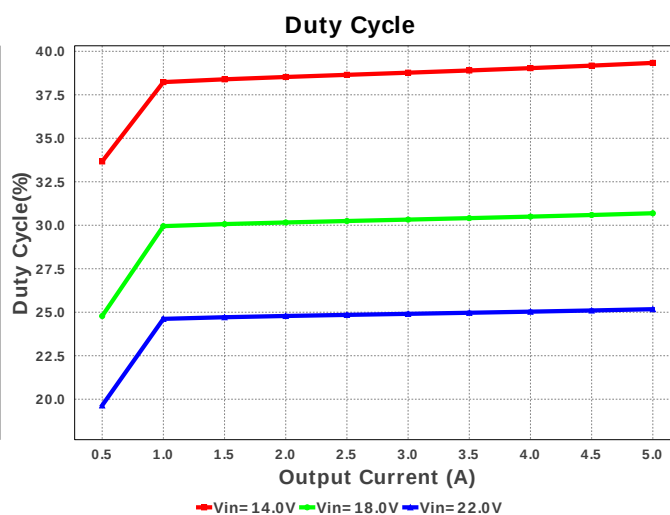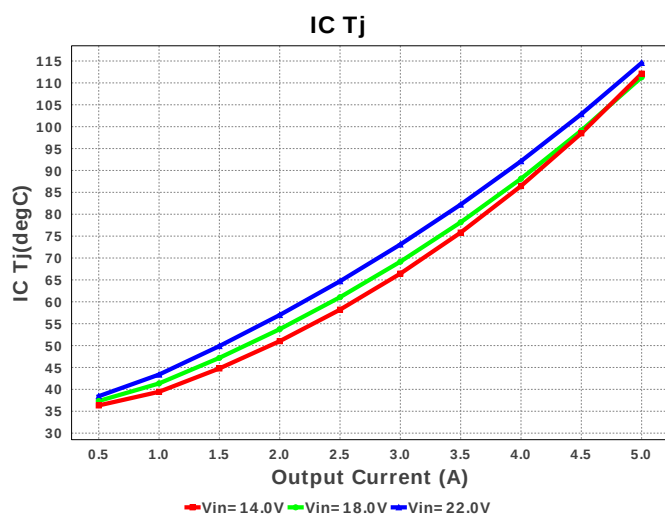

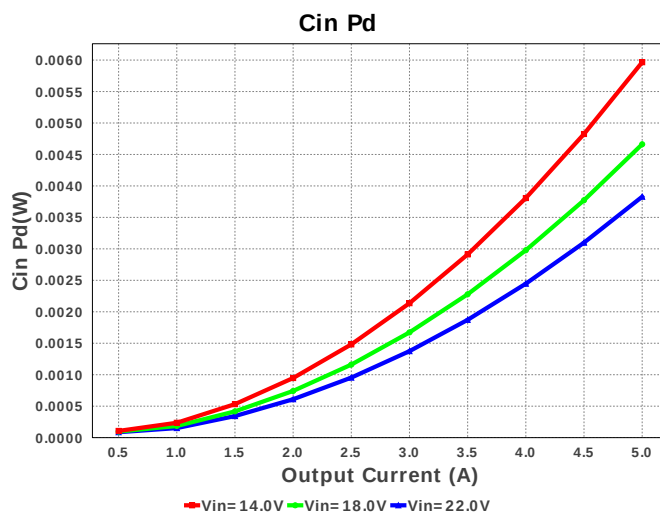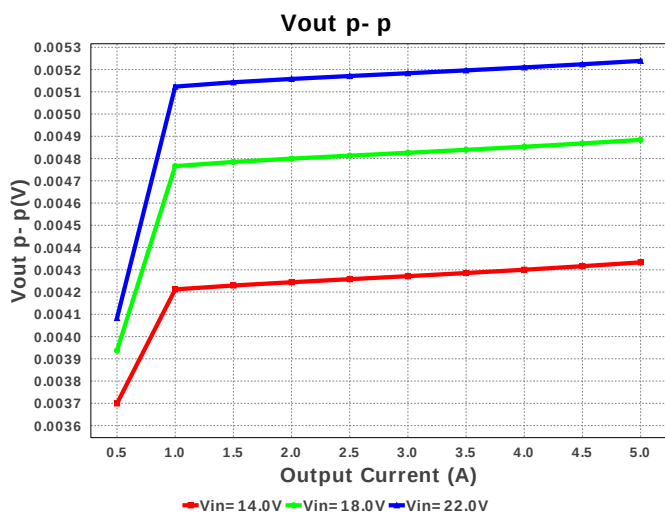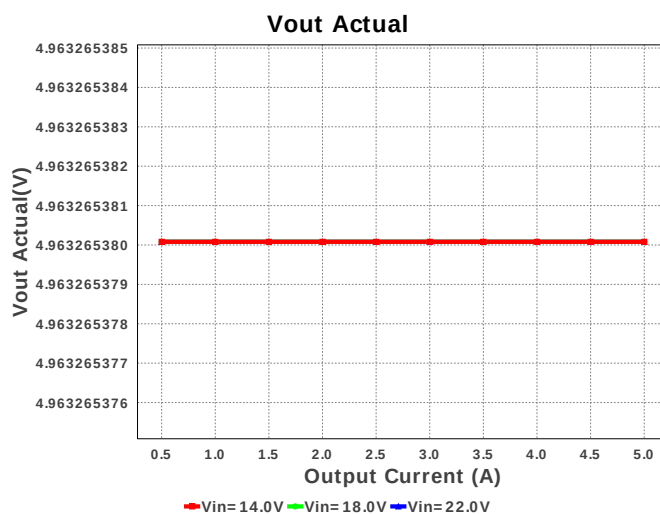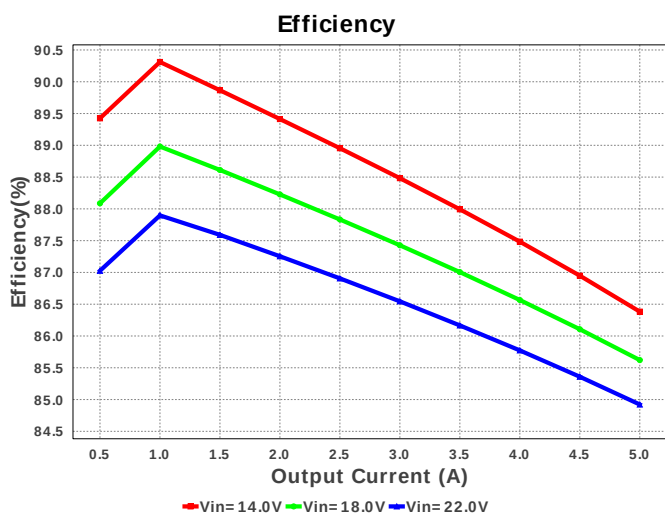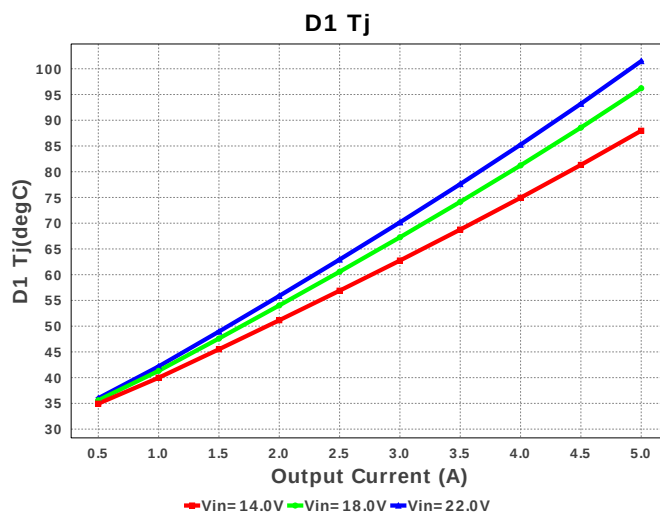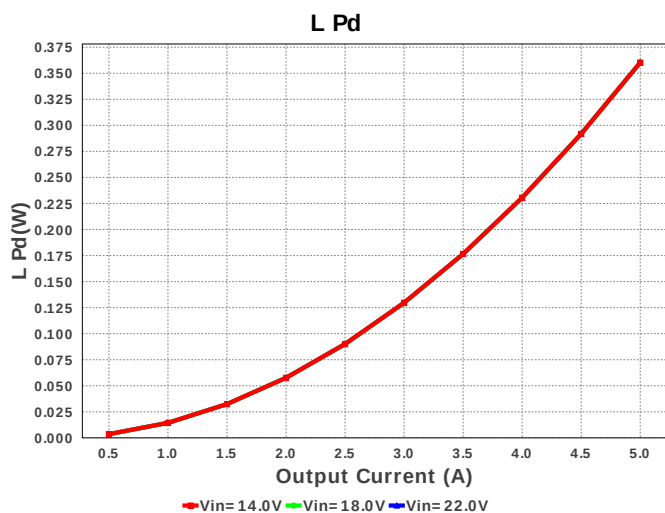

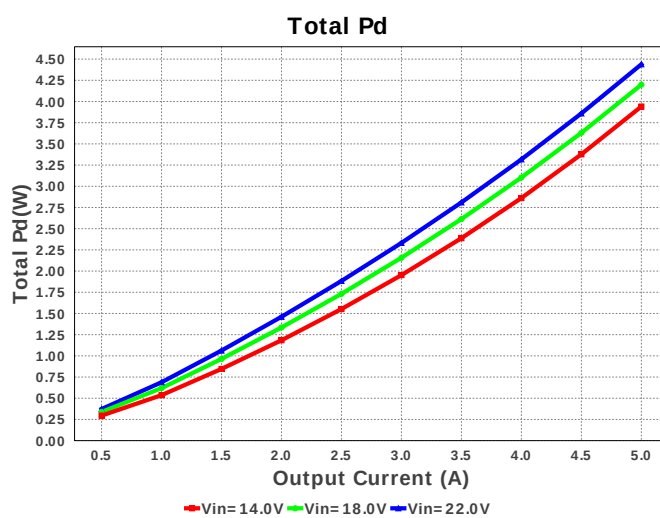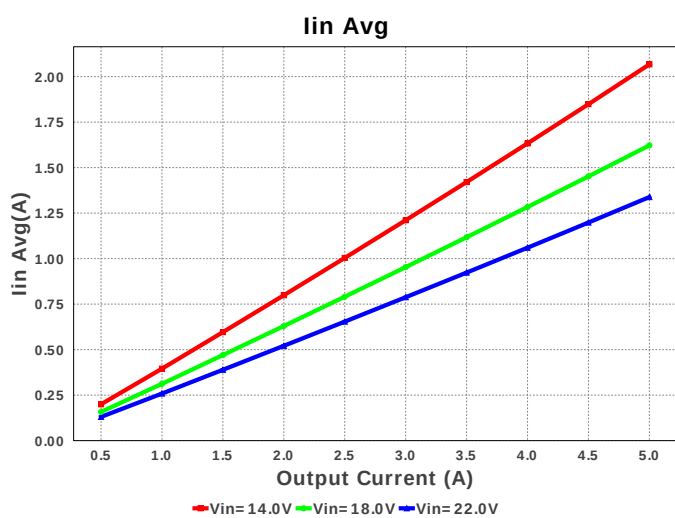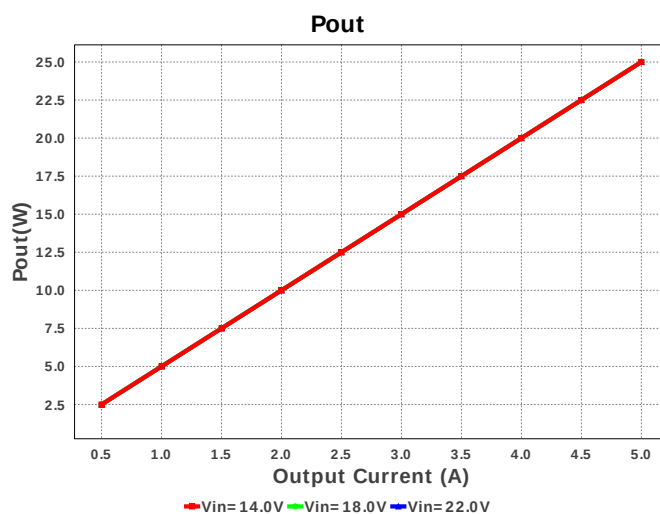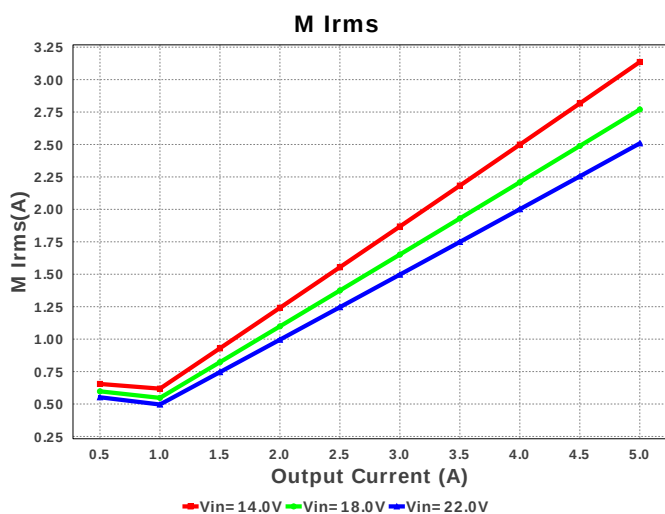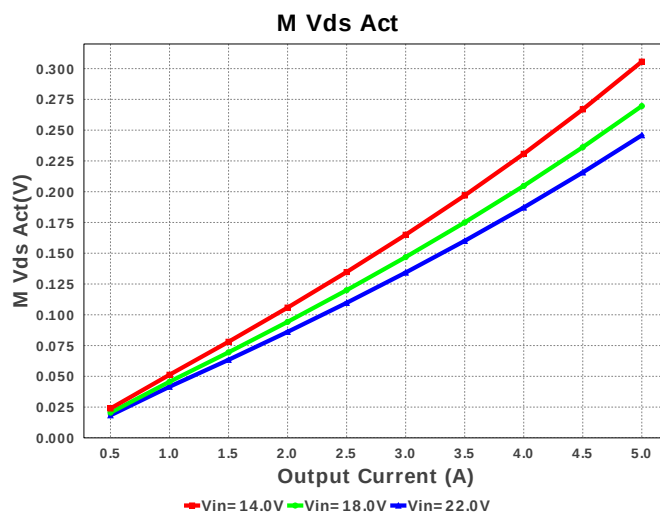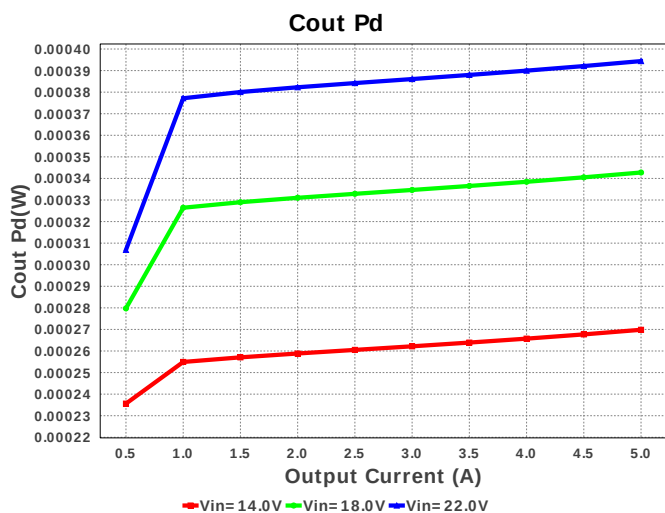

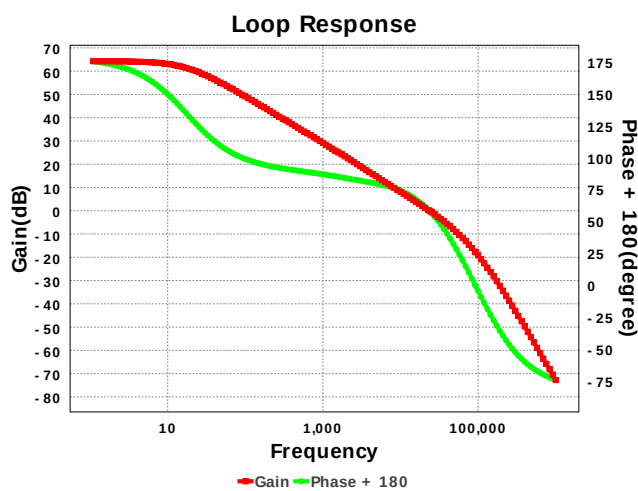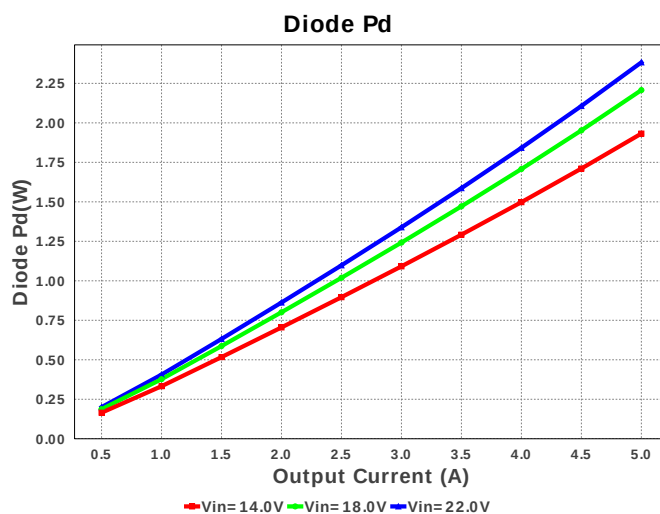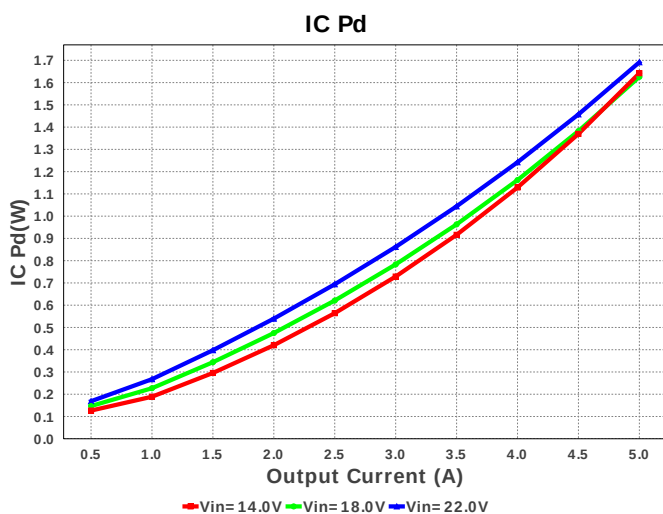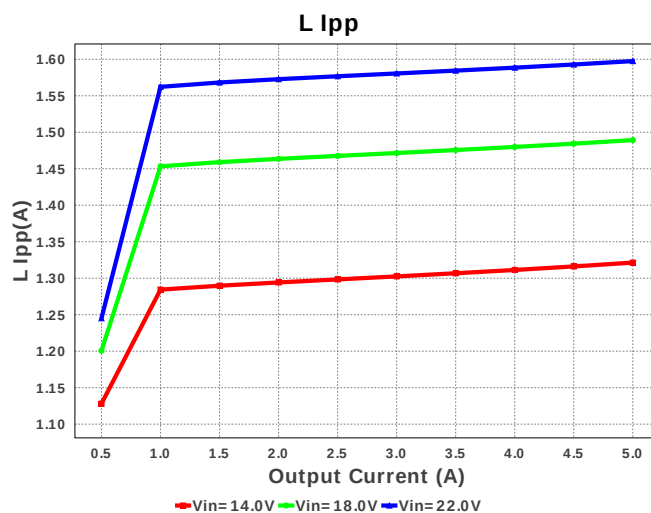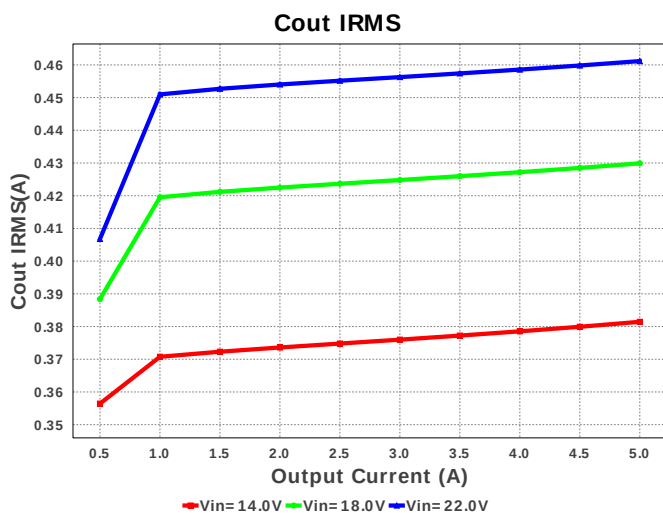

Operating Values

#	Name	Value	Category	Description
1.	BOM Count	14		Total Design BOM count
2.	Total BOM	\$3.06		Total BOM Cost
3.	Cin IRMS	1.957 A	Current	Input capacitor RMS ripple current
4.	Cout IRMS	461.162 mA	Current	Output capacitor RMS ripple current
5.	IC Ipk	5.799 A	Current	Peak switch current in IC
6.	Iin Avg	1.338 A	Current	Average input current
7.	L Ipp	1.598 A	Current	Peak-to-peak inductor ripple current
8.	M1 Irms	2.509 A	Current	Q Iavg
9.	FootPrint	309.0 mm ²	General	Total Foot Print Area of BOM components
10.	Frequency	570.0 kHz	General	Switching frequency
11.	M Vds Act	245.826 mV	General	Voltage drop across the MosFET

#	Name	Value	Category	Description
12.	Pout	25.0 W	General	Total output power
13.	D1 Tj	101.489 degC	Op_Point	D1 junction temperature
14.	Low Freq Gain	64.282 dB	Op_Point	Gain at 10Hz
15.	Vout Actual	4.963 V	Op_Point	Vout Actual calculated based on selected voltage divider resistors
16.	Vout OP	5.0 V	Op_Point	Operational Output Voltage
17.	Cross Freq	23.672 kHz	Op_point	Bode plot crossover frequency
18.	Duty Cycle	25.175 %	Op_point	Duty cycle
19.	Efficiency	84.922 %	Op_point	Steady state efficiency
20.	Gain Marg	-17.872 dB	Op_point	Bode Plot Gain Margin
21.	IC Tj	114.565 degC	Op_point	IC junction temperature
22.	ICThetaJA	50.0 degC/W	Op_point	IC junction-to-ambient thermal resistance
23.	IOUT_OP	5.0 A	Op_point	Iout operating point
24.	Phase Marg	58.722 deg	Op_point	Bode Plot Phase Margin
25.	VIN_OP	22.0 V	Op_point	Vin operating point
26.	Vout p-p	5.239 mV	Op_point	Peak-to-peak output ripple voltage
27.	Cin Pd	3.828 mW	Power	Input capacitor power dissipation
28.	Cout Pd	394.397 μW	Power	Output capacitor power dissipation
29.	Diode Pd	2.383 W	Power	Diode power dissipation
30.	IC Pd	1.691 W	Power	IC power dissipation
31.	L Pd	360.25 mW	Power	Inductor power dissipation
32.	Total Pd	4.439 W	Power	Total Power Dissipation
33.	Vout Tolerance	5.254 %		Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable

Design Inputs

#	Name	Value	Description
1.	Iout	5.0	Maximum Output Current
2.	VinMax	22.0	Maximum input voltage
3.	VinMin	14.0	Minimum input voltage
4.	Vout	5.0	Output Voltage
5.	base_pn	TPS54531	Base Product Number
6.	source	DC	Input Source Type
7.	Ta	30.0	Ambient temperature

Design Assistance

1. **TPS54531** Product Folder : <http://www.ti.com/product/TPS54531> : contains the data sheet and other resources.

Texas Instruments' WEBENCH simulation tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Simulations are created using Texas Instruments' published specifications as well as the published specifications of other device manufacturers. While Texas Instruments does update this information periodically, this information may not be current at the time the simulation is built. Texas Instruments does not warrant the accuracy or completeness of the specifications or any information contained therein. Texas Instruments does not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. Texas Instruments does not warrant that the designs are production worthy.

You should completely validate and test your design implementation to confirm the system functionality for your application prior to production.

Use of Texas Instruments' WEBENCH simulation tools is subject to [Texas Instruments' Site Terms and Conditions of Use](#). Prototype boards based on WEBENCH created designs are provided AS IS without warranty of any kind for evaluation and testing purposes and are subject to the terms of the [Evaluation License Agreement](#).