
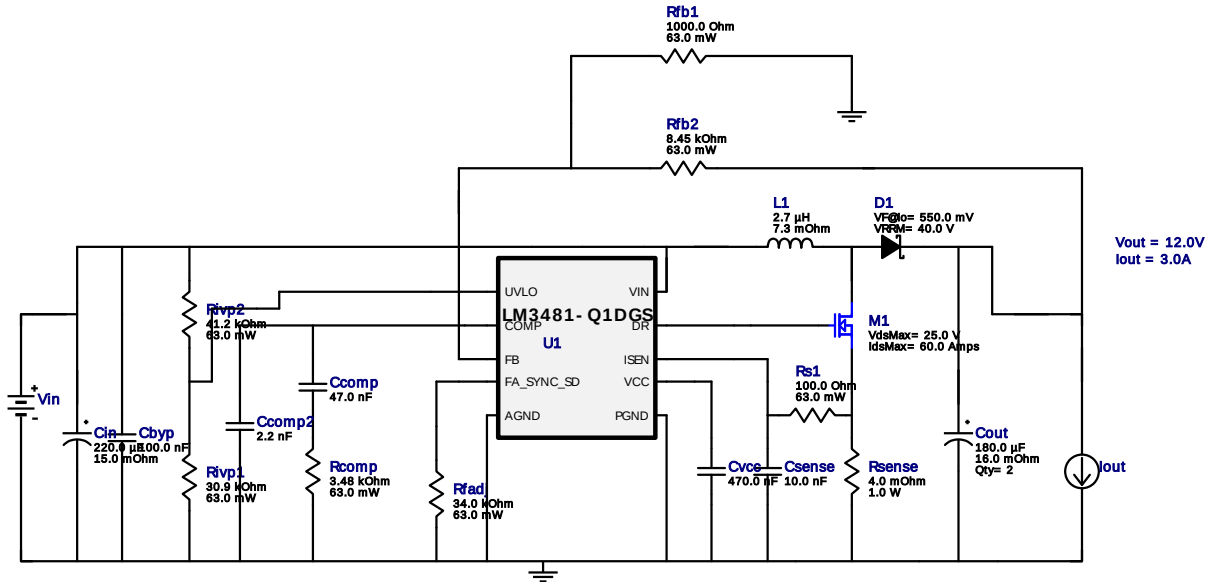


WEBENCH® Design Report






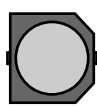
Design : 4737466/36 LM3481QMMX/NOPB
LM3481QMMX/NOPB 3.7V-4.2V to 12.00V @ 3.0A















Electrical BOM







#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	Cbyp	MuRata	GRM155R60J104KA01D Series= X5R	Cap= 100.0 nF VDC= 6.3 V IRMS= 0.0 A	1	\$0.01	 0402 3 mm ²
2.	Ccomp	Taiyo Yuden	TMK212B7473KD-T Series= X7R	Cap= 47.0 nF VDC= 25.0 V IRMS= 0.0 A	1	\$0.01	 0805 7 mm ²
3.	Ccomp2	Yageo America	CC0805KRX7R9BB222 Series= X7R	Cap= 2.2 nF VDC= 50.0 V IRMS= 0.0 A	1	\$0.01	 0805 7 mm ²
4.	Cin	Panasonic	6SVPE220MW Series= SVPE	Cap= 220.0 uF ESR= 15.0 mOhm VDC= 6.3 V IRMS= 3.15 A	1	\$0.20	 CAPSMT_62_E61 53 mm ²
5.	Cout	Panasonic	25SVPF180M Series= ?	Cap= 180.0 uF ESR= 16.0 mOhm VDC= 25.0 V IRMS= 4.65 A	2	\$0.61	 CAPSMT_62_E12 106 mm ²
6.	Csense	MuRata	GRM216R71H103KA01D Series= X7R	Cap= 10.0 nF VDC= 50.0 V IRMS= 0.0 A	1	\$0.01	 0805 7 mm ²
7.	Cvcc	MuRata	GRM155C80J474KE19D Series= X6S	Cap= 470.0 nF VDC= 6.3 V IRMS= 0.0 A	1	\$0.01	 0402 3 mm ²
8.	D1	Diodes Inc.	B540C-13-F	VF@Io= 550.0 mV VRRM= 40.0 V	1	\$0.17	 SMC 83 mm ²







#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
9.	L1	Bourns	SRP1250-2R7M	L= 2.7 μ H DCR= 7.3 mOhm	1	\$0.64	 SRP1250 253 mm ²
10.	M1	Texas Instruments	CSD16323Q3	VdsMax= 25.0 V IdsMax= 60.0 Amps	1	\$0.44	 TRANS_NexFET_Q3 18 mm ²
11.	Rcomp	Vishay-Dale	CRCW04023K48FKED Series= CRCW..e3	Res= 3.48 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
12.	Rfadj	Vishay-Dale	CRCW040234K0FKED Series= CRCW..e3	Res= 34.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
13.	Rfb1	Vishay-Dale	CRCW04021K00FKED Series= CRCW..e3	Res= 1000.0 Ohm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
14.	Rfb2	Vishay-Dale	CRCW04028K45FKED Series= CRCW..e3	Res= 8.45 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
15.	Rivp1	Vishay-Dale	CRCW040230K9FKED Series= CRCW..e3	Res= 30.9 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
16.	Rivp2	Vishay-Dale	CRCW040241K2FKED Series= CRCW..e3	Res= 41.2 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
17.	Rs1	Vishay-Dale	CRCW0402100RFKED Series= CRCW..e3	Res= 100.0 Ohm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
18.	Rsense	Panasonic	ERJ-M1WSF4M0U Series= ERJ	Res= 4.0 mOhm Power= 1.0 W Tolerance= 1.0%	1	\$0.15	 2512 43 mm ²
19.	U1	Texas Instruments	LM3481QMMX/NOPB	Switcher	1	\$0.96	 MUB10A 24 mm ²

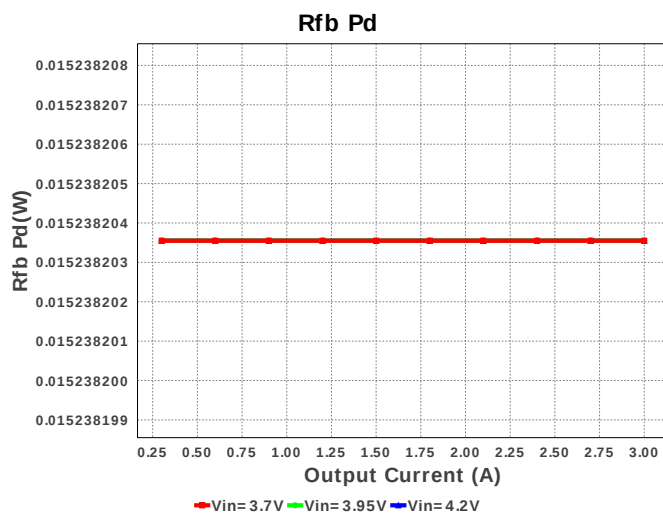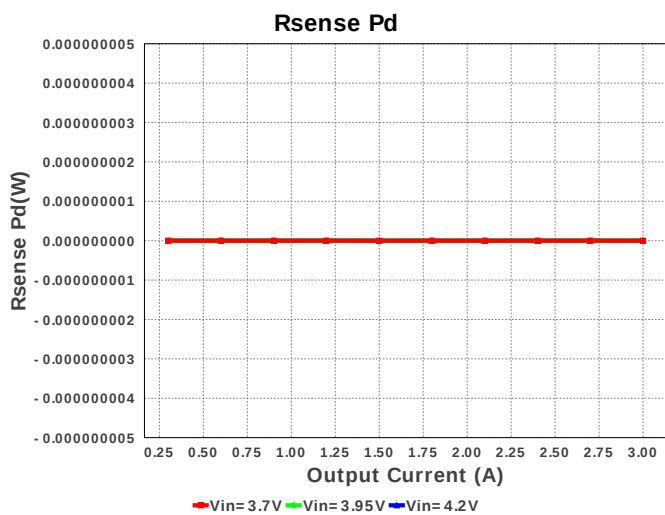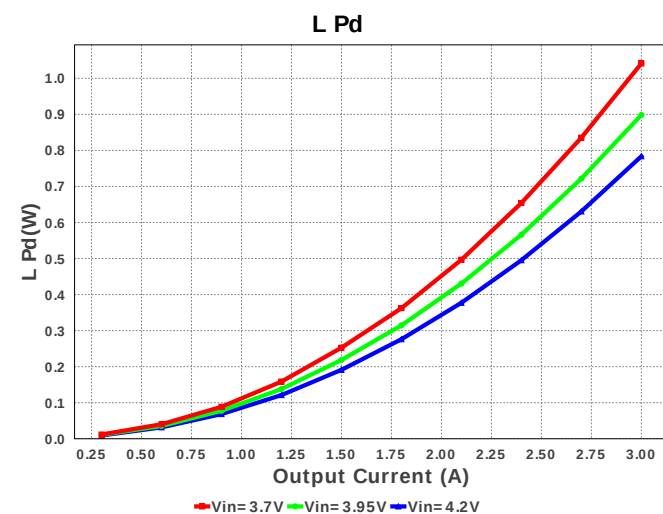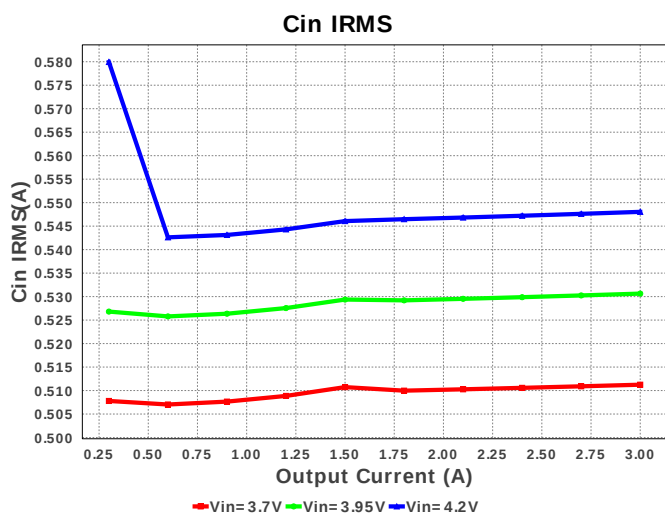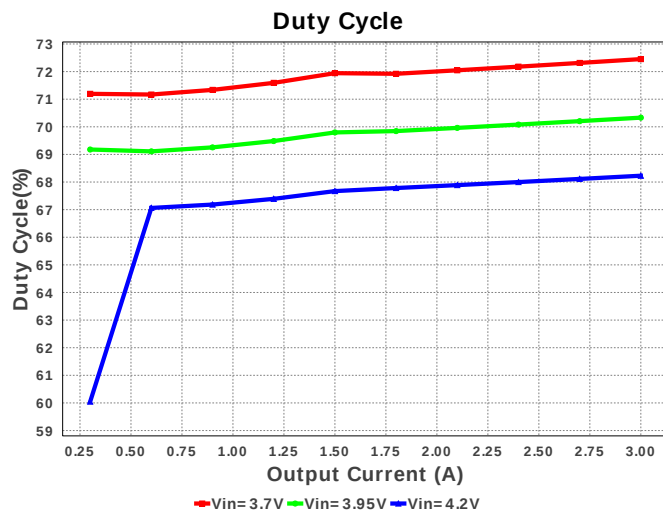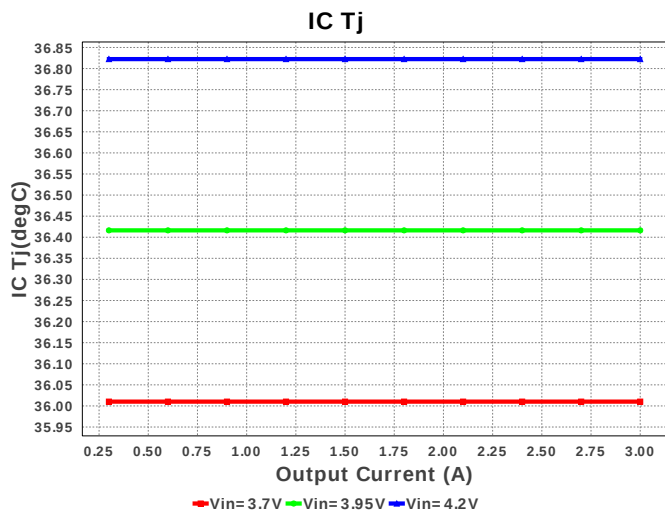

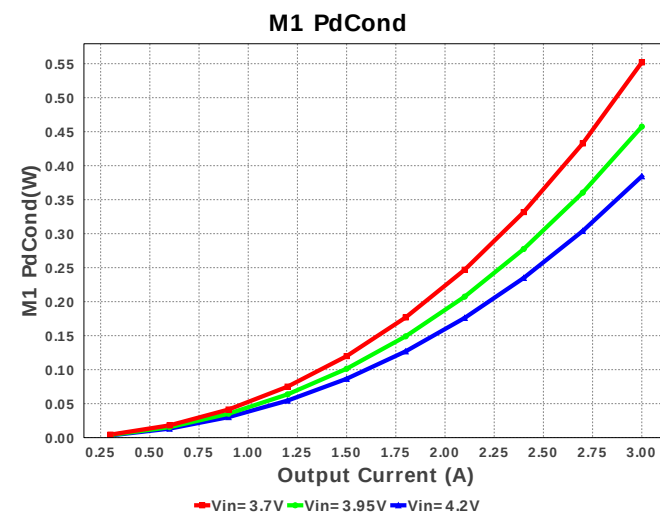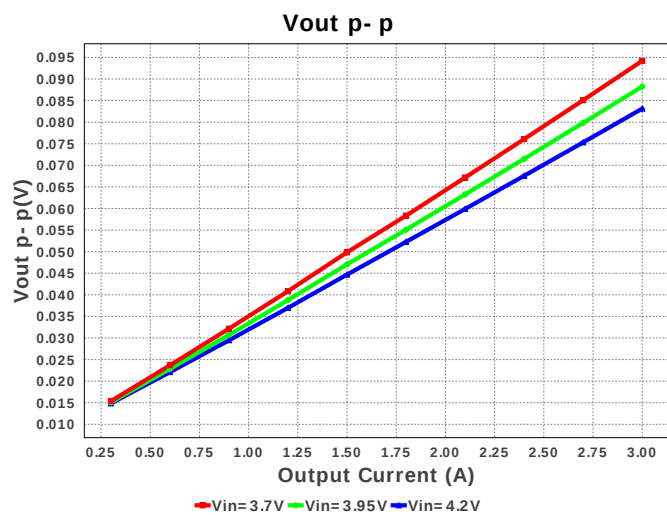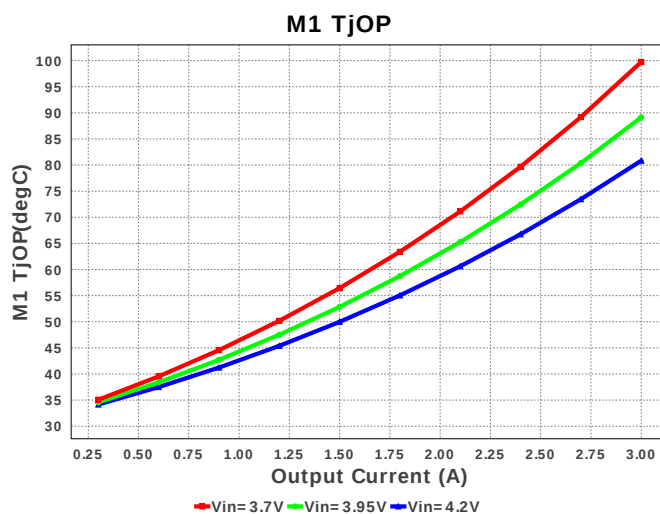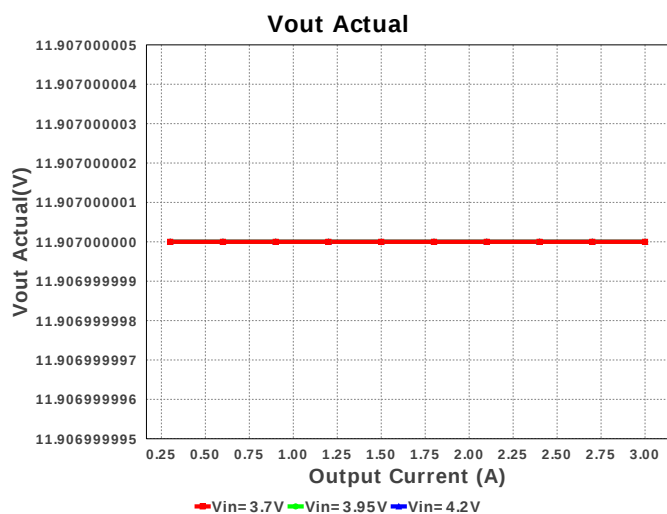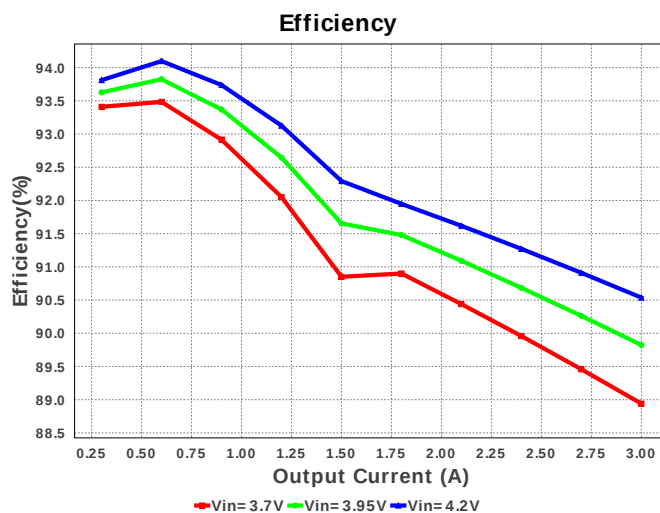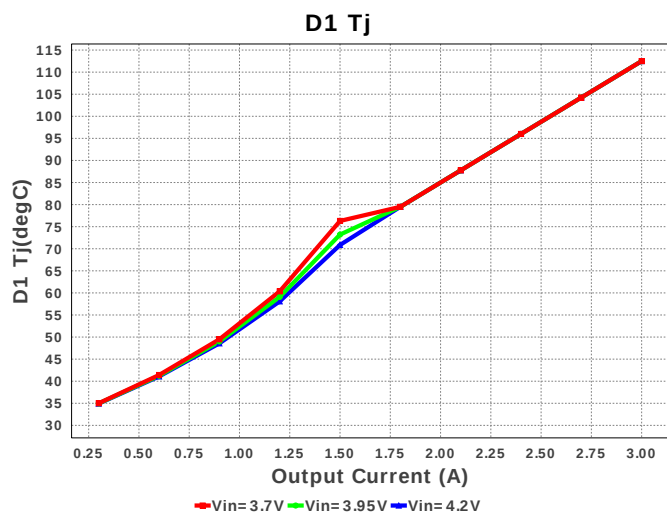

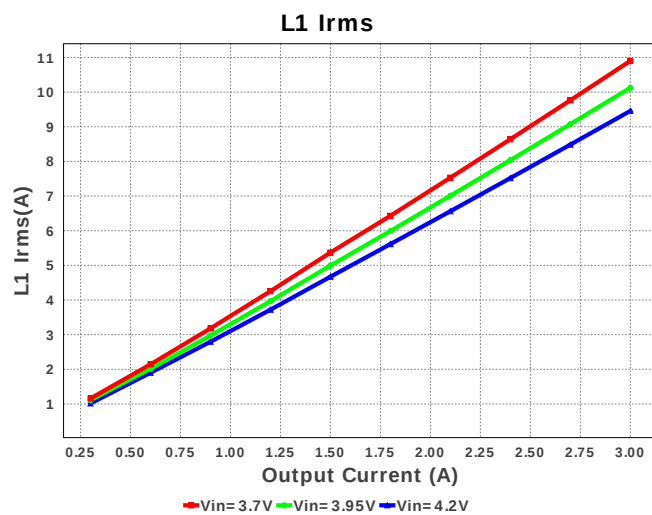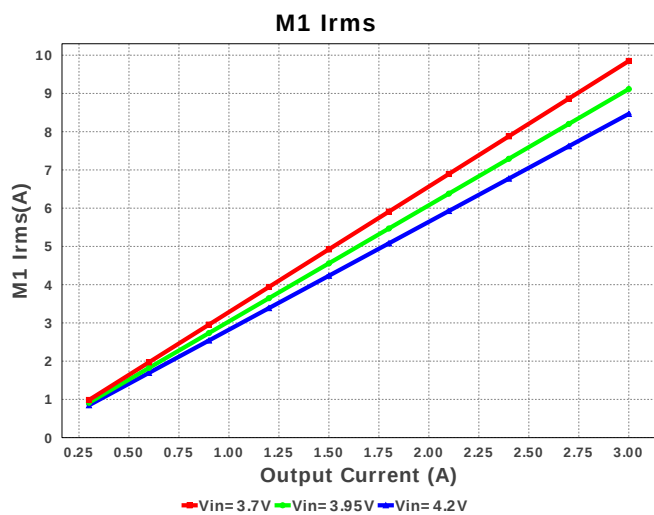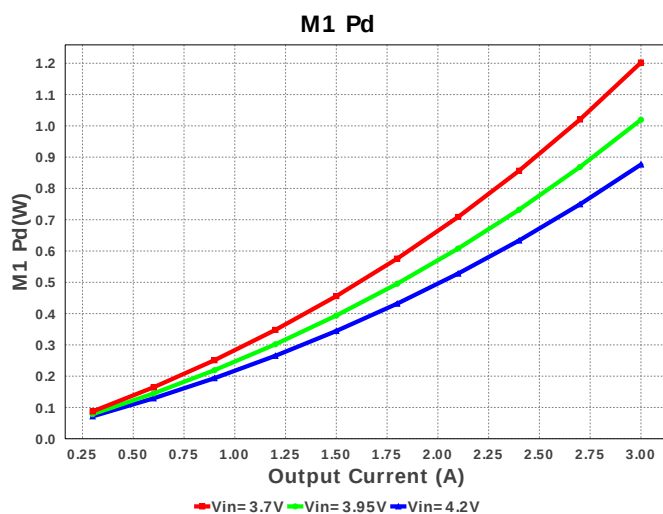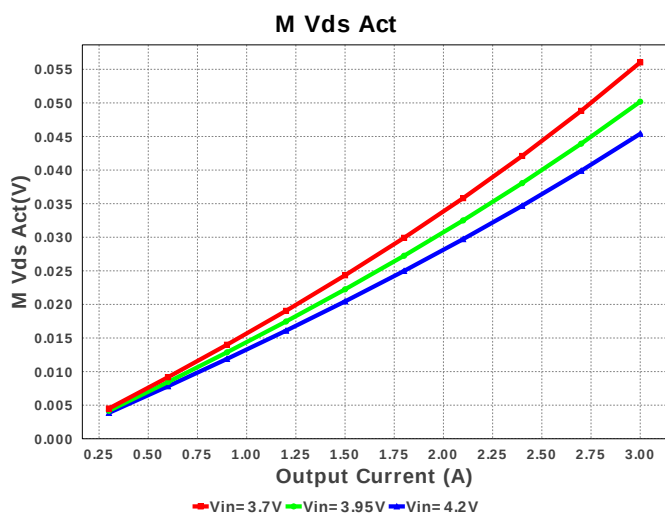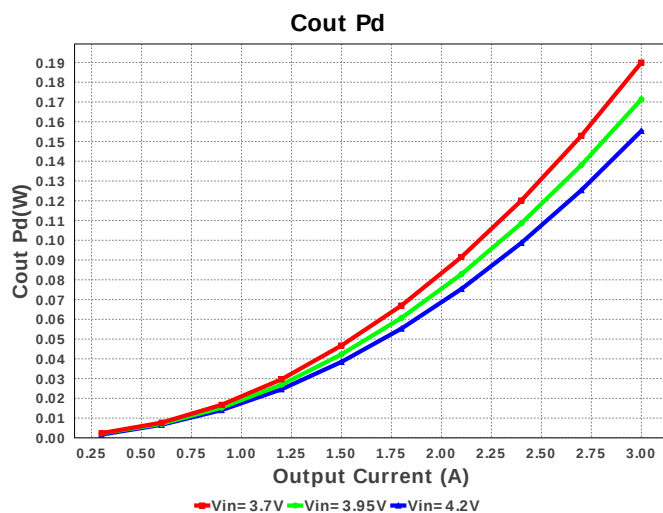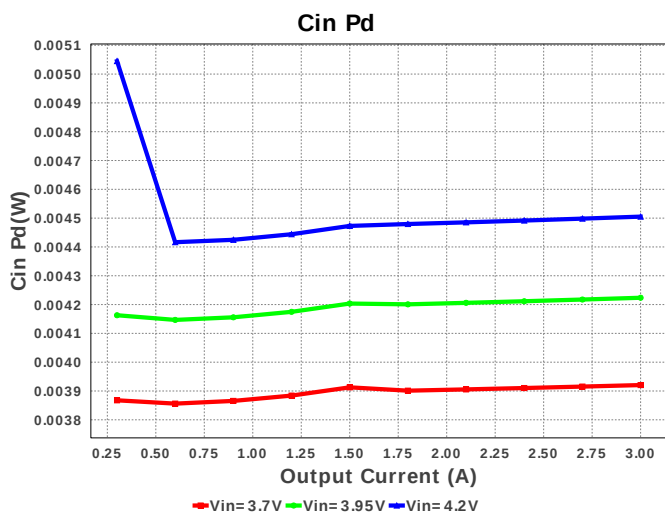

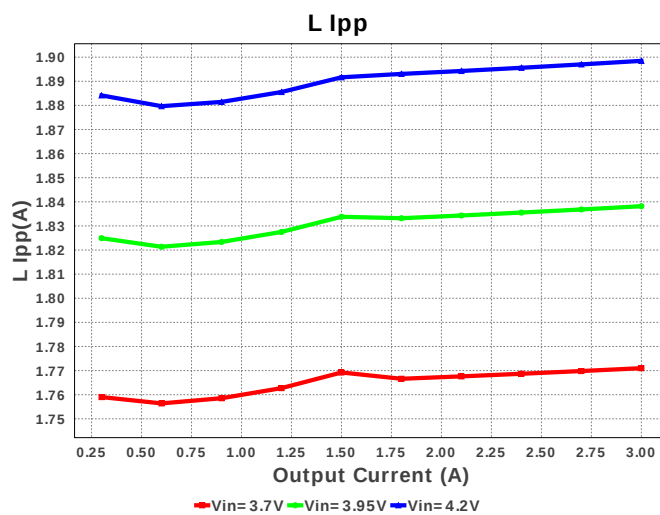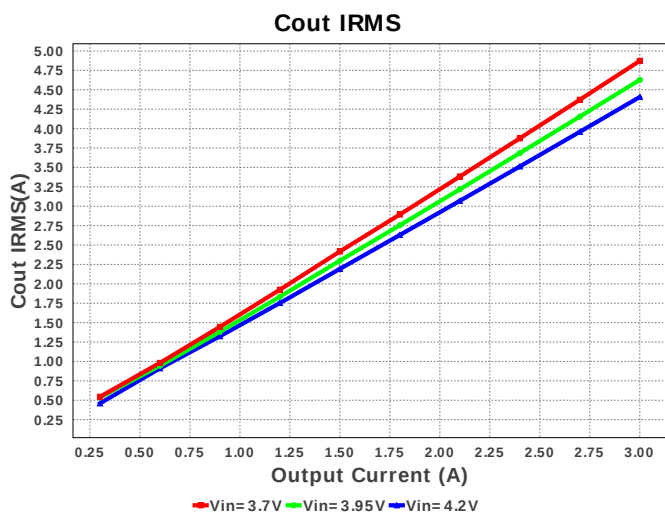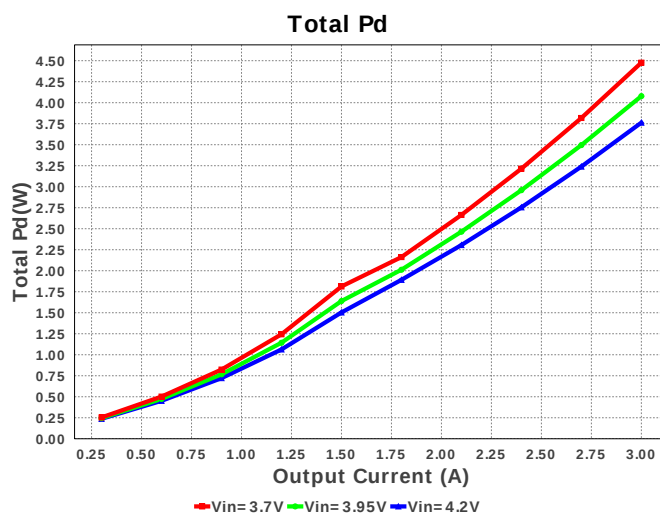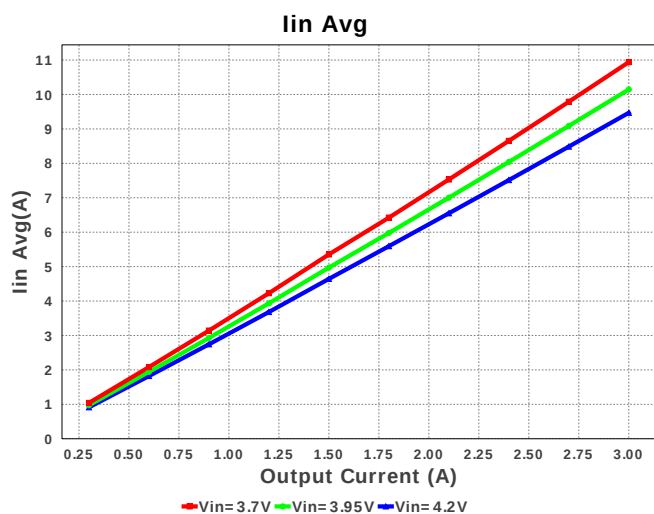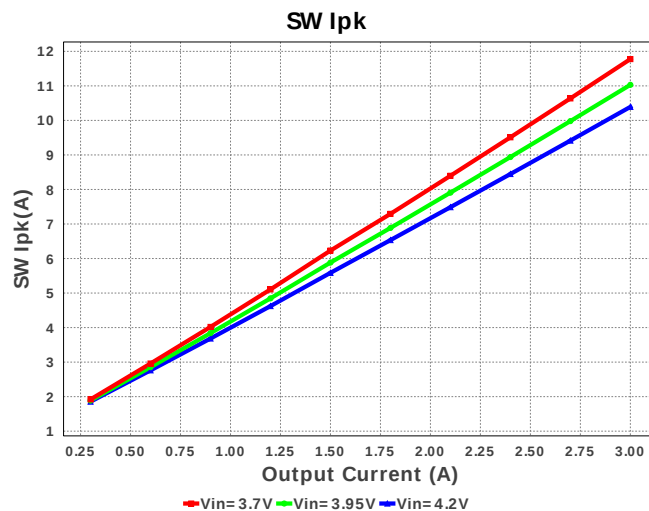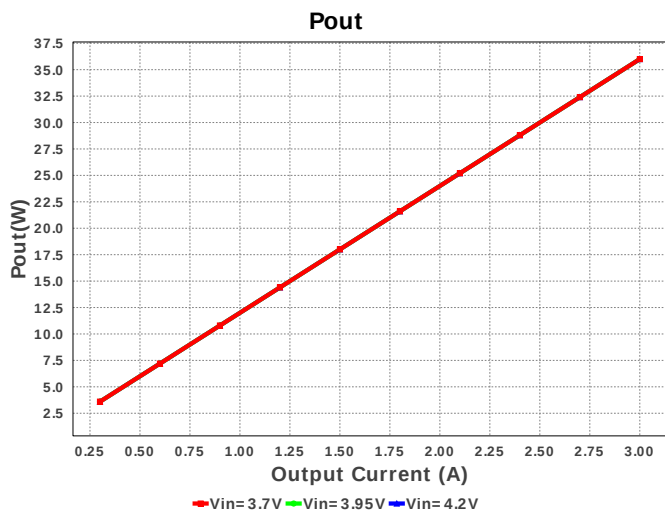

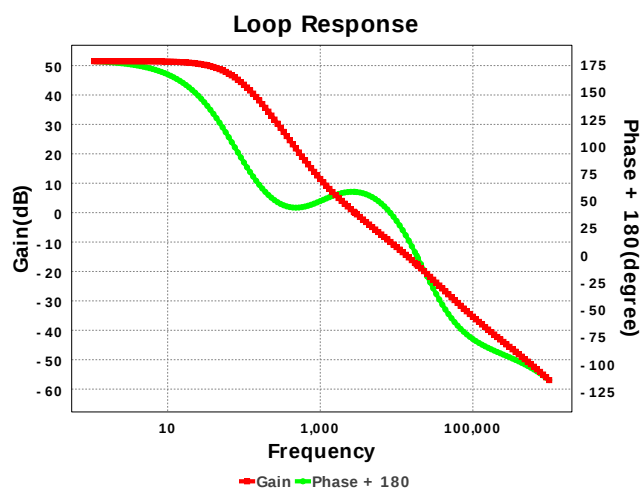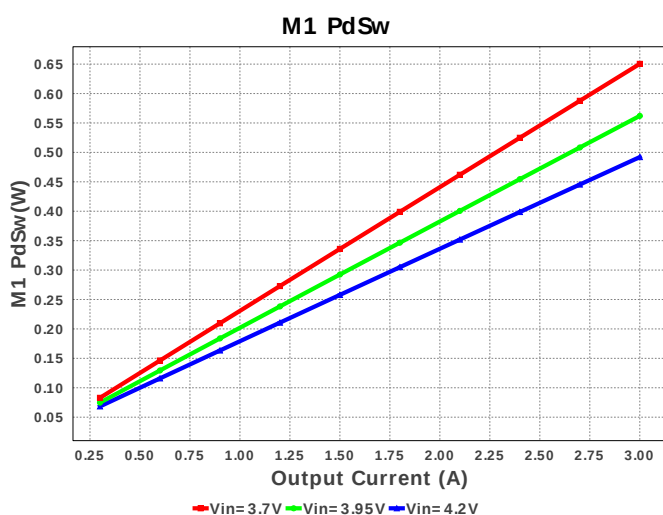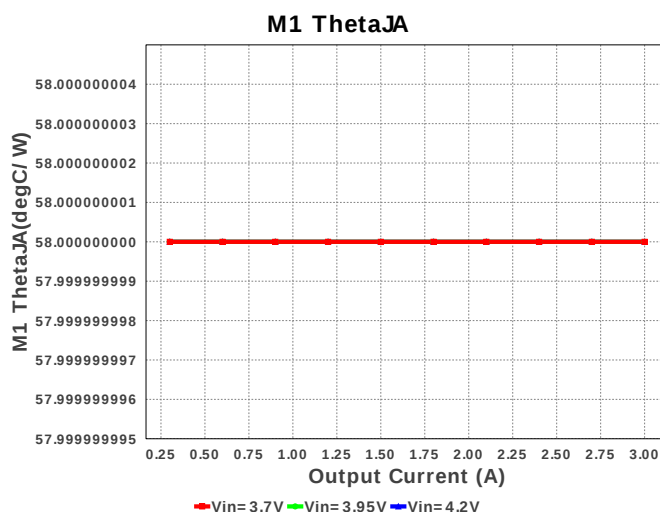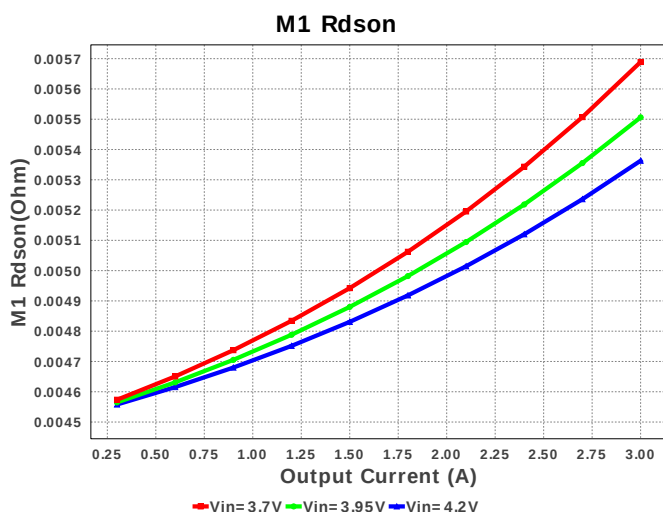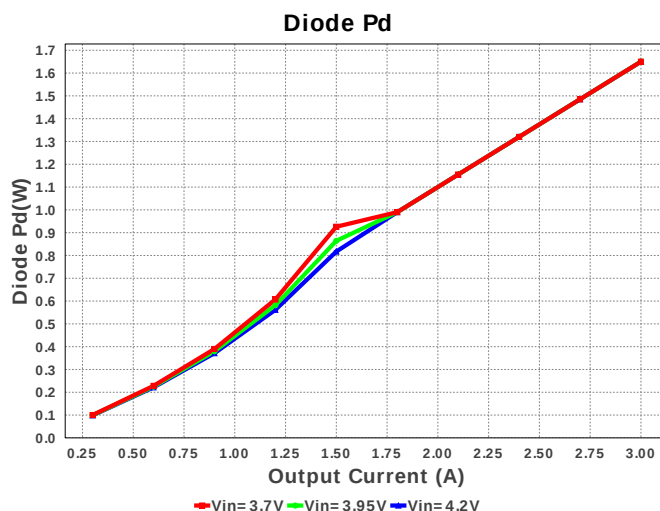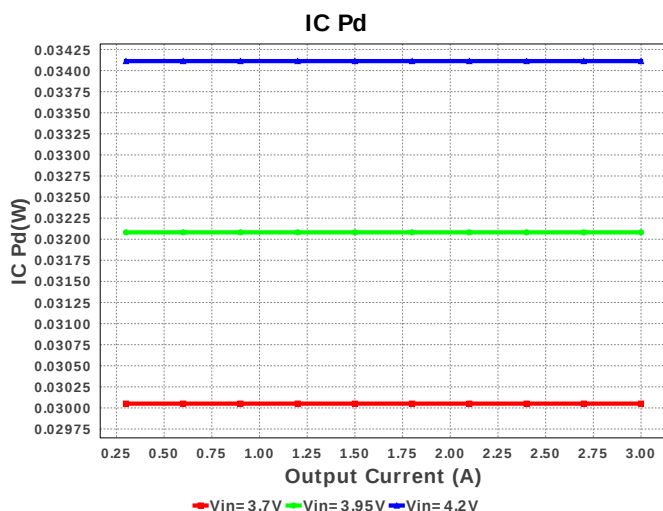

Operating Values

#	Name	Value	Category	Description
1.	Cin IRMS	511.22 mA	Current	Input capacitor RMS ripple current
2.	Cout IRMS	4.872 A	Current	Output capacitor RMS ripple current
3.	Iin Avg	10.938 A	Current	Average input current
4.	L Ipp	1.771 A	Current	Peak-to-peak inductor ripple current
5.	L1 Irms	10.901 A	Current	Inductor ripple current
6.	M1 Irms	9.849 A	Current	M1 MOSFET Irms
7.	SW Ipk	11.774 A	Current	Peak switch current
8.	BOM Count	20	General	Total Design BOM count
9.	FootPrint	734.0 mm ²	General	Total Foot Print Area of BOM components
10.	Frequency	554.021 kHz	General	Switching frequency
11.	IC Tolerance	19.0 mV	General	IC Feedback Tolerance

#	Name	Value	Category	Description
12.	M Vds Act	55.982 mV	General	M Vds
13.	M1 Rdson	5.684 mOhm	General	Drain-Source On-resistance
14.	M1 ThetaJA	58.0 degC/W	General	MOSFET junction-to-ambient thermal resistance
15.	Pout	36.0 W	General	Total output power
16.	Total BOM	\$3.9	General	Total BOM Cost
17.	D1 Tj	112.5 degC	Op_Point	D1 junction temperature
18.	Low Freq Gain	50.248 dB	Op_Point	Gain at 10Hz
19.	Vout Actual	11.907 V	Op_Point	Vout Actual calculated based on selected voltage divider resistors
20.	Vout OP	12.0 V	Op_Point	Operational Output Voltage
21.	Cross Freq	2.511 kHz	Op_point	Bode plot crossover frequency
22.	Duty Cycle	72.448 %	Op_point	Duty cycle
23.	Efficiency	88.953 %	Op_point	Steady state efficiency
24.	Gain Marg	-16.626 dB	Op_point	Bode Plot Gain Margin
25.	IC Tj	35.988 degC	Op_point	IC junction temperature
26.	ICThetaJA	200.0 degC/W	Op_point	IC junction-to-ambient thermal resistance
27.	IOUT_OP	3.0 A	Op_point	Iout operating point
28.	M1 TjOP	99.432 degC	Op_point	M1 MOSFET junction temperature
29.	Phase Marg	56.702 deg	Op_point	Bode Plot Phase Margin
30.	VIN_OP	3.7 V	Op_point	Vin operating point
31.	Vout p-p	94.193 mV	Op_point	Peak-to-peak output ripple voltage
32.	Cin Pd	3.92 mW	Power	Input capacitor power dissipation
33.	Cout Pd	189.905 mW	Power	Output capacitor power dissipation
34.	Diode Pd	1.65 W	Power	Diode power dissipation
35.	IC Pd	29.94 mW	Power	IC power dissipation
36.	L Pd	1.041 W	Power	Inductor power dissipation
37.	M1 Pd	1.197 W	Power	M1 MOSFET total power dissipation
38.	M1 PdCond	551.385 mW	Power	M1 MOSFET conduction losses
39.	M1 PdSw	645.715 mW	Power	M1 MOSFET switching losses
40.	Rfb Pd	15.238 mW	Power	Rfb Power Dissipation
41.	Rsense Pd	421.129 mW	Power	Rsense Power Dissipation
42.	Total Pd	4.471 W	Power	Total Power Dissipation
43.	Vout Tolerance	3.342 %		Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable

Design Inputs

#	Name	Value	Description
1.	Iout	3.0	Maximum Output Current
2.	VinMax	4.2	Maximum input voltage
3.	VinMin	3.7	Minimum input voltage
4.	Vout	12.0	Output Voltage
5.	base_pn	LM3481-Q1	Texas Instruments Base Part Number
6.	source	DC	Input Source Type
7.	ta	30.0	Ambient temperature

Design Assistance

1. Feature Highlights: Automotive Qualified, Wide supply voltage range Operation of 2.97V to 48V, 1A High Frequency Low side N-FET versatile High Performance Controller

2. LM3481-Q1 Product Folder : <http://www.ti.com/product/LM3481%2DQ1> : contains the data sheet and other resources.

Texas Instruments' WEBENCH simulation tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Simulations are created using Texas Instruments' published specifications as well as the published specifications of other device manufacturers. While Texas Instruments does update this information periodically, this information may not be current at the time the simulation is built. Texas Instruments does not warrant the accuracy or completeness of the specifications or any information contained therein. Texas Instruments does not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. Texas Instruments does not warrant that the designs are production worthy.

You should completely validate and test your design implementation to confirm the system functionality for your application prior to production.

Use of Texas Instruments' WEBENCH simulation tools is subject to [Texas Instruments' Site Terms and Conditions of Use](#). Prototype boards based on WEBENCH created designs are provided AS IS without warranty of any kind for evaluation and testing purposes and are subject to the terms of the [Evaluation License Agreement](#).