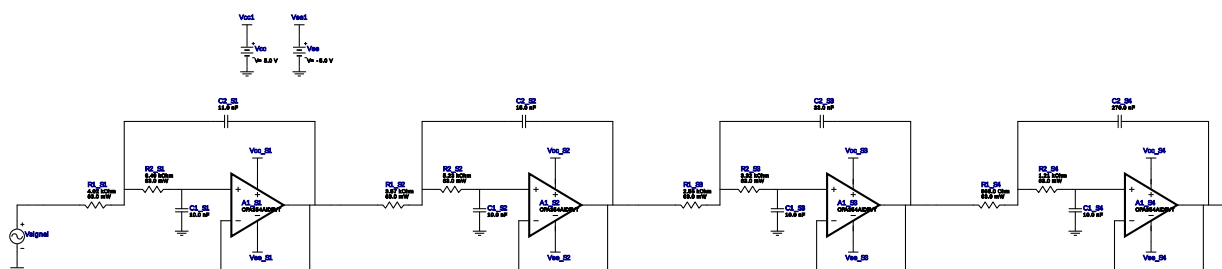


WEBENCH[®] Design Report

Design : 4738714/9 OPA354AIDBVT
Lowpass, Sallen Key, Butterworth



My Comments

No comments

Electrical BOM

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	A1_S1	Texas Instruments, Inc.	OPA354AIDBVT	GbwTyp= 250.0MHz VccMin= 2.5 V VccMax= 5.5 V	1	\$0.80	 DBV0005A 15 mm ²
2.	A1_S2	Texas Instruments, Inc.	OPA354AIDBVT	GbwTyp= 250.0MHz VccMin= 2.5 V VccMax= 5.5 V	1	\$0.80	 DBV0005A 15 mm ²
3.	A1_S3	Texas Instruments, Inc.	OPA354AIDBVT	GbwTyp= 250.0MHz VccMin= 2.5 V VccMax= 5.5 V	1	\$0.80	 DBV0005A 15 mm ²
4.	A1_S4	Texas Instruments, Inc.	OPA354AIDBVT	GbwTyp= 250.0MHz VccMin= 2.5 V VccMax= 5.5 V	1	\$0.80	 DBV0005A 15 mm ²
5.	C1_S1	Kemet	C0603C103J5RACTU Series= X7R	Cap= 10.0 nF VDC= 50.0 V Tolerance= 5.0 %	1	\$0.01	 0603 5 mm ²
6.	C1_S2	Kemet	C0603C103J5RACTU Series= X7R	Cap= 10.0 nF VDC= 50.0 V Tolerance= 5.0 %	1	\$0.01	 0603 5 mm ²
7.	C1_S3	Kemet	C0603C103J5RACTU Series= X7R	Cap= 10.0 nF VDC= 50.0 V Tolerance= 5.0 %	1	\$0.01	 0603 5 mm ²
8.	C1_S4	Kemet	C0603C103J5RACTU Series= X7R	Cap= 10.0 nF VDC= 50.0 V Tolerance= 5.0 %	1	\$0.01	 0603 5 mm ²
9.	C2_S1	Samsung Electro-Mechanics	CL32C113JBHNNNE Series= C0G/NP0	Cap= 11.0 nF VDC= 50.0 V Tolerance= 5.0 %	1	\$0.10	 1210 15 mm ²
10.	C2_S2	Kemet	C0603C153G4GAC7867 Series= C0G/NP0	Cap= 15.0 nF VDC= 16.0 V Tolerance= 2.0 %	1	\$0.21	 0603 5 mm ²
11.	C2_S3	AVX	08053A332JAT2A Series= C0G/NP0	Cap= 33.0 nF VDC= 25.0 V Tolerance= 5.0 %	1	\$0.06	 0805 7 mm ²
12.	C2_S4	Kemet	C2220C274J5GACTU Series= C0G/NP0	Cap= 270.0 nF VDC= 50.0 V Tolerance= 5.0 %	1	\$1.68	 2220 54 mm ²

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
13.	R1_S1	Vishay-Dale	CRCW04024K02FKED Series= CRCW..e3	Res= 4.02 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²
14.	R1_S2	Vishay-Dale	CRCW04023K57FKED Series= CRCW..e3	Res= 3.57 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²
15.	R1_S3	Vishay-Dale	CRCW04022K55FKED Series= CRCW..e3	Res= 2.55 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²
16.	R1_S4	Vishay-Dale	CRCW0402866RFKED Series= CRCW..e3	Res= 866.0 Ohm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²
17.	R2_S1	Vishay-Dale	CRCW04026K49FKED Series= CRCW..e3	Res= 6.49 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²
18.	R2_S2	Vishay-Dale	CRCW04025K23FKED Series= CRCW..e3	Res= 5.23 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²
19.	R2_S3	Vishay-Dale	CRCW04023K32FKED Series= CRCW..e3	Res= 3.32 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²
20.	R2_S4	Vishay-Dale	CRCW04021K21FKED Series= CRCW..e3	Res= 1.21 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²

Design Inputs


#	Name	Value	Description
1.	FilterType	Lowpass	
2.	FilterResponse	Butterworth	
3.	FilterOrder	8.0	
4.	FilterTopology	Sallen_Key	
5.	NumberOfStages	4.0	
6.	PassbandFrequency	3.0 k	
7.	StopbandAttenuation	-45.0	
8.	StopbandFrequency	6.0 k	
9.	Gain	1.0	
10.	DualSupply	+/-5.0 V	Power supply(s) to active chips
11.	ResistorTolerance	E96	Resistor series - 1% Passive resistor tolerance
12.	CapacitorTolerance	E24	Capacitor series - 5% Passive capacitance tolerance
13.	SeedCapacitance	10.0 n	Seed Capacitance to start design of filter

Design Assistance

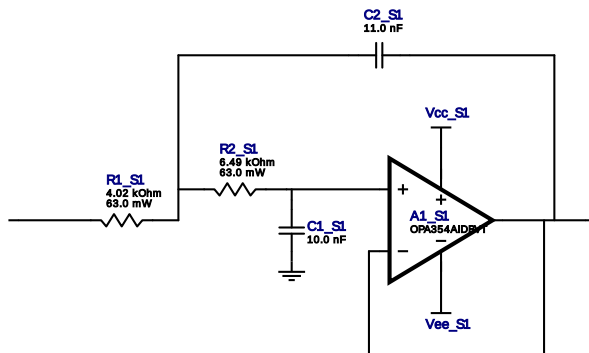1. **OPA354AIDBVT** Product Folder : <http://www.ti.com/product/OPA354> : contains the data sheet and other resources.

Filter Stage :1

Cutoff Frequency 3.0 kHz
 Min GBW Req'd 153.0 kHz
 Stage Gain 1.0 V/V
 Stage Q 510.0 m
 Stage Topology Sallen_Key




Electrical BOM

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	A1_S1	Texas Instruments, Inc.	OPA354AIDBVT	GbwTyp= 250.0MHz VccMin= 2.5 V VccMax= 5.5 V	1	\$0.80	 DBV0005A 15 mm ²
2.	C1_S1	Kemet	C0603C103J5RACTU Series= X7R	Cap= 10.0 nF VDC= 50.0 V Tolerance= 5.0 %	1	\$0.01	 0603 5 mm ²
3.	C2_S1	Samsung Electro-Mechanics	CL32C113JBHNNNE Series= C0G/NP0	Cap= 11.0 nF VDC= 50.0 V Tolerance= 5.0 %	1	\$0.10	 1210 15 mm ²
4.	R1_S1	Vishay-Dale	CRCW04024K02FKED Series= CRCW..e3	Res= 4.02 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
5.	R2_S1	Vishay-Dale	CRCW04026K49FKED Series= CRCW..e3	Res= 6.49 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²

Filter Stage :2

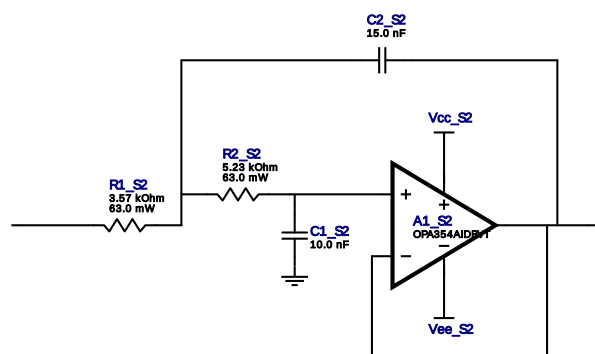Cutoff Frequency 3.0 kHz
 Min GBW Req'd 180.0 kHz
 Stage Gain 1.0 V/V
 Stage Q 600.0 m
 Stage Topology Sallen_Key




Electrical BOM

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	A1_S2	Texas Instruments, Inc.	OPA354AIDBVT	GbwTyp= 250.0MHz VccMin= 2.5 V VccMax= 5.5 V	1	\$0.80	 DBV0005A 15 mm ²
2.	C1_S2	Kemet	C0603C103J5RACTU Series= X7R	Cap= 10.0 nF VDC= 50.0 V Tolerance= 5.0 %	1	\$0.01	 0603 5 mm ²
3.	C2_S2	Kemet	C0603C153G4GAC7867 Series= C0G/NP0	Cap= 15.0 nF VDC= 16.0 V Tolerance= 2.0 %	1	\$0.21	 0603 5 mm ²
4.	R1_S2	Vishay-Dale	CRCW04023K57FKED Series= CRCW..e3	Res= 3.57 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
5.	R2_S2	Vishay-Dale	CRCW04025K23FKED Series= CRCW..e3	Res= 5.23 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²

Filter Stage :3

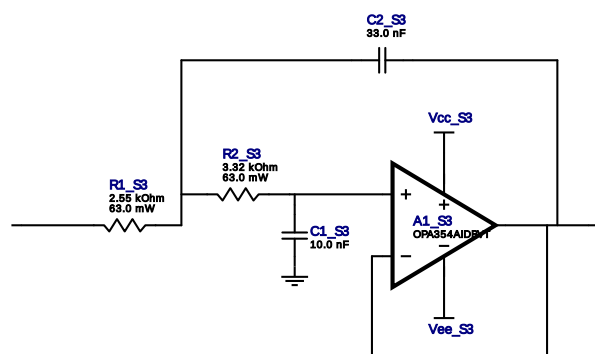Cutoff Frequency 3.0 kHz
 Min GBW Req'd 270.0 kHz
 Stage Gain 1.0 V/V
 Stage Q 900.0 m
 Stage Topology Sallen_Key




Electrical BOM

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	A1_S3	Texas Instruments, Inc.	OPA354AIDBVT	GbwTyp= 250.0MHz VccMin= 2.5 V VccMax= 5.5 V	1	\$0.80	 DBV0005A 15 mm ²
2.	C1_S3	Kemet	C0603C103J5RACTU Series= X7R	Cap= 10.0 nF VDC= 50.0 V Tolerance= 5.0 %	1	\$0.01	 0603 5 mm ²
3.	C2_S3	AVX	08053A332JAT2A Series= C0G/NP0	Cap= 33.0 nF VDC= 25.0 V Tolerance= 5.0 %	1	\$0.06	 0805 7 mm ²
4.	R1_S3	Vishay-Dale	CRCW04022K55FKED Series= CRCW..e3	Res= 2.55 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
5.	R2_S3	Vishay-Dale	CRCW04023K32FKED Series= CRCW..e3	Res= 3.32 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²

Filter Stage :4

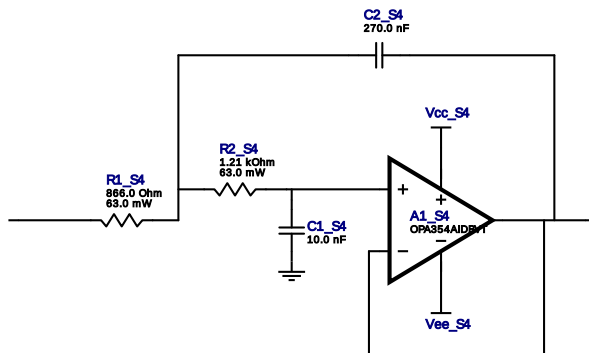Cutoff Frequency 3.0 kHz
 Min GBW Req'd 768.0 kHz
 Stage Gain 1.0 V/V
 Stage Q 2.56
 Stage Topology Sallen_Key



Electrical BOM

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	A1_S4	Texas Instruments, Inc.	OPA354AIDBVT	GbwTyp= 250.0MHz VccMin= 2.5 V VccMax= 5.5 V	1	\$0.80	 DBV0005A 15 mm²
2.	C1_S4	Kemet	C0603C103J5RACTU Series= X7R	Cap= 10.0 nF VDC= 50.0 V Tolerance= 5.0 %	1	\$0.01	 0603 5 mm²
3.	C2_S4	Kemet	C2220C274J5GACTU Series= C0G/NP0	Cap= 270.0 nF VDC= 50.0 V Tolerance= 5.0 %	1	\$1.68	 2220 54 mm²
4.	R1_S4	Vishay-Dale	CRCW0402866RFKED Series= CRCW..e3	Res= 866.0 Ohm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm²
5.	R2_S4	Vishay-Dale	CRCW04021K21FKED Series= CRCW..e3	Res= 1.21 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm²

Texas Instruments' WEBENCH simulation tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Simulations are created using Texas Instruments' published specifications as well as the published specifications of other device manufacturers. While Texas Instruments does update this information periodically, this information may not be current at the time the simulation is built. Texas Instruments does not warrant the accuracy or completeness of the specifications or any information contained therein. Texas Instruments does not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. Texas Instruments does not warrant that the designs are production worthy.

You should completely validate and test your design implementation to confirm the system functionality for your application prior to production.

Use of Texas Instruments' WEBENCH simulation tools is subject to [Texas Instruments' Site Terms and Conditions of Use](#). Prototype boards based on WEBENCH created designs are provided AS IS without warranty of any kind for evaluation and testing purposes and are subject to the terms of the [Evaluation License Agreement](#).