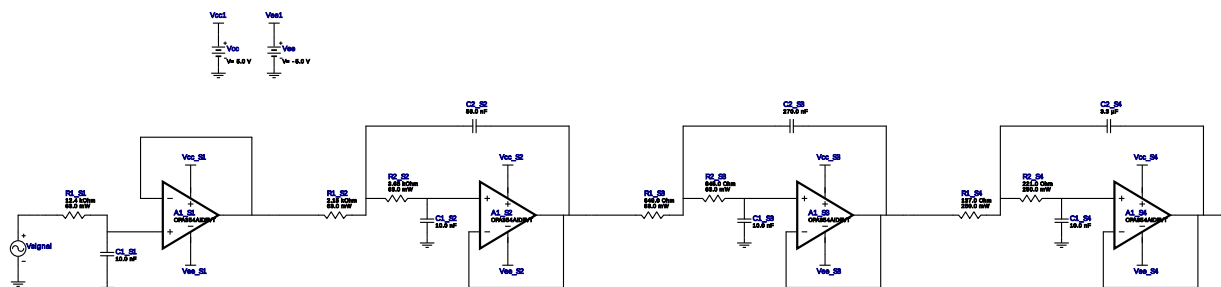


WEBENCH[®] Design Report

Design : 4738714/10 OPA354AIDBVT
Lowpass, Sallen Key, Chebyshev 0.5 dB



My Comments

No comments

Electrical BOM

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	A1_S1	Texas Instruments, Inc.	OPA354AIDBVT	GbwTyp= 250.0MHz VccMin= 2.5 V VccMax= 5.5 V	1	\$0.80	 DBV0005A 15 mm ²
2.	A1_S2	Texas Instruments, Inc.	OPA354AIDBVT	GbwTyp= 250.0MHz VccMin= 2.5 V VccMax= 5.5 V	1	\$0.80	 DBV0005A 15 mm ²
3.	A1_S3	Texas Instruments, Inc.	OPA354AIDBVT	GbwTyp= 250.0MHz VccMin= 2.5 V VccMax= 5.5 V	1	\$0.80	 DBV0005A 15 mm ²
4.	A1_S4	Texas Instruments, Inc.	OPA354AIDBVT	GbwTyp= 250.0MHz VccMin= 2.5 V VccMax= 5.5 V	1	\$0.80	 DBV0005A 15 mm ²
5.	C1_S1	Kemet	C0603C103J5RACTU Series= X7R	Cap= 10.0 nF VDC= 50.0 V Tolerance= 5.0 %	1	\$0.01	 0603 5 mm ²
6.	C1_S2	Kemet	C0603C103J5RACTU Series= X7R	Cap= 10.0 nF VDC= 50.0 V Tolerance= 5.0 %	1	\$0.01	 0603 5 mm ²
7.	C1_S3	Kemet	C0603C103J5RACTU Series= X7R	Cap= 10.0 nF VDC= 50.0 V Tolerance= 5.0 %	1	\$0.01	 0603 5 mm ²
8.	C1_S4	Kemet	C0603C103J5RACTU Series= X7R	Cap= 10.0 nF VDC= 50.0 V Tolerance= 5.0 %	1	\$0.01	 0603 5 mm ²
9.	C2_S2	AVX	12065A562JAT2A Series= C0G/NP0	Cap= 56.0 nF VDC= 50.0 V Tolerance= 5.0 %	1	\$0.11	 1206 11 mm ²
10.	C2_S3	Kemet	C2220C274J5GACTU Series= C0G/NP0	Cap= 270.0 nF VDC= 50.0 V Tolerance= 5.0 %	1	\$1.68	 2220 54 mm ²
11.	C2_S4	CUSTOM	CUSTOM Series= ?	Cap= 3.3 uF VDC= 0.0 V Tolerance= 0.0 %	1	NA	CUSTOM 0 mm ²
12.	R1_S1	Vishay-Dale	CRCW040212K4FKED Series= CRCW..e3	Res= 12.4 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
13.	R1_S2	Vishay-Dale	CRCW04022K15FKED Series= CRCW..e3	Res= 2.15 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
14.	R1_S3	Vishay-Dale	CRCW0402649RFKED Series= CRCW..e3	Res= 649.0 Ohm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
15.	R1_S4	Panasonic	ERJ-8ENF1370V Series= ERJ-8E	Res= 137.0 Ohm Power= 250.0 mW Tolerance= 1.0%	1	\$0.01	 1206 11 mm ²
16.	R2_S2	Vishay-Dale	CRCW04023K65FKED Series= CRCW..e3	Res= 3.65 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
17.	R2_S3	Vishay-Dale	CRCW0402845RFKED Series= CRCW..e3	Res= 845.0 Ohm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
18.	R2_S4	Panasonic	ERJ-8ENF2210V Series= ERJ-8E	Res= 221.0 Ohm Power= 250.0 mW Tolerance= 1.0%	1	\$0.01	 1206 11 mm ²

Design Inputs


#	Name	Value	Description
1.	FilterType	Lowpass	
2.	FilterResponse	Chebyshev_05dB	
3.	FilterOrder	7.0	
4.	FilterTopology	Sallen_Key	
5.	NumberOfStages	4.0	
6.	PassbandFrequency	5.0 k	
7.	StopbandAttenuation	-45.0	
8.	StopbandFrequency	8.0 k	
9.	Gain	1.0	
10.	DualSupply	+/-5.0 V	Power supply(s) to active chips
11.	ResistorTolerance	E96	Resistor series - 1% Passive resistor tolerance
12.	CapacitorTolerance	E24	Capacitor series - 5% Passive capacitance tolerance
13.	SeedCapacitance	10.0 n	Seed Capacitance to start design of filter

Design Assistance

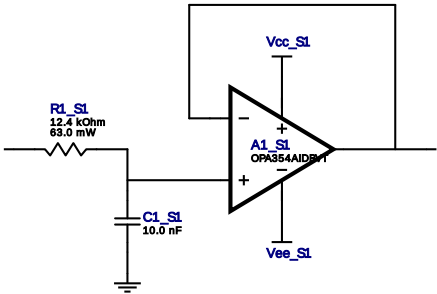1. **OPA354AIDBVT** Product Folder : <http://www.ti.com//product/OPA354> : contains the data sheet and other resources.

Filter Stage :1

Cutoff Frequency 1.281 kHz
Min GBW Req'd 64.042 kHz
Stage Gain 1.0 V/V
Stage Q 500.0 m
Stage Topology Real_Pole




Electrical BOM

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	A1_S1	Texas Instruments, Inc.	OPA354AIDBVT	GbwTyp= 250.0MHz VccMin= 2.5 V VccMax= 5.5 V	1	\$0.80	 DBV0005A 15 mm ²
2.	C1_S1	Kemet	C0603C103J5RACTU Series= X7R	Cap= 10.0 nF VDC= 50.0 V Tolerance= 5.0 %	1	\$0.01	 0603 5 mm ²
3.	R1_S1	Vishay-Dale	CRCW040212K4FKED Series= CRCW..e3	Res= 12.4 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²

Filter Stage :2

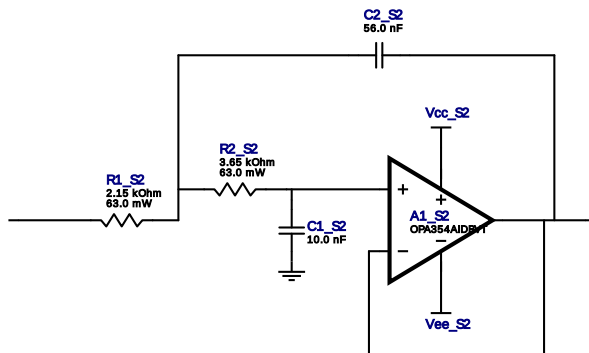Cutoff Frequency 2.519 kHz
 Min GBW Req'd 275.109 kHz
 Stage Gain 1.0 V/V
 Stage Q 1.092
 Stage Topology Sallen_Key




Electrical BOM

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	A1_S2	Texas Instruments, Inc.	OPA354AIDBVT	GbwTyp= 250.0MHz VccMin= 2.5 V VccMax= 5.5 V	1	\$0.80	 DBV0005A 15 mm ²
2.	C1_S2	Kemet	C0603C103J5RACTU Series= X7R	Cap= 10.0 nF VDC= 50.0 V Tolerance= 5.0 %	1	\$0.01	 0603 5 mm ²
3.	C2_S2	AVX	12065A562JAT2A Series= C0G/NP0	Cap= 56.0 nF VDC= 50.0 V Tolerance= 5.0 %	1	\$0.11	 1206 11 mm ²
4.	R1_S2	Vishay-Dale	CRCW04022K15FKED Series= CRCW..e3	Res= 2.15 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
5.	R2_S2	Vishay-Dale	CRCW04023K65FKED Series= CRCW..e3	Res= 3.65 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²

Filter Stage :3

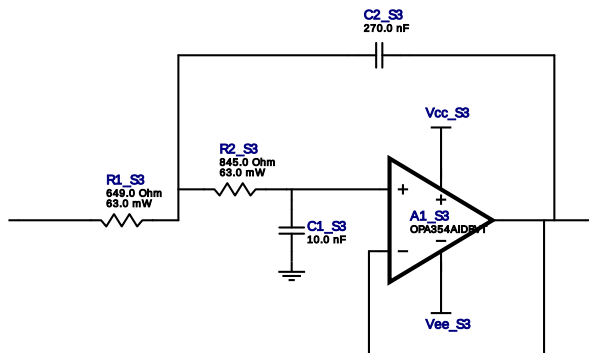Cutoff Frequency 4.114 kHz
 Min GBW Req'd 1.06 MHz
 Stage Gain 1.0 V/V
 Stage Q 2.576
 Stage Topology Sallen_Key




Electrical BOM

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	A1_S3	Texas Instruments, Inc.	OPA354AIDBVT	GbwTyp= 250.0MHz VccMin= 2.5 V VccMax= 5.5 V	1	\$0.80	 DBV0005A 15 mm ²
2.	C1_S3	Kemet	C0603C103J5RACTU Series= X7R	Cap= 10.0 nF VDC= 50.0 V Tolerance= 5.0 %	1	\$0.01	 0603 5 mm ²
3.	C2_S3	Kemet	C2220C274J5GACTU Series= C0G/NP0	Cap= 270.0 nF VDC= 50.0 V Tolerance= 5.0 %	1	\$1.68	 2220 54 mm ²
4.	R1_S3	Vishay-Dale	CRCW0402649RFKED Series= CRCW..e3	Res= 649.0 Ohm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
5.	R2_S3	Vishay-Dale	CRCW0402845RFKED Series= CRCW..e3	Res= 845.0 Ohm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²

Filter Stage :4

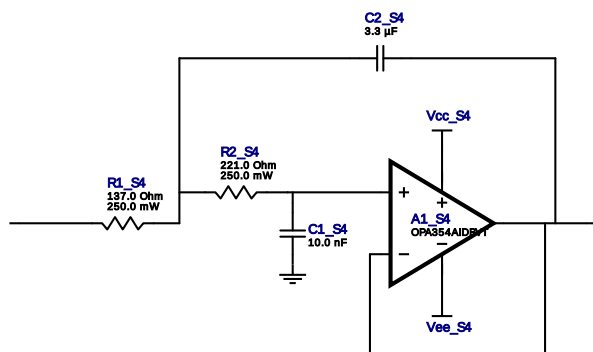Cutoff Frequency 5.04 kHz
 Min GBW Req'd 4.456 MHz
 Stage Gain 1.0 V/V
 Stage Q 8.842
 Stage Topology Sallen_Key



Electrical BOM

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	A1_S4	Texas Instruments, Inc.	OPA354AIDBVT	GbwTyp= 250.0MHz VccMin= 2.5 V VccMax= 5.5 V	1	\$0.80	 DBV0005A 15 mm ²
2.	C1_S4	Kemet	C0603C103J5RACTU Series= X7R	Cap= 10.0 nF VDC= 50.0 V Tolerance= 5.0 %	1	\$0.01	 0603 5 mm ²
3.	C2_S4	CUSTOM	CUSTOM Series= ?	Cap= 3.3 uF VDC= 0.0 V Tolerance= 0.0 %	1	NA	CUSTOM 0 mm ²
4.	R1_S4	Panasonic	ERJ-8ENF1370V Series= ERJ-8E	Res= 137.0 Ohm Power= 250.0 mW Tolerance= 1.0%	1	\$0.01	 1206 11 mm ²
5.	R2_S4	Panasonic	ERJ-8ENF2210V Series= ERJ-8E	Res= 221.0 Ohm Power= 250.0 mW Tolerance= 1.0%	1	\$0.01	 1206 11 mm ²

Texas Instruments' WEBENCH simulation tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Simulations are created using Texas Instruments' published specifications as well as the published specifications of other device manufacturers. While Texas Instruments does update this information periodically, this information may not be current at the time the simulation is built. Texas Instruments does not warrant the accuracy or completeness of the specifications or any information contained therein. Texas Instruments does not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. Texas Instruments does not warrant that the designs are production worthy.

You should completely validate and test your design implementation to confirm the system functionality for your application prior to production.

Use of Texas Instruments' WEBENCH simulation tools is subject to [Texas Instruments' Site Terms and Conditions of Use](#). Prototype boards based on WEBENCH created designs are provided AS IS without warranty of any kind for evaluation and testing purposes and are subject to the terms of the [Evaluation License Agreement](#).