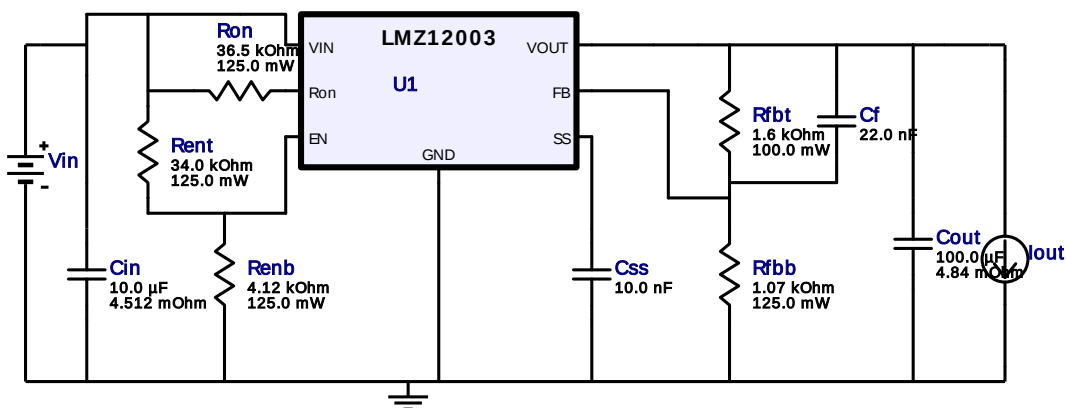


WEBENCH® Design Report

Design : 4749713/8 LMZ12003TZ-ADJ/NOPB
LMZ12003TZ-ADJ/NOPB 11.0V-17.0V to 2.00V @ 3.0A


Vout = 2.0V
Iout = 3.0A




Electrical BOM

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	Cf	Yageo America	CC0805KRX7R9BB223 Series= X7R	Cap= 22.0 nF VDC= 50.0 V IRMS= 0.0 A	1	\$0.01	0805 7 mm ²
2.	Cin	MuRata	GRM31CR61E106KA12L Series= X5R	Cap= 10.0 μ F ESR= 4.512 m Ω VDC= 25.0 V IRMS= 2.447 A	1	\$0.05	1206_190 11 mm ²
3.	Cout	MuRata	GRM31CD80G107ME39L Series= X6T	Cap= 100.0 μ F ESR= 4.84 m Ω VDC= 4.0 V IRMS= 4.3381 A	1	\$0.14	1206_190 11 mm ²
4.	Css	MuRata	GRM216R71H103KA01D Series= X7R	Cap= 10.0 nF VDC= 50.0 V IRMS= 0.0 A	1	\$0.01	0805 7 mm ²
5.	Renb	Panasonic	ERJ-6ENF4121V Series= ERJ-6E	Res= 4.12 k Ω Power= 125.0 mW Tolerance= 1.0%	1	\$0.01	0805 7 mm ²
6.	Rent	Panasonic	ERJ-6ENF3402V Series= ERJ-6E	Res= 34.0 k Ω Power= 125.0 mW Tolerance= 1.0%	1	\$0.01	0805 7 mm ²
7.	Rfbb	Panasonic	ERJ-6ENF1071V Series= ERJ-6E	Res= 1.07 k Ω Power= 125.0 mW Tolerance= 1.0%	1	\$0.01	0805 7 mm ²
8.	Rfbbt	Susumu Co Ltd	RR1220P-162-D Series= RR12	Res= 1.6 k Ω Power= 100.0 mW Tolerance= 0.5%	1	\$0.01	0805 7 mm ²
9.	Ron	Panasonic	ERJ-6ENF3652V Series= ERJ-6E	Res= 36.5 k Ω Power= 125.0 mW Tolerance= 1.0%	1	\$0.01	0805 7 mm ²


#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
10.	U1	Texas Instruments	LMZ12003TZ-ADJ/NOPB	Switcher	1	\$5.92	 TZA07A 199 mm ²

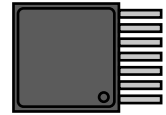TZA07A 199 mm²


Vout p- p

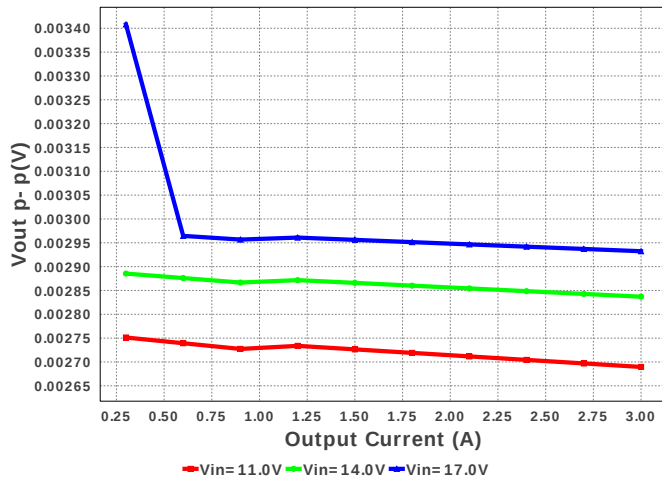


Duty Cycle






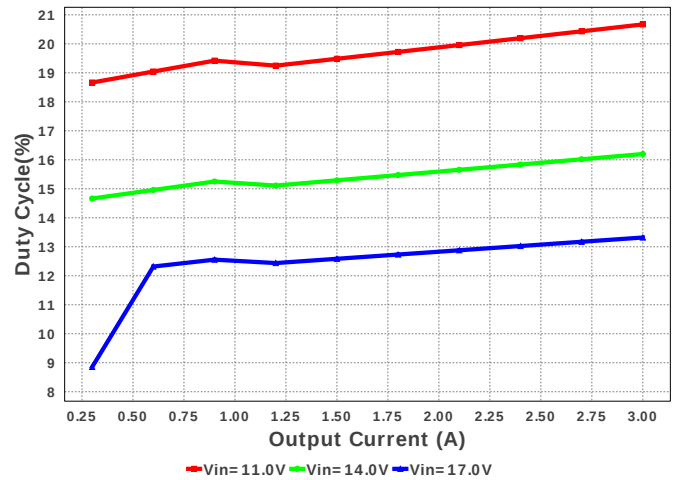








Vout Actual

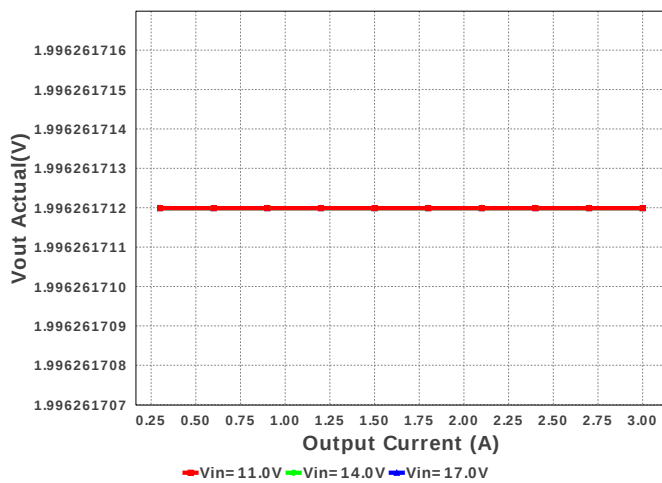

Efficiency

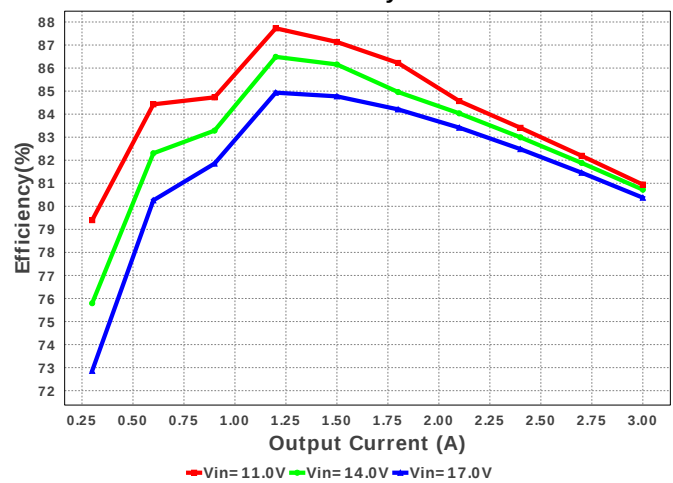

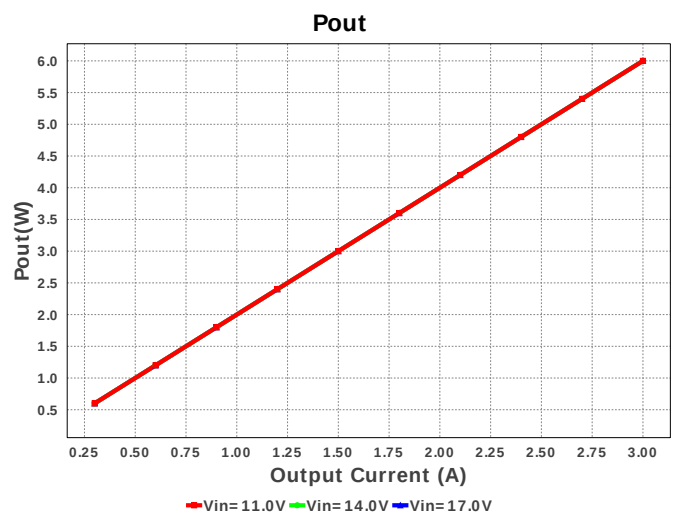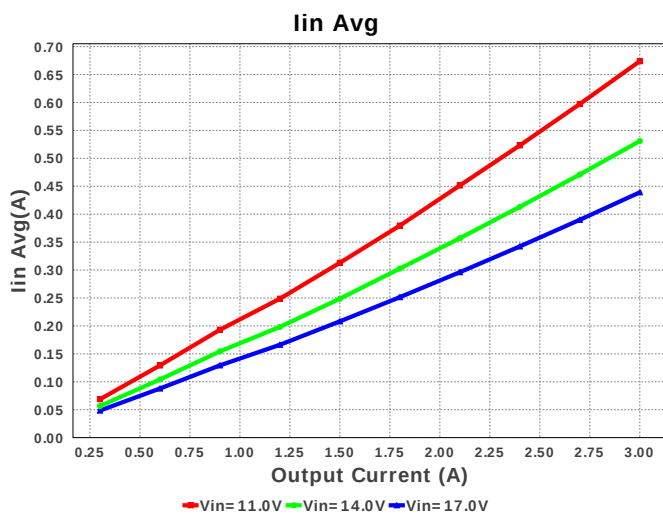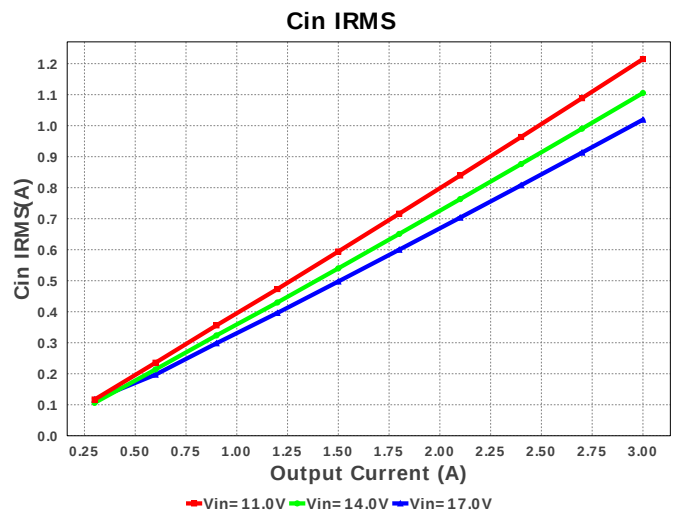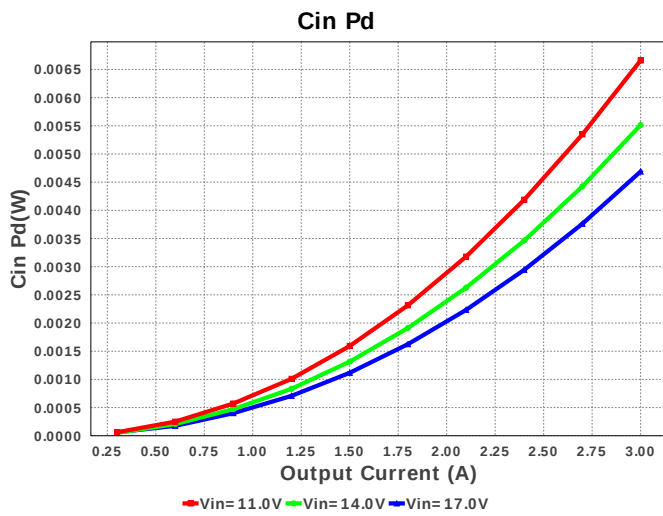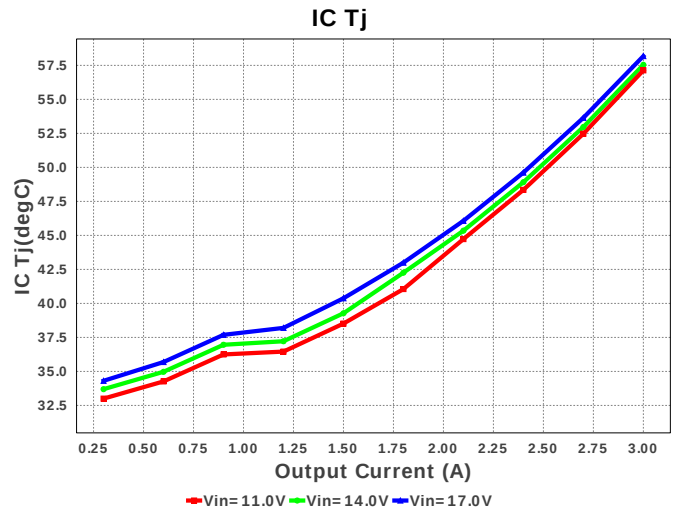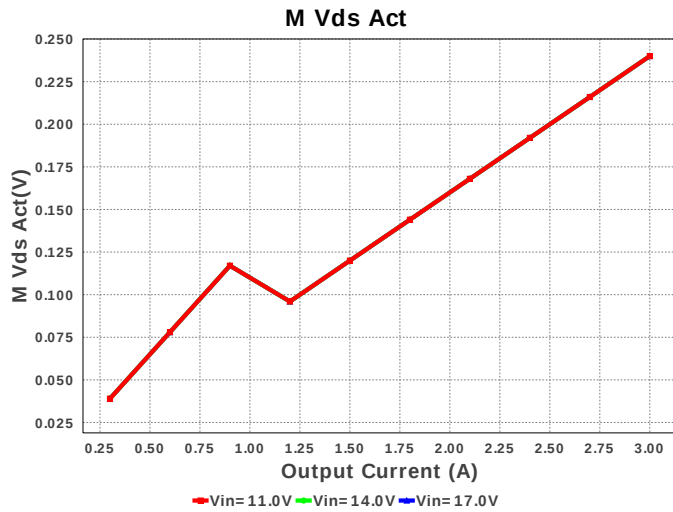

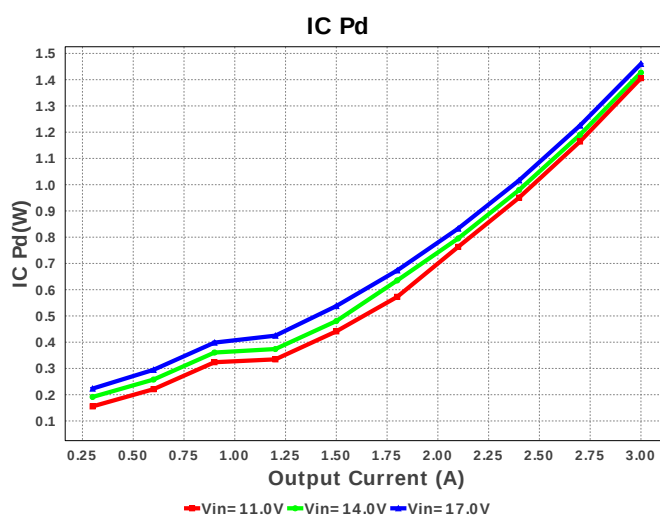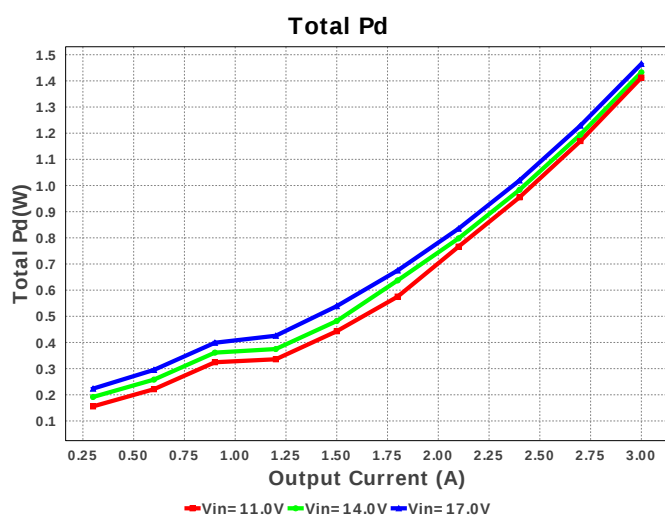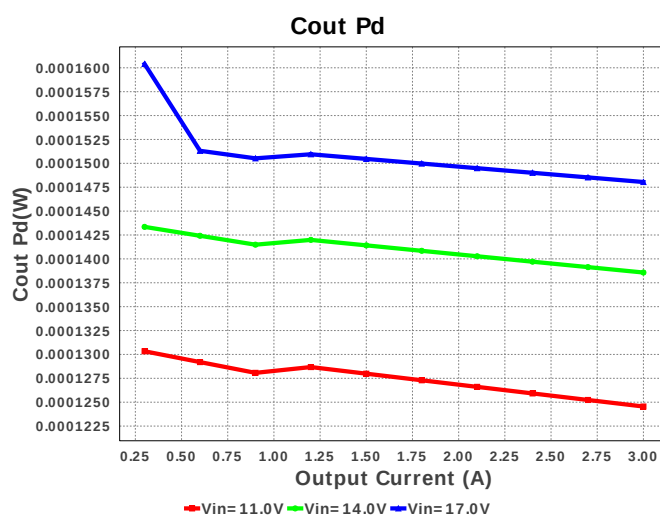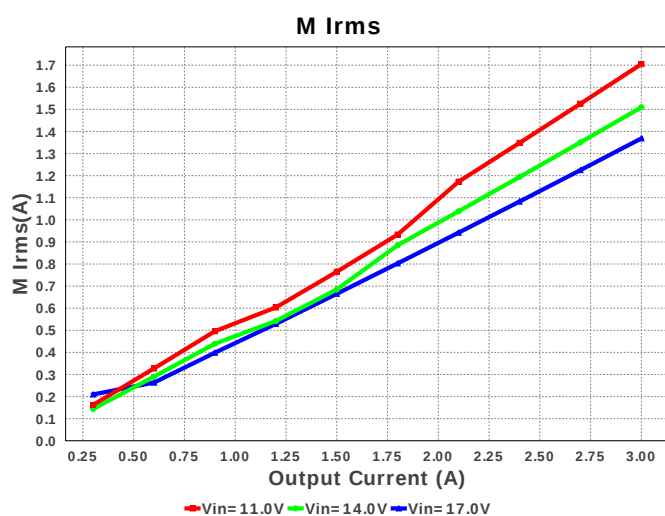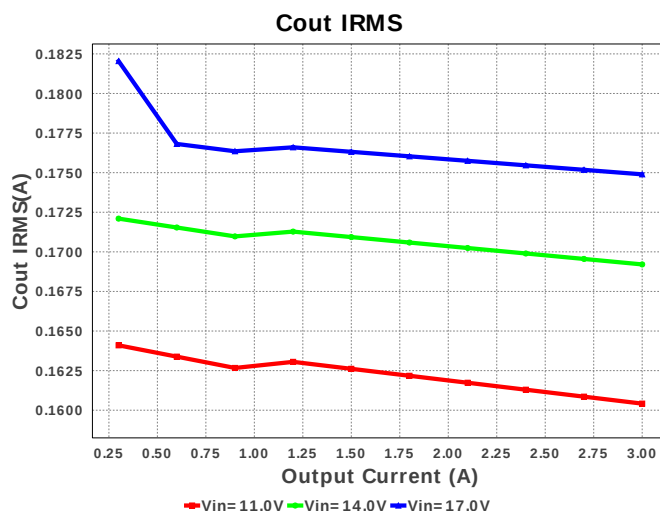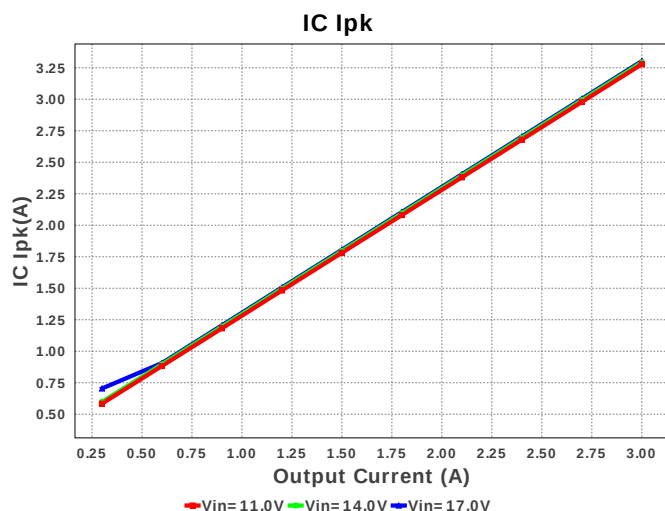

Operating Values

#	Name	Value	Category	Description
1.	Cin IRMS	1.019 A	Current	Input capacitor RMS ripple current
2.	Cout IRMS	174.894 mA	Current	Output capacitor RMS ripple current
3.	IC Ip _k	3.303 A	Current	Peak switch current in IC
4.	I _{in} Avg	433.72 mA	Current	Average input current
5.	M1 Irms	1.369 A	Current	Q ₁ I _{avg}
6.	BOM Count	10	General	Total Design BOM count
7.	FootPrint	268.0 mm ²	General	Total Foot Print Area of BOM components
8.	Frequency	421.496 kHz	General	Switching frequency
9.	IC Tolerance	20.0 mV	General	IC Feedback Tolerance
10.	M V _{ds} Act	240.0 mV	General	Voltage drop across the MosFET
11.	P _{out}	6.0 W	General	Total output power

#	Name	Value	Category	Description
12.	Total BOM	\$6.18	General	Total BOM Cost
13.	Vout Actual	1.996 V	Op_Point	Vout Actual calculated based on selected voltage divider resistors
14.	Vout OP	2.0 V	Op_Point	Operational Output Voltage
15.	Duty Cycle	13.319 %	Op_point	Duty cycle
16.	Efficiency	81.375 %	Op_point	Steady state efficiency
17.	IC Tj	56.41 degC	Op_point	IC junction temperature
18.	ICThetaJA	19.3 degC/W	Op_point	IC junction-to-ambient thermal resistance
19.	IOUT_OP	3.0 A	Op_point	Iout operating point
20.	VIN_OP	17.0 V	Op_point	Vin operating point
21.	Vout p-p	2.932 mV	Op_point	Peak-to-peak output ripple voltage
22.	Cin Pd	4.688 mW	Power	Input capacitor power dissipation
23.	Cout Pd	148.045 μ W	Power	Output capacitor power dissipation
24.	IC Pd	1.368 W	Power	IC power dissipation
25.	Total Pd	1.373 W	Power	Total Power Dissipation
26.	Vout Tolerance	3.431 %		Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable

Design Inputs

#	Name	Value	Description
1.	Iout	3.0	Maximum Output Current
2.	VinMax	17.0	Maximum input voltage
3.	VinMin	11.0	Minimum input voltage
4.	Vout	2.0	Output Voltage
5.	base_pn	LMZ12003	Base Product Number
6.	source	DC	Input Source Type
7.	Ta	30.0	Ambient temperature

Design Assistance

1. **LMZ12003** Product Folder : <http://www.ti.com/product/LMZ12003> : contains the data sheet and other resources.

Texas Instruments' WEBENCH simulation tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Simulations are created using Texas Instruments' published specifications as well as the published specifications of other device manufacturers. While Texas Instruments does update this information periodically, this information may not be current at the time the simulation is built. Texas Instruments does not warrant the accuracy or completeness of the specifications or any information contained therein. Texas Instruments does not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. Texas Instruments does not warrant that the designs are production worthy.

You should completely validate and test your design implementation to confirm the system functionality for your application prior to production.

Use of Texas Instruments' WEBENCH simulation tools is subject to [Texas Instruments' Site Terms and Conditions of Use](#). Prototype boards based on WEBENCH created designs are provided AS IS without warranty of any kind for evaluation and testing purposes and are subject to the terms of the [Evaluation License Agreement](#).