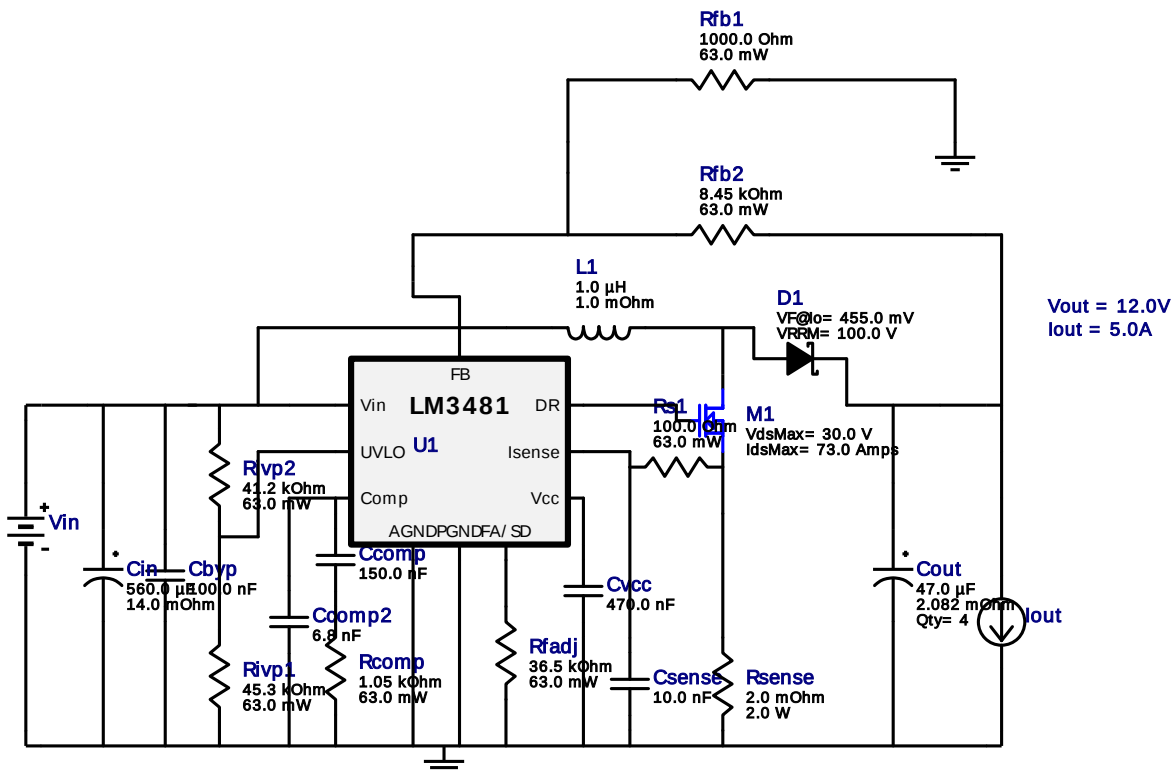



WEBENCH[®] Design Report







Design : 4761085/7 LM3481MM/NOPB
LM3481MM/NOPB 3.0V-9.0V to 12.00V @ 5.0A















Electrical BOM







#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	Cbyp	MuRata	GRM155R61A104KA01D Series= X5R	Cap= 100.0 nF VDC= 10.0 V IRMS= 0.0 A	1	\$0.01	0402 3 mm ²
2.	Ccomp	MuRata	GRM155R60J154KE01D Series= X5R	Cap= 150.0 nF VDC= 6.3 V IRMS= 0.0 A	1	\$0.01	0402 3 mm ²
3.	Ccomp2	Yageo America	CC0805KRX7R9BB682 Series= X7R	Cap= 6.8 nF VDC= 50.0 V IRMS= 0.0 A	1	\$0.01	0805 7 mm ²
4.	Cin	Panasonic	16SVPF560M Series= ?	Cap= 560.0 uF ESR= 14.0 mOhm VDC= 16.0 V IRMS= 4.95 A	1	\$0.61	 CAPSMT_62_E12 106 mm ²
5.	Cout	TDK	C3216X5R1E476M160AC Series= X5R	Cap= 47.0 uF ESR= 2.082 mOhm VDC= 25.0 V IRMS= 5.0279 A	4	\$0.35	 1206 11 mm ²
6.	Csense	MuRata	GRM216R71H103KA01D Series= X7R	Cap= 10.0 nF VDC= 50.0 V IRMS= 0.0 A	1	\$0.01	0805 7 mm ²
7.	Cvcc	MuRata	GRM155C80J474KE19D Series= X6S	Cap= 470.0 nF VDC= 6.3 V IRMS= 0.0 A	1	\$0.01	0402 3 mm ²






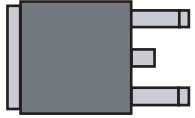
#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
8.	D1	STMicroelectronics	STPS20M100SG-TR	VF@Io= 455.0 mV VRRM= 100.0 V	1	\$1.33	 DDPAK 210 mm ²
9.	L1	Coilcraft	XAL1010-102MEB	L= 1.0 µH DCR= 1.0 mOhm	1	\$1.71	 XAL1010 160 mm ²
10.	M1	Texas Instruments	CSD17307Q5A	VdsMax= 30.0 V IdsMax= 73.0 Amps	1	\$0.25	 TRANS_NexFET_Q5A 55 mm ²
11.	Rcomp	Vishay-Dale	CRCW04021K05FKED Series= CRCW..e3	Res= 1.05 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
12.	Rfadj	Vishay-Dale	CRCW040236K5FKED Series= CRCW..e3	Res= 36.5 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
13.	Rfb1	Vishay-Dale	CRCW04021K00FKED Series= CRCW..e3	Res= 1000.0 Ohm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
14.	Rfb2	Vishay-Dale	CRCW04028K45FKED Series= CRCW..e3	Res= 8.45 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
15.	Rivp1	Vishay-Dale	CRCW040245K3FKED Series= CRCW..e3	Res= 45.3 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
16.	Rivp2	Vishay-Dale	CRCW040241K2FKED Series= CRCW..e3	Res= 41.2 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
17.	Rs1	Vishay-Dale	CRCW0402100RFKED Series= CRCW..e3	Res= 100.0 Ohm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
18.	Rsense	Ohmite	FCSL64R002GER Series= FCSL	Res= 2.0 mOhm Power= 2.0 W Tolerance= 2.0%	1	\$0.37	2512_WIDE 43 mm ²
19.	U1	Texas Instruments	LM3481MM/NOPB	Switcher	1	\$0.80	 MUB10A 24 mm ²

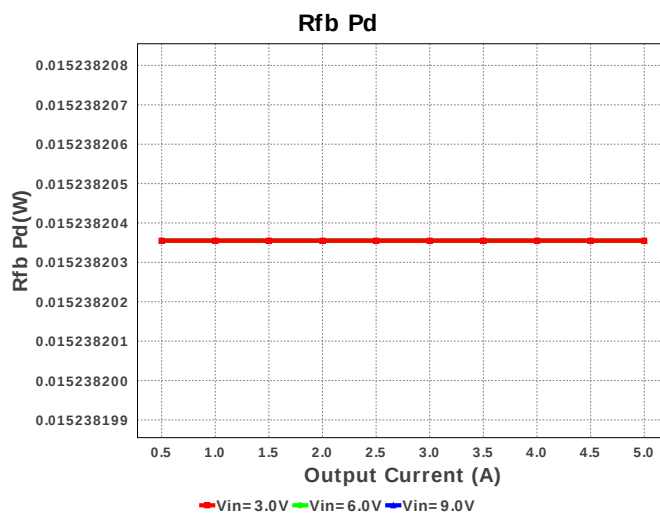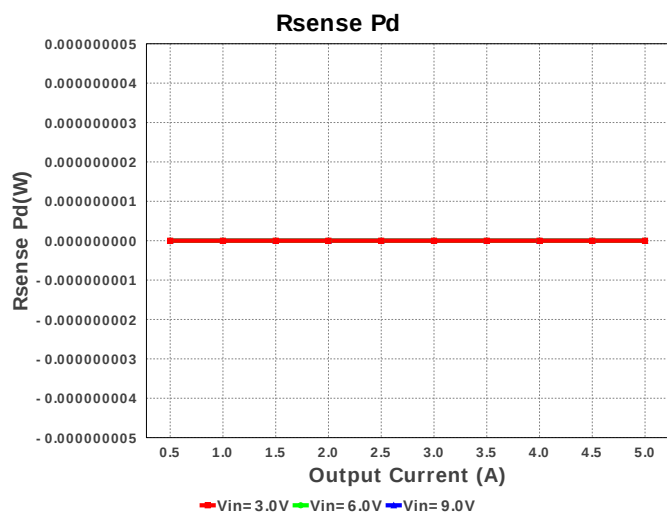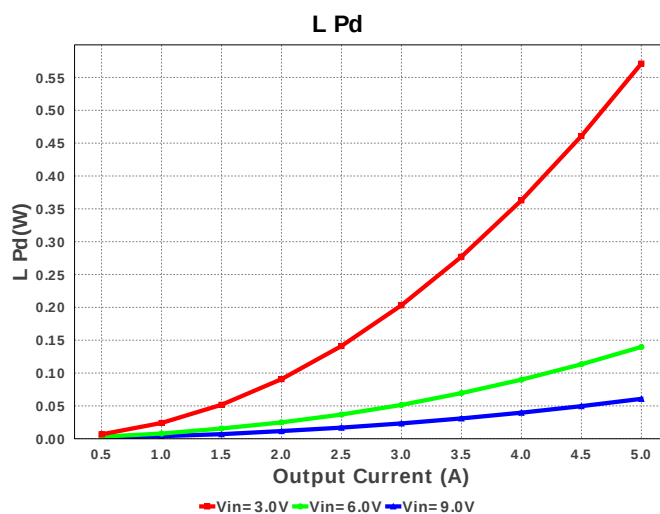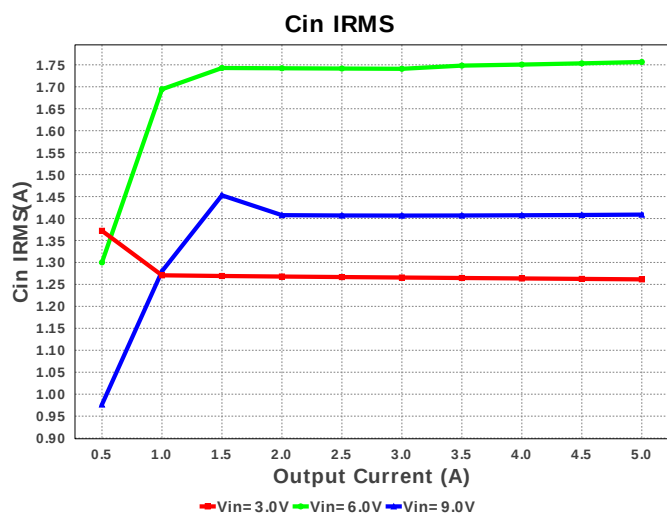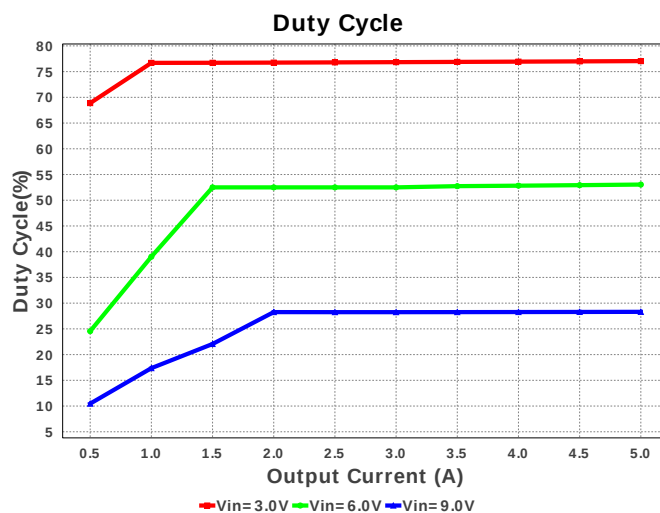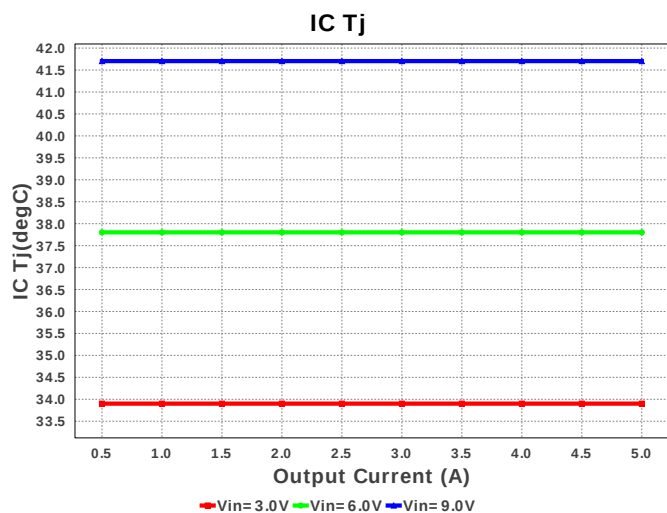

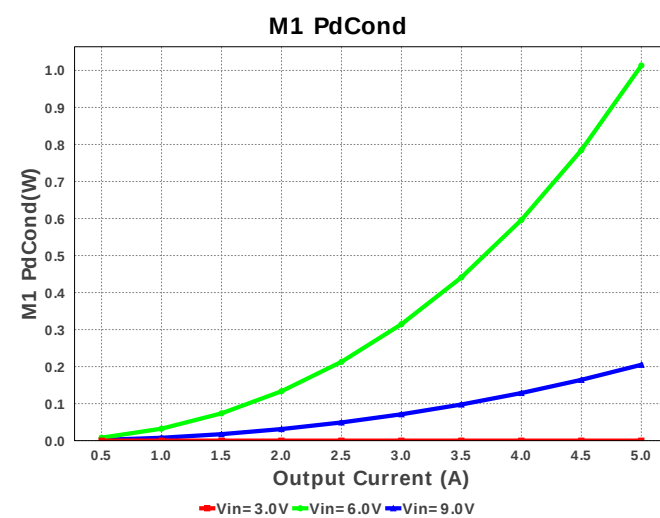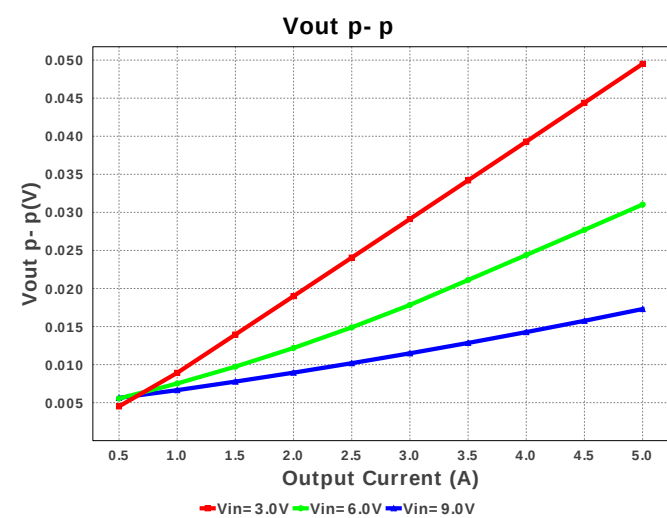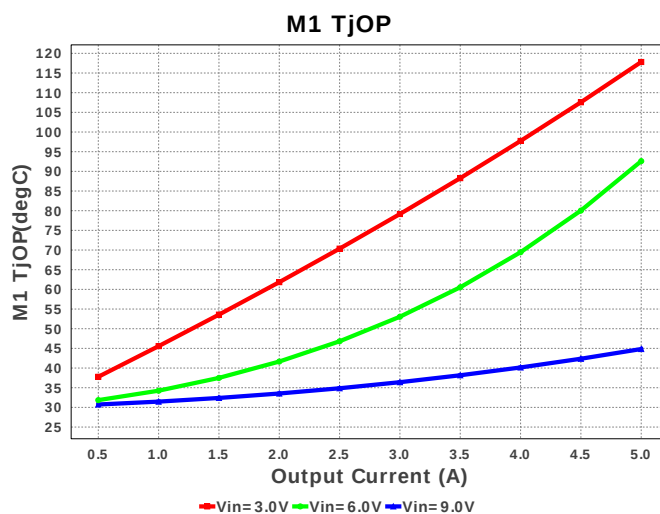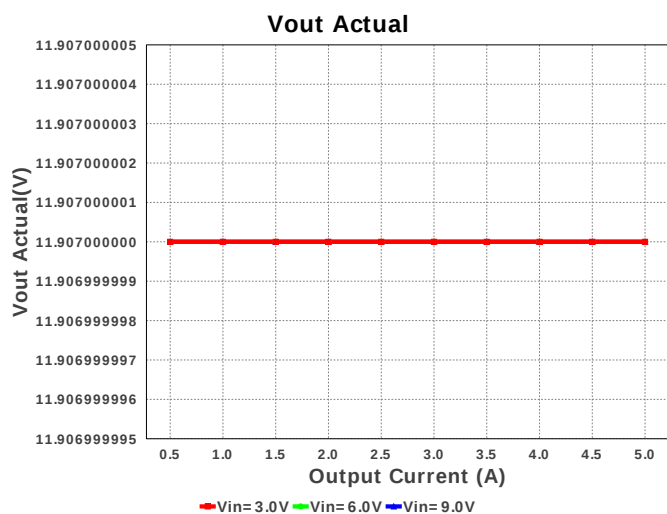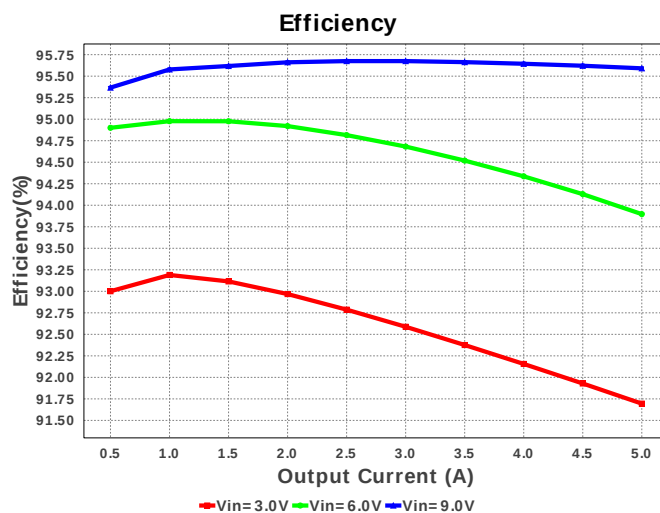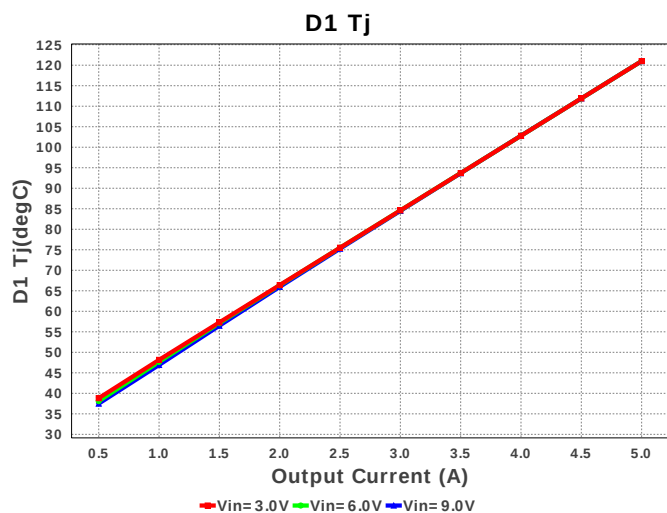

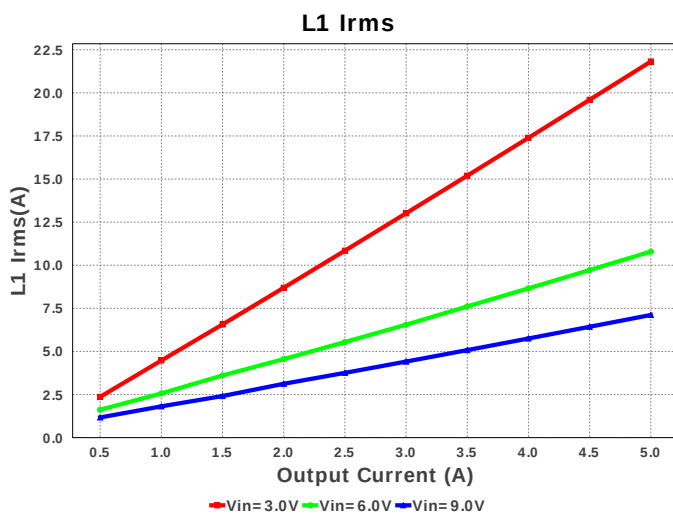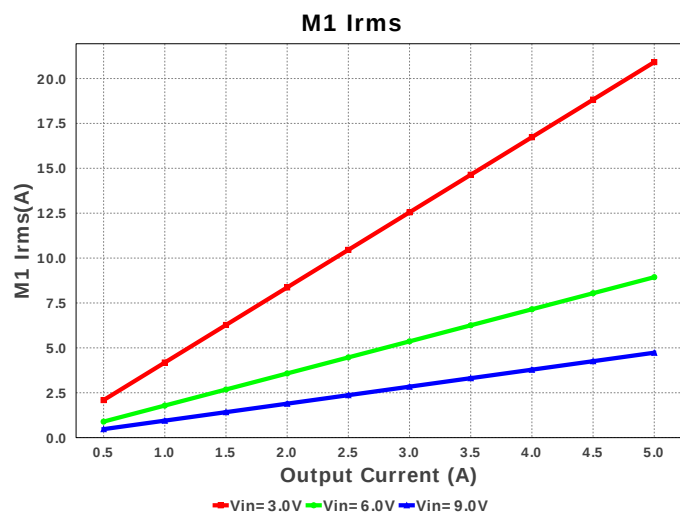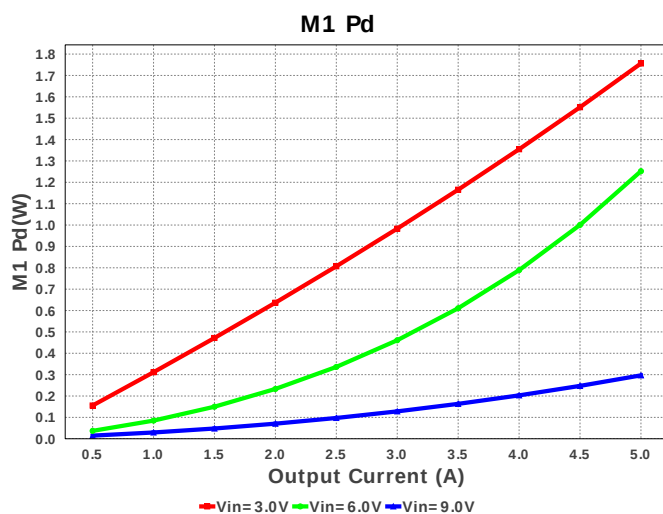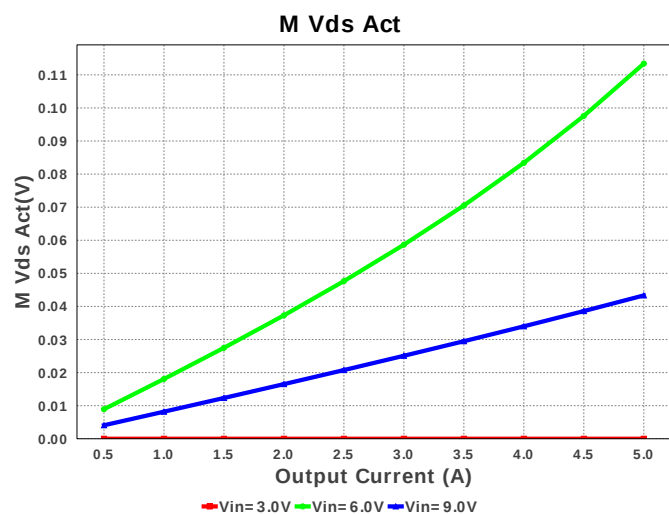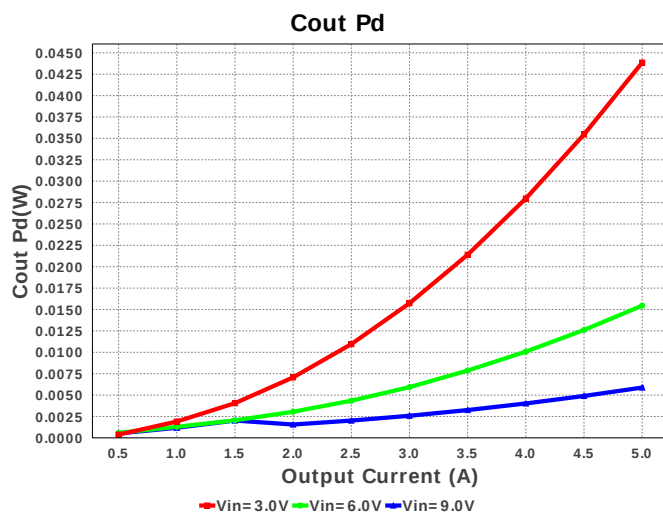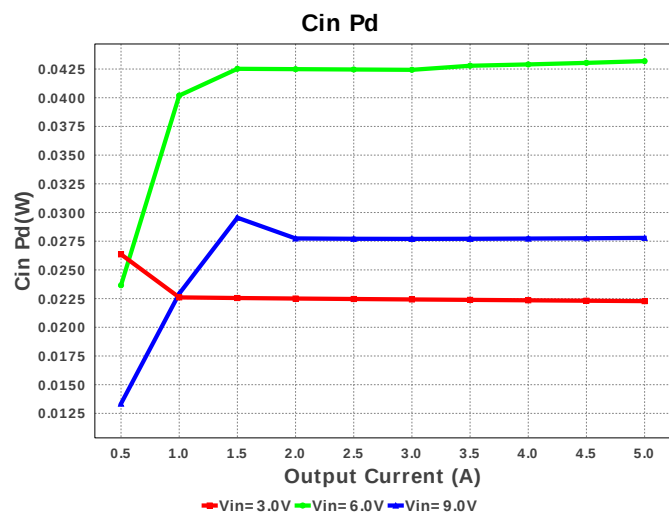

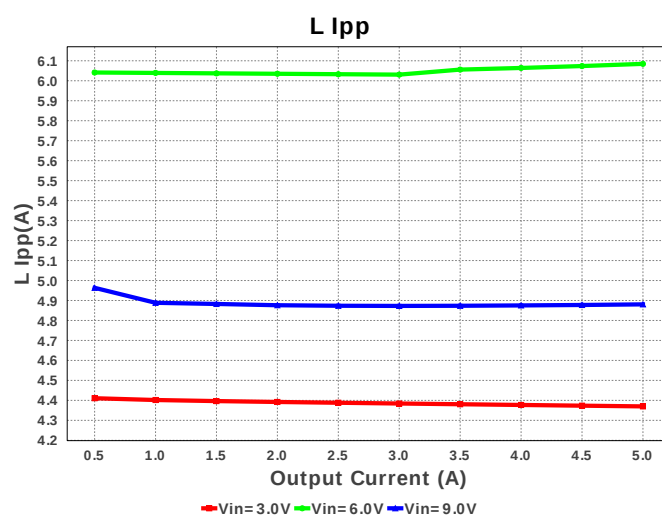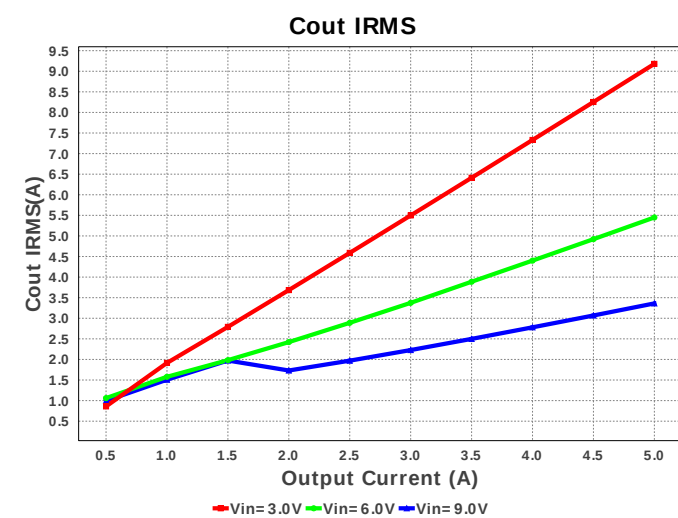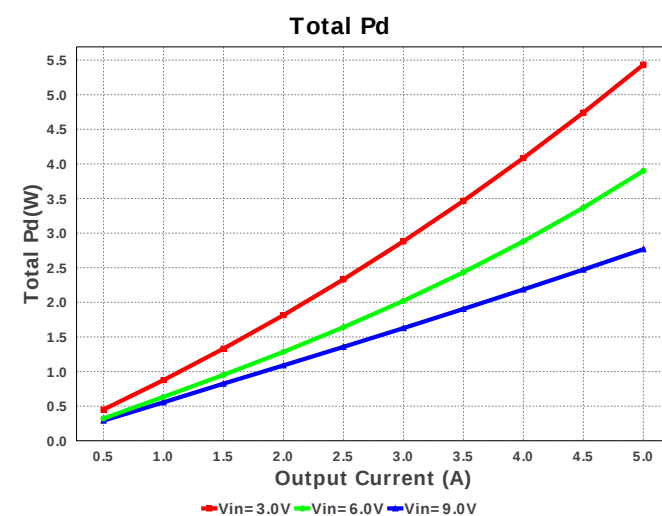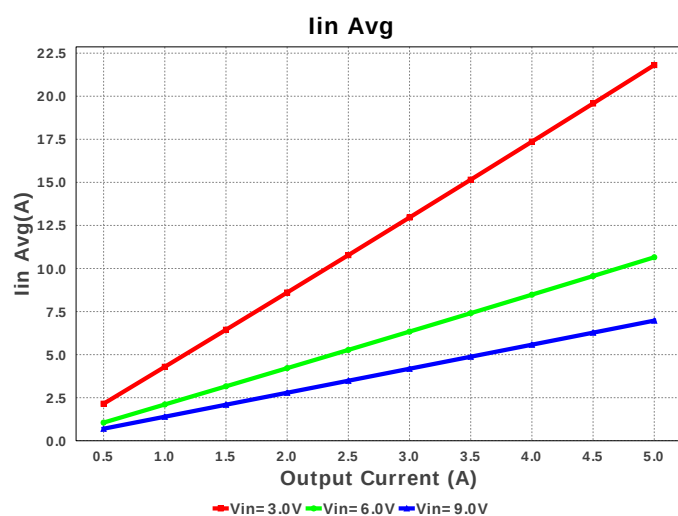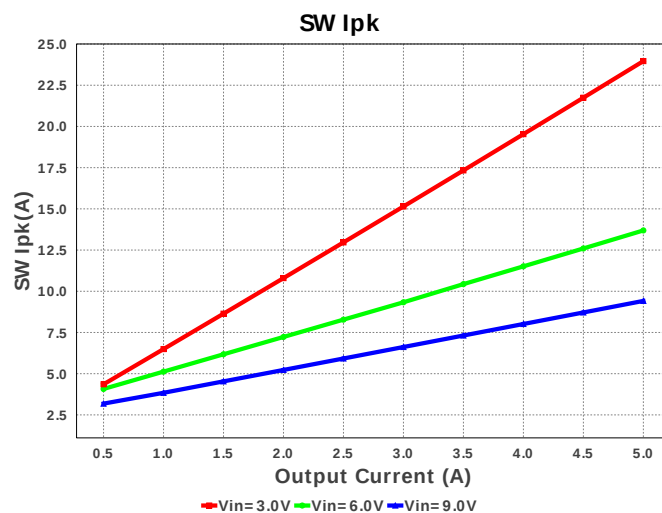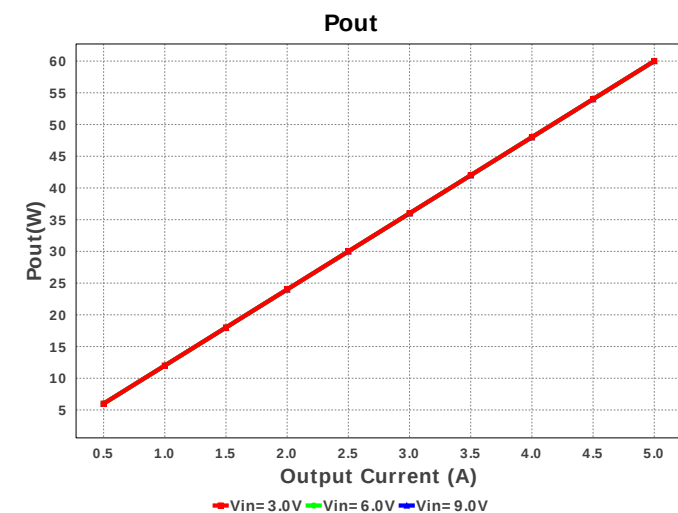

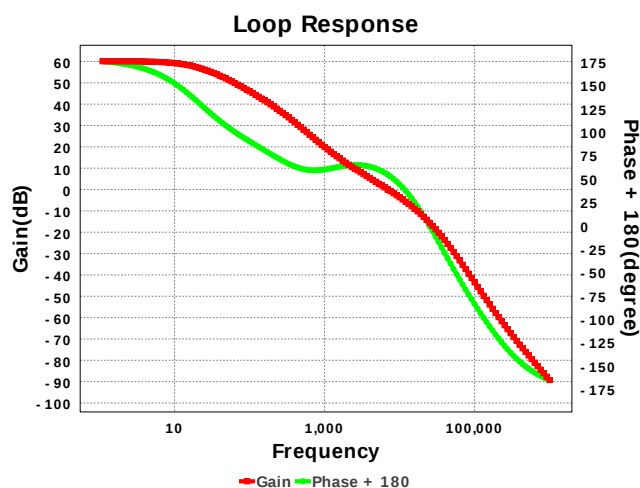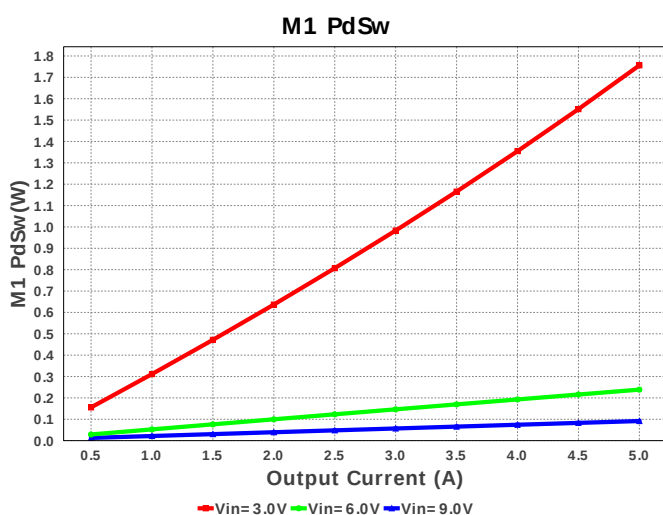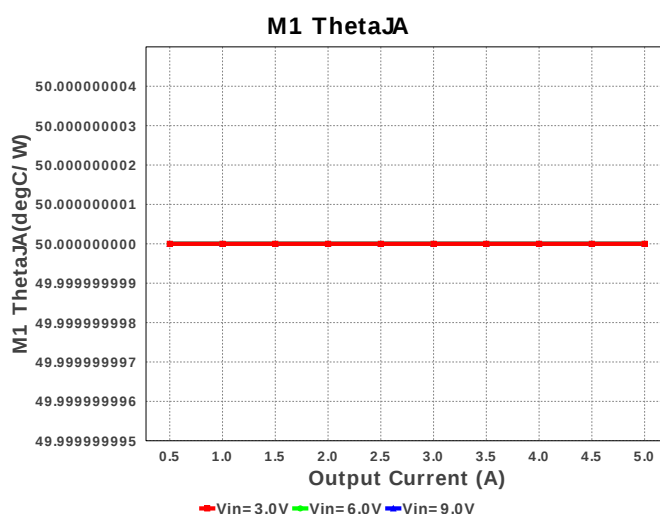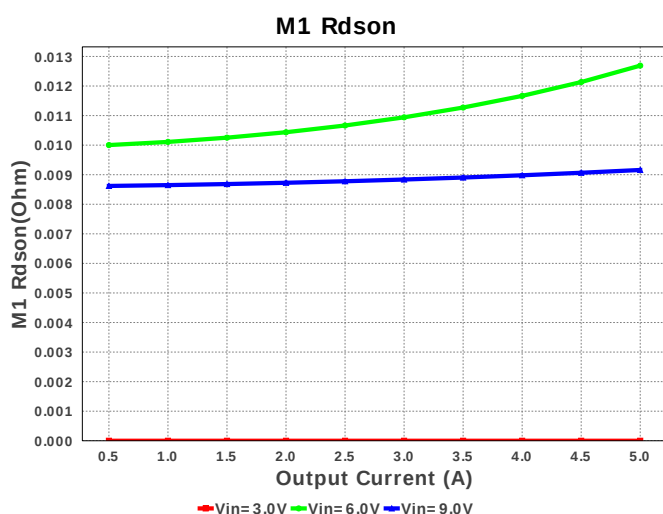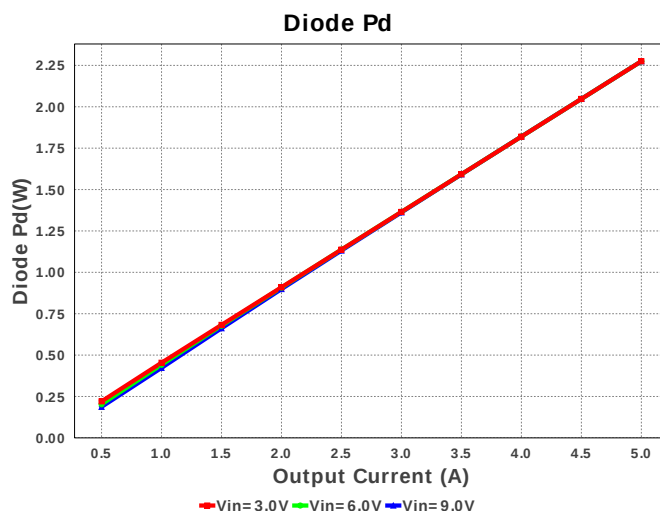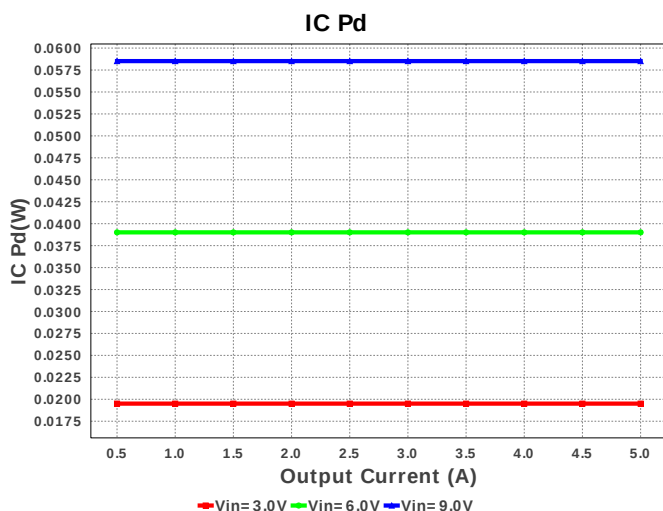

Operating Values

#	Name	Value	Category	Description
1.	Cin IRMS	1.262 A	Current	Input capacitor RMS ripple current
2.	Cout IRMS	9.181 A	Current	Output capacitor RMS ripple current
3.	Iin Avg	21.815 A	Current	Average input current
4.	L Ipp	4.37 A	Current	Peak-to-peak inductor ripple current
5.	L1 Irms	21.82 A	Current	Inductor ripple current
6.	M1 Irms	20.915 A	Current	M1 MOSFET Irms
7.	SW Ipk	23.968 A	Current	Peak switch current
8.	BOM Count	22	General	Total Design BOM count
9.	FootPrint	685.0 mm ²	General	Total Foot Print Area of BOM components
10.	Frequency	521.23 kHz	General	Switching frequency
11.	IC Tolerance	19.0 mV	General	IC Feedback Tolerance

#	Name	Value	Category	Description
12.	M Vds Act	0.0 V	General	M Vds
13.	M1 Rdson	0.0 Ohm	General	Drain-Source On-resistance
14.	M1 ThetaJA	50.0 degC/W	General	MOSFET junction-to-ambient thermal resistance
15.	Pout	60.0 W	General	Total output power
16.	Total BOM	\$6.59	General	Total BOM Cost
17.	D1 Tj	121.0 degC	Op_Point	D1 junction temperature
18.	Low Freq Gain	50.235 dB	Op_Point	Gain at 10Hz
19.	Vout Actual	11.907 V	Op_Point	Vout Actual calculated based on selected voltage divider resistors
20.	Vout OP	12.0 V	Op_Point	Operational Output Voltage
21.	Cross Freq	2.853 kHz	Op_point	Bode plot crossover frequency
22.	Duty Cycle	77.047 %	Op_point	Duty cycle
23.	Efficiency	91.68 %	Op_point	Steady state efficiency
24.	Gain Marg	-15.089 dB	Op_point	Bode Plot Gain Margin
25.	IC Tj	33.91 degC	Op_point	IC junction temperature
26.	ICThetaJA	200.0 degC/W	Op_point	IC junction-to-ambient thermal resistance
27.	IOUT_OP	5.0 A	Op_point	Iout operating point
28.	M1 TJOP	118.331 degC	Op_point	M1 MOSFET junction temperature
29.	Phase Marg	60.643 deg	Op_point	Bode Plot Phase Margin
30.	VIN_OP	3.0 V	Op_point	Vin operating point
31.	Vout p-p	55.366 mV	Op_point	Peak-to-peak output ripple voltage
32.	Cin Pd	22.281 mW	Power	Input capacitor power dissipation
33.	Cout Pd	43.869 mW	Power	Output capacitor power dissipation
34.	Diode Pd	2.275 W	Power	Diode power dissipation
35.	IC Pd	19.551 mW	Power	IC power dissipation
36.	L Pd	571.324 mW	Power	Inductor power dissipation
37.	M1 Pd	1.767 W	Power	M1 MOSFET total power dissipation
38.	M1 PdCond	0.0 W	Power	M1 MOSFET conduction losses
39.	M1 PdSw	1.767 W	Power	M1 MOSFET switching losses
40.	Rfb Pd	15.238 mW	Power	Rfb Power Dissipation
41.	Rsense Pd	861.817 mW	Power	LED Current Rsns Power Dissipation
42.	Total Pd	5.445 W	Power	Total Power Dissipation
43.	Vout Tolerance	3.342 %		Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable

Design Inputs

#	Name	Value	Description
1.	Iout	5.0	Maximum Output Current
2.	VinMax	9.0	Maximum input voltage
3.	VinMin	3.0	Minimum input voltage
4.	Vout	12.0	Output Voltage
5.	base_pn	LM3481	Base Product Number
6.	source	DC	Input Source Type
7.	Ta	30.0	Ambient temperature

Design Assistance

1. **LM3481** Product Folder : <http://www.ti.com/product/LM3481> : contains the data sheet and other resources.

Texas Instruments' WEBENCH simulation tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Simulations are created using Texas Instruments' published specifications as well as the published specifications of other device manufacturers. While Texas Instruments does update this information periodically, this information may not be current at the time the simulation is built. Texas Instruments does not warrant the accuracy or completeness of the specifications or any information contained therein. Texas Instruments does not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. Texas Instruments does not warrant that the designs are production worthy.

You should completely validate and test your design implementation to confirm the system functionality for your application prior to production.

Use of Texas Instruments' WEBENCH simulation tools is subject to [Texas Instruments' Site Terms and Conditions of Use](#). Prototype boards based on WEBENCH created designs are provided AS IS without warranty of any kind for evaluation and testing purposes and are subject to the terms of the [Evaluation License Agreement](#).